


★ Multivibrators Using logic gates.

3


Applications

- ① Astable Multivibrators → Square Wave generator
(Free running mv)
- ② Monostable multivibrators → { (a) Pulse generator
(b) Pulse stretcher.
(One shot mv)
- ③ Bistable multivibrators → 1-bit memory.

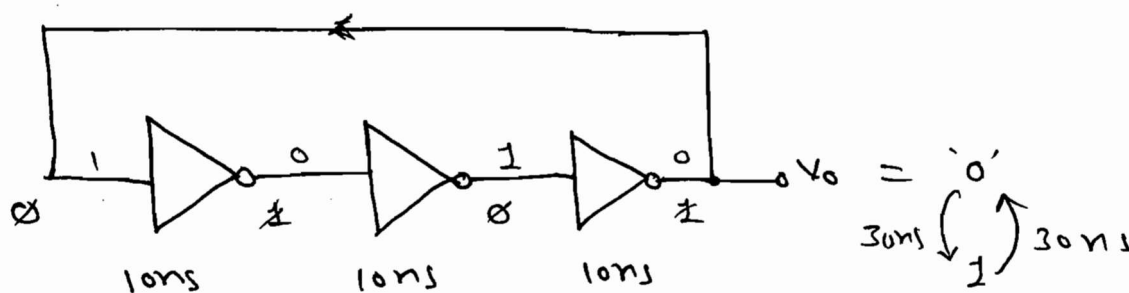* Astable Multivibrators Using logic gate.



'0', '1' = Unstable States.

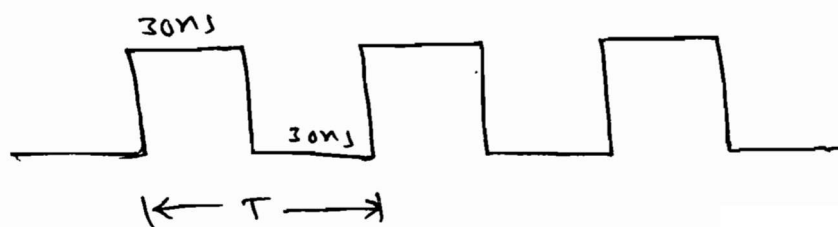


$$\therefore T = 60 \text{ ns}$$

→ Time period of Square wave

$$T = 2 \times (\text{sum of Propagation Delays of all Inverters})$$


* Bistable Multivibrators.

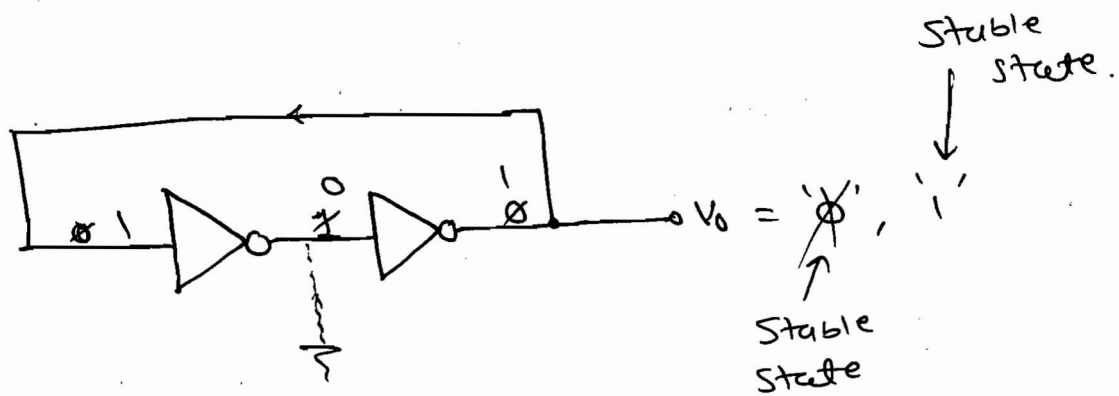

NOTE:

- If odd no. of Inverters then ~~As~~ Astable mv.
- If even no. of Inverters then Bistable mv.

* Monostable Multivibrator

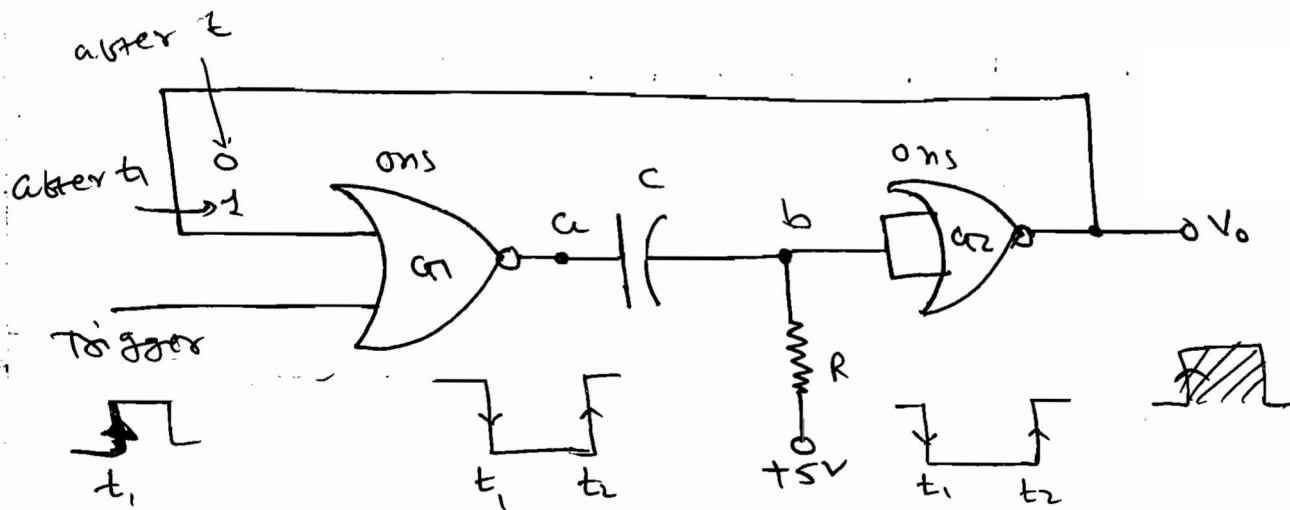


- After T_1 , the feedback came at gate (1) input is equal to '1' which means the $V_a = 0$. Capacitor charges to $+5V$ with time constant RC .

- After capacitor charges to $+5V$ volts.


hence the capacitor discharges.

* Pulse Stretching.

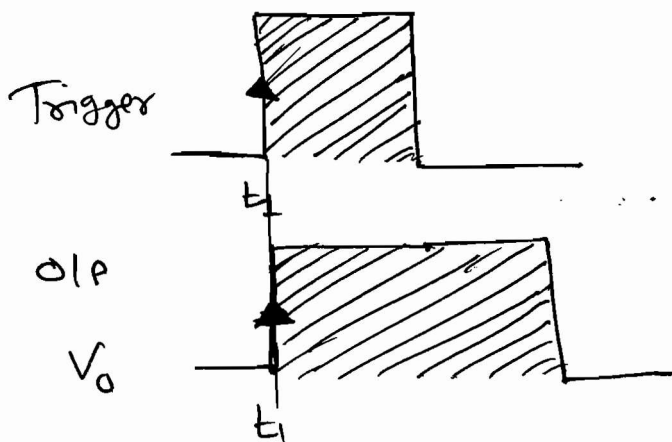


Ex- Determine the following multivibrators:

a)

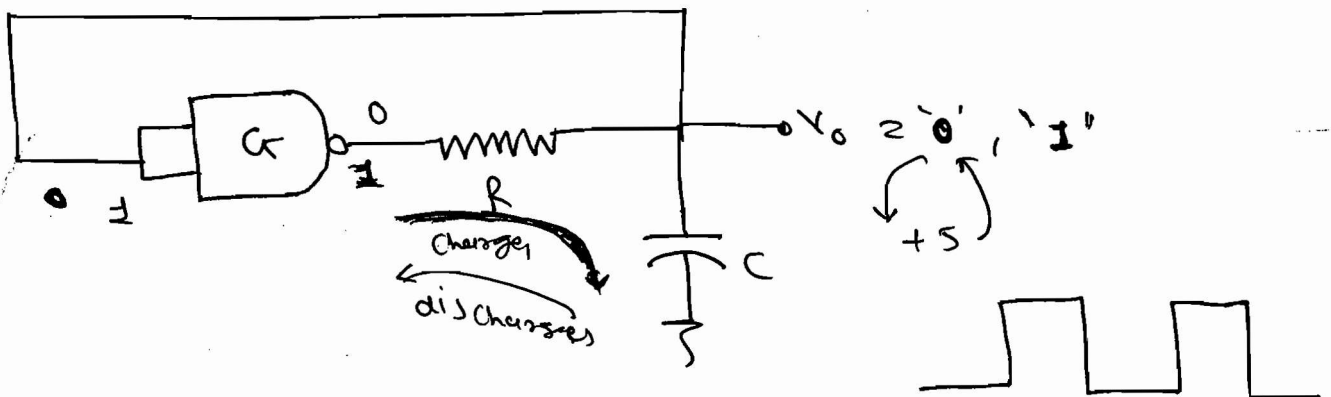


→ so, it is Astable mv.


b)

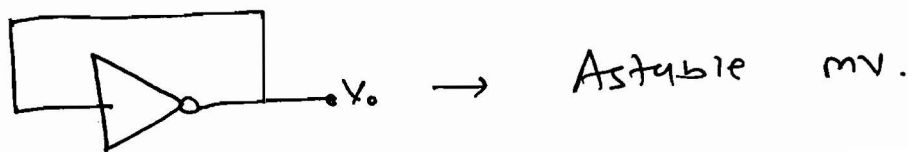


c)

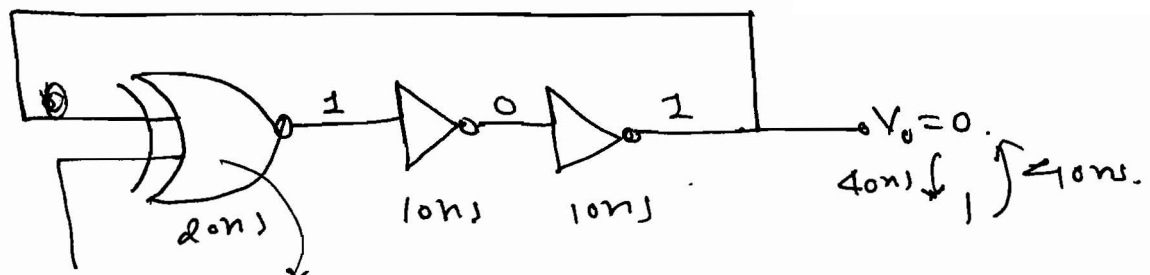

④

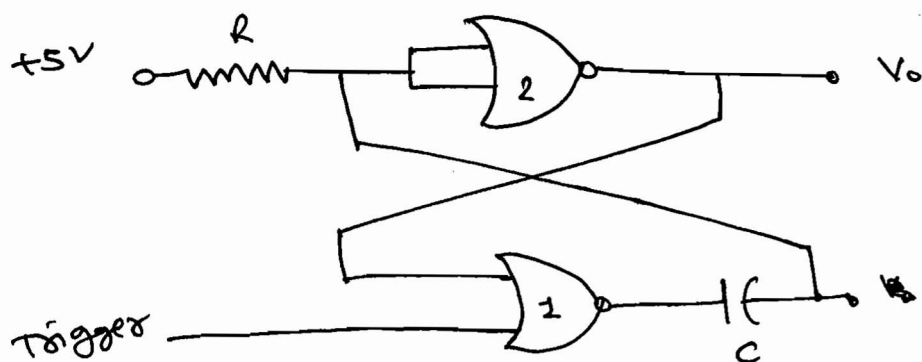


|||

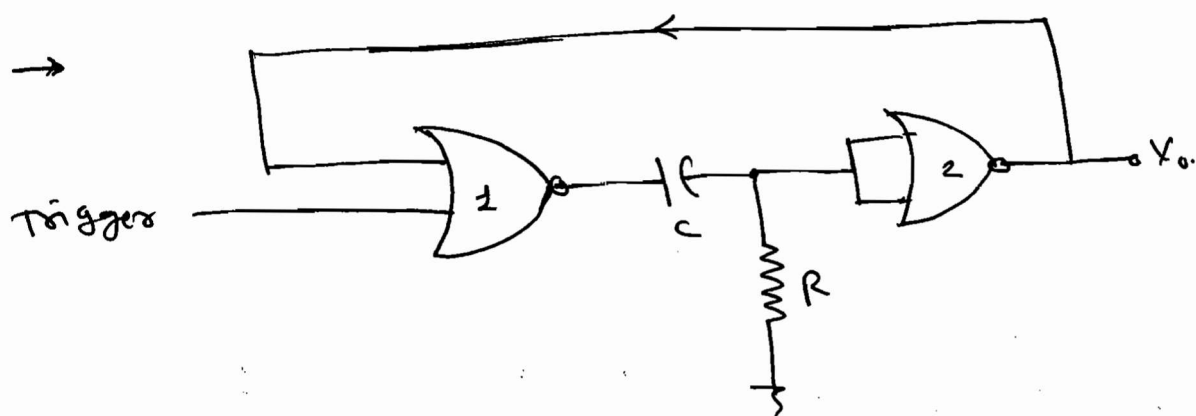

→ Now it is look like monostable mv.
 So, given ckt is monostable mv.

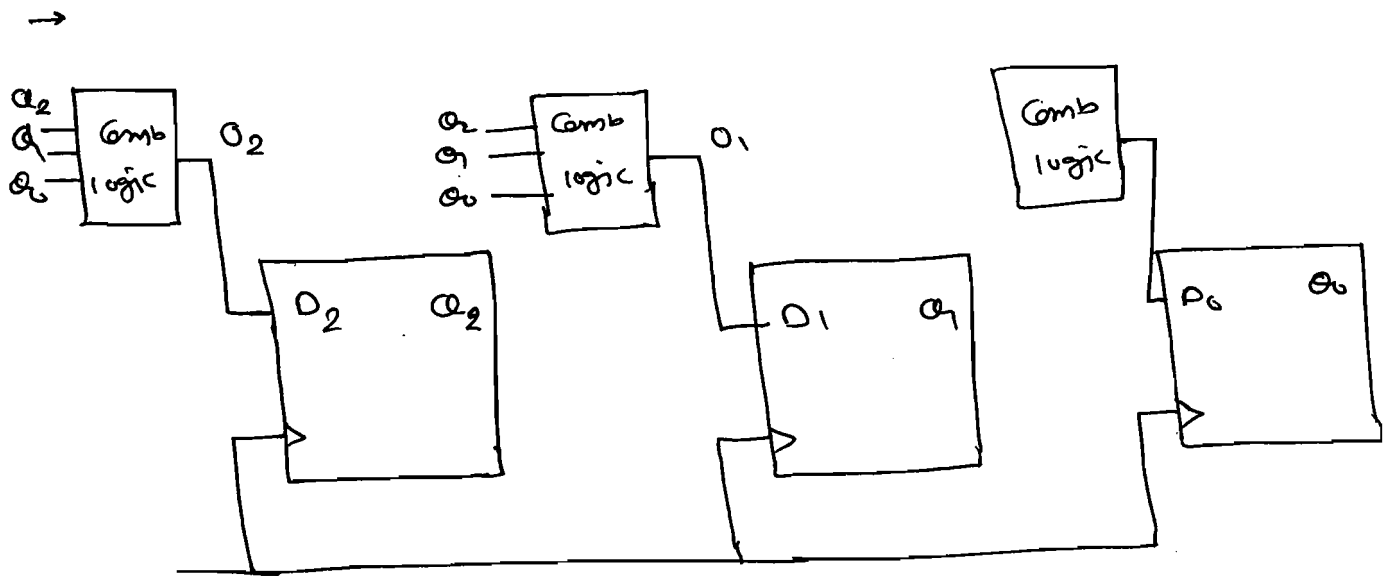Ex- In the following circuits determine the values of $Q_2, Q_1, Q_0 = ?$ if it is counting the following sequence $\rightarrow 101, 010, 110$



→ This is nothing but design a Sync Counter using D-FF which counts through the states 5, 2, 6, 5, ...


→ at time of design use excitation table
→ at time of analysis use truth table.

→

	P.S.			N.S			FF Inputs		
	Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	D_2	D_1	D_0
⑤	1	0	1	0	1	0	0	1	0
②	0	1	0	1	1	0	1	1	0
⑥	1	1	0	1	0	1	1	0	1

→ $D_2 = Q_1$

$D_2 = \sum m(2, 5) + d(0, 3, 1, 4, 7)$

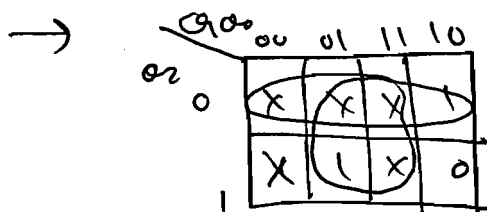

$\therefore D_1 = \bar{Q}_2 + Q_0$

$$D_1 = \sum m(6) + d(0, 1, 3, 4, 7)$$

	$\sigma_0 \sigma_1$	σ_1	σ_2	σ_3
σ_0	X	X	X	0
σ_1	X	0	X	1

$$D_1 = \bar{\sigma}_0 \sigma_1 (7) \sigma_2 \sigma_3$$