

NETWORKS TEST 3


Number of Questions: 25

Time: 60 min.

Directions for questions 1 to 25: Select the correct alternative from the given choices.


1. The response of a network is $i(t) = 2t.e^{-5t}$ A for $t \geq 0$, the value of 't' at which the $i(t)$ will become maximum, is
 (A) 0.2 sec (B) 0.4 sec
 (C) 0.25 sec (D) 0.8 sec

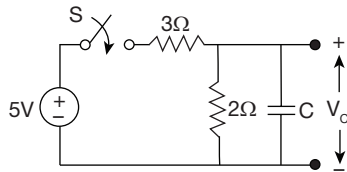2. In the network shown below, it is given that $V_c = 2.5V$ and $\frac{dV_c}{dt} = -8V/s$ at a time 't', where t is the time constant after the switch 'S' is closed. What is the value of 'C'?



- (A) 3.25 mF (B) 1.25 mF
 (C) 1 μF (D) 0.052 F

3.

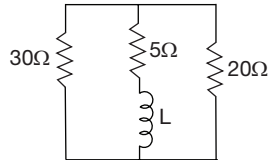

If the time constant of circuit is 1.5 msec. Then the value of L is _____


- (A) 18 mH (B) 25.5 mH
 (C) 5.3 mH (D) 30 mH
4. In an A.C series RLC circuit, the voltage across R and L is 20V, voltage across L and C is 9V and voltage across RLC is 15V. Then the ratio of $\frac{V_L}{V_C}$ is _____
 [Assume $V_L > V_C$].
 (A) 0.64 (B) 2.52
 (C) 3.43 (D) 2.28

5. A network has a transfer function

$$Z(S) = \frac{3s+2}{0.5s+3}$$


If the current $i(t)$ is a unity step function, the steady – state value of $V(t)$ is given by

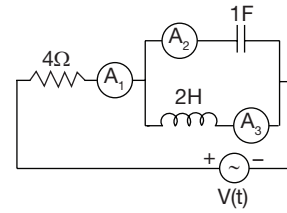- (A) 0 (B) 1.5
 (C) 2/3 (D) ∞
6. Consider the circuit shown in figure
 If A_1 , A_2 and A_3 are ideal ammeters. If A_1 and A_3 reads 8A and 3A respectively, then A_2 should read _____



- (A) 5A (B) 11A
 (C) 8.66A (D) None

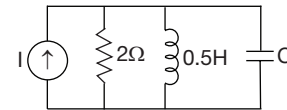7. Consider the circuit shown in below
 If the roots of the response is complex conjugate then the value of C is _____




- (A) 0.25 F (B) 15 mF
 (C) 30 mF (D) 32 mF

8. The coil of a certain relay is operated by 15V battery. If the coil has a resistance of 200 Ω and an inductance of 25 mH and the current needed to pull in is 40 mA, calculate the relay delay time.

- (A) 0.11 ms (B) 0.15 ms
 (C) 1.25 ms (D) 0.5 ms


9. Consider the circuit shown in below.

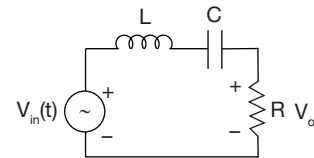

It is a


- (A) BSF (B) APF
 (C) BPF (D) HPF

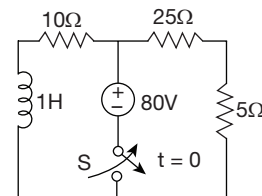10. In the circuit shown in the figure given below, the switch is opened at $t = 0$, after having been closed for a long time. What is the current through 25Ω resistor?




- (A) $8.e^{-10t}$ A (B) $6.e^{-10t}$ A
 (C) $8.e^{-40t}$ Amp (D) $4.e^{-40t}$ A

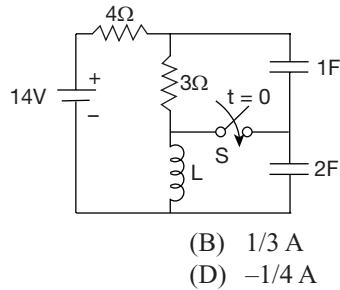11. The circuit given below is in steady state for a long time with switch S open, The switch is closed at $t = 0$. The current through switch will be _____



- (A) $2/3$ A (B) $1/3$ A
(C) 0 (D) $-1/4$ A


12. Consider the circuit shown in figure

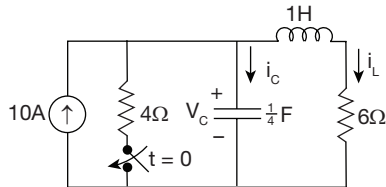

Determine the values of $\frac{di_L(0^+)}{dt}$ and $\frac{dV_c(0^+)}{dt}$

- (A) -10 A/sec and 0
(B) 10 A/sec and -60 V/sec
(C) 12.5 A/sec and 45 V/sec
(D) 0 and -60 V/sec


13. Consider the circuit shown in below.

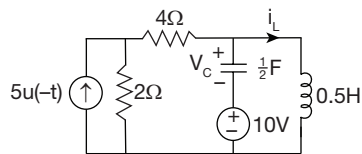

The values of $\frac{di(0^+)}{dt}$ and $\frac{dV_c(0^+)}{dt}$ would be ____

- (A) 0 and $-10/3$ V/sec
(B) 3.2 A/sec and 4 V/sec
(C) -2.5 A/sec and $-5/3$ V/sec
(D) 0 and 2.5 V/sec


14. Consider the circuit shown below

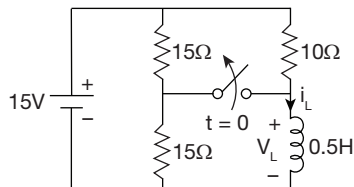

Find the energy stored in the inductor at $t = 0^+$.

- (A) 1.25 mJ (B) 4.5 mJ
(C) 3.12 J (D) 1.56 J


15. Consider the circuit shown in below

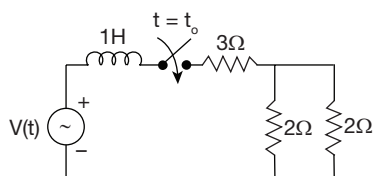

If $V(t) = 4 \sin 2t$ volts, the circuit is in transient free condition, then the value of t_0 is ____

- (A) 13.28 sec (B) 2.25 sec
(C) 0.2318 sec (D) 3.25 msec


16.

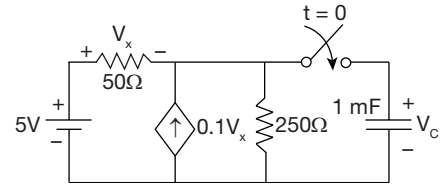

Find the value of V_c at $t = 2$ ms.


- (A) 1.06 V (B) 0.75 V
(C) 3.5 V (D) 1.25 V

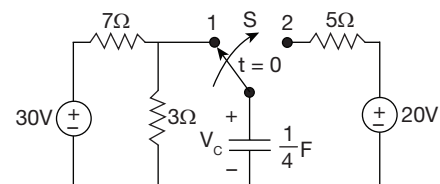17. For the circuit shown in figure below, the switch has been in position 1 for a long time. At $t = 0$, the switch is moved to position 2. Then, the capacitor voltage $V_c(t)$ for $t > 0$ is ____



- (A) $(9 + 11.e^{-4t/5})$ volts (B) $(20 - 11.e^{-4t/5})$ volts
(C) $(20 + 9.e^{-1.25t})$ volts (D) $(9 + 11.e^{-1.25t})$ volts

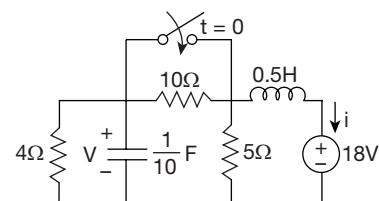
18. Consider the circuit shown in below figure



Find the steady state values of voltage and current.


- (A) 10V, 8.1A (B) 18V, -8.1 A
(C) 8V, 4.5A (D) 6V, 9A

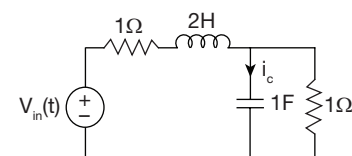19. If $i_c(t) = -5.e^{-2.5t}$ A, the voltage of the source of the given circuit, $V_{in}(t)$ is given by



- (A) $-16.e^{-2.5t}$ V (B) $14.e^{-2.5t}$ V
(C) $8.e^{-2.5t}$ V (D) $-10.e^{-2.5t}$ V


20.

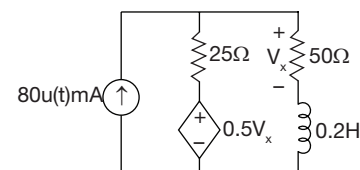

Find $V_x(t)$ for all t ?

- (A) $1.6[1 - e^{-150t}]u(t)$ mV (B) $80[1 - e^{-150t}]u(t)$ mV
(C) $2.5[1 - e^{-75t}]u(t)$ V (D) $1.6[1 - e^{-75t}]u(t)$ mV

21. Consider the circuit shown in figure

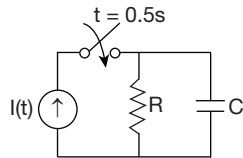


If $i(t) = I_m \cos(2t + \phi)$ Amp and time constant of the circuit is $\frac{1}{2}$ sec.

At what value of ϕ , the circuit gives transient free response?

- (A) 135° (B) 1.356 rad
(C) 77.70° (D) B and C

Common Data for 22 and 23:

Consider the circuit shown in figure

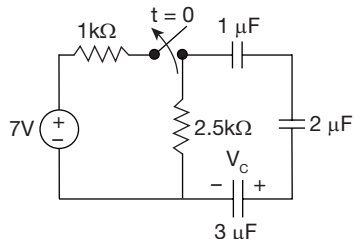


22. Find the $V_c(t)$.

- (A) $5.e^{-1000t/1.36}$ V (B) $0.9.e^{-1000t/1.36}$ Volts
(C) $3.2.e^{-1000t/6}$ V (D) $0.9.e^{-500t/3}$ Volts

23. At $t = 1$ ms the power dissipated by the 2.5 kΩ is _____.

- (A) 1.52 mW (B) 1.78 mW
(C) 2.3 mW (D) 4.4 mW

Common Data for 24 and 25:

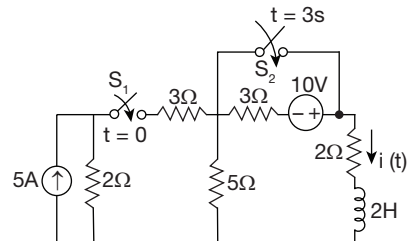

24. Find the $i(t)$ for $0 < t < 3$.

- (A) $2\left(1 - e^{-\frac{15t}{4}}\right)$ A (B) $2\left(1 + e^{-\frac{15t}{4}}\right)$ A
(C) $2e^{-\frac{15t}{4}}$ A (D) $e^{-\frac{15t}{4}}$ A

25. Calculate $i(t)$ for $t > 3$

- (A) $1.11 - 0.88.e^{-4/9(t-3)}$ A
(B) $2 - 0.88.e^{-2.25t}$ A
(C) $1.11 + 0.88.e^{-2.25(t-3)}$ A
(D) $1.11 - 0.88.e^{-4/9t}$ A

ANSWER KEYS

- | | | | | | | | | | |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 1. A | 2. D | 3. B | 4. D | 5. C | 6. B | 7. D | 8. A | 9. C | 10. C |
| 11. A | 12. D | 13. A | 14. D | 15. C | 16. A | 17. B | 18. B | 19. B | 20. A |
| 21. D | 22. B | 23. C | 24. A | 25. C | | | | | |

HINTS AND EXPLANATIONS

1. For $i(t)$ to be maximum only when

$$\frac{di(t)}{dt} = 0 \text{ and } \frac{d^2 i(t)}{dt^2} < 0$$

Given $i(t) = 2t.e^{-5t}$ A


$$\frac{di}{dt} = 2\{e^{-5t} + t.(-5).e^{-5t}\} = 0$$

$$1 - 5t = 0$$

$$t = 1/5 \text{ sec}$$

Choice (A)

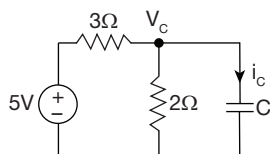2. After closing the switch the given circuit becomes



$$\frac{V_c - 5}{3} + \frac{V_c}{2} + C \cdot \frac{dV_c}{dt} = 0$$

$$2V_c - 10 + 3V_c + 6C \frac{dV_c}{dt} = 0$$

Given $V_c = 2.5$ volts

$$\frac{dV_c}{dt} = -8 \text{ V/sec}$$

$$5V_c - 10 = 6 \times 8V$$

$$C = \frac{2.5}{48} \text{ F}$$

$$= 0.052 \text{ Farads}$$

Choice (D)


3. $R_{eq} = 5 + 20 \parallel 30 = 17 \Omega$

$$\tau = \frac{L}{R} \Rightarrow L = 1.5 \times 17 \text{ mH}$$

$$L = 25.5 \text{ mH}$$

Choice (B)

4. From the given data

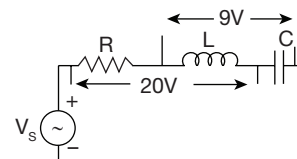

$$V_L - V_C = 9V$$

$$V_S = 15V$$

$$(15)^2 = V_R^2 + (9)^2$$

$$V_R = 12V \text{ and } V_x = \sqrt{V_R^2 + V_L^2}$$

$$(20)^2 = (12)^2 + V_L^2$$

$$V_L = 16V$$

$$V_L - V_C = 9V$$

$$V_C = 16 - 9 = 7 \text{ volts}$$

$$\therefore \frac{V_L}{V_C} = 2.28$$

Choice (D)

$$5. Z(S) = \frac{V(S)}{I(S)} = \frac{3S+2}{0.5S+3}$$

$$I(S) = \frac{1}{S}$$

$$V(S) = Z(S) \cdot I(S)$$

$$V(S) = \frac{(3S+2)}{S(0.5S+3)}$$

$\therefore$ steady state value nothing but final value

$$\therefore V = \lim_{s \rightarrow 0} s \cdot V(S) = \frac{2}{3} V$$

Choice (C)

6. From the given circuit

$$I_1 = I_s = 8A$$

$$I_3 = I_L = 3A$$

$$\therefore \text{ we know } I_s = \sqrt{I_R^2 + (I_L - I_C)^2}$$

$$\text{But } I_R = 0$$

$$I_s = (I_L - I_C) \text{ or } I_C - I_L$$

$$\therefore I_C = I_L + I_s = 11 \text{ Amp}$$

Choice (B)

7. From the given data

Roots are complex conjugate, so it is a under damped system

$$\therefore \xi < 1$$

$$\xi = \frac{1}{2Q}$$

$$Q = R \sqrt{\frac{C}{L}} \text{ for parallel RLC circuits}$$

$$\therefore \frac{1}{2R} \sqrt{\frac{L}{C}} < 1$$

$$\frac{1}{4} \sqrt{\frac{1}{2C}} < 1$$

$$\frac{1}{2C} < 16$$

$$C > \frac{1}{32}$$

$$C > 31.25 \text{ mF}$$

$$\therefore \text{ Let } C = 32 \text{ mF}$$

Choice (D)

8. The current through the coil is given by

$$i(t) = i(\infty) + \{i(0) - i(\infty)\} \cdot e^{-t/\tau}$$

$$i(0) = 0, i(\infty) = \frac{15}{200} = 75 \text{ mA}$$

$$\tau = \frac{L}{R} = \frac{30 \times 10^{-3}}{200} = 0.15 \text{ ms}$$

$$i(t) = 75[1 - e^{-t/\tau}] \text{ mA}$$

$$\text{If } i(t_d) = 40 \text{ mA, then } t_d = ?$$

$$40 = 75[1 - e^{-t/\tau}]$$

$$e^{-t/\tau} = 0.466$$

$$-\frac{t_d}{\tau} = \ln(0.466)$$

$$t_d = 0.7621\tau = 0.11 \text{ msec}$$

Choice (A)

9. At low frequencies $f \rightarrow 0 \text{ Hz}$

$L \rightarrow$ short circuit

$C \rightarrow$ open circuit

$$I_R = 0 \text{ Amp}$$

$$\therefore V_o = 0 \text{ volts at high frequencies}$$


$$f \rightarrow \infty$$

$L \rightarrow$ open circuit

$C \rightarrow$ short circuit

$$I_R = 0$$

$$\therefore V_o = 0$$

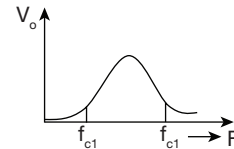


BPF

Choice (C)

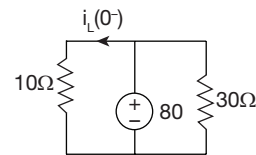10. Initially at $t = 0^-$ switch was closed

In steady state the inductor behaves like short circuit



$$i_L(0^-) = \frac{80}{10} = 8 \text{ Amp}$$

For $t \geq 0$:-

Switch is opened at $t > 0$

$\therefore$ for $t > 0$ it becomes source free circuit

$$i_L(t) = I_o \cdot e^{-t/\tau} \text{ A}$$

$$\tau = \frac{L_{eq}}{R_{eq}}$$

$$L = 1H$$

$$R_{eq} = (10 + 30) \Omega = 40 \Omega$$

$$\tau = 1/40$$

$$i_L(t) = 8 \cdot e^{-40t} \text{ Amp}$$


Choice (C)

11. For $t < 0$:-

At $t = 0^-$; switch opened, the circuit is in steady state

3.28 | Networks Test 3

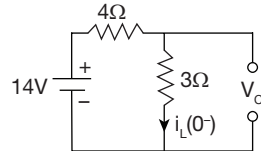$\therefore L \rightarrow$ short circuit
 $C \rightarrow$ open circuit




$$i_L(0^-) = \frac{14}{7} = 2A$$

$$V_C(0^-) = 6V$$

$$\therefore V_{1F}(0^-) = \frac{6 \times 2}{3} = 4V$$

$$V_{2F}(0^-) = \frac{6 \times 1}{3} = 2V$$

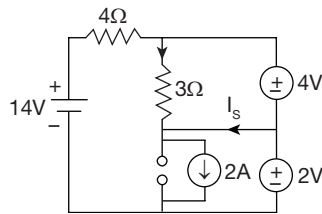$\therefore$ for $t > 0$, the circuit becomes shown below



$$\therefore i_L = i_{3\Omega} + I_s$$


$$2 = \frac{4}{3} + I_s$$

$$I_s = 2 - \frac{4}{3} = 2/3 \text{ Amp}$$

Choice (A)

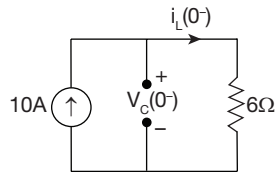12. For $t < 0$:-


In steady state the equivalent circuit becomes



$$i_L(0^-) = 10A = i_L(0^+)$$

$$V_C(0^-) = 60V = V_C(0^+)$$

For $t > 0$:-

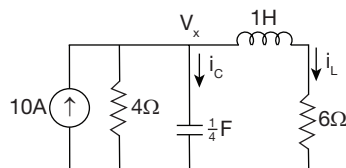

$$-10 + \frac{V_x}{4} + i_c + i_L = 0$$

$$i_c = \frac{CdV_c}{dt}$$

$$V_L = L \cdot \frac{di_L}{dt}$$

But $V_x = V_C$

$$-10 + \frac{V_c}{4} + C \cdot \frac{dV_c}{dt} + i_L = 0$$

at $t = 0^+$

$$C \frac{dV_c(0^+)}{dt} = 10 - \frac{V_c(0^+)}{4} - i_L(0^+)$$

$$= 10 - 15 - 10$$

$$\frac{dV_c(0^+)}{dt} = \frac{-15}{\frac{1}{4}}$$

$$\frac{dV_c(0^+)}{dt} = -60 \text{ V/sec}$$

$$V_x = V_L + 6i_L$$

$$V_x = V_C$$

$$V_C(0^+) = L \frac{di_L(0^+)}{dt} + 6i_L(0^+)$$


$$60 - 6 \times 10 = \frac{L di_L}{dt}$$

$$\frac{di_L}{dt} = 0 \text{ A/sec}$$

Choice (D)

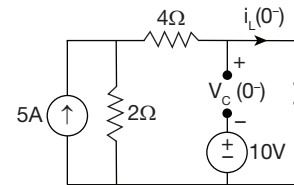13. For $t < 0$:-

At $t = 0^-$, the circuit is in steady state




$$V_C(0^-) = -10V = V_C(0^+)$$

$$i_L(0^-) = \frac{2}{6} \times 5 = \frac{5}{3}A = i_L(0^+)$$

for $t > 0$:-

$$5u(-t) = 0 \Rightarrow \text{open circuit}$$

The equivalent circuit becomes

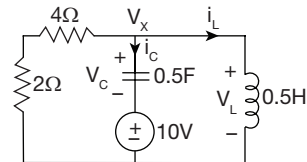

$$V_L = V_C + 10$$

$$\frac{L \cdot di_L(0^+)}{dt} = V_C(0^+) + 10$$

$$\frac{di_L(0^+)}{dt} = 0$$

at $t = 0^+$

$$V_x(0^+) = V_C(0^+) + 10V$$

$$V_x(0^+) = 0V$$

$$\therefore i_c = -i_L$$

$$i_c = \frac{C \cdot dV_c}{dt} = -i_L$$


$$\frac{dV_c(0^+)}{dt} = \frac{-i_L(0^+)}{C} = -\frac{5}{3} \times 2$$

$$= -\frac{10}{3} \text{ V/sec}$$

Choice (A)

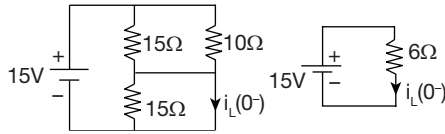14. For $T < 0$:- Switch was closed,

$\therefore$ The circuit becomes shown in below



$$i_L(0^-) = \frac{15}{6} = 2.5 \text{ Amp}$$

$$i_L(0^+) = 2.5 \text{ Amp}$$

$$W = \frac{1}{2} L I_o^2 = \frac{1}{2} \times 0.5 \times (2.5)^2$$

$$= 1.5625 \text{ Joules}$$

Choice (D)

15. for $t < t_0$:-

Switch opened

For $t > t_0$:-

For RL series circuits, transient free condition is

$$\omega t_0 + \phi = \tan^{-1} \omega \tau$$

where $\phi = 0$

$$\omega = 2 \text{ rad/sec}$$

$$\tau = \frac{L}{R} = \frac{1}{4}$$

$$2t_0 = \tan^{-1} \left[\frac{1}{2} \right] = 0.4636$$

$$t_0 = 0.2318 \text{ sec}$$

Choice (C)

16. For $t < 0$:-

Switch opened;

$$\therefore V_c(0^-) = 0 = V_c(0^+)$$


For $t > 0$:-

At $t = 0^+$ switch closed

$$V_c(0^+) = 0V$$

$\therefore$ As $t \rightarrow \infty$; circuit is in steady state

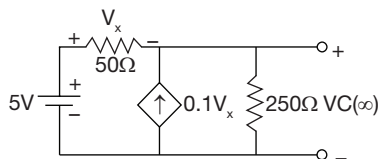In S.S capacitor behaves like an open circuit.



$$\frac{V_c(\infty) - 5}{50} + \frac{V_c(\infty)}{250} = 0.1V_x$$

$$\text{but } 5 - V_x - V_c(\infty) = 0$$

$$V_x = 5 - V_c(\infty)$$

$$6V_c(\infty) - 25 = 25[5 - V_c(\infty)]$$

$$31V_c(\infty) = 150$$

$$V_c(\infty) = 4.83 \text{ volts}$$


$$\therefore V_c(t) = V_c(\infty) + \{V_c(0^+) - V_c(\infty)\} \cdot e^{-t/\tau}$$

$$\therefore V_c(t) = 4.83[1 - e^{-t/\tau}] \cdot u(t)$$

τ :-

$$\tau = RC$$

$$R = R_{th}:-$$

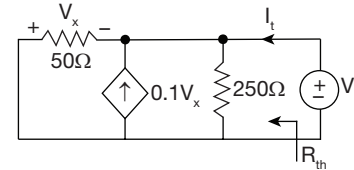

$$-I_t + \frac{V_t}{250} + \frac{V_t}{50} - 0.1V_x = 0$$

$$V_t + V_x = 0$$

$$V_x = -V_t$$

$$\frac{6V_t}{250} = I_t - 0.1V_t$$

$$6V_t = 250 I_t - 25 V_t$$

$$31V_t = 250 I_t$$

$$R_{th} = \frac{V_t}{I_t} = \frac{250}{31} = 8.064 \Omega$$

$$\tau = 8.064 \times 1 \text{ m sec}$$

$$\tau = 8.064 \text{ m sec}$$


$$V_c(t) = 4.83[1 - e^{-124t}]u(t) \text{ at } t = 2 \text{ m sec}$$

$$V_c(2\text{m}) = 1.06 \text{ volts}$$

Choice (A)

17. For $t < 0$:- The switch connected to position 1.

at $t = 0^-$

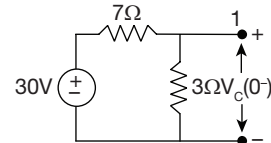


ckt is in S.S

$$\therefore V_c(0^-) = \frac{3}{10} \times 30 = 9V = V_c(0^+)$$

For $t > 0$:- Switch $\rightarrow$ position 2.

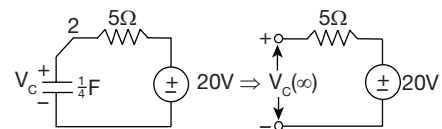The circuit becomes of $t \rightarrow \infty$ (in steady state)



$$\therefore V_c(\infty) = 20V$$

$$\therefore V_c(t) = V_c(\infty) + \{V_c(0^+) - V_c(\infty)\} \cdot e^{-t/\tau}$$

$$\tau = RC = 5 \times \frac{1}{4} = 1.25 \text{ sec}$$

$$V_c(t) = 20 + \{9 - 20\} \cdot e^{-t/1.25} \text{ volts}$$

$$V_c(t) = 20 - 11 \cdot e^{-4t/5} \text{ volts}$$

Choice (B)


3.30 | Networks Test 3

18. In steady state

$C \rightarrow$ open circuit

$L \rightarrow$ short circuit

The equivalent circuit is

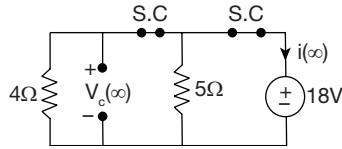

$$V_c(\infty) = 18V$$

$$\frac{18}{4} + \frac{18}{5} + i(\infty) = 0$$

$$18 \times 9 = -20 i(\infty)$$

$$i(\infty) = -8.1 \text{ Amp}$$

Choice (B)

19. We know

$$i_c = C \cdot \frac{dv_c}{dt}$$

$$V_c = \frac{1}{C} \int i_c(t) \cdot dt$$

$$= \frac{1}{1} \int -5 \cdot e^{-2.5t} \cdot dt$$

$$V_c = \frac{-5}{-2.5} \cdot e^{-2.5t} = 2 \cdot e^{-2.5t} \text{ volts}$$

$$I_R = \frac{V_c}{R} = 2 \cdot e^{-2.5t} \text{ Amp}$$

$$I_{in} = I_C + I_R$$

$$= -3 \cdot e^{-2.5t}$$

$$V_{in} - I_{in} \times 1 - L \cdot \frac{dI_{in}}{dt} - V_c = 0$$

$$V_{in} = I_{in} + V_c + VL$$

$$V_L = 2 \cdot \frac{d}{dt} \{-3 \cdot e^{-2.5t}\}$$

$$V_L = 6 \times 2.5 \cdot e^{-2.5t} \text{ volts}$$

$$V_{in} = -3 \cdot e^{-2.5t} + 2 \cdot e^{-2.5t} + 15 \cdot e^{-2.5t}$$

$$V_{in} = 14 \cdot e^{-2.5t} \text{ volts}$$

Choice (B)

20. For $t < 0$:-


The independent current source deactivates (open circuit)

$$\therefore i_L(0^-) = 0 \text{ Amp} = i_L(0^+)$$

For $t > 0$:-

If $t \rightarrow \infty$, the circuit is in steady state

$L \rightarrow$ short circuit

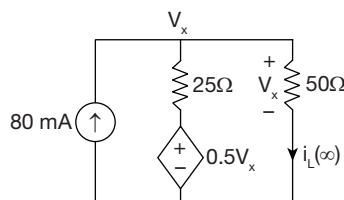

$$-80\text{mA} + \frac{0.5V_x}{25} + i_L(\infty) = 0$$

$$V_x = \frac{i_L(\infty)}{50}$$

$$80 \times 10^{-3} = \frac{i_L(\infty)}{50} \times \frac{1}{50} + i_L(\infty)$$

$$i_L(\infty) \left[1 + \frac{1}{25 \times 10^2} \right] = 80 \times 10^{-3}$$

$$i_L(\infty) = 79.96 \text{ mA}$$

$$\therefore i_L(t) = i(\infty) + [i(0^-) - i(\infty)] \cdot e^{-t/\tau}$$

$$i_L^L(t) = i(\infty) [1 - e^{-t/\tau}] u(t)$$


$$\tau = \frac{L_{eq}}{R_{eq}}$$

Res:-

(i) Deactivate all the independent sources.

(ii) Connect one test source

(iii) Find the equivalent resistance

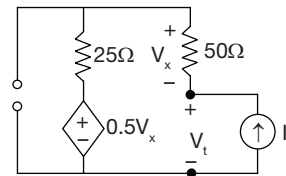

$$\therefore R_{th} = \frac{V_t}{I_t}$$

$$V_t + V_x - 25 I_t - 0.5 V_x = 0$$

$$V_t = 25 I_t + 50 I_t$$

$$\frac{V_t}{I_t} = R_{th} = 75 \Omega$$

$$\tau = \frac{0.5}{75} = \frac{1}{150} \text{ sec}$$

$$\therefore i_L(t) = 79.96 [1 - e^{-150t}] \cdot u(t) \text{ mA}$$

$$\therefore V_x = \frac{i_L(t)}{50}$$

$$V_x(t) \approx 1.6 [1 - e^{-150t}] \cdot u(t) \text{ mV}$$

Choice (A)

21. We know, the transient free conditions

$$\omega t_o + \phi = \tan^{-1} (\omega \tau + \pi/2) \text{ [for cosinusoidal input]}$$

$$2 t_o + \phi = \left\{ \tan^{-1} \left[2 \times \frac{1}{2} \right] + \frac{\pi}{2} \right\}$$

$$t_o = 1 \text{ sec}$$

$$\phi = \frac{\pi}{4} + \frac{\pi}{2} -$$


$$\phi = \frac{3\pi}{4} - 2$$

$$= 1.356 \text{ rad or } 77.70^\circ$$


Choice (D)

22. For $t < 0$:- Switch closed at $t = 0^-$; circuit is in steady state

$C \rightarrow$ open circuit

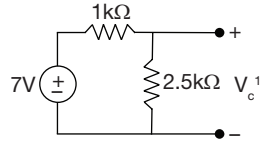
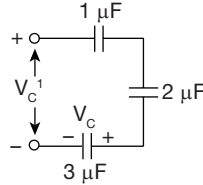
$$V_c^1 = \frac{2.5}{3.5} \times 7 = 5V$$



$$V_c = \frac{\frac{2}{3} \times V_c^1}{\frac{2}{3} + 3}$$

$$V_c = \frac{2 \times 5}{11} = 0.9V$$

For $t > 0$:-

$S \rightarrow$ opened;

$\therefore$ Source free RC circuit

$$V_c(t) = V_o \cdot e^{-t/\tau}$$

$$\tau = R, C$$

$$C_{eq} = [1 \mu f \parallel 2 \mu f \parallel 3 \mu f]$$

$$= \left(\frac{2}{3} \mu f \parallel 3 \mu f \right) = \frac{6}{11} \mu f$$

$$R = 2.5 \text{ k}\Omega$$

$$\tau = 1.36 \text{ m sec}$$

$$\therefore V_c(t) = 0.9 \cdot e^{-t/1.36 \times 10^{-3}} \text{ volts}$$

Choice (B)

$$23. P = VI = \frac{V_c^2}{R}$$

$$V_c^1(t) = 5 \cdot e^{-t/1.36 \times 10^{-3}} \text{ volts}$$

$$V_c^1(1ms) = 5 \cdot e^{-1/1.36} = 2.4 \text{ volts}$$

$$P = \frac{5.767}{2.5} \text{ mW} = 2.3 \text{ mW}$$

Choice (C)

24. Consider three time intervals $t \leq 0$, $0 \leq t < 3$ and $t \geq 3$ separately.


For $t < 0$, switches S_1 and S_2 are open so that $i = 0$

$$\therefore i(0^-) = i(0^+) = 0$$

For $0 \leq t < 3$: $S_1 \rightarrow$ closed

S_2 is still open

The equivalent circuit becomes

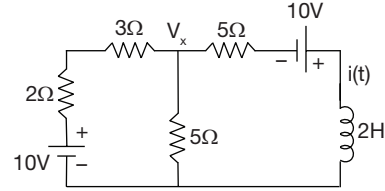

$$\therefore S_1 \text{ is closed forever, } i(\infty) = \frac{V_x + 10}{5}$$

$$\frac{V_x - 10}{5} + \frac{V_x}{5} + \frac{V_x + 10}{5} = 0$$

$$3V_x = 0$$

$$V_x = 0$$

$$\therefore i(\infty) = 2 \text{ Amp}$$

$$i(t) = i(\infty) + \{i(0^-) - i(\infty)\} \cdot e^{-t/\tau}$$

$$\tau = \frac{L_{eq}}{R_{eq}}$$

$$R_{eq} = 5 + (5 \parallel 5) = 7.5 \Omega$$

$$\tau = \frac{2}{7.5} = \frac{4}{15} \text{ sec}$$

$\therefore$ for $0 \leq t < 3$:-


$$i(t) = 2 \left\{ 1 - e^{-\frac{15}{4}t} \right\}; 0 \leq t < 3 \quad \text{Choice (A)}$$

25. For $t \geq 3$, S_1 and S_2 both are closed, thus the initial current in case 2 is

$$i(3) = i(3^-) = 2 \{ 1 - e^{-45/4} \} A$$

$$= 1.999 \approx 2A$$

The equivalent circuit for $t \geq 3$:-

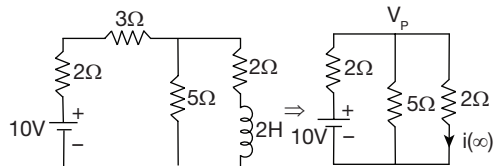

$$\frac{V_p - 10}{5} + \frac{V_p}{5} + \frac{V_p}{2} = 0$$

$$2V_p - 10 + 2.5V_p = 0$$

$$4.5V_p = 10 \Rightarrow V_p = 2.22 \text{ V}$$

$$i(\infty) = 1.11 \text{ Amp}$$

$$i(t) = i(\infty) + \{i(t_0) - i(\infty)\} e^{-(t-t_0)/\tau}$$

$$\tau = 2 + (5 \parallel 5) = 4.5$$

$$\tau = \frac{2}{4.5} = \frac{4}{9} \text{ sec}$$

$$\therefore i(t) = 1.11 + \{2 - 1.11\} \cdot e^{-9/4(t-3)} A$$

$$i(t) = 1.11 + 0.88 e^{-2.25(t-3)} A \text{ for } t \geq 3 \quad \text{Choice (C)}$$