

CHAPTER

3.3

BASIC FET CIRCUITS

Statement for Q.1–3:

In the circuit shown in fig. P3.3.1–3 the transistor parameters are as follows:

Threshold voltage $V_{TN} = 2 \text{ V}$

Conduction parameter $K_n = 0.5 \text{ mA} / \text{V}^2$

 


Fig. P3.3.1–3

1. $V_{GS} = ?$

- (A) 2.05 V (B) 6.43 V
(C) 4.86 V (D) 3.91 V

2. $I_D = ?$

- (A) 1.863 mA (B) 1.485 mA
(C) 0.775 mA (D) None of the above

3. $V_{DS} = ?$

- (A) 4.59 V (B) 3.43 V
(C) 5.35 V (D) 6.48 V

Statement for Q.4–6:

In the circuit shown in fig. P3.3.4–6 the transistor parameter are as follows:

$V_{TN} = 2 \text{ V}$, $k'_n = 60 \mu\text{A} / \text{V}^2$, $\frac{W}{L} = 60$

 


Fig. P3.3.4–6

4. $V_{GS} = ?$

- (A) -3.62 V (B) 3.62 V
(C) -0.74 V (D) 0.74 V

5. $I_D = ?$

- (A) 13.5 mA (B) 10 mA
(C) 19.24 mA (D) 4.76 mA

6. $V_{DS} = ?$

- (A) 2.95 V (B) 11.9 V
(C) 3 V (D) 12.7 V

16. The parameter of the transistor in fig. P3.3.16 are $V_{TN} = 1.2 \text{ V}$, $K_n = 0.5 \text{ mA} / \text{V}^2$ and $\lambda = 0$. The voltage V_{DS} is

 


Fig. P3.3.16

- (A) 1.69 V (B) 1.52 V
(C) 1.84 V (D) 0

17. The parameter of the transistor in fig. P3.3.17 are $V_{TN} = 0.6 \text{ V}$ and $K_n = 0.2 \text{ mA} / \text{V}^2$. The voltage V_S is

 


Fig. P3.3.17

- (A) 1.72 V (B) -1.72 V
(C) 7.28 V (D) -7.28 V

18. In the circuit of fig. P3.3.18 the transistor parameters are $V_{TN} = 1.7 \text{ V}$ and $K_n = 0.4 \text{ mA} / \text{V}^2$.

 


Fig. P3.3.18

If $I_D = 0.8 \text{ mA}$ and $V_D = 1 \text{ V}$, then value of resistor R_S and R_D are respectively

- (A) 2.36 kΩ, 5 kΩ (B) 5 kΩ, 2.36 kΩ
(C) 6.43 kΩ, 8.4 kΩ (D) 8.4 kΩ, 6.43 kΩ

19. In the circuit of fig. P3.3.19 the PMOS transistor has parameter $V_{TP} = -1.5 \text{ V}$, $k'_p = 25 \mu\text{A} / \text{V}^2$, $L = 4 \mu\text{m}$ and $\lambda = 0$. If $I_D = 0.1 \text{ mA}$ and $V_{SD} = 2.5 \text{ V}$, then value of W will be

 


Fig. P3.3.19

- (A) 15 μm (B) 1.6 μm
(C) 32 μm (D) 3.2 μm

20. The PMOS transistor in fig. P3.3.20 has parameters

$$V_{TP} = -1.2 \text{ V}, \quad \frac{W}{L} = 20, \quad \text{and} \quad k'_p = 30 \mu\text{A} / \text{V}^2.$$

 


Fig. P3.3.20

If $I_D = 0.5 \text{ mA}$ and $V_D = -3 \text{ V}$, then value of R_S and R_D are

- (A) 4 kΩ, 5.8 kΩ (B) 4 kΩ, 5 kΩ
(C) 5.8 kΩ, 4 kΩ (D) 5 kΩ, 4 kΩ

21. The parameters for the transistor in circuit of fig. P3.3.21 are $V_{TN} = 2 \text{ V}$ and $K_n = 0.2 \text{ mA} / \text{V}^2$. The power dissipated in the transistor is

 


Fig. P3.3.21

- (A) 5.84 mW (B) 2.34 mW
(C) 0.26 mW (D) 58.4 mW

Statement for Q.22–23:

Consider the circuit shown in fig. P3.2.22–33.

 


Fig. P3.3.22-23

The both transistor have parameter as follows

$$V_{TN} = 0.8 \text{ V}, \quad k'_n = 30 \text{ } \mu\text{A} / \text{V}^2$$

22. If the width-to-length ratios of M_1 and M_2 are

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 40$$

The output V_o is

- (A) -2.5 V (B) 2.5 V
(C) 5 V (D) 0 V

23. If the ratio is $\left(\frac{W}{L}\right)_1 = 40$ and $\left(\frac{W}{L}\right)_2 = 15$, then V_o is

- (A) 2.91 V (B) 2.09 V
(C) 3.41 V (D) 1.59 V

24. In the circuit of fig. P3.324. the transistor parameters are $V_{TN} = 1 \text{ V}$ and $k'_n = 36 \text{ } \mu\text{A} / \text{V}^2$. If $I_D = 0.5 \text{ mA}$, $V_1 = 5 \text{ V}$ and $V_2 = 2 \text{ V}$ then the width to-length ratio required in each transistor is

 


Fig. P3.3.24

$$\left(\frac{W}{L}\right)_1 \quad \left(\frac{W}{L}\right)_2 \quad \left(\frac{W}{L}\right)_3$$

- (A) 1.75 6.94 27.8
(B) 4.93 10.56 50.43
(C) 35.5 22.4 8.53
(D) 56.4 38.21 12.56

25. The transistors in the circuit of fig. P3.3.25 have parameter $V_{TN} = 0.8 \text{ V}$, $k'_n = 40 \text{ } \mu\text{A} / \text{V}^2$ and $\lambda = 0$. The width-to-length ratio of M_2 is $\left(\frac{W}{L}\right)_2 = 1$. If $V_o = 0.10 \text{ V}$ when $V_i = 5 \text{ V}$, then $\left(\frac{W}{L}\right)_1$ for M_1 is

 


Fig. P3.3.25

- (A) 47.5 (B) 28.4
(C) 40.5 (D) 20.3

Statement for Q.26–27:

All transistors in the circuit in fig. P3.3.26–27 have parameter $V_{TN} = 1 \text{ V}$ and $\lambda = 0$.

 


Fig. P3.3.26–27

The conduction parameter are as follows:

$$K_{n1} = 400 \text{ } \mu\text{A} / \text{V}^2$$

$$K_{n2} = 200 \text{ } \mu\text{A} / \text{V}^2$$

$$K_{n3} = 100 \text{ } \mu\text{A} / \text{V}^2$$

$$K_{n4} = 80 \text{ } \mu\text{A} / \text{V}^2$$

26. $I_{D1} = ?$

- (A) 0.23 mA (B) 0.62 mA
(C) 0.46 mA (D) 0.31 mA

27. $I_{D4} = ?$

- (A) 0.62 mA (B) 0.31 mA
(C) 0.46 mA (D) 0.92 mA

28. For the circuit in fig. P3.3.28 the transistor parameters are $V_{TN} = 0.8 \text{ V}$ and $k'_n = 30 \mu\text{A} / \text{V}^2$. If output voltage is $V_o = 0.1 \text{ V}$, when input voltage is $V_i = 4.2 \text{ V}$, the required transistor width-to length ratio is

 


Fig. P3.3.28

- (A) 1.568 (B) 0.986
(C) 0.731 (D) 1.843

29. For the transistor in fig. P3.3.29 parameters are $V_{TN} = 1 \text{ V}$ and $K_n = 12.5 \mu\text{A} / \text{V}^2$. The Q-point (I_D, V_{DS}) is

 


Fig. P3.3.29.

- (A) (1 mA, 8 V) (B) (0.2 mA, 4 V)
(C) (1.17 mA, 8 V) (D) (0.23 mA, 3.1V)

30. For an n -channel JFET, the parameters are $I_{DSS} = 6 \text{ mA}$ and $V_p = -3 \text{ V}$. If $V_{DS} > V_{DS(sat)}$ and $V_{GS} = -2 \text{ V}$, then I_D is

- (A) 16.67 mA (B) 0.67 mA
(C) 5.55 mA (D) 1.67 mA

31. For the circuit in fig. P3.3.32 the transistor parameters are $V_p = -3.5 \text{ V}$, $I_{DSS} = 18 \text{ mA}$, and $\lambda = 0$. The value of V_{DS} is

 


Fig. P3.3.32

- (A) 7.43 V (B) 8.6 V
(C) -1.17 V (D) 1.17 V

32. A p -channel JFET biased in the saturation region with $V_{SD} = 5 \text{ V}$ has a drain current of $I_D = 2.8 \text{ mA}$, and $I_D = 0.3 \text{ mA}$ at $V_{GS} = 3 \text{ V}$. The value of I_{DSS} is

- (A) 10 mA (B) 5 mA
(C) 7 mA (D) 2 mA

Statement for Q.33–34:

For the p -channel transistor in the circuit of fig. P3.3.33–34 the parameters are $I_{DSS} = 6 \text{ mA}$, $V_p = 4 \text{ V}$ and $\lambda = 0$.

 


Fig. P3.3.33–34

- 33.** The value of I_{DQ} is
(A) 8.86 mA (B) 6.39 mA
(C) 4.32 mA (D) 1.81 mA

- 34.** The value of V_{SD} is
(A) -4.28 V (B) 2.47 V
(C) 4.28 V (D) 2.19 V

35. The transistor in the circuit of fig. P3.3.35 has parameters $I_{DSS} = 8 \text{ mA}$ and $V_p = -4 \text{ V}$. The value of V_{DSQ} is

 


Fig. P3.3.35

- (A) 2.7 V (B) 2.85 V
(C) -1.30 V (D) 1.30 V

SOLUTIONS

1. (A) $R_1 = 32 \text{ k}\Omega$, $R_2 = 18 \text{ k}\Omega$, $V_{DD} = 10 \text{ V}$

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \left(\frac{18}{18 + 32} \right) 10 = 3.6 \text{ V}$$

Assume that transistor in saturation region

$$I_D = \frac{V_S}{R_S} = \frac{V_G - V_{GS}}{R_S} = K_n (V_{GS} - V_{TN})^2$$

$$R_S = 2 \text{ k}\Omega, \quad K_n = 0.5 \text{ mA/V}^2$$

$$3.6 - V_{GS} = (2)(0.5)(V_{GS} - 0.8)^2 \Rightarrow V_{GS} = 2.05 \text{ V}$$

2. (C) $I_D = \frac{V_G - V_{GS}}{R_S} = \frac{3.6 - 2.05}{2\text{k}} = 0.775 \text{ mA}$

3. (C) $V_{DS} = V_{DD} - I_D(R_D + R_S)$

$$= 10 - 0.775(4 + 2) = 5.35 \text{ V}$$

$$V_{DS(sat)} = V_{GS} - V_{TN} = (2.05 - 0.8) = 1.25 \text{ V}$$

$V_{DS} > V_{DS(sat)}$ as assumed.

4. (B) $R_1 = 14 \text{ k}\Omega$, $R_2 = 6 \text{ k}\Omega$, $R_S = 0.5 \text{ k}\Omega$, $R_D = 1.2 \text{ k}\Omega$

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) (20) - 10 = \left(\frac{6}{14 + 6} \right) (20) - 10 = -4 \text{ V}$$

Assume transistor in saturation

$$I_D = \frac{V_S - (-10)}{R_S} = \frac{V_G - V_{GS} + 10}{R_S} = K_n (V_{GS} - V_{TN})^2$$

$$K_n = \frac{k'_n}{2} \frac{W}{L} = \frac{(60)(60 \times 10^{-6})}{2} = 1.8 \text{ mA/V}^2$$

$$\Rightarrow -4 - V_{GS} + 10 = (0.5)(1.8)(V_{GS} - 2)^2$$

$$\Rightarrow V_{GS} = 3.62, -0.74 \text{ V}, V_{GS} \text{ will be positive.}$$

5. (D) $I_D = \frac{V_G - V_{GS} + 10}{R_S} = \frac{-4 - 3.62 + 10}{0.5\text{k}} = 4.76 \text{ mA}$

6. (B) $10 = I_D(R_S + R_D) + V_{DS} - 10$

$$V_{DS} = 20 - 4.76(1.2 + 0.5) = 11.9 \text{ V}$$

$$V_{DS(sat)} = V_{GS} - V_{TN} = 3.62 - 2 = 1.62 \text{ V}$$

$V_{DS} = 11.9 \text{ V} > V_{DS(sat)}$, Assumption is correct.

7. (B) $R_1 = 8 \text{ k}\Omega$, $R_2 = 22 \text{ k}\Omega$, $R_S = 0.5 \text{ k}\Omega$, $R_D = 2 \text{ k}\Omega$

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) (20) - 10 = \left(\frac{22}{8 + 22} \right) (20) - 10 = 4.67 \text{ V}$$

Assume transistor in saturation

$$I_D = \frac{10 - V_S}{R_S} = K_P (V_{SG} + V_{TP})^2$$

$$V_S = V_G + V_{SG}$$

$$10 - (4.67 + V_{SG}) = (0.5)(1)(V_{GS})$$

$$\Rightarrow V_{SG} = 3.77 \text{ V}, -1.77 \text{ V}, V_{SG} \text{ is positive voltage.}$$

8. (A) $I_D = \frac{10 - V_S}{R_S} = \frac{10 - (V_G + V_{GS})}{R_S}$

$$= \frac{10 - (4.67 + 3.77)}{0.5} = 3.12 \text{ mA}$$

9. (C) $10 = I_D(R_S + R_D) + V_{SD} - 10$

$$V_{SD} = 20 - I_D(R_S + R_D) = 20 - 2.12(2 + 0.5) = 12.2 \text{ V}$$

10. (C) Assume transistor in saturation.

$$I_D = 0.4 \text{ mA}, \quad 0.4 = K_P (V_{GS} + V_{TP})^2$$

$$0.4 = (0.2)(V_{SG} - 0.8)^2 \Rightarrow V_{SG} = \sqrt{2} + 0.8 = 2.21 \text{ V}$$

$$V_G = 0, \quad V_{SG} = V_S - V_G = V_S$$

11. (A) $V_D = I_D R_D - 5 = (0.4)(5) - 5 = -3 \text{ V}$

$$V_{SD} = V_S - V_D = 2.21 - (-3) = 5.21 \text{ V}$$

12. (C) $R_1 = 14.5 \text{ k}\Omega$, $R_2 = 5.5 \text{ k}\Omega$,

$$R_S = 0.6 \text{ k}\Omega, \quad R_D = 0.8 \text{ k}\Omega,$$

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) (10) - 5 = \left(\frac{5.5}{14.5 + 5.5} \right) (10) - 5 = -2.25 \text{ V}$$

Assume transistor in saturation.

$$I_D = \frac{V_S - (-5)}{R_S} = K_n (V_{GS} - V_{TN})^2$$

$$V_S = V_G - V_{GS}$$

$$-2.25 - V_{GS} + 5 = (0.6)(0.5)(V_{GS} - (-1))^2$$

$$\Rightarrow V_{GS} = 1.24, -6.58 \text{ V}$$

V_{GS} is positive. Thus (D) is correct option.

13. (D) $I_D = \frac{V_S + 5}{R_S} = \frac{V_G - V_{GS} + 5}{R_S} = \frac{-2.25 - 1.24 + 5}{0.6\text{k}}$

$$= 2.52 \text{ mA}, \text{ Therefore (D) is correct option.}$$

14. (B) $5 = I_D(R_S + R_D) + V_{DS} - 5$

$$V_{DS} = 10 - I_D(R_S + R_D) = 10 - 2.52(0.8 + 0.6) = 6.47 \text{ V}$$

$$V_{DS(sat)} = V_{GS} - V_{TH} = 1.24 - (-1) = 2.24$$

$V_{DS} > V_{DS(sat)}$, Assumption is correct.

15. (B) $I_S = 50 \mu\text{A} = I_D, I_D = K_n (V_{GS} - V_{TN})^2$

$$\Rightarrow 50 \times 10^{-6} = 0.5 \times 10^{-3} (V_{GS} - 1.2)^2 \Rightarrow V_{GS} = 1.516 \text{ V},$$

$$V_G = 0, \quad V_S = V_G - V_{GS} = -1.516 \text{ V}$$

$$V_{DS} = V_D - V_S = 5 - (-1.516) = 6.516 \text{ V}$$

16. (B) $I_D = 50 \mu\text{A} = K_n (V_{GS} - V_{TN})^2$

$$\Rightarrow 50 \times 10^{-6} = 0.5 \times 10^{-3} (V_{GS} - 1.2)^2$$

$$V_{GS} = 1.52 \text{ V}, \quad V_{GS} = V_{DS}$$

$$17. \text{ (B) } I_D = K_n (V_{GS} - V_{TN})^2$$

$$\Rightarrow 0.25 = 0.2(V_{GS} - 0.6)^2 \Rightarrow V_{GS} = 1.72 \text{ V},$$

$$V_{GS} = V_G - V_S, \quad V_G = 0, \quad V_S = -1.72 \text{ V}$$

$$18. \text{ (A) } I_D = \frac{5 - V_D}{R_D} = 0.8 \text{ mA}, \quad R_D = \frac{6 - 1}{0.8 \text{ m}} = 5 \text{ k}\Omega$$

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$\Rightarrow 0.8 = (0.4)(V_{GS} - 1.7)^2 \Rightarrow V_{GS} = 3.11 \text{ V}$$

$$V_{GS} = V_G - V_S, \quad V_G = 0, \quad V_S = -3.11 \text{ V}$$

$$I_D = 0.8 \text{ mA} = \frac{-3.11 - (-5)}{R_S} \Rightarrow R_S = 2.36 \text{ k}\Omega$$

$$19. \text{ (C) } V_{SD} = V_{SG}, \quad I_D = \frac{k'_p}{2} \frac{W}{L} (V_{GS} + V_{TP})^2$$

$$10^{-4} = \left(\frac{25}{2}\right) \left(\frac{W}{4}\right) (2.5 - 1.5)^2 \Rightarrow W = 32 \text{ }\mu\text{m}$$

$$20. \text{ (D) } K_p = \left(\frac{30 \times 10^{-6}}{2}\right) (20) = 0.3 \text{ mA/V}^2$$

$$I_D = K_p (V_{SG} + V_{TP})^2 \Rightarrow 0.5 = 0.3(V_{SG} - 1.2)^2$$

$$\Rightarrow V_{SG} = 2.49 \text{ V}, \quad V_G = 0$$

$$V_S = V_{SG} = 2.49 \text{ V}$$

$$I_D = \frac{5 - V_S}{R_S} \Rightarrow R_S = \frac{5 - 2.49}{0.5 \text{ m}} = 5.02 \text{ k}\Omega$$

$$I_D = \frac{V_D - (-5)}{R_D} \Rightarrow R_D = \frac{-3 + 5}{0.5 \text{ m}} = 4 \text{ k}\Omega$$

21. (B) Assume transistor in saturation

$$I_D = \frac{10 - V_{GS}}{10 \text{ k}} = K_n (V_{GS} - V_{TN})^2$$

$$10 - V_{GS} = (10)(0.2)(V_{GS} - 2)^2$$

$$\Rightarrow V_{GS} = 3.77 \text{ V}, \quad -0.27 \text{ V}, \quad V_{GS} \text{ will be } 3.77 \text{ V}$$

$$V_{GS} = V_{DS} = 3.77 \text{ V}$$

$$I_D = \frac{10 - 3.77}{10 \text{ k}} = 0.623 \text{ mA}$$

$$\text{Power} = I_D V_{DS} = 2.35 \text{ mW}$$

$$V_{DS} > V_{GS} - V_{TN} \text{ assumption is correct.}$$

22. (B) For both transistor $V_{DS} = V_{GS}$,

$V_{DS} > V_{GS} - V_{TN}$ Therefore both transistor are in saturation.

$$I_{D1} = I_{D2} \Rightarrow K_{n1} (V_{GS1} - V_{TN1})^2 = K_{n2} (V_{GS2} - V_{TN2})^2$$

$$K_{n1} = K_{n2}, \quad V_{TN1} = V_{TN2}$$

$$V_{GS1} = V_{GS2} = \frac{5}{2} \text{ V}$$

$$V_o = V_{GS2} = 2.5 \text{ V}$$

$$23. \text{ (A) } \left(\frac{W}{L}\right)_1 > \left(\frac{W}{L}\right)_2 \text{ thus } V_{GS1} < V_{GS2}$$

$$40(V_{GS1} - 0.8)^2 = 15(V_{GS2} - 0.8)^2$$

$$V_{GS2} = 5 - V_{GS1}$$

$$1.63(V_{GS1} - 0.8) = (5 - V_{GS1} - 0.8)$$

$$V_{GS1} = 2.09, \quad V_{GS2} = 2.91 \text{ V}, \quad V_o = V_{GS2} = 2.91 \text{ V}$$

24. (A) Each transistor is biased in saturation because

$$V_{DS} = V_{GS} \text{ and } V_{DS} > V_{GS} - V_{TN}$$

$$\text{For } M_3, \quad V_2 = 2 \text{ V} = V_{GS3}$$

$$I_D = 0.5 = \left(\frac{36 \times 10^{-3}}{2}\right) \left(\frac{W}{L}\right)_3 (2 - 1)^2 \Rightarrow \left(\frac{W}{L}\right)_3 = 27.8$$

$$\text{For } M_2, \quad V_{GS2} = V_1 - V_2 = 5 - 2 = 3 \text{ V}$$

$$I_D = 0.5 = \left(\frac{36 \times 10^{-3}}{2}\right) \left(\frac{W}{L}\right)_2 (3 - 1)^2 \Rightarrow \left(\frac{W}{L}\right)_2 = 6.94$$

$$\text{For } M_1, \quad V_{GS1} = 10 - V_1 = 10 - 5 = 5 \text{ V}$$

$$I_D = 0.5 = \left(\frac{36}{2} \times 10^{-5}\right) \left(\frac{W}{L}\right)_1 (5 - 1)^2 \Rightarrow \left(\frac{W}{L}\right)_1 = 1.74$$

25. (D) M_2 is in saturation because

$$V_{GS2} = V_{DS2} > V_{GS2} - V_{TN}$$

M_1 is in non saturation because

$$V_{GS1} = V_i = 5 \text{ V}, \quad V_{DS1} = V_D = 0 \text{ V}$$

$$V_{DS1} < V_{GS1} - V_{TN}, \quad I_{D1} = I_{D2}$$

$$\left(\frac{W}{L}\right)_1 [2(V_{GS1} - V_{TN1})V_{DS1} - V_{DS1}^2] = \left(\frac{W}{L}\right)_2 (V_{GS2} - V_{TN2})^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_1 [2(5 - 0.8)(0.1) - (0.1)^2] = (1)(5 - 0.1 - 0.8)^2$$

$$\left(\frac{W}{L}\right)_1 (0.83) = 16.81 \Rightarrow \left(\frac{W}{L}\right)_1 = 20.3$$

$$26. \text{ (B) } I_{D1} = K_{n1} (V_{GS1} - V_{TN})^2 = K_{n2} (V_{GS2} - V_{TN})^2$$

$$V_{GS1} = 5 - V_{GS2} \Rightarrow (5 - V_{GS2} - 1)^2 = 200 (V_{GS2} - 1)^2$$

$$\Rightarrow V_{GS2} = 2.76 \text{ V}, \quad V_{GS1} = 2.24 \text{ V}$$

$$I_{D1} = 400 \times 10^{-6} (2.24 - 1)^2 = 0.62 \text{ mA}$$

$$27. \text{ (B) } V_{GS2} = V_{GS3} = 2.76 \text{ V}$$

$$I_{D4} = K_{n4} (V_{GS4} - V_{TN})^2 = K_{n3} (V_{GS3} - V_{TN})^2$$

$$= 100 \times 10^{-6} (2.76 - 1)^2 = 0.31 \text{ mA}$$

$$28. \text{ (C) } V_{GS} = 4.2 \text{ V}, \quad V_{DS} = 0.1 \text{ V}$$

$V_{DS} < V_{GS} - V_{TN}$, Thus transistor is in non saturation.

$$I_D = \frac{5 - 0.1}{10 \text{ k}} = 0.49 \text{ mA}$$

$$I_D = \frac{k'_n}{2} \frac{W}{L} \{2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2\}$$