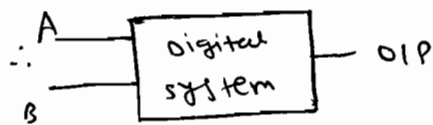


★ Don't Care Condition:

→ In a digital system for a non-occurring i/p, the o/p can be considered as either 0 (or) 1 during its simplification and it is called the don't Care Condition.

$$F_{A(B)} = \sum m(0, 2) + d(3)$$




AB	F
00	1
01	0
10	1
11	1/0

← don't care condition.

Ex-1 Design BCD to 9's Comp. of BCD Code converter.

Ans:

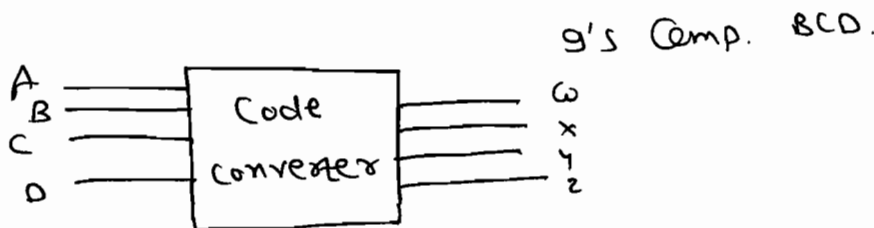

0000
⋮
1001

Don't care { 1011 → x
⋮
1111 → x

	BCD				g's Comp. of BCD			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	1	0	0	1
1	0	0	0	1	1	0	0	0
2	0	0	1	0	0	1	1	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	0	1
5	0	1	0	1	0	1	0	0
6	0	1	1	0	0	1	0	1
7	0	1	1	1	0	0	1	0
8	1	0	0	0	0	0	1	0
9	1	0	0	1	0	0	0	1

(i) for $\underline{W}$:

	CD			
AB	00	01	11	10
00	1	1		
01				
11				
10				

$$W = \bar{A} \bar{B} \bar{C}$$

(ii) for $\underline{X}$:

$$X = \sum m(2, 3, 4, 5) + d(m(11, \dots, 15))$$

	CD			
AB	00	01	11	10
00			1	1
01	1	1		
11	x	x	x	x
10			x	x

$$X = B \bar{C}$$

$$(iii) Y = C$$

direct form T.T

$$(iv) Z = \bar{D}$$

direct form T.T

* NOTE:

→ The purpose of minimization is to reduce the number of logic gates and no. of inputs.

$$\text{Ex-1 (i) } F_1(A, B, C) = \sum m(0, 2, 3, 5, 7) + d(1, 6, 7).$$

$$(ii) F_2(A, B, C) = \sum m(0, 1, 2, 3, 6) + d(4, 5, 7).$$

$$\text{Find } F_3 = F_1 + F_2$$

$$F_4 = F_1 \cdot F_2.$$

$$\text{Ans: (i) } \sum m(0, 2, 3, 5) + d(1, 6, 7)$$

	BC	00	01	11	10
A					
0		1	X	1	1
1			1	X	X

$$F_1 = \bar{A} + C + B.$$

$$(ii) \sum m(0, 1, 2, 3, 6) + d(4, 5, 7).$$

	BC	00	01	11	10
A					
0		1	1	1	1
1		X	X	X	1

$$F_2 = 1.$$

$$\therefore F_3 = F_1 + F_2 = 1 + (\bar{A} + C) = 1$$

$$F_4 = F_1 \cdot F_2 = F_1 = \bar{A} + C$$

(0/0)

$1 + d = 1$	$0 \cdot d = 0$
$0 + d = d$	$1 \cdot d = d$
$d + d = d$	$d \cdot d = d$

$$F_3 = F_1 + F_2 = \sum m(0, 1, 2, 3, 5, 6) + d(4, 7)$$

$$F_4 = F_1 \cdot F_2 = \sum m(0, 2, 3) + d(1, 6, 7, 5)$$

Ex-2




$$F_1(A, B, C) = \sum m(0, 3, 5, 6) + d(2, 4, 7)$$
$$F_2(A, B, C) = \sum m(1, 2, 3, 6) + d(0, 5, 7)$$

Ans:


$$F_3 = F_1 + F_2 = \sum m(0, 1, 2, 3, 5, 6) + d(2, 4, 7)$$

$$F_4 = F_1 \cdot F_2 = \sum m(3, 6) + d(0, 2, 5, 7)$$

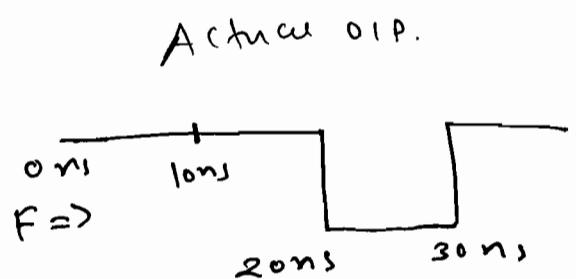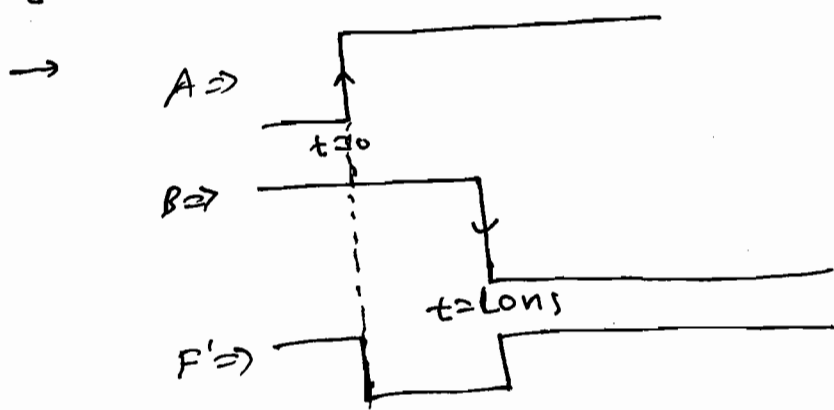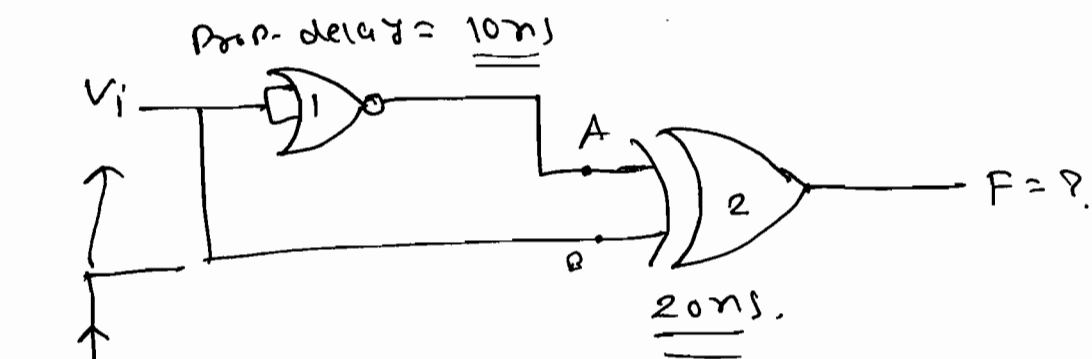Ex-3 Determine the waveform at the o/p of the following logic ckt.



Ex-2

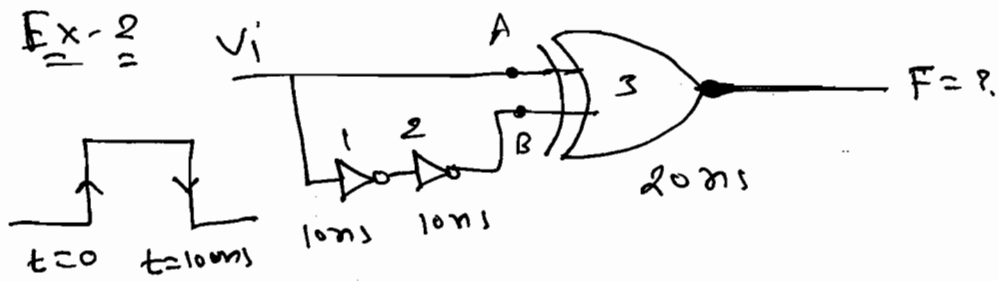 $\rightarrow A \Rightarrow$ $B \Rightarrow$ $F \Rightarrow$

Actual output
 $\downarrow$
 $F \Rightarrow$

