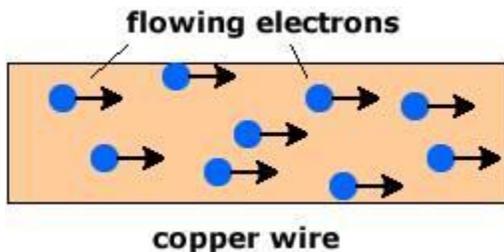


Electric Current

Improve your learning

Q. 1. Explain how electron flow causes electric current with Lorentz- Drude theory of electrons.

Answer : According to Drude and Lorentz conductors like metals contain a large number of free electrons while the positive ions are fixed in their position. In an open circuit in a conductor electrons move randomly so net charge is zero. But in closed circuit the electrons have an ordered motion, so there is a net charge crossing through any cross section of the conductor thus causes an electric current to flow.



Q. 2. How does a battery work? Explain.

Answer : i. When a conducting wire is connected to the terminals of the battery, a potential difference is created between the ends of the conductor.

ii. This potential difference sets up an electrical field throughout the conductor. The conductor contains large number of electrons.

iii. The electrons near the positive terminal of battery are attracted by it and start to move towards positive terminal.


iv. As a result, the amount of positive charge on the plate decreases.

v. So, the electric force becomes weaker than chemical force and the chemical force pulls negative ions from the positive plate (anode) and makes them move towards the negative plate (cathode).

vi. The negative terminal pushes one electron into the conductor because of stronger repulsion between the negative terminal and negative ion.

vii. Hence, the total number of electrons in the conductor remains constant during the current flow.

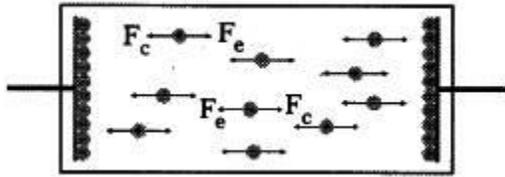viii. The above process continues till equilibrium is attained between electric force and chemical force.



Q. 3. White the difference between potential difference and emf.

Answer : Potential difference is the work done by the electric force on unit positive charge to move it through a distance l from point A to B is called potential difference between these two points. $V = W/q = f_e l/q$

Where V = potential difference;

W = work done by the electric force

q = free charge

l = distance

f_e = force exerted by the electric field

The work done by the chemical force to move unit positive charge from negative terminal to positive terminal of the battery is called electromotive force.

$EMF = W/q = Fd/q$

Q. 4. How can you verify that the resistance of a conductor is temperature dependent?

Answer : a. A bulb was taken and its resistance was measured using a multimeter in open circuit.

b. The bulb is connected to a circuit and switch is put on.

c. The bulb glows and after few minutes it gets heated up.

d. Again the resistance of the bulb is measured using a multimeter.

e. Value of resistance is found to be more in the second case than in the first case.

f. As the temperature of the filament in bulb increases the resistance of bulb also increases.

Thus we can say resistance of a conductor is temperature dependent.

Q. 5. What do you mean by electric shock? Explain how it takes place.

Answer : When we touch a live wire of 240 V some amount of current flows through our body which disturbs the functioning of organs inside our body. This disturbance which is caused inside our body is felt like an electric shock.

When a potential difference exists between one part of the body and another part an electric shock is experienced. The resistance of body is not uniform throughout. When current flows through our body it chooses a path which offers low resistance. It can prove fatal if more amount of current passes through our body.

Q. 6. Derive $R = \rho l/A$.

Answer : Resistance of a conductor R is directly proportional to its length L at constant temperature and cross-sectional area

$$R \propto L \text{ ----equation 1}$$

Resistance R of a conductor is inversely proportional to its cross-sectional area A at constant temperature and length.

$$R \propto \frac{1}{A} \text{ ----- equation 2}$$

Combining equation 1 and 2 we get-

$$R \propto \frac{L}{A}$$


So

$$R = \frac{\rho l}{A}$$

Where ρ is proportionality constant and is called specific resistance or resistivity.

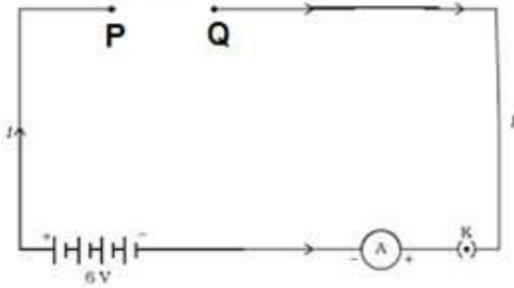Q. 7. How do you verify that resistance of a conductor is proportional to the length of the conductor for constant cross-section area and temperature?


Answer : A circuit is prepared by using a cell, key, ammeter as shown in below figure.



Iron wires of different lengths but same cross-sectional area were taken. Connect one wire between terminals P and Q. The ammeter reading was noted. The same procedure was repeated for other wires. We will observe that current decreases with increase in the length of wire. Resistance increases with increase in length and current decreases. Thus we can prove resistance of a conductor is proportional to the length of the conductor for constant cross-section area and temperature.

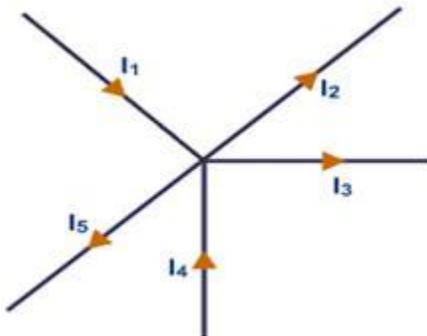Q. 8. Explain Kirchhoff's laws with examples.

Answer : Kirchhoff's junction law states that at any junction point in a circuit where the current can divide the sum of currents into the junction is equal to the sum of currents leaving the junction.



Here I_1, I_4 are currents into the junction whereas I_2, I_3, I_5 are currents out of a junction.
So $I_1 + I_4 = I_2 + I_3 + I_5$

Kirchhoff's loop law- The algebraic sum of increases and decreases in potential difference across various components of a closed circuit loop must be zero.

For loop ACDBA

$$-V_2 + I_2R_2 - I_1R_1 + V_1 = 0$$

For loop EFDCE

$$-(I_1 + I_2) R_3 - I_2R_2 + V_2 = 0$$

Q. 9. What is a value of 1 KWH in Joules?

Answer : 1 KWH = 1 KW x 1 hour

= 1000 W x 60 x 60 sec

= 36 x 10⁵ W.sec

So 1KWH = 3.6 x 10⁶ joules

Q. 10. Explain overloading of the household circuit.


Answer : In our house, the live wires entering our house meter have a potential difference of 240 V and minimum-maximum limit of current drawn from mains is 5-20 A. if the current drawn exceeds 20 A it causes overheating which may cause a fire. It happens mostly when many appliances are connected to a circuit. This is called overloading.

Q. 11. Why do we use fuses in household circuits?

Answer : Electric fuses are connected in household circuits to prevent damages due to overloading. It is a thin wire with a low melting point when current flow exceeds the limit the fuse wire gets heated up and melts. Thus circuit breaks and current flow stops. Thus appliances are saved from being damaged.

Q. 12. Deduce the expression for the equivalent resistance of three resistors connected in series.

Answer :

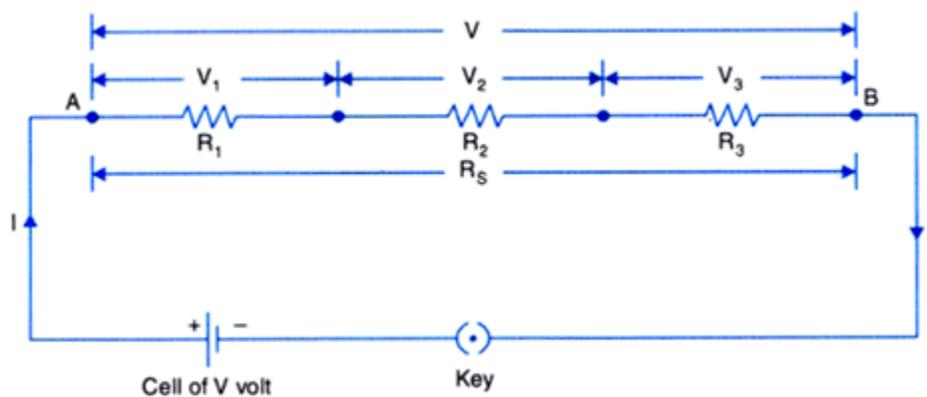

Series combination of resistors: If a number of resistors are joined end to end so that the same current flows through each of them in succession, then the resistors are said to be connected in series.

As shown in the figure, consider three resistors R_1 , R_2 , R_3 connected in series. Suppose a current I flows through the circuit when a cell of V volt is connected across the combination.

By Ohm's law, the potential differences across the three resistors will be,

$$V_1 = IR_1, V_2 = IR_2, V_3 = IR_3$$

If R_s be the equivalent resistance of the series combination, then on applying a potential difference V across it, the same current I must flow through it.

Therefore,

$$V = IR_s$$

But $V = V_1 + V_2 + V_3$


$$\therefore IR_s = IR_1 + IR_2 + IR_3$$

i.e., $IR_s = I(R_1 + R_2 + R_3)$

$$R_s = R_1 + R_2 + R_3$$

Q. 13. Deduce the expression for the equivalent resistance of three resistors connected in parallel.

Answer :

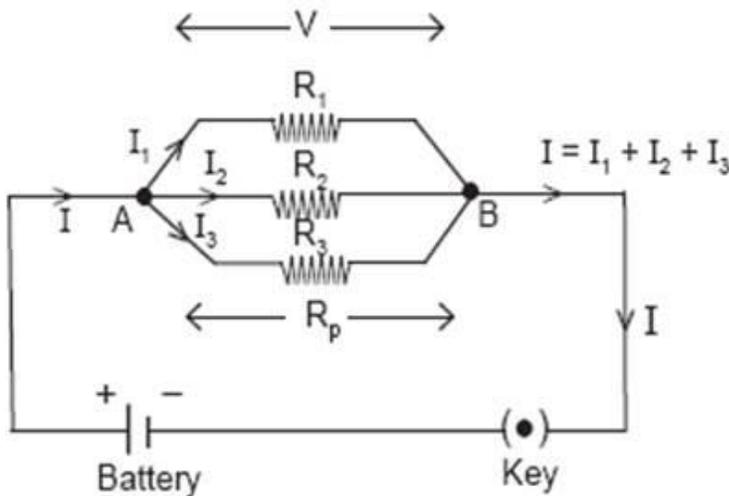

The parallel combination of resistors: If a number of resistors are connected in between two common points so that each of them provides a separate path for current, then they are said to be connected in parallel.

As shown in the figure, consider three resistors R_1 , R_2 , R_3 connected in parallel.

Suppose a current I flows through the circuit when a cell of voltage V is connected across the combination. The current I at point A is divided into three parts I_1 , I_2 , I_3 through the resistors R_1 , R_2 , R_3 respectively. These three parts recombine at point B to give the same current I .

$$\therefore I = I_1 + I_2 + I_3$$

As all the three resistors have been connected between the same two points A and B, voltage V across each of them is same. By Ohm's law,

$$I_1 = \frac{V}{R_1} \quad I_2 = \frac{V}{R_2} \quad I_3 = \frac{V}{R_3}$$

If R_p be the equivalent resistance of parallel combination, then,

$$I = \frac{V}{R_p}$$

$$\text{But } I = I_1 + I_2 + I_3$$

$$\therefore \frac{V}{R_p} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\text{or } \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Q. 14. Silver is a better conductor of electricity than copper. Why do we use copper wire for conduction of electricity?

Answer : Though silver is the best conductor of electricity it is very expensive so we use copper wire for conduction of electricity. Copper is also more readily available and cheaper, affordable as compared to silver so we use copper wire instead of silver wires for conduction of electricity.

Q. 15. Two bulbs have ratings 100 W, 220V and 60 W, 220 V. Which one has the greater resistance?

Answer :

$$\text{We know } P = \frac{V^2}{R}$$

$$\text{So } R = \frac{V^2}{P}$$

First bulb

$$R = \frac{220 \times 220}{100} = 484 \text{ ohm}$$

Second bulb

$$R = \frac{220 \times 220}{60} = 806.66 \text{ ohm}$$

So second bulb with 60 W, 220 V has greater resistance.

Q. 16. Why don't we use series arrangement of electrical appliances like bulb, Television, fan and others in domestic circuits?

Answer : The current is same throughout the circuit in series combination. So we cannot connect various electrical appliances as they draw different amount of current to operate. Secondly if one appliance connect in a series circuit fails other appliances will also not work as circuit will break. So we prefer parallel arrangement of electrical appliances like bulb, Television, fan and others in domestic circuits.

Q. 17. A wire of length 1m and radius 0.1 mm has a resistance of 100Ω. Find the resistivity of the material.

Answer :

Given - $R = 100 \text{ ohm}$;

$l = 1 \text{ m}$

$r = 0.1 \text{ mm} = 0.0001 \text{ m}$

To find resistivity = ?

We know $R = \rho l/A$

$$\rho = \frac{R \times A}{l}$$

where A = cross sectional area

$$A = \pi r^2$$

$$A = \frac{22}{7} \times 0.0001 \times 0.0001$$

$$A = 0.00000022/7 \text{ m}^2$$

$$\rho = \frac{100 \times 0.00000022}{7 \times 1}$$

Resistivity = 3.142×10^{-6} ohm.m

Q. 18. Why do we consider tungsten as a suitable material for making the filament of a bulb?

Answer :

Tungsten has high resistance and high melting point. So when the filament will glow it can withstand high temperature and emits light without getting melted. So tungsten is considered as a suitable material for making the filament of a bulb.

Q. 19. Are the head lights of a car connected in series or parallel? Why?

Answer : The head lights of the car are connected in parallel so that if one does not work other will continue to work. If one of the lights get fused then other will work without causing any difficulty.

Q. 20. Why should we connect electrical appliances in parallel in a household circuit? What happens if they are connected in series?

Answer : We should connect electrical appliances in parallel so that each appliance would get full voltage. If one appliance is faulty, other appliance will continue working. Each appliance will get the desired current according to their resistance.

If they will be connected in a series resistance will be more so the current flow will decrease. The same amount of current will flow through every appliance which is not required. All appliances should have to use simultaneously even though we do not need them. We cannot use independent switches for individual appliances.


Q. 21. Suppose that you have three resistors each of value $30\ \Omega$. How many resistors can you obtain by various combinations of these three resistors? Draw diagrams in support of your predictions.

Answer :


We can connect all three in series.




We can connect all three in parallel.

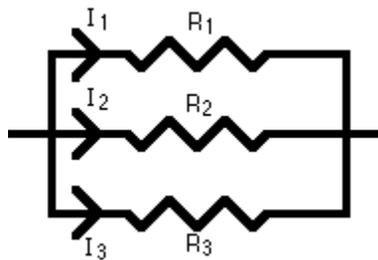

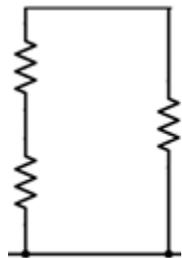We can connect two in series and one parallel to them.



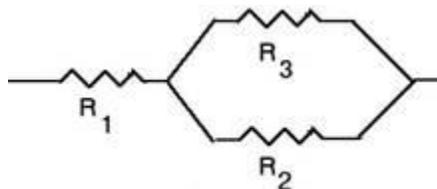We can connect two in parallel and one in series with them.



Q. 22. State Ohm's law. Suggest an experiment to verify it and explain the procedure.

Answer :

Ohm's law:

The current through a conductor element is proportional to the potential difference applied between its ends provided the temperature remains constant.

$$V = IR$$


Aim: To show that the ratio of V/I is a constant for a conductor.

Materials required: 5 dry cells of 1.5 V each, conducting wires, an ammeter, a voltmeter, thin iron spoke of length 10 cm, LED and key.

Procedure: i) Connect a circuit as shown in the figure.

ii) Solder the conducting wires to the ends of the iron spoke and close the key.

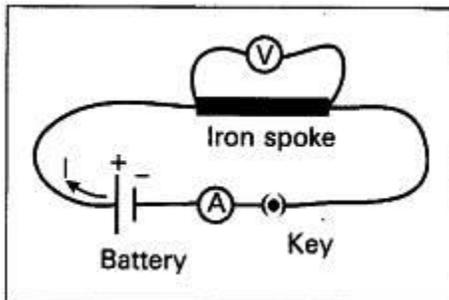iii) Note the reading of ammeter (current) and voltmeter (potential difference) and tabulate them.



iv) Now connect two cells in the circuit and note the respective readings of ammeter and voltmeter in the above table.

v) Repeat the above procedure using three cells, four cells, and five cells respectively.

vi) Record the values of potential difference and current corresponding to each case in the table.

vii) Find V/I for each set of values.

viii) We notice that V/I is constant.


ix) From this, we can conclude that potential difference between the ends of the iron spoke is directly proportional to the current passing through it. This is Ohm's law.

Q. 23 A. Take a battery and measure the potential difference. Make a circuit and measure the potential difference when the battery is connected in the circuit. Is there any difference in potential difference of battery?

Answer : When battery is not connected in a circuit its chemicals are not used up. So it gives a different reading of potential difference. But when the battery is used in a circuit the voltage slowly decreases as it is consumed, chemical energy stored in it converts to electrical energy. So we obtain a difference in potential difference before and after using a battery in the electrical circuit.

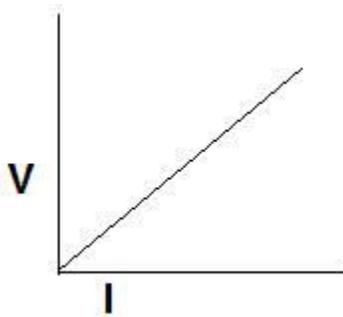
Q. 23 B. Measure the resistance of a bulb (filament) in open circuit with a multi-meter. Make a circuit with elements such as a bulb, a battery of 12V and key in series. Close the key. Then again measure the resistance of the same bulb (filament) every 30 seconds. Record the observations in a proper table. What can you conclude from the above results?

Answer : We can measure current in ammeter and voltage using voltmeter every 30 seconds. We will find the resistance by applying formula $R = V/I$ i.e. Ohm's law for every reading of ammeter and voltmeter. We will see resistance is constant. Since resistance is constant so it represents Ohm's law. If we plot a graph taking voltage in Y axis and current in X axis, a straight line will be obtained indicating that resistance is constant and it obeys Ohm's law.



Q. 24. Draw a circuit diagram for a circuit in which two resistors A and B are connected in series with a battery and a voltmeter is connected to measure the potential difference across the resistor A.

Answer :

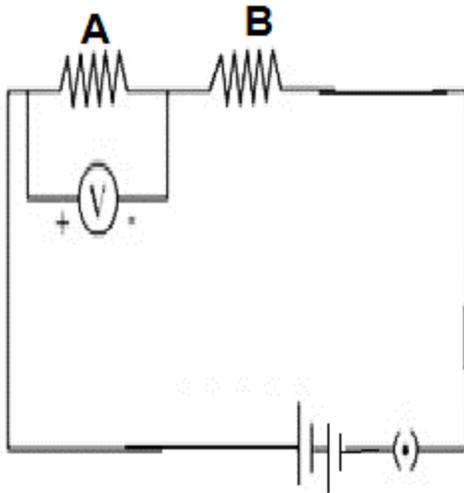

In the above circuit diagram there are two resistors A and B which are connected in series. To resistor A voltmeter is connected in parallel. A battery and a key is also connected. When key is switched on current will flow across resistors. If key is off no current flows across both the resistors.

Q. 25. How can you appreciate the role of a small fuse in house wiring circuit in preventing damage to various electrical appliances connected in the circuit?

Answer : Electric fuses are connected in household circuits to prevent damages due to overloading. It is a thin wire with low melting point, when current flow exceeds the limit the fuse wire gets heated up and melts. Thus circuit breaks and current flow stops. Thus appliances and household wiring are saved from being damaged.

Q. 26. In the figure Q-26 the potential at A is _____ when the potential at B is zero.



fig-Q26

Answer :

At point A potential difference $V = IR$

So $V = 1 \times 5 = 5 \text{ V}$

Q. 27. Observe the circuit and answer the questions given below.

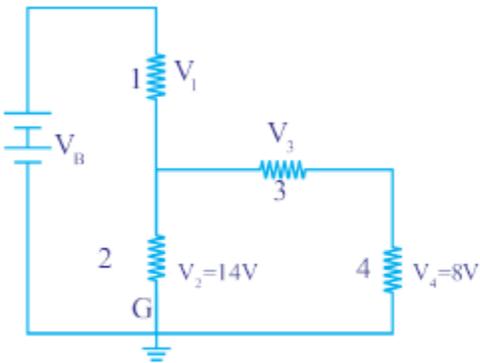


fig-Q27

- i. Are resistors 3 and 4 in series?**
- ii. Are resistors 1 and 2 in series**
- iii. Is the battery in series with any resistor?**
- iv. What is the potential drop across the resistor 3?**
- v. What is the total emf in the circuit if the potential drop across resistor 1 is 6V?**

Answer : i. Yes, resistors 3 and 4 are in series as they are connected end to end.

ii. Yes, resistors 1 and 2 are in series.

iii. Yes, the battery is in series with resistors 1 and 2.

iv. Resistors 3 and 4 are in series and combination of both are in parallel with 2 so $V_3 + V_4 = V_2$

$$V_3 + 8 = 14$$

$$V_3 = 6 \text{ V}$$

So potential drop across resistor 3 is 6 V

v. Total emf = $14 + 6 = 20 \text{ V}$

Q. 28. If the resistance of your body is 100000Ω that would be the current that flows in your body when you touch the terminals of a 12V battery?

Answer : Given $R = 100000 \text{ ohm}$

$$V = 12 \text{ V}$$

To find I

We know $V = IR$

$$\text{So } I = V/R$$

$$I = 12/100000$$

$$I = 0.00012 \text{ A}$$

Q. 29. A uniform wire of resistance 100 Ω melted and recast into wire of length doubles that of the original. What would be the resistance of the new wire formed?

Answer : Given R of original wire = 100 ohm

When length is l, R = 100 ohm

When length is 2l, R' = ?

We know $R = \rho l/A$

$$R' = \rho 2l/A$$

$$R' = 2 \rho l/A$$

$$R' = 2R \text{ [since } \rho l/A = R \text{]}$$

$$\text{So } R' = 2 \times 100$$

$$R' = 200 \text{ ohm}$$

Q. 30. A house has 3 tube lights, two fans and a Television. Each tube light draws 40W. The fan draws 80W and the Television draws 60W. On the average, all the tube lights are kept on for five hours, two fans for 12 hours and the television for five hours every day. Find the cost of electric energy used in 30 days at the rate of Rs. 3.00 per Kwh.

Answer : 1 tube light consume power = 40 W

So 3 tube lights will consume = $3 \times 40 = 120 \text{ W}$

They are kept on for 5 hours so energy consumed = $120 \times 5 = 600 \text{ Wh}$

1 fan consume power = 80 W

2 fans will consume = $80 \times 2 = 160 \text{ W}$

They work for 12 hours, so energy consumed = $160 \times 12 = 1920 \text{ Wh}$

Television consumes power = 60 W

It works for 5 hours, so energy consumed = $60 \times 5 = 300$ Wh

Total energy consumed in 1 day = $600 + 1920 + 300 = 2820$ Wh = 2.820 Kwh

Consumption for energy in 30 days = 30×2.820 KWh

Cost is Rs 3 for 1 kWh

So total amount = $3 \times 30 \times 2.820 =$ Rs 253.80