







SR. PHYSICS

89.	A cell of emf2V delivers current equal to 20% of	99.	Twenty four cells each of emf 1.5V and internal
	the maximum current it can produce through a		resistance 0.5 ohms are to be connected to a 3
	resistance 4Ω . Its internal resistance is		ohm resistance. For maximum current through this
	1) 0.1Ω 2) 1Ω 3) 0.5Ω 4) 1.5Ω		resistance what will be the number of rows and
90.	A battery of emf 12V is connected to an external		number of columns that you connect these cells.
10.	resistance of 20_{O} and it is found a potential		1) 12 cells in series 2 rows in parallel
	difference of 10V The internal resistance of		2) 8 cells in series 3 rows in parallel
	hattery is		3) 4 cells in series 6 rows in parallel
	$\begin{array}{c} 1 \\ 1 \\ 1 \\ 1 \\ 1 \\ 1 \\ 2 \\ 1 \\ 2 \\ 1 \\ 2 \\ 2$		4) 6 cells in series 4 rows in parallel
01	$\frac{1}{2} \frac{1}{2} \frac{1}$		KIRCHHOFF'S LAWS - WHEATSTONE
91.	A battery of four cells in series each naving an emi		BRIDGE
	of 1.5 V and internal resistance 1 $(\underline{0})$ are connected	100.	A,B,C and D are four coils of wires of 2, 2, 2 and
	in series with an ammeter, a coil of resistance 2Ω		3 ohm resistances respectively and are arranged
	and a filament lamp. If the ammeter reads $0.5A$,		to form a Wheatstone bridge. The resistance which
	the resistance of the filment lamp is		the coil 'D' must be shunted in order that the bridge
	$1)4_{\Omega} 2)6_{\Omega} 3)2_{\Omega} 4)12_{\Omega}$		may be balanced is.
92.	A battery has six cells in series. Each has an emf		1) 4_{Ω} 2) 6_{Ω} 3) 3_{Ω} 4) 8_{Ω}
	1.5V and internal resistance 1 ohm. If an external	101.	In a Wheatstone bridge the four arms have each
	load of 24_{Ω} is connected to it. The potential		resistance of 50 ohm. The Galvanometer current
	drop across the load is		is.
	1) 7.2V 2) 0.3V 3) 6.8V 4) 0.4V		1) Zero 2) 1A 3) 2A 4) 1.8A
93.	A battery has four cells in parallel each has an emf	102.	In a balanced Wheatstone bridge, a cell of emf
	1.5V and internal resistance 0.8 ohm. The current		2 volt is connected between the ends of the
	delivered by it to a load of 2.8 ohm. is		diagonal, AC. What will be the pontential
	1) 0.2A 2) 0.4A 3) 0.5A 4) 0.6A		difference between the ends of the diagonal B and
94.	While connecting 6 cells in a battery in series, in a		D.
	tape recorder, by mistake one cell is connected		1) Zero 2) 2V 3) 1V 4) 4V
	with reverse polarity. If the effective resistance of	103.	The resistance between A and B is
	load is 24 ohm and internal resistance of each		
	cell is one ohm and emf 1.5V, the current		1 Ω <u>3</u> Ω
	devlivered by the battery is		50 × ···
	1) 0.1A 2) 0.2A 3) 0.3A 4) 0.4A		A ma B
95.	The internal resistance of a cell of emf 1.5V, if it		20 - 00
	can deliver a maximum current of 3 A is		288
	$1)0.5\Omega$ 2)4.5 Ω 3)2 Ω 4)1 Ω		1) $\frac{200}{56}\Omega$ 2) 12Ω 3) $\frac{6}{3}\Omega$ 4) $\frac{9}{4}\Omega$
96.	When a battery of internal resistance 0.5 ohm is	104	The resistance between A and D is
	connected to a thick copper slab a current of 12A.	104.	The resistance between A and D is
	passes through it. The emf of the cell is		4Ω 2Ω
	1) 6V 2) 24V 3) 12V 4) 4V		
97.	When a resistor of 2α is connected across the		ີ §2Ω _{2Q} § 8Ω § 2Ω
· · ·	terminals of a battery a current of 2A is found to		
	flow. When a second resistor of 8° is connected		4Ω B
	in series with the first. the current is reduced to 1 A		1) 8 0 2) 4 0 3) 3.75 0 4) 2 0
	The emf and internal resistance of the battery is	105	If each resistance in the net work shown in figure
	1) 12V 40 2) 10V 20	105.	is 10 o The resistance between A and B is
	3) 16V 60 $4) 16V 40$		is 10(2). The resistance between A and D is
98	Five cells of emf 1 5V and internal resistance 0.2		
20.	ohm are connected in series. The maximum		
	current that can be delivered is		
	(1)7.5A (2) 1.5A (3) 4A (4) 2A		
SP F		7	

SR. PHYSICS

CURRENT ELECRTRYCITY

