

NETWORKS TEST 4


Number of Questions: 25

Time: 60 min.

Directions for questions 1 to 25: Select the correct alternative from the given choices.


1. Calculate the average power absorbed by an impedance $Z = (25 - j50) \Omega$, when a voltage $V = 120^\circ \angle 0^\circ V$ is applied across it.
 (A) 29W (B) 32W
 (C) 115.2W (D) None

2. Consider the circuit shown in figure

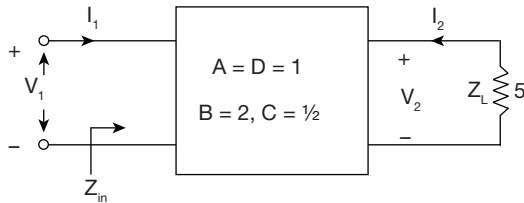

The input impedance Z_{in} is _____.

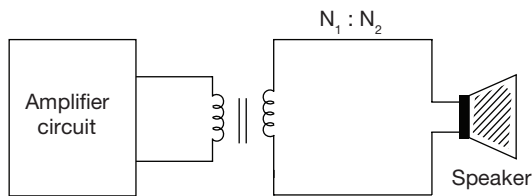
- (A) 3.5 Ω (B) 2 Ω
 (C) 7 Ω (D) 5 Ω
3. The ideal transformer in figure is used to match the amplifier circuit to the loud speaker to achieve maximum power transfer.



If the output impedance of the amplifier is 192 Ω and the internal impedance of the speaker is 48 Ω . Then the required turns ratio ($N_1 : N_2$) is _____

- (A) 2 : 1 (B) 1 : 2
 (C) 1 : 3 (D) 1 : 4
4. The coefficient of coupling for two coils having $L_1 = 2H$, $L_2 = 8H$ and $M = 2H$ is
 (A) 2 (B) 0.25
 (C) 4 (D) 0.5


5.

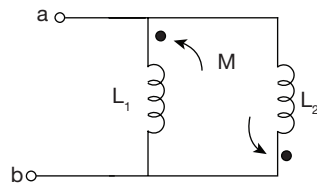

Two coils are mutually coupled with $L_1 = 10H$ and $L_2 = 40H$ and $k = 0.5$. Then the maximum possible equivalent inductance in between the terminals 'a' and 'b' is _____

- (A) 30H (B) 4.28H
 (C) 5H (D) 8H

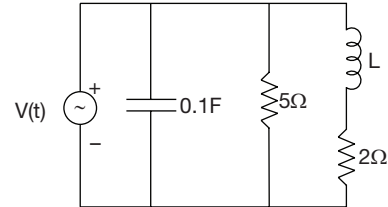
6. Consider the parallel RLC circuit shown in below.



If resonant frequency $\omega_o = 2$ rad/sec, then the value of L is _____

- (A) 0.5H (B) 2H
 (C) A and B (D) 4H

7. Consider the graph shown in below.

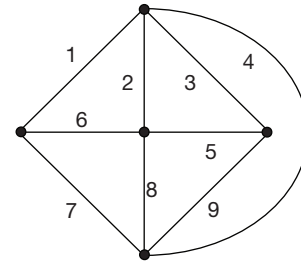


Match List – I with List – II:

List – I		List – II	
P	Links	a	2, 5, 6, 8
Q	f-loops	b	1, 4, 5, 9
R	twigs	c	1, 2, 3, 4
S	f-cut set	d	2, 3, 6, 7, 8
		e	3, 4, 9

- (A) P – d, Q – e, R – c, S – a
 (B) P – c, Q – d, R – a, S – e
 (C) P – c, Q – d, R – b, S – e
 (D) P – d, Q – e, R – b, S – a

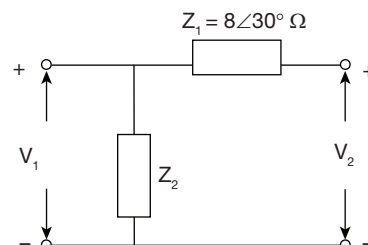8. Two networks are connected in cascade as shown in the figure, with the usual notations the equivalent A , B , C and D constants are obtained. Given that $D = 3 \angle 0^\circ$, the value of Z_2 is _____.




- (A) $0.25\angle-30^\circ \Omega$ (B) $2\angle-30^\circ \Omega$
 (C) $4\angle30^\circ \Omega$ (D) $4\angle-30^\circ \Omega$

9. The resonant frequency of an RLC series circuit is 1.5 MHz with the resonating capacitor of 15 pF. The bandwidth is 10 kHz. Then the effective values of the resistor R is _____.

- (A) 92 Ω (B) 1.25 k Ω
 (C) 47.15 Ω (D) 4.25 k Ω


10.

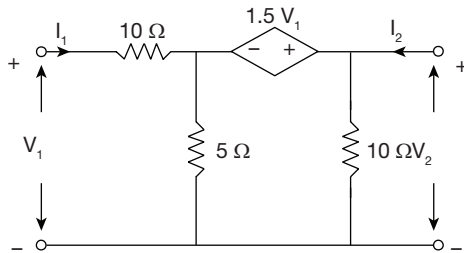

The h -parameters (h_{11} and h_{21}) of the circuit is _____

- (A) 4 Ω and -2.2 (B) 4 Ω and 5/11
 (C) 2.5 Ω and -2.2 (D) $\frac{11}{5} \Omega$ and 1.2


11. Consider the circuit shown in below

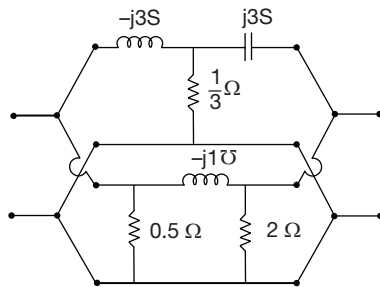

The y -parameters of the port network would be _____


- (A) $\begin{bmatrix} 5-j4 & -3+j1 \\ -3+j1 & 3.5+j2 \end{bmatrix} \bar{V}$ (B) $\begin{bmatrix} 5+j4 & 3+j1 \\ 3+j1 & 3+j2 \end{bmatrix} \bar{V}$
 (C) $\begin{bmatrix} 5-j4 & -3+j1 \\ -3-j1 & 3.5+j2 \end{bmatrix}$ (D) None of these

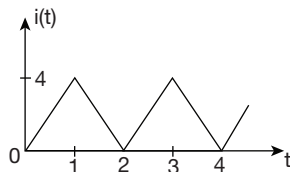12. The RMS value of the current wave form $i(t)$ is _____.



- (A) $\frac{4}{\sqrt{3}} \text{ A}$ (B) $\frac{2}{\sqrt{3}} \text{ A}$
 (C) $\frac{\sqrt{3}}{2} \text{ A}$ (D) $4\sqrt{3} \text{ A}$

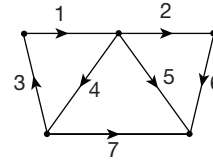
13. Determine the fundamental cutset matrix for the given directed graph.



(Consider tree branches 3, 4, 5 and 6)

- (A) $\begin{bmatrix} 1 & 0 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 1 & 0 & 1 \\ 0 & 1 & 0 & 0 & 1 & 1 & 0 \end{bmatrix}$
 (B) $\begin{bmatrix} -1 & 0 & +1 & 0 & 0 & 0 & 0 \\ -1 & 0 & 0 & +1 & 0 & 0 & -1 \\ 0 & +1 & 0 & 0 & +1 & 0 & +1 \\ 0 & -1 & 0 & 0 & 0 & +1 & 0 \end{bmatrix}$
 (C) $\begin{bmatrix} 0 & 0 & 1 & -1 & 0 & 0 & 1 \\ 1 & 0 & 0 & 1 & 0 & 0 & 1 \\ 0 & 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & -1 & 0 & 0 & 0 & 1 & 0 \end{bmatrix}$
 (D) None of these

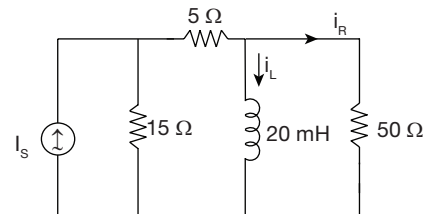
14. If $I_s = 5 \cos 500 t \text{ A}$, In the circuit shown in figure



Then the circuit $i_L(t)$ is _____

- (A) $2 \cos (500t - 26.56^\circ) \text{ A}$
 (B) $0.8 \sin (500t + 26^\circ) \text{ A}$
 (C) $5 \cos (500t + 30^\circ) \text{ A}$
 (D) None of these
15. Two magnetically uncoupled inductive coils have quality factors 10 and 15 at the chosen operating frequency. Their respective resistances are 5 Ω and 20 Ω . When connected in series, their effective Q -factor at the same operating frequency is _____.
- (A) 14 (B) 20
 (C) 6 (D) 30

16. Consider the network shown in below

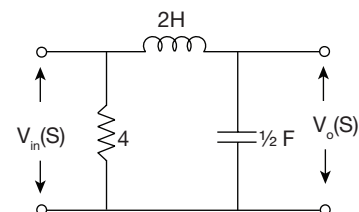


The impulse response $h(t)$ is _____

- (A) $\cos t$ (B) $\sin t$
 (C) $2 \sin 2t$ (D) $1/2 \cos 2t$


3.34 | Networks Test 4

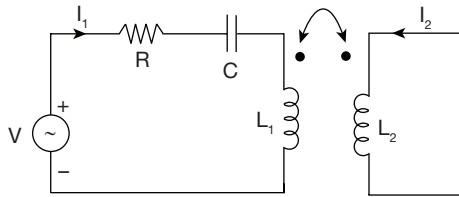17. Determine the resonance frequency of the circuit shown in figure is _____.




Consider $R = 15 \Omega$, $C = 3 \mu\text{F}$ and $L_1 = 40 \text{ mH}$, $L_2 = 10 \text{ mH}$ and $M = 5 \text{ mH}$.

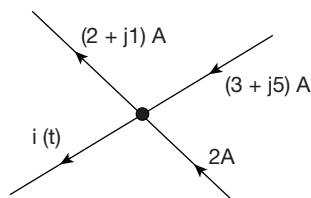- (A) 500 Hz (B) 474.5 Hz
(C) 375 Hz (D) 2.98 kHz
18. In the circuit shown below, if $f = 50 \text{ Hz}$, then the current $i(t)$ is _____




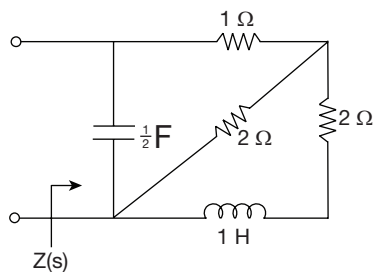- (A) $5 \cos(100t + 53.13^\circ) \text{ A}$
(B) $5 \cos(100\pi t + 53.13^\circ) \text{ A}$
(C) $25 \cos(50t + 36^\circ) \text{ A}$
(D) $2.5 \sin(100\pi t + 36^\circ) \text{ A}$
19. The current through voltage across the 150 mF capacitor is given by $I_c(s) = \frac{2s+3}{(s+2)}$.
The steady state voltage across capacitor is _____
- (A) 0 (B) 10V
(C) ∞ (D) 6.7V
20. Consider the circuit shown in below.




The value of $Z(s)$ is _____

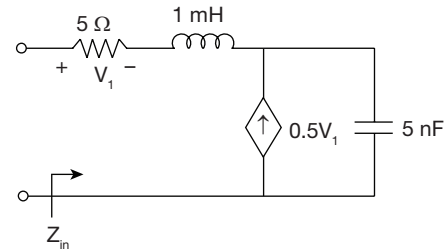- (A) $\frac{3(8+2s)}{3s^2+10s+8}$ (B) $\frac{(8+3s)}{s^2+10s+8}$
(C) $\frac{2(8+3s)}{3s^2+10s+8}$ (D) $\frac{2(8+3s)}{s^2+10s+8}$
21. For the circuit shown below the resonant frequency f_o is _____.




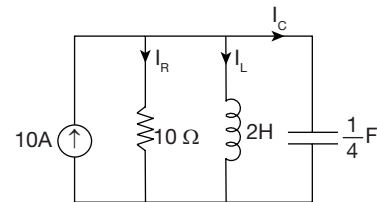- (A) 125 kHz (B) 150 kHz
(C) 830 kHz (D) 133 kHz
- 22.




At resonance I_C and I_L would be

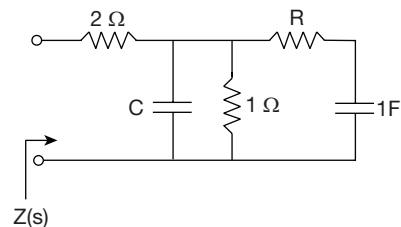- (A) $25\sqrt{2} \angle 90^\circ \text{ A}$, $25\sqrt{2} \angle -90^\circ \text{ A}$
(B) $2\sqrt{2} \angle 90^\circ \text{ A}$, $2\sqrt{2} \angle -90^\circ \text{ A}$
(C) $25\sqrt{2} \angle -90^\circ \text{ A}$, $25\sqrt{2} \angle 90^\circ \text{ A}$
(D) $j2\sqrt{2} \text{ A}$, $-j2\sqrt{2} \text{ A}$
23. The network realization of RC impedance function, $Z(s) = \frac{2s^2+7s+3}{s^2+3s+1}$, is as shown below what are the values of R and C ?




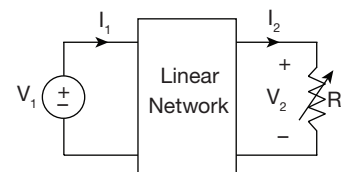- (A) 1 ohm, 1F (B) 2 ohm, 0.5F
(C) 1 ohm, 0.5F (D) 2 ohm, 2F
24. In a linear network, a 1Ω resistor consumes a power of 4 W, when voltage source of 4 V is applied to the circuit and 16 W when the voltage source is replaced by an 8 V source the power consumed by the 1Ω resistor when 10 V is applied will be



- (A) 25W (B) 20W
(C) 18W (D) 30W

25. Consider the following circuit.

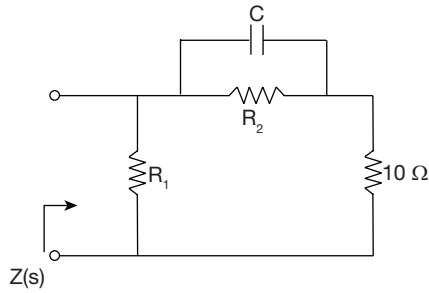

In the above circuit $Z(s) = 6$ as $s \rightarrow \infty$ and $Z(s) = 5 \Omega$ as $s \rightarrow 0$. What are the values of R_1 and R_2 ?

- (A) 5Ω and 10Ω
 (B) 10Ω and 5Ω
 (C) 15Ω and 5Ω
 (D) 10Ω and 7.5Ω

ANSWER KEYS

- | | | | | | | | | | |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 1. C | 2. B | 3. A | 4. D | 5. B | 6. C | 7. D | 8. C | 9. C | 10. A |
| 11. A | 12. A | 13. B | 14. A | 15. A | 16. B | 17. B | 18. B | 19. B | 20. C |
| 21. D | 22. A | 23. A | 24. A | 25. B | | | | | |

HINTS AND EXPLANATIONS

1. $P = V_{rms} \cdot I_{rms} \cdot \cos \phi$

$$P = \frac{1}{2} \times V_m \cdot I_m \cdot \cos(\theta_v - \theta_i)$$

$$I_{rms} = \frac{V}{Z} = \frac{120 \angle 0^\circ}{25(1 - j2)} = 2.146 \angle 63.43^\circ \text{ Amp}$$

$$P = \frac{1}{2} \times 120 \times 2.146 \times 2 \cos(0 - 63.43^\circ) \text{ Watts}$$

$$= 115.2 \text{ Watts}$$

Choice (C)

2. We know T -parameters are defined in terms of

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$


$$Z_{in} = \frac{V_1}{I_1} = \frac{AV_2 - BI_2}{CV_2 - DI_2}$$

$$\text{But } V_2 = -Z_L I_2$$

$$\therefore Z_{in} = \frac{AZ_L + B}{CZ_L + D} = \frac{5 + 2}{2.5 + 1} = \frac{7}{3.5} = 2 \Omega$$

Choice (B)

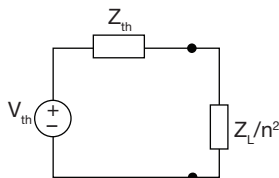3. Replace the amplifier circuit with the thevenin's equivalent circuit.



$$\therefore Z_{th} = 192 \Omega \text{ and } \frac{Z_L}{n^2} = 48 \Omega$$

$$Z_{th} = \frac{Z_L}{n^2} \text{ for max power}$$

$$\text{Where } n = \frac{N_2}{N_1}$$

$$\text{We know } R_s = \frac{R_L}{n^2}$$

$$n^2 = \frac{48}{192} = \frac{1}{4}$$

$$N_1 : N_2 = 2:1$$

Choice (A)

4. We know

$$k = \frac{M}{\sqrt{L_1 L_2}} = \frac{2}{4} = \frac{1}{2}$$

$$k = 0.5$$

Choice (D)

$$5. M = K \sqrt{L_1 L_2}$$

$$= 0.5 \sqrt{10 \times 40} = 10 \text{ H}$$

For parallel opposing configuration

$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$

$$= \frac{400 - 100}{50 + 20} = \frac{300}{70} = 4.28 \text{ H}$$

Choice (B)

$$6. Y = 0.2 + j\omega(0.1) + \frac{1}{2 + j\omega L}$$

$$Y = 0.2 + j\omega(0.1) + \frac{2 - j\omega L}{4 + (\omega_o L)^2}$$

At resonance $\text{Im}\{Y\} = 0$

$$\omega = \omega_o$$

$$\omega_o(0.1) = \frac{\omega_o L}{4 + (\omega_o L)^2}$$

$$4 + (\omega_o L)^2 = 10 L$$

$$\text{But given } \omega_o = 2 \text{ r/s}$$

$$4 L^2 = 10 L - 4$$

$$\begin{aligned}
 2L^2 - 5L + 2 &= 0 \\
 2L^2 - 4L - L + 2 &= 0 \\
 2L\{L - 2\} - 1\{L - 2\} &= 0 \\
 L = 2 \text{ and } L = \frac{1}{2}
 \end{aligned}$$

Choice (C)

7. Tree branches are called twigs

$$\therefore \text{no. of twigs} = N - 1$$

$$\text{Here } N = 5$$

$$\therefore \text{Twigs} = 4$$

Select the twigs, without forming closed loop.

Co-tree branches are called links

$$\therefore \text{Total branches} = \text{Twigs} + \text{links}$$

f -loops: It consists only one link and one or more than one twigs

f -cut set: It is a removal of one tree branch at a time.

It consists only one tree branch and others links.

Choice (D)

$$8. [T] = \begin{bmatrix} 1 & Z_1 \\ \frac{1}{Z_2} & 1 + \frac{Z_1}{Z_2} \end{bmatrix}$$

$$\therefore D = 1 + \frac{Z_1}{Z_2}$$

$$2 = \frac{Z_1}{Z_2}$$

$$Z_2 = \frac{Z_1}{2} = 4 \angle 30^\circ \Omega$$

Choice (C)

$$9. f_o = 1.5 \text{ MHz}$$

$$BW = 10 \text{ kHz}$$

$$Q = \frac{f_o}{BW} = \frac{1.5 \times 10^6}{10^4} = 150$$

$$\text{We know } Q = \frac{|X_c|}{R}$$

$$R = \frac{1}{2\pi f_o C \times Q}$$

$$R = \frac{10^{12}}{2\pi \times 1.5 \times 10^6 \times 15 \times 150}$$

$$R = \frac{10^6}{2\pi \times 1.5 \times 15 \times 150}$$

$$R = 47.15 \Omega$$

Choice (C)


10. h-parameters are defined in terms of

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$\text{Let } V_2 = 0$$

$$h_{11} = \frac{V_1}{I_1}$$

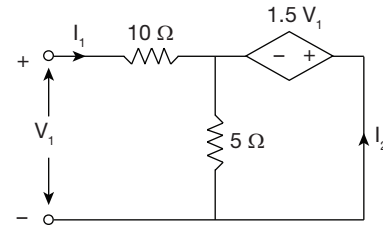

$$V_1 = 10 I_1 - 1.5 V_1$$

$$2.5 V_1 = 10 I_1$$

$$V_1 / I_1 = 4 \Omega$$

$$I_1 + I_2 = \frac{-1.5 V_1}{5}$$

$$\text{But } V_1 = 4 I_1$$

$$I_1 + I_2 = -0.3 \times 4 I_1$$


$$2.2 I_1 = -I_2$$

$$\frac{I_2}{I_1} = -2.2$$

Choice (A)

11. Two networks N_1 and N_2 are connected in parallel

$$\therefore y = [Y_1] + [Y_2]$$

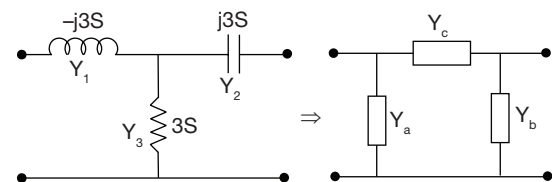

$y - \Delta$ conversion

$$y_a = y_1 + y_3 + \frac{y_1 y_3}{y_2}$$

$$= (-j3 + 3) + \frac{(-j3)(3)}{j3} = -j3 \text{ S}$$

$$Y_b = Y_2 + Y_3 + \frac{y_2 y_3}{y_1}$$


$$= (j3 + 3) + \frac{(j3)(3)}{-j3} = j3 \text{ S}$$

$$y_c = Y_1 + Y_2 + \frac{y_1 y_2}{y_3} = 0 + 3 \text{ S}$$

$$y_c = 3 \text{ S}$$

$$[Y]_1 = \begin{bmatrix} y_a + y_c & -y_c \\ -y_c & y_b + y_c \end{bmatrix} = \begin{bmatrix} (3 - j3) & -3 \\ -3 & 3 + j3 \end{bmatrix} \text{ } \Omega$$

and second network N_2 is

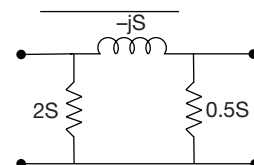

$$[Y]_2 = \begin{bmatrix} 2-j1 & j1 \\ j1 & 0.5-j1 \end{bmatrix} \text{ } \mathcal{U}$$


$$[Y] = [y_1] + [y_2]$$

$$= \begin{bmatrix} 3+2-j3-j1 & -3+j1 \\ -3+j1 & 3+0.5+j3-j1 \end{bmatrix}$$

$$= \begin{bmatrix} 5-j4 & -3+j1 \\ -3+j1 & 3.5+j2 \end{bmatrix} \text{ } \mathcal{U}$$

$$12. I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

Consider one period of $i(t)$
 $T = 2$

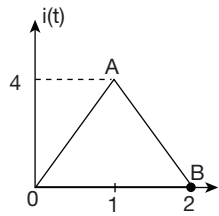

$0(0,0) A(1,4)$

$$i(t) = \left(\frac{4-0}{1-0} \right) (t-0)$$

$i(t) = 4t$; for $0 < t < 1$

for A to B straight line

$A(1,4) B(2,0)$

$$i(t) - 4 = \left(\frac{0-4}{2-1} \right) (t-1)$$

$i(t) = -4t + 8$; $1 < t < 2$

$$\therefore I_{rms}^2 = \frac{1}{2} \left[\int_0^1 i^2(t) dt + \int_1^2 i^2(t) dt \right]$$

$$= \frac{1}{2} \left[\int_0^1 16t^2 dt + \int_1^2 (-4t+8)^2 dt \right]$$

$$= \frac{1}{2} \times \frac{16}{3} [1] + \frac{16}{2} \left[\int_1^2 (t^2 - 4t + 4) dt \right]$$

$$I_{rms}^2 = 2.666 + 8 \left[\frac{t^3}{3} - 2t^2 + 4t \right]_1^2$$

$$= 2.666 + 8 \left[\frac{7}{3} - 2(3) + 4 \right]$$


$$= \left(\frac{8}{3} + \frac{8}{3} \right) \text{ Amp}$$

$$I_{rms}^2 = \frac{16}{3}$$

$$I_{rms} = \frac{4}{\sqrt{3}} \text{ Amp}$$

Choice (A)

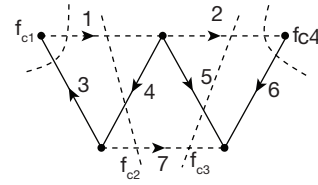13. Number of cut sets = Number of twigs = 4



$\therefore$ Cut set nothing but removal of tree branch.

Consider the twig direction is +ve

$$f_{c1} \rightarrow 1, 3$$

$$f_{c2} \rightarrow 1, 4, 7$$


$$f_{c3} \rightarrow 2, 5, 7$$

$$f_{c4} \rightarrow 2, 6$$

	Branches						
Cut sets	1	2	3	4	5	6	7
f_{c1}	-1	0	+1	0	0	0	0
f_{c2}	-1	0	0	+1	0	0	-1
f_{c3}	0	+1	0	0	+1	0	+1
f_{c4}	0	-1	0	0	0	1	0

Choice (B)

14.

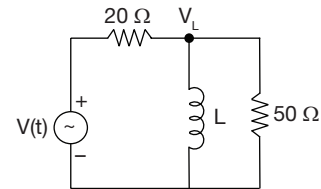

$$V(t) = 15 \text{ V} \quad i(t) = 75 \cos 500t \text{ V}$$

$$\omega = 500$$

$$\frac{V_L - V(t)}{20} + \frac{V_L}{j\omega L} + \frac{V(t)}{50} = 0$$

$$5[V_L - V(t)] + (-j10V_L) + 2V(t) = 0$$

$$5V_L - 5V(t) - j10V_L + 2V(t) = 0$$

$$V_L(5 - j10) = 3V(t)$$

$$V_L = \frac{3}{5} \frac{V(t)}{(1 - j2)}$$

$$i_L(t) = \frac{V_L}{X_L} = \frac{3}{5} \times \frac{75 \cos 500t}{(1 - j2)(j10)}$$

$$i_L(t) = \frac{4.5 \cos 500t}{(2 + j1)}$$

$$i_L(t) = 2 \cos(500t - 26.56^\circ) \text{ Amp}$$

Choice (A)

$$15. Q = \frac{X_L}{R}$$

$$q_1 = \frac{\omega L_1}{R_1}; \quad q_2 = \frac{\omega L_2}{R_2}$$

Choice (A)

If two are connected in series

$$\therefore \text{overall } Q = \frac{\omega(L_1 + L_2)}{R_1 + R_2}$$

$$Q = \frac{q_1 R_1 + q_2 R_2}{R_1 + R_2}$$

$$Q = \frac{10 \times 5 + 15 \times 20}{25}$$

$$Q = 14$$

Choice (A)

$$16. \frac{V_o(s) - V_{in}(s)}{2S} + \frac{V_o(s)}{\frac{2}{S}} = 0$$

$$V_o(s) - V_{in}(s) + S^2 V_o(s) = 0$$


$$V_o(s)[1 + S^2] = V_{in}(s)$$

$$\frac{V_o(s)}{V_{in}(s)} = \frac{1}{1 + S^2} = H(s)$$

$$h(t) = \sin t$$

Choice (B)

17.

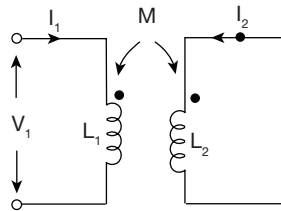

Secondary voltage $V_2 = 0$

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$0 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$\text{Sub } \frac{d}{dt} = j\omega$$

$$V_1 = j\omega L_1 I_1 + Mj\omega I_2$$

$$j\omega L_2 I_2 = -Mj\omega I_1$$

$$I_2 = \frac{-MI_1}{L_2}$$

$$V_1 = j\omega L_1 I_1 - j\omega \frac{M^2 I_1}{L_2}$$

$$V_1 = j\omega \left(L_1 - \frac{M^2}{L_2} \right) I_1$$

$$\therefore L_{eq} = L_1 - \frac{M^2}{L_2} = 37.5 \text{ mH}$$

$$\omega_o = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$

$$= \frac{1}{\sqrt{37.5 \times 10^{-3} \times 3 \times 10^{-6}}}$$

$$= \frac{10^4}{\sqrt{3.75 \times 3}} = 2.98 \times 10^3 \text{ rad/sec}$$

$$f_o = 474.5 \text{ Hz}$$

Choice (B)

$$18. i(t) + (2 + j1) = (5 + j5)$$

$$\therefore i = (3 + j4) \text{ Amp}$$

$$I = 5 \angle \tan^{-1}(4/3)$$

$$= 5 \angle 53.13^\circ \text{ Amp S}$$

$$i(t) = 5 \cos(2\pi \times 50 t + 53.13^\circ) \text{ A}$$

$$i(t) = 5 \cos(100\pi t + 53.13^\circ) \text{ Amp}$$

Choice (B)

$$19. V_C(\infty) = \lim_{s \rightarrow 0} s V_C(s)$$

$$I_C = C \frac{dV_C}{dt}$$

$$I_C(s) = sC V_C(s)$$

$$V_C(s) = \frac{1}{sC} I(s)$$

$$V_C(\infty) = \lim_{s \rightarrow 0} s \left(\frac{2s+3}{s+2} \right) \times \frac{10^3}{150}$$

$$s \rightarrow 0 = 10V$$

Choice (B)

$$20. Z(s) = \left(\frac{2}{s} \right) \parallel [1 + (2+s) \parallel 2]$$


$$= \frac{2}{s} \parallel \left[1 + \frac{4+2s}{4+s} \right] = \left(\frac{2}{s} \right) \parallel \left[\frac{8+3s}{4+s} \right]$$

$$= \frac{\left(\frac{2}{s} \right) \left(\frac{8+3s}{4+s} \right)}{\frac{2}{s} + \frac{8+3s}{4+s}} = \frac{2(8+3s)}{8+2s+8s+3s^2}$$

$$Z(s) = \frac{2(8+3s)}{3s^2 + 10s + 8}$$

Choice (C)

21.

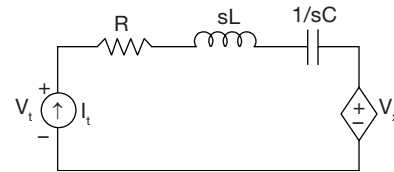

$$V_t - V_x = RI_t + sLI_t + \frac{I_t}{sC}$$

$$\text{But } V_x = 0.5V_t \times 1/sC$$

$$V_t = 5 I_t$$

$$V_x = \frac{2.5 I_t}{sC}$$

$$V_t = I_t \left[5 + sL + \frac{1}{sC} + \frac{2.5}{sC} \right]; \frac{V_t}{I_t} = Z(s)$$

$$Z(s) = 5 + j\omega 1 \times 10^{-3} - \frac{j3.5}{\omega \times 5 \times 10^{-9}}$$

at resonance image $Z(s) = 0$

$$\therefore \omega^2 = \frac{3.5}{5 \times 10^{-9} \times 10^{-3}}$$

$$\omega^2 = \frac{3.5}{5} \times 10^{12}$$

$$\omega = 836.66 \times 10^3 \text{ rad/sec}$$

$$f_o = 133.158 \text{ kHz}$$

22. At resonance $I_L + I_C = 0$

$$\therefore I_L = QI \angle -90^\circ \text{ A}$$

$$I_C = QI \angle 90^\circ \text{ A}$$

$$Q = R \sqrt{\frac{C}{L}}$$

$$Q = 10 \times \sqrt{\frac{1}{8}} = 3.53$$

$$\therefore I_L = 25\sqrt{2} \angle -90^\circ \text{ A}$$

$$I_C = 25\sqrt{2} \angle 90^\circ \text{ A}$$

23. $Z(s) = 2 + \left[\frac{1}{sC} \parallel \left\{ 1 \parallel \left(R + \frac{1}{s} \right) \right\} \right]$

$\therefore$ By comparison we can get
 $R = 1 \Omega$ and $C = 1 \text{ F}$

24. $V_1 = AV_2 + BI_2$

$$I_1 = CV_2 + DI_2$$

When $V_1 = 4 \text{ V}$ and $P = 4 \text{ W}$

$$\therefore P = I_2^2 R_L$$

$$I_2 = \sqrt{\frac{P}{R_L}} \text{ and } P = \frac{V_2^2}{R_L}$$

Choice (D)

Choice (A)

Choice (A)

$$V_2 = \sqrt{P \cdot R_L} \text{ as } R_L = 2$$

$$4 = A\sqrt{P \cdot R} + B\sqrt{\frac{P}{R}}$$

$$4 = A\sqrt{4} + B\sqrt{4}$$

$$2A + 2B = 4$$

$$A + B = 2$$

$\rightarrow$ (i)

$$8 = A\sqrt{16} + B\sqrt{16}$$

$$8 = 4A + 4B$$

$$\therefore A + B = 2$$

$$V_1 = 10$$

$$10 = 5A + 5B$$

$$\therefore V_2 = 5 \text{ and } I_2 = 5$$

$$P = I_2^2 \cdot R_L = 25 \times 1 = 25 \text{ W}$$

Choice (A)

25. If $S \rightarrow \infty \Rightarrow C = \text{short circuit}$

$$S \rightarrow 0 \Rightarrow C \rightarrow \text{open circuit}$$

$$\therefore \text{for } S \rightarrow 0$$

$$Z(s) = R_1 \parallel (R_2 + 10)$$

$$\text{For } S \rightarrow \infty$$

$$Z(s) = R_1 \parallel 10 = 5 \Omega$$

$$R_1 = 10 \Omega$$

$$10 \parallel (R_2 + 10) = 6$$

$$\frac{10 \times (R_2 + 10)}{R_2 + 20} = 6$$

$$10R_2 + 100 = 6R_2 + 140$$

$$4R_2 = 20$$

$$R_2 = 5 \Omega$$

Choice (B)