

Transistor Biasing Circuits


4

Biasing is about stabilizing I_C and V_{CE} so as to ensure that transistor remains in active region for entire range of input signal.

Fixed Bias

$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

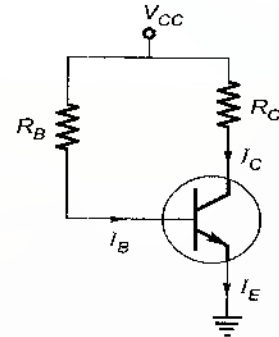


Emitter feedback bias


- Collector current I_C

$$I_C \cong \frac{V_{CC} - V_{CE}}{R_E + R_C}$$

(assuming β to be large)

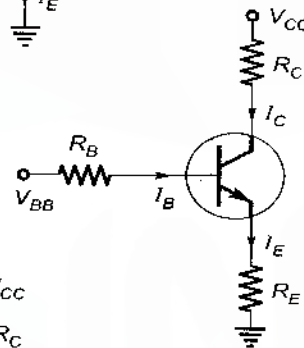

Collector-feedback bias (self bias)

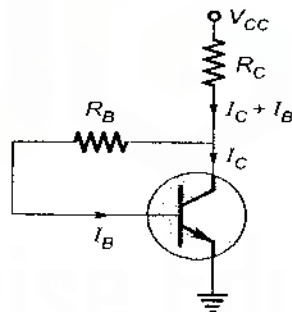

$$I_C \cong \frac{V_{CC} - V_{CE}}{R_C}$$


[Assuming β to be large or $I_B \cong 0$]

or


$$I_C = \left[\frac{V_{CC} - V_{CE}}{R_C} \right] \times \left(\frac{\beta}{\beta + 1} \right)$$

[Exact value]

Voltage Divider Bias (universal bias)

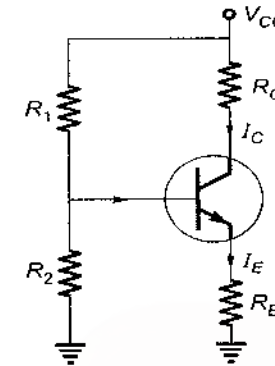

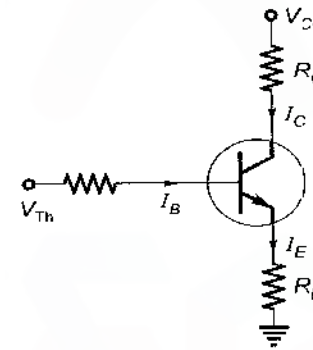- Widely used in linear circuits and is as Equivalent circuit will be \rightarrow (thevenine equivalent)



$$\text{where, } V_{Th} = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$R_{Th} = R_1 \parallel R_2$$

$$I_C \cong \frac{V_{CC} - V_{CE}}{R_C + R_E}$$

[Assuming β to be large]

$$I_E = \frac{V_{Th} - V_{BE}}{R_E + \left(\frac{R_{Th}}{\beta + 1} \right)}$$

Bias Stabilization

- Stabilization is about making the Q -point independent of changes in temperature and changes in transistor parameters.
- If I_{CO} , V_{BE} and β changes simultaneously then net change in I_C .

$$\Delta I_C = \frac{\partial I_C}{\partial I_{CO}} \Delta I_{CO} + \frac{\partial I_C}{\partial V_{BE}} \Delta V_{BE} + \frac{\partial I_C}{\partial \beta} \Delta \beta$$

where, $\frac{\partial I_C}{\partial I_{CO}} = S \rightarrow$ Current stability factor.

$\frac{\partial I_C}{\partial V_{BE}} = S' \rightarrow$ Voltage stability factor

$\frac{\partial I_C}{\partial \beta} = S_\beta$ or $S'' \rightarrow$ Amplification stability factor.

Note:

Out of three stability factor S is most significant reason being, if S is within tolerable limit then other S' and S'' are guaranteed to remain within tolerable limit.

$$S_{\text{ideal}} = 1$$

Practically S should be less than 20.

For Voltage Divider Bias Circuit

current stability factor,

$$S = \frac{(\beta + 1)(R_{Th} + R_E)}{R_{Th} + (\beta + 1)R_E}$$

Note:

R_E must be large for lesser value of S , but it also decreases the gain.

- Alternate Evaluation of S

$$S = \frac{(\beta + 1)}{1 - \beta \frac{\partial I_B}{I_C}}$$

- Condition for effective stabilization

$$S = \frac{(\beta + 1)(R_E + R_{Th})}{R_{Th} + (\beta + 1)R_E} \quad [\text{For voltage divider circuit}]$$

$$S = \frac{(\beta + 1)}{1 + \frac{\beta}{\left(1 + \frac{R_{Th}}{R_E}\right)}} \quad ; \quad \text{if } \frac{R_{Th}}{R_E} \ll 1 \quad \text{then } S \rightarrow 1$$

For Collector Feedback Bias Circuit

$$S = \frac{(1 + \beta)(R_B + R_C)}{R_B + (1 + \beta)R_C} \quad ; \quad \text{if } \frac{R_B}{R_C} \ll 1 \quad \text{then } S \rightarrow 1$$

For Fixed Bias Circuit

$$S = (\beta + 1) \rightarrow \text{very large} \rightarrow \text{highly unstable.}$$

Condition to Avoid Thermal Run Away

- Thermal resistance (θ)

$$\theta = \frac{T_J - T_A}{P_D} \quad (^\circ\text{C/Watt or } ^\circ\text{K/Watt})$$

where,

T_J = Junction temperature (collector junction)

T_A = Ambient temperature in Kelvin.

P_D = Power dissipated across collector junction.

- A transistor will be thermally stable if

$$\frac{\partial P_C}{\partial T_J} \leq \frac{\partial P_D}{\partial T_J} \leq \frac{1}{\theta} \quad \frac{\partial P_C}{\partial T_J} \rightarrow \text{Rate at which heat is released.}$$

$$\frac{\partial P_D}{\partial T_J} \rightarrow \text{Rate at which heat is dissipated.}$$

- For thermal stability $\frac{V_{CC}}{2} > V_{CE}$.

■■■■■