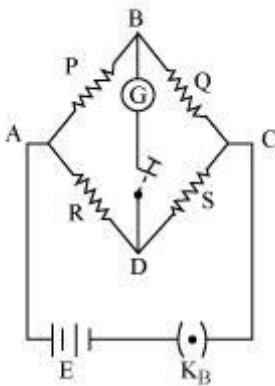


12. Current Electricity

Kirchhoff's laws:


- First law: In any electrical network, the algebraic sum of the currents, $\sum I$, meeting at a junction is always zero.
- Second law: The algebraic sum of all the potential drops and emfs along any closed path in a network is zero.

Wheatstone bridge:



$\frac{P}{Q} = \frac{R}{S}$

Metre Bridge:

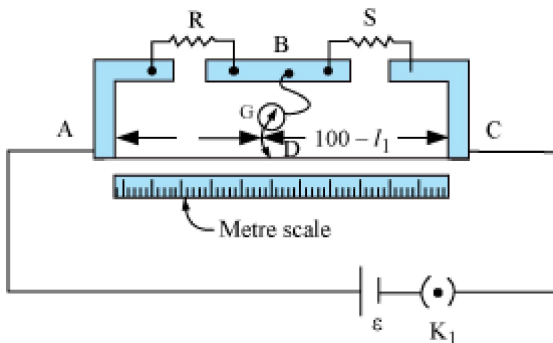

Here $\frac{R}{S} = \frac{l_1}{100 - l_1}$ therefore $R = \frac{S l_1}{100 - l_1}$

Causes of probable errors while using a metre bridge:

- Uneven thickness of the wire used in the metre bridge
- Contact resistances developed at the ends of the wire of the metre bridge
- Ends of the wire not coinciding with the 0 and 100 cm marks of a metre scale
- We can minimise the errors in a metre bridge by using wire of uniform thickness and repeating the experiment by changing the position of the unknown resistance.
- In Kelvin's method, the resistance of galvanometer is given by


$$G \text{ space equals space } R \text{ cross times open parentheses fraction numerator } l \text{ subscript } g \text{ over denominator } 100 \text{ minus } 1 \text{ subscript } g \text{ end fraction close parentheses}$$
 , where R is the resistance and l_g is the point where the galvanometer shows the same deflection as shown while the jockey was not touching the wire.

- **Potentiometer**

It works on the principle that on passing a constant current, the potential drop across any portion of the wire is directly proportional to the length of that portion.
 i.e., $V \propto l$

- **Applications of a Potentiometer**

Comparison of emfs of two cells

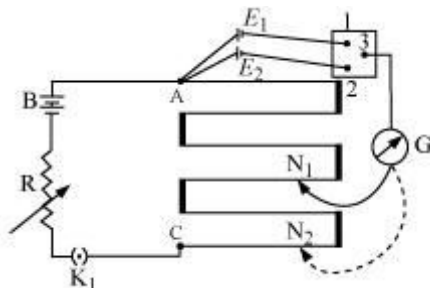


$$E_1 E_2 = l_1 l_2$$

Measurement of internal resistance of a cell

$$r = R \frac{l_1 l_2 - l_1}{l_2 - l_1}$$

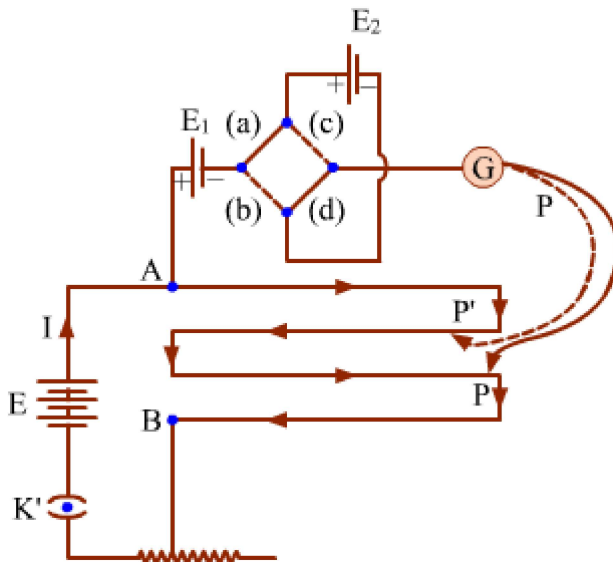Comparison of emfs using the sum and difference method



$$E_1 E_2 = L_1 + L_2 \quad L_1 - L_2$$

- **Sensitivity of Potentiometer**

The smallest potential difference that can be measured with a potentiometer is known as its sensitivity. The sensitivity of a potentiometer can be increased by decreasing its potential gradient (E/l). The potential gradient can be decreased by following ways:

- Increasing the length of potentiometer

- Decreasing the current in the potentiometer wire circuit if the wire is of fixed length
- **Precautions to be taken while using a potentiometer**
 - The potentiometer wire must be uniform.
 - The resistance of potentiometer wire should be high.
 - The emf of the battery must be greater than the emfs that are to be compared.
- **Advantages of a potentiometer**
 - It can measure the terminal potential difference as well as the emf of a cell.
 - Its accuracy can also be increased by increasing the length of the wire.
- **Disadvantages of a potentiometer**
 - It cannot directly indicate the value of the potential difference.
 - It is not portable.