

CHAPTER

1.3

METHODS OF ANALYSIS

1. $v_1 = ?$

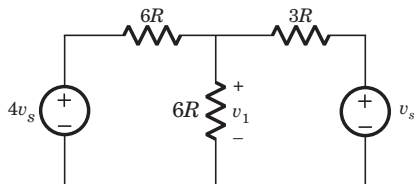


Fig. P1.3.1

(A) $0.4v_s$

(B) $1.5v_s$

(C) $0.67v_s$

(D) $2.5v_s$

2. $v_a = ?$

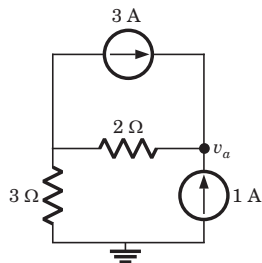


Fig. P1.3.2

(A) -11 V

(B) 11 V

(C) 3 V

(D) -3 V

3. $v_1 = ?$

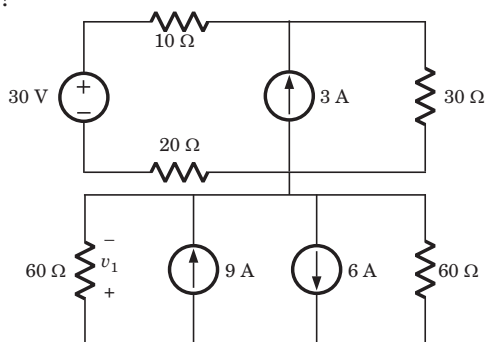


Fig. P1.3.3

(A) 120 V

(B) -120 V

(C) 90 V

(D) -90 V

4. $v_a = ?$

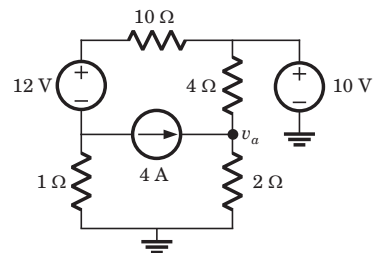


Fig. P1.3.4

(A) 4.33 V

(B) 4.09 V

(C) 8.67 V

(D) 8.18 V

5. $v_2 = ?$

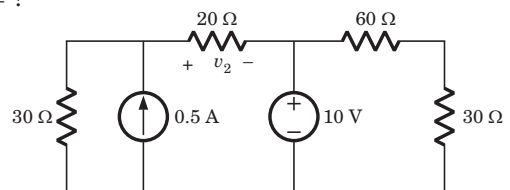


Fig. P1.3.5

(A) 0.5 V

(B) 1.0 V

(C) 1.5 V

(D) 2.0 V

6. $i_b = ?$

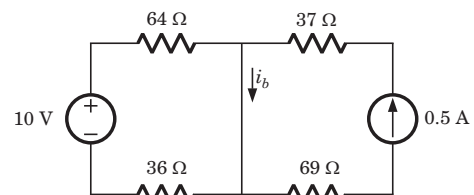


Fig. P1.3.6

(A) 0.6 A

(B) 0.5 A

(C) 0.4 A

(D) 0.3 A

7. $i_1 = ?$

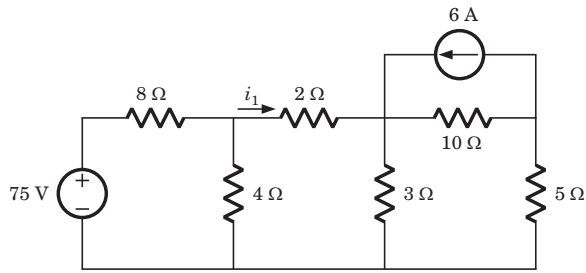


Fig. P1.3.7

- (A) 3.3 A (B) 2.1 A
(C) 1.7 A (D) 1.1 A

8. $i_1 = ?$

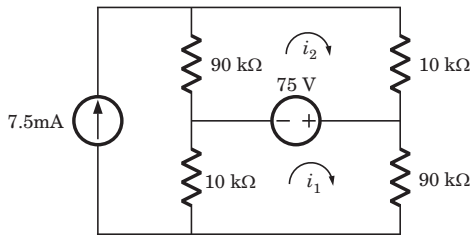


Fig. P1.3.8

- (A) 1 mA (B) 1.5 mA
(C) 2 mA (D) 2.5 mA

9. $i_1 = ?$

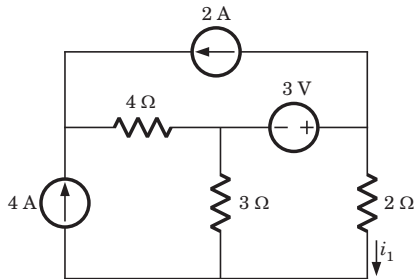


Fig. P1.3.9

- (A) 4 A (B) 3 A
(C) 6 A (D) 5 A

10. $i_1 = ?$

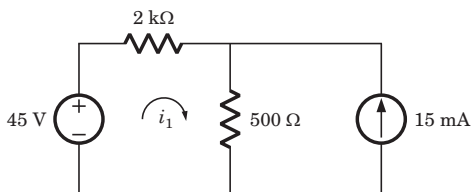


Fig. P1.3.10

- (A) 20 mA (B) 15 mA
(C) 10 mA (D) 5 mA

11. $i_1 = ?$

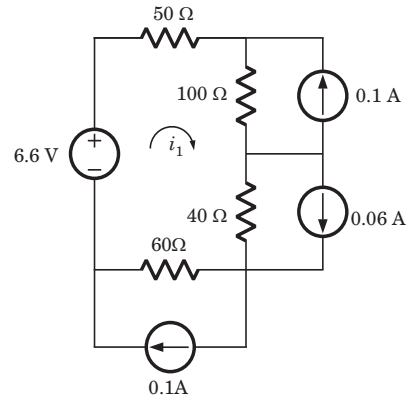


Fig. P1.3.11

- (A) 0.01 A (B) -0.01 A
(C) 0.03 A (D) 0.02 A

12. The value of the current measured by the ammeter in Fig. P1.3.12 is

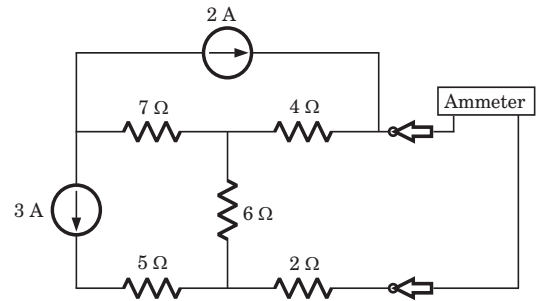


Fig. P1.3.12

- (A) $\frac{2}{3}$ A (B) $\frac{5}{3}$ A
(C) $-\frac{5}{6}$ A (D) $\frac{2}{9}$ A

13. $i_1 = ?$

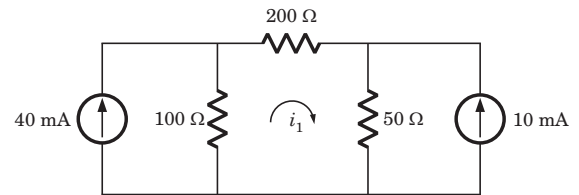


Fig. 1.3.13

- (A) 10 mA (B) -10 mA
(C) 0.4 mA (D) -0.4 mA

14. The values of node voltage are $v_a = 12$ V, $v_b = 9.88$ V and $v_c = 5.29$ V. The power supplied by the voltage source is

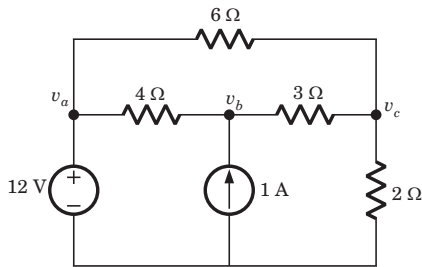


Fig. 1.3.14

- (A) 19.8 W (B) 27.3 W
(C) 46.9 W (D) 54.6 W

15. $i_1, i_2, i_3 = ?$

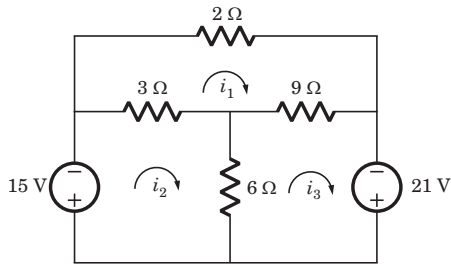


Fig. P1.3.15

- (A) 3 A, 2 A, and 4 A (B) 3 A, 3 A, and 8 A
(C) 1 A, 3 A, and 4 A (D) 1 A, 2 A, and 8 A

16. $v_o = ?$

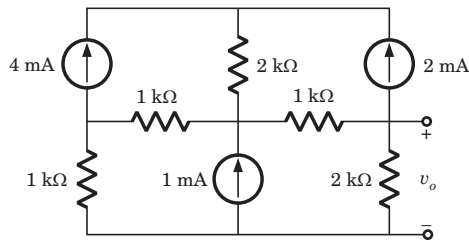


Fig. P1.3.16

- (A) $\frac{6}{5}$ V (B) $\frac{8}{5}$ V
(C) $\frac{6}{7}$ V (D) $\frac{5}{7}$ V

17. The mesh current equation for the circuit in Fig. P1.3.17 are

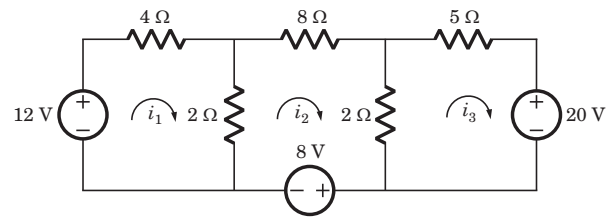


Fig. 1.3.17

(A)
$$\begin{bmatrix} 4 & -2 & 0 \\ -2 & 8 & -2 \\ 0 & -2 & 5 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ -8 \\ 20 \end{bmatrix}$$

(B)
$$\begin{bmatrix} 6 & -2 & 0 \\ 2 & -12 & 2 \\ 0 & 2 & -7 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 8 \\ 20 \end{bmatrix}$$

(C)
$$\begin{bmatrix} 6 & -2 & 0 \\ -2 & 12 & -2 \\ 0 & -2 & 7 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 8 \\ 20 \end{bmatrix}$$

(D)
$$\begin{bmatrix} 4 & -2 & 0 \\ 2 & -8 & 2 \\ 0 & 2 & -5 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 8 \\ 20 \end{bmatrix}$$

18. For the circuit shown in Fig. P1.3.18 the mesh equation are

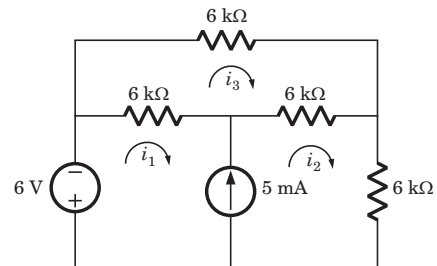


Fig. 1.3.18

(A)
$$\begin{bmatrix} 6k & -12k & -12k \\ -6k & 6k & -18k \\ -1k & -1k & 0k \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} -6 \\ 0 \\ 5 \end{bmatrix}$$

(B)
$$\begin{bmatrix} 6k & 12k & -12k \\ -6k & -6k & 18k \\ -1k & 1k & 0k \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} -6 \\ 0 \\ 5 \end{bmatrix}$$

(C)
$$\begin{bmatrix} -6k & -12k & 12k \\ 6k & -6k & 18k \\ 1k & 1k & 0k \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} -6 \\ 0 \\ 5 \end{bmatrix}$$

(D)
$$\begin{bmatrix} -6k & 12k & -12k \\ -6k & 6k & -18k \\ -1k & 1k & 0k \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} -6 \\ 0 \\ 5 \end{bmatrix}$$

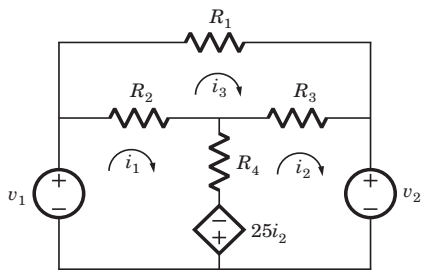


Fig. P1.3.25

The value of R_4 is

- (A) 40 (B) 15
(C) 5 (D) 20

26. $v_a = ?$

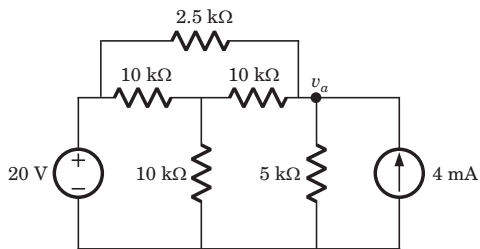


Fig. P1.3.26

- (A) 26 V (B) 19 V
(C) 13 V (D) 18 V

27. $v = ?$

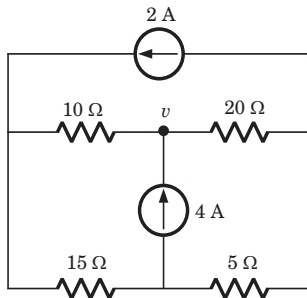


Fig. P.3.1.27

- (A) 60 V (B) -60 V
(C) 30 V (D) -30 V

28. $i_1 = ?$

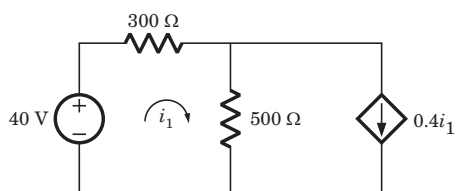


Fig. P1.3.28

- (A) 66.67 mA (B) 46.24 mA
(C) 23.12 mA (D) 33.33 mA

29. $v_a = ?$

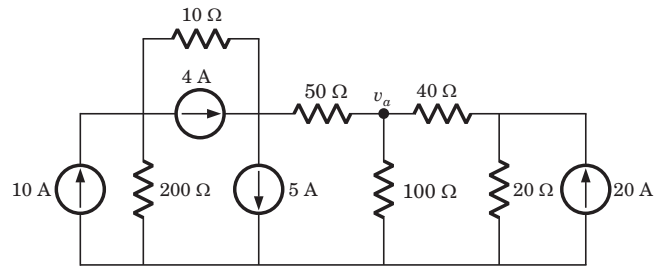


Fig. P1.3.29

- (A) 342 V (B) 171 V
(C) 198 V (D) 396 V

30. $i_a = ?$

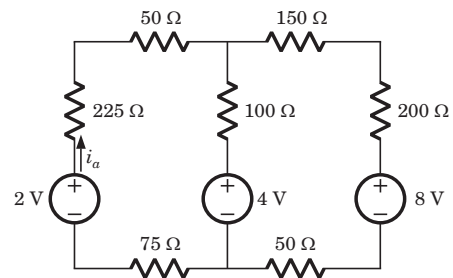


Fig. P1.3.30

- (A) 14 mA (B) -6.5 mA
(C) 7 mA (D) -21 mA

31. $v_2 = ?$

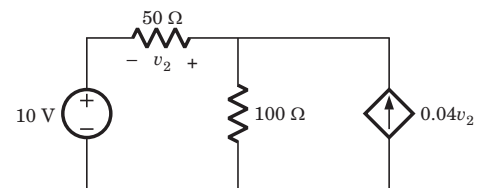


Fig. P1.3.31

- (A) 5 V (B) 75 V
(C) 3 V (D) 10 V

32. $i_1 = ?$

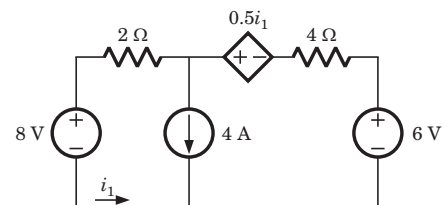


Fig. P1.3.32

- (A) -1.636 A (B) -3.273 A
 (C) -2.314 A (D) -4.628 A

33. $v_x = ?$

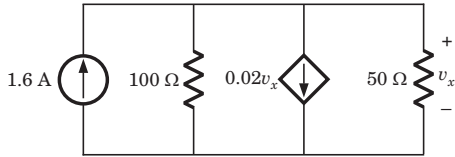


Fig. P1.3.33

- (A) 32 V (B) -32 V
 (C) 12 V (D) -12 V

34. $i_b = ?$

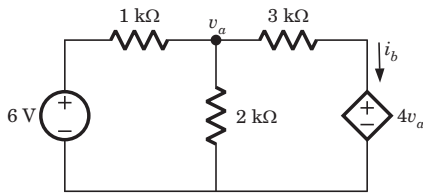


Fig. P1.3.34

- (A) 4 mA (B) -4 mA
 (C) 12 mA (D) -12 mA

35. $v_b = ?$

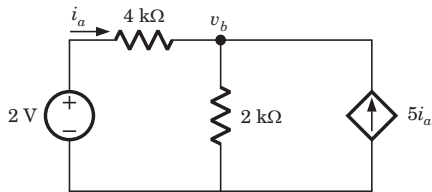


Fig. P1.3.35

- (A) 1 V (B) 1.5 V
 (C) 4 V (D) 6 V

36. $v_x = ?$

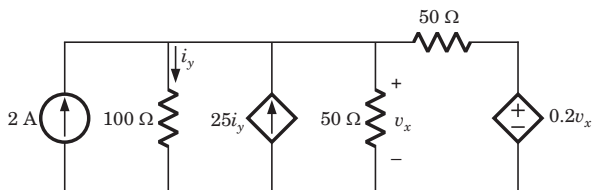


Fig. P1.3.36

- (A) -3 V (B) 3 V
 (C) 10 V (D) -10 V

37. $v_a = ?$

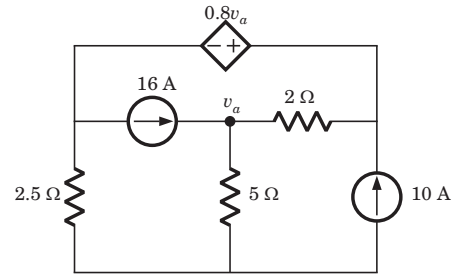


Fig. P1.3.37

- (A) 25.91 V (B) -25.91 V
 (C) 51.82 V (D) -51.82 V

38. For the circuit of Fig. P1.3.38 the value of v_s , that will result in $v_1 = 0$, is

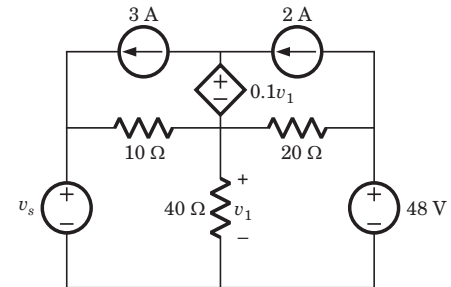


Fig. P1.3.38

- (A) 28 V (B) -28 V
 (C) 14 V (D) -14 V

39. $i_1, i_2 = ?$

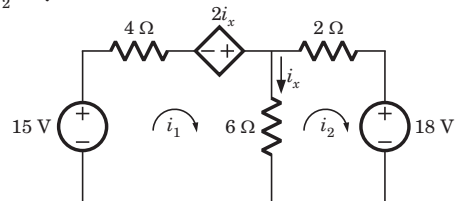


Fig. P1.3.39

- (A) $2.6\text{ A}, 1.4\text{ A}$ (B) $2.6\text{ A}, -1.4\text{ A}$
 (C) $1.6\text{ A}, 1.35\text{ A}$ (D) $1.2\text{ A}, -1.35\text{ A}$

40. $v_1 = ?$

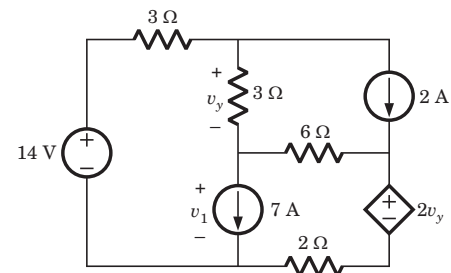


Fig. P1.3.40

- (A) 10 V (B) -10 V
(C) 7 V (D) -7 V

41. $v_x = ?$

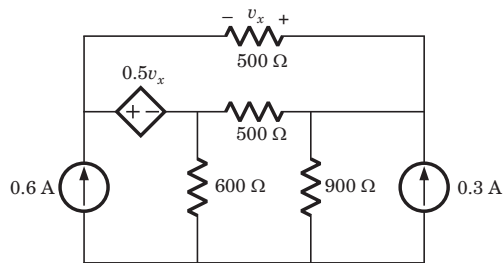


Fig. P1.3.41

- (A) 9 V (B) -9 V
(C) 10 V (D) -10 V

42. The power being dissipated in the $2\ \Omega$ resistor in the circuit of Fig. P1.3.42 is

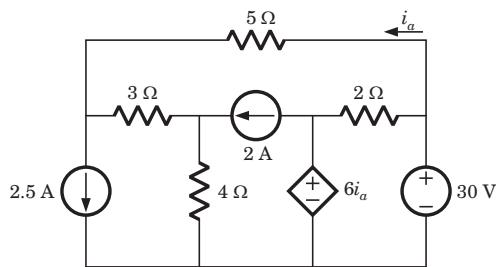


Fig. P1.3.42

- (A) 76.4 W (B) 305.6 W
(C) 52.5 W (D) 210.0 W

43. $i_1 = ?$

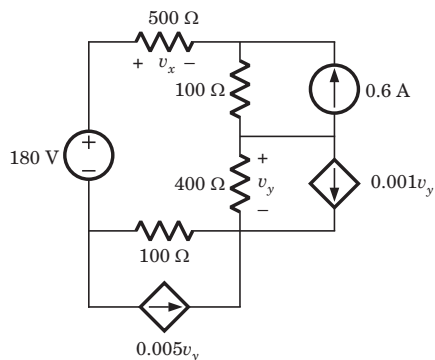


Fig. P1.3.43

- (A) 0.12 A (B) 0.24 A
(C) 0.36 A (D) 0.48 A

SOLUTIONS

1. (B) Applying the nodal analysis

$$v_1 = \frac{\frac{4v_s + v_s}{6R + 3R}}{\frac{1}{6R} + \frac{1}{3R} + \frac{1}{6R}} = 15v_s$$

2. (C) $v_a = 2(3 + 1) + 3(1) = 11\text{ V}$

3. (D) $-\frac{v_1}{60} + \frac{-v_1}{60} + 6 = 9 \Rightarrow v_1 = -90\text{ V}$

4. (C) $\frac{v_a - 10}{4} + \frac{v_a}{2} = 4 \Rightarrow v_a = 8.67\text{ V}$

5. (D) $\frac{v_2}{20} + \frac{v_2 + 10}{30} = 0.5 \Rightarrow v_2 = 2\text{ V}$

6. (B) Using Thevenin equivalent and source transform

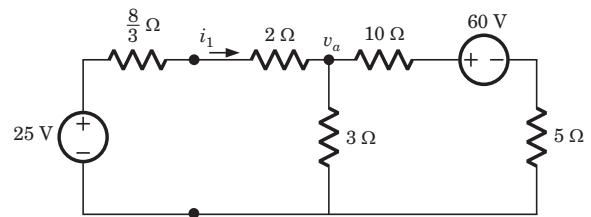


Fig. S.1.3.6

$$v_a = \frac{\frac{25}{\frac{8}{3} + 2} + \frac{60}{15}}{\frac{3}{14} + \frac{1}{3} + \frac{1}{15}} = 15.23\text{ V}$$

$$i_1 = \frac{25 - 15.23}{\frac{14}{3}} = 2.09\text{ A}$$

7. (A) $i_b = \frac{10}{64 + 36} + 0.5 = 0.6\text{ A}$

8. (B) $75 = 90ki_1 + 10k(i_1 - 7.5\text{m})$

$$150 = 100ki_1 \Rightarrow i_1 = 1.5\text{ mA}$$

9. (B) $3 = 2i_1 + 3(i_1 - 4) \Rightarrow i_1 = 3\text{ A}$

10. (B) $45 = 2ki_1 + 500(i_1 + 15\text{m})$

$$\Rightarrow i_1 = 15\text{ mA}$$

11. (D)

$$6.6 = 50i_1 + 100(i_1 + 0.1) + 40(i_1 - 0.06) + 60(i_1 - 0.1)$$

$$i_1 = 0.02\text{ A}$$

38. (D) If $v_1 = 0$, the dependent source is a short circuit

$$\frac{v_1}{40} + \frac{v_1 - v_s}{10} + \frac{v_1 - 48}{20} = 2 - 3 \Rightarrow v_1 = 0$$

$$-\frac{v_s}{10} - \frac{48}{20} = -1 \Rightarrow v_s = -14 \text{ V}$$

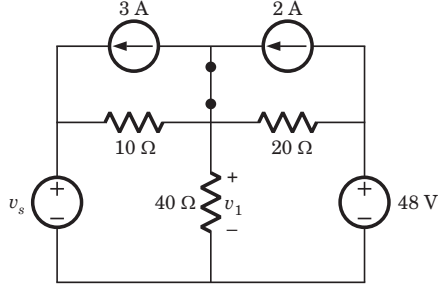


Fig. S1.3.38

$$i_a = \frac{30 + 7.5 + 2}{12} = 3.29 \text{ A} \Rightarrow 6i_a = 19.75 \text{ V}$$

voltage across 2Ω resistor

$$30 - 19.75 = 10.25 \text{ V},$$

$$P = \frac{(10.25)^2}{2} = 52.53 \text{ W}$$

43. (A) $v_x = 500i_1$

$$v_y = 400(i_1 - 0.001v_x) = 400(i_1 - 0.5i_1) = 200i_1$$

$$180 = 500i_1 + 100(i_1 - 0.6) + 200i_1 + 100(i_1 + 0.005v_y)$$

$$180 = 900i_1 - 60 + 100 \times 0.005 \times 200i_1$$

$$i_1 = 0.12 \text{ A}$$

39. (D) $i_x = i_1 - i_2$

$$15 = 4i_1 - 2(i_1 - i_2) + 6(i_1 - i_2)$$

$$\Rightarrow 8i_1 - 4i_2 = 15 \quad \dots(i)$$

$$-18 = 2i_2 + 6(i_2 - i_1)$$

$$\Rightarrow 3i_1 - 4i_2 = 9 \quad \dots(ii)$$

$$i_1 = 12 \text{ A}, i_2 = -1.35 \text{ A}$$

40. (B) $14 = 3i_1 + v_y + 6(i_1 - 2 - 7) + 2v_y + 2(i_1 - 7)$

$$v_y = 3(i_1 - 2)$$

$$14 = 3i_1 + 9(i_1 - 2) + 6(i_1 - 9) + 2(i_1 - 7)$$

$$14 = 20i_1 - 18 - 54 - 14 \Rightarrow i_1 = 5 \text{ A}$$

$$v_1 = 6(5 - 2 - 7) + 2 \times 3(5 - 2) + 2(5 - 7) = -10 \text{ V}$$

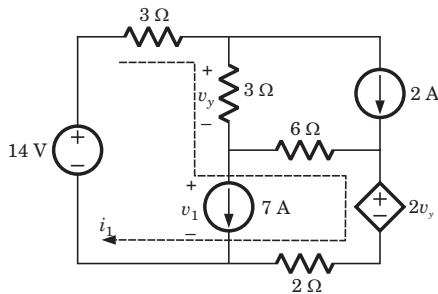


Fig. S1.3.40

41. (D) Let i_1 and i_2 be two loop current

$$0.5v_x = 500i_1 + 500(i_1 - i_2),$$

$$v_x = -500i_1$$

$$\Rightarrow 5i_1 - 2i_2 = 0 \quad \dots(i)$$

$$500(i_2 - i_1) + 900(i_2 + 0.3) + 600(i_2 - 0.6) = 0$$

$$-5i_1 + 20i_2 = 0.9 \quad \dots(ii)$$

$$i_1 = 20 \text{ mA}, v_x = -500 \times 20\text{m} = -10 \text{ V}$$

42. (C) $30 = 5i_a + 3(i_a - 2.5) + 4(i_a - 2.5 + 2)$