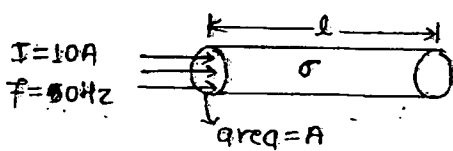



Transmission Lines

- (1) In ele. engg. 2 wire Tx line is used Xfer energy at low freq. (50 Hz)
- (2) In comm. engg. 2 wire Tx line is used to Xfer electromagnetic energy at very high freq. ($> 1 \text{ MHz}$)
- (3) Tx line problems can be solve using EM theory method solving maxwells eqn (or) network theory method (KVL, KCL).
we prefer n/w theory method because it is simpler.

(4) Tx lines parameters:-





$$R = \frac{l}{\sigma A}$$

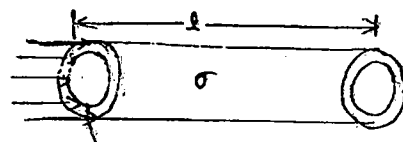

$I = 10 \text{ A}$ in (2 πr) area decreased

$$f = 10^7 \text{ Hz}$$
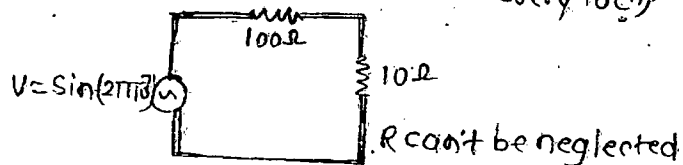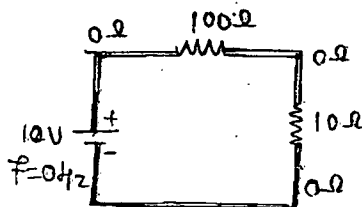
$$R_{AC} = \frac{l}{\sigma A} \quad (\text{Resistance increases every } 10\%)$$



(i) $R \rightarrow$ Whenever high freq. signal flowing through a cond^r cross sectional area decreases, so that resistance comes in to the picture of every location.

$R \rightarrow$ series resistance of both cond^r per meter length ($\frac{\Omega}{\text{m}}$)

* For a perfect cond^r ($\sigma_c = \infty$)

$$R = \frac{l}{\sigma_c A} = \frac{l}{\infty} = 0$$

(ii) $L \rightarrow$ Whenever current goes through a cond^r inductance is present.

$L \rightarrow$ series inductance of both cond^r per meter length ($\frac{\text{H}}{\text{m}}$)

(iii) $G \rightarrow$ If the dielectric b/n the cond^r is imperfect then conductance exist.


$G \rightarrow$ shunt conductance per meter length ($\frac{\text{S}}{\text{m}}$)

* If the dielectric is perfect $\sigma_m = 0$, $\epsilon_1 = \frac{\sigma_m A}{l} = 0$

(iv) $C \rightarrow$ Whenever 2 cond^s are separated by dielectric then capacitance exist.
 $C \rightarrow$ Shunt capacitance per meter length $(\frac{F}{m})$

1st req:

Tx lines eq circuit $\rightarrow$

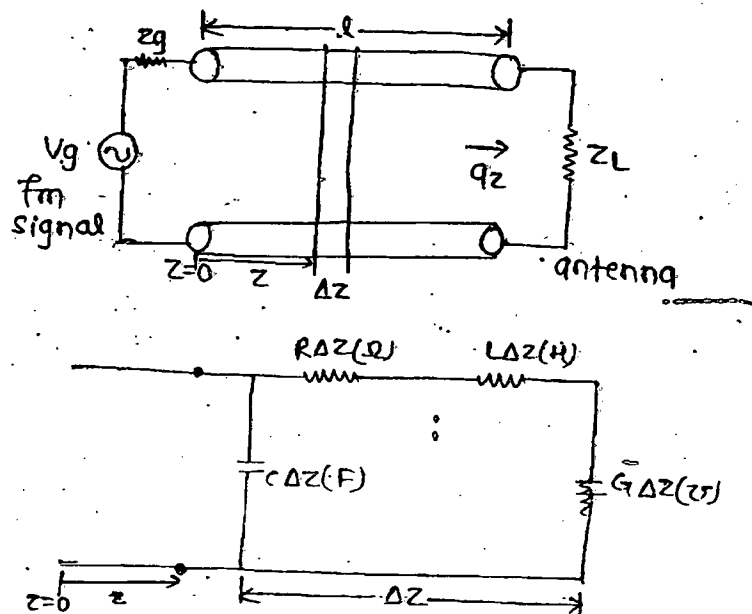

1st req:

Tx lines eqⁿ in phasor domain $\rightarrow$

$$-\frac{\partial V_s}{\partial z} = (R + j\omega L) I_s$$

$$\frac{\partial V_s}{\partial z} = -Z I_s \quad \text{--- (i)}$$

$$\boxed{Z = R + j\omega L \left(\frac{\Omega}{m} \right)}$$

$$-\frac{\partial I_s}{\partial z} = (G + j\omega C) V_s$$

$\downarrow$ $\downarrow$
 $\left(\frac{V}{m} \right)$ $\left(\frac{F}{m} \right)$

$$\frac{\partial I_s}{\partial z} = -Y V_s \quad \text{--- (ii)}$$

$$\boxed{Y = G + j\omega C \left(\frac{S}{m} \right)}$$

$$\frac{\partial^2 V_s}{\partial z^2} = (R + j\omega L)(G + j\omega C) V_s$$

$$\frac{\partial^2 V_s}{\partial z^2} = \gamma^2 V_s \quad (3) \quad (\nabla^2 \bar{E}_s = \gamma^2 \bar{E}_s)$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} = \alpha + j\beta$$

$$\frac{\partial^2 I_s}{\partial z^2} = \gamma^2 I_s \quad (4) \quad (\nabla^2 \bar{H}_s = \gamma^2 \bar{H}_s)$$

$$Z_0 = \sqrt{\frac{R + j\omega L \left(\frac{n}{\epsilon_0}\right)}{G + j\omega C \left(\frac{\mu}{\mu_0}\right)}} = (\Omega)^2 = \Omega \quad (\text{characteristic impedance})$$

Note →

(i) Lossless transmission → $(\alpha = 0) (\beta \neq 0)$

• If the Tx lines condⁿ are perfect then $(R = 0)$,

If the dielectric is perfect $(G = 0)$.

Then $\gamma = \sqrt{(0 + j\omega L)(0 + j\omega C)} = j\omega\sqrt{LC} = \alpha + j\beta$

compare; $\boxed{\alpha = 0, \beta = \omega\sqrt{LC}}$

(ii) Increase the freq. so that $\omega L \gg R$; $\omega C \gg G$ then R, G can be neglected.


-- $\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$

R, G are neglected


$\gamma = \sqrt{(j\omega L)(j\omega C)} = j\omega\sqrt{LC} = \alpha + j\beta$

$\boxed{\alpha = 0, \beta = \omega\sqrt{LC}}$


(iii) Distortionless transmission →

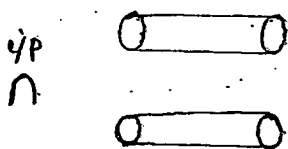

No loss ($\alpha = 0$)
No distortion

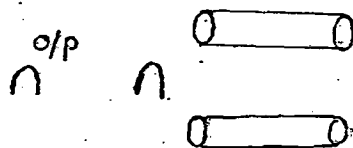

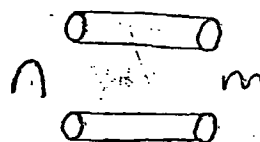loss is present ($\alpha \neq 0$)
No distortion



distortion is present

Defination → If the TL line is distortionless then the α must be constant
 β must be linear fⁿ of freq.

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\gamma = \sqrt{R(1 + j\omega \frac{L}{R})G(1 + j\omega \frac{C}{G})}$$

If $\frac{L}{R} = \frac{C}{G}$ $LG = RC$ Condⁿ to have a distortionless TL.

$$\gamma = \sqrt{RG(1 + j\omega \frac{L}{R})^2}$$

$$\gamma = \sqrt{RG} (1 + j\omega \frac{L}{R})$$

$$\gamma = \sqrt{RG} + \sqrt{RG} \cdot \frac{L}{R} j\omega = \sqrt{RG} + j\omega \sqrt{\frac{G}{R}} L$$

$$\gamma = \sqrt{RG} + j\omega L \sqrt{\frac{C}{L}}$$

$$\gamma = \sqrt{RG} + j\sqrt{LC}\omega = \alpha + j\beta$$

$$\alpha = \sqrt{RG} = \text{constant}$$

$$\beta = \omega\sqrt{LC} \Rightarrow \beta \propto \omega \text{ linear fⁿ of freq.}$$

Note →

General

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

Lossless
 $(R=G=0)$

$$\gamma = j\omega\sqrt{LC}$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

Distortionless
 $LG = RC$

$$\gamma = \sqrt{RG} + j\omega\sqrt{LC}$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

Note →

- | | | |
|---------------------------------------|---|------------------|
| (i) $R=G=0$ | } lossless | } Distortionless |
| (ii) $\omega L \gg R, \omega C \gg G$ | | |
| (iii) $LG=RC$ | } distortionless
$\alpha=\sqrt{RG}, \beta=\omega\sqrt{LC}$ | |

* Lossless tx line is distortionless but distortionless does not mean lossless.

Note →

(i) We know that for a coaxial cable

$$C = \frac{2\pi\epsilon}{\ln(b/a)} \left(\frac{F}{m} \right); L = \frac{\mu}{2\pi} \ln\left(\frac{b}{a}\right) \left(\frac{H}{m} \right)$$

$$\boxed{LC = \mu\epsilon}$$

* For a lossless coaxial tx line

$$Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{\frac{\mu}{2\pi} \ln(b/a)}{\frac{2\pi\epsilon}{\ln(b/a)}}} = \frac{1}{2\pi} \ln\left(\frac{b}{a}\right) \sqrt{\frac{\mu}{\epsilon}}$$


$$Z_0 = \frac{1}{2\pi} \sqrt{\frac{\mu_0}{\epsilon_0}} \sqrt{\frac{\mu_r}{\epsilon_r}} \ln\left(\frac{b}{a}\right)$$

$$= \frac{1}{2\pi} (120\pi) \frac{1}{\sqrt{\epsilon_r}} \ln\left(\frac{b}{a}\right)$$

$$\boxed{Z_0 = \sqrt{\frac{L}{C}} = \frac{60}{\sqrt{\epsilon_r}} \ln\left(\frac{b}{a}\right) \Omega}$$

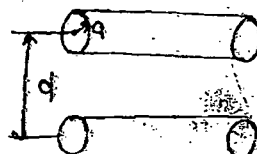(ii) For a lossless 2 wire line

$$\boxed{Z_0 = \frac{120}{\sqrt{\epsilon_r}} \ln\left(\frac{d}{a}\right)}$$



$a \rightarrow$ Radius of the cond^r

$d \rightarrow$ distance between the centers of cond^r

(C) βz is ~~called~~ electrical length of TL line

$$(4) \quad v_p = \frac{\omega}{\beta} = \frac{\omega}{\omega \sqrt{\mu\epsilon}} = \frac{1}{\sqrt{\mu\epsilon}} = \frac{c}{\sqrt{\mu_r \epsilon_r}}$$

$$v_p = \frac{c}{\sqrt{\mu_r \epsilon_r}}$$

$$(5) \quad \beta = \frac{2\pi}{\lambda}$$

$$\lambda = \frac{c}{\sqrt{\epsilon_r \mu_r}}$$

(Not req)
Solution of TL line eqn $\rightarrow$

$$\frac{\partial^2 v_s}{\partial z^2} = \gamma^2 v_s \quad \text{--- (i)}$$

$$\frac{\partial^2 E_{xs}}{\partial z^2} = \gamma^2 E_{xs}$$

Solution

$$E_{xs} = E_{i0} e^{-\gamma z} + E_{r0} e^{+\gamma z}$$

$$v_s = \underbrace{V^+ e^{-\gamma z}}_{\text{Incident}} + \underbrace{V^- e^{+\gamma z}}_{\text{Reflected}} \quad \text{--- (ii)}$$

Similarly

$$\frac{\partial^2 I_s}{\partial z^2} = \gamma^2 I_s \quad \text{--- (iii)}$$

$$I_s = \underbrace{I^+ e^{-\gamma z}}_{\text{Incident}} + \underbrace{I^- e^{+\gamma z}}_{\text{Reflected}} \quad \text{--- (iv)}$$

$V^+ \rightarrow$ Initial value of voltage of incident wave

$I^+ \rightarrow$ Initial value of current of incident wave

$V^- \rightarrow$ Initial value of voltage of Reflected wave

$I^- \rightarrow$ Initial value of current of Reflected wave

Relation b/n V^+ , I^+ & V^- , $I^- \rightarrow$

$$\frac{\partial v_s}{\partial z} = -Z I_s \quad \text{--- (v)}$$

From (2) (4) in (5)

$$\frac{\partial}{\partial z} (V^+ e^{-\gamma z} + V^- e^{+\gamma z}) = -Z (I^+ e^{-\gamma z} + I^- e^{+\gamma z})$$

$$V^+ \underline{e^{-\gamma z}} (-\gamma) + V^- \underline{e^{+\gamma z}} (\gamma) = -Z I^+ \underline{e^{-\gamma z}} - Z I^- \underline{e^{+\gamma z}}$$

Compare the coefficients $\rightarrow$

$$V^+(-\gamma) = -Z(I^+)$$


$$\left(\frac{V}{I}\right) \frac{V^+}{I^+} = \frac{Z}{\gamma} = \frac{R+j\omega L}{\sqrt{(R+j\omega L)(G+j\omega C)}} = \sqrt{\frac{R+j\omega L}{G+j\omega C}} (\Omega) = Z_0$$

$$\boxed{\frac{V^+}{I^+} = Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}} = \text{defined as characteristic impedance}}$$

$$V^-(-\gamma) = -Z I^- \Rightarrow \frac{V^-}{I^-} = \frac{-Z}{\gamma} = -Z_0$$

$$\boxed{\frac{V^-}{I^-} = -Z_0}$$

Load Impedance $\rightarrow$

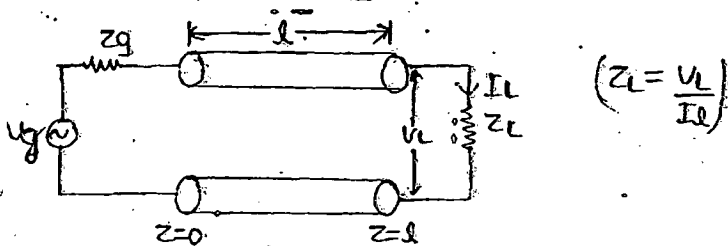

$$Z_L = \frac{V_L}{I_L} = \frac{V^+ e^{-\gamma l} + V^- e^{+\gamma l}}{I^+ e^{-\gamma l} + I^- e^{+\gamma l}} = \frac{V^+ e^{-\gamma l} + V^- e^{+\gamma l}}{\frac{V^+}{Z_0} e^{-\gamma l} - \frac{V^-}{Z_0} e^{+\gamma l}}$$

$$Z_L = Z_0 \times \frac{(V^+ e^{-\gamma l}) \left[1 + \frac{V^- e^{+\gamma l}}{V^+ e^{-\gamma l}} \right]}{(V^+ e^{-\gamma l}) \left[1 - \frac{V^- e^{+\gamma l}}{V^+ e^{-\gamma l}} \right]}$$

$$\therefore \Gamma_L = \frac{V^- e^{+\gamma l}}{V^+ e^{-\gamma l}}$$

$$Z_L = Z_0 \times \frac{1 + \Gamma_L}{1 - \Gamma_L} \Rightarrow \frac{Z_L}{Z_0} = \frac{1 + \Gamma_L}{1 - \Gamma_L}$$

$$\boxed{\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}}$$

$$\Gamma = \frac{\eta_2 - \eta_1}{\eta_2 + \eta_1}$$

Reflection coefficient →

Case(1) → Reflection coefficient at load = $\Gamma_L = \frac{\text{Reflected vol. at load}}{\text{incident vol. at load}}$

$$= \frac{V^- e^{\gamma l}}{V^+ e^{\gamma l}} \quad \text{--- (i)}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = |\Gamma_L| e^{j\theta_L}$$

(Complex)


Case(2) → Reflection coefficient at a z from the source end.

$$\Gamma(z) = \frac{V^- e^{\gamma z}}{V^+ e^{\gamma z}} \quad \text{--- (ii)}$$

Case(3) → Reflection coefficient at a distance " d " from load end is

$$\Gamma(d) = |\Gamma_L| e^{-2\alpha d} e^{j(\theta_L - 2\beta d)}$$

Explanation →

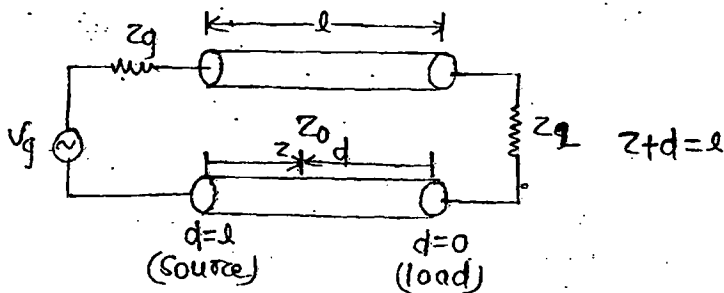

In general mismatch occurs at load. So we measure from load.

Reflection coefficient at d distance is obtained by putting $z=l-d$ in eqn (2)

$$\begin{aligned} \Gamma(d) &= \frac{V^- e^{\gamma(l-d)}}{V^+ e^{\gamma(l-d)}} = \frac{V^- e^{\gamma l}}{V^+ e^{\gamma l}} \cdot e^{-2\gamma d} \quad \left| \gamma = \alpha + j\beta \right. \\ &= |\Gamma_L| e^{-2(\alpha + j\beta)d} \\ &= |\Gamma_L| e^{j\theta_L} e^{-2\alpha d} e^{-j2\beta d} \\ &= |\Gamma_L| e^{-2\alpha d} e^{j(\theta_L - 2\beta d)} \end{aligned}$$

Transmission Coefficient →

$$T_L = 1 + \Gamma_L$$

$$T_L = 1 + \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{2Z_L}{Z_L + Z_0} \quad \left| \quad T = \frac{2\eta_2}{\eta_1 + \eta_2} \right.$$

Standing Wave Ratio →

$$\text{Voltage standing wave Ratio} = VSWR = \frac{|V|_{\max}}{|V|_{\min}}$$

$$\text{Current standing wave Ratio} = ISWR = \frac{|I|_{\max}}{|I|_{\min}}$$

$$VSWR = ISWR = SWR = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$|\Gamma| = \frac{SWR - 1}{SWR + 1}$$

Note →

(1) If load is SC → $Z_L = 0$; $\Gamma_L = \frac{0 - Z_0}{0 + Z_0} = -1$

$$|\Gamma_L| = 1$$

If load is OC → $Z_L = \infty$; $\Gamma_L = \frac{Z_L(1 - \frac{Z_0}{Z_L})}{Z_L(1 + \frac{Z_0}{Z_L})} = \frac{1 - \frac{Z_0}{\infty}}{1 + \frac{Z_0}{\infty}} = 1$

$$|\Gamma_L| = 1$$

In this case complete standing wave is present.

(2) If $Z_L = Z_0$; $|\Gamma_L| = 0$; $SWR = \frac{1 + 0}{1 - 0} = 1$

In this case no standing wave on a tx line. It is also called as flat tx line.

(3) If Z_L, Z_0 are real & $Z_L > Z_0$ then $SWR = \frac{Z_L}{Z_0}$

If Z_L, Z_0 are real & $Z_0 > Z_L$ then $SWR = \frac{Z_0}{Z_L}$

$$\text{For 1st. } SWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = 1 + \frac{\left| \frac{Z_L - Z_0}{Z_L + Z_0} \right|}{1 - \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right|} = 1 + \frac{Z_L - Z_0}{Z_L + Z_0}$$

For 2nd case;

$$SWR = \frac{1 + \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right|}{1 - \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right|} = \frac{1 + \frac{Z_0 - Z_L}{Z_0 + Z_L}}{1 - \frac{Z_0 - Z_L}{Z_0 + Z_L}}$$

(4) Range :-

$$\begin{array}{ccc} 0 & \leq | \Gamma | & \leq 1 \\ \downarrow & & \downarrow \\ 1 & \leq SWR & \leq \infty \end{array}$$

Tx line impedance at a distance "d" from the load end →

$$Z(d) = Z_0 \frac{Z_L + Z_0 \tanh(\gamma d)}{Z_0 + Z_L \tanh(\gamma d)} \quad \text{--- (i)}$$

* For a lossless th line $\alpha = 0$; $\gamma = j\beta$, $Z_0 = \sqrt{\frac{L}{C}} = R_0$ (Real)

$$\tanh(j\theta) = j \tan \theta$$

$$\tanh(j\beta d) = j \tan(\beta d)$$


$$Z(d) = R_0 \frac{Z_L + j R_0 \tan(\beta d)}{R_0 + j Z_L \tan(\beta d)} \quad \text{--- (ii)}$$

Tx line length is represented in terms of λ because $\tan(\beta d)$ can be calculated

$$\beta d = \frac{2\pi}{\lambda} d \quad \text{if } d \text{ is given in terms of } \lambda \text{ then } \beta d \text{ comes in radian}$$

Eqn of γ, Z_0 →

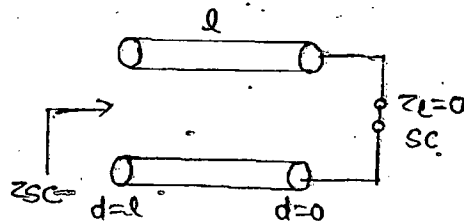
* Measure sending end impedance with sc at load



$$Z(d=l) \equiv Z_0 \frac{0 + Z_0 \tanh(\gamma l)}{Z_0 + 0}$$

$$Z_{sc} = Z_0 \tanh(\gamma l) \text{ ————— (i)}$$

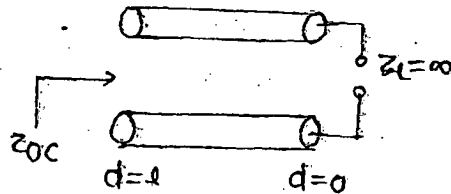* Measure sending end impedance with oc at load.



$$Z(d=l) = \frac{Z_0 + Z_0 \tanh(\gamma l)}{0 + \tanh(\gamma l)}$$

$$Z_{oc} = Z_0 \coth(\gamma l) \text{ ————— (ii)}$$

From (i) x (ii)


$$Z_{sc} \cdot Z_{oc} = Z_0^2$$

$$Z_0 = \sqrt{Z_{sc} \cdot Z_{oc}} \text{ ————— (iii)}$$

From (i) $\div$ (ii)

$$\gamma = \frac{1}{l} \tanh^{-1} \sqrt{\frac{Z_{sc}}{Z_{oc}}} \text{ ————— (iv)}$$

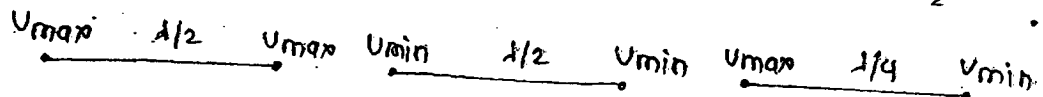Note $\rightarrow$ On a TL line all the parameters (Z, I, V , etc) repeat for a $\frac{\lambda}{2}$ distance



Explanation $\rightarrow$

$$\begin{aligned} * Z(d=0) &= Z_0 \frac{Z_L + jZ_0 \tan(0)}{Z_0 + jZ_L \tan(0)} \\ &= Z_0 \frac{Z_L + 0}{Z_0 + 0} = Z_L \text{ ————— (i)} \end{aligned}$$


* Z at $\pi/2$ at $d=\pi/2$

$$\beta d = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{2} = \pi$$

$$\begin{aligned}
 Z(d=\frac{\lambda}{2}) &= Z_0 \frac{Z_L + jZ_0 \tan(\pi)}{Z_0 + jZ_L \tan(\pi)} \\
 &= Z_0 \frac{Z_L + 0}{Z_0 + 0} = Z_L \quad (2)
 \end{aligned}$$

Note → For a $\frac{\lambda}{4}$ length tx line {quarter wavelength tx line}

$$Z_{in} \cdot Z_L = Z_0^2$$

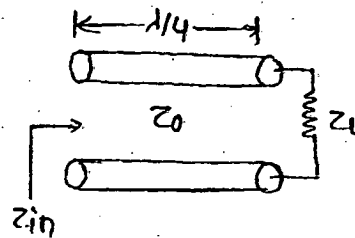

Explanation →

$$d = \frac{\lambda}{4}, \quad \beta d = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \frac{\pi}{2}$$

$$Z(d=\frac{\lambda}{4}) = Z_0 \frac{Z_L + jZ_0 \tan(\pi/2)}{Z_0 + jZ_L \tan(\pi/2)}$$

$$= Z_0 \left(\frac{jZ_0}{jZ_L} \right)$$

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

$$Z_0^2 = Z_{in} Z_L$$

* Normalized impedance → It is the ratio of impedance & Z_0 , denoted by z .

Example → Normalised load impedance $= z_L = \frac{Z_L}{Z_0}$ (unit less)

* $\max^m$ normalised impedance is present at the locⁿ of vol. $\max^m (V_{max})$ & is equal to SWR i.e. $z_{max} = SWR$

$$z_{max} = \frac{Z_{max}}{Z_0}$$


$$z_{max} = \frac{V_{max}}{I_{min}} \cdot \frac{1}{Z_0} = \frac{V_{max}}{Z_0 I_{min}} = \frac{V_{max}}{V_{min}} = SWR$$

* x_{min}^{min} normalised impedance is present at the locⁿ of V_{min} i.e. equal to $\frac{1}{SWR}$ i.e. $Z_{min} = \frac{1}{SWR}$

$$Z_{min} = \frac{Z_{min}}{Z_0} = \frac{V_{min}}{\frac{I_{max}}{Z_0}} = \frac{V_{min}}{I_{max} Z_0} = \frac{V_{min}}{V_{max}}$$

$$Z_{min} = \frac{1}{\left(\frac{V_{max}}{V_{min}}\right)} = \frac{1}{SWR}$$

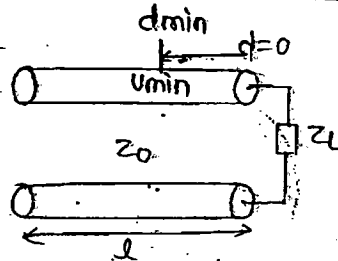* Location of 1st voltage min^m (d_{min}) from the load $\rightarrow$



$$\Gamma(d) = |\Gamma| e^{-2\alpha d} e^{j(\theta_L - 2\beta d)}$$

d_{min} is obtained

$$\theta_L - 2\beta d_{min} = -\pi$$

$$d_{min} = \frac{1}{4\pi} (\pi + \theta_L) \quad \text{--- (i) } \Gamma = |\Gamma| e^{j\theta_L}$$

d_{min} Location of 1st V_{max} is $d_{max} = d_{min} \pm \frac{\lambda}{4}$

Note $\rightarrow$

(i) If Z_L, Z_0 real & $Z_L > Z_0$ then V_{max} is at load

Explanation $\rightarrow$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = +ve = e^{j0} \Rightarrow \theta_L = 0$$

$$d_{min} = \frac{1}{4\pi} (\pi + 0) = \frac{\lambda}{4}$$

$$d_{max} = d_{min} \pm \frac{\lambda}{4}$$

$$= \frac{1}{4} \pm \frac{1}{4}$$

$$= 0, \frac{1}{2}$$

(2) If z_L, z_0 are real & $z_0 > z_L$ then V_{min} is at load

Explanation $\rightarrow$

$$\Gamma_L = \frac{z_L - z_0}{z_L + z_0} = -ve \Rightarrow e^{-j\pi} \Rightarrow \theta_L = -\pi$$

$$d_{min} = \frac{1}{4\pi} (\pi - \pi) = 0$$