

CHAPTER

1.9

MAGNETICALLY COUPLED CIRCUITS

Statement for Q.1-2:

In the circuit of fig. P1.9.1-2 $i_1 = 4 \sin 2t$ A, and $i_2 = 0$.

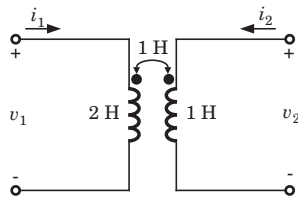


Fig. P1.9.1-2

1. $v_1 = ?$

- (A) $-16 \cos 2t$ V (B) $16 \cos 2t$ V
(C) $4 \cos 2t$ V (D) $-4 \cos 2t$ V

2. $v_2 = ?$

- (A) $2 \cos 2t$ V (B) $-2 \cos 2t$ V
(C) $8 \cos 2t$ V (D) $-8 \cos 2t$ V

Statement for Q.3-4:

Consider the circuit shown in Fig. P1.9.3-4

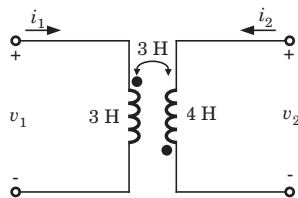


Fig. P1.9.5-6

3. If $i_1 = 0$ and $i_2 = 2 \sin 4t$ A, the voltage v_1 is

- (A) $24 \cos 4t$ V (B) $-24 \cos 4t$ V
(C) $15 \cos 4t$ V (D) $-15 \cos 4t$ V

4. If $i_1 = e^{-2t}$ V and $i_2 = 0$, the voltage v_2 is

- (A) $-6e^{-2t}$ V (B) $6e^{-2t}$ V
(C) $15e^{-2t}$ V (D) $-15e^{-2t}$ V

Statement for Q.5-6:

Consider the circuit shown in fig. P19.5-6

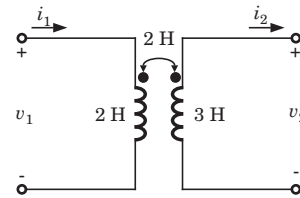


Fig. P1.9.5-6

5. If current $i_1 = 3 \cos 4t$ A and $i_2 = 0$, then voltage v_1 and v_2 are

- (A) $v_1 = -24 \sin 4t$ V, $v_2 = -24 \sin 4t$ V
(B) $v_1 = 24 \sin 4t$ V, $v_2 = -36 \sin 4t$ V
(C) $v_1 = 15 \sin 4t$ V, $v_2 = \sin 4t$ V
(D) $v_1 = -15 \sin 4t$ V, $v_2 = -\sin 4t$ V

6. If current $i_1 = 0$ and $i_2 = 4 \sin 3t$ A, then voltage v_1 and v_2 are

- (A) $v_1 = 24 \cos 3t$ V, $v_2 = 36 \cos 3t$ V
(B) $v_1 = 24 \cos 3t$ V, $v_2 = -36 \cos 3t$ V
(C) $v_1 = -24 \cos 3t$ V, $v_2 = 36 \cos 3t$ V
(D) $v_1 = -24 \cos 3t$ V, $v_2 = -36 \cos 3t$ V

Statement for Q.7-8:

In the circuit shown in fig. P1.9.7-8, $i_1 = 3 \cos 3t$ A and $i_2 = 4 \sin 3t$ A.

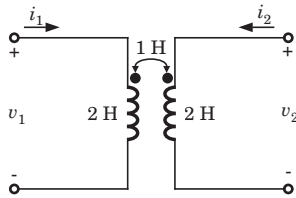


Fig. P1.9.7-8

7. $v_1 = ?$

- (A) $6(-2 \cos t + 3 \sin t)$ V (B) $6(2 \cos t + 3 \sin t)$ V
(C) $-6(2 \cos t + 3 \sin t)$ V (D) $6(2 \cos t - 3 \sin t)$ V

8. $v_2 = ?$

- (A) $3(8 \cos 3t - 3 \sin t)$ V (B) $6(2 \cos t + 3 \sin t)$ V
(C) $3(8 \cos 3t + 3 \sin 3t)$ V (D) $6(2 \cos t - 3 \sin t)$ V

Statement for Q.9-10:

In the circuit shown in fig. P1.9.9-10, $i_1 = 5 \sin 3t$ A and $i_2 = 3 \cos 3t$ A

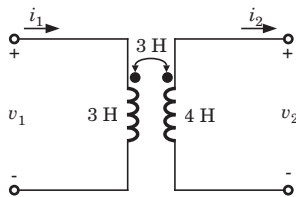


Fig. P1.9.9-10

9. $v_1 = ?$

- (A) $9(5 \cos 3t + 3 \sin 3t)$ V (B) $9(5 \cos 3t - 3 \sin 3t)$ V
(C) $9(4 \cos 3t + 5 \sin 3t)$ V (D) $9(5 \cos 3t - 3 \sin 3t)$ V

10. $v_2 = ?$

- (A) $9(-4 \sin 3t + 5 \cos 3t)$ V (B) $9(4 \sin 3t - 5 \cos 3t)$ V
(C) $9(-4 \sin 3t - 5 \cos 3t)$ V (D) $9(4 \sin 3t + 5 \cos 3t)$ V

11. In the circuit shown in fig. P1.9.11 if current $i_1 = 5 \cos(500t - 20^\circ)$ mA and $i_2 = 20 \cos(500t - 20^\circ)$ mA, the total energy stored in system at $t=0$ is

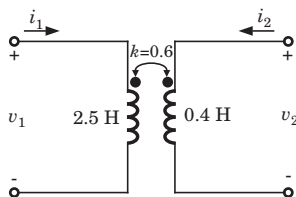


Fig. P1.9.11

- (A) 151.14 μ J (B) 45.24 μ J
(C) 249.44 μ J (D) 143.46 μ J

12. $L_{eq} = ?$

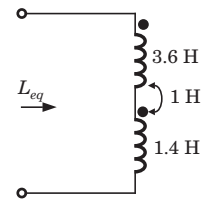


Fig. P1.9.12

- (A) 4 H (B) 6 H
(C) 7 H (D) 0 H

13. $L_{eq} = ?$

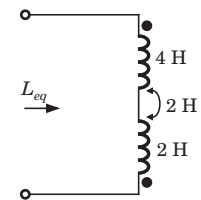


Fig. P1.9.13

- (A) 2 H (B) 4 H
(C) 6 H (D) 8 H

14. $L_{eq} = ?$

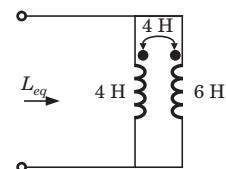


Fig. P1.9.14

- (A) 8 H (B) 6 H
(C) 4 H (D) 2 H

15. $L_{eq} = ?$

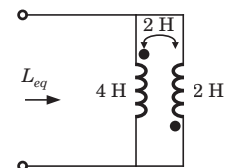


Fig. P1.9.15

- (A) 0.4 H (B) 2 H
(C) 1.2 H (D) 6 H

16. The equivalent inductance of a pair of a coupled inductor in various configuration are

- (a) 7 H after series adding connection
(b) 1.8 H after series opposing connection
(c) 0.5 H after parallel connection with dotted terminal connected together.

The value of L_1 , L_2 and M are

- (A) 3 H, 1.6 H, 1.2 H (B) 1.6 H, 3 H, 1.4 H
(C) 3.7 H, 0.7 H, 1.3 H (D) 2 H, 3 H, 3 H

17. $L_{eq} = ?$

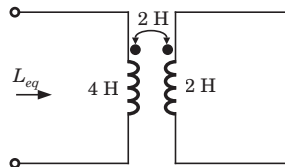


Fig. P1.9.17

- (A) 0.2 H (B) 1 H
(C) 0.4 H (D) 2 H

18. $L_{eq} = ?$

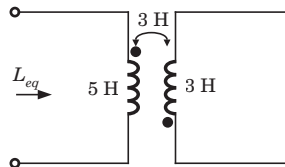


Fig. P1.9.18

- (A) 1 H (B) 2 H
(C) 3 H (D) 4 H

19. In the network of fig. P1.9.19 following terminal are connected together

- (i) none (ii) A to B
(iii) B to C (iv) A to C

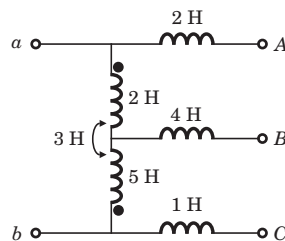


Fig. P1.9.19

The correct match for equivalent inductance seen at terminal $a - b$ is

- | | (i) | (ii) | (iii) | (iv) |
|-----|------|---------|-------|----------|
| (A) | 1 H | 0.875 H | 0.6 H | 0.75 H |
| (B) | 13 H | 0.875 H | 0.6 H | 0.75 H |
| (C) | 13 H | 7.375 H | 6.6 H | 2.4375 H |
| (D) | 1 H | 7.375 H | 6.6 H | 2.4375 H |

20. $L_{eq} = ?$

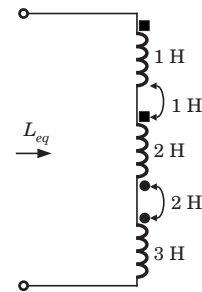


Fig. P1.9.20

- (A) 1 H (B) 2 H
(C) 3 H (D) 4 H

21. $L_{eq} = ?$

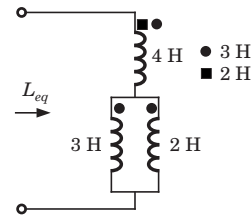


Fig. P1.9.21

- (A) $\frac{41}{5}$ H (B) $\frac{49}{5}$ H
(C) $\frac{51}{5}$ H (D) $\frac{39}{5}$ H

Statement for Q.22-24:

Consider the circuit shown in fig. P1.9.22-24.

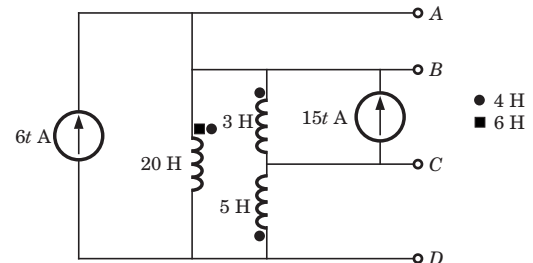


Fig. P1.9.22-24

22. The voltage V_{AG} of terminal AD is

- (A) 60 V (B) -60 V
(C) 180 V (D) 240 V

23. The voltage v_{BG} of terminal BD is

- (A) 45 V (B) 33 V
(C) 69 V (D) 105 V

24. The voltage v_{CG} of terminal CD is

- (A) 30 V (B) 0 V
(C) -36 V (D) 36 V

33. In the circuit of fig. P1.9.33 the $\omega = 2$ rad/s. The resonance occurs when C is

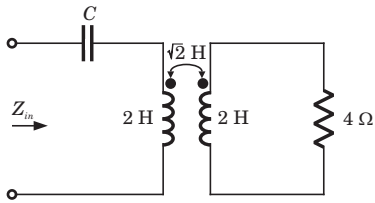


Fig. P1.9.33

- (A) 1 F (B) $\frac{1}{2}$ F
(C) $\frac{1}{3}$ F (D) $\frac{1}{6}$ F

34. In the circuit of fig. P1.9.34, the voltage gain is zero at $\omega = 333.33$ rad/s. The value of C is

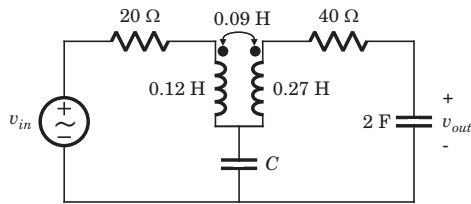


Fig. P1.9.34

- (A) 100 μ F (B) 75 μ F
(C) 50 μ F (D) 25 μ F

35. In the circuit of fig. P1.9.35 at $\omega = 333.33$ rad/s, the voltage gain v_{out}/v_{in} is zero. The value of C is

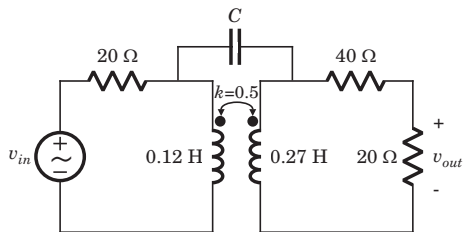


Fig. P1.9.35

- (A) 3.33 mF (B) 33.33 mF
(C) 3.33 μ F (D) 33.33 μ F

36. The Thevenin equivalent at terminal ab for the network shown in fig. P1.9.36 is

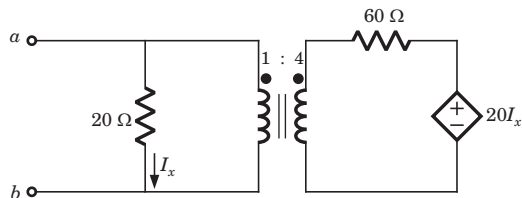


Fig. P1.9.36

- (A) 6 V, 10 Ω (B) 6 V, 4 Ω
(C) 0 V, 4 Ω (D) 0 V, 10 Ω

37. In the circuit of fig. P1.9.37 the maximum power delivered to R_L is

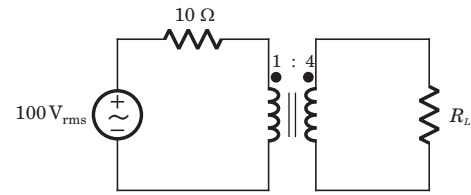


Fig. P1.9.37

- (A) 250 W (B) 200 W
(C) 150 W (D) 100 W

38. The average power delivered to the 8 Ω load in the circuit of fig. P1.9.38 is

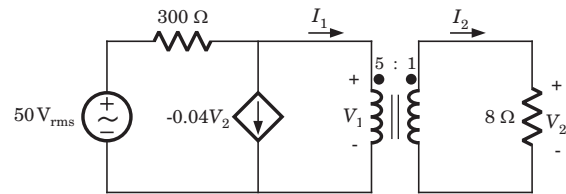


Fig. P1.9.38

- (A) 8 W (B) 1.25 kW
(C) 625 kW (D) 2.50 kW

39. In the circuit of fig. P1.9.39 the ideal source supplies 1000 W, half of which is delivered to the 100 Ω load. The value of a and b are

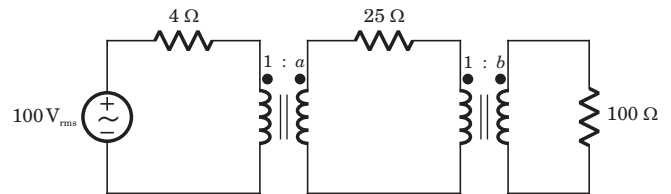


Fig. P1.9.39

- (A) 6, 0.47 (B) 5, 0.89
(C) 0.89, 5 (D) 0.47, 6

40. $I_2 = ?$

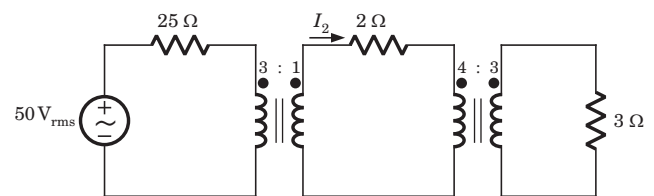


Fig. P1.9.40

- (A) 1.65 A_{rms} (B) 0.18 A_{rms}
(C) 0.66 A_{rms} (D) 5.90 A_{rms}

41. $V_2 = ?$

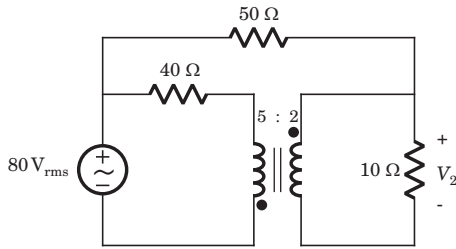


Fig. P1.9.41

- (A) -12.31 V (B) 12.31 V
 (C) -9.231 V (D) 9.231 V

42. The power being dissipated in 400Ω resistor is

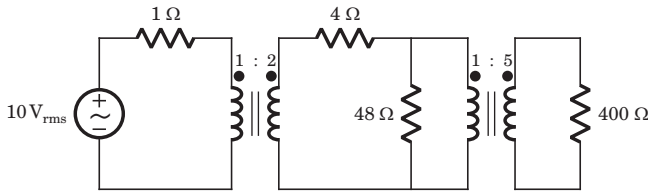


Fig. P1.9.42

- (A) 3 W (B) 6 W
 (C) 9 W (D) 12 W

43. $I_x = ?$

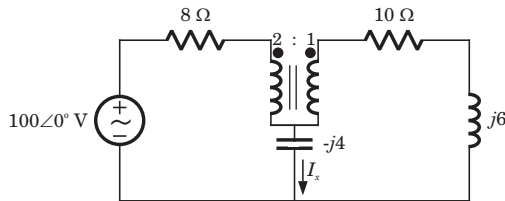


Fig. P1.9.43

- (A) $1.921 \angle 57.4^\circ \text{ A}$ (B) $2.931 \angle 59.4^\circ \text{ A}$
 (C) $1.68 \angle 43.6^\circ \text{ A}$ (D) $1.79 \angle 43.6^\circ \text{ A}$

44. $Z_{in} = ?$

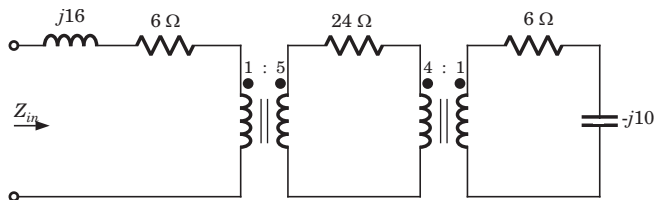


Fig. P1.9.44

- (A) $46.3 + j6.8 \Omega$ (B) $432.1 + j0.96 \Omega$
 (C) $10.8 + j9.6 \Omega$ (D) $615.4 + j0.38 \Omega$

SOLUTIONS

1. (B) $v_1 = 2 \frac{di_1}{dt} + 1 \frac{di_2}{dt} = 2 \frac{di_1}{dt} = 16 \cos 2t \text{ V}$

2. (C) $v_2 = (1) \frac{di_2}{dt} + (1) \frac{di_1}{dt} = \frac{di_1}{dt} = 8 \cos 2t \text{ V}$

3. (B) $v_1 = 3 \frac{di_1}{dt} - 3 \frac{di_2}{dt} = -3 \frac{di_2}{dt} = -24 \cos 4t \text{ V}$

4. (C) $v_2 = 4 \frac{di_2}{dt} - 3 \frac{di_1}{dt} = -3 \frac{di_1}{dt} = 6e^{-2t} \text{ V}$

5. (A) $v_1 = 2 \frac{di_1}{dt} - 2 \frac{di_2}{dt} = 2 \frac{di_1}{dt} = -24 \sin 4t \text{ V}$

$v_2 = -3 \frac{di_2}{dt} + 2 \frac{di_1}{dt} = 2 \frac{di_1}{dt} = -24 \sin 4t \text{ V}$

6. (D) $v_1 = 2 \frac{di_1}{dt} - 2 \frac{di_2}{dt} = -2 \frac{di_2}{dt} = -24 \cos 3t \text{ V}$

$v_2 = 3 \frac{di_2}{dt} + 2 \frac{di_1}{dt} = -3 \frac{di_2}{dt} = -36 \cos 3t \text{ V}$

7. (A) $v_1 = 2 \frac{di_1}{dt} + 1 \frac{di_2}{dt}$
 $= -18 \sin t + 12 \cos t = 6(2 \cos t - 3 \sin t) \text{ V}$

8. (A) $v_2 = 2 \frac{di_2}{dt} + 1 \frac{di_1}{dt}$
 $= 24 \cos 3t - 9 \sin 3t = 3(8 \cos 3t - 3 \sin 3t) \text{ V}$

9. (A) $v_1 = 3 \frac{di_1}{dt} - 3 \frac{di_2}{dt}$
 $= 45 \cos 3t + 27 \sin 3t = 9(5 \cos 3t + 3 \sin 3t) \text{ V}$

10. (D) $v_2 = -4 \frac{di_2}{dt} + 3 \frac{di_1}{dt}$
 $= 36 \sin 3t + 45 \cos 3t = 9(4 \sin 3t + 5 \cos 3t) \text{ V}$

11. (A) $W = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2$

At $t = 0$, $i_1 = 4 \cos(-20^\circ) = 4.7 \text{ mA}$

$i_2 = 20 \cos(-20^\circ) = 18.8 \text{ mA}$,

$M = 0.6 \sqrt{2.5 \times 0.4} = 0.6$

$W = \frac{1}{2} (2.5)(4.7)^2 + \frac{1}{2} (0.4)(18.8)^2 + 0.6(4.7)(18.8)$

$= 151.3 \mu\text{J}$

12. (C) $L_{eq} = L_1 + L_2 + 2M = 7 \text{ H}$

$$13. (A) L_{eq} = L_1 + L_2 - 2M = 4 + 2 - 2 \times 2 = 2 \text{ H}$$

$$14. (C) L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} = \frac{24 - 16}{6 + 4 - 8} = 4 \text{ H}$$

$$15. (A) L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M} = \frac{8 - 4}{6 + 4} = 0.4 \text{ H}$$

$$16. (C) L_1 + L_2 + 2M = 7, L_1 + L_2 - 2M = 1.8$$

$$\Rightarrow L_1 + L_2 = 4.4, M = 1.3$$

$$\frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} = 0.5, L_1 L_2 - 1.3^2 = 0.5 \times 1.8$$

$$L_1 L_2 = 2.59, (L_1 - L_2)^2 = 4.4^2 - 4 \times 2.59 = 9$$

$$L_1 - L_2 = 3, L_1 = 3.7, L_2 = 0.7$$

$$17. (D) L_{eq} = L_1 - \frac{M^2}{L_2} = 4 - \frac{4}{2} = 2 \text{ H}$$

$$18. (B) L_{eq} = L_1 - \frac{M^2}{L_2} = 5 - \frac{9}{3} = 2 \text{ H}$$

19. (A)

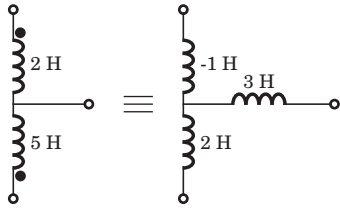


Fig. S.1.9.19

$$20. (D) V_{L1} = 1sI + 1sI = 2sI$$

$$V_{L2} = 2sI + 1sI - 2sI = sI,$$

$$V_{L3} = 3sI - 2sI = sI$$

$$V_L = V_{L1} + V_{L2} + V_{L3} = 4sI \Rightarrow L_{eq} = 4 \text{ H}$$

21. (B) Let I_1 be the current through 4 H inductor and I_2 and I_3 be the current through 3 H, and 2 H inductor respectively

$$I_1 = I_2 + I_3, V_2 = V_3$$

$$3sI_2 + 3sI_1 = 2sI_3 + 2sI_1$$

$$\Rightarrow 3I_2 + I_1 = 2I_3 \Rightarrow 4I_2 = I_3$$

$$\Rightarrow I_2 = \frac{I_1}{5}, I_3 = \frac{4}{5}I_1$$

$$V = 4sI_1 + 3sI_2 + 2sI_3 + 3sI_2 + 3sI_1$$

$$= 7sI_1 + \frac{6s}{5}I_1 + \frac{2 \times 4s}{5}I_1$$

$$V = \frac{49}{5}sI_1, L_{eq} = \frac{49}{5} \text{ H}$$

$$22. (C) v_{AG} = 20 \frac{d(6t)}{dt} + 4 \frac{d(15t)}{dt} = 180 \text{ V}$$

$$23. (B) v_{BG} = 3 \frac{d(15t)}{dt} + 4 \frac{d(6t)}{dt} - 6 \frac{d(6t)}{dt} = 33 \text{ V}$$

$$24. (C) v_{CG} = -6 \frac{d(6t)}{dt} = -36 \text{ V}$$

$$25. (B) Z = Z_{11} + \frac{\omega^2 M^2}{Z_{22}}$$

$$= 4 + j(50) \left(\frac{1}{10} \right) + \frac{(50)^2 \left(\frac{1}{5} \right)^2}{5 + j(50) \frac{1}{2}}$$

$$= 4.77 + j1.15 \Omega$$

$$26. (B) V_s = j(0.8)10(12 \angle 0) - j(0.2)(10)(2 \angle 0)$$

$$+ [3 + j(0.5)(10)](12 \angle 0 + 2 \angle 0)$$

$$= 9.6 + j21.6 = 26.64 \angle 66.04^\circ \text{ V}$$

$$27. (A) [j(100\pi)(2) + 10]I_2 + j(100\pi)(0.4)(2 \angle 0) = 0$$

$$\Rightarrow I_2 = -0.4 - j0.0064,$$

$$V_o = 10I_2 = -4 - j0.064$$

$$= 4 \angle -179.1^\circ$$

$$\Rightarrow v_o = 4 \cos(100\pi t - 179.1^\circ) \text{ V}$$

$$28. (B) 30 \angle 30^\circ = I(-j6 + j8 - j4 + j12 - j4 + 10)$$

$$\Rightarrow I = \frac{30 \angle 30^\circ}{(10 + j6)} = 2.57 - j0.043$$

$$V_o = I(j12 - j4 + 10)$$

$$= (2.57 - j0.043)(10 + 8j)$$

$$= 26.067 + j20.14 = 32.9 \angle 37.7^\circ \text{ V}$$

29. (A)

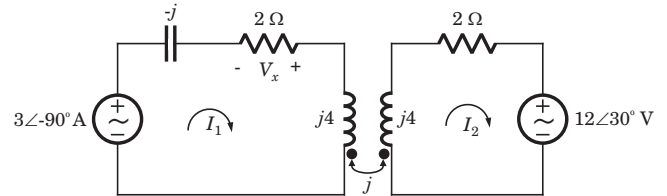


Fig. S.1.9.29

$$(-j + 2 + j4)I_1 - jI_2 = -j3$$

$$(j4 + 2)I_2 - jI_1 = -12 \angle 30^\circ \text{ V}$$

$$I_1 = -1.45 - j0.56,$$

$$V_x = -2I_1 = 2.9 + j1.12$$

$$= 3.11 \angle 21.12^\circ \text{ V}$$

30. (D)

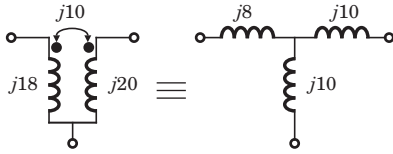


Fig. S1.9.30

$$Z_{eq} = 10 + j8 + \frac{(j14)(j10 + 2 - j6)}{j14 + j10 + 2 - j6}$$

$$= 11.2 + j11.2 \Omega$$

31. (C) $Z_{in} = (-j6) \parallel (Z_o)$

$$Z_o = j20 + \frac{(12)^2}{(j30 + j5 - j2 + 4)} = 0.52 + j15.7$$

$$Z_{in} = \frac{(-j6)(0.52 + j15.7)}{(-j6 + 0.52 + j15.7)} = 0.20 - j9.7 \Omega$$

32. (D) $M = k\sqrt{L_1 L_2}$, $M^2 = 160 \times 10^{-12}$

$$Z_{in} = j\omega L_1 + \frac{\omega^2 M^2}{Z_L + j\omega L_2}$$

$$= j250 \times 10^3 \times 2 \times 10^{-6} + \frac{(250 \times 10^3)^2 \times 160 \times 10^{-12}}{2 + j10 + j \times 250 \times 10^3 \times 80 \times 10^{-6}}$$

$$Z_{in} = 0.02 + j0.17 \Omega$$

33. (D)

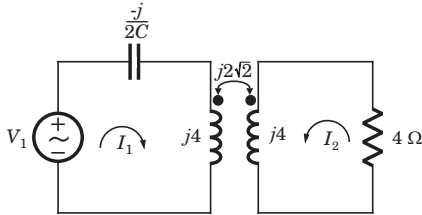


Fig. S1.9.33

$$V_1 = -\frac{jI_1}{2C} + j4I_1 + j2\sqrt{2}I_2$$

$$0 = (4 + 4j)I_2 + j2\sqrt{2}I_1$$

$$\Rightarrow I_2 = \frac{-j\sqrt{2}I_1}{2(1 + j)}$$

$$\frac{V_1}{I_1} = \frac{-j}{2C} + j4 + \frac{2}{1 + j} = \frac{-j + j8C + 2C - j2C}{2C}$$

$$Z_{in} = \frac{-j + j8C + 2C - j2C}{2C}$$

$$\text{Im}(Z_{in}) = 0 \Rightarrow -j + j8C - j2C = 0$$

$$\Rightarrow C = \frac{1}{6}$$

34. (A) $j30 - \frac{3j}{1000C} = 0$, $C = 100 \mu\text{F}$

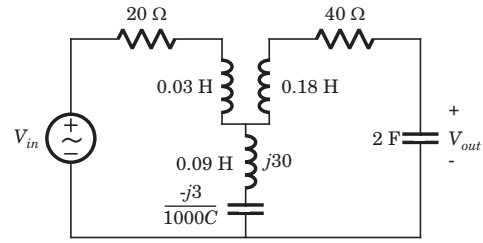


Fig. P1.9.34

35. (D) The π equivalent circuit of coupled coil is shown in fig. S1.9.35

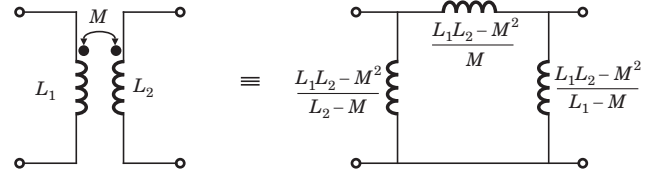


Fig. S1.9.35

$$\frac{L_1 L_2 - M^2}{M} = \frac{\sqrt{L_1 L_2}(1 - k^2)}{k} = \frac{\sqrt{0.12 \times 0.27}(10.5^2)}{0.5} = 0.27$$

Output is zero if $\frac{-j}{0.27\omega} + jC\omega = 0$

$$C = \frac{1}{0.27\omega^2} = 33.33 \mu\text{F}$$

36. (C) Applying 1 V test source at ab terminal,

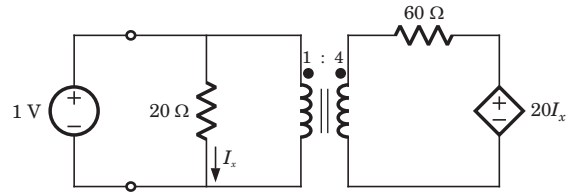


Fig. S1.9.36

$$V_{ab} = 1 \text{ V}, I_x = \frac{1}{20} = 0.05 \text{ A}, V_2 = 4 \text{ V},$$

$$4 = 60 I_2 + 20 \times 0.05 \Rightarrow I_2 = 0.05 \text{ A}$$

$$I_{in} = I_x + I_1 = I_x + 4I_2 = 0.25 \text{ A}$$

$$R_{TH} = \frac{1}{I_{in}} = 4 \Omega, V_{TH} = 0$$

37. (A) Impedance seen by $R_L = 10 \times 4^2 = 160 \Omega$

For maximum power $R_L = 160 \Omega$, $Z_o = 10 \Omega$

$$P_{Lmax} = \left(\frac{100}{10 + 10} \right)^2 \times 10 = 250 \text{ W}$$

38. (B) $I_2 = \frac{V_2}{8}$, $I_1 = \frac{I_2}{5} = \frac{V_2}{40}$, $V_1 = 5V_2$