

CHAPTER

1.6

THE RLC CIRCUITS

1. The natural response of an RLC circuit is described by the differential equation

$$\frac{d^2v}{dt^2} + 2\frac{dv}{dt} + v = 0, \quad v(0) = 10, \quad \frac{dv(0)}{dt} = 0.$$

The $v(t)$ is

- (A) $10(1+t)e^{-t}$ V (B) $10(1-t)e^{-t}$ V
(C) $10e^{-t}$ V (D) $10te^{-t}$ V

2. The differential equation for the circuit shown in fig. P1.6.2. is

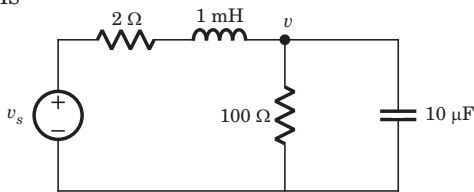


Fig. P1.6.2

- (A) $v''(t) + 3000v'(t) + 1.02 \times 10^8 v(t) = 10^8 v_s(t)$
(B) $v''(t) + 1000v'(t) + 1.02 \times 10^8 v(t) = 10^8 v_s(t)$
(C) $\frac{v''(t)}{10^8} + \frac{2v'(t)}{10^5} + 1.02v(t) = v_s(t)$
(D) $\frac{v''(t)}{10^8} + \frac{2v'(t)}{10^5} + 1.98v(t) = v_s(t)$

3. The differential equation for the circuit shown in fig. P1.6.3 is

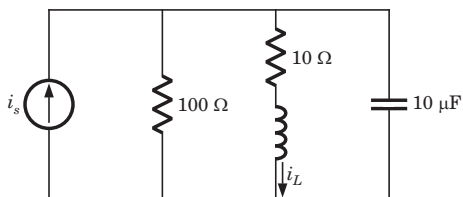


Fig. P1.6.3

- (A) $i_L''(t) + 1100i_L'(t) + 11 \times 10^8 i_L(t) = 10^8 i_s(t)$
(B) $i_L''(t) + 1100i_L'(t) + 11 \times 10^8 i_L(t) = 10^8 i_s(t)$
(C) $\frac{i_L''(t)}{10^8} + \frac{11i_L'(t)}{10^4} + 11i_L(t) = i_s(t)$
(D) $\frac{i_L''(t)}{10^8} + \frac{11i_L'(t)}{10^4} + 11i_L(t) = i_s(t)$

4. In the circuit of fig. P1.6.4 $v_s = 0$ for $t > 0$. The initial condition are $v(0) = 6$ V and $dv(0)/dt = -3000$ V/s. The $v(t)$ for $t > 0$ is

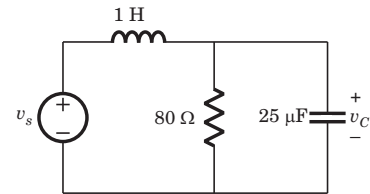


Fig. P1.6.4

- (A) $-2e^{-100t} + 8e^{-400t}$ V (B) $6e^{-100t} + 8e^{-400t}$ V
(C) $6e^{-100t} - 8e^{-400t}$ V (D) None of the above

5. The circuit shown in fig. P1.6.5 has been open for a long time before closing at $t = 0$. The initial condition is $v(0) = 2$ V. The $v(t)$ for $t > 0$ is

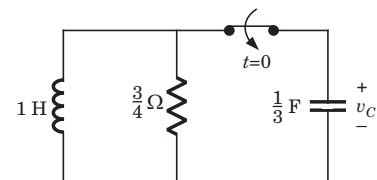


Fig. P1.6.5

- (A) $5e^{-t} - 7e^{-3t}$ V (B) $7e^{-t} - 5e^{-3t}$ V
(C) $-e^{-t} + 3e^{-3t}$ V (D) $3e^{-t} - e^{-3t}$ V

Statement for Q.6–7:

Circuit is shown in fig. P.1.6. Initial conditions are $i_1(0) = i_2(0) = 11$ A

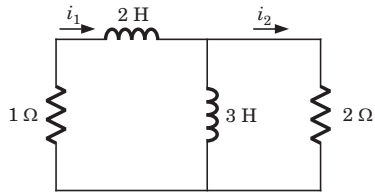


Fig. P.1.6.6–7

6. $i_1(1\text{ s}) = ?$

- (A) 0.78 A (B) 1.46 A
(C) 2.56 A (D) 3.62 A

7. $i_2(1\text{ s}) = ?$

- (A) 0.78 A (B) 1.46 A
(C) 2.56 A (D) 3.62 A

8. $v_C(t) = ?$ for $t > 0$

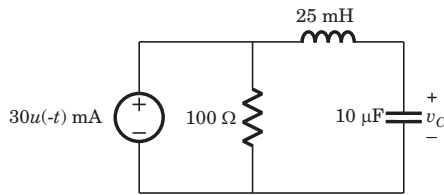


Fig. P.1.6.8

- (A) $4e^{-1000t} - e^{-2000t}$ V (B) $(3 + 6000t)e^{-2000t}$ V
(C) $2e^{-1000t} + e^{-2000t}$ V (D) $(3 - 6000t)e^{-2000t}$ V

9. The circuit shown in fig. P.1.6.9 is in steady state with switch open. At $t=0$ the switch is closed. The output voltage $v_C(t)$ for $t > 0$ is

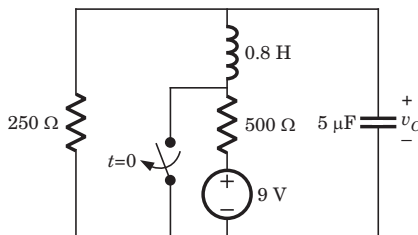


Fig. P.1.6.9

- (A) $-9e^{-400t} + 12e^{-300t}$
(B) $e^{-400t}[3\cos 300t + 4\sin 300t]$
(C) $e^{-300t}[3\cos 400t + 4\sin 300t]$
(D) $e^{-300t}[3\cos 400t + 2.25\sin 300t]$

10. The switch of the circuit shown in fig. P.1.6.10 is opened at $t=0$ after long time. The $v(t)$, for $t > 0$ is

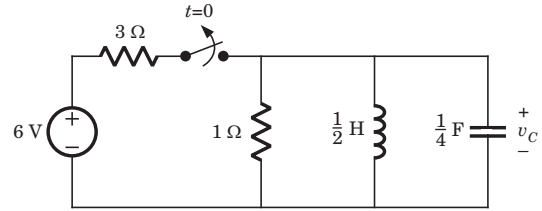


Fig. P.1.6.10

- (A) $4e^{-2t} \sin 2t$ V (B) $-4e^{-2t} \sin 2t$ V
(C) $4e^{-2t} \cos 2t$ V (D) $-4e^{-2t} \cos 2t$ V

11. In the circuit of fig. P.1.6.23 the switch is opened at $t=0$ after long time. The current $i_L(t)$ for $t > 0$ is

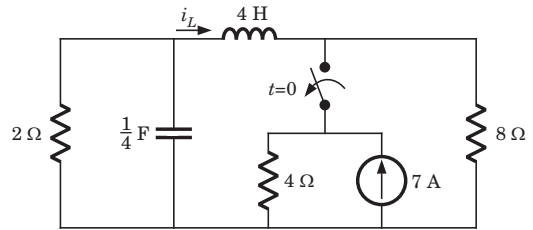


Fig. P.1.6.11

- (A) $e^{-2t}(2\cos t + 4\sin t)$ A (B) $e^{-2t}(3\sin t - 4\cos t)$ A
(C) $e^{-2t}(-4\sin t + 2\cos t)$ A (D) $e^{-2t}(2\sin t - 4\cos t)$ A

Statement for Q.12–14:

In the circuit shown in fig. P.1.6.12–14 all initial condition are zero.

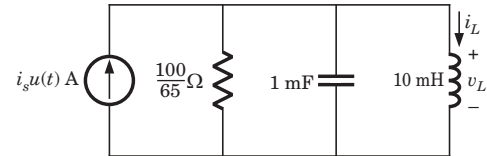


Fig. P.1.5.12-14

12. If $i_s(t) = 1$ A, then the inductor current $i_L(t)$ is

- (A) 1 A (B) t A
(C) $t + 1$ A (D) 0 A

13. If $i_s(t) = 0.5t$ A, then $i_L(t)$ is

- (A) $0.5t + 3.25 \times 10^{-3}$ A (B) $2t - 3250$ A
(C) $0.5t - 0.25 \times 10^{-3}$ A (D) $2t + 3250$ A

14. If $i_s(t) = 2e^{-250t}$ A then $i_L(t)$ is

- (A) $\frac{4000}{3}te^{-250t}$ A (B) $\frac{4000}{3}e^{-250t}$ A
(C) $\frac{200}{7}e^{-250t}$ A (D) $\frac{200}{7}te^{-250t}$ A

15. The forced response for the capacitor voltage $v_c(t)$ is

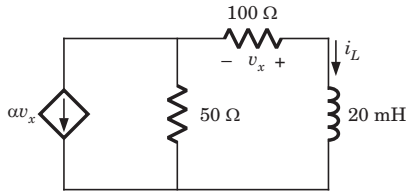


Fig. P1.6.15

- (A) $0.2t + 1.17 \times 10^{-3} \text{ V}$ (B) $0.2t - 1.17 \times 10^{-3} \text{ V}$
 (C) $1.17 \times 10^{-3}t - 0.2 \text{ V}$ (D) $1.17 \times 10^{-3}t + 0.2 \text{ V}$

16. For a RLC series circuit $R = 20 \Omega$, $L = 0.6 \text{ H}$, the value of C will be
 [CD =critically damped, OD =over damped, UD =under damped].

CD	OD	UD
(A) $C = 6 \text{ mF}$	$C > 6 \text{ mF}$	$C < 6 \text{ mF}$
(B) $C = 6 \text{ mF}$	$C < 6 \text{ mF}$	$C > 6 \text{ mF}$
(C) $C > 6 \text{ mF}$	$C = 6 \text{ mF}$	$C < 6 \text{ mF}$
(D) $C < 6 \text{ mF}$	$C = 6 \text{ mF}$	$C > 6 \text{ mF}$

17. The circuit shown in fig. P1.6.17 is critically damped. The value of R is

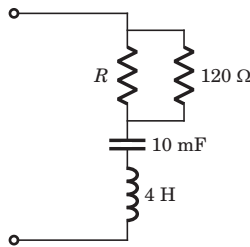


Fig. P1.6.17

- (A) 40Ω (B) 60Ω
 (C) 120Ω (D) 180Ω

18. The step response of an RLC series circuit is given by

$$\frac{d^2 i(t)}{dt^2} + \frac{2di(t)}{dt} + 5i(t) = 10, i(0^+) = 2, \frac{di(0^+)}{dt} = 4.$$

The $i(t)$ is

- (A) $1 + e^{-t} \cos 4t \text{ A}$ (B) $4 - 2e^{-t} \cos 4t \text{ A}$
 (C) $2 + e^{-t} \sin 4t \text{ A}$ (D) $10 + e^{-t} \sin 4t \text{ A}$

19. In the circuit shown in fig. P 1.5.19 $v(t)$ for $t > 0$ is

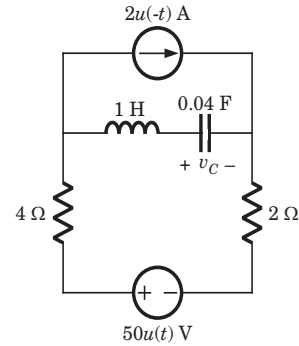


Fig. P1.6.19

- (A) $50 - (46.5 \sin 3t + 62 \cos 3t)e^{-4t} \text{ V}$
 (B) $50 + (46.5 \sin 3t + 62 \cos 3t)e^{-4t} \text{ V}$
 (C) $50 + (62 \cos 4t + 46.5 \sin 4t)e^{-3t} \text{ V}$
 (D) $50 - (62 \cos 4t + 46.5 \sin 4t)e^{-3t} \text{ V}$

20. In the circuit of fig. P1.6.20 the switch is closed at $t = 0$ after long time. The current $i(t)$ for $t > 0$ is

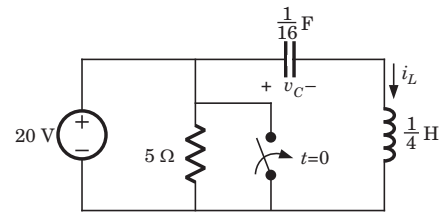


Fig. P1.6.20

- (A) $-10 \sin 8t \text{ A}$ (B) $10 \sin 8t \text{ A}$
 (C) $-10 \cos 8t \text{ A}$ (D) $10 \cos 8t \text{ A}$

21. In the circuit of fig. P1.6.21 switch is moved from 8 V to 12 V at $t = 0$. The voltage $v(t)$ for $t > 0$ is

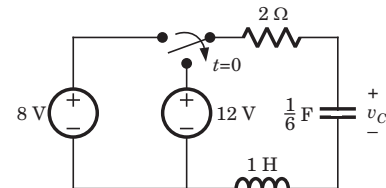


Fig. P1.6.21

- (A) $12 - (4 \cos 2t + 2 \sin 2t)e^{-t} \text{ V}$
 (B) $12 - (4 \cos 2t + 8 \sin 2t)e^{-t} \text{ V}$
 (C) $12 + (4 \cos 2t + 8 \sin 2t)e^{-t} \text{ V}$
 (D) $12 + (4 \cos 2t + 2 \sin 2t)e^{-t} \text{ V}$

22. In the circuit of fig. P1.5.22 the voltage $v(t)$ is

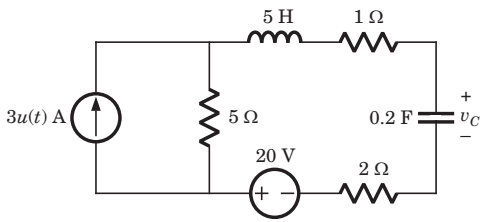


Fig. P1.6.22

- (A) $40 - (20 \cos 0.6t + 15 \sin 0.6t)e^{-0.8t}$ V
- (B) $35 + (15 \cos 0.6t + 20 \sin 0.6t)e^{-0.8t}$ V
- (C) $35 - (15 \cos 0.6t + 20 \sin 0.6t)e^{-0.8t}$ V
- (D) $35 - 15 \cos 0.6t e^{-0.8t}$ V

23. In the circuit of fig. P1.6.23 the switch is opened at $t=0$ after long time. The current $i(t)$ for $t > 0$ is

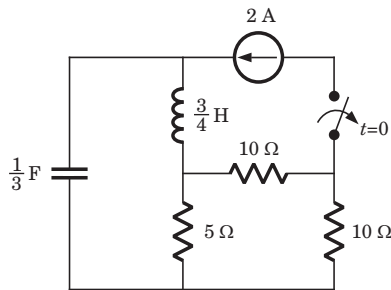


Fig. P1.6.23

- (A) $e^{-2.306t} + e^{-0.869t}$ A
- (B) $-e^{-2.306t} + 2e^{-0.869t}$ A
- (C) $e^{-4.431t} + e^{-0.903t}$ A
- (D) $2e^{-4.431t} - e^{-0.903t}$ A

24. In the circuit of fig. P1.6.24 switch is moved from position a to b at $t=0$. The $i_L(t)$ for $t > 0$ is

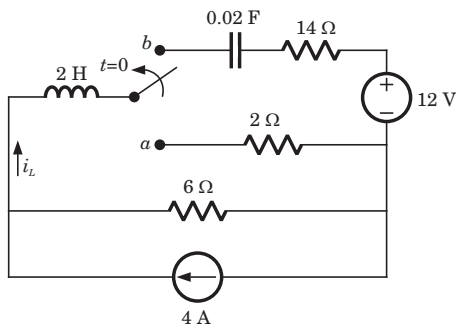


Fig. P1.6.24

- (A) $(4 - 6t)e^{4t}$ A
- (B) $(3 - 6t)e^{-4t}$ A
- (C) $(3 - 9t)e^{-5t}$ A
- (D) $(3 - 8t)e^{-5t}$ A

25. In the circuit shown in fig. P1.6.25 a steady state has been established before switch closed. The $i(t)$ for $t > 0$ is

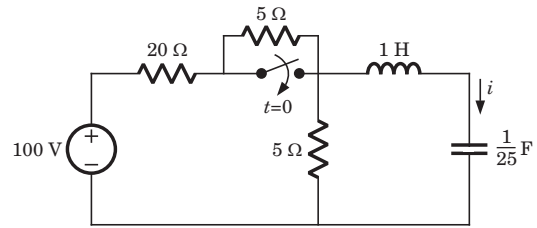


Fig. P1.6.25

- (A) $0.73e^{-2t} \sin 4.58t$ A
- (B) $0.89e^{-2t} \sin 6.38t$ A
- (C) $0.73e^{-4t} \sin 4.58t$ A
- (D) $0.89e^{-4t} \sin 6.38t$ A

26. The switch is closed after long time in the circuit of fig. P1.6.26. The $v(t)$ for $t > 0$ is

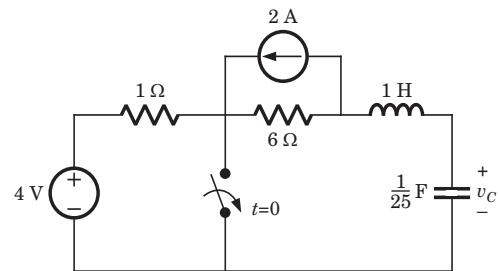


Fig. P1.6.26

- (A) $-8 + 6e^{-3t} \sin 4t$ V
- (B) $-12 + 4e^{-3t} \cos 4t$ V
- (C) $-12 + (4 \cos 4t + 3 \sin 4t)e^{-3t}$ V
- (D) $-12 + (4 \cos 4t + 6 \sin 4t)e^{-3t}$ V

27. $i(t) = ?$

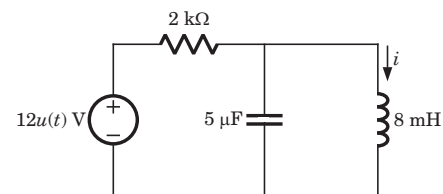


Fig. P1.6.27

- (A) $6 - (6 \cos 500t + 6 \sin 5000t)e^{-50t}$ mA
- (B) $8 - (8 \cos 500t + 0.06 \sin 5000t)e^{-50t}$ mA
- (C) $6 - (6 \cos 5000t + 0.06 \sin 5000t)e^{-50t}$ mA
- (D) $6e^{-50t} \sin 5000t$ mA

28. In the circuit of fig. P1.6.28 $i(0) = 1$ A and $v(0) = 0$. The current $i(t)$ for $t > 0$ is

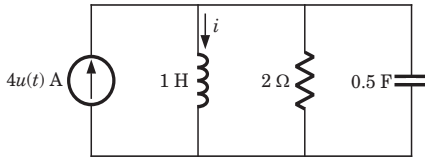


Fig. P1.6.28

- (A) $4 + 6.38 e^{-0.5t}$ A (B) $4 - 6.38 e^{-0.5t}$ A
 (C) $4 + (3 \cos 1.32t + 1.13 \sin 1.32t)e^{-0.5t}$ A
 (D) $4 - (3 \cos 1.32t + 1.13 \sin 1.32t)e^{-0.5t}$ A

29. In the circuit of fig. P1.6.29 a steady state has been established before switch closed. The $v_o(t)$ for $t > 0$ is

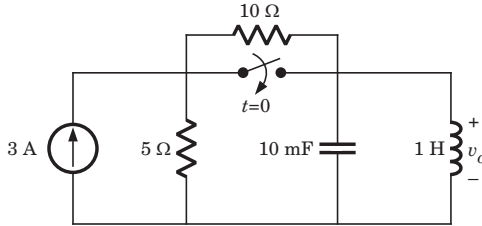


Fig. P1.6.29

- (A) $100te^{-10t}$ V (B) $200te^{-10t}$ V
 (C) $400te^{-50t}$ V (D) $800te^{-50t}$ V

30. In the circuit of fig. P1.6.30 a steady state has been established before switch closed. The $i(t)$ for $t > 0$ is

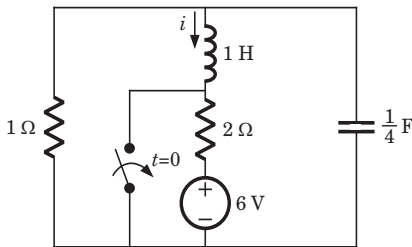


Fig. P1.6.30

- (A) $2e^{-2t} \sin 2t$ A (B) $-e^{-2t} \sin 2t$ A
 (C) $-2(1-t)e^{-2t}$ A (D) $2(1-t)e^{-2t}$ A

31. In the circuit of fig. P1.6.31 a steady state has been established. The $i(t)$ for $t > 0$ is

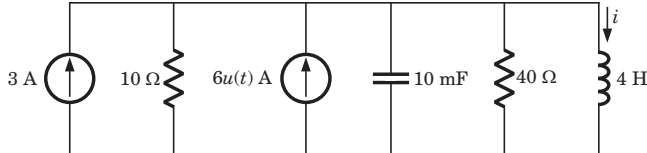


Fig. P1.6.31

- (A) $9 + 2e^{-10t} - 8e^{-2.5t}$ A (B) $9 - 8e^{10t} + 2e^{-2.5t}$ A
 (C) $9 + (2 \cos 10t + \sin 10t)e^{-2.5t}$ A
 (D) $9 + (\cos 10t + 2 \sin 10t)e^{-2.5t}$ A

SOLUTIONS

1. (A) $s^2 + 2s + 1 = 0 \Rightarrow s = -1, -1$,

$$v(t) = (A_1 + A_2 t)e^{-t}$$

$$v(0) = 10 \text{ V}, \quad \frac{dv(0)}{dt} = 0 = -1A_1 + A_2$$

$$A_1 = A_2 = 10$$

2. (A) $i_L = \frac{v}{100} + 10 \times 10^{-6} \frac{dv}{dt}$

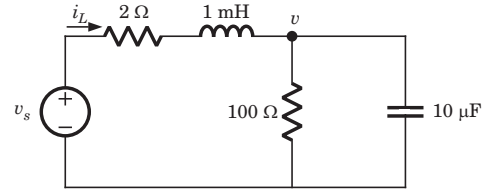


Fig. S1.6.2

$$v_s = 2i_L + 10^{-3} \frac{di_L}{dt} + v$$

$$= 2 \left(\frac{v}{100} + 10^{-6} \times 10^{-t} \frac{dv}{dt} \right) + 10^{-3} \left(\frac{1}{100} \frac{dv}{dt} + 10 \times 10^{-6} \frac{d^2 v}{dt^2} \right) + v$$

$$10^8 v_s(t) = v''(t) + 3000v'(t) + 102v(t)$$

3. (C) $i_s = \frac{v_C}{100} + i_L + 10\mu \frac{dv_C}{dt}$

$$v_C = 10i_L + 10^{-3} \frac{di_L}{dt}$$

$$i_s = 0.1i_L + 10^{-5} \frac{di_L}{dt} + i_L + 10^{-5} \frac{d}{dt} (10i_L + 10^{-3} \frac{di_L}{dt})$$

$$= 0.1i_L + 10^{-5} \frac{di_L}{dt} + i_L + 10^{-4} \frac{di_L}{dt} + 10^{-8} \frac{d^2 i_L}{dt^2}$$

$$\Rightarrow \frac{i_L''(t)}{10^8} + \frac{1.1}{10^4} i_L'(t) + 1.1i_L(t) = i_s(t)$$

4. (A) $\frac{v}{80} + 25\mu \frac{dv}{dt} + \int (v - v_s) dt = 0$

$$\Rightarrow \frac{d^2 v}{dt^2} + 500 \frac{dv}{dt} + 40000 = 0$$

$$s^2 + 500s + 40000 = 0$$

$$\Rightarrow s = -100, -400,$$

$$v(t) = Ae^{-100t} + Be^{-400t}$$

$$A + B = 6, -100A - 400B = -3000 \Rightarrow B = 8, A = -2$$

5. (C) The characteristic equation is $s^2 + \frac{s}{RC} + \frac{1}{LC} = 0$

After putting the values, $s^2 + 4s + 3 = 0$

$$v(t) = Ae^{-t} + Be^{-3t},$$

$$v(0^+) = 2 \text{ V} \Rightarrow A + B = 2$$

$$i_L(0^+) = 0 \Rightarrow i_R(0) = \frac{2}{3/4} = \frac{8}{3},$$

$$-C \frac{dv(0^+)}{dt} = \frac{8}{3} \Rightarrow \frac{dv(0^+)}{dt} = -8,$$

$$-A - 3B = -8, \quad B = 3, \quad A = -1$$

$$6. \text{ (D) } i_1 + 5 \frac{di_1}{dt} - 3 \frac{di_2}{dt} = 0,$$

$$2i_2 + \frac{3di_2}{dt} - 3 \frac{di_1}{dt} = 0$$

$$(1 + 5s)i_1 - 3si_2 = 0, \quad -3si_1 + (2 + 3s)i_2 = 0$$

$$(1 + 5s)i_1 - \frac{(3s)(3s)i_1}{2 + 3s} = 0$$

$$\Rightarrow 6s^2 + 13s + 2 = 0$$

$$\Rightarrow s = -\frac{1}{6}, -2$$

$$i_1 = A e^{-\frac{1}{6}t} + B e^{-2t}, \quad i(0) = A + B = 11$$

In differential equation putting $t=0$ and solving

$$\frac{di_1(0^+)}{dt} = -\frac{33}{2}, \quad \frac{di_2(0^+)}{dt} = -\frac{143}{6}$$

$$-\frac{A}{6} - 2B = -\frac{33}{2}, \Rightarrow A = 3, B = 8,$$

$$i_1 = 3e^{-\frac{t}{6}} + 8e^{-2t},$$

$$i_1(1 \text{ s}) = 3e^{-\frac{1}{6}} + 8e^{-2} = 3.62 \text{ A}$$

$$7. \text{ (A) } i_2 = C e^{\frac{t}{6}} + D e^{-2t}$$

$$i_2(0) = 11 = C + D, \quad \frac{di_2(0)}{dt} = \frac{-143}{6} = -\frac{C}{6} - 2D$$

$$C = -1 \quad \text{and} \quad D = 12$$

$$i_2 = -e^{\frac{t}{6}} + 12e^{-2t} \text{ A}, \quad i_2(1 \text{ s}) = e^{\frac{1}{6}} + 12e^{-2} = 0.78 \text{ A}$$

$$8. \text{ (B) } v_C(0^+) = 30 \text{ m} \times 100 = 3 \text{ V}$$

$$C \frac{dv_C(0^-)}{dt} = i_L(0^-) = 0 = i_L(0^+) = C \frac{dv_C(0^+)}{dt}$$

$$s^2 + \frac{100}{25 \times 10^{-3}} s + \frac{1}{25 \times 10^{-3} \times 10 \times 10^{-6}} = 0$$

$$\Rightarrow s = -2000, -2000$$

$$v_C(t) = (A_1 + A_2 t) e^{-2000t}$$

$$\frac{dv_C(t)}{dt} = A_2 e^{-2000t} + (A_1 + A_2 t) e^{-2000t} (-2000)$$

$$v_C(0^+) = A_1 = 3, \quad \frac{dv_C(0)}{dt} = A_2 - 2000 \times 3 = 0$$

$$\Rightarrow A_2 = 6000$$

$$9. \text{ (B) } v_C(0^+) = 3 \text{ V}, \quad i_L(0^+) = -12 \text{ mA}$$

$$\frac{v_C}{250} + i_L + 5 \times 10^{-6} \frac{dv_C}{dt} = 0$$

$$\frac{3}{250} - 12 \text{ m} + 5 \times 10^{-6} \frac{dv_C(0^+)}{dt} = 0 \Rightarrow \frac{dv_C(0^+)}{dt} = 0$$

$$s^2 + \frac{s}{250 \times 5 \times 10^{-6}} + \frac{1}{0.8 \times 5 \times 10^{-6}} = 0$$

$$\Rightarrow s^2 + 800s + 25 \times 10^4 = 0$$

$$\Rightarrow s = -400 \pm j300$$

$$v_C(t) = e^{-400t} (A_1 \cos 300t + A_2 \sin 300t)$$

$$A_1 = 3, \quad \frac{dv_C(0)}{dt} = -400A_1 + 300A_2, \quad A_2 = 4$$

$$10. \text{ (B) } v(0^+) = 0, \quad i_L(0^+) = 2 \text{ A}, \quad \frac{1}{4} \frac{dv_C(0^+)}{xdt} = -2$$

$$s^2 + 4s + 8 = 0 \Rightarrow s = -2 \pm j2$$

$$v_C(t) = e^{-2t} (A_1 \cos 2t + A_2 \sin 2t)$$

$$A_1 = 0, \quad \frac{dv_C(0^+)}{dt} = -8 = -2(0 + 0) + (0 + 2A_2), \quad A_2 = -4$$

$$11. \text{ (D) } i_L(0^+) = -4, \quad v_C(0^+) = 8 \text{ V}$$

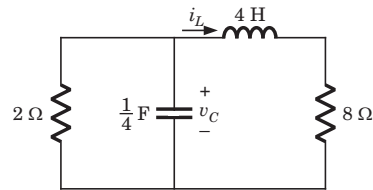


Fig. S1.6.11

$$4 \frac{di_L(0^+)}{dt} = 8 - (-4) \times 8 \Rightarrow \frac{di_L(0^+)}{dt} = 10$$

$$\frac{s}{4} v_C + \frac{1}{2} v_C + i_L = 0, \quad v_C = 4si_L + 8i_L$$

$$s^2 i_L + 4si_L + 5 = 0, \quad s = -2 \pm j$$

$$i_L(t) = e^{-2t} (A_1 \cos t + A_2 \sin t)$$

$$A_1 = -4, \quad \frac{di_L(0^+)}{dt} = 10 = -2(A_1 + 0) + A_2, \quad A_2 = 2$$

$$12. \text{ (A) } i_s = \frac{v}{100/65} + 10^{-3} \frac{dv}{dt} + i_L, \quad v = 10 \times 10^{-3} \frac{di_L}{dt}$$

$$i_s = \frac{65}{100} (10 \times 10^{-3}) \frac{di_L}{dt} + 10^{-3} (10 \times 10^{-3}) \frac{d^2 i_L}{dt^2} + i_L = 0$$

$$\frac{d^2 i_L}{dt^2} + 650 \frac{di_L}{dt} + 10^5 i_L = 10^5 i_s$$

$$\text{Trying } i_L(t) = B$$

$$0 + 0 + 10^5 B = 10^5, \quad B = 1, \quad i_L = 1 \text{ A}$$

$$13. \text{ (A) Trying } i_L(t) = At + B,$$

$$0 + 650A + (At + B)10^5 = 10^5(0.5t), \quad A = 0.5$$

$$\frac{di(0^+)}{dt} = \frac{-16}{3} = -4.431 \text{ A} - 0.903B$$

$$A = 1, B = 1$$

$$24. (C) v_C(0) = 0, \quad i_L(0) = \frac{4 \times 6}{6 + 2} = 3$$

$$0.02 \frac{dv_C(0)}{dt} = i_L(0) = 3 \Rightarrow \frac{dv_C(0)}{dt} = 150$$

$$\alpha = \frac{6 + 14}{2 \times 2} = 5, \quad \omega_o = \frac{1}{\sqrt{2 \times 0.02}} = 5$$

$\alpha = \omega_o$ critically damped

$$v(t) = 12 + (A + Bt)e^{-5t}$$

$$0 = 12 + A, \quad 150 = -5A + B \Rightarrow A = -12, \quad B = 90$$

$$v(t) = 12 + (90t - 12)e^{-5t}$$

$$i_L(t) = 0.02(-5)e^{-5t}(90t - 12) + 0.02(90)e^{-5t} = (3 - 9t)e^{-5t}$$

$$25. (A) v(0^+) = \frac{100 \times 5}{5 + 5 + 20} = \frac{50}{3}, \quad i_L(0^+) = 0$$

$$i_f = 0 \text{ A}$$

$$\frac{di_L(0^+)}{dt} = 20 - \frac{50}{3} = \frac{10}{3}$$

$$\alpha = \frac{4}{2 \times 1} = 2, \quad \omega_o = \frac{1}{\sqrt{1 \times \frac{1}{25}}} = 5$$

$$s = -2 \pm \sqrt{4 - 25} = -2 \pm j4.58$$

$$i(t) = (A \cos 4.58t + B \sin 4.58t)e^{-2t}$$

$$26. (A) i_L(0^+) = 0, \quad v_L(0^+) = 4 - 12 = -8$$

$$\frac{1}{25} \frac{dv_L(0^+)}{dt} = i_L(0^+) = 0$$

$$\alpha = \frac{6}{2} = 3, \quad W_o = \frac{1}{\sqrt{1 \times 1/25}} = 5$$

$$\beta = -3 \pm \sqrt{9 - 25} = -3 \pm j4$$

$$v_1(t) = -12 + (A \cos 4t + B \sin 4t)e^{-3t}$$

$$v_L(0) = -8 = 12 + A, \quad \Rightarrow A = -4$$

$$\frac{dv_L(0)}{dt} = 0 = -3A + 4B, \quad \Rightarrow B = 3$$

$$27. (C) \alpha = \frac{1}{2RC} = \frac{1}{2 \times 2k \times 54} = 50$$

$$W_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{8m \times 5\mu}} = 5000$$

$\alpha < W_o$, underdamped response.

$$s = -50 \pm \sqrt{50^2 - 5000^2} = -50 \pm j5000$$

$$i(t) = 6 + (A \cos 5000t + B \sin 5000t)e^{-50t} \text{ mA}$$

$$i(0) = 6 = 6 + A, \quad \Rightarrow A = -6$$

$$\frac{di(0)}{dt} = -50A + 5000B = 0, \quad B = -0.06$$

$$28. (D) i(0^+) = 1 \text{ A}, \quad v(0^+) = \frac{Ldi(0^+)}{dt}$$

$$\alpha = \frac{1}{2 \times 2 \times 0.5} = 0.5, \quad W_o = \frac{1}{\sqrt{1 - 0.5}} = \sqrt{2}$$

$$s = -0.5 \pm \sqrt{0.5^2 - 2} = 0.5 \pm j1.323$$

$$i(t) = 4 + (A \cos 1.32t + B \sin 1.32t)e^{-0.5t}$$

$$1 = 4 + A, \quad \Rightarrow A = -3$$

$$\frac{di(0)}{dt} = 0 = 0.5A + 1.32B, \quad B = -1.13$$

$$29. (B) V_o(0^+) = 0, \quad i_L(0^+) = 1 \text{ A}$$

$$\frac{di_L(0^+)}{dt} = v_1(0) = 0$$

$$\alpha = \frac{1}{2 \times 5 \times 0.01} = 10, \quad W_o = \frac{1}{\sqrt{1 \times 0.01}} = 10$$

$\alpha = W_o$, so critically damped response

$$s = -10, -10$$

$$i(t) = 3(A + Bt)e^{-10t}, \quad i(0) = 1 = 3 + A$$

$$\frac{di(0^+)}{dt} = -10A + B$$

$$i_L(t) = 3 - (2 + 20t)e^{-10t}, \quad v_o = \frac{Ldi_L(t)}{dt} = 200te^{-10t}$$

$$30. (C) i(0^+) = \frac{-6}{1 + 2} = -2 \text{ A}, \quad v_c(0^+) = 2 \times 1 = 2 = \frac{di(0^+)}{dt}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 1 \times 0.25} = 2, \quad W_o = \frac{1}{\sqrt{LC}} = 2$$

$\alpha = W_o$, critically damped response

$$s = -2, -2$$

$$i(t) = (A + Bt)e^{-2t}, \quad A = -2$$

$$\frac{di(t)}{dt} = (-2 + Bt)e^{-2t}(-2) + (0 + B)e^{-2t}$$

$$\text{At } t = 0, \Rightarrow B = -2$$

$$31. (A) i(0^+) = 3 \text{ A}, \quad v_C(0^+) = 0 \text{ V} = \frac{4di(0^+)}{dt}$$

$$i_s = 9 \text{ A}, \quad R = 10 \parallel 40 = 8 \Omega$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 8 \times 0.01} = 6.25$$

$$W_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{4 \times 0.01}} = 5$$

$\alpha > W_o$, so overdamped response

$$s = -6.25 \pm \sqrt{6.25^2 - 25} = -10, -2.5$$

$$i(t) = 9 + Ae^{-10t} + Be^{-2.5t}$$

$$3 = 9 + A + B, \quad 0 = -10A - 2.5B$$

$$\text{On solving, } A = 2, B = -8$$
