


## ANALOG CIRCUITS TEST 4

Number of Questions: 25

Time: 60 min.

**Directions for questions 1 to 25:** Select the correct alternative from the given choices.

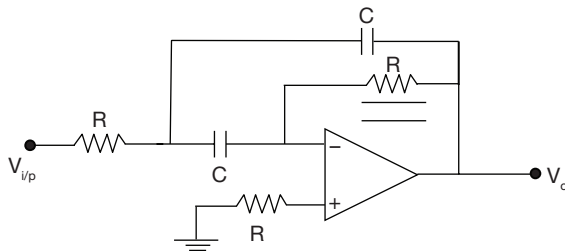
1. At higher frequency ( $>1\text{MHz}$ ), the phase shift of an RC-coupled amplifier is  
 (A) equal to  $180^\circ$  (B) above  $180^\circ$   
 (C) below  $180^\circ$  (D) None of the above
2. An amplifier with open loop voltage gain  $A_v = 800 \pm 50$  is available. It is required to have an amplifier whose gain varies by not more than  $\pm 0.5\%$ . Find reverse transmission factor  $\beta$  of the feedback network.  
 (A) 1.43% (B) 2.5%  
 (C) 4% (D) 3.7%
3. Below network represents a




- (A) low pass filter (B) high pass filter  
 (C) band pass filter (D) band stop filter
4. Match List-I with List-II where List-I contains type of feedback and List-II have input impedance ( $Z_{ip}$ ) and output impedance ( $Z_{op}$ )

| List-I             | List-II                                       |
|--------------------|-----------------------------------------------|
| (p) current series | (1) $Z_{ip}$ increases and $Z_{op}$ decreases |
| (q) current shunt  | (2) $Z_{ip}$ increases and $Z_{op}$ increases |
| (r) voltage series | (3) $Z_{ip}$ decreases and $Z_{op}$ decreases |
| (s) voltage shunt  | (4) $Z_{ip}$ decreases and $Z_{op}$ increases |

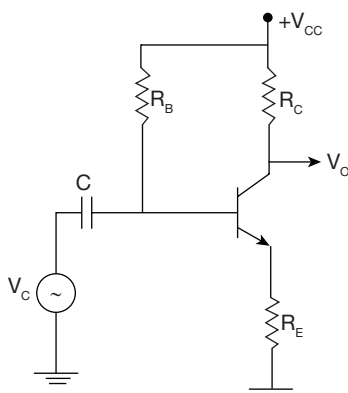- (A) p-2, q-4, r-1, s-3 (B) p-4, q-2, r-3, s-1  
 (C) p-3, q-1, r-2, s-4 (D) p-2, q-3, r-4, s-1
5. Below circuit configuration indicates which type of feedback connection?




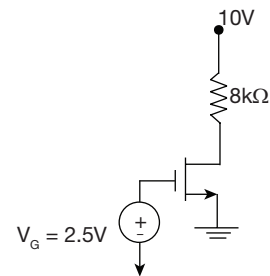- (A) Voltage series feedback  
 (B) Voltage shunt feedback  
 (C) Current series feedback  
 (D) Current shunt feedback
6. The cascode amplifier is a multistage configuration of  
 (A) CE-CC (B) CE-CB  
 (C) CC-CB (D) CB-CC
  7. For FET shown in below figure has  $V_{TN} = 1.5\text{V}$ ,  $k_n = 2\text{ mA/V}^2$ . The FET is in saturation and  $I_D = 1\text{mA}$  then small signal voltage gain  $A_v$  is




- (A) -64 (B) -32  
 (C) 16 (D) 48

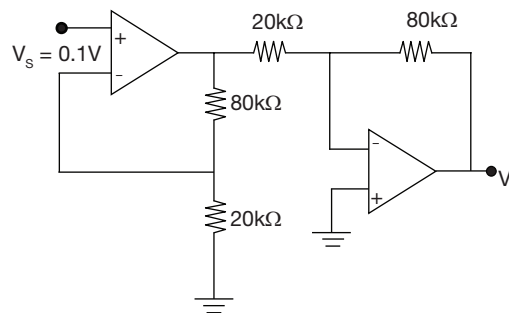8. Find out output voltage ( $V_o$ ), assume that the op-Amps in below circuit are ideal.




- (A) 2 V (B) 0.5 V  
 (C) -0.5 V (D) -2V

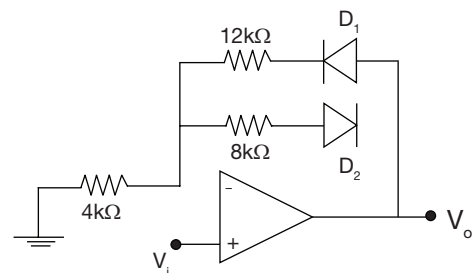9. Find output voltage  $V_o$  at  $V_i = 4\text{V}$  for below circuit. [Assume that diodes are ideal.]




- (A) -12V (B) 16V  
 (C) 4V (D) -8V

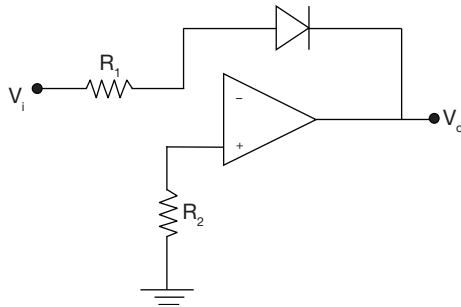
10. In below Op-Amp circuit, the output voltage ( $V_o$ ) for  $V_i > 0$ , is proportional to



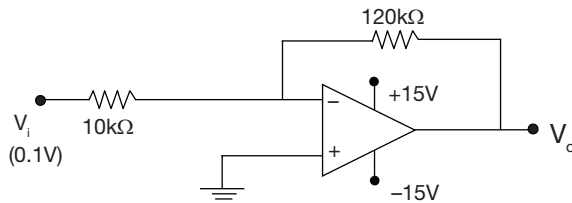
- (A)  $V_i$   
 (B)  $\sqrt{V_i}$   
 (C)  $\ln(k V_i)$   
 (D)  $e^{kV_i}$
11. Differential amplifier is invariably used in input stage of all Op-Amps. This is done to provide the Op-Amp with a very high
- (A) open-loop gain  
 (B) Bandwidth  
 (C) CMRR  
 (D) slew rate
12. If the frequency of operation is 0.5 MHz and Op-Amp slew rate is 0.8 V/ $\mu$ s. Then output  $V_o$  is



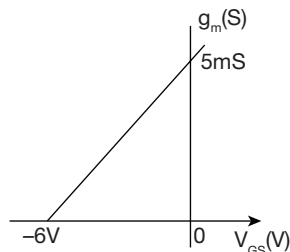- (A) more distorted  
 (B) 15V  
 (C) No distortion  
 (D) -15V
13. Plot  $g_m$  versus  $V_{GS}$  for the JFET, find drain current  $I_D$  at  $V_{GS} = -4V$




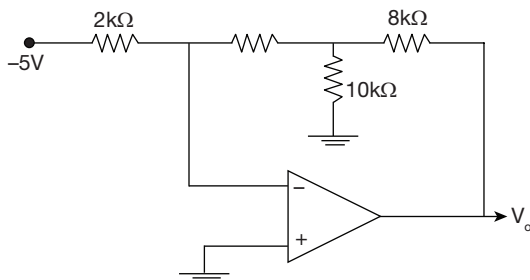- (A) 30 mA  
 (B) 20 mA  
 (C) 1.67 mA  
 (D) 15 mA
14. Output voltage of below circuit is




- (A) -40.5 V  
 (B) 12.5 V  
 (C) 42.5 V  
 (D) 35 V

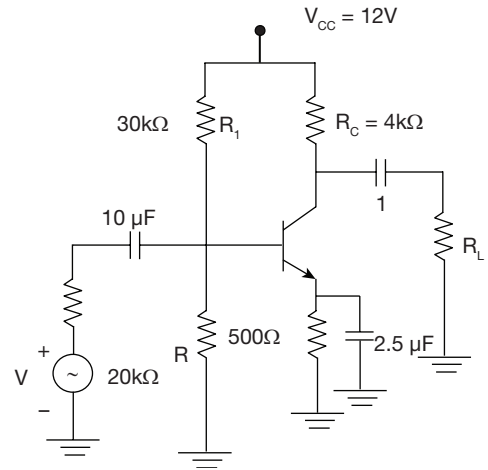15. Find  $f_\beta$  where junction capacitances are  $C_\pi = 25$  pF,  $C_\mu = 8$  pF,  $C_{ce} = 2$  pF and  $\beta = 150$ .




- (A) 9.1 MHz  
 (B) 11.13 MHz  
 (C) 30 MHz  
 (D) 20.5 MHz

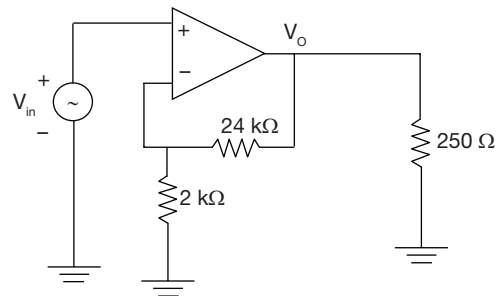16. An Op-amp having the following parameters is connected as a non inverting amplifier,  $A = 2 \times 10^5$ ,  $R_i = 5$  M $\Omega$ ,  $R_o = 150$   $\Omega$ ,  $f_o = 10$ Hz. Then output impedance after feedback ( $R_{of}$ ) is




- (A) 7.8 m $\Omega$   
 (B) 9.75 m $\Omega$   
 (C) 2.3 m $\Omega$   
 (D) 3.25 m $\Omega$

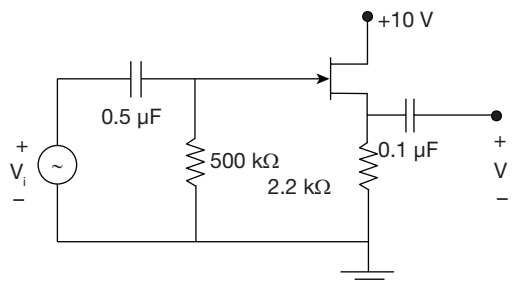17. A dc analysis of the source follower network has  $V_{GSQ} = -2.5$  V and  $I_{DQ} = 2.36$  mA. Then find voltage gain  $A_v$ . [ $I_{DSS} = 12$  mA,  $V_P = -5$  V,  $Y_{OS} = 74$   $\mu$ S]




- (A) 0.48  
 (B) 0.84  
 (C) 0.24  
 (D) 1.2

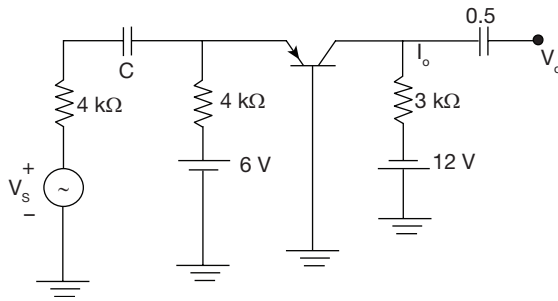18. For the common-base amplifier, output impedance is




[ $\because h_{ib} = 15 \Omega$ ,  $h_{rb} = 88.3 \times 10^{-6}$ ,  $h_{fb} = -0.9$ ,  $h_{ob} = 0.18 \mu S$ ]

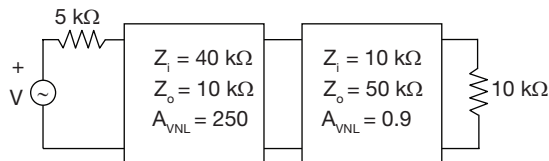
- (A) 5 MΩ (B) 6 MΩ  
(C) 7 MΩ (D) 4 MΩ
19. Find total current gain for the system



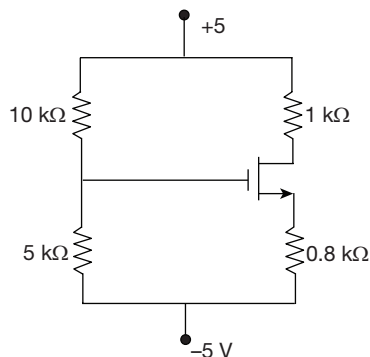
- (A) -497.5 (B) 277.7  
(C) -208 (D) 187
20. An amplifier with a lower cut-off frequency of 50 Hz is to be employed for amplification of square waves for the tilt on the output waveform not to exceed 5%. The lowest input frequency that can be amplified is
- (A) 2.5 kHz  
(B) 3.14 kHz  
(C) 10 kHz  
(D) 17.5 kHz
21. In below circuit the transistor parameters are  $V_{Th} = -1.2V$  and  $K_n = 0.8 \text{ mA/V}^2$  then find drain current



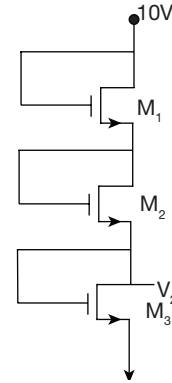- (A) 1.27 mA (B) 1.75 mA  
(C) 1.55 mA (D) 1.97 mA
22. In below circuit, the EMOSFET parameters are  $V_{Th} = 1V$ ,  $V_{GS} = 3V$  and  $k_n = 30 \mu A/V^2$ . If  $I_D = 1 \text{ mA}$ ,  $V_2 = 2V$ . Then width to length ratio required in EMOSFET  $M_1$ , is



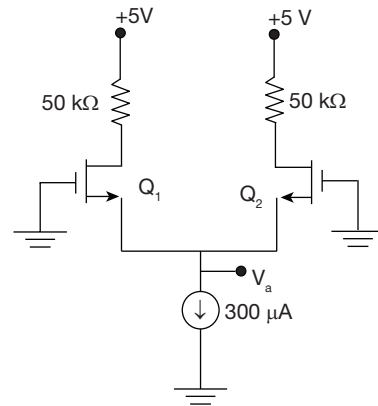- (A) 4.16 (B) 3.67  
(C) 2.82 (D) 5.32
23. In the following circuit, transistors  $Q_1$  and  $Q_2$  has the following parameters. [Transistors are in saturation]




$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 15$$

$$(V_{Th})_1 = (V_{Th})_2 = 1 \text{ V}$$

$$(k_n^1)_1 = (k_n^1)_2 = 75 \mu A/V^2$$


Then find  $V_a$ .

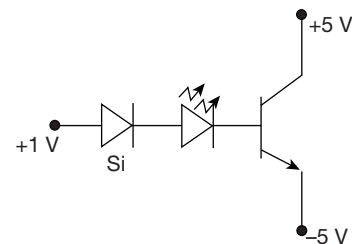- (A) 1.365 V (B) -2.14 V  
(C) 2.14 V (D) -1.516 V
24. The transistor in below circuit is in  $[V_{\gamma_{Si}} = 0.7V, V_{\gamma_{red}} = 1.8V]$



- (A) active region  
(B) saturation region  
(C) cut-off region  
(D) None of the above

25.

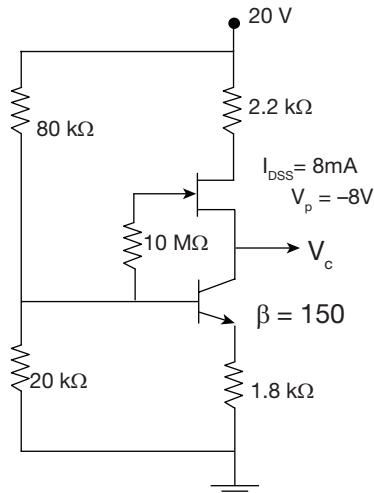
 Determine the value of  $V_c$  in above given network?


- (A) 4 V  
(B) 6 V  
(C) 8 V  
(D) zero V

## ANSWER KEYS

- |       |       |       |       |       |       |       |       |       |       |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 1. C  | 2. A  | 3. C  | 4. A  | 5. C  | 6. B  | 7. B  | 8. D  | 9. B  | 10. C |
| 11. C | 12. A | 13. C | 14. C | 15. A | 16. B | 17. B | 18. A | 19. A | 20. B |
| 21. B | 22. A | 23. D | 24. A | 25. C |       |       |       |       |       |

## HINTS AND EXPLANATIONS

1.

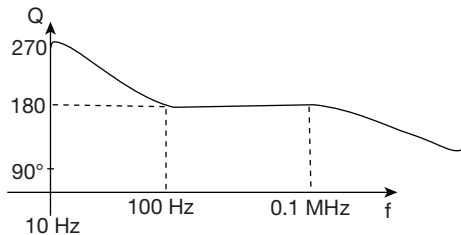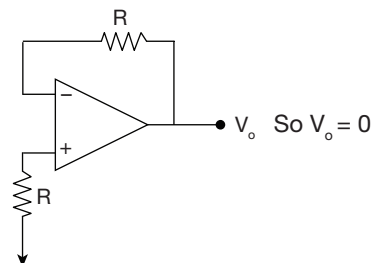
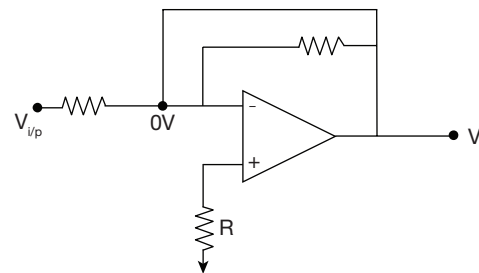

 Phase plot for an  $R$ - $C$  coupled amplifier Choice (C)

 2.  $A_v = 800 \pm 50$ 

$$\frac{\partial A_F}{A_F} = \pm 0.5\%; \quad \frac{\partial A_F}{A_F} = \frac{\partial A}{A} \left( \frac{1}{1 + \beta A} \right)$$

$$\Rightarrow \frac{0.5}{100} = \frac{50}{800} \left( \frac{1}{1 + \beta(800)} \right)$$

$$\Rightarrow \beta = 1.43\%. \quad \text{Choice (A)}$$

 3. If  $f \rightarrow 0$ , capacitor is open circuited then  $n/w$  looks like

 If  $f \rightarrow \infty$ , capacitors will short circuited then  $n/w$  looks like


So it represents a band pass filter Choice (C)

4. Choice (A)

 5. The current through  $R_E$  results in a feedback voltage that opposes the source signal applied, so that  $V_o$  is reduced. It has current series feedback connection.

Choice (C)

6. CASCODE amplifier is CE – CB configuration.

Choice (B)

 7.  $A_v = -g_m R_D$ 

$$\Rightarrow g_m = 2k(V_{GS} - V_{Th})$$

$$\Rightarrow V_{GS} = 2.5V$$

$$\Rightarrow g_m = 2 \times 2 \times 10^{-3} [2.5 - 1.5]$$

$$= 4ms$$


$$A_v = -4 \times 10^{-3} \times 8 \times 10^3$$

$$= -32$$

Choice (B)

### 3.172 | Analog Circuits Test 4

8.

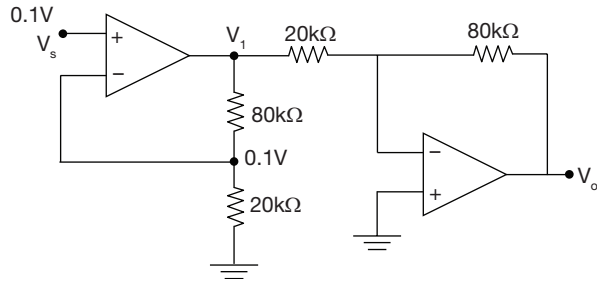


$$0.1V = \frac{V_1 \times 20}{80 + 20}$$

$$V_1 = 0.5V$$

$$\Rightarrow V_o = \frac{-R_F}{R_i} \times V_1 = -2V$$

Choice (D)

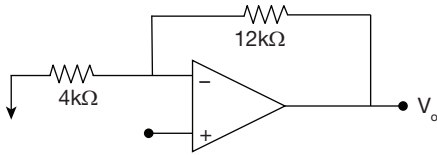9. Input is given to positive terminal so output  $V_o$  is +ve.  
The  $D_1$  is on and  $D_2$  is off



$$V_o = V_i \left( 1 + \frac{12}{4} \right) = 16V$$

Choice (B)

10. Given circuit is logarithmic amplifier

$$V_o = V_T \ln \left( \frac{V_i}{R_s I_s} \right)$$

$$\text{So } V_o \propto \ln(kV_i)$$

Choice (C)

11. Differential amplifier reduced common mode gain then CMRR will increase.

Choice (C)

$$12. A_{CL} = -\left( \frac{120}{10} \right) - 12$$

$$\frac{SR \geq \omega |A_{CL}| V_i}{10^{-6} \times 12 \times 0.1} \geq \omega$$

$$\Rightarrow \omega \leq \frac{2}{3} \text{ MHz} \Rightarrow f_{\max} = 0.106 \text{ MHz}$$

Frequency of operation is greater than maximum frequency so output has distortion.

Choice (A)

$$13. g_m = \frac{2I_{DSS}}{|V_P|} \left[ 1 - \frac{V_{GS}}{V_P} \right]$$

from graph  $V_P = -6$  at  $V_{GS} = 0V$

$$\Rightarrow I_{DSS} = \frac{5 \times 10^{-3} \times 6}{2} = 15 \text{ mA}$$


$$I_D = I_{DSS} \left[ 1 - \frac{V_{GS}}{V_P} \right]^2$$

$$\Rightarrow I_D = 15 \times 10^{-3} \left[ 1 - \frac{4}{6} \right]^2$$

$$= \frac{15}{9} \times 10^{-3} = 1.67 \text{ mA}$$

Choice (C)

14.

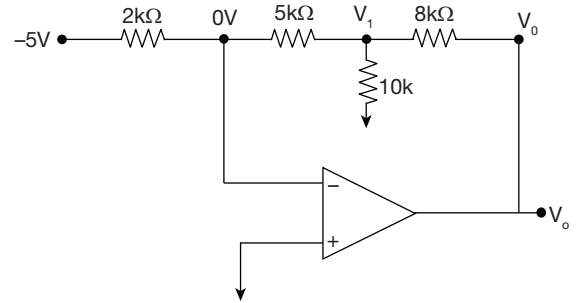

$$\text{KCL at Node } 0V \text{ is } \frac{0 - (-5)}{2} + \frac{0 - V_1}{5} = 0; \frac{25}{2} = V_1$$


$$\Rightarrow \text{KCL at Node } V_1 \text{ is } \frac{V_1 - 0}{5} + \frac{V_1}{10} + \frac{V_1 - V_o}{8} = 0$$

$$\Rightarrow V_1 \left[ \frac{1}{5} + \frac{1}{10} + \frac{1}{8} \right] = \frac{V_o}{8}$$

$$\Rightarrow V_o = 42.5V$$

Choice (C)
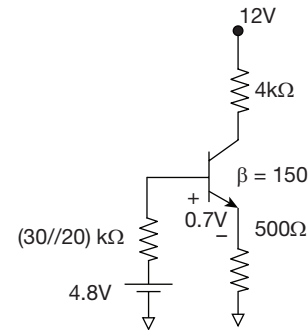
$$15. f_\beta = \frac{1}{2\pi\beta r_e (C_{be} + C_{bc})}$$



$$r_e = \frac{V_T}{I_E}$$

$$I_E = 7.07 \text{ mA}$$

$$\Rightarrow r_e = \frac{25 \text{ mV}}{7.07 \text{ mA}} = 3.53$$

$$f_\beta = \frac{1}{2\pi \times 150 \times 3.53 \times (25 + 8) \times 10^{-12}} = 9.1 \text{ MHz}$$

Choice (A)

$$16. \text{Feedback factor is } = \frac{2}{2 + 24} = \frac{2}{26}$$

$$R_{OF} = \frac{R_o}{1 + A\beta} = \frac{150}{1 + 2 \times 10^5 \times \frac{2}{26}} = 9.75 \text{ m}\Omega$$

Choice (B)

$$17. \quad g_m = \frac{2I_{DSS}}{|V_P|} \left[ 1 - \frac{V_{GSQ}}{V_P} \right] = \frac{2 \times 12}{5} \left[ 1 - \frac{(-2.5)}{(-5)} \right] = 2.4 \text{ mS}$$


$$A_v = \frac{g_m R_s}{1 + g_m R_s} = \frac{2.4 \times 10^{-3} \times 2.2 \times 10^3}{1 + 2.4 \times 10^{-3} \times 2.2 \times 10^3}$$
$$= \frac{5.28}{6.28} = 0.84. \quad \text{Choice (B)}$$

$$\mathbf{18.} \ Z_o = Z_L || Z_o^1$$

$$\text{Where } Z_o^1 = \frac{1}{h_{ob} - \left[ h_{fb} h_{rb} / (h_{ib} + R_s) \right]}$$

$$Z_o = \frac{1}{0.18 \times 10^{-6} - \left[ \frac{(-0.9)(88.3 \times 10^{-6})}{(0.015 + 4) \times 10^3} \right]} = 5 \text{ M}\Omega$$

19.

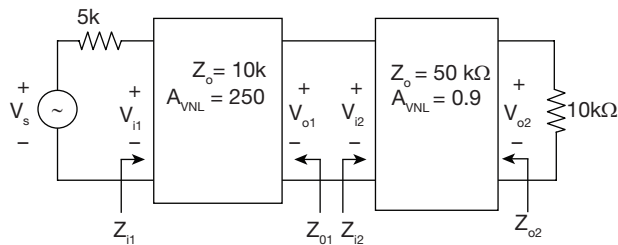

$$A_{V_1} = \frac{V_{o_1}}{V_{i_1}} = \frac{Z_{i_2}}{Z_{i_2} + Z_{o_1}} A_{V_{NL1}} = \frac{10 \times 10^3 \times 250}{(10 + 10) \times 10^3} = 125$$

$$A_{V_2} = \frac{R_L}{R_L + Z_{o_2}} A_{V_{NL2}} = \frac{10^4}{10^4 + 50} \times 0.9 = 0.99$$

$$A_{V_T} = A_{V_1} . A_{V_2} = 124.37$$

$$\Rightarrow A_{i_T} = -A_{V_T} \frac{Z_i}{R_L} = 124.37 \times \frac{40}{10} = -497.5$$

Choice (A)

$$\begin{aligned} 20. \quad & \frac{\pi f_L}{f} < \frac{5}{100} \\ \Rightarrow & \frac{100\pi \times 50}{5} < f; 3.14 \text{ kHz} < f \end{aligned}$$


Choice (B)

21.  $V_{th} = \frac{5 \times 5}{15} = \frac{5}{3} \text{ V}$

$$5 + V_G = \frac{5}{3}$$

$$V_G = \frac{-10}{3} \text{ V}$$

$$V_{GS} = V_G - V_S$$

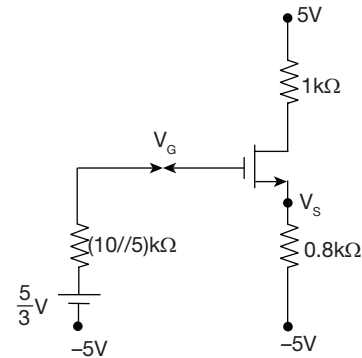


$$I_D = \frac{V_S + 5}{0.8k\Omega} = k_n [V_{GS(on)} - V_T]^2$$

$$\frac{(V_s + 5)}{0.8} = 0.8 \left[ \frac{-10}{3} - V_s + 1.2 \right]^2$$

$$\Rightarrow V_s = -3.6$$

$$\Rightarrow I_D = \frac{(-3.6 + 5)10}{8} \text{ mA} = 1.75 \text{ mA} \quad \text{Choice (B)}$$

**22.**

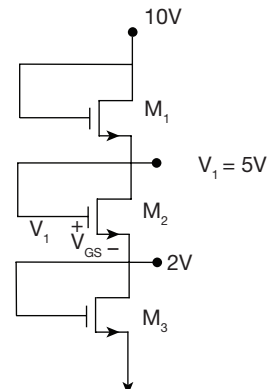

For every EMOSFET in given problem  $V_{GS} = V_{DS}$  and  $V_{DS} > V_{GS} - V_{th}$  so all are in saturation region

$$V_{GS2} = 3 = V_{DS3}$$

$$V_{GS1} = V_{GS2} + 2 = 5V$$

$$\Rightarrow V_{GS1} = 5V$$

$$1\text{mA} = I_D = \frac{30 \times 10^{-6}}{2} [5 - 1]^2 \left[ \frac{W}{L} \right]$$


$$1 \times 10^{-3} = 15 \times 10^{-6} \times 16 \times \left(\frac{W}{L}\right)_1$$

$$\Rightarrow 4.16 = \left( \frac{W}{L} \right)_1$$

Choice (A)

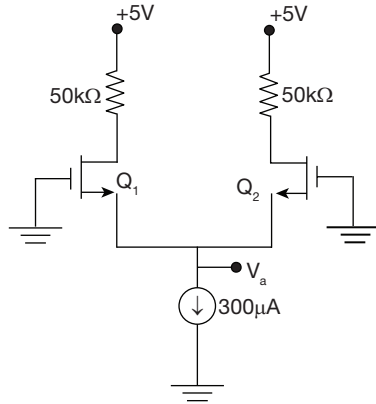**23.**  $V_a = -V_{GS}$

Both transistors have same parameters so current flow in each transistor is equal to  $150\text{ }\mu\text{A}$



$$I_D = 150 \times 10^{-6} = \frac{(k_n') \left( \frac{W}{L} \right)}{2} (V_{GS} - 1)^2$$


$$\Rightarrow 300 \times 10^{-6} = 75 \times 10^{-6} \times 15 (V_{GS} - 1)^2$$

$$\Rightarrow \sqrt{\frac{20}{75}} + 1 = V_{GS} = 1.516 = -V_a$$

$$\Rightarrow V_a = -1.516.$$

Choice (D)

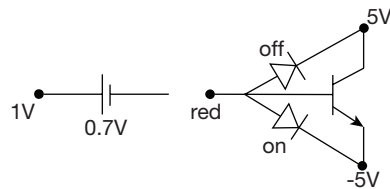
24. Si diode is ON but other diode is off



So transistor is in active region

Choice (A)

25. Reducing the network to

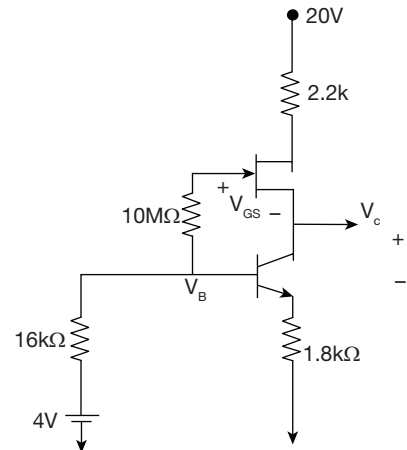

$$\beta R_E > 10 R_2 \text{ so } I_C = \frac{4 - 0.7}{1.8 \text{ k}\Omega}$$

$$= \frac{3.3}{1.8} \text{ mA} = 1.83 \text{ mA}$$

$$I_C = I_D = I_S = 1.83 \text{ mA}$$

$$I_D = I_{DSS} \left[ 1 - \frac{V_{GS}}{V_P} \right]^2$$

$$\Rightarrow 1.8 = 8 \left[ 1 + \frac{V_{GS}}{8} \right]^2$$

$$\Rightarrow V_{GS} = -4.02 \Rightarrow \text{KVL at } V_B \text{ to } V_C$$

$$V_{GS} + V_C = V_B$$

$$V_C = 4 + 4.02 \approx 8 \text{ V.}$$

Choice (C)