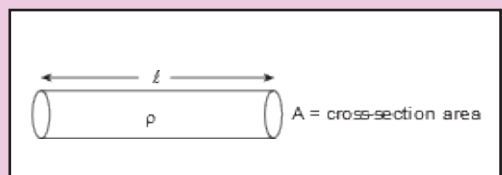


Resistance depending on temperature


- Resistivity of conductor increase with increase in temperature.
- Resistivity of semiconductor decreases with increases in temperature

Resistance, (R)




$$R = \frac{\rho l}{A}$$

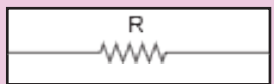- Unit of Resistance Ohm (Ω)
- Dependency of R on temperature (T)
 $R_2 = R_1(1 + \alpha(T_2 - T_1))$
 α = Temperature coefficient of resistance
- Symbol





- Rheostat is variable resistance

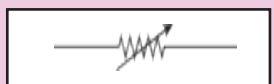

Resistance colour code
 $R = \text{1st digit} - \text{2nd digit} \times \text{3rd digit} + \text{4th digit} \%$

Ohm's Law

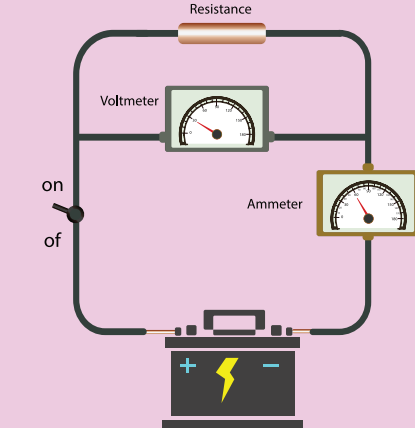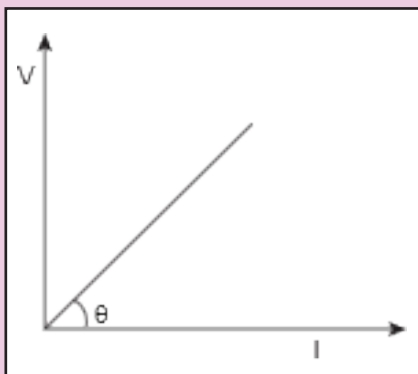- If physical condition remain same current $I \propto V \Rightarrow V = IR$
- R-electric resistance substances which obey Ohm's law called Ohmic and that do not obey called non-ohmic substances.
- Ohm's law is not valid for semi-conductor
- For Ohmic substances $\tan \theta = \frac{V}{I} = R$



S.I. Unit Ampere
(A) Coulomb Second


Rate of flow

$$\text{Instantaneous, } i = \frac{dQ}{dt}$$

$$\text{Average, } i = \frac{\Delta Q}{\Delta t}$$

By convection, direction of flow of positive charge is taken as direction of flow of current.
Drift velocity (V_d)

Drift velocity (V_d)

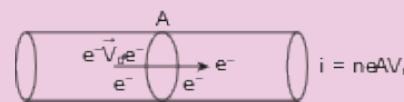

$$i = neAV_d = \frac{ne^2 A \tau E}{m} = neAl_e E = neA\mu_e \frac{V}{l}$$

Average uniform velocity acquired by free electron.

$$V_d = \frac{i}{neA} = \frac{J}{ne} = \frac{V}{\rho l ne} \text{ or } \frac{eE}{m} \tau$$

$$V_d = \mu_e E \quad (\tau \text{ is avg. time between collisions})$$

$$\text{mobility, } \mu_e = \frac{V_d}{E} \quad (\rho \text{ is resistivity unit is } \Omega \cdot \text{m})$$

In terms of relaxation time τ

$$R = \frac{ml}{ne^2 \tau A} \text{ and } \rho = \frac{m}{ne^2 \tau}$$

n , τ , and ρ are properties of material.

Electric Energy and Power

Principle of bulb

- Resistance of bulb, $R = \frac{V^2}{P}$ or $R \propto \frac{1}{P}$ (V and P is rated value on bulb)
- In parallel, $P = P_1 + P_2$
- In Series, $\frac{1}{P} = \frac{1}{P_1} + \frac{1}{P_2}$
- In parallel a bulb having more rated power glows more brightly.
- In series a bulb having less rated power glows more brightly.

- Heat energy developed across a resistor

$$H = I^2 R t; \quad t = \text{time}$$

- Power, $P = I^2 R = \frac{V^2}{R}$

- For transmission cable, power loss, $p_c = I^2 R_c = \frac{P^2 R_c}{V_c^2}$, $P = \text{const.}$

Grouping of cells

Cell in Series.

$$\text{Current in the circuits, } I = \frac{n\varepsilon}{R + nr}$$

Cell in Parallel

$$\text{Current in the circuit, } I = \frac{\varepsilon}{R + \frac{r}{m}}$$

Conductivity (σ)

$$\sigma = \frac{1}{\text{Resistivity}} = \frac{1}{\rho}$$

$$\text{Unit} = \frac{1}{\Omega \text{m}} = \frac{1}{\text{ohm} \cdot \text{m}} \text{ or } \frac{\text{mho}}{\text{m}}$$

$$\text{Conductance, } C = \frac{1}{\text{Resistance}} = \frac{1}{R}$$

Unit is mho (Ω^{-1})

Grouping of Resistance


Series grouping of resistance

- Equivalent resistance, $R_s = R_1 + R_2 + R_3 \dots$
- Current flow through each resistance is same.
- Potential difference, $V \propto R$

Parallel grouping of resistance

Equivalent resistance.
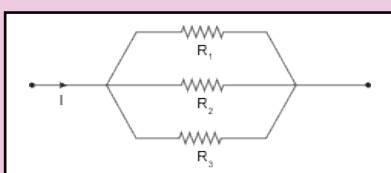
$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$



Potential difference across each resistance same

current distribution in each resistance, $I \propto \frac{1}{R}$

Some Important Formula


- After stretching, its length increases by n times then resistance will increase by n^2 times i.e.,

If radius be reduced to $\frac{1}{n}$ times then area of cross-section decreases $\frac{1}{n^2}$ time so the

- resistance become n^4 times i.e., $R_2 = n^4 R_1$
- Using n conductors of equal resistance, the number of possible combination is 2^{n-1} .

If the resistance of n conductors are totally different, then the numbers of possible

- combination will be 2^n .

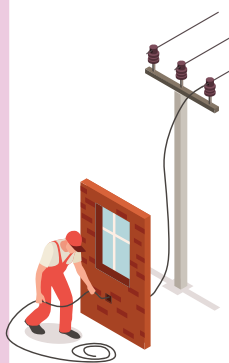

Electric Cell :

Source of energy that maintains continuous flow of charge in a circuit.

$$\text{EMF of cell, } \varepsilon = \frac{W}{q}$$

Cells in Series and Parallel

$$\text{i.e., mixed current in the circuit, } I = \frac{n\varepsilon}{nr + R + R}$$

Electric Current

$$\text{Current, } I = \frac{q}{t} = \frac{ne}{t}$$

- In case of electron revolving in a circle of radius r with speed V ,
- Period of revolution, $T = \frac{2\pi r}{V}$
- Frequency of revolution, $f = \frac{V}{2\pi r}$
- Current at any point of orbit is $I = \frac{e}{T} = \frac{eV}{2\pi r}$

Current density, (J)


Current per unit cross-section area perpendicular to current flow.

$$J = \frac{I}{A} = \frac{E}{\rho}$$

Potentiometer

Used to

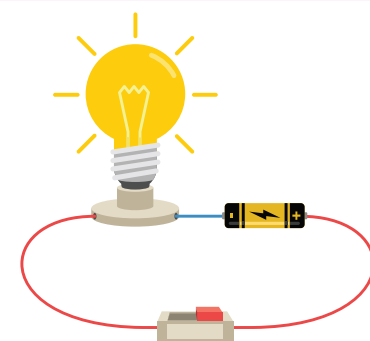- (i) compare emfs $\frac{E_1}{E_2} = \frac{l_1}{l_2}$
- (ii) final internal resistance of cell $r = \left(\frac{E}{V} - 1 \right) S$



When cell is discharging

When cell is discharging current inside the cell is from cathode to anode current $I = \frac{E}{r + R}$

$$\text{or } E = IR + Ir = V + Ir \text{ or } V = E - Ir$$

When cell charging

When cell is charging current inside the cell is from anode to cathode.

$$\text{Current, } I = \frac{V - E}{r} \text{ or } V = E + Ir$$

When cell is open circuit

$$R = \infty$$

$$I = \frac{E}{R + r} = 0 \text{ and } V = E$$

When cell is short circuited

$$R = 0 \text{ and } I = \frac{-E}{R + r} \text{ and } V = IR = 0$$

Power transferred to load by cell

$$P = I^2 R = \frac{E^2 R}{(r + R)^2} \text{ and } P = P_{\text{max}}$$

$$\text{if } \frac{dP}{dR} \text{ and } P = P_{\text{max}} \text{ if } r = R$$

$$P_{\text{max}} = \frac{E^2}{4r} = \frac{E^2}{4R}$$

Kirchoff's laws

1st law/ Junction law

- Algebraic sum of all the current meeting at junction is zero. i.e., $\sum I = 0$

2nd law/loop rule

Algebraic sum in potential around any closed loop is zero

Meter bridge

Based on wheat stone bridge

$$\frac{P}{Q} = \frac{R}{S} = \frac{l}{100 - l} = \frac{R}{S}$$

Balanced Condition of wheat Stone bridge

$$\frac{P}{Q} = \frac{R}{S}$$

Potential gradient (x)

Potential difference per unit length of wire


$$x = \frac{V}{L} = \frac{\text{Volt}}{\text{m}}$$

$$\text{where, } V = IR = \left(\frac{e}{(R + R_n + r)} \right) \times \frac{R}{L}$$

Sensitivity of Potentiometer

- A potentiometer is more sensitive, if it measures a small potential difference more accurately.

Resistance colour code

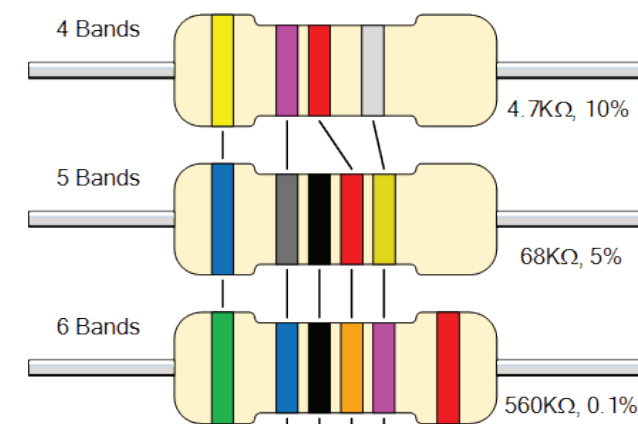

1st Digit	2nd Digit	3rd Digit	Multiplier	Tolerance	Temperature Coefficient
0	0	0	0.01	10%	100ppm
1	1	1	0.1	5%	50ppm
2	2	2	1	2%	15ppm
3	3	3	10	1%	25ppm
4	4	4	100	0.5%	
5	5	5	1000	0.25%	
6	6	6	10000	0.1%	
7	7	7	100000	0.05%	
8	8	8	1000000		
9	9	9			

