
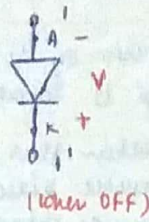


Power Electronics



Switches :

→ Diode blocks voltage of opp. polarity or in reverse direction. (One quadrant)

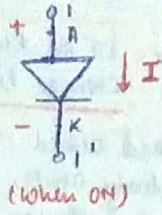(current always flows in a for direction)





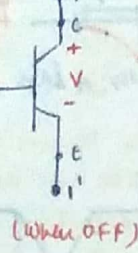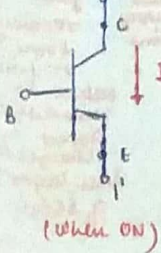→ BJT block voltage of same polarity or in same direction. (One quadrant)



→ Same is the case for MOSFET and IGBT.

SCR :

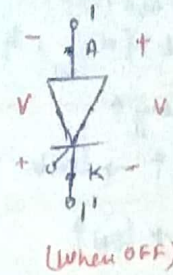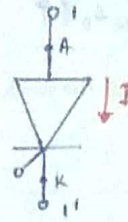

+ SCR can develop blocking voltage in both direction +ve and -ve.
→ It is bipolar unidirectional
→ Two quadrant switch.

→ Operates in R.B.M, F.B.M, F.C.M (OFF) (ON)

→ In FCM and FBM, $J_1, J_3 \rightarrow S-C$ or $F-B$
 $J_2 \rightarrow O-C$ or $R-B$.

→ Half controlled device.

→ When the S.C.R is conducting or in F.B.M then the junction J_2 breaks down but it is not getting forward biased.

→ at R.B.M, $I_{AK} = 0$ $V_{AK} = -V$


at F.B.M, $I_{AK} = 0$ $V_{AK} = +V$

at F.C.M, $I_{AK} = +ve$, $V_{AK} = 0$. ("S.C. hoga diode").


Two Quadrant Example :

(1) SCR

(2)

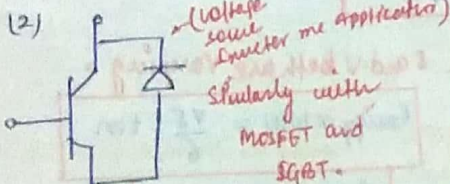

(3)

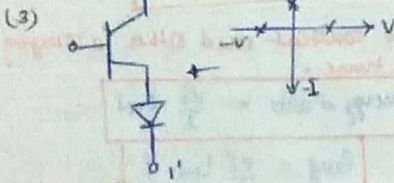

→ V_{BO} (Forward Break over voltage or forward break down voltage) is always specified by manufacturer

→ V_{BO} is the final voltage rating of the S.C.R

→ Under Gate Triggering :

$$q_2 = I_g \times t$$

$$I_g \propto \frac{1}{V_{BO}}$$

$$I_g \propto \frac{1}{\text{depth layers}}$$

$\frac{dv}{dt}$ Triggering : Same voltage across capacitor ke same time ka change hota hai. Hence $V = V_{AK}$.

$$\frac{dv}{dt} = \text{charging} \times \frac{1}{C_j}$$

→ $\frac{dv}{dt}$ is always related with noise signal not with the actual supply voltage.

→ $I_{charging} \geq I_L$ (latching current) $\Rightarrow$ SCR-ON


→ $(\frac{dv}{dt})_{operated} > (\frac{dv}{dt})_{specified} \Rightarrow$ SCR-ON

→ $I_{AK} > I_L \Rightarrow$ SCR ON

→ $I_{AK} < I_H \Rightarrow$ SCR OFF

$$t_{on} (\text{pulse width}) = \frac{L \times \text{inductor current}}{\text{source voltage}}$$

Four quadrant :

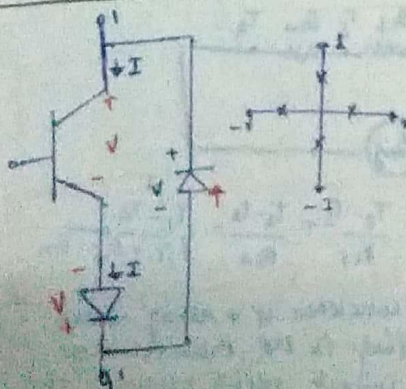

Switching Characteristics during Turn ON Process :-


→ SCR (OFF) $\xrightarrow{\text{TURN ON PROCESS}}$ SCR (ON)

$V_{AK} \rightarrow \text{max}$
 $I_{AK} \rightarrow \text{zero}$

$V_{AK} \rightarrow \text{min or } 0$
 $I_{AK} \rightarrow \text{max}$

$$T_{ON} = t_d + t_r + t_s$$

delay time, rise time, spread time

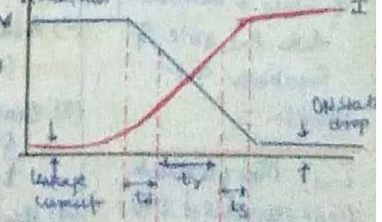

Switching characteristics during Turn ON Process

$t_{on} = t_d + t_r + t_s$


→ t_r is most dominating, and to reduce t_{on} , we need to reduce t_r and that can be done by controlling $(\frac{di}{dt})$. As $f \propto \frac{1}{T_{on}}$, if $t_{on} \downarrow$, $f \uparrow$ and switching frequency $\uparrow$.

→ high $(\frac{di}{dt}) \rightarrow f \uparrow \rightarrow t_{on} \downarrow$

→ low $(\frac{di}{dt}) \rightarrow f \downarrow \rightarrow t_{on} \uparrow$

But if $(\frac{di}{dt})_{operated} > (\frac{di}{dt})_{specified} \rightarrow$ SCR damage
 if $(\frac{di}{dt})_{operated} < (\frac{di}{dt})_{specified} \rightarrow$ SCR will be safe.

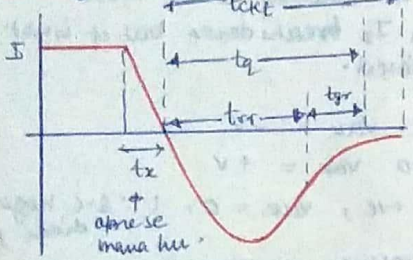→ During rise time, Power loss will be maximum



→ Total turn-off time = $t_x + t_{rr}$
 → Device turn-off time = $t_{rr} + t_{gr}$

→ In ideal situation, t_{rr} and $t_{gr} = 0$, characteristic will look like:

Note: (1) Agar diode ko reverse biased kije, aur storage time t_s ya rise time t_r ka bat kija to $V_{ak} = 0$ balki diode ko short karega upto t_s aur t_r chhote nikalenge. Ckt me.

(2) The switching characteristics of SCR, BJT, MOSFET, IGBT or diode are all same.

→ Switch ON ya OFF hora, current dekh ke backeage na ki voltage.

→ surge current, fault current, overcurrent are related to overcurrent protection. use $I^2 t = \text{constant}$

dv Protection:

 Voltage Snubber ckt.
 If noise is introduced, then the role of snubber ckt starts.


T_{on} : time for which diode remained ON.
 t_{on} : time for which diode remained ON.

Switching characteristic during Turn OFF process:


→ After ideal condition hai, aur reverse biased kije to instant P-N Junction open switch ki tarah kam nai karega. Tada time lega off hone me.

→ The time taken by the device for the removal of the stored charge is known as storage time.

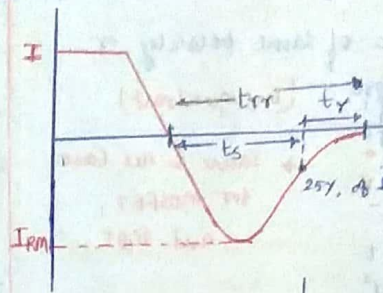→ The time taken from forward biased steady state condition to reverse biased steady state condition is known as Reverse recovery time t_{rr} .




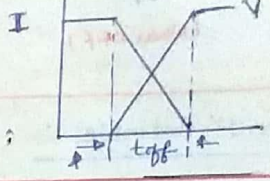$t_g = t_{rr} + t_{gr}$
 device recovery time
 gate recovery time or time taken to remove the stored charges in base layer of SCR.




$P_{avg} = \frac{1}{T} \int P dt$

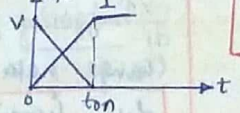Case 1: when i and v both are varying.
 Energy or $w(t) = \frac{VI}{6} \cdot t_{on}$



$P_{avg} = \frac{VI}{6} \cdot t_{on} \cdot f$

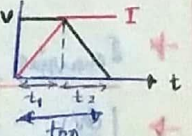Case 2: when one is constant and other is varying at a time.




Energy or $w(t) = \frac{VI}{2} \cdot t_{on}$

$P_{avg} = \frac{VI}{2} \cdot t_{on} \cdot f$

$T_j > T_c > T_s > T_a$
 Junction temp, case temp, sink temp, atmosphere temp.

Equivalent thermal ckt.

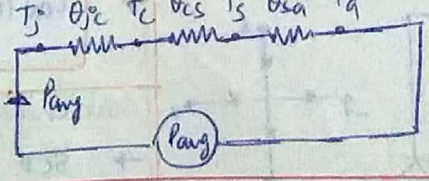

$P_{avg} = \frac{T_j - T_c}{\theta_{jc}} = \frac{T_c - T_s}{\theta_{cs}} = \frac{T_s - T_a}{\theta_{sa}} = \frac{T_j - T_a}{\theta_{jc} + \theta_{cs} + \theta_{sa}}$

Imp Note: If somewhere it is asking about the device rating in SCR, then always calculate its current rating because the power is associated with current (Practically).



Thermal Protection:

Analogy b/w Electrical and Thermal Quantity.


Electrical	Thermal Quantity
(1) charge (C)	(1) Heat (J) or watt-sec
(2) Potential diff (V)	(2) Temperature different (°C)
(3) current (I) $= \frac{Q}{t} = C/sec$	(3) Power = Avg power = watt or J/sec
(4) Resistance = $\frac{V}{I}$	(4) Thermal resistance = $\frac{^\circ C}{watt}$

Characteristics of SCR:

Complete gate driving ckt:

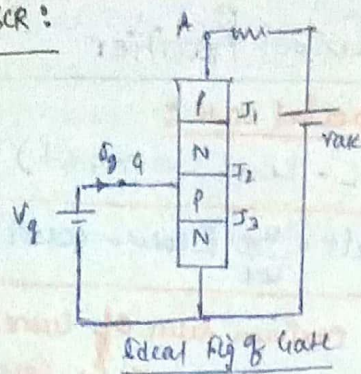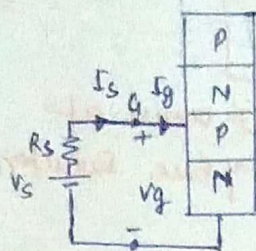

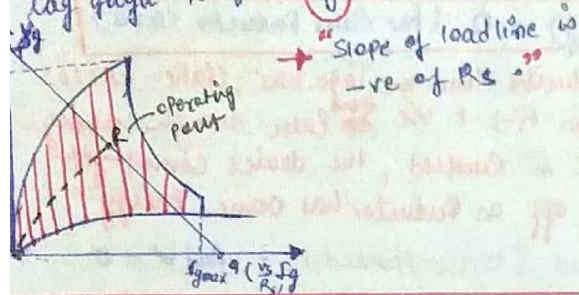yad rakha hai agar 'a' aur 'k' ke bich me Resistance lag gaya to fir $I_g \neq I_s$.



Efficiency for series and Parallel operation:


$$\eta_{\text{string}} = \frac{\text{voltage across the string}}{(\text{Individual rating of SCR}) \times (\text{No. of SCR})}$$

$$\eta_{\text{string}} = \frac{\text{current through the string}}{(\text{Individual current rating of SCR}) \times (\text{No. of SCR})}$$

$$\text{Derating factor (D.F.)} = 1 - \eta_{\text{string}}$$

Negative temp coefficient device :- BJT, SCR.

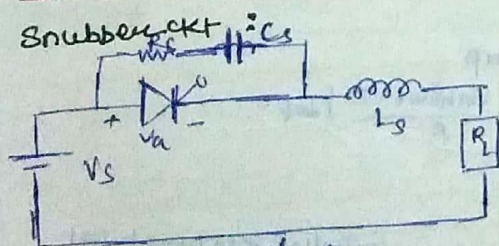Special note: Jab diode ya SCR capacitor ke parallel me laga hai to during charging of capacitor, SCR will be OFF and once capacitor is fully charged then while discharging, SCR will be ON.



$$I_s = \frac{V_s}{\left(\frac{dV_a}{dt}\right)_{\text{avg}}}$$

$$R_s = \frac{\left(\frac{dV_a}{dt}\right)}{\left(\frac{dI_g}{dt}\right)}$$

$$I_s = \frac{4S_1^2 L_s}{(R_s + R_L)^2}$$

Continuous Gate Triggering :-

- In FCM, we apply continuous Gate Triggering.
- For High Inductive load, we use continuous gate triggering.
- If nothing is mentioned or nothing is available for calculation of turn ON time then we go for **Gate Pulse width**.

condition of Continuous Gate Triggering :-

$$I_{g \text{ avg}} = V_g I_g = I_{g \text{ max}}$$

Pulse Gate Triggering :-

$$I_{g \text{ avg}} = I_{g \text{ max}} \times D = I_{g \text{ max}} \times \frac{T_{ON}}{T}$$

$$I_{g \text{ max}} = V_g I_g$$

If $T_{ON} < 100 \mu\text{sec}$, then we will always use **Pulse Triggering**.

If $T_{ON} > 100 \mu\text{sec}$, then we will always use **Continuous Gate Triggering**.


Kabhi bhi I_g ki do value aye to us value ko select karna hai jo 2 to 3 times $I_{g \text{ max}}$ ho.

$$R = \frac{n V_1 - V_s}{(n-1) \Delta I_L}$$

$$C = \frac{\Delta Q (n-1)}{V_1 n - V_s}$$


n = no. of SCR in series.
 V_s = Source voltage
 V_1 = Individual rating of SCR
 ΔI_L = leakage current
 ΔQ = Charge in charge.

TRICK FOR FINDING the RMS and Avg value:

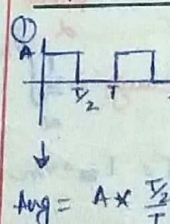

$$\text{Avg} = A \times \frac{T/2}{T} = A/2$$

$$RMS = \frac{A}{\sqrt{2}}$$

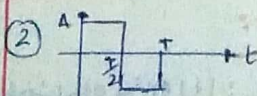

$$\text{Avg} = A \times \frac{T/2}{T} = A/2$$

$$RMS = A \times \sqrt{\frac{T/2}{T}} = A/\sqrt{2}$$

$$\text{Avg} = \frac{\text{Amplitude} \times \text{Duration of signal exist}}{\text{Time period}}$$

$$RMS = \text{Amplitude} \times \sqrt{\frac{\text{Duration of signal exist}}{\text{Time period}}}$$

Symmetrical Square pulse/waveform me half ko to bus aur phir Time period bhi half hogaya aur use RMS and Avg nikalo.

Symmetrical waveform ke avg. value = 0

SINGLE PHASE Control Rectifier

Single phase Half wave controlled and uncontrolled Rectifier :-

(1) R-Load :

- $i_o(t) = \frac{V_m \sin \omega t}{R}$ → $\beta = \pi$
- $V_o(t) = \frac{V_m \sin \omega t}{R}$ → $\alpha = \text{firing Angle}$
- $P.S.V = V_m$ → For uncontrolled $\alpha = 0$ - in case of R-Load.

(2) R-L Load :

(a) controlled : **Note** : Jab Jab Inductor me reverse bias hone ka condition π se age Jaega qki reverse bias jab hogi jab Inductor current apni Energy khatam karega qki π pe source Reverse bias hota hai aur furant Inductor Energy loose nai karega isliye π ke Bad hr reverse bias hogi aur off ~~hoga~~ hogi.

$$i.e. \pi < \beta < 2\pi$$

- Firing Angle = α
- Extinction angle = β
- $V_{o(avg)} = \frac{1}{2\pi} \int_{\alpha}^{\beta} \frac{V_m \sin \omega t}{R} d\omega t$
- $V_{o(avg)} = I_{o(avg)} R$
- For Inductor avg voltage always zero.

(b) uncontrolled : $\alpha = 0$ in all results of controlled.

(3) R-E Load :

controlled : (1) ~~Reverse bias~~ meter.

(2) R-E load corresponds to battery charging like we are charging battery at our home.

Stp 1 hi ake jab jab hi supply reverse biased hone ke Sawagid conduction hota hai but baki load me esa nai hai Thyristor/diode get reverse biased.

- Exactly at α and β , current = 0
- Firing Angle = α
- Extinction Angle = $\beta_2 = \theta_2$
- Increase of R-E load.

Special case :

(1) L-Load (controlled) :-

$$i_L(t) = \frac{V_m}{\omega L} [\cos \alpha - \cos \omega t]$$

→ maximum value of current occurs at $\omega t = \pi$ in case of pure Inductor.

→ Firing Angle = α

→ Extinction Angle = $2\pi - \alpha$

→ $V_{o(avg)} = 0$ (For pure Inductor case)

→ agar Inductor load me laga hai, dake akele ye phir R-L-E me ~~hoga~~ even though supply voltage is Reverse, the device cannot get turned off as Inductor has some Energy.

(2) L-Load (uncontrolled) :- Put $\alpha = 0$

$$i_L(t) = \frac{V_m}{\omega L} [1 - \cos \omega t]$$

For average value integrating limit 0 to 2π

→ Here also maximum value of current occurs at $\omega t = \pi$ in case of pure Inductor.

→ current (i_L) becomes zero at $\omega t = 2\pi$.

→ Firing angle = $\alpha = 0$

→ Extinction angle = $2\pi - \alpha = 2\pi$

→ $V_{o(avg)} = 0$ (For pure Inductor)

$$\theta_1 = \sin^{-1} \left(\frac{E}{V_m} \right) \text{ and } \theta_2 = \pi - \theta_1$$

$$\theta_1 < \alpha \leq \theta_2$$

$$I_{o(avg)} = \frac{1}{2\pi} \int_{\alpha}^{\beta_2 \text{ or } \theta_2} \left(\frac{V_m \sin \omega t - E}{R} \right) d\omega t$$


$$P.I = E_{avg} + V_m$$

uncontrolled : Put $\alpha = 0$, in controlled relations to get all relations of uncontrolled

Important :

(1) turn-off : (1) only applicable for controlled rectifier.
→ ye wo time hai jab Thyristor ke across ka voltage (V_r) negative hota hai.
 $V_r + \frac{2\pi + \alpha}{\omega} \Rightarrow \text{turn-off} = \frac{2\pi + \alpha - \pi}{\omega} = \frac{\pi + \alpha}{\omega}$

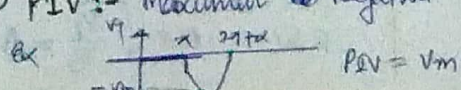(2) PIV :- Maximum Negative voltage across thyristor.



Best approach to get the relations of single phase "Half Wave Rectifier":

Formulae for RLE Load (controlled):

(1) α range:

$$\alpha_{min} \leq \alpha \leq \alpha_{max}$$

$$\theta_1 \leq \alpha \leq \theta_2$$

$$\theta_1 = \sin^{-1} \left(\frac{E}{V_m} \right)$$

$$\theta_2 = \pi - \theta_1$$

(2) Extinction angle:

$$\rightarrow \text{Extinction angle} = \beta$$

(3) * Conduction Angle:

$$\rightarrow \text{Conduction Angle} = \gamma = \beta - \alpha$$

(4) conduction time (t_c):

$$\rightarrow t_c = \frac{\gamma}{\omega} = \frac{\beta - \alpha}{\omega}$$

(5) $V_o(\text{avg})$

$$\rightarrow V_o(\text{avg}) = I_o(\text{avg})R + E$$

(6) P_{SV}

$$\rightarrow P_{SV} = V_m + E$$

(5) cut turn off time:

$$t_{\text{cut off}} = \frac{2\pi + \theta_1 - \beta}{\omega}$$

(6) $I_o(\text{avg})$:

$$I_o(\text{avg}) = \frac{1}{2\pi R} [V_m(\cos \alpha - \cos \beta) - E(\beta - \alpha)]$$

$\rightarrow$ For half wave rectifier source current follows o/p current $\therefore I_{ms} = I_{or}$

Very Important Note:-

- upar likhe hue formulae ko use karte hue hum same load ke lie formulae derive karenge.
- jis load me 'E' hoga usme 'E' ki value daleenge aur jisme nai hoga usme $E=0$ karenge.
- cut off ka concept uncontrolled ke lie nai hai.
- for uncontrolled, $\alpha = \theta_1$ (always).
- Jab 'L' aega load me tabhi β ko β leenge ($\beta < \pi$) i.e. for R-L and RLE load extinction angle = β .
- for R and R-E load, $\beta = \theta_2$ (always) as in R-load $\theta_2 = \pi$, $\therefore$ in that case $\beta = \pi$.
- for pure 'L' load, $\beta = 2\pi - \alpha$

$$\rightarrow P_{\text{avg (battery)}} = I_o(\text{avg}) \cdot E$$

$$\rightarrow \text{Power dissipated over battery} = I_o^2 R$$

- Continuous conduction is only possible with RL or RLE load.
- R and RE donot provide continuous conduction.
- But R and RE load provide continuous conduction in 3 ϕ Rectifier.

1- ϕ Full wave controlled and uncontrolled Rectifier (2 pulse):-

Assumptions:

- The load current is continuous and ripple free i.e. a constant dc value of I_o .
- All devices are ideal (losses = 0).

Note: For continuous ripple free conduction in case of RLE and RL load, there is no significant of θ_1 and θ_2 . Hence operation with R-L and RLE load will be same.

$\rightarrow$ agar question me bole ki load me 'L' hai ya load current constant hai to samjh jana hai ki continuous conduction ka relation hai.

$\rightarrow$ agar load me L hai aur kuch nai bola hai conduction ke bare me to by default continuous ripple free manna hai (only in full wave rectifier me).

Controlled single phase mid point Rectifier :-

Rectifier :-

- Firing Angle = α
- Extinction angle = $\beta = \pi + \alpha$ ***
- Conduction time (t_c) = $\frac{\gamma}{\omega} = \frac{\beta - \alpha}{\omega} = \frac{\pi}{\omega}$

→ $t_{\text{ext off}} = \frac{\pi - \alpha}{\omega}$

→ $P_{\text{EV}} = 2 V_m$

→ $V_o(\text{avg}) = \frac{2 V_m \cos \alpha}{\pi}$ ***

ye bus R-L or RLE load ke lie hai jab full wave rectifier hoga aur do constant aur ripple free hoga.

- $I_o(\text{avg})$ + isko nikalne ke lie $V_o(\text{avg})$ nikal ke load me kuc laga do
- Avg current in each thyristor = $\frac{I_o}{2}$
- Rms current in each thyristor = $\frac{I_o}{\sqrt{2}}$
- $V_o(\text{avg}) = I_o(\text{avg}) R + E \rightarrow RLE \text{ load.}$

Uncontrolled single phase mid point Rectifier :-

- Firing angle = $\alpha = 0^\circ$
- Put α in all results of controlled.

→ $V_o(\text{avg}) = \frac{2 V_m}{\pi}$

→ $I_o(\text{avg}) = \frac{1}{\pi} \int_{\alpha}^{\beta} \left(\frac{V_m \sin \omega t - E}{R} \right) d\omega t$

Important

$I_o(\text{avg}) = \frac{1}{\pi} [V_m (\cos \alpha - \cos \beta) - E (\beta - \alpha)]$

Single phase Full Bridge Rectifier :-

Below results only applicable for RL or RLE load

Controlled :-


- Firing angle = α
- Extinction angle (β) = $\pi + \alpha$ *
- Conduction angle (γ) = $\beta - \alpha = \pi$
- Conduction time = $\frac{\pi}{\omega}$
- $t_{\text{ext}} = \frac{\pi - \alpha}{\omega}$ *

→ $V_o(\text{avg}) = \frac{2 V_m \cos \alpha}{\pi} \rightarrow V_{\text{avg}}$

→ $P_{\text{EV}} = V_m$

→ Avg. current in each thyristor = $\frac{I_o}{2}$

Source current :-

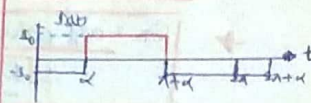


$I_{s(\text{avg})} = 0$ (∵ symmetrical)
 $I_{s(\text{rms})} = \frac{I_o}{2}$

Time period = 2π .

Uncontrolled :-

- Firing angle = $\alpha = 0$
- Put $\alpha = 0$ in all results of controlled.
- $V_o(\text{avg}) = \frac{2 V_m}{\pi}$
- $P_{\text{EV}} = V_m$

Source current :-

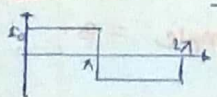


$I_{s(\text{avg})} = 0$
 $I_{s(\text{rms})} = \frac{I_o}{2}$

Discontinuous conduction of 1- ϕ Full wave Rectifier : (R or R-E load).

→ Jab tak RL or RLE load me full wave rectifier one discontinuous current mil bold hai tab tak iske results bas R or RLE load ke lie use honge.

→ Power (active) me bus fundamental component contribute karta hai, harmonic wasteful power deta hai.

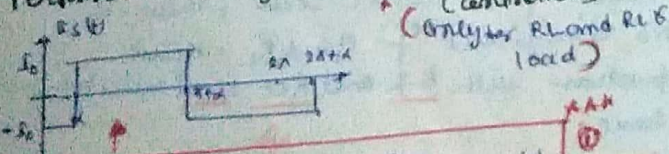Performance Analysis of 1- ϕ Full wave Rectifier :-



$I_{\text{THD}} = \frac{\sum_{n=2,4,6} \frac{I_n}{n} \times I_o (\sin^2 \omega t - n \alpha)}{I_o}$ ***

→ Fundamental source rms current $I_{s1} = \frac{\text{Peak}}{\sqrt{2}} = \frac{2\sqrt{2} I_o}{\pi}$

→ Rms value of source current $I_{s1} = I_o = \sqrt{I_{s2}^2 + I_{s3}^2 + I_{s5}^2 + \dots}$

→ $C.D.F = \frac{I_{s1}}{I_{s1}} = 0.9$ mainly use and home chahi

→ D.F or (Input Fundamental P.F) :- cosine angle of supply voltage and fundamental component of source current = $\cos \alpha$

→ Input Power factor

$$= (C.D.F \times D.F) = \cos \phi$$

→ Input Active Power :-

It is always contributed by fundamental components.


$$P_{active} = V_s I_{s1} \cos \phi$$

$$P_{active} = V_o I_o$$

→ Reactive Power :-

$$Q_{reactive} = V_o I_o \tan \phi$$

$$Q_{reactive} = V_s I_{s1} \sin \phi$$

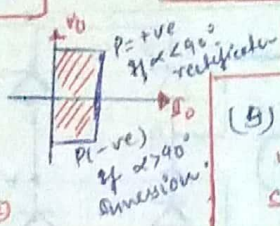

Special Note :

- (1) Jabhi CER ka voltage drop de dia question me to mean formula (Jisse haki formula nikalenge) use E ko E' se replace korege aur $E' = E + \text{voltage drop across CER}$
- (2) O, bhi badal jaega i.e. $D_1 = \sin^{-1}(\frac{E'}{V_m})$
- (3) agr d nai dia hai to min lenge i.e. D_1 .
- (4) $V_o(\text{avg}) = I_o(\text{avg}) R + E - V_T$
 But ye tabhi use karna hai jab R' kisi kisi ho, agr R unknown hua to E' wale method se jenge.
- (5) agr question me braking action kha dia to E ki polarity badalni padegi. Ye phir power load se source ki taraf jaegi to bhi E ki polarity badalenge qki wo braking inversion ka case hata hai.

Special Note : Agr kabhi question me de dia ki ~~initial~~ initial current zero hai aur $t = t_o$ pe switch close hoga to t_o is firing angle.

Concept of Power factor :

$$(1) \text{ Input power factor} = C.D.F \times D.F$$

$$(2) \text{ Input power factor} = \cos \phi = \frac{V_o I_o}{V_{s1} I_{s1}}$$

only applicable for R-L and R-LE load.

$$(3) \text{ Input power factor for R load} = \cos \phi = \frac{I_o R^2}{V_{s1} I_{s1}}$$

$$(4) \text{ Input power factor for R-E load} = \cos \phi = \frac{I_o^2 R + E I_o}{V_{s1} I_{s1}}$$


$I_o \rightarrow$ o/p average current
 $I_{s1} \rightarrow$ o/p rms current.

$$V_{s1} = I_{s1} \cos \phi = V_{s1} I_{s1} \cos \phi$$

$$P = V_o I_o \text{ - only for RL and RLE load.}$$

For inversion $\alpha > 90^\circ$
 for rectification $\alpha < 90^\circ$

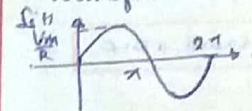→ Agr full wave rectifier hai aur load me $\sin^2 R$ hai to I_o (source current) ka waveform sinusoidal hata hai.



→ **Special note:** For R-E load

$$P_{dc} = I_o(\text{avg}) E$$

$$P_{ac} = I_o(\text{rms})^2 R + I_o E$$

→ In full wave rectifier, with continuous conduction (RL or RLE load),


$$O/P \text{ RMS Voltage} = \text{Source RMS Voltage}$$

→ For R-load

$$I_{o \text{ rms}} = \left[\frac{V_m^2}{2\pi R^2} \left[\frac{1}{2}(\beta - \alpha) + \frac{\sin 2\alpha}{4} \right] \right]^{1/2}$$


SINGLE PHASE SEMICONVERTER :- one quadrant operation converter. (Assumed to be ripple free and continuous).

(a) Symmetrical semiconverter :

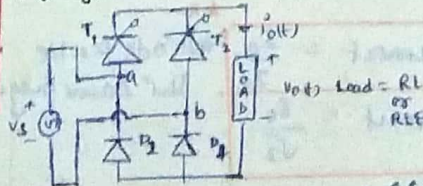

Conduction angle for each Diode and SCR = π , therefore it is called symmetrical configuration.

(b) Asymmetrical semiconverter :-

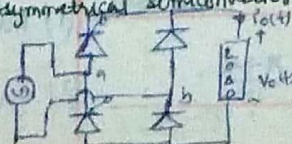

Conduction angle of T_1 and $T_2 = \pi - \alpha$
 conduction angle of D_1 and $D_2 = \pi + \alpha$
 ∴ conduction angle of T_1 and D_1 are different ∴ they are called asymmetrical.

Formulae and performance analysis of symmetrical and asymmetrical converters :-

$$V_{o(avg)} = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t$$


$$V_{o(avg)} = \frac{V_m}{\pi} [1 + \cos \alpha]$$

only valid when load is RL or RLE and I_o is ripple free and continuous.

$$PIV = V_m$$

for semiconverter

Source current:

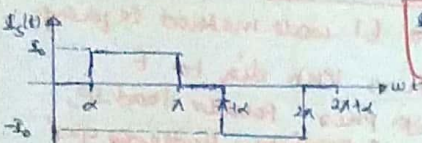

$$I_{s(rms)} = I_o \sqrt{\frac{\pi - \alpha}{\pi}}$$

$$I_{s(avg)} = 0$$

symmetrical current

$$I_{sn(t)} = \sum_{n=1,3,5}^{\infty} \frac{4}{n\pi} I_o \cos\left(\frac{n\alpha}{2}\right) \sin\left(n\omega t - \frac{n\alpha}{2}\right)$$

1. Fundamental rms of source current:

$$I_{s1} = \frac{4 I_o \cos \alpha / 2}{\pi \sqrt{2}} = \frac{2\sqrt{2} I_o \cos \alpha / 2}{\pi}$$

2. D.F.:

$$D.F. = \cos \alpha / 2$$

3. I.P.F.:

$$I.P.F. = C.D.F \times D.F.$$

4. Active Power:-

$$P = V_{s(rms)} I_{s1} \cos \alpha / 2$$

or

$$P = V_o I_o$$

only for RL or RLE load.

5. Reactive Power

$$Q = V_{s(rms)} I_{s1} \sin \alpha / 2$$

or

$$Q = V_o I_o \tan \alpha / 2$$

only for RL or RLE load.

→ agar semi converter me se ek SCR open hogya to semiconverter half wave rectifier ki tarah behave karega.

→ semi converter me RE load aya to uski full wave rectifier ka discontinuous wala case laga do i.e

$$V_{o(avg)} = \frac{1}{\pi} [V_m (\cos \alpha - \cos \beta) - E(\beta - \alpha)]$$

Symmetrical

In case of symmetrical semiconverter:

$$\text{Average thyristor current} = \frac{I_o}{2}$$


mode ke lie shi same hoga

$$\text{Rms thyristor current} = \frac{I_o}{\sqrt{2}}$$

→ conduction time t_c for symmetrical semiconverter = π / ω (Diode and SCR both)


→ conduction time t_c for asymmetrical S.C (for diode) = $\frac{\pi + \alpha}{\omega}$

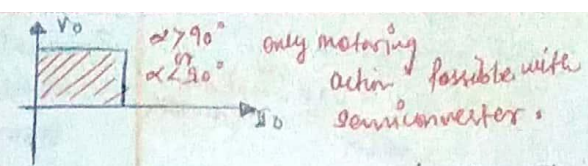→ t_c for asymmetrical S.C (for thyristor) = $\frac{\pi - \alpha}{\omega}$



Free wheeling diode is used in Symmetrical configuration. In asymmetrical, F.W.D is inbuilt.

Special case:

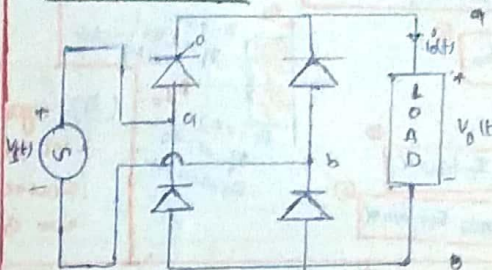

$$V_{o(avg)} = \frac{V_m}{2\pi} [3 + \cos \alpha]$$

Only true for R or RL or RLE continuous. Ripple free conduction.

→ Not true for RE load.

Special note: agar R or R-E load aye

semiconverter me with discontinuous current to semiconverter ka behaviour full wave bridge rectifier ki tarah hoga i.e we will use $V_{o(avg)} = \frac{1}{\pi} [V_m (\cos \alpha - \cos \beta) - E(\beta - \alpha)]$

Note: Kisi question me o/p current continuous aur constant de dia hai to uska rms value avg value ke barabar aega. i.e Rms value average value ke barabar hoga na ki average value rms value ke.

For symmetrical semiconverter:

$$t_{\text{off}} = \frac{\pi - \alpha}{\omega}$$

For asymmetrical semiconverter:

$$t_{\text{off}} = \frac{\pi}{\omega}$$

In case of Asymmetrical semiconverter:-

For Thyristor:

$$(1) \text{ Average current} = I_o \times \frac{\pi - \alpha}{2\pi}$$

$$(2) \text{ Rms current} = I_o \times \sqrt{\frac{\pi - \alpha}{2\pi}}$$

For diode:

$$(1) \text{ Avg. current} = I_o \times \frac{\pi + \alpha}{2\pi}$$

$$(2) \text{ Rms current} = I_o \times \sqrt{\frac{\pi + \alpha}{2\pi}}$$

Effect of Source Inductance :-

- Same sidha sidha ye karna hai jise formula m α hai waha bus α ko $\alpha + \mu$ se replace kardo.

μ : overlap angle.
 During overlap period, T and F.D both conducts.

① 1- ϕ Half wave rectifier :-

→ $V_{o(avg)} \text{ with } L_s = \frac{V_m}{2\pi} [1 + \cos(\alpha + \mu)]$


→ Reduction in voltage due to L_s (ΔV):

$\Delta V = \frac{V_m}{2\pi} [\cos(\alpha + \mu) - \cos \alpha]$

→ $\Delta V = f L_s I_o$

→ Conduction Angle of Thyristor (with L_s) = $\alpha + \mu$

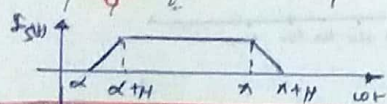Phase α → μ ko α ko $\alpha + \mu$ se replace kardo. Har formula jo banega usme α → $\alpha + \mu$ se replace hota dikhega.



Basic:

PHASE voltages:

$V_{an}(t) = V_m \sin \omega t$
 $V_{bn}(t) = V_m \sin(\omega t - 120^\circ)$
 $V_{cn}(t) = V_m \sin(\omega t - 240^\circ)$
 or
 $V_m \sin(\omega t + 120^\circ)$

Line voltages:

$V_{ab}(t) = \sqrt{3} V_m \cos(\omega t - 60^\circ)$
 $V_{bc}(t) = \sqrt{3} V_m \cos(\omega t - 180^\circ)$
 $V_{ca}(t) = \sqrt{3} V_m \cos(\omega t - 300^\circ)$
 or
 $\sqrt{3} V_m \cos(\omega t + 60^\circ)$

→ $PIV = \sqrt{3} V_m = V_{ML}$

→ conduction time of each diode = 120°

→ $V_{o(avg)} = \frac{3\sqrt{3} V_m}{2\pi} = \frac{3 V_{ML}}{2\pi}$


② 1- ϕ Full wave Rectifier:

→ $V_{o(avg)} \text{ with } L_s = \frac{V_m}{\pi} [\cos \alpha + \cos(\alpha + \mu)]$

→ conduction period of each SCR = $\pi + \mu$

→ $\Delta V = \frac{V_m}{\pi} [\cos \alpha - \cos(\alpha + \mu)]$

→ $\Delta V = 4 f L_s I_o$

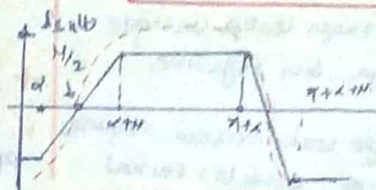

NOTE: fundamental current lags source voltage by $\mu/2$ angle.
 ∴ Fundamental Power factor = $\cos(\mu/2)$

③ 3 ϕ Full wave Rectifier:-

→ $\Delta V = \frac{3 V_m}{2\pi} [\cos \alpha - \cos(\alpha + \mu)]$

→ $\Delta V = 6 f L_s I_o$

→ During overlap period μ the 3 thyristors in conduct.

- Overlap angle $\propto$ Supply frequency
 $\propto$ Load current
 $\propto$ Source Inductance
 $\propto \frac{1}{\text{Supply voltage}}$

3- ϕ Rectifier

Common Cathode Connection: Same thile V_s ka graph bana lo i.e phase voltages ka waveform aur phir un waveform ka maximum ko trace kardo wahi V_o ka waveform hoga.

for example:

→ 3 diodes me me phase wo conduct karega jiska Anode potential maximum positive hoga.

→ aur ss connection me Ek bar me Ek hi diode conduct karega, jo diode conduct kia, usi ka phase voltage, o/p voltage me appear hoga. for example, agor phase 'a' wala diode conduct kia, to $V_o(t) = V_{an}(t)$ hoga.

→ aur jo do diode off blnge us samay unke across line voltage appear hoga. for example. phase 'a' ka diode conduct kia, to $V_o = V_{ba}$.

and $V_{o3}(\text{Phase C diode}) = V_{ca}$

→ It is a 3-pulse converter.

Common Mode connection of 3 ϕ Rectifier:-

- It's a 3 pulse converter.
- In this connection, the anode potential of all three diodes are at same potential. Out of 3 diode, the one will conduct whose Cathode potential is at maximum negative.
- Same bhi supply i.e phase voltages ke same phase ka waveform hoga aur usay hi ko minimum lelo aur usahi volt ka graph hoga.
- Same bhi jo diode on hoga uska voltage output me appear hoga but negative sign ke saath.
- Same jo diode off honge uske across voltage ko appear honge. For ex - diode 1 on hai to V_{D2} (b phase diode) = V_{ab}
 V_{D3} (c phase diode) = V_{ac}

PIV = $\sqrt{3} V_{mp} = V_{ML}$


Each conduction duration of diode = 120°

3 pulse converter.

$V_{avg} = \frac{3\sqrt{3}V_{mp}}{2\pi} = \frac{3V_{ML}}{2\pi}$

3- ϕ Half wave rectifier :- (controlled).

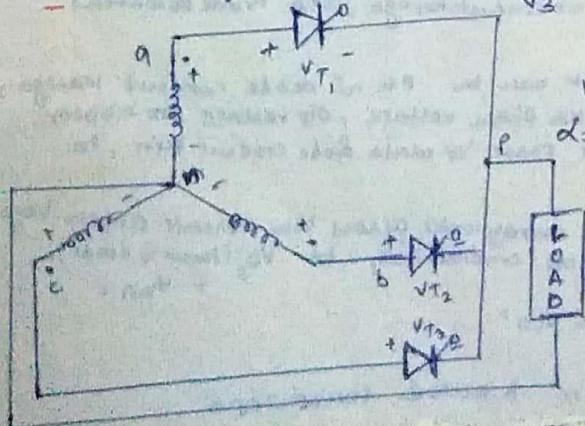- 3 pulse converter.
- Each thyristor will conduct maximum for 120° (Aise kum bhi kr skta hai).
- Each phase will conduct 120° .
- Average value of SCR current = $\frac{I_o}{3}$.
- RMS current of SCR = $\frac{I_o}{\sqrt{3}}$.
- Avg. value of source current = $\frac{I_o}{3}$.
- RMS value of source current = $\frac{I_o}{\sqrt{3}}$.



3- ϕ Mid point connection :-


- Same Hai Ek winding ko 2 tukdo me tod die hai aur $a_1, a_2, b_1, b_2, c_1, c_2$ karte hain 6 terminals milenge. Hain Ek phase me Ek diode thega common cathode connection me.
- $V_{a1}(t) = V_{mp} \sin \omega t$
 $V_{a2}(t) = V_{mp} \sin(\omega t - 120^\circ)$
 $V_{c1}(t) = V_{mp} \sin(\omega t + 120^\circ)$
 $V_{a2}(t) = -V_{a1}(t)$; $V_{b2}(t) = -V_{b1}(t)$;
 $V_{c2}(t) = -V_{c1}(t)$.

- Same Hai diode 60° ke liye conduct krta hai.
- Same bhi jo diode conduct krta hai phase voltage us samay 0p me appear hoga.
- PIV nikalne ke liye kisi bhi Ek diode ko lelo off state me aur ussamy bhi Ek hi diode conduct krta hoga beki 5 diode off honge.

- Manlo PIV nikalte same D_3 ke aur c_2 terminal se juda hai aur usay D_1 diode conduct krta jo terminal a_1 se juda hai to $V_{D3} = V_{c2a1}(t)$ hoga.

PIV = $+2V_{mp} = \frac{2}{\sqrt{3}} V_{ML}$

For Resistive load :-

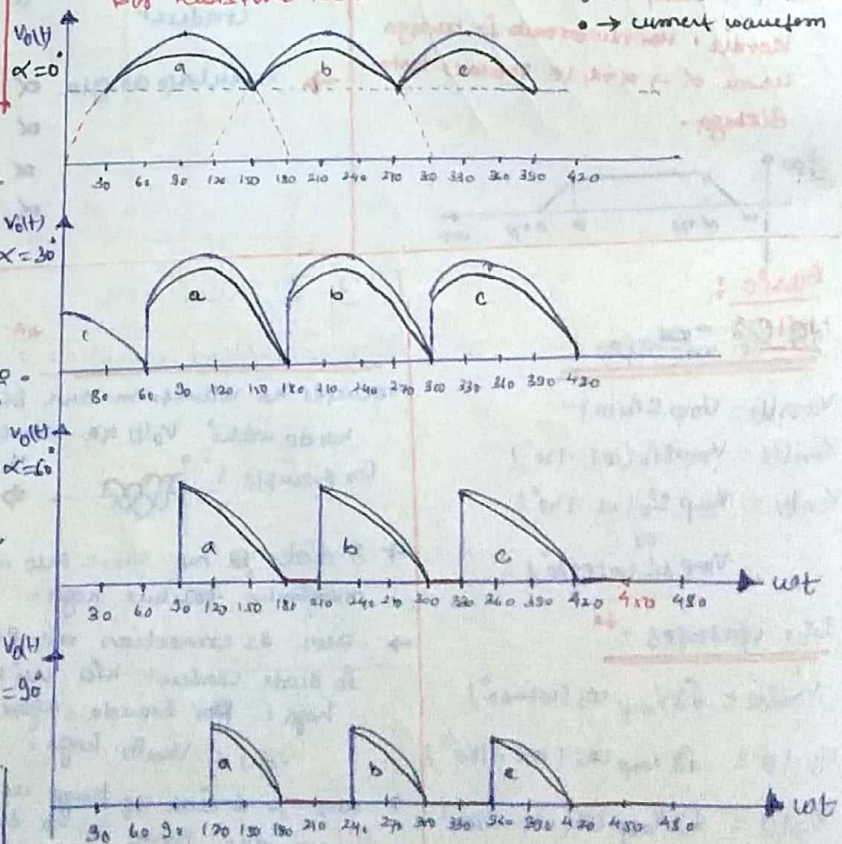

- Special Note :-
- (1) T_1 will start conducting at $30^\circ + \alpha$
 - (2) T_2 will start conducting at $150^\circ + \alpha$
 - (3) T_3 will start conducting at $270^\circ + \alpha$

→ In 3 ϕ Half wave rectifier, the dead end point is 180° i.e. current will become zero at 180° .

→ $PDI = \sqrt{3} V_{mp} = V_{mL}$ **

→ for $\alpha < 60^\circ$, $V_o(t)$ ka peak $V_s(t)$ ke peak ke barabar hoga.

→ But for $\alpha > 60^\circ$, $V_o(t)$ ka peak less than $V_s(t)$ hoga.

for R Load :-

→ Case 1: $\alpha < 30^\circ \rightarrow$ continuous conduction (Load current) $\frac{1}{3\pi} \int_{\alpha}^{180+\alpha} V_{mp} \sin \omega t dt$

$V_o(\text{avg}) = \frac{8\sqrt{3} V_{mp} \cos \alpha}{2\pi}$ $\sim \frac{2\sqrt{3}}{\pi} V_{mp} \cos \alpha$

→ Case 2: $\alpha > 30^\circ \rightarrow$ discontinuous conduction $V_o(\text{avg}) = \frac{1}{3\pi} \int_{\alpha}^{180+\alpha} V_{mp} \sin \omega t dt$

$V_o(\text{avg}) = \frac{3 V_{mp}}{2\pi} [1 + \cos(30^\circ + \alpha)]$


for range of 3 ϕ half wave rectifier, range of α is $0 < \alpha < 150^\circ$

→ $V_o(\text{avg}) = \frac{3\sqrt{3} V_{mp} \cos \alpha}{2\pi}$

- $V_o(\text{avg})$ in case of half wave rectifier for R, RL or RLE load is same.

Half wave Rectifier (3 ϕ) with RL and RLE load with continuous ripple free conduction :-

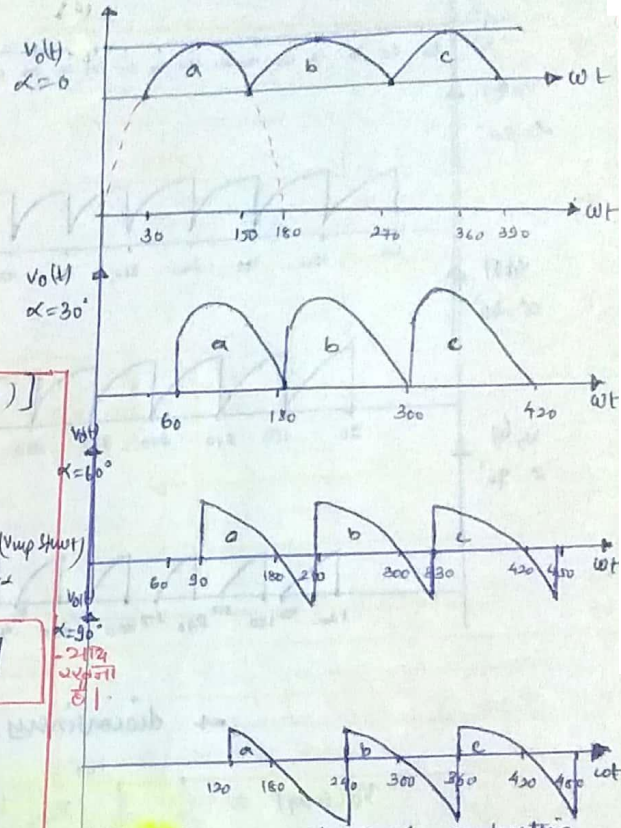range of α : $0^\circ < \alpha < 150^\circ$




Here for one value of α , conduction angle of each SCR will always be 120° .


3 ϕ Full wave rectifier (6-pulse converter).

- It is a 6 pulse converter.
- Each SCR will conduct for max^m 120° .
- Each pair of SCR will conduct max^m for 60° .
- Each phase will conduct for 240° .
- Average value of SCR current $= \frac{I_o}{3}$
- RMS value of SCR current $= \frac{I_o}{\sqrt{3}}$
- Avg. value of source current $= 0$
- RMS value of source current $= I_o \sqrt{\frac{2}{3}}$

→ $PDI = V_{mL} = \sqrt{3} V_{mp}$ **

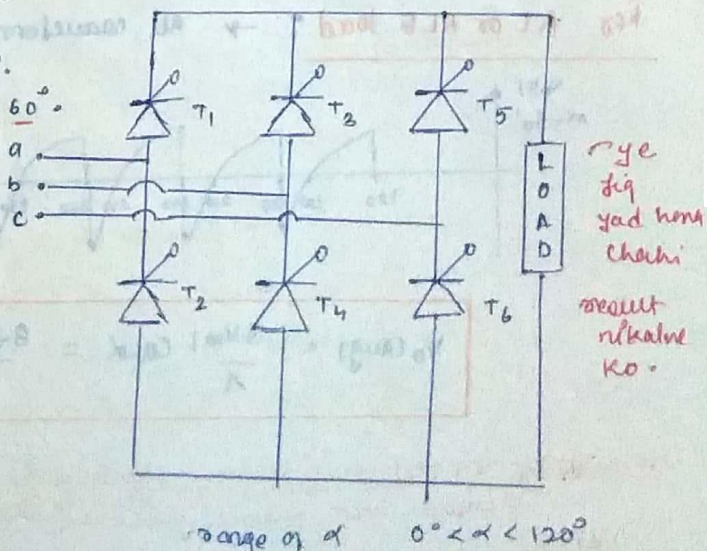

For R-load:

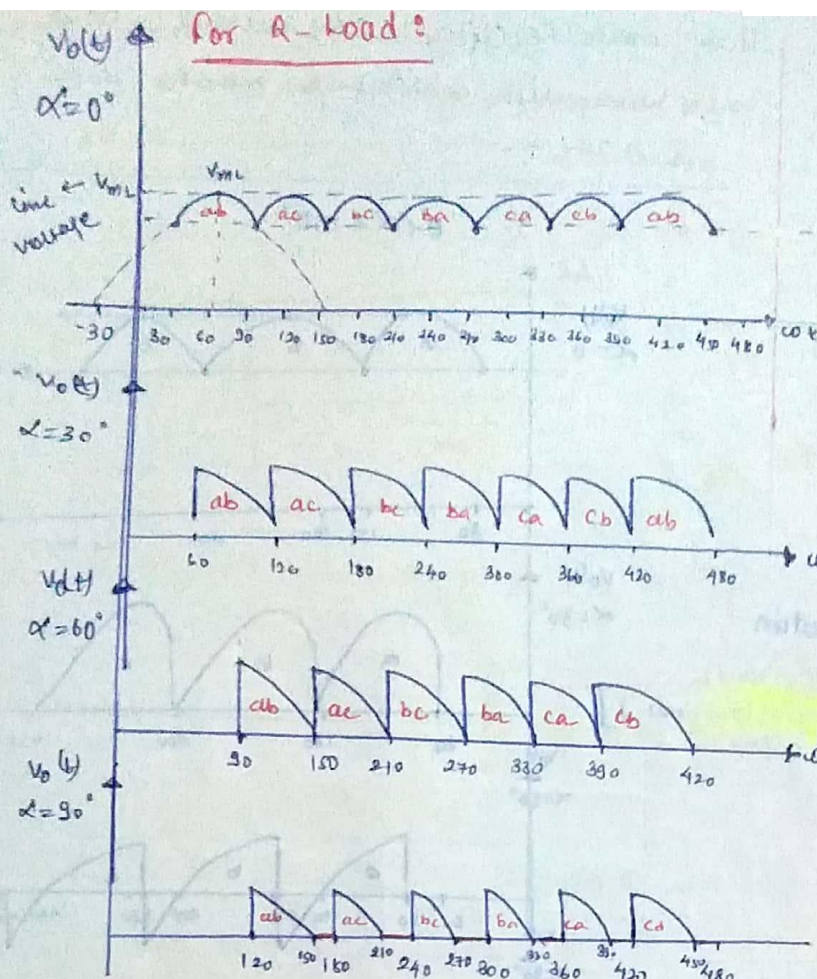

→ $V_o(t)$ $\alpha=0$ ka graph yad hona chahiye, usi ko reference leke $\alpha=30, 60, 90$ pe banalenge.

→ ab aur ac phelenge ye yad rehna chahiye. thir 10 repeat har wo uske age wale se replace hogi.

For Ex:
 $\begin{matrix} ab & ac & bc & ba \\ \downarrow & \downarrow & \downarrow & \downarrow \\ \text{same} & \text{change with next} & \text{same} & \text{change with next} \end{matrix}$

→ For R load:

CASE I: $\alpha < 60^\circ \rightarrow$ Continuous conduction.

$$V_o(\text{avg}) = \frac{1}{2\pi} \int_{30+\alpha}^{30+\alpha+360} V_{mL} \sin(\omega t + 30^\circ) d\omega t$$

$$V_o(\text{avg}) = \frac{3V_{mL} \cos \alpha}{\pi} = \frac{3\sqrt{3} V_{mp} \cos \alpha}{\pi}$$


CASE II: $\alpha > 60^\circ \rightarrow$ discontinuous condition

$$V_o(\text{avg}) = \frac{1}{2\pi} \int_{30+\alpha}^{150} V_{mL} \sin(\omega t + 30^\circ) d\omega t$$

→ In 3 ϕ full wave rectifier dead point is 150° .

$$V_o(\text{avg}) = \frac{3V_{mL}}{\pi} [1 + \cos(60^\circ + \alpha)]$$

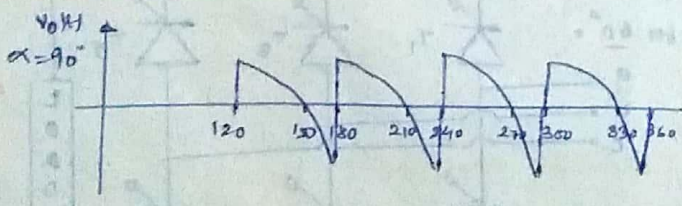For RL or RLE load: → All waveforms till $\alpha = 60^\circ$ are same as above.




$$V_o(\text{avg}) = \frac{3V_{mL} \cos \alpha}{\pi} = \frac{3\sqrt{3} V_{mp} \cos \alpha}{\pi}$$

NOTE: (1) For 3 ϕ Full wave rectifier for Pure R load, $\alpha < 60^\circ$ me continuous conduction always but supply free not always that's $V_o(\text{avg}) \neq 0$ (come).

(2) Advance angle beta to, $\alpha = 180^\circ$ - advance firing karna hai aur inversion ka case hogi uski formula me E ko - E se replace karenge.

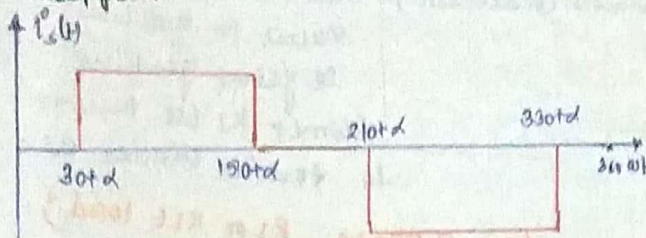(3) In 3 ϕ Full wave rectifier, 2 Thyristor conduct karte hai Ek time pe to agle uski voltage drop dia to V_o me $2V_T$ ghatenge aur 3 ϕ half wave dia to V_o me V_T ghatenge abi usme Ek thyristor on rehata hai Ek konme.

Performance Analysis of 3-φ Full wave Rectifier :-



Instantaneous value of source current :-

$$i_{sn}(t) = \sum_{n=1,3,5} \frac{4}{n\pi} I_0 \sin\left(\frac{n\alpha}{3}\right) \cdot \sin(n\omega t - n\alpha)$$

→ $I_{sr1} = \frac{\text{Peak}}{\sqrt{2}} = \frac{\sqrt{6} I_0}{\sqrt{2}} \rightarrow$ Input fundamental power factor or D.F. = $\cos \alpha$

→ $I_{sr} = I_0 \frac{\sqrt{2}}{3}$

→ D.P.F. = C.D.F. $\times \cos \alpha$

→ $C.D.F. = \frac{3}{\lambda} = \frac{I_{sr1}}{I_{sr}} = 0.955$

→ $P = V_0 I_0$ or $P = \sqrt{3} V_{srm} \cdot I_{srm} \cdot \cos \phi$

→ $Q = V_0 I_0 \tan \phi$

→ $\cos \phi = \frac{V_0 I_0}{\sqrt{3} I_{sr} V_{se}}$

Line values

Remember :-

1-φ Rectifier	$0 < \alpha < \pi$
3-φ Half wave	$0 < \alpha < 150^\circ$
3-φ Full wave	$0 < \alpha < 120^\circ$

Special Note :-

ckt turn off time :-

(1) For $\alpha < 60^\circ$,

$$\text{turn off} = \frac{240^\circ - \alpha}{\omega}$$

(2) For $\alpha > 60^\circ$,

$$\text{turn off} = \frac{180^\circ - \alpha}{\omega}$$

Note :- whenever we are taking the duration of ckt turn off time, take only the first negative portion of the V_f .

Special Note :- agao 3φ me R-E load agya

half wave rectifier ke case me to

$$I_0(\text{avg}) = \frac{3}{2\pi R} [V_m (\cos \alpha' - \cos \beta) - E (\beta - \alpha')]$$

Here $\alpha' = \alpha + 30^\circ$


Application of free wheeling diode :-

Free wheeling diode does not come into action if R load is there.

(Pure)

Free wheeling diode only takes place when the o/p voltage is going to be negative.

Case 1 :- 1-φ Full wave rectifier.

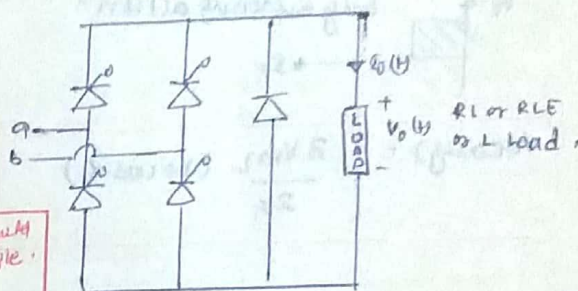


$V_0(\text{avg})$ (without F.D) = $\frac{2 V_m \cos \alpha}{\pi}$

$V_0(\text{avg})$ (with F.D) = $\frac{V_m}{\pi} [1 + \cos \alpha]$

Free wheeling lagana se P.F. Increase or Improve.

Semi-converter ke formula bhi yahi hai.

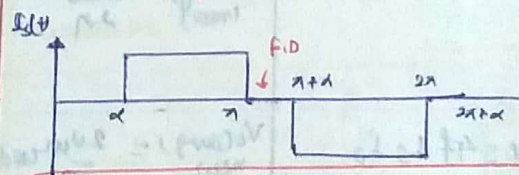as $V_0 \uparrow$, $P \uparrow$ then $\cos \phi \uparrow$.



$$i_{sn}(t) = \sum_{n=1,3,5} \frac{4}{n\pi} I_0 \cos\left(\frac{n\alpha}{2}\right) \sin(n\omega t - \frac{n\alpha}{2})$$

same as semi-converter result.

NOTE :- There is no need of the wheeling diode in 1-φ Full wave diode bridge rectifier under continuous ripple free conduction.

Case 2 :- 3-φ Full wave Rectifier :-

→ $\alpha \leq 60^\circ$, at this point V_0 is always +ve, hence F.D will not conduct.
→ $\alpha > 60^\circ$, V_0 has negative spikes there for F.D will conduct after $\alpha > 60^\circ$.

Conduction angle of F.W.D in 3-φ Full wave rectifier in one cycle of input = $\alpha - 60^\circ$ ($\alpha > 60^\circ$).

$$V_0(\text{avg}) = \frac{3 V_m}{\pi} [1 + \cos(60^\circ + \alpha)]$$

Same as Resistive load when $\alpha > 60^\circ$

Cases: 3 ϕ half wave.

- For $\alpha < 30^\circ$, F.W.D will not conduct ($\therefore$ continuous conduction)
- For $\alpha > 30^\circ$, F.W.D will conduct.


$$\text{Conduction Angle} = \alpha - 30^\circ$$

$\alpha > 30^\circ$

$$V_o(\text{avg}) (\text{with F.D}) = \frac{3}{2\pi} V_{mL} [1 + \cos(\alpha + 30^\circ)]$$


3- ϕ ^{semi} Convertor:-

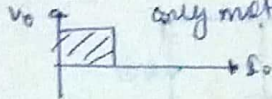- 3- ϕ Bridge, 3 SCRs and 3 diodes are there.
- only metering action.



$$V_o(\text{avg}) = \frac{3}{2\pi} V_{mL} (1 + \cos \alpha)$$

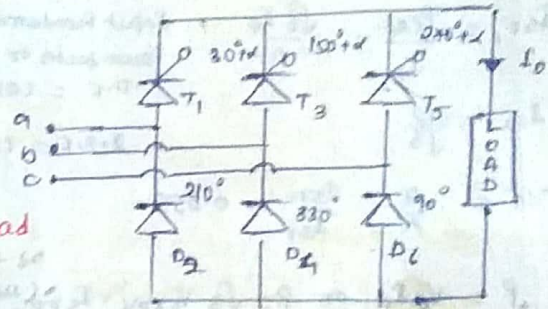- for any load
(continuous or discontinuous)



→ range of α : $0 \leq \alpha \leq 180^\circ$.

NOTE: Kabhi pucha
Peak instantaneous
value to graph
se gaene ya phir
current ke lie pucha
to formulae series se.

for 3 phase, RL or RLE load;

$$\cos \phi = \frac{V_o I_o}{\sqrt{3} V_{sL} I_{sL}}$$

if α is or
supply me
discrete hai

Source Inductance Effect at a glance:

converter	Average volt drop across source inductor	Average load voltage
1 pulse converter (1- ϕ Half wave rectifier)	$\Delta V = f L_s I_o$	$V_o(\text{avg})_{\text{new}} = \frac{V_{mp}}{2\pi} (1 + \cos \alpha) - f L_s I_o$
2 pulse converter (1- ϕ , full wave)	$\Delta V = 4 f L_s I_o$	$V_o(\text{avg})_{\text{new}} = \frac{2 V_{mp} \cos \alpha}{\pi} - 4 f L_s I_o$ $V_o(\text{avg})_{\text{new}} = \frac{V_{mp}}{\pi} [\cos \alpha + \cos(\alpha + \pi)]$
3 pulse converter (3- ϕ , Half wave)	$\Delta V = 3 f L_s I_o$	$V_o(\text{avg})_{\text{new}} = \frac{3 V_{mL} \cos \alpha}{2\pi} - 3 f L_s I_o$ $V_o(\text{avg})_{\text{new}} = \frac{3 V_{mL}}{4\pi} [\cos \alpha + \cos(\alpha + \pi)]$
6 pulse converter (3- ϕ , full wave)	$\Delta V = 6 f L_s I_o$	$V_o(\text{avg})_{\text{new}} = \frac{3 V_{mL} \cos \alpha}{\pi} - 6 f L_s I_o$ $V_o(\text{avg})_{\text{new}} = \frac{3 V_{mL}}{2\pi} [\cos \alpha + \cos(\alpha + \pi)]$