

CHAPTER

1.10

TWO PORT NETWORK

Statement for Q.1-4:

The circuit is given in fig. P.1.10.1-4

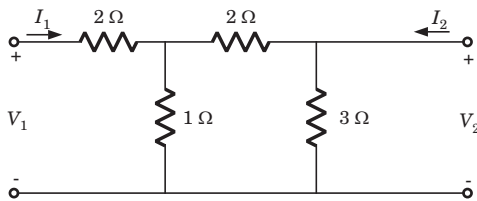


Fig. P.1.10.1-4

1. $[z] = ?$

(A) $\begin{bmatrix} -\frac{1}{2} & -\frac{3}{2} \\ -\frac{17}{6} & \frac{1}{2} \end{bmatrix}$

(B) $\begin{bmatrix} \frac{1}{2} & \frac{3}{2} \\ \frac{17}{6} & \frac{1}{2} \end{bmatrix}$

(C) $\begin{bmatrix} \frac{17}{6} & -\frac{1}{2} \\ -\frac{1}{6} & \frac{3}{2} \end{bmatrix}$

(D) $\begin{bmatrix} \frac{17}{6} & \frac{1}{2} \\ \frac{1}{6} & \frac{3}{2} \end{bmatrix}$

2. $[y] = ?$

(A) $\begin{bmatrix} \frac{3}{8} & \frac{1}{8} \\ \frac{1}{8} & \frac{17}{24} \end{bmatrix}$

(B) $\begin{bmatrix} \frac{3}{8} & -\frac{1}{8} \\ -\frac{1}{8} & \frac{17}{24} \end{bmatrix}$

(C) $\begin{bmatrix} \frac{17}{6} & \frac{1}{2} \\ \frac{1}{2} & \frac{3}{2} \end{bmatrix}$

(D) $\begin{bmatrix} \frac{17}{6} & -\frac{1}{2} \\ -\frac{1}{8} & \frac{3}{2} \end{bmatrix}$

3. $[h] = ?$

(A) $\begin{bmatrix} \frac{6}{17} & -\frac{3}{17} \\ \frac{3}{17} & \frac{24}{17} \end{bmatrix}$

(B) $\begin{bmatrix} \frac{8}{3} & \frac{1}{3} \\ -\frac{1}{3} & \frac{2}{3} \end{bmatrix}$

(C) $\begin{bmatrix} \frac{6}{17} & \frac{3}{17} \\ -\frac{3}{17} & \frac{24}{17} \end{bmatrix}$

(D) $\begin{bmatrix} \frac{8}{3} & -\frac{1}{3} \\ \frac{1}{3} & \frac{2}{3} \end{bmatrix}$

4. $[T] = ?$

(A) $\begin{bmatrix} \frac{17}{3} & 8 \\ 2 & 3 \end{bmatrix}$

(B) $\begin{bmatrix} \frac{17}{3} & -8 \\ -2 & 3 \end{bmatrix}$

(C) $\begin{bmatrix} -\frac{17}{3} & -8 \\ 2 & -3 \end{bmatrix}$

(D) $\begin{bmatrix} \frac{17}{3} & -8 \\ 2 & -3 \end{bmatrix}$

5. $[z] = ?$

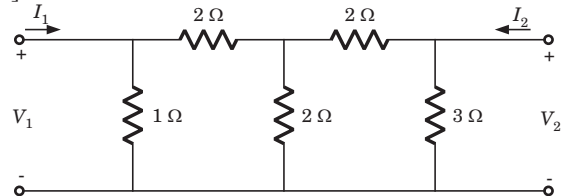


Fig. P.1.10.5

(A) $\begin{bmatrix} \frac{21}{16} & \frac{1}{8} \\ \frac{1}{8} & \frac{7}{12} \end{bmatrix}$

(B) $\begin{bmatrix} \frac{7}{9} & \frac{1}{6} \\ \frac{1}{6} & \frac{7}{4} \end{bmatrix}$

(C) $\begin{bmatrix} \frac{21}{16} & -\frac{1}{8} \\ -\frac{1}{8} & \frac{7}{12} \end{bmatrix}$

(D) $\begin{bmatrix} \frac{7}{9} & \frac{1}{3} \\ \frac{1}{3} & \frac{7}{4} \end{bmatrix}$

6. $[y] = ?$

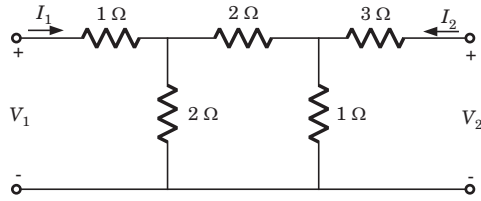


Fig. P.1.10.6

(A) $\begin{bmatrix} \frac{11}{41} & \frac{2}{41} \\ \frac{2}{41} & \frac{19}{41} \end{bmatrix}$

(B) $\begin{bmatrix} \frac{11}{41} & -\frac{2}{41} \\ -\frac{2}{41} & \frac{19}{41} \end{bmatrix}$

(C) $\begin{bmatrix} \frac{19}{41} & \frac{2}{41} \\ \frac{2}{41} & \frac{11}{41} \end{bmatrix}$

(D) $\begin{bmatrix} \frac{19}{41} & -\frac{2}{41} \\ -\frac{2}{41} & \frac{11}{41} \end{bmatrix}$

Statement for Q.7-10:

A two port is described by $V_1 = I_1 + 2V_2$,
 $I_2 = -2I_1 + 0.4V_2$

7. $[z] = ?$

(A) $\begin{bmatrix} 11 & -5 \\ -5 & 2.5 \end{bmatrix}$

(B) $\begin{bmatrix} 11 & 5 \\ 5 & 2.5 \end{bmatrix}$

(C) $\begin{bmatrix} 1 & -2 \\ 5 & 0.4 \end{bmatrix}$

(D) $\begin{bmatrix} 1 & 2 \\ -2 & 0.4 \end{bmatrix}$

8. $[y] = ?$

(A) $\begin{bmatrix} 11 & 5 \\ 5 & 2.5 \end{bmatrix}$

(B) $\begin{bmatrix} 1 & -2 \\ -2 & 4.4 \end{bmatrix}$

(C) $\begin{bmatrix} -2 & 4.4 \\ 4 & -2 \end{bmatrix}$

(D) $\begin{bmatrix} 11 & -5 \\ -5 & 2.5 \end{bmatrix}$

9. $[h] = ?$

(A) $\begin{bmatrix} 3 & -6 \\ 4 & -4 \end{bmatrix}$

(B) $\begin{bmatrix} 4 & -2 \\ -2 & 4.4 \end{bmatrix}$

(C) $\begin{bmatrix} 1 & 2 \\ -2 & 0.4 \end{bmatrix}$

(D) $\begin{bmatrix} 11 & 5 \\ 5 & 2.5 \end{bmatrix}$

10. $[T] = ?$

(A) $\begin{bmatrix} 2.2 & 0.5 \\ 0.2 & 0.5 \end{bmatrix}$

(B) $\begin{bmatrix} 2.2 & -0.5 \\ 0.2 & -0.5 \end{bmatrix}$

(C) $\begin{bmatrix} 1 & 2 \\ -2 & 0.4 \end{bmatrix}$

(D) $\begin{bmatrix} 1 & -2 \\ -2 & -0.4 \end{bmatrix}$

11. $[y] = ?$

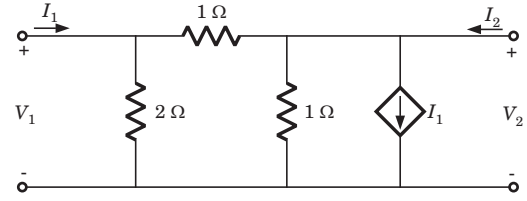


Fig. P.1.10.11

(A) $\begin{bmatrix} \frac{1}{2} & 1 \\ \frac{3}{2} & -1 \end{bmatrix}$

(B) $\begin{bmatrix} \frac{3}{2} & -1 \\ \frac{1}{2} & 1 \end{bmatrix}$

(C) $\begin{bmatrix} \frac{1}{2} & \frac{1}{2} \\ -\frac{1}{4} & \frac{3}{4} \end{bmatrix}$

(D) $\begin{bmatrix} -\frac{1}{4} & \frac{3}{4} \\ \frac{1}{2} & \frac{1}{2} \end{bmatrix}$

12. $[z] = ?$

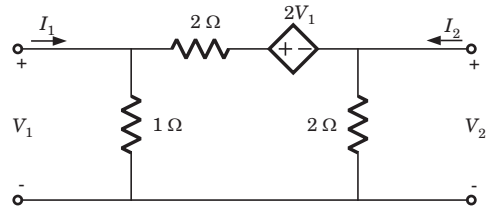


Fig. P.1.10.12

(A) $\begin{bmatrix} \frac{4}{3} & \frac{2}{3} \\ -\frac{2}{3} & \frac{2}{3} \end{bmatrix}$

(B) $\begin{bmatrix} \frac{1}{2} & -\frac{1}{2} \\ \frac{1}{2} & 1 \end{bmatrix}$

(C) $\begin{bmatrix} -\frac{2}{3} & \frac{2}{3} \\ \frac{4}{3} & \frac{2}{3} \end{bmatrix}$

(D) $\begin{bmatrix} \frac{1}{2} & 1 \\ \frac{1}{2} & -\frac{1}{2} \end{bmatrix}$

13. $[y] = ?$

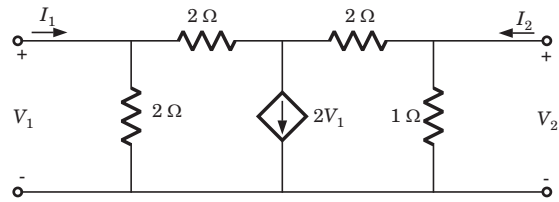


Fig. P.1.10.13

(A) $\begin{bmatrix} \frac{7}{4} & -\frac{1}{4} \\ \frac{1}{2} & \frac{5}{4} \end{bmatrix}$

(B) $\begin{bmatrix} \frac{7}{4} & -\frac{1}{4} \\ \frac{3}{4} & \frac{5}{4} \end{bmatrix}$

(C) $\begin{bmatrix} \frac{10}{19} & \frac{2}{19} \\ \frac{6}{19} & \frac{14}{19} \end{bmatrix}$

(D) $\begin{bmatrix} \frac{6}{19} & \frac{14}{19} \\ \frac{10}{19} & \frac{2}{19} \end{bmatrix}$

14. $[z] = ?$

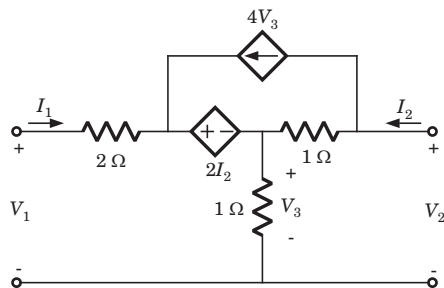


Fig. P.1.10.14

(A) $\begin{bmatrix} 2 & 3 \\ 3 & 3 \end{bmatrix}$

(B) $\begin{bmatrix} -3 & -2 \\ 3 & 3 \end{bmatrix}$

(C) $\begin{bmatrix} 3 & 3 \\ 3 & 2 \end{bmatrix}$

(D) $\begin{bmatrix} 3 & 3 \\ -3 & -2 \end{bmatrix}$

15. $[z] = ?$

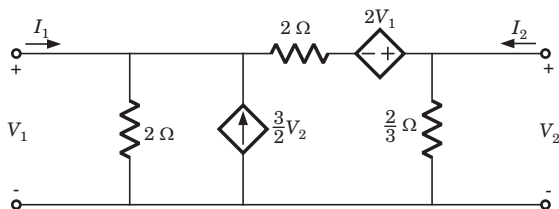


Fig. P.1.1.15

(A) $\begin{bmatrix} 2 & 2 \\ 3/2 & 2 \end{bmatrix}$

(B) $\begin{bmatrix} -2 & 3/2 \\ 2 & -2 \end{bmatrix}$

(C) $\begin{bmatrix} 2 & 3/2 \\ 2 & 2 \end{bmatrix}$

(D) $\begin{bmatrix} 2 & -2 \\ -3/2 & 2 \end{bmatrix}$

16. $[y] = ?$

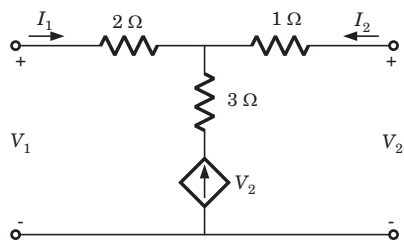


Fig. P.1.10.16

(A) $\begin{bmatrix} -1 & 1 \\ -1 & -2 \end{bmatrix}$

(B) $\begin{bmatrix} 1 & -1 \\ 1 & -2 \end{bmatrix}$

(C) $\begin{bmatrix} -2/3 & 1/3 \\ -1/3 & -1/3 \end{bmatrix}$

(D) $\begin{bmatrix} -2/3 & -1/3 \\ 1/3 & -1/3 \end{bmatrix}$

17. $[z] = ?$

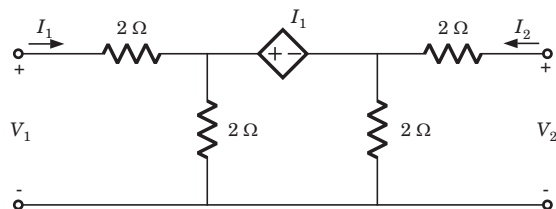


Fig. P.1.10.17

(A) $\begin{bmatrix} 3 & 2 \\ 6 & 1/7 \end{bmatrix}$

(B) $\begin{bmatrix} 6 & 1/7 \\ 3 & 2 \end{bmatrix}$

(C) $\begin{bmatrix} 7/4 & 1 \\ 1/2 & 3 \end{bmatrix}$

(D) $\begin{bmatrix} 1/2 & 3 \\ 7/4 & 1 \end{bmatrix}$

18. $[T] = ?$

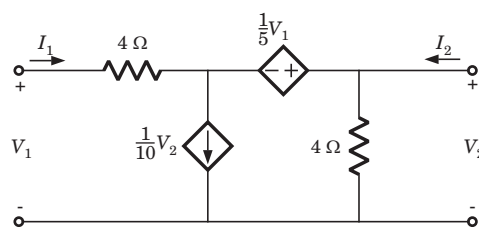


Fig. P.1.10.18

(A) $\begin{bmatrix} 0.35 & -1 \\ 2 & -3.33 \end{bmatrix}$

(B) $\begin{bmatrix} 2 & -3.33 \\ 0.35 & -1 \end{bmatrix}$

(C) $\begin{bmatrix} 2 & 3.33 \\ 0.35 & 1 \end{bmatrix}$

(D) $\begin{bmatrix} 0.35 & 1 \\ 2 & 3.33 \end{bmatrix}$

19. $[h] = ?$

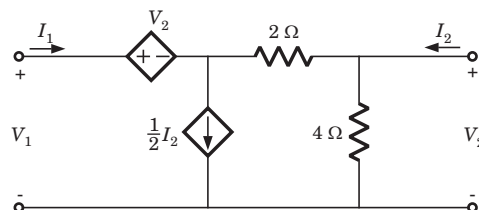


Fig. P.1.10.19

(A) $\begin{bmatrix} 4 & 3/2 \\ -2 & 1/2 \end{bmatrix}$

(B) $\begin{bmatrix} -2 & 1/2 \\ 4 & 3/2 \end{bmatrix}$

(C) $\begin{bmatrix} 4 & -3/2 \\ 2 & 1/2 \end{bmatrix}$

(D) $\begin{bmatrix} 2 & 1/2 \\ 4 & -3/2 \end{bmatrix}$

- (A) $\begin{bmatrix} Z_a + Z_{ab} & Z_{ab} \\ Z_{ab} & Z_b + Z_{ab} \end{bmatrix}$ (B) $\begin{bmatrix} Z_a - Z_{ab} & Z_{ab} \\ Z_{ab} & Z_b - Z_{ab} \end{bmatrix}$
 (C) $\begin{bmatrix} Z_a + Z_{ab} & -Z_{ab} \\ -Z_{ab} & Z_b + Z_{ab} \end{bmatrix}$ (D) $\begin{bmatrix} Z_{ab} - Z_a & Z_{ab} \\ Z_{ab} & Z_{ab} - Z_b \end{bmatrix}$

27. $[y] = ?$

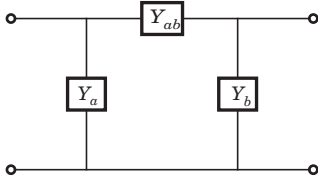


Fig. P.1.10.27

- (A) $\begin{bmatrix} Y_a + Y_{ab} & -Y_{ab} \\ -Y_{ab} & Y_b + Y_{ab} \end{bmatrix}$ (B) $\begin{bmatrix} Y_a - Y_{ab} & Y_{ab} \\ Y_{ab} & Y_b - Y_{ab} \end{bmatrix}$
 (C) $\begin{bmatrix} Y_{ab} - Y_a & Y_{ab} \\ Y_{ab} & Y_{ab} - Y_a \end{bmatrix}$ (D) $\begin{bmatrix} Y_a - Y_{ab} & -Y_{ab} \\ -Y_{ab} & Y_b - Y_{ab} \end{bmatrix}$

28. The y -parameters of a 2-port network are

$$[y] = \begin{bmatrix} 5 & 3 \\ 1 & 2 \end{bmatrix} \text{ S}$$

A resistor of 1 ohm is connected across as shown in fig. P.1.10.28. The new y -parameter would be

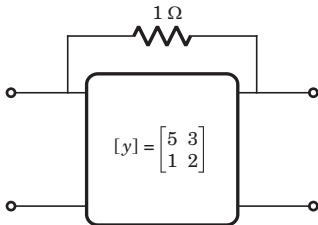


Fig. P.1.10.28

- (A) $\begin{bmatrix} 6 & 4 \\ 2 & 3 \end{bmatrix} \text{ S}$ (B) $\begin{bmatrix} 6 & 2 \\ 0 & 3 \end{bmatrix} \text{ S}$
 (C) $\begin{bmatrix} 5 & 4 \\ 2 & 2 \end{bmatrix} \text{ S}$ (D) $\begin{bmatrix} 4 & 4 \\ 2 & 1 \end{bmatrix} \text{ S}$

29. For the 2-port of fig. P.1.10.29, $[y_a] = \begin{bmatrix} 2 & 0 \\ 0 & 10 \end{bmatrix} \text{ mS}$

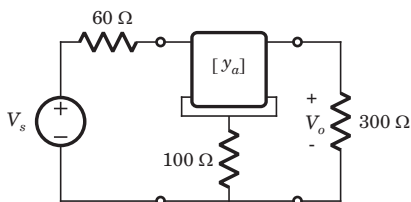


Fig. P.1.10.29

The value of $\frac{V_o}{V_s}$ is

- (A) $\frac{3}{32}$ (B) $\frac{1}{16}$
 (C) $\frac{2}{33}$ (D) $\frac{1}{17}$

30. The T-parameters of a 2-port network are

$$[T] = \begin{bmatrix} 2 & 1 \\ 1 & 1 \end{bmatrix}$$

If such two 2-port network are cascaded, the z -parameter for the cascaded network is

- (A) $\begin{bmatrix} 2 & -2 \\ -\frac{1}{2} & 1 \end{bmatrix}$ (B) $\begin{bmatrix} \frac{5}{3} & -\frac{1}{3} \\ -\frac{1}{3} & \frac{2}{3} \end{bmatrix}$
 (C) $\begin{bmatrix} \frac{5}{3} & \frac{1}{3} \\ \frac{1}{3} & \frac{2}{3} \end{bmatrix}$ (D) $\begin{bmatrix} 2 & 2 \\ \frac{1}{2} & 1 \end{bmatrix}$

31. $[y] = ?$

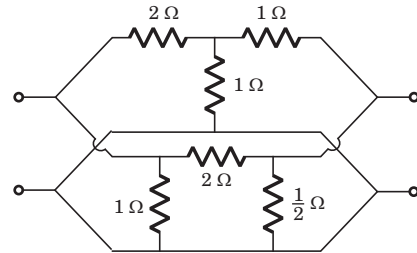


Fig. P.1.10.31

- (A) $\begin{bmatrix} \frac{19}{10} & -\frac{9}{10} \\ \frac{9}{10} & \frac{31}{10} \end{bmatrix}$ (B) $\begin{bmatrix} \frac{19}{10} & -\frac{7}{10} \\ \frac{7}{10} & \frac{31}{10} \end{bmatrix}$
 (C) $\begin{bmatrix} \frac{19}{10} & \frac{9}{10} \\ \frac{9}{10} & \frac{31}{10} \end{bmatrix}$ (D) $\begin{bmatrix} \frac{19}{10} & \frac{7}{10} \\ \frac{7}{10} & \frac{31}{10} \end{bmatrix}$

32. $[y] = ?$

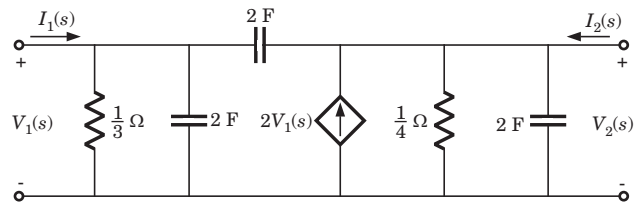


Fig. P.1.10.32

- (A) $\begin{bmatrix} s+3 & 2s \\ 2s+2 & 4 \end{bmatrix}$ (B) $\begin{bmatrix} s+3 & -2s \\ -2s-2 & 4s+4 \end{bmatrix}$
 (C) $\begin{bmatrix} s+3 & -2s \\ -2s-2 & 4 \end{bmatrix}$ (D) $\begin{bmatrix} 3s+3 & -2s \\ -2s-2 & 4s+4 \end{bmatrix}$

33. $h_{21} = ?$

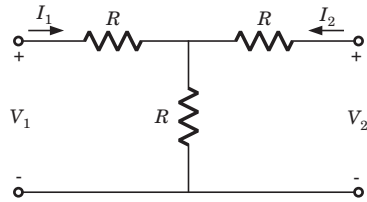


Fig. P.1.10.33

- (A) $-\frac{3}{2}$ (B) $\frac{1}{2}$
 (C) $-\frac{1}{2}$ (D) $\frac{3}{2}$

34. In the circuit shown in fig. P.1.10.34, when the voltage V_1 is 10 V, the current I is 1 A. If the applied voltage at port-2 is 100 V, the short circuit current flowing through at port 1 will be

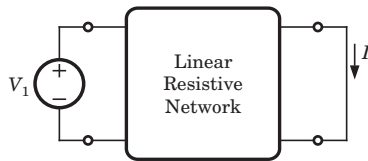


Fig. P.1.10.34

- (A) 0.1 A (B) 1 A
 (C) 10 A (D) 100 A

35. For a 2-port symmetrical bilateral network, if transmission parameters $A = 3$ and $B = 1 \Omega$, the value of parameter C is

- (A) 3 (B) 8 S
 (C) 8Ω (D) 9

36. A 2-port resistive network satisfy the condition $A = D = \frac{3}{2} B = \frac{4}{3} C$. The z_{11} of the network is

- (A) $\frac{4}{3}$ (B) $\frac{3}{4}$
 (C) $\frac{2}{3}$ (D) $\frac{3}{2}$

37. The circuit shown in fig. P.1.10.37 is reciprocal if a is

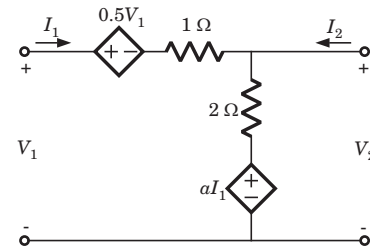


Fig. P.1.10.37

- (A) 2 (B) -2
 (C) 1 (D) -1

38. $Z_{in} = ?$

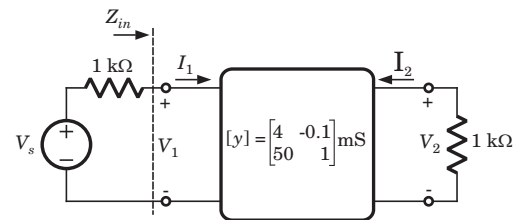


Fig. P.1.10.38

- (A) 86.4Ω (B) 64.3Ω
 (C) 153.8Ω (D) 94.3Ω

39. $V_1, V_2 = ?$

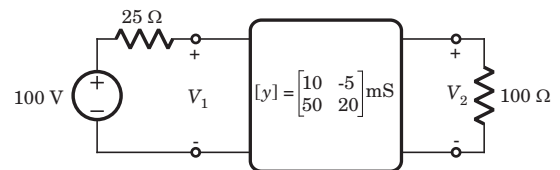


Fig. P.1.10.39

- (A) -68.6 V, 114.3 V (B) 68.6 V, -114.3 V
 (C) 114.3 V, -68.6 V (D) -114.3 V, 68.6 V

40. A 2-port network is driven by a source $V_s = 100 \text{ V}$ in series with 5Ω , and terminated in a 25Ω resistor. The impedance parameters are

$$[z] = \begin{bmatrix} 20 & 2 \\ 40 & 10 \end{bmatrix} \Omega$$

The Thevenin equivalent circuit presented to the 25Ω resistor is

- (A) 80 V, 2.8Ω (B) 160 V, 6.8Ω
 (C) 100 V, 2.4Ω (D) 120 V, 6.4Ω

$$[z] = \begin{bmatrix} \frac{7}{4} & 1 \\ \frac{1}{2} & 3 \end{bmatrix}$$

18. (D) Let I_3 be the clockwise loop current in center loop

$$I_1 = \frac{V_2}{10} + I_3, \quad V_2 = 4(I_2 + I_3) \Rightarrow I_3 = 0.25V_2 - I_2$$

$$\Rightarrow I_1 = 0.35V_2 - I_2 \quad \dots(i)$$

$$V_1 = 4I_1 - 0.2V_1 + V_2$$

$$12V_1 = 4(0.35V_2 - I_2) + V_2 = 2.4V_2 - 4I_2$$

$$\Rightarrow V_1 = 2V_2 - 3.33I_2 \quad \dots(ii)$$

19. (A) $V_2 = 4\left(I_2 + I_1 - \frac{I_2}{2}\right) \Rightarrow I_2 = -2I_1 + \frac{1}{2}V_2 \quad \dots(ii)$

$$I_1 = \frac{I_2}{2} + \frac{(V_1 - V_2) - V_2}{2} = -I_1 + \frac{V_2}{4} + \frac{V_1}{2} - V_2$$

$$\Rightarrow V_1 = 4I_1 + \frac{3}{2}V_2 \quad \dots(i)$$

20. (B) $I_1 = -V_2 + \frac{V_1}{1} + \frac{V_1 - V_2}{2} = \frac{3}{2}V_1 - \frac{3}{2}V_2 \quad \dots(i)$

$$I_2 = 2V_1 + \frac{V_2}{1} + \frac{V_2 - V_1}{2} = \frac{3}{2}V_1 + \frac{3}{2}V_2 \quad \dots(ii)$$

21. (D) $I_1 = 2V_1 + jV_1 + j(V_1 - V_2)$

$$\Rightarrow I_1 = (2 + j2)V_1 - jV_2 \quad \dots(i)$$

$$I_2 = \frac{V_2}{1} + V_1 + j(V_2 - V_1) = (1 - j)V_1 + (1 + j)V_2 \quad \dots(ii)$$

22. (B) $V_1 = \frac{I_1}{s} + sI_1 + sI_2 = \left(\frac{1}{s} + s\right)I_1 + sI_2 \quad \dots(i)$

$$V_2 = 2I_2 + 2sI_2 + sI_1 \Rightarrow V_2 = sI_1 + (2 + 2s)I_2 \quad \dots(ii)$$

23. (D) $Z_R = \frac{9}{n^2} = \frac{9}{9} = 1$

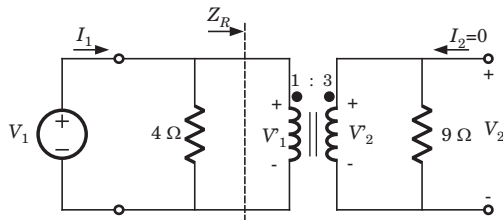


Fig. S1.10.23a

$$V_1 = (4 \parallel 1)I_1 = \frac{4}{5}I_1 \Rightarrow z_{11} = \frac{V_1}{I_1} = 0.8$$

$$V_2 = V'_2 = nV'_1 = 3\left(\frac{4}{5}I_1\right) \Rightarrow z_{21} = \frac{V_2}{I_1} = 2.4,$$

$$Z'_R = n^2 4 = 36$$

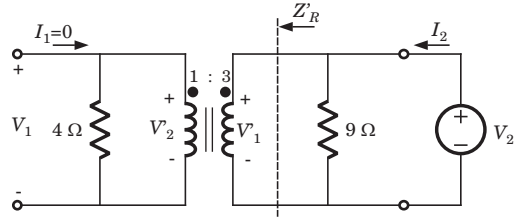


Fig. S1.10.23b

$$V_2 = (36 \parallel 9)I_2 = 7.2I_2 \Rightarrow z_{22} = \frac{V_2}{I_2} = 7.2,$$

$$z_{12} = z_{21} = 2.4$$

24. (C) $V_1 = 3sI_1 + 3sI_1 - 3sI_1 + 3sI_1 + 2sI_2$

$$\Rightarrow V_1 = 6sI_1 + 2sI_2 \quad \dots(i)$$

$$V_2 = 3sI_2 + 2sI_1 \Rightarrow V_2 = 2sI_1 + 3sI_2 \quad \dots(ii)$$

25. (C) $V_1 = \frac{V_2}{5} + 0(-I_2), \quad I_1 = (0)V_2 + 5(-I_2)$

26. (A) $V_1 = (Z_a + Z_{ab})I_1 + Z_{ab}I_2 \quad \dots(i)$

$$V_2 = (Z_a + Z_{ab})I_2 + Z_{ab}I_1 = Z_{ab}I_1 + (Z_a + Z_{ab})I_2 \quad \dots(ii)$$

27. (A) $I_1 = (V_1 - V_2)Y_{ab} + V_1Y_a$

$$\Rightarrow I_1 = V_1(Y_a + Y_{ab}) - V_2Y_{ab} \quad \dots(i)$$

$$I_2 = (V_2 - V_1)Y_{ab} + V_2Y_b = -V_1Y_{ab} + V_2(Y_b + Y_{ab}) \quad \dots(ii)$$

28. (B) y -parameter of 1Ω resistor network are

$$\begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix}$$

$$\text{New } y\text{-parameter} = \begin{bmatrix} 5 & 3 \\ 1 & 2 \end{bmatrix} + \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix} = \begin{bmatrix} 6 & 2 \\ 0 & 3 \end{bmatrix}.$$

29. (A) $[z_a] = \begin{bmatrix} 2 \text{ mS} & 0 \\ 0 & 10 \text{ mS} \end{bmatrix}^{-1} = \begin{bmatrix} 5000 & 0 \\ 0 & 100 \end{bmatrix}$

$$[z] = \begin{bmatrix} 5000 & 0 \\ 0 & 100 \end{bmatrix} + \begin{bmatrix} 100 & 100 \\ 100 & 100 \end{bmatrix} = \begin{bmatrix} 600 & 100 \\ 100 & 200 \end{bmatrix}$$

$$V_1 = 600I_1 + 100I_2, \quad V_2 = 100I_1 + 200I_2$$

$$V_s = 60I_1 + V_1 = 660I_1 + 100I_2, \quad V_2 = V_o = -300I_2$$

$$V_o = 100I_1 - \frac{2}{3}V_o \Rightarrow I_1 = \frac{V_o}{60}$$

$$V_s = 11V_o - \frac{V_o}{3} \Rightarrow \frac{V_o}{V_s} = \frac{3}{32}$$

30. (C) $[T_N] = \begin{bmatrix} 2 & 1 \\ 1 & 1 \end{bmatrix} \begin{bmatrix} 2 & 1 \\ 1 & 1 \end{bmatrix} = \begin{bmatrix} 5 & 3 \\ 3 & 2 \end{bmatrix}$

$$V_1 = 5V_2 - 3I_2, \quad I_1 = 3V_2 - 2I_2$$

$$3V_1 - 5I_1 = I_2 \Rightarrow V_1 = \frac{5}{3}I_1 + \frac{1}{3}I_2 \quad \dots(i)$$

$$V_2 = \frac{1}{3}I_1 + \frac{2}{3}I_2 \quad \dots(ii)$$

31. (B)

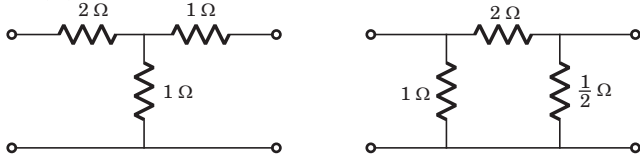


Fig. S.1.10.31a & b

$$[z_a] = \begin{bmatrix} 3 & 1 \\ 1 & 2 \end{bmatrix}, [y_a] = \begin{bmatrix} \frac{2}{5} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{3}{5} \end{bmatrix}, [y_b] = \begin{bmatrix} \frac{3}{2} & -\frac{1}{2} \\ -\frac{1}{2} & \frac{5}{2} \end{bmatrix}$$

$$[y] = [y_a] + [y_b] = \begin{bmatrix} \frac{19}{10} & -\frac{7}{10} \\ -\frac{7}{10} & \frac{31}{10} \end{bmatrix}$$

$$32. (D) [y_a] = \begin{bmatrix} 3s & -2s \\ -2s & 4s \end{bmatrix}, [y_b] = \begin{bmatrix} 3 & 0 \\ -2 & 4 \end{bmatrix}$$

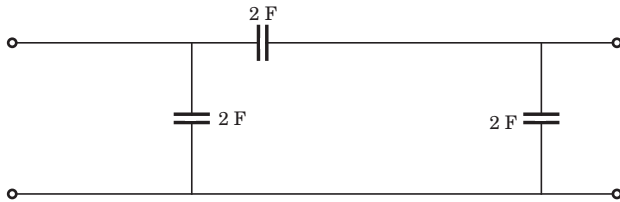


Fig. S.1.10.32a

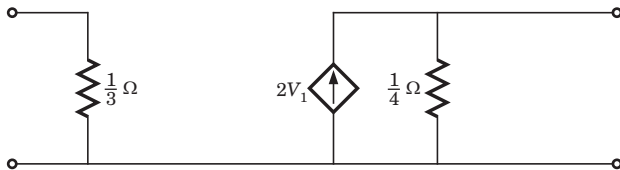


Fig. S.1.10.32b

$$[y] = [y_a] = [y_b] = \begin{bmatrix} 3s + 3 & -2s \\ -2s - 2 & 4s + 4 \end{bmatrix}$$

$$33. (C) h_{21} = \frac{I_2}{I_1} \bigg|_{V_2=0}, -I_2 = \frac{I_1 R}{R + R}, \frac{I_2}{I_1} = -\frac{1}{2}$$

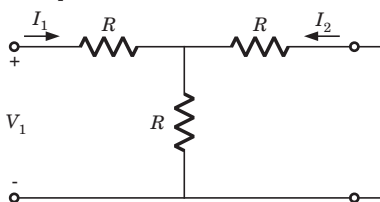


Fig. S.1.10.33

$$34. (C) \frac{I_2}{V_1} \bigg|_{V_2=0} = y_{21} = \frac{1}{10} = 0.1$$

$$\text{Interchanging the port } \frac{I'_2}{V'_1} = 0.1, I'_2 = 100 \times 0.1 = 10$$

35. (B) For symmetrical network $A = D = 3$

For bilateral $AD - BC = 1, 9 - C = 1, C = 8 \text{ S}$

$$36. (A) z_{11} = \frac{A}{C} = \frac{4}{3}$$

$$37. (A) V_1 = 0.5V_1 + I_1 + 2(I_1 + I_2) + aI_1$$

$$\Rightarrow V_1 = (6 + 2a)I_1 + 4I_2 \quad \dots(i)$$

$$V_2 = 2(I_1 + I_2) + aI_1 \Rightarrow V_2 = (2 + a)I_1 + 2I_2 \quad \dots(ii)$$

For reciprocal network

$$z_{12} = z_{21}, 4 = 2 + a \Rightarrow a = 2$$

$$38. (C) I_1 = 4 \times 10^3 V_1 - 0.1 \times 10^{-3} V_2$$

$$I_2 = 50 \times 10^{-3} V_1 + 10^{-3} V_2, V_2 = -10^3 I_2$$

$$-10^{-3} V_2 = 50 \times 10^{-3} V_1 + 10^{-3} V_2, V_2 = -25 V_1$$

$$10^3 I_1 = 4 V_1 + 2.5 V_1, \frac{V_1}{I_1} = \frac{10^3}{6.5} = 153.8$$

$$39. (B) I_1 = 10 \times 10^{-3} V_1 - 5 \times 10^{-3} V_2,$$

$$100 = 25 I_1 + V_1$$

$$100 - V_1 = 0.25 V_1 - 0.125 V_2 \Rightarrow 800 = 10 V_1 - V_2 \quad \dots(i)$$

$$I_2 = 50 \times 10^{-3} V_1 + 20 \times 10^{-3} V_2, V_2 = -100 I_2$$

$$V_2 = -5 V_1 - 2 V_2 \Rightarrow 3 V_2 + 5 V_1 = 0 \quad \dots(ii)$$

$$\text{From (i) and (ii) } V_1 = 68.6 \text{ V}, V_2 = -114.3 \text{ V.}$$

$$40. (B) 100 = 5 I_1 + V_1, V_1 = 20 I_1 + 2 I_2$$

$$\Rightarrow 100 = 25 I_1 + 2 I_2, V_2 = 40 I_1 + 10 I_2$$

$$800 - 5 V_2 = -34 I_2 \Rightarrow V_2 = 160 + 6.8 I_2$$

$$V_{TH} = 160 \text{ V}, R_{TH} = 6.8 \Omega$$

$$41. (B) V_1 = z_{11} I_1, V_2 = z_{21} I_1, \frac{V_2}{V_1} = \frac{z_{21}}{z_{11}}$$

$$42. (B) I_2 = y_{21} V_1 + y_{22} V_2, I_2 = -V_2 Y_L$$

$$y_{21} V_1 + (y_{22} + Y_L) V_2 = 0, \frac{V_2}{V_1} = \frac{-y_{21}}{(y_{22} + Y_L)}$$

$$43. (A) V_2 = z_{21} I_1 + z_{22} I_2, V_2 = -Z_L I_2$$

$$V_2 = z_{21} I_1 + z_{22} \left(-\frac{V_2}{Z_L} \right)$$

$$V_2 (Z_L + z_{22}) = z_{21} Z_L I_1, \frac{V_2}{I_1} = \frac{z_{21} Z_L}{z_{22} + Z_L}$$
