


Networks Test 5

Number of Questions: 25


Time: 60 min.

Directions for questions 1 to 25: Select the correct alternative from the given choices.

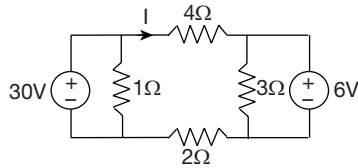
1. For the circuit shown in figure below the value of current I is _____



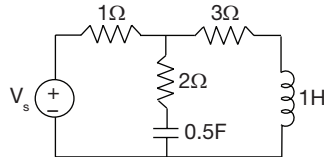
- (A) 2A (B) 6A
(C) 8A (D) 4A
2. If the power dissipated in the circuit shown below is 16W, then the value of V_s will be _____



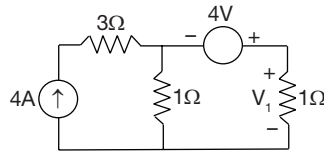- (A) 8V (B) 4V
(C) 2V (D) 6V
3. The value of V_1 in the circuit shown in the given figure is




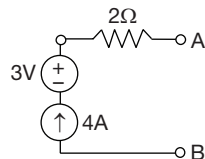- (A) -4V (B) 2V
(C) 4V (D) 0
4. Consider the network shown in below figure.




The Thevenin's voltage across the terminals 'A' and 'B' is _____.

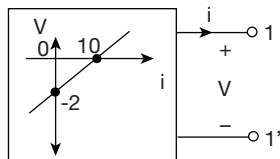- (A) 3V (B) -3V
(C) 10V (D) Indeterminate
5. The resistance seen from the terminals 1 and 1' of the device whose characteristic is shown in the figure below is



- (A) 5 Ω (B) 0.2 Ω
(C) 0.25 Ω (D) 0.4 Ω

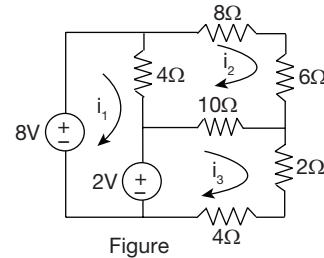
6. Consider the circuit shown in below figure



Determine the values of i_1 and i_3 .


- (A) 1.9A and 0.38A (B) 1.9A and 0.78A
(C) 0.4A and 0.38A (D) 0.78A and 1.4A

7. The current i_1 is _____

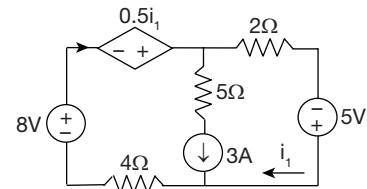

- (A) -1.2A (B) 0.15A
(C) 0.1816A (D) 2.15A


- 8.

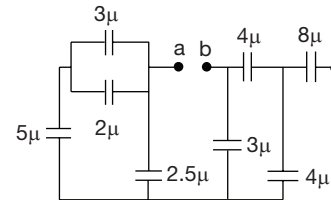

The equivalent capacitance between the terminals 'a' and 'b' _____.

- (A) 2.5 μF (B) 5 μF
(C) 10 μF (D) 12.5 μF


- 9.

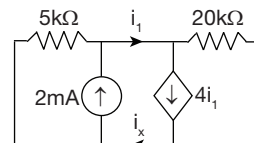

Determine the value of i_x ?

- (A) -0.18 mA (B) -1.8 mA
(C) 2.8 mA (D) -2.25 mA


10. Consider the network shown in below.

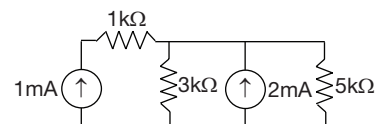

Determine the power dissipated by the $5\text{k}\Omega$ resistor

- (A) 1.58 mW
(B) 2.5 mW
(C) 6.328 mW
(D) 12.5 mW


11. Consider the circuit shown below.

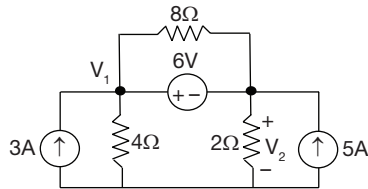

The values of V_1 and V_2 are respectively ____.

- (A) -8.66V and -14.66V
(B) 2.32 and -4.32V
(C) 14.66V and 8.66V
(D) 24V and 18V


12.

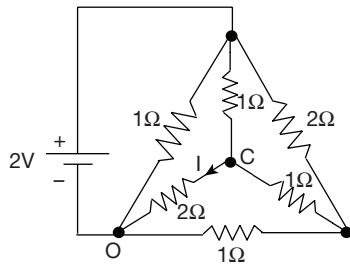

The current (I) through the branch (OC) is ____.


- (A) 0.3A
(B) 0.5714A
(C) 3.44A
(D) 0.8572A

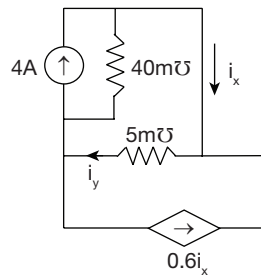13. The power across the dependent source is ____.




- (A) zero
(B) 15.42W
(C) 26.8W
(D) -16.13W

14. Find the value of current i_1 ?

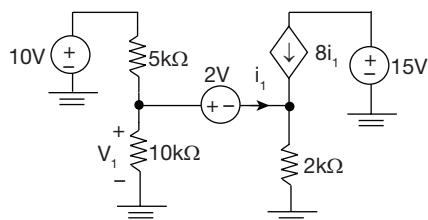

- (A) 0.317 mA
(B) 0.5 mA
(C) 0.218 mA
(D) 1.23 mA


15. Consider the circuit shown in below.

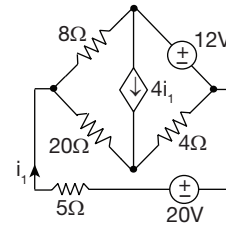

If only 20V voltage source is acting alone. Then the current i_1 is ____.


- (A) 0.72A
(B) 4.2A
(C) 0.32A
(D) 0.648A

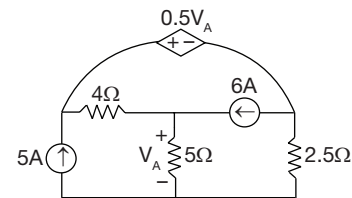16. The voltage across the 5Ω resistor is ____.



- (A) 20.28V
(B) 10.4V
(C) 12.5V
(D) 3.42V


17.

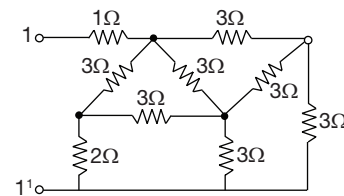

The input resistance of the given circuit is ____.

- (A) 5.4 Ω
(B) 1.5 Ω
(C) 3.2 Ω
(D) 2.57 Ω


18.

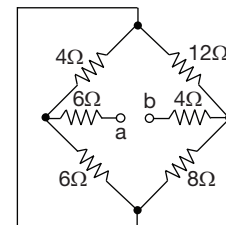

The equivalent resistance R_{ab} is ____.

- (A) 16.42 Ω
(B) 11.6 Ω
(C) 17.2 Ω
(D) 20 Ω

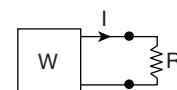19. The block-box, W contains independent sources. If $I = 4\text{A}$ and 2A for $R = 0$ and 3Ω , respectively, then what is the value of R for $I = 3\text{A}$?



- (A) 1 Ω
(B) 2 Ω
(C) 2.5 Ω
(D) 1.5 Ω

3.42 | Networks Test 5

20. For the circuit as shown in figure 1, the current through the ammeter is $4 \angle -30^\circ \text{A}$. What is the current in the ammeter for the circuit in figure 2?

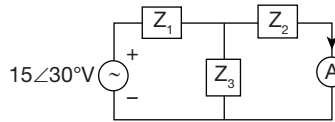


Figure 1



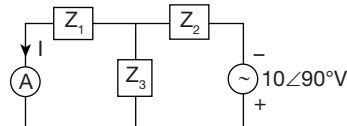


Figure 2

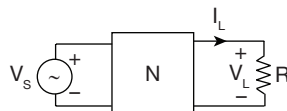- (A) $-2.66 \angle 30^\circ \text{A}$ (B) $2.66 \angle -30^\circ \text{A}$
 (C) $1.5 \angle 60^\circ \text{A}$ (D) $-1.5 \angle 30^\circ \text{A}$
21. In the circuit shown below, for different values of R , the values of V and I are given, others remaining same.
 When $R = \infty$, $V_L = 7.5 \text{V}$
 When $R = 0$, $I_L = 3 \text{A}$
 When $R = 5 \Omega$, the value of V_L is given by




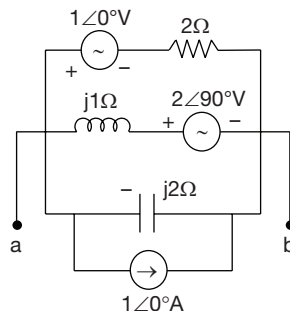- (A) 2.5V (B) 6V
 (C) 5V (D) 3V
22. Replace the below shown circuit by a single current source in parallel with an impedance.



- (A) $1.25 \angle -45^\circ \text{A}$ in series with $2\sqrt{2} \angle -45^\circ \Omega$
 (B) 2.5A in series with $2 \angle -45^\circ \Omega$
 (C) $1.25 \angle 90^\circ \text{A}$ in series with $2\sqrt{2} \angle 45^\circ \Omega$
 (D) None of these

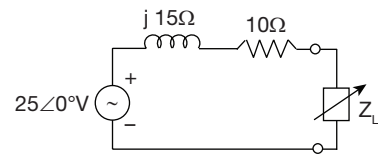
23. The maximum power that can be transferred in the load Z_L in the below circuit is ____.



- (A) 15.625W (B) 7.8125W
 (C) 4.75W (D) 8.66W

Data for questions 24 and 25:

Consider the circuit shown in below.

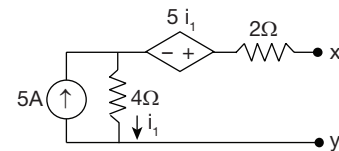


24. Find the thevenin's equivalent network across the load terminals 'x' and 'y'.
 (A) $V_{th} = 45 \text{V}$ and $R_{th} = 3 \Omega$
 (B) $V_{th} = 45 \text{V}$ and $R_{th} = 11 \Omega$
 (C) $V_{th} = 5 \text{V}$ and $R_{th} = 11 \Omega$
 (D) $V_{th} = -5 \text{V}$ and $R_{th} = 8 \Omega$
25. The maximum power transferred to the load terminals 'x' and 'y' is ____.
 (A) 184W (B) 46W
 (C) 96W (D) 102W

ANSWER KEYS

- | | | | | | | | | | |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 1. D | 2. A | 3. C | 4. D | 5. B | 6. A | 7. C | 8. A | 9. A | 10. C |
| 11. C | 12. B | 13. D | 14. C | 15. D | 16. A | 17. D | 18. C | 19. A | 20. A |
| 21. C | 22. A | 23. D | 24. C | 25. B | | | | | |

HINTS AND EXPLANATIONS

1. Redrawing the given circuit

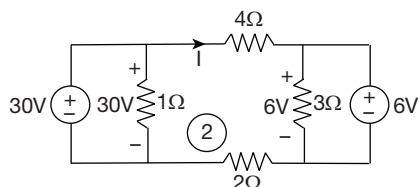

Apply mesh in loop 2 $-4I - 6 - 2I + 30 = 0$
 $6I = 24$

$I = 4 \text{ Amps}$

Choice (D)

2. From the given data $P_d = 16 \text{W}$


But source is d.c

$\therefore f = 0$ or circuit is in steady state

$$C = \frac{1}{2\pi fc} = \infty \Rightarrow o.c$$

$L \rightarrow S.C$

It becomes

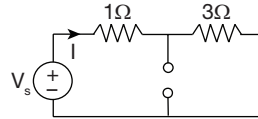

$$P = I^2 R$$


$$16 = I^2 \times 4$$

$$I = 2A$$

$$V_s = I.R = 2 \times 4 = 8V$$

Choice (A)

3.

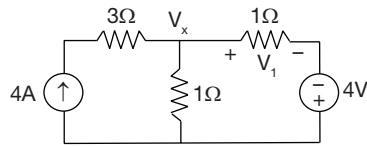

$$-4 + \frac{V_x}{1} + \frac{V_x + 4}{1} = 0$$

$$V_x = 0V$$

$$\therefore -V_1 + 4 = 0$$

$$V_1 = 4 \text{ volts}$$

Choice (C)

4. $V_{th} = V_{oc}$

$\therefore$ current flowing through the circuit is zero.


But given $I = 4A$

$\therefore$ KCL is not satisfying

$\therefore$ We can't determine V_{th} value

Choice (D)

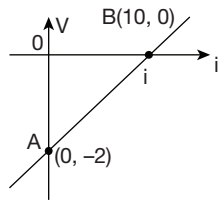5. Given that $V-I$ characteristics of circuit is



$A(0, -2), B(10, 0)$

x -axis $\rightarrow$ current

y -axis $\rightarrow$ voltage

we know

$$y - y_1 = \frac{y_2 - y_1}{x_2 - x_1} \cdot (x - x_1)$$

$$V + 2 = \frac{0 + 2}{10 - 0} [i - 0]$$

$$V = \frac{1}{5}i - 2$$

$$V = iR + V^1$$

$$\therefore R = 1/5 \Omega = 0.2 \Omega$$

Choice (B)

6. Applying mesh analysis

Apply KVL in each mesh

$$-8 + 4(i_1 - i_2) + 2 = 0$$

$$4(i_1 - i_2) = 6$$

$$i_1 - i_2 = 1.5$$

$\rightarrow$ (i)

$$14i_2 + 10(i_2 - i_3) + 4(i_2 - i_1) = 0$$

$$28i_2 - 4i_1 - 10i_3 = 0$$

$$i_1 - 7i_2 + 2.5i_3 = 0$$

$\rightarrow$ (ii)

$$10(i_3 - i_2) + 6i_3 - 2 = 0$$

$$-10i_2 + 16i_3 = 2$$

$$-5i_2 + 8i_3 = 1$$

$\rightarrow$ (iii)

From (i), (ii) and (iii) we get

$$i_1 = 1.9 \text{ Amp}, i_2 = 0.4 \text{ Amp and } i_3 = 0.38 \text{ Amp}$$


Choice (A)

7. The current source existing between two meshes.

$\therefore$ Apply super mesh concept

Let current in mesh I.

$$\therefore I - i_1 = 3A$$

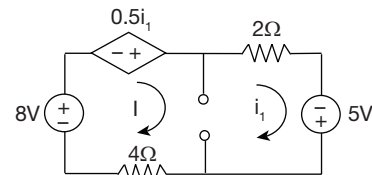

$$8 + 0.5i_1 - 2i_1 + 5 - 4I = 0$$

$$13 = 4I + 1.5i_1$$

$$I = 3 + i_1$$

$$13 = 12 + 4i_1 + 1.5i_1$$

$$5.5i_1 = 1$$

$$i_1 = 0.1818 \text{ Amp}$$


Choice (C)

2nd method:-

Calculate i_1 value by using Nodal Analysis.

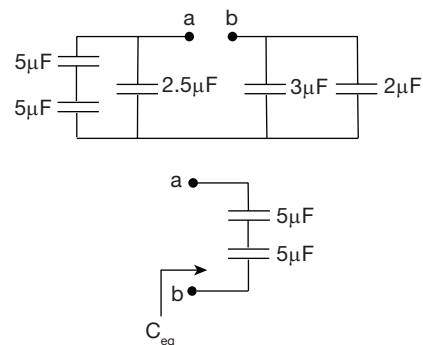8. $8\mu F$ capacitor does effect on the circuit


$\therefore$ the simplified circuit becomes



$$\Rightarrow C_{eq} = (5 \parallel 5) \mu F = 2.5 \mu F$$

Choice (A)

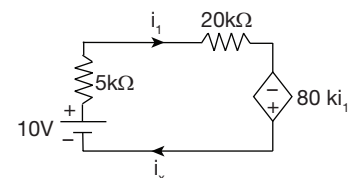9. Simplify the given network, by this source transformation




3.44 | Networks Test 5

$$\therefore 10 - 25k i_1 + 80k i_1 = 0$$

$$i_1 = -\frac{10}{55} \text{ mA} = -0.1818 \text{ mA} \quad \text{Choice (A)}$$

10.

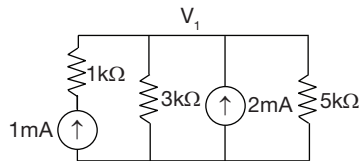

Apply nodal analysis at node V_1

$$-1\text{mA} + \frac{V_1}{3\text{k}} - 2\text{mA} + \frac{V_1}{5\text{k}} = 0$$

$$\frac{V_1}{3} + \frac{V_1}{5} = 3$$

$$8V_1 = 3 \times 3 \times 5$$

$$V_1 = 5.625$$

$$P = VI = \frac{V^2}{R} = 6.328 \text{ mW} \quad \text{Choice (C)}$$

11. From the given network Ideal voltage source exciting between two nodes V_1 and V_2 .

$\therefore$ It is super node

$$V_1 - 6 - V_2 = 0$$

$$V_1 - V_2 = 6 \quad \rightarrow (i)$$

Apply node equations at V_1 and V_2 [super node]

$$-3 + \frac{V_1}{4} + \frac{V_1 - V_2}{8} + \frac{V_2 - V_1}{8} + \frac{V_2}{2} - 5 = 0$$

$$\therefore \frac{V_1}{4} + \frac{V_2}{2} = 8$$

$$V_1 + 2V_2 = 32 \quad \rightarrow (ii)$$

From (i) and (ii)

$$2V_1 - 2V_2 = 12$$


$$V_1 + 2V_2 = 32$$

$$3V_1 = 44$$

$$V_1 = \frac{44}{3} \text{ volts} = 14.66 \text{ volts}$$

$$V_2 = V_1 - 6 = \frac{26}{3} = 8.66 \text{ V} \quad \text{Choice (C)}$$

12. Redraw the given circuit

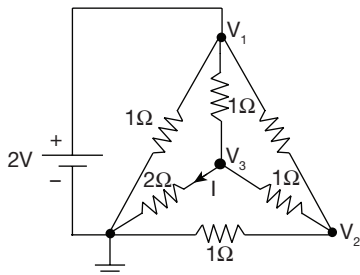

From the circuit $V_1 = 2$

Apply nodal analysis at node V_2 and V_3 $\rightarrow (i)$

$$\frac{V_2 - V_1}{2} + \frac{V_2 - 0}{1} + \frac{V_2 - V_3}{1} = 0$$

$$5V_2 - V_1 - 2V_3 = 0$$

$$V_1 - 5V_2 + 2V_3 = 0 \quad \rightarrow (ii)$$

$$\frac{V_3 - V_1}{1} + \frac{V_3}{2} + \frac{V_3 - V_2}{1} = 0$$

$$5V_3 - 2V_1 - 2V_2 = 0$$

$$2V_1 + 2V_2 - 5V_3 = 0 \quad \rightarrow (iii)$$

From (i), (ii) and (iii) we get


$$V_1 = 2V \text{ and } V_2 = 0.857V$$

$$V_3 = 1.1428V$$

$$I = \frac{V_3}{2} = 0.5714 \text{ Amp}$$

Choice (B)

13. Redraw the given circuit

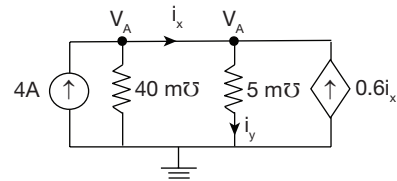

Apply nodal analysis at node V_A

$$-4 + V_A \times 40 \times 10^{-3} + V_A \times 5 \times 10^{-3} - 0.6 i_x = 0$$

$$45 \times 10^{-3} V_A = 4 + 0.6 i_x$$

$$i_x = 4 - V_A \times 40 \times 10^{-3}$$

$$0.6 i_x = 2.4 - 24 \times 10^{-3} V_A$$

$$69 V_A = (4 + 2.4) \times 10^3$$

$$V_A = 92.75 \text{ volts}$$

$$P = V_A I$$


$$= -92.75 \times 0.6 i_x$$

$$I_x = 0.289 \text{ Amp}$$

$$P = -16.13 \text{ W}$$

Choice (D)

14. Redraw the given circuit.

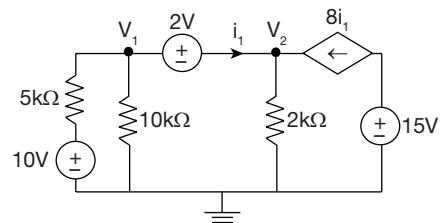

Applying supernode concept

$$\therefore V_1 - V_2 = 2V \quad \rightarrow (i)$$

$$\frac{V_1 - 10}{5\text{k}} + \frac{V_1}{10\text{k}} + \frac{V_2}{2\text{k}} = 8i_1$$

$$V_2 = 18k i_1$$

$$2V_1 - 20 + V_1 + 5V_2 = 80k i_1$$

$$3V_1 + 5V_2 - 20 = \frac{80}{18} V_2$$

$$3V_1 + 0.555V_2 = 20$$

$$V_1 = 5.94 \text{ volts}$$

$$V_2 = 3.94 \text{ volts}$$

$$V_2 = 9 i_1 \times 2\text{k}$$

$\rightarrow (ii)$


$$i_1 = \frac{3.94}{18} \text{ mA} = 0.218 \text{ mA}$$

2nd Method:-

Simplify the given circuit by using source transformation and get the value.

Choice (C)

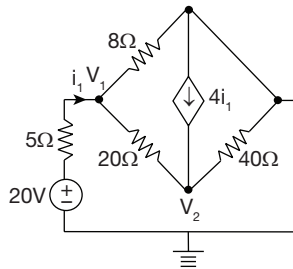15. Apply super position theorem to the given network.
Case (i) only 20V acting alone



$$\frac{V_1}{8} + \frac{V_1 - 20}{5} + \frac{V_1 - V_2}{20} = 0$$

$$5V_1 + 8V_1 - 160 + 2V_1 - 2V_2 = 0$$

$$15V_1 - 2V_2 = 160 \rightarrow (i)$$

As node V_2

$$\frac{V_2 - V_1}{20} + \frac{V_2}{40} = 4i_1 \quad i_1 = \frac{20 - V_1}{5}$$

$$2V_2 - 2V_1 + V_2 = 4 \times 40 \times \left[\frac{20 - V_1}{5} \right]$$

$$3V_2 - 2V_1 = 640 - 32V_1$$

$$30V_1 + 3V_2 = 640 \rightarrow (ii)$$

From (i) and (ii)

$$V_1 = 16.76 \text{ volts}$$


$$V_2 = 45.71 \text{ volts}$$

$$i_1 = \frac{20 - 16.76}{5}$$

$$i_1 = 0.648 \text{ Amp}$$

Choice (D)

16.

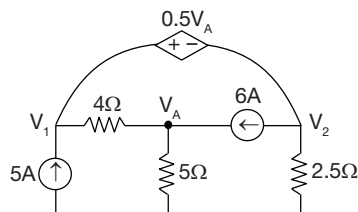

$$V_1 - V_2 = 0.5V_A$$

Applying super node concept at node V_1 and V_2

$$-5 + \frac{V_1 - V_A}{4} + \frac{V_2}{2.5} + 6 = 0$$

$$2.5(V_1 - V_A) + 4V_2 + 10 = 0$$

$$2.5V_1 + 4V_2 - 2.5V_A + 10 = 0$$

$$2.5V_1 + 4V_2 - 5(V_1 - V_2) + 10 = 0$$

$$-2.5V_1 + 9V_2 + 10 = 0$$

$$2.5V_1 - 9V_2 = 10 \rightarrow (i)$$

Apply nodal analysis at node V_A

$$\frac{V_A - V_1}{4} + \frac{V_A}{5} - 6 = 0$$

$$5V_A - 5V_1 + 4V_A = 120$$

$$9V_A - 5V_1 = 120$$

$$V_A = 2(V_1 - V_2)$$

$$18(V_1 - V_2) - 5V_1 = 120$$

$$13V_1 - 18V_2 = 120 \rightarrow (ii)$$

From (i) and (ii)





$$V_1 = 12.5 \text{ volts}$$

$$V_2 = 2.36 \text{ volts}$$

$$\therefore V_A = 2(V_1 - V_2) = 20.28 \text{ volts}$$

Choice (A)

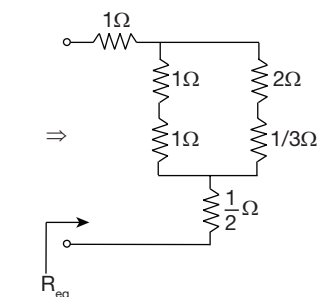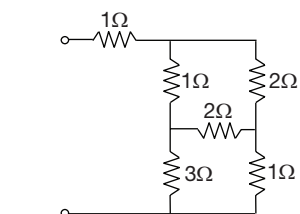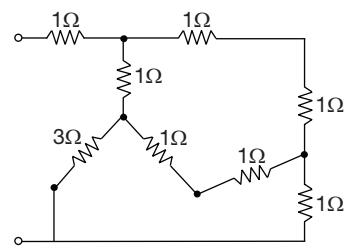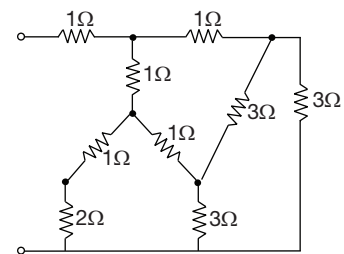
17. Simply the given network by using Δ - Y conversion.



$$R_{eq} = 1 + \{2 \parallel 7/3\} + \frac{1}{2} = 2.57 \Omega$$

Choice (D)

18. Redraw the given network

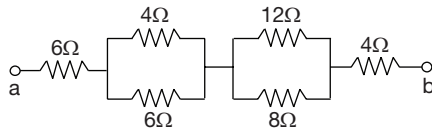


$$\therefore R_{ab} = 10 + \{4 \parallel 6\} + \{12 \parallel 8\}$$

$$= 10 + 2.4 + 4.8 = 17.2 \Omega$$

Choice (C)

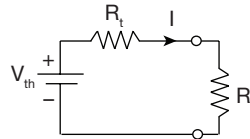19. Represent the block box its thevenin's model it becomes



$$I = \frac{V_{th}}{R_{th} + R}$$

If $R = 0$ and $I = 4A$

$$\frac{V_{th}}{R_{th}} = 4 \Rightarrow V_{th} = 4 R_{th}$$

→ (i)

$$2 = \frac{V_{th}}{R_{th} + 3}$$

→ (ii)

$$V_{th} = 2 R_{th} + 6$$

From (i) and (ii)

$$R_{th} = 3 \Omega \text{ and } V_{th} = 12V$$

$$\therefore I = \frac{V_{th}}{R_{th} + R}$$

$$3 = \frac{12}{3 + R}$$

$$9 + 3R = 12$$

$$3R = 3$$

$$R = 1 \Omega$$

Choice (A)


20. From the Reciprocity theorem $\frac{V_1}{V_2} = \frac{I_1}{I_2} = \text{constant}$

$$\frac{15 \angle 30^\circ}{-10 \angle 90^\circ} = \frac{4 \angle -30^\circ}{I_2}$$

$$\therefore I_2 = \frac{-40 \angle 60^\circ}{15 \angle 30^\circ} = -2.66 \angle 30^\circ \text{ Amp}$$

Choice (A)

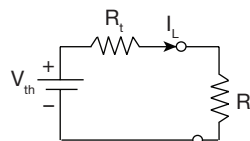21. The equivalent model of given network is




$$\therefore R = \infty; \text{ open circuit}$$

$$\therefore V_{OC} = V_{th} = 7.5V$$

$$R = 0; \text{ short circuit}$$

$$\therefore I_{SC} = I_N = 3A$$

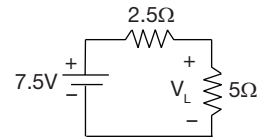
$$R_N = R_{th} = \frac{V_{oc}}{I_{sc}} = 2.5 \Omega$$



$$V_L = \frac{5}{7.5} \times 7.5 = 5 \text{ volts}$$

Choice (C)

22. Redrawing the given circuit

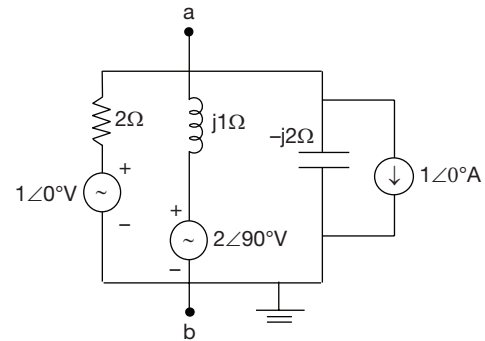

$$\frac{V_A - 1}{2} + \frac{V_A - 2 \angle 90^\circ}{j1} + \frac{V_A}{-j2} + 1 = 0$$

$$0.5V_A - 0.5 - jV_A + 2 + j0.5V_A + 1 = 0$$

$$V_A \{0.5 - j0.5\} = -2.5$$

$$V_A = \frac{-5}{1 - j1} = -3.53 \angle 45^\circ V$$

$R_{th} =$

(i) Deactive all the Independent sources.

$\therefore V \rightarrow S.C., I \rightarrow O.C.$


$$R_{ab} = R_{th} = [2 \parallel (j1) \parallel (-j2)] = 2 \{1 - j1\}$$

$$= 2\sqrt{2} \angle -45^\circ \Omega$$

$$V = I \cdot R_{th}$$

$$\therefore I_N = -1.248 \angle -45^\circ A$$
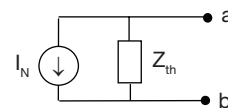
$$Z_{th} = 2\sqrt{2} \angle -45^\circ \Omega$$



Choice (A)


23. $Z_L = Z_S^*$

$$P = \frac{|V_{th}|^2}{4|Z_{th}|} = \frac{(25)^2}{4 \times \sqrt{100 + 225}} = \frac{625}{72.111}$$

$$= 8.66 \text{ watts}$$

Choice (D)

24.

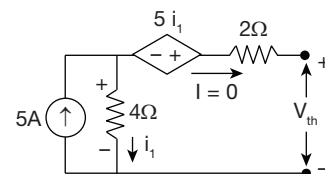


$$\therefore V_{th} - 2 \times 0 - 5i_1 - 4i_1 = 0$$

But $i_1 = 5A$
 $V_{th} = 45 \text{ volts}$

R_{th} :-

To calculate R_{th}

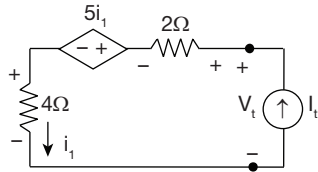- (i) Deactivate all the independent sources
- (ii) Connect one test source across the terminals 'x' and 'y'.



$$\therefore V_t - 2I_t - 5I_t - 4I_t = 0$$


$$V_t = 11 I_t$$

$$\frac{V_t}{I_t} = R_{th} = 11 \Omega$$

$$\therefore V_{th} = 45V \text{ and } R_{th} = 11 \Omega$$

Choice (C)

25.

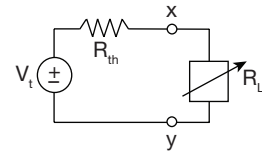

$$\therefore P_{\max} = \frac{V_{th}^2}{4 R_{th}} = \frac{(45)^2}{4 \times 11} = 46 \text{ watts.}$$

Choice (B)