
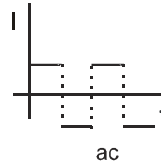
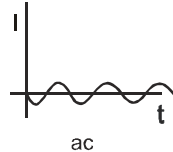
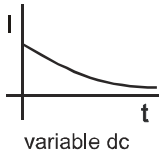
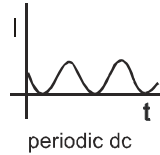


## 17. ALTERNATING CURRENT
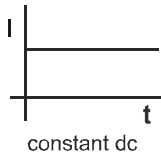
### 1. AC AND DC CURRENT :

A current that changes its direction periodically is called alternating current (AC). If a current maintains its direction constant it is called direct current (DC).




### 3. ROOT MEAN SQUARE VALUE:

Root Mean Square Value of a function, from  $t_1$  to  $t_2$ , is defined as  $f_{rms} = \sqrt{\frac{\int_{t_1}^{t_2} f^2 dt}{t_2 - t_1}}$ .
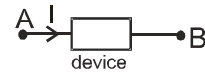
### 4. POWER CONSUMED OR SUPPLIED IN AN AC CIRCUIT:

$$\text{Average power consumed in a cycle} = \frac{\int_0^{\frac{2\pi}{\omega}} P dt}{\frac{2\pi}{\omega}} = \frac{1}{2} V_m I_m \cos \phi$$

$$= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cdot \cos \phi = V_{rms} I_{rms} \cos \phi.$$



Here  $\cos \phi$  is called **power factor**.

### 5. SOME DEFINITIONS:

The factor  $\cos \phi$  is called **Power factor**.

$I_m \sin \phi$  is called **wattless current**.


**Impedance**  $Z$  is defined as  $Z = \frac{V_m}{I_m} = \frac{V_{rms}}{I_{rms}}$

$\omega L$  is called **inductive reactance** and is denoted by  $X_L$

$\frac{1}{\omega C}$  is called **capacitive reactance** and is denoted by  $X_C$
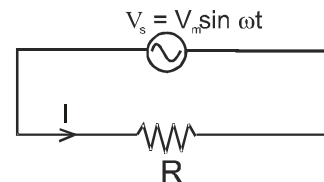
### 6. PURELY RESISTIVE CIRCUIT:

$$I = \frac{V_s}{R} = \frac{V_m \sin \omega t}{R} = I_m \sin \omega t$$



$$I_m = \frac{V_m}{R}$$

$$I_{rms} = \frac{V_{rms}}{R}$$

$$\langle P \rangle = V_{rms} I_{rms} \cos \phi = \frac{V_{rms}^2}{R}$$

## 7. PURELY CAPACITIVE CIRCUIT:

$$I = \frac{V_m}{\frac{1}{\omega C}} \cos \omega t$$



$$= \frac{V_m}{X_C} \cos \omega t = I_m \cos \omega t.$$

$X_C = \frac{1}{\omega C}$  and is called capacitive reactance.

$I_m$  leads by  $V_m$  by  $\pi/2$  Diagrammatically (phasor diagram) it is represented as



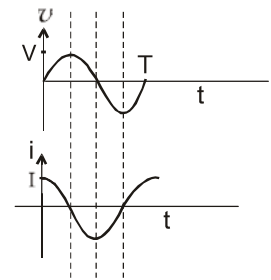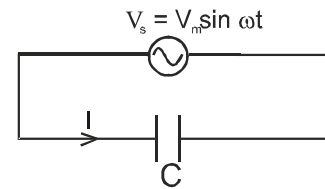Since  $\phi = 90^\circ$ ,  $\langle P \rangle = V_{rms} I_{rms} \cos \phi = 0$




## MAGNETIC EFFECT OF CURRENT & MAGNETIC FORCE ON CHARGE/CURRENT

### 1. Magnetic field due to a moving point charge


$$B = \frac{\mu_0}{4\pi} \frac{q(v \times r)}{r^3}$$

### 2. Biot-savart's Law

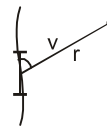


$$d\vec{B} = \frac{\mu_0 I}{4\pi} \frac{d\vec{\ell} \times \vec{r}}{r^3}$$
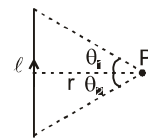
### 3. Magnetic field due to a straight wire




$$B = \frac{\mu_0}{4\pi} \frac{I}{r} (\sin \theta_1 + \sin \theta_2)$$
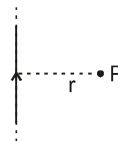
### 4. Magnetic field due to infinite straight wire




$$B = \frac{\mu_0}{2\pi} \frac{I}{r}$$

5. **Magnetic field due to circular loop**

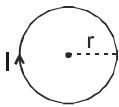
(i) At centre   $B = \frac{\mu_0 NI}{2r}$

(ii) At Axis  $B = \frac{\mu_0}{2} \frac{NIR^2}{(R^2 + x^2)^{3/2}}$

6. **Magnetic field on the axis of the solenoid**

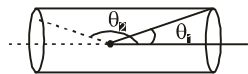  $B = \frac{\mu_0 nI}{2} (\cos \theta_1 + \cos \theta_2)$


7. **Ampere's Law**

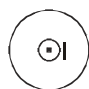  $\oint \mathbf{B} \cdot d\mathbf{\ell} = \mu_0 I$

8. **Magnetic field due to long cylindrical shell**

$B = 0, r < R$

$= \frac{\mu_0 I}{2\pi r}, r > R$

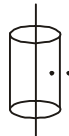


9. **Magnetic force acting on a moving point charge**


a.  $\mathbf{F} = q(\mathbf{v} \times \mathbf{B})$

(i)  $\mathbf{v} \perp \mathbf{B}$

$r = \frac{mv}{qB}$

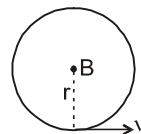

$T = \frac{2\pi m}{qB}$

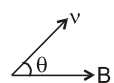(ii) 

$r = \frac{mv \sin \theta}{qB}$

$T = \frac{2\pi m}{qB}$

Pitch =  $\frac{2\pi mv \cos \theta}{qB}$

b.  $\mathbf{F} = q[(\mathbf{v} \times \mathbf{B}) + \mathbf{E}]$

10. Magnetic force acting on a current carrying wire

$$F = I(\ell \cdot B)$$

11. Magnetic Moment of a current carrying loop

$$M = N \cdot I \cdot A$$

12. Torque acting on a loop

$$\vec{\tau} = \vec{M} \times \vec{B}$$

13. Magnetic field due to a single pole

$$B = \frac{\mu_0}{4\pi} \cdot \frac{m}{r^2}$$

14. Magnetic field on the axis of magnet

$$B = \frac{\mu_0}{4\pi} \cdot \frac{2M}{r^3}$$

15. Magnetic field on the equatorial axis of the magnet

$$B = \frac{\mu_0}{4\pi} \cdot \frac{M}{r^3}$$

16. Magnetic field at point P due to magnet

$$B = \frac{\mu_0}{4\pi} \cdot \frac{M}{r^3} \sqrt{1 + 3 \cos^2 \theta}$$

