

Measurement of Resistance



Classification of Resistance

- Low resistance:** All resistance of the order of 1Ω and below.
Example: Winding coils of electrical motors, generators and transformers.
- Medium resistance:** Resistances from 1Ω upwards to about $0.1 M\Omega$
Example: Resistance of heaters, potentiometers.
- High resistance:** All resistances of the order of $0.1 M\Omega$ and above.
Example: Insulation of electrical cable and windings, insulation of motors generators and transformers.

Measurement of Medium Resistance

The different methods employed are:


- Ammeter-voltmeter method
- Wheatstone bridge method
- Ohmmeter method
- Substitution method

1. Ammeter Voltmeter Method

$$R_m = \frac{\text{voltmeter reading } V}{\text{ammeter reading } I}$$

where, R_m = measured value of resistance

(a) Circuit for higher resistance

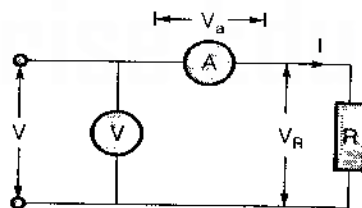

□ True value of resistance

$$R = R_{m1} - R_a$$

$$R_m = R_{m1} \left(1 - \frac{R_a}{R_{m1}} \right)$$

where, R_{m1} = Measured value of resistance


R_a = Resistance of ammeter

□ Relative error

$$\epsilon_r = \frac{R_{m1} - R}{R} = \frac{R_a}{R}$$

- To get minimum error, the test resistance should be more than the ammeter resistance so that this adjustment is suitable for measurement of high resistance.

(b) Circuit for lower resistance

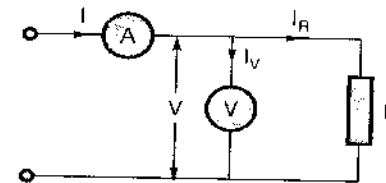

□ True value of resistance

$$R = \frac{R_{m2} R_v}{R_v - R_{m2}}$$

where, R_{m2} = Measured value of resistance

R_v = Resistance of voltmeter

For $R_v \gg R_{m2}$

$$R = R_{m2} \left(1 + \frac{R_{m2}}{R_v} \right)$$

□ Relative error

$$\epsilon_r = \frac{R_{m2} - R}{R} = \frac{-R_{m2}^2}{R_v R} \quad \left[\text{For } R_v \gg R_{m2} \right]$$

□ Approximate relative error

$$\epsilon = -\frac{R}{R_v} \quad \left[\text{For } R_{m2} \approx R \right]$$


- This circuit is suitable for measurement of low resistance under medium scale range to get minimum error.

Note:

Relative errors for above two cases are equal when true value of resistance,

$$R = \sqrt{R_a R_v}$$

2. Wheatstone Bridge

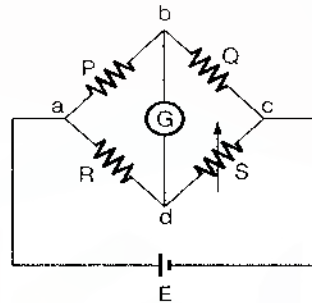

□ At balance

$$R = S \frac{P}{Q}$$

□ Sensitivity of Wheatstone bridge

$$S_B = \frac{\theta}{\Delta R/R} = \frac{S_v E S R}{(R+S)^2} \quad ; \text{ mm}$$

$$S_B = \frac{S_v E}{\frac{P}{Q} + 2 + \frac{Q}{P}}$$

where, S_v = Voltage sensitivity of galvanometer, mm/volt

E = Bridge voltage

P, Q = Branch resistances

θ = Deflection of galvanometer, mm

□ For a bridge with equal arms

$$S_B = \frac{S_v E}{4}$$


Note:

- For maximum bridge sensitivity

$$\frac{P}{Q} = \frac{R}{S} = 1$$

- Sensitivity of bridge is most important parameter as compared to accuracy, precision and resolution.

Equivalent circuit of Wheatstone bridge

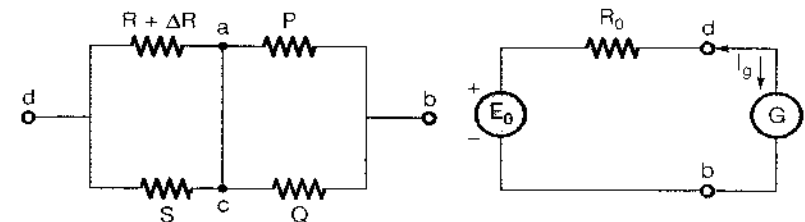

□ Galvanometer current

$$I_g = \frac{E_0}{R_0 + G}$$

where E_0 = Thevenin's or open circuit voltage appearing between terminals b and d with galvanometer circuit open circuited.

G = Resistance of the galvanometer circuit

$$E_0 = E \left[\frac{R + \Delta R}{2R + \Delta R} - \frac{1}{2} \right] \approx E \left(\frac{\Delta R}{4R} \right) \quad \text{as } \Delta R \ll R$$

ΔR = Change in resistance R

□ Thevenin equivalent resistance of bridge

$$R_0 = \frac{RS}{R+S} + \frac{PQ}{P+Q}$$

❑ Galvanometer deflection

$$\theta = \frac{S_v E S \Delta R}{(R + S)^2} = \frac{S_i E S \Delta R}{(R_0 + G)(R + S)^2}$$

where, S_i = Current sensitivity of galvanometer

❑ Bridge sensitivity

$$S_B = \frac{\theta}{\Delta R/R} = \frac{S_i E S R}{(R_0 + G)(R + S)^2}$$

❑ Current Sensitivity

$$S_i = \frac{\theta}{I_g}; \text{ mm}/\mu\text{A}$$

θ = Deflection in galvanometer

I_g = Current in galvanometer

❑ Voltage Sensitivity

$$S_v = \frac{\theta}{V_{Th}}; \text{ mm}/\text{V}$$


V_{Th} = Voltage across galvanometer

Note:

In Wheatstone bridge method, the effect of lead resistance is not eliminated hence it is not suitable for measurement of low resistance.

3. Ohmmeters

(a) Series Type Ohmmeter

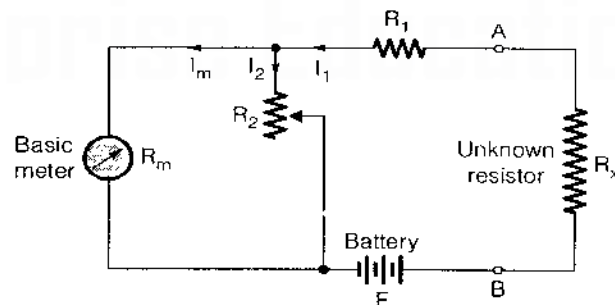

❑ Half scale resistance

$$R_h = R_1 + \frac{R_2 R_m}{R_2 + R_m}$$

❑ Meter current

$$I_m = \frac{E R_2}{(R_h + R_x)(R_2 + R_m)}$$


❑ Full scale deflection current

$$I_{fs} = \frac{E R_2}{R_h(R_2 + R_m)}$$

❑ Friction of full scale reading

$$S = \frac{I_m}{I_{fs}} = \frac{R_h}{R_x + R_h}$$

(b) Shunt Type Ohmmeter

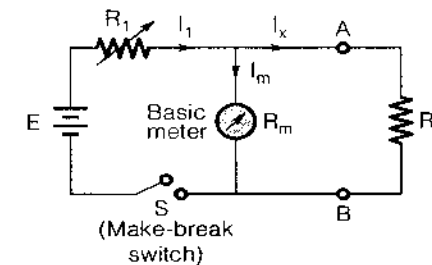

❑ Half scale reading of unknown resistance R_x is

$$R_h = \frac{R_1 R_m}{R_1 + R_m}$$

❑ Half scale reading of the meter

$$I_h = 0.5 I_{fs} = \frac{E R_h}{R_1 R_m + R_h(R_1 + R_m)}$$

where, R_m = Internal resistance of meter

R_1 = Adjustable resistor (as shown in figure)


E = Supply voltage

Measurement of low Resistance

The different methods employed are:

- (i) Kelvin's double bridge method
- (ii) Ammeter voltmeter method
- (iii) Potentiometer method

Kelvin's Double Bridge Method

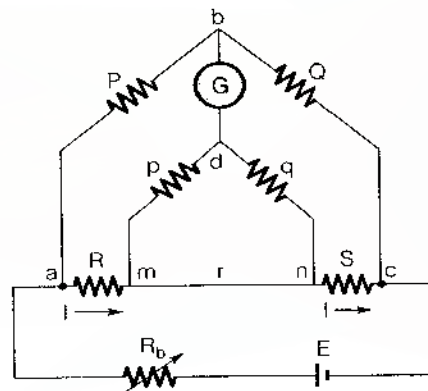

□ For zero galvanometer deflection

$$E_{ab} = E_{amd}$$

$$R = \frac{P}{Q} \cdot S + \frac{qr}{p+q+r} \left[\frac{P}{Q} - \frac{p}{q} \right]$$

□ If $\frac{P}{Q} = \frac{p}{q}$

then

$$R = \frac{P}{Q} \cdot S$$

Note:

Accuracies by Kelvin double bridge method


- (i) From $1000 \mu\Omega$ to 1.0Ω : 0.05%
- (ii) From $100 \mu\Omega$ to $1000 \mu\Omega$: 0.5% to 0.05%
- (iii) From $10 \mu\Omega$ to $100 \mu\Omega$: 0.5% to 0.2%

Measurement of High Resistance

The difference methods employed are:

- (i) Loss of charge method
- (ii) Meggar
- (iii) Direct deflection method
- (iv) Megohm bridge

1. Loss of Charge Method

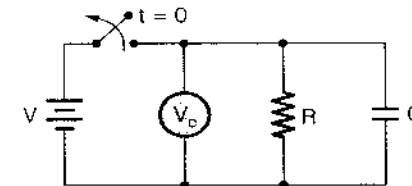

$$R = \frac{0.4343 t}{C \log_{10} \left(\frac{V}{V_c} \right)}$$


2. Meggar

- Meggar works on the principle of electrodynamicometer.
- Meggar is used to measure the insulation resistance of cable, motor and generator, etc.
- Deflecting torque angle is proportional to the resistance of the insulator, which is under test.
- It is also used to check the continuity of cable.
- No external control torque provided.
- Air friction damping is used.
- No need of external power supply.


Note:

High resistance have a guard terminal which is used to avoid leakage current.

Carry Foster Slide Wire Bridge

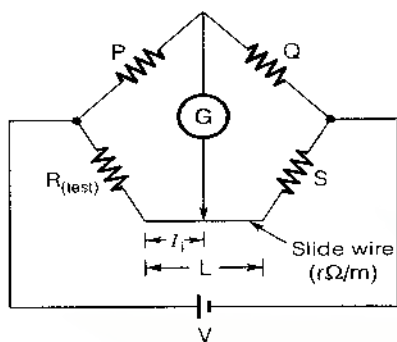

(Bridge-1)

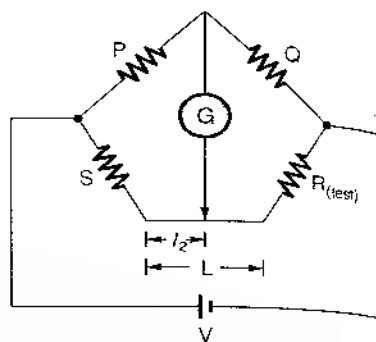

(Bridge-2)

From bridge (1)

$$\frac{P}{Q} + 1 = \frac{R + S + Lr}{S + (L - l_1)r} \quad \dots (i)$$

From bridge (2)

$$\frac{P}{Q} + 1 = \frac{R + S + Lr}{R + (L - l_2)r} \quad \dots (ii)$$

Equating equation (i) and (ii)

$$\boxed{R - S = (l_2 - l_1)r}$$

Note:

Carry Foster bridge method is used for medium resistance measurement by comparing with standard resistance.

.....

