

# CAPACITANCE

1. (i)  $q \propto V \Rightarrow q = CV$   
 $q$  : Charge on positive plate of the capacitor  
 $C$  : Capacitance of capacitor.  
 $V$  : Potential difference between positive and negative plates.

(ii) Representation of capacitor :  $-| \text{---} |$  ,  $-| \text{---} |$

(iii) Energy stored in the capacitor :  $U = \frac{1}{2} CV^2 = \frac{Q^2}{2C} = \frac{QV}{2}$

(iv) Energy density =  $\frac{1}{2} \epsilon_0 \epsilon_r E^2 = \frac{1}{2} \epsilon_0 K E^2$

$\epsilon_r$  = Relative permittivity of the medium.

$K = \epsilon_r$  : Dielectric Constant

For vacuum, energy density =  $\frac{1}{2} \epsilon_0 E^2$

(v) Types of Capacitors :

(a) **Parallel plate capacitor**

$$C = \frac{\epsilon_0 \epsilon_r A}{d} = K \frac{\epsilon_0 A}{d}$$

$A$  : Area of plates

$d$  : distance between the plates (  $\ll$  size of plate )

(b) **Spherical Capacitor :**


- Capacitance of an isolated spherical Conductor (hollow or solid )

$$C = 4 \pi \epsilon_0 \epsilon_r R$$


$R$  = Radius of the spherical conductor

- Capacitance of spherical capacitor

$$C = 4\pi\epsilon_0 \frac{ab}{(b-a)}$$

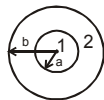


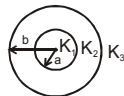- $$C = \frac{4\pi\epsilon_0 K_2 ab}{(b-a)}$$



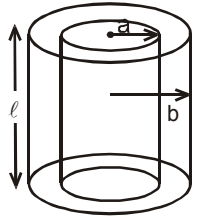(c) **Cylindrical Capacitor :**  $\ell \gg \{a, b\}$

$$\text{Capacitance per unit length} = \frac{2\pi\epsilon_0}{\ln(b/a)} \text{ F/m}$$



- (vi) Capacitance of capacitor depends on
- (a) Area of plates
  - (b) Distance between the plates
  - (c) Dielectric medium between the plates.
- (vii) Electric field intensity between the plates of capacitor


$$E = \frac{\sigma}{\epsilon_0} = \frac{V}{d}$$

$\sigma$  : Surface charge density

- (viii) Force experienced by any plate of capacitor :  $F = \frac{q^2}{2A\epsilon_0}$
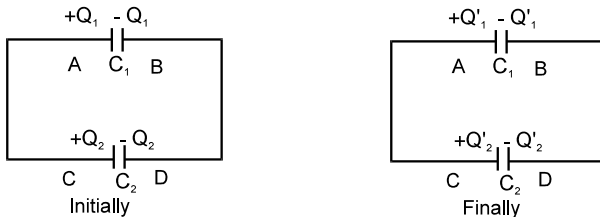
## 2. DISTRIBUTION OF CHARGES ON CONNECTING TWO CHARGED CAPACITORS:

When two capacitors are  $C_1$  and  $C_2$  are connected as shown in figure



- (a) Common potential :

$$\Rightarrow V = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2} = \frac{\text{Total charge}}{\text{Total capacitance}}$$

$$(b) \quad Q_1' = C_1 V = \frac{C_1}{C_1 + C_2} (Q_1 + Q_2)$$

$$Q_2' = C_2 V = \frac{C_2}{C_1 + C_2} (Q_1 + Q_2)$$

(c) Heat loss during redistribution :


$$\Delta H = U_i - U_f = \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} (V_1 - V_2)^2$$

The loss of energy is in the form of Joule heating in the wire.


### 3. Combination of capacitor :

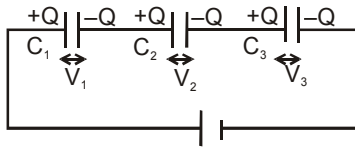(i) Series Combination

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \quad V_1 : V_2 : V_3 = \frac{1}{C_1} : \frac{1}{C_2} : \frac{1}{C_3}$$



(ii) Parallel Combination :

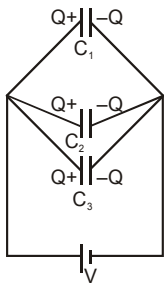


$$C_{eq} = C_1 + C_2 + C_3$$

$$Q_1 : Q_2 : Q_3 = C_1 : C_2 : C_3$$

### 4. Charging and Discharging of a capacitor :

(i) Charging of Capacitor ( Capacitor initially uncharged ):

$$q = q_0 ( 1 - e^{-t/\tau} )$$

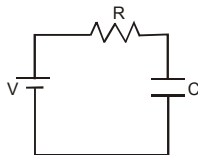


$q_0$  = Charge on the capacitor at steady state

$$q_0 = CV$$

$\tau$  : Time constant  $= CR_{eq}$ .
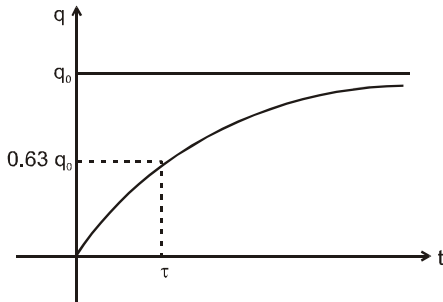
$$I = \frac{q_0}{\tau} e^{-t/\tau} = \frac{V}{R} e^{-t/\tau}$$





(ii) Discharging of Capacitor :

$$q = q_0 e^{-t/\tau}$$

$q_0$  = Initial charge on the capacitor


$$I = \frac{q_0}{\tau} e^{-t/\tau}$$

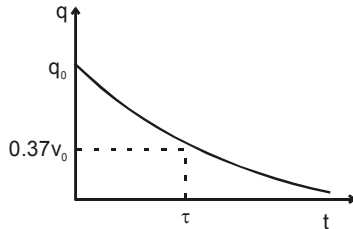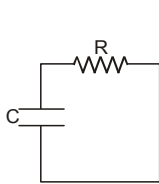

## 5. Capacitor with dielectric :

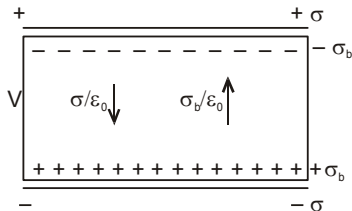(i) Capacitance in the presence of dielectric :

$$C = \frac{K\varepsilon_0 A}{d} = KC_0$$



$C_0$  = Capacitance in the absence of dielectric.

$$(ii) \quad E_{in} = E - E_{ind} = \frac{\sigma}{\epsilon_0} - \frac{\sigma_b}{\epsilon_0} = \frac{\sigma}{K\epsilon_0} = \frac{V}{d}$$


$E : \frac{\sigma}{\epsilon_0}$  Electric field in the absence of dielectric

$E_{ind}$  : Induced (bound) charge density.


$$(iii) \quad \sigma_b = \sigma \left(1 - \frac{1}{K}\right).$$

## 6. Force on dielectric

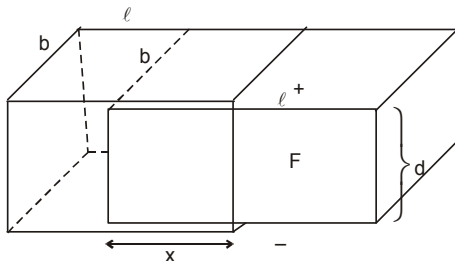(i) When battery is connected  $F = \frac{\epsilon_0 b(K-1)V^2}{2d}$



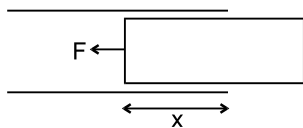(ii) When battery is not connected  $F = \frac{Q^2}{2C^2} \frac{dC}{dx}$



\* Force on the dielectric will be zero when the dielectric is fully inside.