

# CHAPTER

# 4.4

## DIGITAL LOGIC FAMILIES

### Statement for Q.1-2:

Consider the DL circuit of fig. P4.4.1-2.

 


Fig. P4.4.1-2

1. For positive logic the circuit is a  
 (A) AND (B) OR  
 (C) NAND (D) NOR
2. For negative logic the circuit is a  
 (A) AND (B) OR  
 (C) NAND (D) NOR
3. The diode logic circuit of fig. P4.4.3 is a

 


Fig. P4.4.3

- (A) AND (B) OR  
 (C) NAND (D) NOR

4. In the circuit shown in fig. P4.4.4. the output Z is

 


Fig. P4.4.4

- (A)  $AB + \bar{C}$  (B)  $\overline{ABC}$   
 (C)  $\overline{ABC}$  (D)  $ABC$

### Statement for Q.5-7:

Consider the AND circuit shown in fig. P4.4.5-7. The binary input levels are  $V(0) = 0$  V and  $V(1) = 25$  V. Assume ideal diodes. If  $V_1 = V(0)$  and  $V_2 = V(1)$ , then  $V_o$  is to be at 5 V. However, if  $V_1 = V_2 = V(1)$ , then  $V_o$  is to rise above 5 V.

 


Fig. P4.4.5-7

5. If  $V_{ss} = 20$  V and  $V_1 = V_2 = V(1)$ , the diode current  $I_{D1}$ ,  $I_{D2}$ , and  $I_{D0}$  are  
 (A) 1 mA, 1 mA, 4 mA (B) 1 mA, 1 mA, 5 mA  
 (C) 5 mA, 5mA, 1 mA (D) 0, 0, 0

6. If  $V_{ss} = 40 \text{ V}$  and both input are at HIGH level then, diode current  $I_{D1}$ ,  $I_{D2}$  and  $I_{D0}$  are respectively

- (A) 0.4 mA, 0.4 mA, 0 (B) 0, 0, 1 mA  
(C) 0.4 mA, 0.4 mA, 1 mA (D) 0, 0, 0

7. The maximum value of  $V_{ss}$  which may be used is

- (A) 30 V (B) 25 V  
(C) 125 V (D) 20 V

8. The ideal inverter in fig. P4.4.8 has a reference voltage of 2.5 V. The forward voltage of the diode is 0.75 V. The maximum number of diode logic circuit, that may be cascaded ahead of the inverter without producing logic error, is

 


Fig. P4.4.8

- (A) 3 (B) 4  
(C) 5 (D) 9

9. Consider the TTL circuit in fig. P4.4.9. The value of  $V_H$  and  $V_L$  are respectively

 


Fig. P4.4.9

- (A) 5 V, 0 V (B) 4.8 V, 0 V  
(C) 4.8 V, 0.2 V (D) 5 V, 0.2 V

#### Statement Q.10-11:

Consider the resistor transistor logic gate of fig. P4.4.10-11.

 


Fig. P4.4.10-11

10. For positive logic the gate is

- (A) AND (B) OR  
(C) NAND (D) NOR

11. For negative logic the gate is

- (A) AND (B) OR  
(C) NAND (D) NOR

#### Statement for Q.12-13:

Consider the RTL circuit of fig. P4.4.12-13.

 


Fig. P4.4.12-13

12. If  $V_{o1}$  is taken as the output, then circuit is a

- (A) AND (B) OR  
(C) NAND (D) NOR

13. If  $V_{o2}$  is taken as output, then circuit is a

- (A) AND (B) OR  
(C) NAND (D) NOR

#### Statement for Q.14-15:

Consider the TTL circuit of fig. P4.4.14. If either or both  $V_1$  and  $V_2$  are logic LOW,  $Q_1$  is driven to saturation.

 


Fig. P4.4.14-15

22. The circuit shown in fig. P4.4.22 is

 


Fig. P4.4.22

- (A) NAND (B) NOR  
(C) AND (D) OR

23. The circuit shown in fig. P4.4.23 acts as a

 


Fig. P4.4.23

- (A) NAND (B) NOR  
(C) AND (D) OR

24. The circuit shown in fig. P4.4.24 implements the function

 


Fig. P4.4.24

- (A)  $ABC + \overline{ABC}$  (B)  $ABC + \overline{(A + B + C)}$   
(C)  $\overline{ABC} + \overline{(A + B + C)}$  (D) None of the above

25. The circuit shown in fig. P4.4.25. implements the function

 


Fig. P4.4.25

- (A)  $(A + B)C + D$  (B)  $\overline{(AB + C)}D$   
(C)  $\overline{(A + B)C + D}$  (D)  $(AB + C)D$

26. Consider the CMOS circuit shown in fig. P4.4.26. The output Y is

 


Fig. P4.4.26

- (A)  $\overline{(A + C)}B$  (B)  $\overline{(A + B)}C$   
(C)  $AB + C$  (D)  $AB + \overline{C}$

27. The CMOS circuit shown in fig. P4.4.27 implement

 


Fig. P4.4.27

- (A)  $\overline{AB + CD + E}$  (B)  $\overline{(A + B)(C + D)E}$   
(C)  $AB + CD + E$  (D)  $(A + B)(C + D)E$

$V_1$		$V_2$		$V_o$	
Actual	Logic	Actual	Logic	Actual	Logic
$V_H$	1	$V_H$	1	$V_{CE(sat)}$	0
$V_L$	0	$V_L$	0	$V_{CE}$	1
$V_H$	1	$V_L$	0	$V_{CE(sat)}$	0
$V_L$	0	$V_H$	1	$V_{CE(sat)}$	0

**13. (B)** The  $Q_3$  stage is simply an inverter (a NOT gate). Thus output  $V_{o2}$  is the logic complement of  $V_{o1}$ . Therefore this is a OR gate.

**14. (A)** When  $Q_1$  is saturated,  $V_{o1}$  is logic LOW otherwise  $V_{o1}$  is logic HIGH. The following truth table shows AND logic

$V_1$	$V_2$	$V_{o1}$
1	1	1
0	1	0
1	0	0
0	0	0

**15. (C)** The  $Q_2$  stage is simply an inverter. Thus output  $V_{o2}$  is the logic complement of  $V_{o1}$ .

**16. (C)** If  $V_1 = V_2 \leq V_L$ ,  $V_{o1} \approx V_{CC}$ . If  $V_1(V_2) > V_H$ , while  $V_2(V_1) \leq V_L$ ,  $Q_1(Q_2)$  is ON and  $Q_2(Q_1)$  is OFF and  $V_{o1} \approx V_{CC}$ . If  $V_1 = V_2 > V_H$ , both  $Q_1$  and  $Q_2$  are ON and  $V_{o1} \approx 2V_{CE(sat)}$ . The truth table shows NAND logic

$V_1$		$V_2$		$V_o$	
Actual	Logic	Actual	Logic	Actual	Logic
$V_L$	0	$V_L$	0	$V_{CC}$	1
$V_H$	1	$V_L$	0	$V_{CC}$	1
$V_L$	0	$V_H$	1	$V_{CC}$	1
$V_H$	1	$V_H$	1	$2V_{CE(sat)}$	0

**17. (A)** The  $Q_3$  stage is simple an inverter. Hence AND logic.

**18. (C)** For each successive gate, that has a transistor in saturation, the current required is

$$I_{B(sat)} = \frac{I_{C(sat)}}{\beta} = \frac{V_{CC} - V_{CE(sat)}}{\beta R_C} = \frac{5 - 0.2}{50(640)} = 0.15 \text{ mA}$$

For  $n$  attached gate  $I_o = nI_{B(sat)}$ .

To assure no logic error  $V_o = V_{CC} - I_o R_C > V_H = 3.5 \text{ V}$

$$n \leq \frac{V_{CC} - 3.5}{R_C I_{B(sat)}} = \frac{5 - 3.5}{640(0.15\text{mA})} = 15.6 \Rightarrow n \leq 15$$

**19. (A)** Let  $V_1 = V_2 = 0 \text{ V}$ , then  $M_3$  will be ON,  $M_1$  and  $M_2$  OFF and  $M_4$  ON, hence  $V_o = -V_{DD}$ . Let  $V_1 = 0 \text{ V}$  and  $V_2 = -V_{DD}$  then  $M_3$  will be ON,  $M_1$  OFF  $M_4$  OFF,  $M_2$  ON, hence  $V_o = -V_{DD}$ . Let  $V_1 = -V_{DD}$  and  $V_2 = 0 \text{ V}$ , then  $M_3$  OFF,  $M_4$  ON,  $M_2$  OFF hence  $V_o = -V_{DD}$ . Finally if  $V_1 = V_2 = -V_{DD}$ ,  $M_3$  and  $M_4$  will be OFF and  $M_1, M_2$  will be ON, hence  $V_o = 0 \text{ V}$ . Thus the given CMOS gate satisfies the function of a negative NAND gate.

**20. (C)** If  $V_A = -V_{DD}$  then  $M_1$  is ON and  $V_Y = 0 \text{ V}$ . If  $V_B = V_C = -V_{DD}$  and  $V_A = 0 \text{ V}$  then  $M_3$  and  $M_2$  are ON but  $M_1$  is OFF hence  $V_Y = 0 \text{ V}$ . If  $V_A = 0 \text{ V}$  and either or both  $V_B, V_C$  are  $0 \text{ V}$  then  $M_1$  is OFF and either or both  $M_2$  and  $M_3$  will be OFF, which implies no current flowing through  $M_4$  hence  $V_Y = -V_{DD}$ . Thus given circuit satisfies the logic equation  $\overline{A + BC}$ .

**21. (A)** Let  $V_1 = V_2 = 0 \text{ V} = V(0)$  then  $M_4$  and  $M_3$  will be ON and  $M_2, M_1$  OFF hence  $V_o = V_{DD} = V(1)$ . Let  $V_1 = 0 \text{ V}$ ,  $V_2 = V_{DD}$  then  $M_4$  and  $M_2$  will be ON but  $M_3$  and  $M_1$  will be OFF hence  $V_o = 0 = V(0)$ . Let  $V_1 = V_{DD}$ ,  $V_2 = 0 \text{ V}$ , then  $M_4$  and  $M_3$  will be OFF and  $M_1$  ON hence  $V_o = 0 \text{ V} = V(0)$ . Finally if  $V_1 = V_2 = V_{DD}$ ,  $M_1$  and  $M_2$  will be ON but  $M_4$  will be OFF hence  $V_o = 0 \text{ V} = V(0)$ . Thus the given CMOS satisfy the function of a positive NOR gate.

**22. (A)** If either one or both the inputs are  $V(0) = 0 \text{ V}$  the corresponding FET will be OFF, the voltage across the load FET will be  $0 \text{ V}$ , hence the output is  $V_{DD}$ . If both inputs are  $V(1) = V_{DD}$ , both  $M_1$  and  $M_2$  are ON and the output is  $V(0) = 0 \text{ V}$ . It satisfy NAND gate.

**23. (B)** If both the inputs are at  $V(0) = 0 \text{ V}$ , the transistor  $M_1$  and  $M_2$  are OFF, hence the output is  $V(1) = V_{DD}$ . If either one or both of the inputs are at  $V(1) = V_{DD}$ , the corresponding FET will be ON and the output will be  $V(0) = 0 \text{ V}$ . Hence it is a NOR gate.

**24. (B)** If all inputs  $A, B$  and  $C$  are HIGH, then input to inverter is LOW and output  $Y$  is HIGH. If all inputs are LOW, then input to inverter is also LOW and output  $Y$  is HIGH. In all other case the input to inverter is HIGH and output  $Y$  is LOW.

$$\text{Hence } Y = ABC + \overline{ABC} = ABC + (\overline{A + B + C})$$

**25. (C)** The operation of circuit is given below

A B C D	$P_A$ $P_B$ $P_C$ $P_D$	$N_A$ $N_B$ $N_C$ $N_D$	Y
$\times \times \times 1$	$\times \times \times$ OFF	$\times \times \times$ ON	LOW
$\times \times 0 0$	$\times \times$ ON ON	$\times \times$ OFF OFF	HIGH
$0 0 1 0$	ON ON OFF ON	OFF OFF ON OFF	HIGH
$0 1 1 0$	ON OFF OFF ON	OFF ON ON OFF	LOW
$1 0 1 0$	OFF ON OFF ON	ON OFF ON OFF	LOW
$1 1 1 0$	OFF OFF OFF ON	ON ON ON OFF	LOW

$$Y = \overline{(A + B)C + D}$$

**26. (B)** The operation of this circuit is given below :

A B C	$P_A$ $P_B$ $P_C$	$N_A$ $N_B$ $N_C$	Y
$\times \times 0$	$\times \times$ ON	$\times \times$ OFF	HIGH
$0 0 1$	ON ON OFF	OFF OFF ON	HIGH
$\times 1 1$	$\times$ OFF OFF	$\times$ ON ON	LOW
$1 \times 1$	OFF $\times$ OFF	ON $\times$ ON	LOW

$$Y = \overline{(A + B)C}$$

**27. (B)** If input  $E$  is LOW, output will not be LOW. It must be HIGH. Option (B) satisfy this condition.

**28. (A)** In this circuit parallel combination are OR gate and series combination are AND gate.

$$\text{Hence } Y = (A + B)(C + D)(E + F)$$

**29. (A)** When an output is HIGH, it may be as low as  $V_{OH(min)} = 2.4$  V. The minimum voltage that an input will respond to as a HIGH is  $V_{IH(min)} = 2.0$  V. A negative noise spike that can drive the actual voltage below 2.0 V if its amplitude is greater than

$$V_{NH} = V_{OH(min)} - V_{IH(min)} = 2.4 - 2.0 = 0.4 \text{ V}$$

**30. (A)** When an output is LOW, it may be as high as  $V_{OL(max)} = 0.4$  V. The maximum voltage that an input will respond to as a LOW is  $V_{IL(max)} = 0.8$  V. A positive noise spike can drive the actual voltage above the 0.8 V level if its amplitude is greater than

$$V_{NL} = V_{IL(max)} - V_{OL(max)} = 0.8 - 0.4 = 0.4 \text{ V}$$

**31. (B)** A positive noise spike can drive the voltage above 1.0 V level if the amplitude is greater than

$$V_{NL} = V_{IL(max)} - V_{OL(max)} = 1 - 0.1 = 0.9 \text{ V},$$

A negative noise spike can drive the voltage below 3.5 V if the amplitude is greater than

$$V_{NH} = V_{OH(min)} - V_{IH(min)} = 4.9 - 3.5 = 1.4 \text{ V}$$

$$\textbf{32. (B)} V_{IH(min)} = V_{OH(min)} - V_{NH} = -0.8 - 0.5 = -1.3 \text{ V}$$

$$V_{IL(max)} = V_{OL(max)} + V_{NL} = 0.5 + (-2) = -1.5 \text{ V}$$

$$\textbf{33. (C)} V_{NH} = V_{OH(min)} - V_{IH(min)}, V_{NL} = V_{IL(max)} - V_{OL(max)}$$

$$V_{NH} = 2.7 \text{ (for LS)} - 2.0 \text{ (for ALS)} = 0.7 \text{ V}$$

$$V_{NL} = 0.8 \text{ (for ALS)} - 0.5 \text{ (for LS)} = 0.3 \text{ V}$$

$$\textbf{34. (B)} V_{NH} = 2.5 \text{ (for ALS)} - 2.0 \text{ (for LS)} = 0.5 \text{ V}$$

$$V_{NL} = 0.8 \text{ (for LS)} - 0.4 \text{ (for ALS)} = 0.4 \text{ V}$$

$$\textbf{35. (D)} V_{NH(min)} = 0.5 \text{ V}, V_{NL(min)} = 0.3 \text{ V}$$

$$\textbf{36. (B)} \text{ fanout (LOW)} = \frac{I_{OL(max)}}{I_{IL(max)}} = \frac{8\text{m}}{0.1\text{m}} = 80$$

$$\text{fanout (HIGH)} = \frac{I_{OH(max)}}{I_{IH(max)}} = \frac{400\mu}{20\mu} = 20$$

The fanout is chosen the smaller of the two.

**37. (B)** In HIGH state the loading on the output of gate 1 is equivalent to six 74LS input load.

$$\text{Hence load} = 6 \times I_{IH} = 6 \times 20\mu = 120 \mu\text{A}$$

**38. (C)** The NAND gate represent only a single input load in the LOW state. Hence only five loads in the LOW state.

$$\text{load} = 5I_{IL} = 5 \times 0.4 = 2 \text{ mA}$$

\*\*\*\*\*