

Heating Effect of Current

- One *kilowatt* hour is equal to [NCERT 1974; MP PMT 2002]
 - 36×10^5 joules
 - 36×10^3 joules
 - 10^3 joules
 - 10^5 joules
- If R_1 and R_2 are respectively the filament resistances of a 200 *watt* bulb and 100 *watt* bulb designed to operate on the same voltage, then [NCERT 1980; CPMT 1991, 97]
 - R_1 is two times R_2
 - R_2 is two times R_1
 - R_2 is four times R_1
 - R_1 is four times R_2
- Two electric bulbs, one of 200 *volt* 40 *watt* and the other 200 *volt* 100 *watt* are connected in a house wiring circuit [NCERT 1971; CBSE PMT 2000]
 - They have equal currents through them
 - The resistance of the filaments in both the bulbs is same
 - The resistance of the filament in 40 *watt* bulb is more than the resistance in 100 *watt* bulb
 - The resistance of the filament in 100 *watt* bulb is more than the resistance in 40 *watt* bulb
- The two bulbs as in the above question are connected in series to a 200 *volt* line. Then [NCERT 1971, 78]
 - The potential drop across the two bulbs is the same
 - The potential drop across the 40 *watt* bulb is greater than the potential drop across the 100 *watt* bulb
 - The potential drop across the 100 *W* bulb is greater than the potential drop across the 40 *W* bulb
 - The potential drop across both the bulb is 200 *volt*
- Forty electric bulbs are connected in series across a 220 *V* supply. After one bulb is fused, the remaining 39 are connected again in series across the same supply. The illumination will be

[NCERT 1972; Haryana CEE 1996; DPMT 2001]

- (a) More with 40 bulbs than with 39
- (b) More with 39 bulbs than with 40
- (c) Equal in both the cases
- (d) In the ratio of $49^2 : 39^2$

6. The material of fuse wire should have

[BHU 1999; MH CET 2001; CBSE PMT 2003]

- (a) A high specific resistance and high melting point
- (b) A low specific resistance and low melting point
- (c) A high specific resistance and low melting point
- (d) A low specific resistance and a high melting point

7. Two electric bulbs whose resistances are in the ratio of 1 : 2 are connected in parallel to a constant voltage source. The powers dissipated in them have the ratio

[NCERT 1977; MP PMT 1994, 2000]

- (a) 1 : 2
- (b) 1 : 1
- (c) 2 : 1
- (d) 1 : 4

8. A heater coil is cut into two parts of equal length and one of them is used in the heater. The ratio of the heat produced by this half coil to that by the original coil is

[NCERT 1972; AIEEE 2005; CBSE PMT 2005]

- (a) 2 : 1
- (b) 1 : 2
- (c) 1 : 4
- (d) 4 : 1

9. Resistance of one carbon filament and one tungsten lamp are measured individually when the lamp are lit and compared with their respective resistances when cold. Which one of the following statements will be true [NCERT 972]

- (a) Resistance of the carbon filament lamp will increase but that of the tungsten will diminish when hot
- (b) Resistance of the tungsten filament lamp will increase but that of carbon will diminish when hot
- (c) Resistances of both the lamps will increase when hot
- (d) Resistances of both the lamps will decrease when hot

10. The mechanism of the heat produced in a conductor when an electric current flows through it, can be explained on the basis of

- (a) Viscosity
- (b) Friction
- (c) Free electron theory
- (d) Gauss's theorem

11. Two electric bulbs whose resistances are in the ratio of 1 : 2 are connected in series. The powers dissipated in them have the ratio [NCERT 1977]

- (a) 1 : 2
- (b) 2 : 1
- (c) 1 : 1
- (d) 1 : 4

12. You are given a resistance wire of length 50 cm and a battery of negligible resistance. In which of the following cases is largest amount of heat generated

- (a) When the wire is connected to the battery directly
- (b) When the wire is divided into two parts and both the parts connected to the battery in parallel
- (c) When the wire is divided into four parts and all the four connected to the battery in parallel
- (d) When only half the wire is connected to the battery

1136 Heating and Chemical Effect of Current


13. What is immaterial for an electric fuse wire
[MNR 1984; MP PMT 2002; CPMT 1996, 2003]
- Its specific resistance
 - Its radius
 - Its length
 - Current flowing through it
14. The electric bulbs have tungsten filaments of same length. If one of them gives 60 watt and other 100 watt, then
[NCERT 1979]
- 100 watt bulb has thicker filament
 - 60 watt bulb has thicker filament
 - Both filaments are of same thickness
 - It is possible to get different wattage unless the lengths are different
15. Three equal resistors connected in series across a source of e.m.f. together dissipate 10 watt. If the same resistors are connected in parallel across the same e.m.f., then the power dissipated will be
[CBSE PMT 1998; KCET (Engg.) 1999; MP PMT 2003]
- 10 watt
 - 30 watt
 - 10/3 watt
 - 90 watt
16. How much energy in kilowatt hour is consumed in operating ten 50 watt bulbs for 10 hours per day in a month (30 days).
[NCERT 1978, 80; CPMT 1991]
- 1500
 - 5,000
 - 15
 - 150
17. (1) The product of a volt and a coulomb is a joule.
(2) The product of a volt and an ampere is a joule/second.
(3) The product of volt and watt is horse power.
(4) Watt-hour can be measured in terms of electron volt.
State if
[NCERT 1978; MP PMT 2003]
- All four are correct
 - (1), (2) and (4) are correct
 - (1) and (3) are correct
 - (3) and (4) are correct
18. A 25 W, 220 V bulb and a 100 W, 220 V bulb are connected in parallel across a 440 V line
[CBSE PMT 2001]
- Only 100 watt bulb will fuse
 - Only 25 watt bulb will fuse
 - Both bulbs will fuse
 - None of the bulbs will fuse
19. Two electric lamps of 40 watt each are connected in parallel. The power consumed by the combination will be
[CPMT 1984]
- 20 watt
 - 60 watt
 - 80 watt
 - 100 watt
20. Two heating coils, one of fine wire and the other of thick wire of the same material and of the same length are connected in series and in parallel. Which of the following statement is correct
- In series fine wire liberates more energy while in parallel thick wire will liberate more energy
 - In series fine wire liberates less energy while in parallel thick wire will liberate more energy
 - Both will liberate equally
 - In series the thick wire will liberate more while in parallel it will liberate less energy
21. An electric bulb is rated 220 volt and 100 watt. Power consumed by it when operated on 110 volt is
[CPMT 1986; MP PMT 1986, 94; AFMC 2000]
- 50 watt
 - 75 watt
 - 90 watt
 - 25 watt
22. A 25 watt, 220 volt bulb and a 100 watt, 220 volt bulb are connected in series across a 220 volt lines. Which electric bulb will glow more brightly
[MP PET 1999; MP PMT 1999]
- 25 watt bulb
 - 100 watt bulb
 - First 25 watt and then 100 watt
 - Both with same brightness
23. A resistor R_1 dissipates the power P when connected to a certain generator. If the resistor R_2 is put in series with R_1 , the power dissipated by R_1
[CPMT 1985; MNR 1998]
- Decreases
 - Increases
 - Remains the same
 - Any of the above depending upon the relative values of R_1 and R_2
24. An electric fan and a heater are marked as 100 watt, 220 volt and 1000 watt, 220 volt respectively. The resistance of the heater is
- Zero
 - Greater than that of the fan
 - Less than that of the fan
 - Equal to that of the fan
25. According to Joule's law, if the potential difference across a conductor having a material of specific resistance remains constant, then the heat produced in the conductor is directly proportional to
- ρ
 - ρ^2
 - $\frac{1}{\sqrt{\rho}}$
 - $\frac{1}{\rho}$
26. Two heater wires of equal length are first connected in series and then in parallel. The ratio of heat produced in the two cases is
[MNR 1987; UPSEAT 1999; MP PMT 1996, 2000, 01; AIIMS 2000; MP PET 1999, 2002; BHU 2004; Pb PET 2004]
- 2 : 1
 - 1 : 2
 - 4 : 1
 - 1 : 4
27. Two bulbs of equal wattage, one having carbon filament and the other having a tungsten filament are connected in series to the mains, then
- Both bulbs glow equally
 - Carbon filament bulb glows more
 - Tungsten filament bulbs glows more
 - Carbon filament bulb glows less
28. Two identical heaters rated 220 volt, 1000 watt are placed in series with each other across 220 volt lines. If resistance do not change with temperature, then the combined power is
- 1000 watt
 - 2000 watt
 - 500 watt
 - 4000 watt
29. A 25 watt, 220 volt bulb and a 100 watt, 220 volt bulb are connected in parallel across a 220 volt line. Which bulb will glow more brightly
- 25 watt bulb
 - 100 watt bulb
 - Both will have same brightness


- (d) First 25 watt then 100 watt
30. If two bulbs of wattage 25 and 100 respectively each rated at 220 volt are connected in series with the supply of 440 volt, then which bulbs will fuse [MNR 1988]
 (a) 100 watt bulb (b) 25 watt bulb
 (c) None of them (d) Both of them
31. If current in an electric bulb changes by 1%, then the power will change by [AFMC 1996]
 (a) 1% (b) 2%
 (c) 4% (d) $\frac{1}{2}\%$
32. Two identical batteries, each of e.m.f. 2 volt and internal resistance 1.0 ohm are available to produce heat in an external resistance $R = 0.5 \text{ ohm}$ by passing a current through it. The maximum Joulean power that can be developed across R using these batteries is [CBSE PMT 1990; BHU 1997]
 (a) 1.28 watt (b) 2.0 watt
 (c) $\frac{8}{9}$ watt (d) 3.2 watt
33. A constant voltage is applied between the two ends of a metallic wire. If both the length and the radius of the wire are doubled, the rate of heat developed in the wire [MP PMT 1996]
 (a) Will be doubled (b) Will be halved
 (c) Will remain the same (d) Will be quadrupled
34. The heating coils rating at 220 volt and producing 50 cal/sec heat are available with the resistances 55 Ω , 110 Ω , 220 Ω and 440 Ω . The heater of maximum power will be of [MP PMT 1985]
 (a) 440 Ω (b) 220 Ω
 (c) 110 Ω (d) 55 Ω
35. Which of the following statement is false
 (a) Heat produced in a conductor is proportional to its resistance
 (b) Heat produced in a conductor is proportional to the square of the current
 (c) Heat produced in a conductor is proportional to charge
 (d) Heat produced in a conductor is proportional to the time for which current is passed
36. On an electric heater 220 volt and 1100 watt are marked. On using it for 4 hours, the energy consumed in kWh will be
 (a) 2 (b) 4.4
 (c) 6 (d) 8
37. An electric heater kept in vacuum is heated continuously by passing electric current. Its temperature [MP PET 1993]
 (a) Will go on rising with time
 (b) Will stop after sometime as it will loose heat to the surroundings by conduction
 (c) Will rise for sometime and there after will start falling
 (d) Will become constant after sometime because of loss of heat due to radiation
38. Heat produced in a wire of resistance R due to current flowing at constant potential difference is proportional to [MP PET 1993]
 (a) $\frac{1}{R^2}$ (b) $\frac{1}{R}$
 (c) R (d) R^2
39. The power rating of an electric motor which draws a current of 3.75 amperes when operated at 200 V is about
 (a) 1 H.P. (b) 500 W
 (c) 54 W (d) 750 H.P.
40. An electric bulb of 100 watt is connected to a supply of electricity of 220 V. Resistance of the filament is [EAMCET 1981, 82; MP PMT 1993, 97]
 (a) 484 Ω (b) 100 Ω
 (c) 22000 Ω (d) 242 Ω
41. A cable of resistance 10 Ω carries electric power from a generator producing 250 kW at 10000 volt. The current in the cable is
 (a) 25 A (b) 250 A
 (c) 100 A (d) 1000 A
42. In the above question, the power lost in the cable during transmission is
 (a) 12.5 kW (b) 6.25 kW
 (c) 25 kW (d) 3.15 kW
43. The heat generated through 2 ohm and 8 ohm resistances separately, when a condenser of 200 μF capacity charged to 200 V is discharged one by one, will be [MP PET 1993]
 (a) 4 J and 16 J respectively
 (b) 16 J and 4 J respectively
 (c) 4 J and 8 J respectively
 (d) 4 J and 4 J respectively
44. Two bulbs are in parallel and they together consume 48 W from a battery of 6 V. The resistance of each bulb is
 (a) 0.67 Ω (b) 3.0 Ω
 (c) 4.0 Ω (d) 1.5 Ω
45. The heat developed in an electric wire of resistance R by a current I for a time t is [MP PMT 1993; MP PET 2005]
 (a) $\frac{I^2 R t}{4.2} \text{ cal}$ (b) $\frac{I^2 R}{4.2 t} \text{ cal}$
 (c) $\frac{I^2 R}{4.2 t} \text{ cal}$ (d) $\frac{R t}{4.2 I^2} \text{ cal}$
46. Two bulbs, one of 50 watt and another of 25 watt are connected in series to the mains. The ratio of the currents through them is
 (a) 2 : 1
 (b) 1 : 2
 (c) 1 : 1
 (d) Without voltage, cannot be calculated
47. The brightness of a bulb will be reduced, if a resistance is connected in
 (a) Series with it
 (b) Parallel with it
 (c) Series or parallel with it
 (d) Brightness of the bulb cannot be reduced
48. A 100 watt bulb working on 200 volt and a 200 watt bulb working on 100 volt have
 (a) Resistances in the ratio of 4 : 1
 (b) Maximum current ratings in the ratio of 1 : 4
 (c) Resistances in the ratio of 2 : 1
 (d) Maximum current ratings in the ratio of 1 : 2


49. There are two electric bulbs of 40 W and 100 W. Which one will be brighter when first connected in series and then in parallel,
 (a) 40 W in series and 100 W in parallel
 (b) 100 W in series and 40 W in parallel
 (c) 40 W both in series and parallel will be uniform
 (d) 100 W both in series and parallel will be uniform
50. Two resistances R_1 and R_2 when connected in series and parallel with 120 V line, power consumed will be 25 W and 100 W respectively. Then the ratio of power consumed by R_1 to that consumed by R_2 will be [EAMCET 1983]
 (a) 1 : 1 (b) 1 : 2
 (c) 2 : 1 (d) 1 : 4
51. A 220 volt and 800 watt electric kettle and three 220 volt and 100 watt bulbs are connected in parallel. On connecting this combination with 220 volt electric supply, the total current will be
 (a) 0.15 ampere (b) 5.0 ampere
 (c) 5.5 ampere (d) 6.9 ampere
52. You are given three bulbs of 25, 40 and 60 watt. Which of them has lowest resistance [NCERT 1982]
 (a) 25 watt bulb (b) 40 watt bulb
 (c) 60 watt bulb (d) Information is insufficient
53. The value of internal resistance of an ideal cell is [EAMCET 1989]
 (a) Zero (b) 0.5Ω
 (c) 1Ω (d) Infinity
54. Electric power is transmitted over long distances through conducting wires at high voltage because [MP PET 1994]
 (a) High voltage travels faster
 (b) Power loss is large
 (c) Power loss is less
 (d) Generator produced electrical energy at a very high voltage
55. A coil develops heat of 800 cal/sec. When 20 volts is applied across its ends. The resistance of the coil is ($1 \text{ cal} = 4.2 \text{ joule}$)
 (a) 1.2Ω (b) 1.4Ω
 (c) 0.12Ω (d) 0.14Ω
56. Resistances R_1 and R_2 are joined in parallel and a current is passed so that the amount of heat liberated is H_1 and H_2 respectively. The ratio $\frac{H_1}{H_2}$ has the value [MP PMT 1994]
 (a) $\frac{R_2}{R_1}$ (b) $\frac{R_1}{R_2}$
 (c) $\frac{R_1^2}{R_2^2}$ (d) $\frac{R_2^2}{R_1^2}$
57. The internal resistance of a primary cell is 4 ohm. It generates a current of 0.2 amp in an external resistance of 21 ohm. The rate at which chemical energy is consumed in providing the current is
 (a) 0.42 J/s (b) 0.84 J/s
 (c) 5 J/s (d) 1 J/s
58. A heating coil is labelled 100 W, 220 V. The coil is cut in half and the two pieces are joined in parallel to the same source. The energy now liberated per second is [CBSE PMT 1995]
 (a) 200 J (b) 400 J
 (c) 25 J [MP PET 1993] (d) 50 J
59. Which of the following is not a correct statement [MP PET 1995]
 (a) Resistivity of electrolytes decreases on increasing temperature
 (b) Resistance of mercury falls on decreasing its temperature
 (c) When joined in series a 40 W bulb glows more than a 60 W bulb
 (d) Resistance of 40 W bulb is less than the resistance of 60 W bulb
60. Three light bulbs of 40 W, 60 W and 100 W are connected in series with 220 V source. Which one of the bulbs will glow brightest [MP PMT 1995; UP
 (a) 40 W
 (b) 60 W
 (c) 100 W
 (d) All with the same brightness [MP PMT 1975]
61. The energy consumed in 1 kilowatt electric heater in 30 seconds will be
 (a) $6 \times 10^2 \text{ J}$ (b) $4.99 \times 10^7 \text{ J}$
 (c) $9.8 \times 10^6 \text{ J}$ (d) $3 \times 10^4 \text{ J}$
62. Two bulbs of 500 watt and 200 watt are manufactured to operate on 220 volt line. The ratio of heat produced in 500 W and 200 W, in two cases, when firstly they are joined in parallel and secondly in series, will be [MP PET 1996; DPMT 1999]
 (a) $\frac{5}{2}, \frac{2}{5}$ (b) $\frac{5}{2}, \frac{5}{2}$
 (c) $\frac{2}{5}, \frac{5}{2}$ (d) $\frac{2}{5}, \frac{2}{5}$
63. A 60 watt bulb carries a current of 0.5 amp. The total charge passing through it in 1 hour is [MP PMT 1996]
 (a) 3600 coulomb (b) 3000 coulomb
 (c) 2400 coulomb (d) 1800 coulomb
64. An electric heater of resistance 6 ohm is run for 10 minutes on a 120 volt line. The energy liberated in this period of time is [MP PET 1994]
 (a) $7.2 \times 10^3 \text{ J}$ (b) $14.4 \times 10^5 \text{ J}$
 (c) $43.2 \times 10^4 \text{ J}$ (d) $28.8 \times 10^4 \text{ J}$
65. Two bulbs are working in parallel order. Bulb A is brighter than bulb B. If R_A and R_B are their resistance respectively then
 (a) $R_A > R_B$ (b) $R_A < R_B$
 (c) $R_A = R_B$ (d) None of these
66. Two conductors made of the same material are connected across a common potential difference. Conductor A has twice the diameter and twice the length of conductor B. The power delivered to the two conductors P_A and P_B respectively is such that P_A / P_B equals to
 (a) 0.5 (b) 1.0
 (c) 1.5 (d) 2.0
67. A heating coil can heat the water of a vessel from 20°C to 60°C in 30 minutes. Two such heating coils are put in series and then used to heat the same amount of water through the same temperature range. The time taken now will be (neglecting thermal capacity of the coils) [MP PMT 1997]
 (a) 60 minutes (b) 30 minutes
 (c) 15 minutes (d) 7.5 minutes

68. If 2.2 kilowatt power is transmitted through a 10 ohm line at 22000 volt, the power loss in the form of heat will be [MP PMT/PET 1998]
- (a) 0.1 watt (b) 1 watt
(c) 10 watt (d) 100 watt
69. Two resistors having equal resistances are joined in series and a current is passed through the combination. Neglect any variation in resistance as the temperature changes. In a given time interval
- (a) Equal amounts of thermal energy must be produced in the resistors
(b) Unequal amounts of thermal energy may be produced
(c) The temperature must rise equally in the resistors
(d) The temperature must rise unequally in the resistors
70. A 5°C rise in temperature is observed in a conductor by passing a current. When the current is doubled the rise in temperature will be approximately [CBSE PMT 1998]
- (a) 16°C (b) 10°C
(c) 20°C (d) 12°C
71. Watt-hour meter measures [KCET 1994]
- (a) Electric energy (b) Current
(c) Voltage (d) Power
72. An electric lamp is marked 60 W, 230 V. The cost of 1 kilowatt hour of power is Rs. 1.25. The cost of using this lamp for 8 hours is
- (a) Rs. 1.20 (b) Rs. 4.00
(c) Rs. 0.25 (d) Rs. 0.60
73. 4 bulbs marked 40 W, 250 V are connected in series with 250 V mains. The total power is [EAMCET (Engg.) 1995]
- (a) 10 W (b) 40 W
(c) 320 W (d) 160 W
74. Pick out the wrong statement [AMU 1995]
- (a) In a simple battery circuit, the point of lowest potential is the negative terminal of the battery
(b) The resistance of an incandescent lamp is greater when the lamp is switched off
(c) An ordinary 100 W lamp has less resistance than a 60 W lamp
(d) At constant voltage, the heat developed in a uniform wire varies inversely as the length of the wire used
75. Two resistors of $6\ \Omega$ and $9\ \Omega$ are connected in series to a 120 volt source. The power consumed by the $6\ \Omega$ resistor is [SCRA 1994]
- (a) 384 W (b) 576 W
(c) 1500 W (d) 1200 W
76. Electric room radiator which operates at 225 volts has resistance of 50 ohms. Power of the radiator is approximately
- (a) 100 W (b) 450 W
(c) 750 W (d) 1000 W
77. If a power of 100 W is being supplied across a potential difference of 200 V, current flowing is [AFMC 1993]
- (a) 2 A (b) 0.5 A
(c) 1 A (d) 20 A
78. A current of 2 A passing through conductor produces 80 J of heat in 10 seconds. The resistance of the conductor is [CBSE PMT 1993]
- (a) $0.5\ \Omega$ (b) $2\ \Omega$
(c) $4\ \Omega$ (d) $20\ \Omega$
79. A $4\ \mu\text{F}$ conductor is charged to 400 volts and then its plates are joined through a resistance of $1\ \text{k}\Omega$. The heat produced in the resistance is [CBSE PMT 1994]
- (a) 0.16 J (b) 1.28 J
(c) 0.64 J (d) 0.32 J
80. A 10 ohm electric heater operates on a 110 V line. Calculate the rate at which it develops heat in watts [AFMC 1997]
- (a) 1310 W (b) 670 W
(c) 810 W (d) 1210 W
81. A (100 W, 200 V) bulb is connected to a 160 V power supply. The power consumption would be [CBSE PMT 1997; JIPMER 2000]
- (a) 64 W (b) 80 W
(c) 100 W (d) 125 W
82. A battery of e.m.f. 10 V and internal resistance 0.5 ohm is connected across a variable resistance R. The value of R for which the power delivered in it is maximum is given by [BHU 1998; JIPMER 2001, 02; CBSE PMT 2001]
- (a) 2.0 ohm (b) 0.25 ohm
(c) 1.0 ohm (d) 0.5 ohm
83. A piece of fuse wire melts when a current of 15 ampere flows through it. With this current, if it dissipates 22.5 W, the resistance of fuse wire will be [KCET 1994]
- (a) Zero (b) $10\ \Omega$
(c) $1\ \Omega$ (d) $0.10\ \Omega$
84. Two wires 'A' and 'B' of the same material have their lengths in the ratio 1 : 2 and radii in the ratio 2 : 1. The two wires are connected in parallel across a battery. The ratio of the heat produced in 'A' to the heat produced in 'B' for the same time is
- (a) 1 : 2 (b) 2 : 1
(c) 1 : 8 (d) 8 : 1
85. A heater draws a current of 2 A when connected to a 250 V source. The rate of energy dissipation is [JIPMER 1999]
- (a) 500 W (b) 1000 W
(c) 250 W (d) 125 W
86. A bulb rated at (100 W – 200 V) is used on a 100 V line. The current in the bulb is [JIPMER 1999]
- (a) $\frac{1}{4}$ amp (b) 4 amp
(c) $\frac{1}{2}$ amp (d) 2 amp
87. A steel wire has a resistance twice that of an aluminium wire. Both of them are connected with a constant voltage supply. More heat will be dissipated in [Roorkee 1999]
- (a) Steel wire when both are connected in series
(b) Steel wire when both are connected in parallel
(c) Aluminium wire when both are connected in series
(d) Aluminium wire when both are connected in parallel
88. A current i passes through a wire of length l , radius of cross-section r and resistivity ρ . The rate of heat generation is [AMU (Med.) 1999]

1140 Heating and Chemical Effect of Current

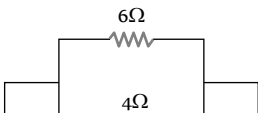- (a) $\frac{i^2 l \rho}{\pi r^2}$ (b) $i^2 \left(\frac{l \rho}{\pi r^2} \right)^2$
- (c) $i^2 l \rho / r$ (d) $i l \rho / r$
89. Which of the following is not equal to *watt* [DPMT 1999]
- (a) $(Amp)^2 \times ohm$ (b) $Amp / Volt$
- (c) $Amp \times Volt$ (d) $Joule / sec$
90. Two wires with resistances R and $2R$ are connected in parallel, the ratio of heat generated in $2R$ and R is [DCE 1999, 2000]
- (a) 1 : 2 (b) 2 : 1
- (c) 1 : 4 (d) 4 : 1
91. If a high power heater is connected to electric mains, then the bulbs in the house become dim, because there is a [BHU 1999; Pb. PMT 2000]
- (a) Current drop (b) Potential drop
- (c) No current drop (d) No potential drop
92. If three bulbs 60 W, 100 W and 200 W are connected in parallel, then
- (a) 200 W bulb will glow more
- (b) 60 W bulb will glow more
- (c) 100 W bulb will glow more
- (d) All the bulbs will glow equally
93. An expression for rate of heat generated, if a current of I ampere flows through a resistance of $R \Omega$, is [Pb. PMT 2000]
- (a) $I^2 R t$ (b) $I^2 R$
- (c) $V^2 R$ (d) $I R$
94. On giving 220 V to a resistor the power dissipated is 40 W then value of resistance is [RPMT 2000]
- (a) 1210 Ω (b) 2000 Ω
- (c) 1000 Ω (d) None of these
95. A 60 watt bulb operates on 220 V supply. The current flowing through the bulb is [MP PMT 2000]
- (a) 11/3 amp (b) 3/11 amp
- (c) 3 amp (d) 6 amp
96. If two bulbs of wattage 25 and 30, each rated at 220 volts, are connected in series with a 440 volt supply, which bulb will fuse [MP PET 2000]
- (a) 25 W bulb (b) 30 W bulb
- (c) Neither of them (d) Both of them
97. Two electric bulbs (60 W and 100 W respectively) are connected in series. The current passing through them is [AMU (Med.) 2000]
- (a) More in 100 W bulb (b) More in 60 W bulb
- (c) Same in both (d) None of these
98. In the circuit shown below, the power developed in the 6 Ω resistor is 6 watt. The power in watts developed in the 4 Ω resistor is
- (a) 16
- (b) 9
- (c) 6
- 
- (d) 4
99. Two wires A and B of same material and mass have their lengths in the ratio 1 : 2. On connecting them to the same source, the rate of heat dissipation in B is found to be 5 W. The rate of heat dissipation in A is [AMU (Engg.) 2000]
- (a) 10 W (b) 5 W
- (c) 20 W (d) None of these
100. If two electric bulbs have 40 W and 60 W rating at 220 V, then the ratio of their resistances will be [BHU 1999; KCET 2001]
- (a) 3 : 2 (b) 2 : 3
- (c) 3 : 4 (d) 4 : 3
101. An electric bulb is designed to draw power P_0 at voltage V_0 . If the voltage is V it draws a power P . Then [KCET 2001]
- (a) $P = \left(\frac{V_0}{V} \right)^2 P_0$ (b) $P = \left(\frac{V}{V_0} \right)^2 P_0$
- (c) $P = \left(\frac{V}{V_0} \right) P_0$ (d) $P = \left(\frac{V_0}{V} \right) P_0$
102. Three bulbs of 40 W, 60 W and 100 W are arranged in series with 220 V. Which bulb has minimum resistance [AFMC 2001]
- (a) 40 W (b) 60 W
- (c) 100 W (d) Equal in all bulbs
103. An electric kettle has two heating coils. When one coil is used, water in the kettle boils in 5 minutes, while when second coil is used, same water boils in 10 minutes. If the two coils, connected in parallel are used simultaneously, the same water will boil in time
- (a) 3 min 20 sec (b) 5 min
- (c) 7 min 30 sec (d) 2 min 30 sec
104. An external resistance R is connected to a battery of e.m.f. V and internal resistance r . The joule heat produced in resistor R is maximum when R is equal to [MP PET 2001]
- (a) r (b) $\frac{r}{2}$
- (c) $2r$ (d) Infinitely large
105. The amount of heat produced in a resistor when a current is passed through it can be found using [Kerala PET 2001]
- (a) Faraday's Law (b) Kirchhoff's Law
- (c) Laplace's Law (d) Joule's Law
106. Two wires have resistance of 2 Ω and 4 Ω connected to same voltage, ratio of heat dissipated at resistance is [UPSEAT 2001]
- (a) 1 : 2 (b) 4 : 3
- (c) 2 : 1 (d) 5 : 2
107. Two electric bulbs rated P_1 watt V volts and P_2 watt V volts are connected in parallel and V volts are applied to it. The total power will be [AMU (Med.) 2000]
- [MP PMT 2001; MP PET 2002]

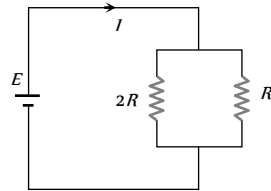- (a) $P_1 + P_2 \text{ watt}$ (b) $\sqrt{P_1 P_2} \text{ watt}$
- (c) $\frac{P_1 P_2}{P_1 + P_2} \text{ watt}$ (d) $\frac{P_1 + P_2}{P_1 P_2} \text{ watt}$
108. n identical bulbs, each designed to draw a power p from a certain voltage supply, are joined in series across that supply. The total power which they will draw is [KCET 2002]
- (a) p/n^2 (b) p/n
- (c) p (d) np
109. A wire when connected to 220 V mains supply has power dissipation P_1 . Now the wire is cut into two equal pieces which are connected in parallel to the same supply. Power dissipation in this case is P_2 . Then $P_2 : P_1$ is [AIIEE 2002]
- (a) 1 (b) 4
- (c) 2 (d) 3
110. An electric bulb marked 40 W and 200 V, is used in a circuit of supply voltage 100 V. Now its power is [AIIMS 2002]
- (a) 100 W (b) 40 W
- (c) 20 W (d) 10 W
111. Electric bulb 50 W-100 V glowing at full power are to be used in parallel with battery 120 V, 10 Ω . Maximum number of bulbs that can be connected so that they glow in full power is
- (a) 2 (b) 8
- (c) 4 (d) 6
112. A bulb has specification of one kilowatt and 250 volts, the resistance of bulb is [MP PMT 2002]
- (a) 125 Ω (b) 62.5 Ω
- (c) 0.25 Ω (d) 625 Ω
113. If a 30 V, 90 W bulb is to be worked on a 120 V line, a resistance of how many ohms should be connected in series with the bulb [MP PMT 2002; KCET 2003]
- (a) 10 ohm (b) 20 ohm
- (c) 30 ohm (d) 40 ohm
114. A fuse wire with radius 1 mm blows at 1.5 amp. The radius of the fuse wire of the same material to blow at 3 A will be [KCET 2003]
- (a) $4^{1/3} \text{ mm}$ (b) $3^{1/4} \text{ mm}$
- (c) $2^{1/2} \text{ mm}$ (d) $3^{1/2} \text{ mm}$
115. Three electric bulbs of rating 60 W each are joined in series and then connected to electric mains. The power consumed by these three bulbs will be [MP PET 2003; CBSE PMT 2004]
- (a) 180 W (b) 60 W
- (c) 20 W (d) $\frac{20}{3} \text{ W}$
116. An electric bulb is rated 60 W, 220 V. The resistance of its filament is [MP PET 2003]
- (a) 708 Ω (b) 870 Ω
- (c) 807 Ω (d) 780 Ω
117. A 220 volt, 1000 W bulb is connected across a 110 volt mains supply. The power consumed will be [AIIEE 2003]
- (a) 1000 W (b) 750 W
- (c) 500 W (d) 250 W
118. Two bulbs of 100 W and 200 W working at 220 volt are joined in series with 220 volt supply. Total power consumed will be approximately. [Pb. PET 2003; BHU 2005]
- (a) 65 watt (b) 33 watt
- (c) 300 watt (d) 100 watt
119. How many calories of heat will be produced approximately in a 210 watt electric bulb in 5 minutes [Pb. PET 2004]
- (a) 80000 cal (b) 63000 cal
- (c) 1050 cal (d) 15000 cal
120. A 5°C rise in the temperature is observed in a conductor by passing some current. When the current is doubled, then rise in temperature will be equal to [BHU 2004]
- (a) 5°C (b) 10°C
- (c) 20°C (d) 40°C
121. If a 2 kW boiler is used everyday for 1 hour, then electrical energy consumed by boiler in thirty days is [BHU 2004]
- (a) 15 unit (b) 60 unit
- (c) 120 unit (d) 240 unit
122. What will happen when a 40 watt, 220 volt lamp and 100 watt, 220 volt lamp are connected in series across 40 volt supply
- (a) 100 watt lamp will fuse (b) 40 watt lamp will fuse
- (c) Both lamps will fuse (d) Neither lamp will fuse [CPMT 2002]
123. What is the ratio of heat generated in R and $2R$ [DCE 2003]
- (a) 2 : 1
- (b) 1 : 2
- (c) 4 : 1
- (d) 1 : 4
- 
124. In an electric heater 4 amp current passes for 1 minute at potential difference of 250 volt, the power of heater and energy consumed will be respectively [DPMT 2003]
- (a) 1 kW, 60 kJ (b) 0.5 kW, 30 kJ
- (c) 10 kW, 600 kJ (d) None of these
125. Some electric bulbs are connected in series across a 220 V supply in a room. If one bulb is fused then remaining bulbs are connected again in series across the same supply. The illumination in the room will [J & K CET 2004]
- (a) Increase (b) Decrease
- (c) Remains the same (d) Not continuous
126. The resistor of resistance ' R ' is connected to 25 V supply and heat produced in it is 25 J/sec. The value of R is [Orissa PMT 2004]
- (a) 225 Ω (b) 1 Ω
- (c) 25 Ω (d) 50 Ω
127. Three bulbs of 40 W, 60 W, 100 W are arranged in series with 220 volt supply which bulb has minimum resistance [Pb. PET 2000]
- (a) 100 W (b) 40 W

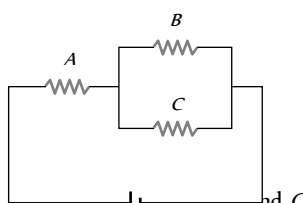
- (c) 60 W (d) Equal in all bulbs
128. If two electric bulbs have 40 W and 60 W rating at 220 V, then the ratio of their resistances will be [Pb. PET 2001]
- (a) 9 : 4 (b) 4 : 3
(c) 3 : 8 (d) 3 : 2
129. A 10 V storage battery of negligible internal resistance is connected across a $50\ \Omega$ resistor. How much heat energy is produced in the resistor in 1 hour [Pb. PET 2001]
- (a) 7200 J (b) 6200 J
(c) 5200 J (d) 4200 J
130. A hot electric iron has a resistance of $80\ \Omega$ and is used on a 200 V source. The electrical energy spent, if it is used for two hours, will be [Pb. PET 2002]
- (a) 8000 Wh (b) 2000 Wh
(c) 1000 Wh (d) 800 Wh
131. The heat produced by a 100 watt heater in 2 minute will be equal to [BCECE 2004]
- (a) $12 \times 10^3\ J$ (b) $10 \times 10^3\ J$
(c) $6 \times 10^3\ J$ (d) $3 \times 10^3\ J$
132. If two wires having resistance R and $2R$. Both joined in series and in parallel then ratio of heat generated in this situation, applying the same voltage, [BCECE 2004]
- (a) 2 : 1 (b) 1 : 2
(c) 2 : 9 (d) 9 : 2
133. Two electric bulbs A and B are rated as 60 W and 100 W. They are connected in parallel to the same source. Then, [KCET 2004]
- (a) Both draw the same current
(b) A draws more current than B
(c) B draws more current than A
(d) Current drawn are in the ratio of their resistances
134. Three identical resistances A, B and C are connected as shown in the given figure. The heat produced will be maximum
- 
- (a) In B (b) In C
(c) In A (d) Same for A, B and C
135. If 2.2 kW power is transmitted through a $100\ \Omega$ line at 22,000 V, the power loss in the form of heat will be [MP PET 2004]
- (a) 0.1 W (b) 1 W
(c) 10 W (d) 100 W
136. A heater coil connected to a supply of a 220 V is dissipating some power P_1 . The coil is cut into half and the two halves are connected in parallel. The heater now dissipates a power P_2 . The ratio of power $P_1 : P_2$ is [AFMC 2004]
- (a) 2 : 1 (b) 1 : 2
(c) 1 : 4 (d) 4 : 1

137. An electric lamp is marked 60 W, 230 V. The cost of a 1 kWh of energy is Rs. 1.25. The cost of using this lamp 8 hrs a day for 30 day is [Kerala (Med.) 2002]
- (a) Rs. 10 (b) Rs. 16
(c) Rs. 18 (d) Rs. 20
138. An electric iron draws 5 amp, a TV set draws 3 amp and refrigerator draws 2 amp from a 220 volt main line. The three appliances are connected in parallel. If all the three are operating at the same time, the fuse used may be of [ISM Dhanbad 1994]
- (a) 20 amp (b) 5 amp
(c) 15 amp (d) 10 amp
139. Match the List I with the List II from the combination shown. In the left side (List I) there are four different conditions and in the right side (List II), there are ratios of heat produced in each resistance for each condition : [ISM Dhanbad 1994]
- | List I | List II |
|---|-----------|
| (I) Two wires of same resistance are connected in series and same current is passed through them | (A) 1 : 2 |
| (II) Two wires of resistance R and $2R\ ohm$ are connected in series and same P.D. is applied across them | (B) 4 : 1 |
| (III) Two wires of same resistance are connected in parallel and same current is flowing through them | (C) 1 : 1 |
| (IV) Two wires of resistances in the ratio 1 : 2 are connected in parallel and same P.D. is applied across them | (D) 2 : 1 |
- (a) I – B; II – A; III – C; IV – D
(b) I – C; II – D; III – C; IV – D
(c) I – B; II – D; III – A; IV – C
(d) I – A; II – B; III – D; IV – C [MP PMT 2004]
140. The electric current passing through a metallic wire produces heat because of [BHU 1994]
- (a) Collisions of conduction electrons with each other
(b) Collisions of the atoms of the metal with each other
(c) The energy released in the ionization of the atoms of the metal
(d) Collisions of the conduction electrons with the atoms of the metallic wires
141. The maximum current that flows through a fuse wire before it blows out varies with its radius as [SCRA 1998]
- (a) $r^{3/2}$ (b) r
(c) $r^{2/3}$ (d) $r^{1/2}$
142. What is immaterial for an electric fuse wire [UPSEAT 1999]
- (a) Specific resistance of the wire
(b) Radius of the wire
(c) Length of the wire
(d) Current flowing through the wire
143. The current flowing through a lamp marked as 50 W and 250 V is

- (a) 5 amp (b) 2.5 amp
(c) 2 amp (d) 0.2 amp

144. Find the power of the circuit


[AIEEE 2002]

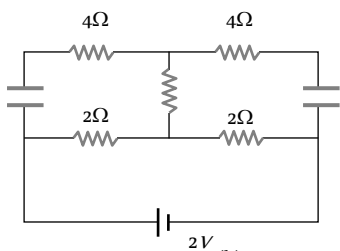

- (a) 1.5 W (b) 2 W
(c) 1 W (d) None of these

145. If in the circuit, power dissipation is 150 W, then R is

[AIEEE 2002]

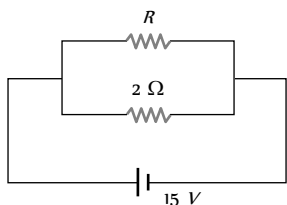

- (a) 2 Ω (b) 6 Ω
(c) 5 Ω (d) 4 Ω

146. Two resistors whose value are in ratio 2 : 1 are connected in parallel with one cell. Then ratio of power dissipated is

[RPMT 2000]

- (a) 2 : 1 (b) 4 : 1
(c) 1 : 2 (d) 1 : 1

147. A heater coil is cut into two equal parts and only one part is now used in the heater. The heat generated will now be

[AIEEE 2005]

- (a) One fourth (b) Halved
(c) Doubled (d) Four times

148. The resistance of hot tungsten filament is about 10 times the cold resistance. What will be the resistance of 100 W and 200 V lamp when not in use

[AIEEE 2005]

- (a) 400 Ω (b) 200 Ω
(c) 40 Ω (d) 20 Ω

149. A 5.0 amp current is setup in an external circuit by a 6.0 volt storage battery for 6.0 minutes. The chemical energy of the battery is reduced by

[KCET 2005]

- (a) $1.08 \times 10^7 J$ (b) $1.08 \times 10^6 volt$
(c) $1.8 \times 10^7 J$ (d) $1.8 \times 10^6 volt$


150. A railway compartment is lit up by thirteen lamps each taking 2.1 amp at 15 volts. The heat generated per second in each lamp will be

- (a) 4.35 cal (b) 5.73 cal
(c) 7.5 cal (d) 2.5 cal

151. Two bulbs X and Y having same voltage rating and of power 40 watt and 60 watt respectively are connected in series across a potential difference of 300 volt, then

[Orissa JEE 2005]

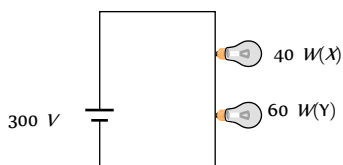- (a) X will glow brighter
(b) Resistance of Y is greater than X



- (c) Heat produced in Y will be greater than X
(d) Voltage drop in X will be greater than Y

152. 3 identical bulbs are connected in series and these together dissipate a power P . If now the bulbs are connected in parallel, then the power dissipated will be

[DPMT 2005]

- (a) $\frac{P}{3}$ (b) $3P$
(c) $9P$ (d) $\frac{P}{9}$

153. A coil takes 15 min to boil a certain amount of water, another coil takes 20 min for the same process. Time taken to boil the same amount of water when both coil are connected in series

- (a) 5 min (b) 8.6 min
(c) 35 min (d) 30 min

Chemical Effect of Current

1. Water can not be made conducting by adding small amount of any of the following except

- (a) Sodium chloride (b) Copper sulphate
(c) Ammonium chloride (d) Sugar

2. The electrochemical equivalent Z of any element can be obtained by multiplying the electrochemical equivalent of hydrogen with

- (a) Atomic weight (b) Molecular weight
(c) Chemical equivalent (d) A constant

3. A silver and zinc voltameter are connected in series and a current i is passed through them for a time t liberating W gm of zinc. The weight of silver deposited is nearly

[NCERT 1973, 76]

- (a) W (b) 1.7 W
(c) 2.4 W (d) 3.5 W

4. To deposit one gm equivalent of an element at an electrode, the quantity of electricity needed is

[IIT 1984; DPMT 1982; MP PET 1998;

MP PMT 1998; 2003]

- (a) One ampere (b) 96000 amperes
(c) 96500 farads (d) 96500 coulombs

5. In an electrolysis experiment, a current i passes through two different cells in series, one containing a solution of $CuSO_4$ and the other a solution of $AgNO_3$. The rate of increase of the weight of the cathodes in the two cells will be

[NCERT 1972]

- (a) In the ratio of the densities of Cu and Ag
(b) In the ratio of the at. weights of Cu and Ag
(c) In the ratio of half the atomic weight of Cu to the atomic weight of Ag
(d) In the ratio of half the atomic weight of Cu to half the atomic weight of Ag

6. To deposit one litre of hydrogen at 22.4 atmosphere from acidulated water, the quantity of electricity that must pass through is

- (a) 1 coulomb (b) 22.4 coulomb
(c) 96500 coulomb (d) 193000 coulomb

7. The amount of substance liberated on electrodes during electrolysis when 1 coulomb of electricity is passed, is
 (a) Chemical equivalent
 (b) Electrochemical equivalent
 (c) Equivalent weight
 (d) One mol
8. For goldplating on a copper chain, the substance required in the form of solution is
 (a) Copper sulphate
 (b) Copper chloride
 (c) Potassium cyanide
 (d) Potassium aurocyanide
9. On passing the current in water voltameter, the hydrogen
 (a) Liberated at anode (b) Liberated at cathode
 (c) Does not liberate (d) Remains in the solution
10. In water voltameter, the electrolysis of takes place [DPMT 1999]
 (a) H_2O (b) H_2SO_4
 (c) H_2O and H_2SO_4 both (d) H_2 and O_2
11. For depositing 1 gm of Cu in copper voltameter on passing 2 amperes of current, the time required will be (For copper $Z = 0.00033 \text{ gm/C}$)
 (a) Approx. 20 minutes (b) Approx. 25 minutes
 (c) Approx. 30 minutes (d) Approx. 35 minutes
12. A battery of e.m.f. 3 volt and internal resistance 1.0 ohm is connected in series with copper voltameter. The current flowing in the circuit is 1.5 amperes. The resistance of voltameter will be
 (a) Zero (b) 1.0 ohm
 (c) 1.5 ohm (d) 2.0 ohm
13. According to Faraday's laws of electrolysis, the amount of decomposition is proportional to [MP PMT 1993]
 (a) $\frac{1}{\text{Time for which current passes}}$
 (b) Electrochemical equivalent of the substance
 (c) $\frac{1}{\text{Current}}$
 (d) $\frac{1}{\text{Electrochemical equivalent}}$
14. If in a voltaic cell 5 gm of zinc is consumed, then we get how many ampere hours? (Given that E.C.E. of Zn is $3.387 \times 10^{-7} \text{ kg/coulomb}$)
 (a) 2.05 (b) 8.2
 (c) 4.1 (d) $5 \times 3.387 \times 10^{-7}$
15. The current flowing in a copper voltameter is 1.6 A. The number of Cu^{++} ions deposited at the cathode per minute are
 (a) 1.5×10^{20} (b) 3×10^{20}
 (c) 6×10^{20} (d) 1×10^{19}
16. In a copper voltameter experiment, current is decreased to one-fourth of the initial value but it is passed for four times the earlier duration. Amount of copper deposited will be [MP PMT 1993]
 (a) Same
 (b) One-fourth the previous value
 (c) Four times the previous value
 (d) $\frac{1}{16}$ th of the previous value
17. A certain charge liberates 0.8 gm of O_2 . The same charge will liberate how many gm of silver [MP PET 1999]
 (a) 108 gm (b) 10.8 gm
 (c) 0.8 gm (d) $\frac{108}{0.8} \text{ gm}$
18. In charging a battery of motor-car, the following effect of electric current is used [MP PET 1993; AFMC 2003]
 (a) Magnetic (b) Heating
 (c) Chemical (d) Induction
19. The Avogadro's number is 6×10^{23} per gm mole and electronic charge is $1.6 \times 10^{-19} \text{ C}$. The Faraday's number is [DPMT 2001]
 (a) $6 \times 10^{23} \times 1.6 \times 10^{-19}$ (b) $\frac{6 \times 10^{23}}{1.6 \times 10^{-19}}$
 (c) $\frac{2}{6 \times 10^{23} \times 1.6 \times 10^{-19}}$ (d) $\frac{1.6 \times 10^{-19}}{6 \times 10^{23}}$
20. In $CuSO_4$ solution when electric current equal to 2.5 faraday is passed, the gm equivalent deposited on the cathode is
 (a) 1 (b) 1.5
 (c) 2 (d) 2.5
21. The atomic weight of silver and copper are 108 and 64. A silver voltameter and a copper voltameter are connected in series and when current is passed 10.8 gm of silver is deposited. The mass of copper deposited will be
 (a) 6.4 gm (b) 12.8 gm
 (c) 3.2 gm (d) 10.8 gm
22. Faraday's laws of electrolysis are related to [IIT 1983]
 (a) The atomic number of positive ion
 (b) The equivalent weight of electrolyte
 (c) The atomic number of negative ion
 (d) The velocity of positive ion
23. In the process of electrolysis, the current is carried out inside the electrolyte by [AMU (Engg.) 1999]
 (a) Electrons
 (b) Atoms
 (c) Positive and negative ions
 (d) All the above
24. The mass of ions deposited during a given interval of time in the process of electrolysis depends on [DPMT 2002]
 (a) The current (b) The resistance
 (c) The temperature (d) The electric power
25. The amount of charge required to liberate 9 gm of aluminium (atomic weight = 27 and valency = 3) in the process of electrolysis is (Faraday's number = 96500 coulombs/gm equivalent) [MP PMT 1994; MP PET 2000]
 (a) 321660 coulombs (b) 69500 coulombs
 (c) 289500 coulombs (d) 96500 coulombs
26. In an electroplating experiment, m gm of silver is deposited when 4 ampere of current flows for 2 minute. The amount (in gm) of silver deposited by 6 ampere of current for 40 second will be [MNR 1991; UPSEAT 2000]

Pb. PET 2004; Orissa JEE 2005]

- (a) $4m$ (b) $m/2$
(c) $m/4$ (d) $2m$
27. In electrolysis, if the duration of the passage of current is doubled, the mass liberated is [EAMCET 1979]
(a) Doubled (b) Halved
(c) Increased four times (d) Remains the same
28. A current of 16 ampere flows through molten NaCl for 10 minute. The amount of metallic sodium that appears at the negative electrode would be [EAMCET 1984]
(a) 0.23 gm (b) 1.15 gm
(c) 2.3 gm (d) 11.5 gm
29. The mass of a substance liberated when a charge ' q ' flows through an electrolyte is proportional to [EAMCET 1984]
(a) q (b) $1/q$
(c) q^2 (d) $1/q^2$
30. A steady current of 5 amps is maintained for 45 mins. During this time it deposits 4.572 gms of zinc at the cathode of a voltmeter. E.C.E. of zinc is [MP PET 1994]
(a) $3.387 \times 10^{-4} \text{ gm/C}$ (b) $3.387 \times 10^{-4} \text{ C/gm}$
(c) $3.384 \times 10^{-3} \text{ gm/C}$ (d) $3.394 \times 10^{-3} \text{ C/gm}$
31. The relation between faraday constant F , electron charge e and avogadro number N is [MP PET 1995]
(a) $F = N/e$ (b) $F = Ne$
(c) $N = F^2$ (d) $F = N^2e$
32. The electrochemical equivalent of magnesium is 0.126 mg/C . A current of 5 A is passed in a suitable solution for 1 hour. The mass of magnesium deposited will be
(a) 0.0378 gm (b) 0.227 gm
(c) 0.378 gm (d) 2.27 gm
33. Two electrolytic cells containing CuSO_4 and AgNO_3 respectively are connected in series and a current is passed through them until 1 mg of copper is deposited in the first cell. The amount of silver deposited in the second cell during this time is approximately
[Atomic weights of copper and silver are respectively 63.57 and 107.88] [MP PMT 1996]
(a) 1.7 mg (b) 3.4 mg
(c) 5.1 mg (d) 6.8 mg
34. A current I is passed for a time t through a number of voltmeters. If m is the mass of a substance deposited on an electrode and z is its electrochemical equivalent, then [MP PMT 1997]
(a) $\frac{zIt}{m} = \text{constant}$ (b) $\frac{z}{mIt} = \text{constant}$
(c) $\frac{I}{zmt} = \text{constant}$ (d) $\frac{It}{zm} = \text{constant}$
35. For electroplating a spoon, it is placed in the voltmeter at [MP PMT/PET 1998]
(a) The position of anode
(b) The position of cathode
(c) Exactly in the middle of anode and the cathode
(d) Anywhere in the electrolyte
36. If nearly 10^5 coulomb liberate 1 gm equivalent of aluminium, then the amount of aluminium (equivalent weight 9) deposited through electrolysis in 20 minutes by a current of 50 amp will be
(a) 0.6 gm (b) 0.09 gm
(c) 5.4 gm (d) 10.8 gm
37. Electroplating does not help in [AIIMS 1998]
(a) Fine finish to the surface
(b) Shining appearance
(c) Metals to become hard
(d) Protect metal against corrosion
38. When a current is passed through water, acidified with a dilute sulphuric acid, the gases formed at the platinum electrodes are
(a) 1 vol. hydrogen (cathode) and 2 vol. oxygen (anode)
(b) 2 vol. hydrogen (cathode) and 1 vol. oxygen (anode)
(c) 1 vol. hydrogen (cathode) and 1 vol. oxygen (anode)
(d) 1 vol. oxygen (cathode) and 2 vol. hydrogen (anode)
39. The negative Zn pole of a Daniel cell, sending a constant current through a circuit, decreases in mass by 0.13g in 30 minutes. If the electrochemical equivalent of Zn and Cu are 32.5 and 31.5 respectively, the increase in the mass of the positive Cu pole in this time is [AIEEE 2003]
(a) 0.242 g (b) 0.190 g
(c) 0.141 g (d) 0.126 g
40. When a copper voltmeter is connected with a battery of e.m.f. 12 volts. 2 gms of copper is deposited in 30 minutes. If the same voltmeter is connected across a 6 volt battery, then the mass of copper deposited in 45 minutes would be [SCRA 1994]
(a) 1 gm (b) 1.5 gm
(c) 2 gm (d) 2.5 gm
41. [MP PMT 1995] The value of current required to deposit 0.972 gm of chromium in 3 hours if the E.C.E. of chromium is $0.00018 \text{ gm per coulomb}$, is
(a) 1 amp (b) 1.5 amp
(c) 0.5 amp (d) 2 amp
42. The current inside a copper voltmeter [Roorkee 1992]
(a) Is half the outside value
(b) Is the same as the outside value
(c) Is twice the outside value
(d) Depends on the concentration of CuSO_4
43. The resistance of a cell does not depend on [RPET 1996]
(a) Current drawn from the cell
(b) Temperature of electrolyte
(c) Concentration of electrolyte
(d) The e.m.f. of the cell
44. The electrochemical equivalent of a metal is $3.3 \times 10^{-7} \text{ kg/coulomb}$. The mass of the metal liberated at the cathode when a 3 A current is passed for 2 seconds will be
(a) $19.8 \times 10^{-7} \text{ kg}$ (b) $9.39 \times 10^{-7} \text{ kg}$
(c) $6.6 \times 10^{-7} \text{ kg}$ (d) $1.1 \times 10^{-7} \text{ kg}$
45. Faraday's 2nd law states that mass deposited on the electrode is directly proportional to [DCE 1999]
(a) Atomic mass (b) Atomic mass \times Velocity

1146 Heating and Chemical Effect of Current

- (c) Atomic mass/Valency (d) Valency
46. The relation between Faraday constant (F), chemical equivalent (E) and electrochemical equivalent (Z) is [SCRA 1994; AFMC 2000]
- (a) $F = EZ$ (b) $F = \frac{Z}{E}$
- (c) $F = \frac{E}{Z}$ (d) $F = \frac{E}{Z^2}$
47. The electrochemical equivalent of a material in an electrolyte depends on [MP PET 2001]
- (a) The nature of the material
- (b) The current through the electrolyte
- (c) The amount of charge passed through electrolyte
- (d) The amount of material present in electrolyte
48. On passing 96500 coulomb of charge through a solution $CuSO_4$ the amount of copper liberated is [MP PMT 2001]
- (a) 64 gm (b) 32 gm
- (c) 32 kg (d) 64 kg
49. If 96500 coulombs of electricity liberates one gram equivalent of any substance, the time taken for a current of 0.15 amperes to deposit 20mg of copper from a solution of copper sulphate is (Chemical equivalent of copper = 32) [Kerala (Engg.) 2002]
- (a) 5 min 20 sec (b) 6 min 42 sec
- (c) 4 min 40 sec (d) 5 min 50 sec
50. How much current should be passed through acidified water for 100 s to liberate 0.224 litre of H_2 [DCE 2002]
- (a) 22.4 A (b) 19.3 A
- (c) 9.65 A (d) 1 A
51. Who among the following scientists made the statement –"Chemical change can produce electricity" [DCE 2004]
- (a) Galvani (b) Faraday
- (c) Coulomb (d) Thomson
52. If a steady current of 4 amp maintained for 40 minutes, deposits 4.5 gm of zinc at the cathode and then the electro chemical equivalent will be [MH CET 2003]
- (a) $51 \times 10^{-17} \text{ gm/C}$ (b) $28 \times 10^{-6} \text{ gm/C}$
- (c) $32 \times 10^{-5} \text{ gm/C}$ (d) $47 \times 10^{-5} \text{ gm/C}$
53. The current flowing in a copper voltameter is 3.2 A. The number of copper ions (Cu^{2+}) deposited at the cathode per minute is
- (a) 0.5×10^{20} (b) 1.5×10^{20}
- (c) 3×10^{20} (d) 6×10^{20}
54. A copper voltameter is connected in series with a heater coil of resistance 0.1Ω . A steady current flows in the circuit for twenty minutes and mass of 0.99 g of copper is deposited at the cathode. If electrochemical equivalent of copper is 0.00033 gm/C , then heat generated in the coil is [Pb. PET 2002]
- (a) 750 J (b) 650 J
- (c) 350 J (d) 250 J
55. E.C.E. of Cu and Ag are 7×10^{-6} and 1.2×10^{-6} . A certain current deposits 14 gm of Cu . Amount of Ag deposited is [Orissa PMT 2004]
- (a) 1.2 gm (b) 1.6 gm
- (c) 2.4 gm (d) 1.8 gm
56. The chemical equivalent of silver is 108. If the current in a silver voltameter is 2 Amp., the time required to deposit 27 grams of silver will be [MP PMT 2004]
- (a) 8.57 hrs (b) 6.70 hrs
- (c) 3.35 hrs (d) 12.50 hrs
57. Two voltmeters, one of copper and another of silver, are joined in parallel. When a total charge q flows through the voltmeters, equal amount of metals are deposited. If the electrochemical equivalents of copper and silver are z_1 and z_2 respectively the charge which flows through the silver voltameter is
- (a) $q \frac{z_1}{z_2}$ (b) $q \frac{z_2}{z_1}$
- (c) $\frac{q}{1 + \frac{z_1}{z_2}}$ (d) $\frac{q}{1 + \frac{z_2}{z_1}}$
58. The chemical equivalent of copper and zinc are 32 and 108 respectively. When copper and silver voltameter are connected in series and electric current is passed through for sometimes, 1.6 g of copper is deposited. Then, the mass of silver deposited will be
- (a) 3.5 g (b) 2.8 g
- (c) 5.4 g (d) None of these
59. Ampere hour is the unit of [Orissa JEE 2005]
- (a) Quantity of charge (b) Potential
- (c) Energy (d) Current

Thermo-Electricity

- The production of e.m.f. by maintaining a difference of temperature between the two junctions of two different metals is known as
 - Joule effect
 - Seebeck effect
 - Peltier effect
 - Thomson effect
- When a current passes through the junction of two different metals, evolution or absorption of heat at the junction is known as
 - Joule effect
 - Seebeck effect
 - Peltier effect
 - Thomson effect
- When a current passes through a wire whose different parts are maintained at different temperatures, evolution or absorption of heat all along the length of wire is known as
 - Joule effect
 - Seebeck effect
 - Peltier effect
 - Thomson effect
- The thermocouple is based on the principle of [MP PET 1984; AFMC 1998; BCECE 2003]
 - Seebeck effect
 - Thomson effect

- (c) Peltier effect (d) Joule effect
5. For a thermocouple, the neutral temperature is 270°C and the temperature of its cold junction is 20°C . If there is no deflection in the galvanometer, the temperature of the hot junction should be
 (a) 210°C (b) 540°C
 (c) 520°C (d) 209°C
6. Thermocouple is a device for the measurement of
 (a) Absolute temperature of a metal
 (b) The temperature difference between two substances
 (c) The couple acting on a wire
 (d) Thermal conductivity of a substance
7. The true statement for thermo e.m.f. of a thermocouple
 (a) Depends on the nature of metals
 (b) Depends only on temperature of cold junction
 (c) Depends only on temperature of hot junction
 (d) Depends on the length of the wires used for thermocouple
8. The direction of current in an iron-copper thermocouple is [MP PET 1995]
 (a) From copper to iron at the hot junction
 (b) From iron to copper at the hot junction
 (c) From copper to iron at cold junction
 (d) No current will flow
9. Peltier coefficient for the junction of a pair of metals is proportional to [MP PMT 1993; MP PET 1997]
 (a) T absolute temperature of the junction
 (b) Square of absolute temperature of the junction
 (c) $\frac{1}{\text{Absolute temperature of the junction}}$
 (d) $\frac{1}{\text{Square of absolute temperature of the junction}}$
10. If for a thermocouple T_n is the neutral temperature, T_c is the temperature of the cold junction and T_i is the temperature of inversion, then [MP PET 2001; AIEEE 2002]
 (a) $T_i = 2T_n - T_c$ (b) $T_n = T_i - 2T_c$
 (c) $T_i = T_n - T_c$ (d) None of these
11. For a thermocouple, the temperature of inversion is that temperature at which thermo e.m.f. is
 (a) Zero (b) Maximum
 (c) Minimum (d) None of the above
12. For a given thermocouple, the thermo e.m.f. can be
 (a) Zero (b) Positive
 (c) Negative (d) All of the above
13. When current is passed in antimony-bismuth couple, then
 (a) The junction becomes hot when the current is from bismuth to antimony
 (b) The junction becomes hot when current flows from antimony to bismuth
 (c) Both junctions become hot
 (d) Both junctions become cold
14. A thermocouple is made of Cu and Fe . If a battery is connected in it, then
 (a) Both junctions will be at the same temperature
 (b) Both junctions will become hot
 (c) One junction will be hotter than the other
 (d) None of these
15. Thermopile is used for [AMU Engg. 2000]
 (a) Collecting the heat energy
 (b) The measurement of radiant heat energy
 (c) The measurement of current
 (d) The change of atomic energy into heat energy
16. When a current of 1 ampere is passed through a conductor whose ends are maintained at temperature difference of 1°C , the amount of heat evolved or absorbed is called
 (a) Peltier coefficient (b) Thomson coefficient
 (c) Thermoelectric power (d) Thermo e.m.f.
17. In a thermocouple, the temperature that does not depend on the temperature of the cold junction is called
 (a) Neutral temperature (b) Temperature of inversion
 (c) Both the above (d) None of the above
18. At neutral temperature, the thermoelectric power $\left(\frac{dE}{dT}\right)$ has the value [MP PET 2003; MP PMT 2004]
 (a) Zero (b) Maximum but negative
 (c) Maximum but positive (d) Minimum but positive
19. In Cu-Fe couple, the flow of current at the temperature of inversion is
 (a) From Fe to Cu through the hot junction
 (b) From Cu to Fe through the hot junction
 (c) Maximum
 (d) None of the above
20. In Seebeck series Sb appears before Bi . In a Sb-Bi thermocouple current flows from [MP PET 1994]
 (a) Sb to Bi at the hot junction
 (b) Sb to Bi at the cold junction
 (c) Bi to Sb at the cold junction
 (d) None of the above
21. Which of the following statement is correct [MP PET 1994]
 (a) Both Peltier and Joule effects are reversible
 (b) Both Peltier and Joule effects are irreversible
 (c) Joule effect is reversible, whereas Peltier effect is irreversible
 (d) Joule effect is irreversible, whereas Peltier effect is reversible
22. For a given temperature difference, which of the following pairs will generate maximum thermo e.m.f. [MP PMT 1994]
 (a) Antimony-bismuth (b) Silver-gold
 (c) Iron-copper (d) Lead-nickel
23. The cold junction of a thermocouple is maintained at 10°C . No thermo e.m.f. is developed when the hot junction is maintained at 530°C . The neutral temperature is [MP PMT 1994]
 (a) 260°C (b) 270°C
 (c) 265°C (d) 520°C
24. Which of the following is not reversible [Manipal MEE 1995; DPMT 2001]
 (a) Joule effect (b) Peltier effect

- (c) Seebeck effect (d) Thomson effect
25. Neutral temperature of a thermocouple is defined as the temperature at which [MP PMT 1996]
 (a) The thermo e.m.f. changes sign
 (b) The thermo e.m.f. is maximum
 (c) The thermo e.m.f. is minimum
 (d) The thermo e.m.f. is zero
26. As the temperature of hot junction of a thermo-couple is increased (while cold junction is at constant temperature), the thermo e.m.f.
 (a) Increases uniformly at constant rate
 (b) Increases slowly in the beginning and more rapidly at higher temperatures
 (c) Increases more rapidly in the beginning but less rapidly at higher temperatures
 (d) In minimum at neutral temperature
27. As the temperature of hot junction increases, the thermo e.m.f.
 (a) Always increases
 (b) Always decreases
 (c) May increase or decrease
 (d) Always remains constant
28. The e.m.f. in a thermoelectric circuit with one junction at 0°C and the other at $t^\circ\text{C}$ is given by $E = At - Bt^2$. The neutral temperature is then [AMU 1995; BCECE 2004]
 (a) $\frac{A}{B}$ (b) $-\frac{A}{2B}$
 (c) $-\frac{B}{2A}$ (d) $\frac{A}{2B}$
29. The temperature of cold junction and neutral temperature of a thermocouple are 15°C and 280°C respectively. The temperature of inversion is [AMU (Engg.) 1999]
 (a) 295°C (b) 265°C
 (c) 545°C (d) 575°C
30. Above neutral temperature, thermo e.m.f. in a thermocouple [AMU (Engg.) 1999]
 (a) Decreases with rise in temperature
 (b) Increases with rise in temperature
 (c) Remains constant
 (d) Changes sign
31. Consider the following two statements *A* and *B*, and identify the correct choice out of given answers
 A. Thermo e.m.f. is minimum at neutral temperature of a thermocouple
 B. When two junctions made of two different metallic wires are maintained at different temperatures, an electric current is generated in the circuit. [EAMCET (Med.) 2000]
 (a) *A* is false and *B* is true (b) *A* is true and *B* is false
 (c) Both *A* and *B* are false (d) Both *A* and *B* are true
32. The temperature at which thermal electric power of a thermo couple becomes zero is called [MP PMT 2001]
 (a) Inversion temperature (b) Neutral temperature
 (c) Junction temperature (d) Null temperature
33. Thomson coefficient of a conductor is $10\mu\text{V/K}$. The two ends of it are kept at 50°C and 60°C respectively. Amount of heat absorbed by the conductor when a charge of 10 C flows through it is
 (a) 1000 J (b) 100 J
 (c) 100 mJ (d) 1 mJ
34. For a thermocouple the neutral temperature is 270°C when its cold junction is at 20°C . What will be the neutral temperature and the temperature of inversion when the temperature of cold junction is increased to 40°C [Kerala PET 2001]
 (a) 290°C , 580°C (b) 270°C , 580°C
 (c) 270°C , 500°C (d) 290°C , 540°C
35. Two ends of a conductor are at different temperatures the electromotive force generated between two ends is [MP PMT 2001; MP PET 2002]
 (a) Seebeck electro motive force (e.m.f.)
 (b) Peltier electro motive force (e.m.f.)
 (c) Thomson electro motive force (e.m.f.)
 (d) None of these
36. The neutral temperature of a thermocouple is 350°C when the cold junction is at 0°C . When the cold junction is immersed in a bath of 30°C , the inversion temperature is [Kerala (Med.) 2002]
 (a) 700°C (b) 600°C
 (c) 350°C (d) 670°C
37. A thermoelectric refrigerator works on [JIPMER 2002]
 (a) Joule effect (b) Seebeck effect
 (c) Peltier effect (d) Thermionic emission
38. If the temperature of cold junction of thermocouple is lowered, then the neutral temperature [JIPMER 2002]
 (a) Increases
 (b) Approaches inversion temperature
 (c) Decreases
 (d) Remains the same
39. Consider the following two statements *A* and *B* and identify the correct choice given in the answers
 (A) Duddells thermo-galvanometer is suitable to measure direct current only
 (B) Thermopile can measure temperature differences of the order of 10^{-3}°C [EAMCET 2003]
 (a) Both *A* and *B* are true (b) Both *A* and *B* are false
 (c) *A* is true but *B* is false (d) *A* is false but *B* is true
40. If $E = at + bt^2$, what is the temperature of inversion [DCE 2003]
 (a) $-\frac{a}{2b}$ (b) $+\frac{a}{2b}$
 (c) $-\frac{a}{b}$ (d) $+\frac{a}{b}$
41. Antimony and bismuth are usually used in a thermocouple, because [EAMCET 2001]
 (a) Negative thermal e.m.f. produced
 (b) Constant thermal e.m.f. produced
 (c) Lower thermal e.m.f. produced
 (d) Higher thermal e.m.f. produced
42. The smallest temperature difference that can be measured with a combination of a thermocouple of thermo e.m.f. $30\mu\text{V}$ per degree and a

galvanometer of 50 ohm resistance, capable of measuring a minimum current of $3 \times 10^{-6} \text{ amp}$ is

[MP PET 2000]

- (a) 0.5 degree (b) 1.0 degree
(c) 1.5 degree (d) 2.0 degree

43. $e = \alpha t - \frac{1}{2} \beta t^2$, If temperature of cold junction is 0°C then

temperature of inversion is

(if $\alpha = 500.0 \mu\text{V}/^\circ\text{C}$, $\beta = 5.0 \mu\text{V}/\text{Square } ^\circ\text{C}$)

[DCE 2001]

- (a) 100 (b) 200
(c) 300 (d) 400

44. If the emf of a thermocouple, one junction of which is kept 0°C is given by $e = at + 1/2 bt^2$ then the neutral temperature will be [J & K CET 2005]

- (a) a/b (b) $-a/b$
(c) $a/2b$ (d) $-1/ab$

Critical Thinking

Objective Questions

1. The resistance of the filament of an electric bulb changes with temperature. If an electric bulb rated 220 volt and 100 watt is connected (220 \times 0.8) volt sources, then the actual power would be


- (a) $100 \times 0.8 \text{ watt}$
(b) $100 \times (0.8)^2 \text{ watt}$
(c) Between $100 \times 0.8 \text{ watt}$ and 100 watt
(d) Between $100 \times (0.8)^2 \text{ watt}$ and $100 \times 0.8 \text{ watt}$

2. An immersion heater is rated 836 watt. It should heat 1 litre of water from 10°C to 40°C in about [AIEEE 2004]

- (a) 200 sec (b) 150 sec
(c) 836 sec (d) 418 sec

3. In the circuit shown in figure, the heat produced in 5 ohm resistance is 10 calories per second. The heat produced in 4 resistance is [IIT 1981; UPSEAT 2002]

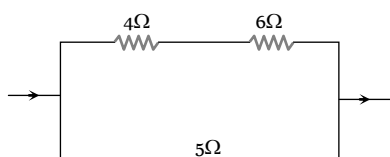- (a) 1 cal/sec
(b) 2 cal/sec
(c) 3 cal/sec
(d) 4 cal/sec



4. A house is served by 220 V supply line in a circuit protected by a 9 ampere fuse. The maximum number of 60 W lamps in parallel that can be turned on, is


- (a) 44 (b) 20
(c) 22 (d) 33

5. Water boils in an electric kettle in 15 minutes after switching on. If the length of the heating wire is decreased to $2/3$ of its initial value, then the same amount of water will boil with the same supply voltage in [MP PMT 1994]

- (a) 15 minutes (b) 12 minutes
(c) 10 minutes (d) 8 minutes

6. In the circuit as shown in the figure, the heat produced by 6 ohm resistance due to current flowing in it is 60 calorie per second. The heat generated across 3 ohm resistance per second will be

- (a) 30 calorie

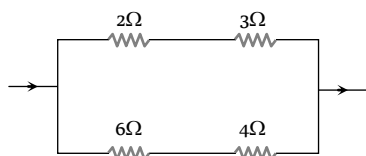

- (b) 60 calorie
(c) 100 calorie
(d) 120 calorie

7. The resistance of a heater coil is 110 ohm . A resistance R is connected in parallel with it and the combination is joined in series with a resistance of 11 ohm to a 220 volt main line. The heater operates with a power of 110 watt. The value of R in ohm is

- (a) 12.22
(b) 24.42
(c) Negative
(d) That the given values are not correct

8. A 500 W heating unit is designed to operate from a 115 volt line. If the line voltage drops to 110 volt, the percentage drop in heat output will be [ISM Dhanbad 1994]

- (a) 10.20% (b) 8.1%
(c) 8.6% (d) 7.6%

9. A heater of 220 V heats a volume of water in 5 minute time. A heater of 110 V heats the same volume of water in [AFMC 1993]

- (a) 5 minutes (b) 8 minutes
(c) 10 minutes (d) 20 minutes


10. An electric kettle takes 4 A current at 220 V. How much time will it take to boil 1 kg of water from room temperature 20°C ? The temperature of boiling water is 100°C [CPMT 1989]

- (a) 6.4 minutes (b) 6.3 minutes
(c) 12.6 minutes (d) 12.8 minutes

11. If a wire of resistance 20Ω is covered with ice and a voltage of 210 V is applied across the wire, then the rate of melting of ice is


- (a) 0.85 g/s (b) 1.92 g/s
(c) 6.56 g/s (d) All of these

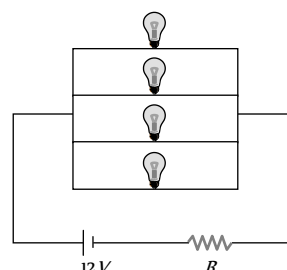12. Four identical electrical lamps are labelled 1.5 V, 0.5 A which describes the condition necessary for them to operate at normal brightness. A 12 V battery of negligible internal resistance is connected to lamps as shown, then [UPSEAT 2001]



- (a) The value of R for normal brightness of each lamp is $(3/4) \Omega$
(b) The value of R for normal brightness of each lamp is $(21/4) \Omega$
(c) Total power dissipated in circuit when all lamps are normally bright is 24 W
(d) Power dissipated in R is 21 W when all lamps are normally bright

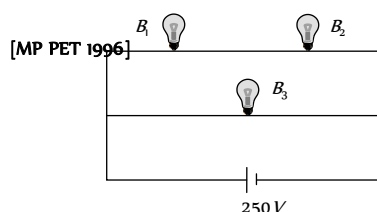
13. A 100 W bulb B_1 and two 60-W bulbs B_2 and B_3 are connected to a 250 V source, as shown in the figure. Now W_1 , W_2 and W_3 are the output powers of the bulbs B_1 , B_2 and B_3 respectively. Then [MP PET 1996]



- (a) $W_1 > W_2 = W_3$ (b) $W_1 > W_2 > W_3$
 (c) $W_1 < W_2 = W_3$ (d) $W_1 < W_2 < W_3$

14. The three resistance of equal value are arranged in the different combinations shown below. Arrange them in increasing order of power dissipation

[IIT-JEE (Screening) 2003]

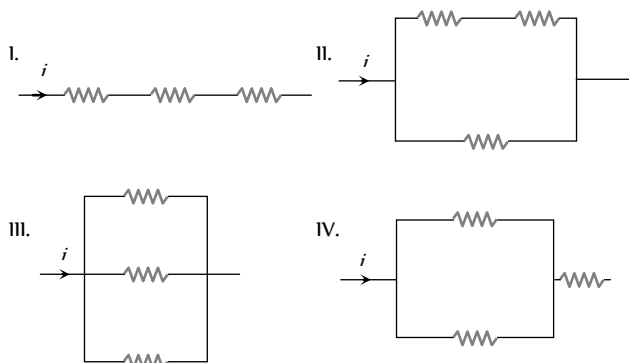

- (a) $\text{III} < \text{II} < \text{IV} < \text{I}$ (b) $\text{II} < \text{III} < \text{IV} < \text{I}$
 (c) $\text{I} < \text{IV} < \text{III} < \text{II}$ (d) $\text{I} < \text{III} < \text{II} < \text{IV}$

15. Silver and copper voltameter are connected in parallel with a battery of e.m.f. 12 V. In 30 minutes, 1 gm of silver and 1.8 gm of copper are liberated. The power supplied by the battery is

- (a) 24.13 J/sec (b) 2.413 J/sec
 (c) 0.2413 J/sec (d) 2413 J/sec

($Z_{\text{Cu}} = 6.6 \times 10^{-4} \text{ gm/C}$ and $Z_{\text{Ag}} = 11.2 \times 10^{-4} \text{ gm/C}$)

16. A silver voltameter of resistance 2 ohm and a 3 ohm resistor are connected in series across a cell. If a resistance of 2 ohm is connected in parallel with the voltameter, then the rate of deposition of silver

[EAMCET 1983]

- (a) Decreases by 25%
 (b) Increases by 25%
 (c) Increases by 37.5%
 (d) Decreases by 37.5%

17. The expression for thermo e.m.f. in a thermocouple is given by the relation $E = 40\theta - \frac{\theta^2}{20}$, where θ is the temperature difference of two junctions. For this, the neutral temperature will be

- (a) 100°C (b) 200°C
 (c) 300°C (d) 400°C

18. For copper-iron (Cu-Fe) couple, the thermo e.m.f. (temperature of cold junction = 0°C) is given by $E = (14\theta - 0.02\theta^2)\mu\text{V}$. The neutral temperature will be

- (a) 350°C (b) 350 K
 (c) 560°C (d) 560 K

19. One junction of a certain thermoelectric couple is at a fixed temperature T_r and the other junction is at temperature T . The thermo electromotive force for this is expressed by $E = K(T - T_r) \left[T_0 - \frac{1}{2}(T + T_r) \right]$. At temperature $T = \frac{1}{2}T_0$, the thermoelectric power is

[MP PMT 1994]

- (a) $\frac{1}{2}KT_0$ (b) KT_0
 (c) $\frac{1}{2}KT_0^2$ (d) $\frac{1}{2}K(T_0 - T_r)^2$

20. The temperature of the cold junction of thermo-couple is 0°C and the temperature of hot junction is $T^\circ\text{C}$. The e.m.f. is $E = 16T - 0.04T^2 \mu\text{ volts}$. The temperature of inversion is

- (a) 200°C (b) 400°C
 (c) 100°C (d) 300°C

21. The temperature of the cold junction of a thermocouple is 0°C and temperature of the hot junction is $T^\circ\text{C}$. The thermo e.m.f. is given by the relation $E = AT - \frac{1}{2}BT^2$ (where $A = 16$ and $B = 0.08$). The temperature of inversion is

- (a) 100°C (b) 300°C
 (c) 400°C (d) 500°C

22. The thermo e.m.f. of a thermo-couple is $25\mu\text{V}/^\circ\text{C}$ at room temperature. A galvanometer of 40 ohm resistance, capable of detecting current as low as 10^{-5} A , is connected with the thermocouple. The smallest temperature difference that can be detected by this system is

[AIEEE 2003]

- (a) 20°C (b) 16°C
 (c) 12°C (d) 8°C

23. An electric bulb rated for 500 watts at 100 volts is used in a circuit having a 200-volt supply. The resistance R that must be put in series with the bulb, so that the bulb draws 500 W is

- (a) 10Ω (b) 20Ω
 (c) 50Ω (d) 100Ω


24. A thermo couple develops $200\mu\text{V}$ between 0°C and 100°C . If it develops $64\mu\text{V}$ and $76\mu\text{V}$ respectively between $(0^\circ\text{C} - 32^\circ\text{C})$ and $(32^\circ\text{C} - 70^\circ\text{C})$ then what will be the thermo emf it develops between 70°C and 100°C

- (a) $65\mu\text{V}$ (b) $60\mu\text{V}$
 (c) $55\mu\text{V}$ (d) $50\mu\text{V}$

[AMU (Engg.) 2000]

25. A thermo couple is formed by two metals X and Y metal X comes earlier to Y in Seebeck series. If temperature of hot junction increases beyond the temperature of inversion. Then direction of current in thermocouple will so

- (a) X to Y through cold junction
 (b) X to Y through hot junction
 (c) Y to X through cold junction

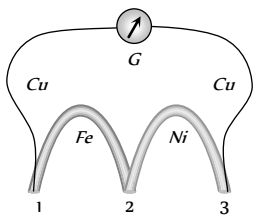- (d) Both (b) and (c)
26. Peltier co-efficient of a thermo couple is 2 nano volts. How much heat is developed at a junction if 2.5 amp current flows for 2 minute
- (a) 6 ergs (b) 6×10^{-7} ergs
(c) 16 ergs (d) 6×10^{-3} erg
27. Resistance of a voltmeter is 2Ω , it is connected in series to a battery of 10 V through a resistance of 3Ω . In a certain time mass deposited on cathode is 1 gm. Now the voltmeter and the 3Ω resistance are connected in parallel with the battery. Increase in the deposited mass on cathode in the same time will be
- (a) 0 (b) 1.5 gm
(c) 2.5 gm (d) 2 gm
28. A current of 1.5 A flows through a copper voltmeter. The thickness of copper deposited on the electrode surface of area 50 cm^2 in 20 minutes will be (Density of copper = 9000 kg/m^3 and E.C.E. of copper = 0.00033 g/C)
- (a) $2.6 \times 10^{-5}\text{ m}$ (b) $2.6 \times 10^{-4}\text{ m}$
(c) $1.3 \times 10^{-5}\text{ m}$ (d) $1.3 \times 10^{-4}\text{ m}$
29. An ammeter, suspected to give inaccurate reading, is connected in series with a silver voltmeter. The ammeter indicates 0.54 A. A steady current passed for one hour deposits 2.024 gm of silver. If the E.C.E. of silver is $1.118 \times 10^{-3}\text{ gmC}^{-1}$, then the error in ammeter reading is
- (a) + 0.04 A (b) + 0.02 A
(c) - 0.03 A (d) - 0.01 A
30. If 1 A of current is passed through CuSO_4 solution for 10 seconds, then the number of copper ions deposited at the cathode will be about
- (a) 1.6×10^{19} (b) 3.1×10^{19}
(c) 4.8×10^{19} (d) 6.2×10^{19}
31. A silver and a copper voltmeters are connected in parallel across a 6 volt battery of negligible resistance. In half an hour, 1 gm of copper and 2 gm of silver are deposited. The rate at which energy is supplied by the battery will approximately be (Given E.C.E. of copper = $3.294 \times 10^{-4}\text{ g/C}$ and E.C.E. of silver = $1.118 \times 10^{-3}\text{ g/C}$)
- (a) 64 W (b) 32 W
(c) 96 W (d) 16 W
32. A thermocouple of resistance 1.6Ω is connected in series with a galvanometer of 8Ω resistance. The thermocouple develops and e.m.f. of $10\mu\text{V}$ per degree temperature difference between two junctions. When one junction is kept at 0°C and the other in a molten metal, the galvanometer reads 8 millivolt. The temperature of molten metal, when e.m.f. varies linearly with temperature difference, will be
- (a) 960°C (b) 1050°C
(c) 1275°C (d) 1545°C
33. The e.m.f. of a thermocouple, one junction of which is kept at 0°C , is given by $e = at + bt^2$ the Peltier co-efficient will be
- (a) $(t + 273)(a + 2bt)$ (b) $(t + 273)(a - 2bt)$
(c) $(t - 273)(a - 2bt)$ (d) $(t - 273)(a + 2bt)$
34. A coil of wire of resistance 50Ω is embedded in a block of ice. If a potential difference of 210 V is applied across the coil, the amount of ice melted per second will be
- (a) 4.12 gm (b) 4.12 kg
(c) 3.68 kg (d) 2.625 gm
35. The same mass of copper is drawn into two wires 1 mm and 2 mm thick. Two wires are connected in series and current is passed through them. Heat produced in the wire is in the ratio
- (a) 2 : 1 (b) 1 : 16
(c) 4 : 1 (d) 16 : 1
36. The temperature of hot junction of a thermo-couple changes from 80°C to 100°C . The percentage change in thermoelectric power is
- (a) 8% (b) 10%
(c) 20% (d) 25%
37. A thermo couple uses Bismuth and Tellurium as the dissimilar metals. The sensitivity of bismuth is $-72\mu\text{V}/^\circ\text{C}$ and that of the tellurium is $500\mu\text{V}/^\circ\text{C}$. If the difference between hot and cold junction is 100°C , then the maximum output will be
- (a) 50 mV (b) 7.2 mV
(c) 42.8 mV (d) 57.2 mV
38. Three wires of copper, iron and nickel are joined to form three junctions as shown in Fig. When the temperature of junction 1 is kept 50°C with the other two junctions at 0°C , the sensitive galvanometer gives a deflection of 14 divisions. When the temperature of junction 3 is kept 50°C , with the other two junctions at 0°C , the galvanometer gives a deflection of 11 divisions. Then the deflection given by the galvanometer, when temperature of the junction 2 is kept at 50°C , with the other two junctions at 0°C , will be
- 
- (a) 3 div (b) 11 div
(c) 14 div (d) 25 div
39. The wiring of a house has resistance 6Ω . A 100 W bulb is glowing. If a geyser of 1000 W is switched on, the change in potential drop across the bulb is nearly [MNR 1998]
- (a) Nil (b) 23 V


- (c) 32 V (d) 12 V

40. A 12 V lead accumulator is being charged using 24 V supply with an external resistance 2Ω . The internal resistance of the accumulator is 1Ω . Find the time in which it will store 360 W-hour energy.

- (a) 1 hr (b) 7.5 hr
(c) 10 hr (d) None of these

41. In a Ag voltameter 2.68 gm of silver is deposited in 10 min. The heat developed in 20Ω resistor during the same period will be

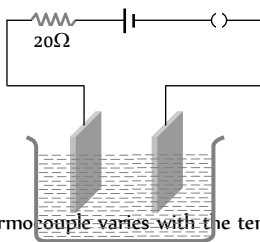- (a) 192 kJ
(b) 192 J
(c) 200 J
(d) 132 kJ




42. The thermo e.m.f. of a thermocouple varies with the temperature θ of the hot junction as $E = a\theta + b\theta^2$ in volts where the ratio a/b is 700°C . If the cold junction is kept at 0°C , then the neutral temperature is [AIIEE 2004]

- (a) 700°C
(b) 350°C
(c) 1400°C
(d) No neutral temperature is possible for this thermocouple

43. In the following circuit, 5Ω resistor develops 45 J/s due to current flowing through it. The power developed per second across 12Ω resistor is [AMU (Engg.) 1999]

- (a) 16 W
(b) 192 W
(c) 36 W
(d) 64 W

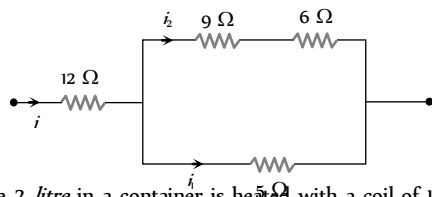


44. Water of volume 2 litre in a container is heated with a coil of 1 kW at 27°C . The lid of the container is open and energy dissipates at rate of 160 J/s. In how much time temperature will rise from 27°C to 77°C [Given specific heat of water is 4.2 kJ/kg]

- (a) 8 min 20 s (b) 6 min 2 s
(c) 7 min (d) 14 min


45. For ensuring dissipation of same energy in all three resistors (R_1, R_2, R_3) connected as shown in figure, their values must be related as [AIIMS 2005]

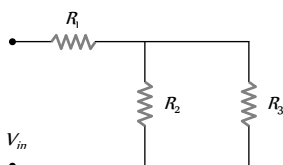- (a) $R_1 = R_2 = R_3$
(b) $R_2 = R_3$ and $R_1 = 4R_2$
(c) $R_2 = R_3$ and $R_1 = \frac{1}{4}R_2$
(d) $R_1 = R_2 + R_3$




1. In a copper voltameter, mass deposited in 30 second is $m\text{ gm}$. If the time-current graph is as shown in figure, ECE of copper is

- (a) m
(b) $m/2$
(c) $0.1m$
(d) $0.6m$

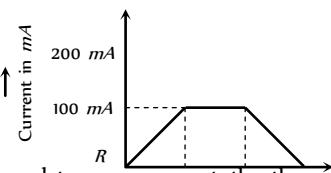


2. Which of the following plots may represent the thermal energy produced in a resistor in a given time as a function of the electric current [MP PMT 1999]


- (a) a
(b) b
(c) c
(d) d

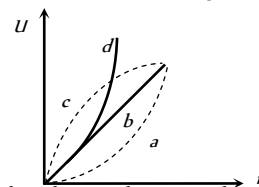

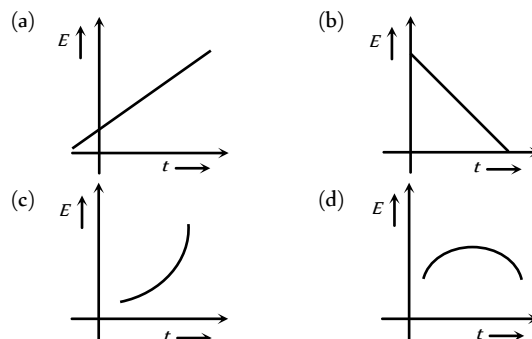
3. Two different metals are joined end to end. One end is kept at constant temperature and the other end is heated to a very high temperature. The graph depicting the thermo e.m.f. is



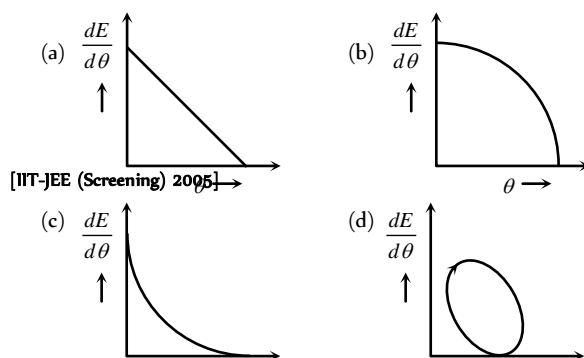
4. Which of the following graphs shows the variation of thermoelectric power with temperature difference between hot and cold junction in thermocouples



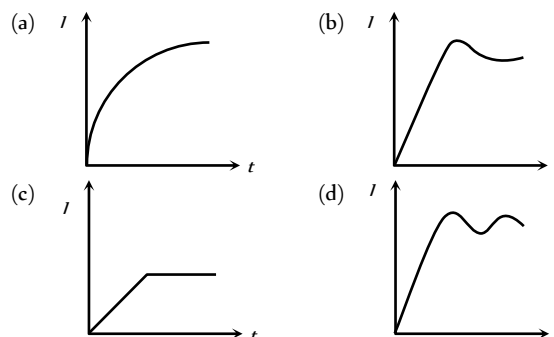5. When an electric heater is switched on, the current flowing through it (i) is plotted against time (t). Taking into account the variation of resistance with temperature, which of the following best represents the resulting curve




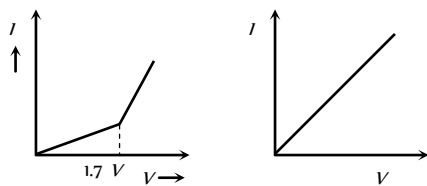6. The V - i graphs A and B drawn for two voltmeters. Identify each graph




- (a) A for water voltmeter and B for Cu voltmeter
 (b) A for Cu voltmeter and B for water voltmeter
 (c) Both A and B represents Cu voltmeter
 (d) None of these

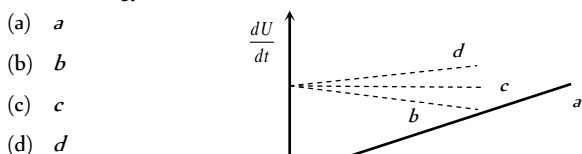
7. A constant current i is passed through a resistor. Taking the temperature coefficient of resistance into account, indicate which of the plots shown in figure best represents the rate of production of thermal energy in the resistor



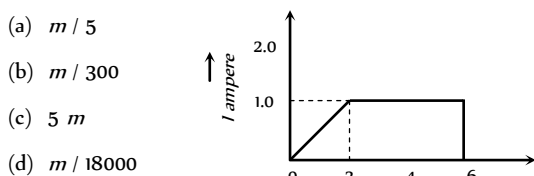8. In a copper voltmeter, mass deposited in 6 minutes is m gram. If the current-time graph for the voltmeter is as shown here, then the E.C.E of the copper is



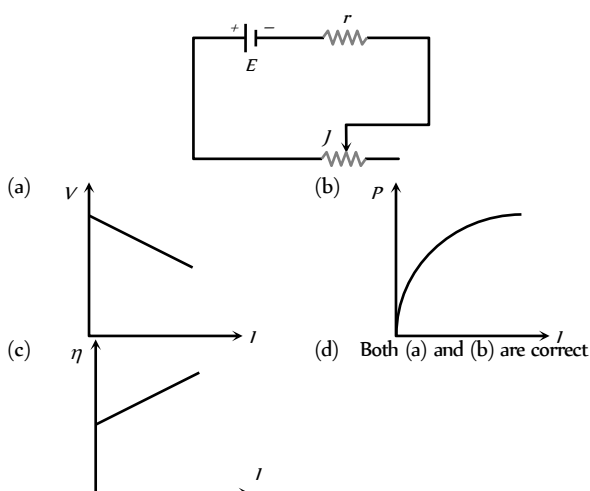- (a) $m/5$
 (b) $m/300$
 (c) $5m$
 (d) $m/18000$
9. Battery shown in figure has e.m.f. E and internal resistance r . Current in the circuit can be varied by sliding the contact J . If at any instant current flowing through the circuit is I , potential difference between terminals of the cell is V , thermal power generated in the cell is equal to η fraction of total electrical power generated in it; then which of the following graph is correct




Read the assertion and reason carefully to mark the correct option out of the options given below :

- (a) If both assertion and reason are true and the reason is the correct explanation of the assertion.
 (b) If both assertion and reason are true but reason is not the correct explanation of the assertion.
 (c) If assertion is true but reason is false.
 (d) If the assertion and reason both are false.
 (e) If assertion is false but reason is true.


- Assertion : The possibility of an electric bulb fusing is higher at the time of switching ON and OFF
 Reason : Inductive effects produce a surge at the time of switch ON and OFF [AIIMS 2003]
- Assertion : The 200 W bulbs glow with more brightness than 100 W bulbs.
 Reason : A 100 W bulb has more resistance than a 200 W bulb.
- Assertion : Fuse wire must have high resistance and low melting point.
 Reason : Fuse is used for small current flow only.
- Assertion : Two electric bulbs of 50 and 100 W are given. When connected in series 50 W bulb glows more but when connected parallel 100 W bulb glows more.
 Reason : In series combination, power is directly proportional to the resistance of circuit. But in parallel combination, power is inversely proportional to the resistance of the circuit.
- Assertion : Two bulbs of same wattage, one having a carbon filament and the other having a metallic filament are connected in series. Metallic bulbs will glow more brightly than carbon filament bulb.
 Reason : Carbon is a semiconductor.
- Assertion : An electric bulb is first connected to a dc source and then to a ac source having the same brightness in both the cases.
 Reason : The peak value of voltage for an A.C. source is $\sqrt{2}$ times the root mean square voltage.
- Assertion : Current is passed through a metallic wire, heating it red. When cold water is poured on half of its portion, then rest of the half portion become more hot.
 Reason : Resistances decreases due to decrease in temperature and so current through wire increases.
- Assertion : Through the same current flows through the line wires and the filament of the bulb but heat produced in the filament is much higher than that in line wires.
 Reason : The filament of bulbs is made of a material of high resistance and high melting point.
- Assertion : Neutral temperature of a thermocouple does not depend upon temperature of cold junction.
 Reason : Its value is constant for the given metals of the couple.
- Assertion : In practical application, power rating of resistance is not important.
 Reason : Property of resistance remain same even at high temperature.
- Assertion : Leclanche cell is used, when constant supply of electric current is not required.
 Reason : The e.m.f. of a Leclanche cell falls, if it is used continuously.

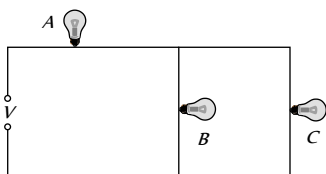12. Assertion : In the given circuit if lamp B or C fuses then light emitted by lamp A decreases.



Reason : Voltage on A decreases.

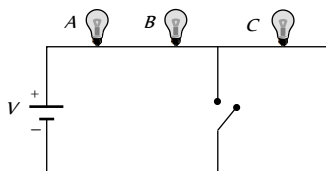13. Assertion : If three identical bulbs are connected in series as shown in figure then on closing the switches. Bulb C short circuited and hence illumination of bulbs A and B decreases.



Reason : Voltage on A and B decreases

14. Assertion : Heat generated continuously in an electric heater but its temperature becomes constant after some time.

Reason : At the stage when heat produced in heater is equal to the heat dissipated to its surrounding the temperature of heater becomes constant.

15. Assertion : Electric appliances with metallic body; e.g. heaters, presses etc, have three pin connections, whereas an electric bulb has a two pin connection. [AIIMS 1996]

Reason : Three pin connections reduce heating of connecting cables.

16. Assertion : A laser beam 0.2 W power can drill holes through a metal sheet, whereas 1000 W torch-light cannot.

Reason : The frequency of laser light is much higher than that of torch light. [AIIMS 1996]

17. Assertion : A domestic electrical appliance, working on a three pin will continue working even if the top pin is removed. [AIIMS 1995]

Reason : The third pin is used only as a safety device.

18. Assertion : In all conductors, for studying the thermoelectric behaviour or metals, lead is taken as a reference metal.

Reason : In lead, the Thomson effect is negative.

19. Assertion : The presence of water molecules makes separation of ions easier in electrolyte.

Reason : The presence of water molecules in electrolyte decreases the resistance of electrolyte.

20. Assertion : Thermocouple acts as a heat engine.

Reason : When two junctions of thermocouple are at different temperature, thermo e.m.f. is produced.

21. Assertion : When temperature of cold junction of a thermocouple is lowered, the value of neutral temperature of this thermocouple is raised.

Reason : When the difference of temperature of two junction is raised, more thermo e.m.f. is produced.

Heating Effect of Current

1	a	2	b	3	c	4	b	5	b
6	c	7	c	8	a	9	b	10	c
11	a	12	c	13	c	14	a	15	d
16	d	17	b	18	c	19	c	20	a
21	d	22	a	23	a	24	c	25	d
26	d	27	c	28	c	29	b	30	b
31	b	32	b	33	a	34	d	35	c
36	b	37	d	38	b	39	a	40	a
41	a	42	b	43	d	44	d	45	a
46	c	47	a	48	b	49	a	50	a
51	b	52	c	53	a	54	c	55	c
56	a	57	d	58	b	59	d	60	a
61	d	62	a	63	d	64	b	65	b
66	d	67	a	68	a	69	a	70	c
71	a	72	d	73	a	74	b	75	a
76	d	77	b	78	b	79	d	80	d
81	a	82	d	83	d	84	d	85	a
86	a	87	a,d	88	a	89	b	90	a
91	b	92	a	93	b	94	a	95	b
96	a	97	c	98	b	99	c	100	a
101	b	102	c	103	a	104	a	105	d
106	c	107	a	108	b	109	b	110	d
111	c	112	b	113	c	114	a	115	c
116	c	117	d	118	a	119	d	120	c
121	b	122	d	123	a	124	a	125	a
126	c	127	a	128	d	129	a	130	c
131	a	132	c	133	c	134	c	135	b
136	c	137	c	138	c	139	b	140	d
141	a	142	c	143	d	144	c	145	b
146	c	147	c	148	c	149	a	150	c
151	a	152	c	153	c				

Chemical Effect of Current

1	d	2	c	3	d	4	d	5	c
6	d	7	b	8	d	9	b	10	a
11	b	12	b	13	b	14	c	15	b
16	a	17	b	18	c	19	a	20	d
21	c	22	b	23	c	24	a	25	d
26	b	27	a	28	c	29	a	30	a
31	b	32	d	33	b	34	a	35	b
36	c	37	c	38	b	39	d	40	b
41	c	42	b	43	d	44	a	45	c
46	c	47	a	48	b	49	b	50	b
51	a	52	d	53	d	54	a	55	c

Answers

56	c	57	d	58	c	59	a
----	---	----	---	----	---	----	---

Thermo-Electricity

1	b	2	c	3	d	4	a	5	c
6	b	7	a	8	a	9	a	10	a
11	a	12	d	13	b	14	c	15	b
16	b	17	a	18	a	19	a	20	b
21	d	22	a	23	b	24	a	25	b
26	c	27	c	28	d	29	c	30	a
31	a	32	b	33	d	34	c	35	c
36	d	37	c	38	d	39	d	40	a
41	d	42	a	43	b	44	b		

Critical Thinking Questions

1	d	2	b	3	b	4	d	5	c
6	d	7	a	8	c	9	d	10	b
11	c	12	b	13	d	14	a	15	a
16	d	17	d	18	a	19	a	20	b
21	c	22	b	23	b	24	b	25	d
26	a	27	b	28	c	29	a	30	b
31	d	32	a	33	a	34	d	35	d
36	d	37	d	38	d	39	b	40	b
41	a	42	d	43	b	44	a	45	c

Graphical Questions

1	b	2	d	3	d	4	a	5	b
6	a	7	d	8	b	9	d		

Assertion and Reason

1	a	2	a	3	c	4	a	5	d
6	e	7	a	8	a	9	b	10	d
11	a	12	a	13	d	14	a	15	c
16	c	17	a	18	c	19	b	20	b
21	d								

Answers and Solutions

Heating Effect of Current

1. (a) $1 \text{ kWh} = 1000 \text{ W} \times 3600 \text{ sec} = 36 \times 10^5 \text{ W-sec (or J)}$

$$2. (b) P \propto \frac{1}{R} \Rightarrow \frac{P_1}{P_2} = \frac{R_2}{R_1} \Rightarrow \frac{200}{100} = \frac{R_2}{R_1} \Rightarrow R_2 = 2R_1$$

$$3. (c) P = \frac{V^2}{R} \Rightarrow R_1 = \frac{V_1^2}{P_1} = \frac{(200)^2}{40} = 1000\Omega$$

$$\text{and } R_2 = \frac{V_2^2}{P_2} = \frac{(200)^2}{100} = 400\Omega$$

4. (b) When two bulbs are connected in series, the current will be same in both the bulbs. As a result potential drop will be more in the bulb of higher resistance *i.e.*, bulb of lower wattage.

5. (b) When 1 bulb fuses, the total resistance of the circuit decreases hence the current increases. Since $P = i^2 R$, therefore illumination increases.

6. (c)

$$7. (c) \text{ We know that } \frac{P_1}{P_2} = \frac{R_2}{R_1} = \frac{2}{1}$$

$$8. (a) P = \frac{V^2}{R} \Rightarrow P \propto \frac{1}{R} \text{ and } R \propto l \therefore P \propto \frac{1}{l} \Rightarrow \frac{P_1}{P_2} = \frac{l_1}{l_2} = \frac{2}{1}$$

$$9. (b) R_{\text{wire}} \propto \text{Temperature and } R_{\text{wire}} \propto \frac{1}{\text{Temperature}}$$

10. (c)

11. (a) In series, current is same in both the bulbs, hence

$$P \propto R (P = i^2 R) \therefore \frac{P_1}{P_2} = \frac{R_1}{R_2} = \frac{1}{2}$$

12. (c) In this case, $P = \frac{V^2}{R}$ or $P \propto \frac{1}{R}$ and R will be minimum, when divided four parts are joints in parallel to the battery.

13. (c) Length is immaterial for an electric fuse wire.

$$14. (a) P_{\text{Rated}} \propto \frac{1}{R} \text{ and } R \propto \frac{1}{(\text{Thickness of filament})^2}$$

$$\text{So } P_{\text{Rated}} \propto (\text{Thickness of filament})^2$$

$$15. (d) \text{ In series } P_s = \frac{P}{n} \Rightarrow 10 = \frac{P}{3} \Rightarrow P = 30 \text{ W}$$

$$\text{In parallel } P_p = nP = 3 \times 30 = 90 \text{ W}$$

$$16. (d) \text{ Energy consumed in kWh} = \frac{\text{Watt} \times \text{hour}}{1000}$$

$$\Rightarrow \text{For 30 days, } P = \frac{10 \times 50 \times 10}{1000} \times 30 = 150 \text{ kWh}$$

$$17. (b) W = qV \text{ also } P = i \times V = \frac{W}{t}$$

18. (c) Because given voltage is very high,

$$19. (c) P_p = nP = 2 \times 40 = 80 \text{ W}$$

20. (a) In series, $P \propto R$ (i is same), *i.e.* in series Fine wire (high R) liberates more energy.

$$\text{In parallel, } P \propto \frac{1}{R} (V \text{ is same}) \text{ i.e. thick wire (less } R) \text{ liberates more energy.}$$

$$21. (d) \text{ Resistance of the bulb} = \frac{V^2}{P_{\text{Rated}}} = \frac{220 \times 220}{100} = 484\Omega$$

1156 Heating and Chemical Effect of Current

When connected with 110 V, the power consumed

$$P_{\text{Consumed}} = \frac{V^2}{R} = \frac{110 \times 110}{484} = 25W$$

22. (a) The resistance of 25 W bulb is greater than 100 W bulb. So for the same current, heat produced will be more in 25 W bulb. So it will glow more brightly.

23. (a) Equivalent resistance in the second case $= R_1 + R_2 = R$

Now, we know that $P \propto \frac{1}{R}$

Since in the second case the resistance $(R_1 + R_2)$ is higher than that in the first case (R) .

Therefore power dissipation in the second case will be decreased.

24. (c) For constant voltage, we know that $P \propto \frac{1}{R}$

So higher the power, lower will be the resistance.

25. (d) $P = \frac{V^2}{R}$ but $R = \frac{\rho l}{A} \Rightarrow P = \frac{V^2}{\rho l / A} = \frac{AV^2}{\rho l}$. Since

$\frac{AV^2}{l}$ is constant as per given conditions So $P \propto \frac{1}{\rho}$.

26. (d) Power consumed means heat produced.

For constant potential difference $P_{\text{consumed}} = \text{Heat} \propto \frac{1}{R_{eq}}$

$$\therefore \frac{H_1}{H_2} = \frac{R_2}{R_1} = \frac{R/2}{2R} = \frac{1}{4}$$

(Since $R_2 = \frac{R \cdot R}{R + R} = \frac{R}{2}$ and $R_1 = R + R = 2R$)

27. (c) Resistance of carbon filament decreases with temperature while that of tungsten increases with temperature
In series $P_{\text{Consumed}} \propto R$ i.e. tungsten bulb will glow more brightly
28. (c) Power of the combination $P_s = \frac{P}{n} = \frac{1000}{2} = 500 \text{ W}$
29. (b) For parallel combination
 $P_{\text{Consumed}} \propto \text{Brightness} \propto P_{\text{Rated}}$
30. (b) Resistance of 25 W bulb $= \frac{220 \times 220}{25} = 1936 \Omega$
Its safe current $= \frac{220}{1936} = 0.11 \text{ amp.}$
Resistance of 100 W bulb $= \frac{220 \times 220}{100} = 484 \Omega$
Its safe current $= \frac{220}{484} = 0.48 \text{ amp.}$
When connected in series to 440 V supply, then the current $I = \frac{440}{(1936 + 484)} = 0.18 \text{ amp.}$
Thus current is greater for 25 W bulb, so it will fuse.
31. (b) $P = i^2 R \Rightarrow \frac{\Delta P}{P} = \frac{2\Delta i}{i}$ ($R \rightarrow \text{Constant}$)
 \Rightarrow % change in power $= 2 \times$ % change in current
 $= 2 \times 1 = 2\%$
32. (b) $P_{\text{max}} = n \left(\frac{E^2}{4r} \right) = 2 \left(\frac{2 \times 2}{4 \times 1} \right) = 2 \text{ W}$
33. (a) $H \propto \frac{1}{R}$ (If $V = \text{constant}$) $\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = \frac{l_2 A_1}{l_1 A_2} = \frac{l_2 r_1^2}{l_1 r_2^2}$
 $\Rightarrow H_2 = 2H_1$
34. (d) $\frac{H}{t} = \frac{V^2}{R} \Rightarrow \frac{H}{t} \propto \frac{1}{R}$
35. (c) $H = i^2 R t$ and $i = \frac{q}{t}$. Hence $H = \frac{q^2 R}{t}$; $\therefore H \propto q^2$
36. (b) $E = \frac{1100 \times 4}{1000} = 4.4 \text{ kWh}$
37. (d) After some time, thermal equilibrium will reach.
38. (b) At constant p.d., heat produced $= \frac{V^2}{R}$ i.e. $H \propto \frac{1}{R}$
39. (a) Power $= 3.75 \times 200 \text{ W} = 750 \text{ W} \approx 1 \text{ H.P.}$
40. (a) $\frac{V^2}{R} = P \Rightarrow R = \frac{V^2}{P} = \frac{220 \times 220}{100} = 484 \Omega$
41. (a) Since $P = VI \Rightarrow I = \frac{P}{V} = \frac{250000}{10000} = 25 \text{ A}$
42. (b) Power lost in cable $= 10 \times (25)^2 = 6250 \text{ W} = 6.25 \text{ kW}$
43. (d) Heat generated in both the cases will be same because the capacitor has the same energy initially
 $= \frac{1}{2} CV^2 = \frac{1}{2} \times 200 \times 10^{-6} \times (200)^2 = 4 \text{ J}$
44. (d) The bulbs are connected in parallel, hence each bulb consumes $\frac{48}{2} = 24 \text{ W}$. Therefore $\frac{V^2}{R} = 24$
 $\Rightarrow R = \frac{6 \times 6}{24} = 1.5 \Omega$
45. (a)
46. (c) The bulbs are in series, hence they will have the same current through them.
47. (a) When resistance is connected in series, brightness of bulb decreases because voltage across the bulb decreases.
48. (b) $R = \frac{V^2}{P} \Rightarrow R_1 = \frac{200 \times 200}{100} = 400 \Omega$ and
 $R_2 = \frac{100 \times 100}{200} = 50 \Omega$. Maximum current rating
 $i = \frac{P}{V}$
So $i_1 = \frac{100}{200}$ and $i_2 = \frac{200}{100} \Rightarrow \frac{i_1}{i_2} = \frac{1}{4}$.
49. (a) $\frac{R_1}{R_2} = \frac{P_2}{P_1} = \frac{100}{40} = \frac{5}{2}$. Resistance of 40 W bulb is $\frac{5}{2}$ times than 100 W. In series, $P = i^2 R$ and in parallel, $P = \frac{V^2}{R}$. So 40 W in series and 100 W in parallel will glow brighter.
50. (a) $P = \frac{V^2}{R} \Rightarrow \frac{P_p}{P_s} = \frac{R_s}{R_p} = \frac{(R_1 + R_2)}{R_1 R_2 / (R_1 + R_2)} = \frac{(R_1 + R_2)^2}{R_1 R_2}$
 $\Rightarrow \frac{100}{25} = \frac{(R_1 + R_2)^2}{R_1 R_2} \Rightarrow \frac{R_1}{R_2} = \frac{1}{1}$
51. (b) Total power $P = (800 + 3 \times 100)$
Also $P = Vi \Rightarrow 1100 = 220 \times i \Rightarrow i = 5 \text{ A}$
52. (c) Because $R \propto \frac{1}{P}$
53. (a) An ideal cell has zero resistance.
54. (c) Power loss in transmission $P_L = \frac{P^2 R}{V^2} \Rightarrow P_L \propto \frac{1}{V^2}$

55. (c) $H = \frac{V^2 t}{4.2 R}$ or $\frac{H}{t} = \frac{V^2}{4.2 R}$
 $\Rightarrow 800 = \frac{20 \times 20}{4.2 \times R} \Rightarrow R = \frac{5}{42} = 0.119 \approx 0.12 \Omega$
56. (a) Heat produced $H = \frac{V^2 t}{4.2 R} = H \propto \frac{1}{R}$ Hence $\frac{H_1}{H_2} = \frac{R_2}{R_1}$
57. (d) $\frac{H}{t} = i^2 R$. Here total $R = (21 + 4) = 25 \Omega$
 \Rightarrow Rate of energy consumed $= 0.2 \times 0.2 \times 25 = 1 \text{ J/s}$
58. (b) When the heating coil is cut into two equal parts and these parts are joined in parallel, the resistance of coil is reduced to one fourth, so power consumed will become 4 times *i.e.* 400 Js⁻¹.
59. (d) The resistance of 40 W bulb will be more and 60 W bulb will be less.
60. (a) In series $P_{\text{Consumed}} \propto \text{Brightness} \propto \frac{1}{P_{\text{Rated}}}$
61. (d) $E = P \times t = 1000 \text{ W} \times 30 \text{ sec} = 3 \times 10^4 \text{ J}$
62. (a) Resistance R_1 of 500 W/bulb $= \frac{(220)^2}{500}$
Resistance R_2 of 200 W/bulb $= \frac{(220)^2}{200}$
When joined in parallel, the potential difference across both the bulbs will be same.
Ratio of heat produced $= \frac{V^2 / R_1}{V^2 / R_2} = \frac{R_2}{R_1} = \frac{5}{2}$
When joined in series, the same current will flow through both the bulbs.
Ratio of heat produced $= \frac{i^2 R_1}{i^2 R_2} = \frac{R_1}{R_2} = \frac{2}{5}$
63. (d) Charge $q = it = 0.5 \text{ A} \times 3600 \text{ sec} = 1800 \text{ coulomb}$
64. (b) $H = i^2 R t = \frac{V^2 t}{R} = \frac{120 \times 120 \times (10 \times 60)}{6} = 14.4 \times 10^5 \text{ joule}$
65. (b) In parallel $P_{\text{consumed}} \propto \text{Brightness} \propto \frac{1}{R}$
 $P_A > P_B$ (given) $\therefore R_A < R_B$
66. (d) $R = \rho \frac{l}{A}$ and $P \propto \frac{1}{R} \Rightarrow P \propto \frac{A}{l} \Rightarrow P \propto \frac{d^2}{l} \Rightarrow P_A = 2P_B$
67. (a) $t_S = t_1 + t_2 = 30 + 30 = 60 \text{ minutes}$
68. (a) For power transmission power loss in line $P_L = i^2 R$

If power of electricity is P and it is transmitted at voltage V , then $P = Vi \Rightarrow i = \frac{P}{V}$

$$P_L = \left(\frac{P}{V} \right)^2 R = \frac{P^2 R}{V^2} = \frac{2.2 \times 10^3 \times 2.2 \times 10^3 \times 10}{22000 \times 22000} = 0.1 \text{ W}$$

69. (a) $P = i^2 R$ (i and R are same)
So P will be same for given resistors.
70. (c) Since $H \propto i^2$, so on doubling the current, the heat produced and hence the rise in temperature becomes four times.
71. (a) Watt-hour meter measures electric energy.
72. (d) Total energy consumed $= \frac{60 \times 8}{1000} = 0.48 \text{ kWh}$
So cost $= 0.48 \times 1.25 = 0.6 \text{ Rs.}$
73. (a) $P_S = \frac{P}{n} = \frac{40}{4} = 10 \text{ W.}$
74. (b) As temperature increases resistance of filament also increases.
75. (a) Current through the combination $i = \frac{120}{(6+9)} = 8 \text{ A}$
So, power consumed by 6Ω resistance
 $P = (8)^2 \times 6 = 384 \text{ W}$
76. (d) $P = \frac{V^2}{R} = \frac{(225)^2}{50} = 1012.5 \approx 1000 \text{ W}$
77. (b) $P = Vi \Rightarrow i = \frac{P}{V} = \frac{100}{200} = 0.5 \text{ A}$
78. (b) $H = i^2 R t \Rightarrow R = \frac{H}{i^2 t} = \frac{80}{4 \times 10} = 2 \Omega$
79. (d) Heat produced = Energy stored in capacitor
 $= \frac{1}{2} C V^2 = \frac{1}{2} \times 4 \times 10^{-6} \times (400)^2 = 0.32 \text{ J}$
80. (d) $P = \frac{V^2}{R} = \frac{(110)^2}{10} = \frac{12100}{10} = 1210 \text{ W}$
81. (a) $P_{\text{consumed}} = \left(\frac{V_A}{V_R} \right)^2 \times P_R = \frac{(160)^2}{(200)^2} \times 100 = 64 \text{ W}$
82. (d) For maximum power $r = R$
83. (d) $P = i^2 R \Rightarrow 22.5 = (15)^2 \times R \Rightarrow R = 0.10 \Omega$
84. (d) $R_1 = \rho \frac{l_1}{A_1}$ and $R_2 = \rho \frac{l_2}{A_2} \Rightarrow \frac{R_1}{R_2} = \frac{l_1}{l_2} \cdot \frac{A_2}{A_1} = \frac{l_1}{l_2} \left(\frac{r_2}{r_1} \right)^2$

Given $\frac{l_1}{l_2} = \frac{1}{2}$ and $\frac{r_1}{r_2} = \frac{2}{1}$ or $\frac{r_2}{r_1} = \frac{1}{2} \Rightarrow \frac{R_1}{R_2} = \frac{1}{8}$

\therefore Ratio of heats $\frac{H_1}{H_2} = \frac{V^2 / R_1}{V^2 / R_2} = \frac{R_2}{R_1} = \frac{8}{1}$

85. (a) $P = Vi = 250 \times 2 = 500 \text{ W}$

86. (a) $P = \frac{V^2}{R} \Rightarrow 100 = \frac{(200)^2}{R} \Rightarrow R = \frac{4 \times 10^4}{10^2} = 400 \Omega$

Now, $i = \frac{V}{R} = \frac{100}{400} = \frac{1}{4} \text{ amp}$

87. (a, d) $R_{\text{steel}} = 2R_{\text{Al}}$. In series $H \propto R$ (i is Same)

So, H will be more in steel wire. In parallel $H \propto \frac{1}{R}$

(V is Same), so H will be more in aluminium wire.

88. (a) $H = i^2 R t \Rightarrow \frac{H}{t} = i^2 R = \frac{i^2 \rho l}{\pi r^2}$

89. (b)

90. (a) $H = \frac{V^2}{R} \cdot t \Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = \frac{R}{2R} = \frac{1}{2}$

91. (b)

92. (a) In parallel $P_{\text{Consumed}} \propto P_{\text{Rated}}$

93. (b)

94. (a) $P = \frac{V^2}{R} \Rightarrow R = \frac{V^2}{P} = \frac{(220)^2}{40} = 1210 \Omega$

95. (b) $P = Vi \Rightarrow i = \frac{P}{V} = \frac{60}{220} = \frac{3}{11} \text{ amp}$

96. (a) In series, $P_{\text{Consumed}} \propto \frac{1}{P_{\text{Rated}}} \propto V_{\text{Applied}}$

i.e. more voltage appears on smaller wattage bulb, so 25 W bulb will fuse

97. (c) Because in series current is same.

98. (b) $P = \frac{V^2}{R} \Rightarrow \frac{P_1}{P_2} = \frac{R_2}{R_1} \Rightarrow \frac{6}{P_2} = \frac{4}{6} = \frac{2}{3} \Rightarrow P_2 = 9 \text{ W}$

99. (c) $\frac{H}{t} = P = \frac{V^2}{R} \Rightarrow P \propto \frac{1}{R}$ also $R \propto \frac{l}{A} \propto \frac{l^2 \rho}{A \cdot l \rho}$

$\Rightarrow R \propto \frac{l^2}{m} \Rightarrow R \propto l^2$ (for same mass)

So $\frac{P_A}{P_B} = \frac{l_B^2}{l_A^2} = \frac{4}{1} \Rightarrow P_A = 20 \text{ W}$

100. (a) $P = \frac{V^2}{R} \Rightarrow \frac{R_1}{R_2} = \frac{P_2}{P_1} = \frac{60}{40} = \frac{3}{2}$

101. (b) $P \propto V^2 \Rightarrow \frac{P}{P_0} = \left(\frac{V}{V_0} \right)^2 \Rightarrow P = \left(\frac{V}{V_0} \right)^2 P_0$

102. (c) $P = \frac{V^2}{R} \Rightarrow R \propto \frac{1}{P}$

So resistance of the 100 W bulb will be minimum

103. (a) In parallel $\frac{1}{t_p} = \frac{1}{t_1} + \frac{1}{t_2} \Rightarrow t_p = \frac{t_1 t_2}{t_1 + t_2}$

$= \frac{5 \times 10}{5 + 10} = \frac{50}{15} = 3.33 \text{ min} = 3 \text{ min. } 20 \text{ sec}$

104. (a) For maximum joule heat produced in resistor external resistance = Internal resistance.

105. (d)

106. (c) $H = \frac{V^2}{R} t \Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = \frac{4}{2} = \frac{2}{1}$

107. (a) If resistances of bulbs are R_1 and R_2 respectively

then in parallel $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow$

$\left(\frac{1}{\frac{V^2}{P_p}} \right) = \left(\frac{1}{\frac{V^2}{P_1}} \right) + \left(\frac{1}{\frac{V^2}{P_2}} \right)$

$\Rightarrow P_p = P_1 + P_2$

108. (b)

109. (b) When wire is cut into two equal parts then power dissipated by each part is $2P_1$

So their parallel combination will dissipate power $P_2 = 2P_1 + 2P_1 = 4P_1$


Which gives $\frac{P_2}{P_1} = 4$

110. (d) $P = \frac{V^2}{R} \Rightarrow \frac{P_2}{P_1} = \frac{V_2^2}{V_1^2}$ ($\because R$ is constant)

$\Rightarrow \frac{P_2}{P_1} = \left(\frac{100}{200} \right)^2 = \frac{1}{4} \Rightarrow P_2 = \frac{P_1}{4} = \frac{40}{4} = 10 \text{ W}$

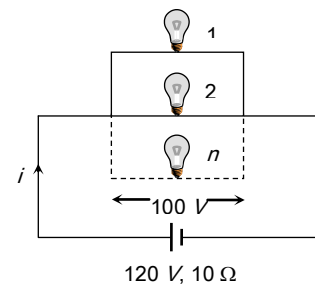111. (c) When each bulb is glowing at full power,

Current from each bulb $= i = \frac{50}{100} = \frac{1}{2} \text{ A}$




So main current $i = \frac{n}{2} A$

$$\text{Also } E = V + ir \Rightarrow 120 = 100 + \left(\frac{n}{2}\right) \times 10 \Rightarrow n = 4$$

$$112. (b) R = \frac{V^2}{P} = \frac{(250)^2}{10^3} = 62.5 \Omega$$

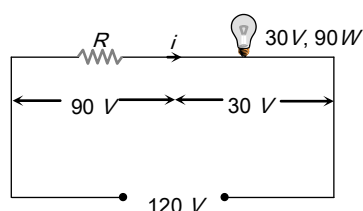113. (c) Suppose resistance R is connected in series with bulb.

$$\text{Current through the bulb } i = \frac{90}{30} = 3 A$$



$$\text{Hence for resistance } V = iR \Rightarrow 90 = 3 \times R \Rightarrow R = 30 \Omega$$

$$114. (a) i \propto r^{3/2} \Rightarrow \frac{r_2}{r_1} = \left(\frac{i_2}{i_1}\right)^{2/3} = \left(\frac{3}{1.5}\right)^{2/3} = (4)^{1/3} \\ \Rightarrow r_2 = (4)^{1/3} \times r_1 = 4^{1/3} (\because r_1 = 1 \text{ mm})$$

$$115. (c) \text{ In series } P' = \frac{P}{n} = \frac{60}{3} = 20 \text{ watts}$$

$$116. (c) R = \frac{V^2}{P} = \frac{(220)^2}{60} = 807 \Omega$$

$$117. (d) \frac{P_1}{P_2} = \left(\frac{V_1}{V_2}\right)^2 \Rightarrow \frac{1000}{P_2} = \left(\frac{220}{110}\right)^2 = 4 \Rightarrow P_2 = 250 W$$

$$118. (a) P_s = \frac{P_1 P_2}{P_1 + P_2} = \frac{100 \times 200}{100 + 200} = \frac{200}{3} \approx 65 \text{ watt}$$

$$119. (d) H = \frac{V^2 t}{R \times J} \text{ Calories} = \frac{P t}{J} = \frac{210 \times 5 \times 60}{4.2} = 15000 \text{ cal}$$

120. (c) Using conservation of energy

Supplied electric energy = absorbed heat energy

$$\Rightarrow i^2 R t = m S T$$

$$\Rightarrow T \propto i^2 \quad (T - \text{change in temperature})$$

i.e. when i is doubled T will be four times i.e.

$$5 \times 4 = 20^\circ C$$

$$121. (b) \text{ Energy} = P \times t = 2 \times 1 \times 30 = 60 \text{ kWh} = 60 \text{ unit}$$


$$122. (d) \text{ Bulb (I) : Rated current } I_1 = \frac{P}{V} = \frac{40}{220} = \frac{2}{11} \text{ amp.}$$

$$\text{Resistance } R_1 = \frac{V^2}{P} = \frac{(220)^2}{40} = 1210 \Omega$$

$$\text{Bulb (II) : Rated current } I_2 = \frac{100}{220} = \frac{5}{11} \text{ amp}$$

$$\text{Resistance } R_2 = \frac{(220)^2}{100} = 484 \Omega$$

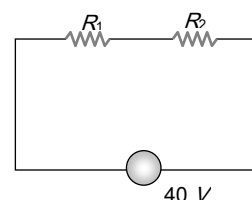When both are connected in series across 40 V supply



Total current through supply

$$I = \frac{40}{P_1 + P_2} = \frac{40}{1210 + 484} = \frac{40}{1254} = 0.03 A$$

This current is less than the rated current of each bulb. So neither bulb will fuse.

Short Trick : Since $V_{\text{Applied}} < V_{\text{Rated}}$, neither bulb will fuse.

123. (a) Both R and $2R$ in parallel (V - constant)

$$\text{So using } P = \frac{V^2}{R} \Rightarrow \frac{P_1}{P_2} = \frac{R_2}{R_1} \Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = \frac{2}{1}$$

124. (a) Power $P = V i t = 250 \times 4 = 1000 W = 1 kW$

$$\text{Energy} = P \times t = 1 \text{ kW} \times 60 \text{ sec} = 60 \text{ kJ}$$

$$125. (a) P = \frac{V^2}{R} \Rightarrow P \propto \frac{1}{R} \quad (V - \text{constant})$$

\therefore When one bulb will fuse out resistance of the series combination will be reduced.

Hence from $P_{\text{Consumed}} \propto \frac{1}{R}$ illumination will increase.


$$126. (c) P = \frac{V^2}{R} \Rightarrow R = \frac{V^2}{P} = \frac{25 \times 25}{25} = 25 \Omega$$

$$127. (a) P_{\text{Rated}} = \frac{V_{\text{Rated}}^2}{R} \Rightarrow R \propto \frac{1}{P_{\text{Rated}}} \quad (V - \text{constant})$$

So bulb of high power will have less resistance.

128. (d) $P_{Rated} \propto \frac{1}{R} \Rightarrow \frac{R_1}{R_2} = \frac{P_2}{P_1} = \frac{60}{40} = \frac{3}{2}$
129. (a) Energy $= \frac{V^2}{R} \times t = \frac{10 \times 10}{50} \times 3600 = 7200 J$
130. (c) Energy $\frac{V^2}{R} t = \frac{200 \times 200 \times 2}{80} = 1000 Wh$
131. (a) Energy $= P \times t = 100 \times 2 \times 60 = 12000 J = 12 \times 10^3 J$
132. (c) Heat $H = \frac{V^2 t}{R} \Rightarrow H \propto \frac{1}{R}$ (If V, t constant)
- $$\Rightarrow \frac{H_S}{H_P} = \frac{R_P}{R_S} = \frac{\left(\frac{R \times 2R}{3R}\right)}{(R+2R)} = \frac{2}{9}$$
133. (c) $i \propto \frac{1}{R}$ and $P \propto \frac{1}{R} \Rightarrow i \propto P$ i.e. in parallel bulb of higher power will draw more current.
134. (c) Resistance of A is greater than the resistance of combination of B and C , hence voltage drop across A will be greater than that across B or C . Also $H = \frac{V^2 t}{R}$
- $$\Rightarrow H \propto V^2 \text{ so } H_A > (H_B = H_C) \quad (R = \text{constant})$$
135. (b) $P = Vi \Rightarrow i = \frac{2.2 \times 10^3}{22000} = \frac{1}{10} A$
- Now loss of power $= i^2 R = \left(\frac{1}{10}\right)^2 \times 100 = 1 W$
136. (c) $P = \frac{V^2}{R}$. If resistance of heater coil is R , then resistance of parallel combination of two halves will be $\frac{R}{4}$
- So $\frac{P_1}{P_2} = \frac{R_2}{R_1} = \frac{R/4}{R} = \frac{1}{4}$
137. (c) Total kWh consumed $= \frac{60 \times 8 \times 30}{1000} = 14.4$
- Hence cost $= 14.4 \times 1.25 = 18 Rs$
138. (c) Current capacity of a fuse wire should be slightly greater than the total rated load current.
139. (b)
140. (d) Colliding electrons lose their kinetic energy as heat.
141. (a) It is called safe current and is proportional to $r^{3/2}$.
142. (c)
143. (d) $i = \frac{P}{V} = \frac{50}{250} = 0.2 amp.$

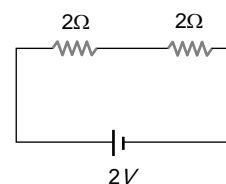144. (c) In steady state the branch containing capacitors, can be neglected. So reduced circuit is as follows



$$\text{Power } P = \frac{V^2}{R} = \frac{(2)^2}{4} = 1 W.$$

145. (b) $P = \frac{V^2}{R_{eq}} \Rightarrow 150 = \frac{(15)^2}{[2R/(R+2)]} = \frac{225 \times (R+2)}{2R}$
- $$\Rightarrow R = \frac{450}{75} = 6 \Omega.$$
146. (c) $P = \frac{V^2}{R} \Rightarrow \frac{P_1}{P_2} = \frac{R_2}{R_1} = \frac{1}{2}$.
147. (c) $H = \frac{V^2 t}{R} \Rightarrow \frac{H_{Half}}{H_{Full}} = \left(\frac{R_{Full}}{R_{Half}}\right) = \frac{R}{R/2} = 2$
- $$\Rightarrow H_{Half} = 2 \times H_{Full}.$$
148. (c) It is given $R_{Hot} = 10 R_{Cold}$ also resistance at rated temperature $R = \frac{V^2}{P} = \frac{200 \times 200}{100} = 400 \Omega$.
- So resistance when lamp not in use.
- $$R_{Cold} = \frac{R_{Hot}}{10} = \frac{400}{10} = 40 \Omega$$
149. (a) The chemical energy reduced in battery
- $$= VIt = 6 \times 5 \times 6 \times 60 J = 10800 J = 1.08 \times 10^4 J$$
150. (c) The heat generated $= I^2 R t = 2.1 \times 15 \times 1 = 31.5 J$
- $$= 31.5 / 4.2 cal = 7.5 cal. \quad [\because 1 cal = 4.2 J]$$
151. (a) Resistance $\propto \frac{1}{\text{power}}$. Thus, 40 W bulb has a high resistance. Because of which there will be more potential drop across 40 W bulb. Thus 40 W bulb will glow brighter.
152. (c) When bulbs are connected in series, $P = \frac{V^2}{R} = \frac{V^2}{3R}$
- When bulbs are connected in parallel,
- $$P' = \frac{V^2}{R''} = \frac{V^2 \times 3}{R} = 3 \times 3P = 9P.$$
153. (c) Time $t_s = t_1 + t_2 = 35 \text{ min.}$

1. (d) As sugar cannot be decomposed into ions and ions are responsible for conduction.
2. (c) $\because \frac{Z_1}{Z_2} = \frac{E_1}{E_2} \Rightarrow Z_2 = \left(\frac{E_2}{E_1}\right) \cdot Z_1$
3. (d) $\frac{m_{Zn}}{m_{Ag}} = \frac{E_{Zn}}{E_{Ag}} \Rightarrow m_{Ag} = W \left(\frac{E_{Ag}}{E_{Zn}}\right) = 3.3 \text{ W} = 3.5 \text{ W}$
4. (d) 96500 *coulombs* of charge is needed to deposit one gram equivalent of an element at an electrode.
5. (c) As $\frac{m_{Cu}}{m_{Ag}} = \frac{E_{Cu}}{E_{Ag}} = \frac{\frac{1}{2}(\text{Atomic weight})_{Cu}}{(\text{Atomic weight})_{Ag}}$
6. (d) $V_2 = \frac{22.4 \times 1}{1} = 22.4 \text{ litre at NTP}$
 $\therefore 11.2 \text{ litre of } H_2 \text{ is liberated by } 96,500 \text{ C}$
 $\therefore 22.4 \text{ litre of } H_2 \text{ is liberated by } 96500 \times 2 = 1,93,000 \text{ C}$
7. (b) From $m = ZQ$, if $Q = 1 \text{ C} \Rightarrow m = Z$
8. (d)
9. (b) Because H^+ has positive charge.
10. (a) Because H_2O is used as electrolyte.
11. (b) $m = Zit \Rightarrow 1 = 0.00033 \times 2 \times t$
 $\therefore t = \frac{1}{0.00066 \times 60} \text{ min} = \frac{100000}{3960} \approx 25 \text{ min}$
12. (b) $3 = 1.5(1+r) \Rightarrow r = 1\Omega$
13. (b)
14. (c) $m = Zit = Zq$; $q = \frac{5 \times 10^{-3}}{3.387 \times 10^{-7}} \text{ amp} \cdot \text{sec}$
or $q = \frac{5 \times 10^{-3}}{3.387 \times 10^{-7} \times 3600} \text{ amp} \cdot \text{hr} = 4.1$
15. (b) Charge $Q = It = 1.6 \times 60 = 96 \text{ C}$
Let n be the number of Cu^{+2} ions, then
 $ne = Q \Rightarrow n = \frac{Q}{e} = \frac{96}{2 \times 1.6 \times 10^{-19}} = 3 \times 10^{20}$
16. (a) In the first case, $Zit = m$
In the second case, $Z \times \frac{i}{4} \times 4t = m$
17. (b) $\frac{\text{Mass of } O_2 \text{ ions}}{\text{Mass of Ag ions}} = \frac{\text{Chemical equivalent of } O_2}{\text{Chemical equivalent of Ag}}$
 $\Rightarrow \frac{0.8}{m} = \frac{8}{108} \Rightarrow m = 10.8 \text{ gm}$
18. (c)
19. (a) $F = Ne = 6 \times 10^{23} \times 1.6 \times 10^{-19}$
20. (d) Since 1 *faraday* deposits 1 *gm* equivalent.
21. (c) Equivalent weight of copper $= \frac{64}{2} = 32$
 $\frac{\text{Equivalent weight of Cu}}{\text{Equivalent weight of Ag}} = \frac{\text{Weight of Cu deposited}}{\text{Weight of Ag deposited}}$
Weight of copper deposited $= \frac{10.8 \times 32}{108} = 3.2 \text{ gm}$
22. (b)
23. (c)
24. (a) $m \propto q \Rightarrow m \propto it$
25. (d) Equivalent weight of aluminium $= \frac{27}{3} = 9$
So 1 *faraday* = 96500 *C* are required to liberate 9 *gm* of *Al*.
26. (b) By Faraday's law, $m \propto it$.
 $\therefore \frac{m_1}{m_2} = \frac{i_1 t_1}{i_2 t_2} \Rightarrow \frac{m}{m_2} = \frac{4 \times 120}{6 \times 40} \Rightarrow m_2 = \frac{m}{2}$
27. (a) $m \propto it$
28. (c) Amount of metallic sodium appears
 $m = Zit = \left(\frac{A}{VF}\right)it$
 $= \left(\frac{23}{1 \times 96500}\right) \times 16 \times 10 \times 60 = 2.3 \text{ gm}$
29. (a)
30. (a) $m = Zit \Rightarrow Z = \frac{m}{it} = \frac{4.572}{5 \times 45 \times 60} = 3.387 \times 10^{-4} \text{ gm / C}$
31. (b) Faraday constant = 1 mole electron charge = *Ne*
 $= 6.02 \times 10^{23} \times 1.6 \times 10^{-19} = 96500$
32. (d) $m = Zit = 0.126 \times 10^{-3} \times 5 \times 3600 = 2.27 \text{ gm}$
33. (b) $\frac{m_1}{m_2} = \frac{E_1}{E_2}$ (By faraday law for same current and time)
Where E_1 and E_2 are the chemical equivalents and m_1 and m_2 are the masses of copper and silver respectively.
 $E = \frac{\text{Atomic weight}}{\text{Valency}} \cdot E_1 = \frac{63.57}{2} = 31.79$ and
 $E_2 = \frac{107.88}{1} = 107.88$
 $\therefore \frac{1 \text{ mg}}{m_2} = \frac{31.79}{107.88} \Rightarrow m_2 = \frac{107.88}{31.79} \text{ mg} = 3.4 \text{ mg}$
34. (a) $m = Zit \Rightarrow \frac{m}{Zit} = 1$ (constant)

35. (b) Positive ions get deposited on cathode.

36. (c) $m = Zit$ or $m \propto it$

$$\therefore \frac{m_1}{m_2} = \frac{i_1 t_1}{i_2 t_2} \Rightarrow \frac{9}{m_2} = \frac{10^5}{50 \times 20 \times 60} \Rightarrow m_2 = 5.4 \text{ gm}$$

37. (c) Electroplating only provides a thin deposition of a metal on the surface which in no way can give hardness to the metal.

38. (b)

39. (d) $m = Zit \Rightarrow \frac{m_{\text{Cu}}}{m_{\text{Zn}}} = \frac{Z_{\text{Cu}}}{Z_{\text{Zn}}}$

$$m_{\text{Cu}} = m_{\text{Zn}} \frac{Z_{\text{Cu}}}{Z_{\text{Zn}}} = 0.13 \times \frac{31.5}{32.5} = 0.126 \text{ g}$$

40. (b) $m = Zit \Rightarrow m = \frac{ZVt}{R} \Rightarrow m \propto Vt \Rightarrow \frac{m_1}{m_2} = \frac{V_1 t_1}{V_2 t_2}$

$$\Rightarrow \frac{2}{m_2} = \frac{12 \times 30}{6 \times 45} \Rightarrow m_2 = 1.5 \text{ gm}$$

41. (c) $i = \frac{m}{Zt} = \frac{0.972}{0.00018 \times 3 \times 3600} = 0.5 \text{ A}$

42. (b) The current through the voltmeter is same as drawn from the battery outside it.

43. (d) The resistance of the cell is independent of e.m.f.

44. (a) $m = Zit = 3.3 \times 10^{-7} \times 3 \times 2 = 19.8 \times 10^{-7} \text{ kg}$

45. (c) $m = zq$, z = atomic mass / valence

46. (c)

47. (a)

48. (b) 1 faraday (96500 C) is the electricity which liberated that amount of substance which is equal to equivalent wt. So liberated amount of Cu is $\frac{63.5}{2}$
 $= 31.25 \text{ gm} \approx 32 \text{ gm}$

49. (b) $m = Zit \Rightarrow 20 \times 10^{-3} = \left(\frac{32}{96500} \right) \times 0.15 \times t$
 $= 6.7 \text{ min} = 6 \text{ min.} 42 \text{ sec}$

50. (b) 22.4 litre H_2 = 1 mole H_2 = N molecules of H_2
 $= 2N$ atom of H

So charge required to liberate 22.4 litre of H_2 = $2Ne$ = $2F$

Hence charge required to liberate 0.224 litre of H_2
 $= \frac{2F}{22.4} \times 0.224 = \frac{2F}{100} = 2 \times 965 \text{ C}$

$$\text{So current } i = \frac{Q}{t} = \frac{2 \times 965}{100} = 19.3 \text{ amp}$$

51. (a)

52. (d) $m = Zit \Rightarrow Z = \frac{m}{it} = \frac{4.5}{4 \times 40 \times 60} = 47 \times 10^{-5} \text{ g/C}$

53. (d) Charge supplied per minute = $3.2 \times 60 = 192 \text{ C}$

Charge $2e$ liberates one Cu^{+2} ion

\therefore No of Cu^{+2} ion liberate by 192 C

$$= \frac{192}{2e} = \frac{192}{2 \times 1.6 \times 10^{-19}} = 6 \times 10^{20}$$

54. (a) $m = Zit \Rightarrow i = \frac{m}{Zt} = \frac{0.99}{0.00033 \times 1200} = 2.5 \text{ A}$

Hence heat generated in the coil is

$$H = i^2 R t = (2.5)^2 \times 0.1 \times 1200 = 750 \text{ J}$$

55. (c) $\frac{m_1}{m_2} = \frac{Z_1}{Z_2} \Rightarrow m_2 = \frac{m_1 Z_2}{Z_1} = \frac{14 \times 1.2 \times 10^{-6}}{7 \times 10^{-6}} = 2.4 \text{ g}$

56. (c) $m = Zit \Rightarrow t = \frac{m}{Zi} = \frac{m \times F}{E \times i} \left(\because Z = \frac{E}{F} \right)$

$$t = \frac{27 \times 96500}{108 \times 2} = 12062.5 \text{ sec} = \frac{12062.5}{3600} \text{ hr} = 3.35 \text{ hr}$$

57. (d) $m = zq \Rightarrow z \propto \frac{1}{q} \Rightarrow \frac{z_1}{z_2} = \frac{q_2}{q_1} \dots\dots(i)$

$$\text{also } q = q_1 + q_2 \Rightarrow \frac{q}{q_2} = \frac{q_1}{q_2} + 1$$

$$\Rightarrow q_2 = \frac{q}{1 + \frac{q_1}{q_2}} \dots\dots(ii)$$

$$\text{From equation (i) and (ii) } q_2 = \frac{q}{1 + \frac{z_2}{z_1}}$$

58. (c) From Faraday's law, m/E = constant

where m = mass of substance deposited, E = chemical equivalent.

$$\therefore \frac{m_2}{m_1} = \frac{E_2}{E_1} \Rightarrow m_2 = \frac{108}{32} \times 1.6 = 5.4 \text{ g}$$

59. (a) $q = it$ = current \times time

Thermo-Electricity

1. (b) Production of e.m.f. by temperature difference is known Seeback effect.

2. (c) Production of heat at junctions due to current is known as Peltier effect.

3. (d)
4. (a)
5. (c) When there is no deflection, then this temperature is called inversion temperature. It is given by the relation
- $$\theta_n = \frac{\theta_i + \theta_c}{2}$$
- Where θ_c is temperature of cold junction = 20°C and neutral temperature $\theta_n = 270^\circ\text{C}$
- $$\therefore \theta_i = 2\theta_n - \theta_c = 540 - 20 = 520^\circ\text{C}$$
6. (b)
7. (a) Thermo e.m.f. of a thermo couple depends on the nature of metals.
8. (a)
9. (a) According to the definition.
10. (a) $T_n = \frac{T_i + T_c}{2} \Rightarrow T_i = 2T_n - T_c$
11. (a)
12. (d)
13. (b) Based on Peltier effect.
14. (c) Peltier effect
15. (b) Thermopile is used for detection of heat radiation and measurement.
16. (b) $H = \sigma i t \Delta\theta \Rightarrow$ If $i = 1\text{ A}$, $\Delta\theta = 1^\circ\text{C}$, $t = 1\text{ sec}$ then $H = \sigma$.
17. (a) According to Seebeck effect
18. (a) At neutral temperature, $\frac{dE}{dT} = 0$
19. (a) According to Seebeck effect.
20. (b)
21. (d)
22. (a) As a rule, more the metals are separated from each other in the thermoelectric series, the greater will be the thermo emf.
23. (b) $T_n = \frac{T_i + T_c}{2} = \frac{10 + 530}{2} = 270^\circ\text{C}$
24. (a) Joule effect is not reversible.
25. (b)
26. (c)
27. (c) The graph between thermo emf and temperature of hot junction is parabolic in shape.
28. (d) At neutral temperature E is maximum so
- $$\frac{dE}{dt} = 0 \Rightarrow \frac{d}{dt}(At - Bt^2) = 0 \Rightarrow A - 2Bt = 0 \Rightarrow t = \frac{A}{2B}$$
29. (c) $t_n = \frac{t_1 + t_c}{2} \Rightarrow 280 = \frac{t_i + 15}{2} \Rightarrow t_i = 545^\circ\text{C}$
30. (a)
31. (a) A is false because at neutral temperature thermo emf is maximum. B is true.
32. (b) Thermo-electric power $P = \frac{dE}{d\theta}$; at t_n , $E \rightarrow$ maximum. So $P \rightarrow$ zero.
33. (d) By using $H = \sigma Q \theta$
- $$\Rightarrow H = (10 \times 10^{-6}) \times 10 \times (60 - 50) = 10^{-3}\text{ J} = 1\text{ mJ}$$
34. (c) No change in neutral temperature but temperature of inversion is $t_i = 2t_n - t_c \Rightarrow t_i = 2 \times 270 - 40 = 500^\circ\text{C}$
35. (c)
36. (d) $t_i = 2t_n - t_c \Rightarrow t_i = 2 \times 350 - 30 = 670^\circ\text{C}$
37. (c)
38. (d) Neutral temperature is independent of temperature of cold junction.
39. (d)
40. (a) $E = at + bt^2$ at inversion temperature E will be minimum
- $$\text{Thus } \frac{dE}{dt} = 0 \Rightarrow \frac{d}{dt}[at + bt^2] = 0$$
- $$\Rightarrow a + 2bt = 0 \Rightarrow t = -\frac{a}{2b}$$
41. (d)
42. (a) $i = \frac{e}{R} \Rightarrow 3 \times 10^{-7} = \frac{(30 \times 10^{-6}) \times \theta}{50} \Rightarrow \theta = 0.5^\circ$
43. (b) $t_n = \frac{\alpha}{\beta} = \left(\frac{500}{5}\right) = 100^\circ\text{C}$
- $$\text{Also } t_n = \frac{t_i + t_c}{2} \Rightarrow 100 = \frac{t_i + 0}{2} \Rightarrow t_i = 200^\circ\text{C}$$
44. (b) At neutral temperature, thermal emf will be maximum.
- $$\therefore \frac{de}{dt} = a + bt$$
- For maximum or minima, $a + bt_n = 0$
- $$\therefore t_n = -a/b$$

Critical Thinking Questions

1. (d) $P_1 = \frac{(220)^2}{R_1}$ and $P_2 = \frac{(220 \times 0.8)^2}{R_2}$

$$\frac{P_2}{P_1} = \frac{(220 \times 0.8)^2}{(220)^2} \times \frac{R_1}{R_2} \Rightarrow \frac{P_2}{P_1} = (0.8)^2 \times \frac{R_1}{R_2} \quad \text{Here } R_2 <$$

R_1

(because voltage decreases from 220 V \rightarrow 220 \times 0.8 V)

It means heat produced \rightarrow decreases)

$$\text{So } \frac{R_1}{R_2} > 1 \Rightarrow P_2 > (0.8)^2 P_1 \Rightarrow P_2 > (0.8)^2 \times 100 \text{ W}$$

$$\text{Also } \frac{P_2}{P_1} = \frac{(220 \times 0.8) i_2}{220 i_1}, \text{ Since } i_2 < i_1 \text{ (we expect)}$$

$$\text{So } \frac{P_2}{P_1} < 0.8 \Rightarrow P_2 < (100 \times 0.8)$$

Hence the actual power would be between $100 \times (0.8)^2 \text{ W}$ and $(100 \times 0.8) \text{ W}$


2. (b) $W = JH \Rightarrow P \times t = J \times m \times s \Delta \theta$

$$\Rightarrow t = \frac{J \times m \times s \Delta \theta}{P} \quad (\text{For water 1 litre} = 1 \text{ kg})$$

$$\Rightarrow t = \frac{4.2 \times 1 \times 1000 \times (40 - 10)}{836} = 150 \text{ sec}$$

Short Trick : use formula $t = \frac{4200 \times m \times \Delta \theta}{P}$

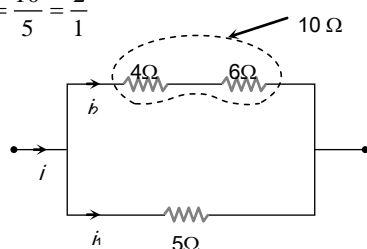3. (b) $\frac{i_1}{i_2} = \frac{R_2}{R_1} = \frac{10}{5} = \frac{2}{1}$



Also heat produced per sec i.e. $\frac{H}{t} = P = i^2 R$

$$\Rightarrow \frac{P_5}{P_4} = \left(\frac{i_1}{i_2} \right)^2 \times \frac{5}{4} = \left(\frac{2}{1} \right)^2 \times \frac{5}{4} = \frac{5}{1} \Rightarrow P_4 = \frac{10}{5} = 2 \text{ cal/s}$$

4. (d) $220 \times 9 = n(60) \Rightarrow n = 33$

5. (c) $H = \frac{V^2}{R} t$

Since supply voltage is same and equal amount of heat will produce, therefore

$$\frac{R_1}{t_1} = \frac{R_2}{t_2} \quad \text{or} \quad \frac{R_1}{R_2} = \frac{t_1}{t_2} \quad \dots(i)$$


$$\text{But } R \propto l \Rightarrow \frac{R_1}{R_2} = \frac{l_1}{l_2} \quad \dots(ii)$$

$$\text{By (i) and (ii), } \frac{l_1}{l_2} = \frac{t_1}{t_2} \quad \dots(iii)$$

$$\text{Now } l_2 = \frac{2}{3} l_1 \Rightarrow \frac{l_1}{l_2} = \frac{3}{2}$$

$$\therefore \text{By equation (iii), } \frac{3}{2} = \frac{15}{t_2} \Rightarrow t_2 = 10 \text{ minutes}$$

6. (d)

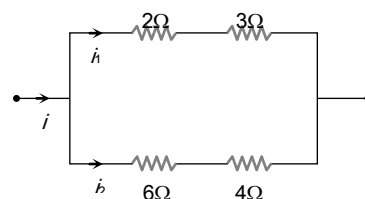

Resistance of upper branch $R_1 = 2 + 3 = 5 \Omega$

Resistance of lower branch $R_2 = 4 + 6 = 10 \Omega$


$$\text{Hence } \frac{i_1}{i_2} = \frac{R_2}{R_1} = \frac{10}{5} = 2$$

$$\frac{\text{Heat generated across } 3 \Omega (H_1)}{\text{Heat generated across } 6 \Omega (H_2)} = \frac{i_1^2 \times 3}{i_2^2 \times 6} = \frac{4}{2} = 2$$

\therefore Heat generated across 3 $\Omega = 120 \text{ cal/sec}$

7. (a) Power consumed by heater is 110 W so by using

$$P = \frac{V^2}{R}$$

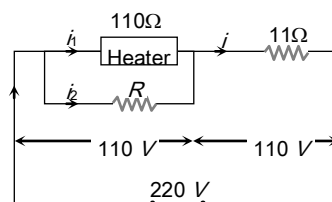

$$110 = \frac{V^2}{110} \Rightarrow V = 110 \text{ V. Also from figure}$$

$$i_1 = \frac{110}{110} = 1 \text{ A and } i = \frac{110}{11} = 10 \text{ A. So } i_2 = 10 - 1 = 9 \text{ A}$$

Applying Ohms law for resistance R , $V = iR$

$$\Rightarrow 110 = 9 \times R \Rightarrow R = 12.22 \Omega$$

8. (c) $P_{\text{consumed}} = \left(\frac{V_A}{V_R} \right)^2 \times P_R = \left(\frac{110}{115} \right)^2 \times 500 = 457.46 \text{ W}$

So, percentage drop in power output

$$= \frac{(500 - 457.46)}{500} \times 100 = 8.6\%$$

9. (d) Heat produced $= \frac{V^2}{R} t$

i.e. when voltage is halved, heat produced becomes one-fourth. Hence time taken to heat the water becomes four times.

10. (b) Electric power consumed by kettle $P = 220 \times 4 \text{ W}$

Heat required

$$H = 1000 \times 1(100 - 20) = 1000 \times 80 \text{ cal} = 4200 \times 80 \text{ J}$$


$$P = \frac{H}{t} \Rightarrow H = P \times t$$

$$\therefore 220 \times 4 \times t = 4200 \times 80 \Rightarrow t = 6.3 \text{ minutes}$$

11. (c) $H = \frac{V^2}{R} \times t = \frac{(210)^2}{20} \times 1 = mL$

$$\therefore \frac{(210)^2}{20} = m \times 80 \times 4.2 \Rightarrow m = 6.56 \text{ g/s}$$

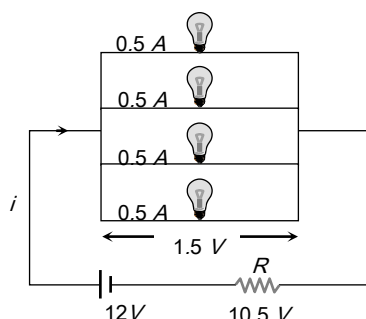12. (b) For normal brightness of each bulb see following circuit. Current through each bulb = 0.5 A



So main current $i = 2 \text{ A}$

Also, voltage across the combination = 1.5 V

So voltage across the resistance = 10.5 V

Hence for resistance $V = iR \Rightarrow 10.5 = 2 \times R$

$$\Rightarrow R = \frac{21}{4} \Omega$$

13. (d) $P = \frac{V^2}{R}$ so $R = \frac{V^2}{P} \Rightarrow R_1 = \frac{V^2}{100}$ and $R_2 = R_3 = \frac{V^2}{60}$

$$\text{Now } W_1 = \frac{(250)^2}{(R_1 + R_2)^2} \cdot R_1, W_2 = \frac{(250)^2}{(R_1 + R_2)^2} \cdot R_2$$

$$\text{and } W_3 = \frac{(250)^2}{R_3}$$

$$W_1 : W_2 : W_3 = 15 : 25 : 64 \text{ or } W_1 < W_2 < W_3$$

14. (a) Power dissipated $\propto R_{\text{equivalent}}$

15. (a) The current taken by the silver voltmeter

$$I_1 = \frac{m}{Zt} = \frac{1}{11.2 \times 10^{-4} \times 30 \times 60} = 0.496 \text{ A}$$


and by copper voltmeter

$$I_2 = \frac{1.8}{6.6 \times 10^{-4} \times 30 \times 60} = 1.515 \text{ A}$$

$$\text{Total current } I = (I_1 + I_2) = 2.011 \text{ A}$$


$$\text{Power } P = IV = 2.011 \times 12 = 24.132 \text{ J/sec}$$

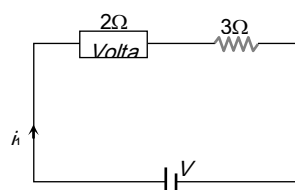16. (d) Initially current through the voltmeter $i_1 = \frac{V}{(3+2)} = \frac{V}{5}$



$$\text{Finally main current } i = \frac{V}{3+1} = \frac{V}{4}$$
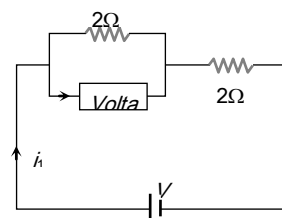
$$\text{Hence current through voltmeter } i_2 = \frac{V}{8}$$



$$\therefore \text{Rate of deposition } (R) = \frac{m}{t} = Zi \Rightarrow R \propto i$$

$$\therefore \% \text{ drop in rate} = \frac{R_2 - R_1}{R_1} \times 100 = \frac{i_2 - i_1}{i_1} \times 100$$

$$= \left(\frac{\frac{V}{8} - \frac{V}{5}}{\frac{V}{5}} \right) \times 100 = -37.5\%$$

17. (d) Comparing the given equation with standard equation

$$E = \alpha t + \frac{1}{2} \beta t^2$$

$$\alpha = 40 \text{ and } \frac{1}{2} \beta = -\frac{1}{20} \Rightarrow \beta = -\frac{1}{10}$$

$$\text{Hence neutral temperature } t_n = -\frac{\alpha}{\beta} = \frac{-40}{-1/10}$$

$$\Rightarrow t_n = 400^\circ \text{C}$$

18. (a) Comparing the given equation with standard equation

$$E = \alpha t + \frac{1}{2} \beta t^2, \text{ we get } \alpha = 14 \text{ and } \frac{1}{2} \beta = -0.02$$

$$\Rightarrow \beta = -0.04$$

Hence neutral temperature

$$t_n = -\frac{\alpha}{\beta} = -\frac{14}{-0.04} = 350^\circ \text{C}$$

19. (a) We know that thermoelectric power $S = \frac{dE}{dT}$

$$\text{Given } E = k(T - T_r) \left[T_0 - \frac{1}{2}(T + T_r) \right]$$

By differentiating the above equation w.r.t. T and

$$\text{Putting } T = \frac{1}{2} T_0, \text{ we get } S = \frac{1}{2} k T_0$$

20. (b) Comparing the given equation with $E = \alpha t + \frac{1}{2} \beta t^2$

$$\text{We get } \alpha = 16 \text{ and } \frac{1}{2} \beta = -0.04 \Rightarrow \beta = -0.08$$

$$\Rightarrow t_n = -\frac{\alpha}{\beta} = -\frac{16}{-0.08} = 200^\circ \text{C}$$

$$\text{Also } t_i = 2t_n - t_c \Rightarrow t_i = 2 \times (200) - 0 = 400^\circ \text{C}$$


21. (c) $m = Zit \Rightarrow 20 \times 10^{-3} = \left(\frac{32}{96500} \right) \times 0.15 \times t$

$$= 6.7 \text{ min} = 6 \text{ min. } 42 \text{ sec.}$$

22. (b) $e = iR \Rightarrow 25 \times 10^{-6} \times \Delta\theta = 10^{-5} \times 40$

$$\Delta\theta = \frac{40 \times 10^{-5}}{25 \times 10^{-6}} = \frac{400}{25} = 16^\circ \text{C}$$

23. (b)

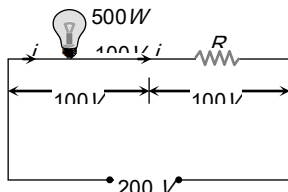

$$\text{Rated current through the circuit } i = \frac{500}{100} = 5 \text{ A}$$

Potential difference across R ,

$$100 = 5 \times R \Rightarrow R = 20 \Omega$$

24. (b) By using $e_0^{100} = e_0^{32} + e_{32}^{70} + e_{70}^{100}$

$$\Rightarrow 200 = 64 + 76 + e_{70}^{100} \Rightarrow e_{70}^{100} = 60 \mu\text{V}$$

25. (d) In the normal condition current flows from X to Y through cold. While after increasing the temperature of hot junction beyond temperature of inversion. The current is reversed i.e. X to Y through hot junction or Y to X through cold junction.


26. (a) $H = \pi it = (2 \times 10^{-9}) \times 2.5 \times (2 \times 60) = 6 \times 10^{-7} \text{ J} = 6 \text{ erg}$

27. (b) Remember mass of the metal deposited on cathode depends on the current through the voltmeter and not on the current supplied by the battery. Hence by

$$\text{using } m = Zit, \text{ we can say } \frac{m_{\text{Parallel}}}{m_{\text{Series}}} = \frac{i_{\text{Parallel}}}{i_{\text{Series}}}$$

$$\Rightarrow m_{\text{Parallel}} = \frac{5}{2} \times 1 = 2.5 \text{ gm.}$$
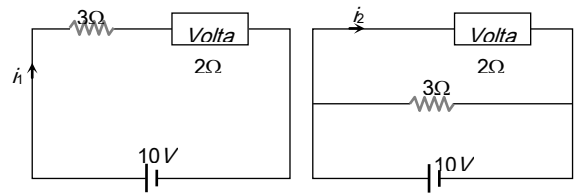
$$\text{Hence increase in mass} = 2.5 - 1 = 1.5 \text{ gm}$$



28. (c) Mass deposited $m = \text{Density} \times \text{Volume of the metal}$

$$\Rightarrow m = \rho \times Ax. \text{ Also } m = Zit, \text{ so } Zit = \rho Ax$$

$$\Rightarrow x = \frac{Zit}{A\rho} = \frac{0.00033 \times 10^{-3} \times 1.5 \times 20 \times 60}{(50 \times 10^{-4}) \times 9000} = 1.3 \times 10^{-5} \text{ m}$$

29. (a) $i = \frac{m}{Zt} = \frac{2.0124}{1.118 \times 10^{-3} \times 3600} = 0.5 \text{ A}$

$$\Rightarrow \text{Error} = 0.54 - 0.5 = 0.04 \text{ A}$$

30. (b) Total charge supplied $= 1 \times 10 = 10 \text{ C}$

\therefore 2 electronic charge ($3.2 \times 10^{-19} \text{ C}$) liberates one Cu^{++} ion

\therefore Number of Cu^{++} ions liberated by 10 C charge

$$= \frac{1}{3.2 \times 10^{-19}} \times 10 = 3.1 \times 10^{19}$$

31. (d) $\therefore m = Zit$ or $i = \frac{m}{Zt}$

For silver voltmeter

$$i_1 = \frac{m_1}{Z_1 t} = \frac{2}{1.118 \times 10^{-3} \times 1800} = 0.994 \text{ amp}$$

For copper voltmeter

$$i_2 = \frac{m_2}{Z_2 t} = \frac{1}{3.294 \times 10^{-4} \times 1800} = 1.687 \text{ amp}$$

$$\therefore \text{Power of circuit} = V(i_1 + i_2) = 6 \times (0.994 + 1.687)$$

$$= 6 \times 2.681 \approx 16 \text{ W}$$

32. (a) Let the temperature of molten metal is $t^\circ \text{C}$.

The thermo-emf $e = 10 \times 10^{-6} t \text{ volt}$

Current in the circuit

$$i = \frac{e}{R + R_G} = \frac{10^{-5} t}{8 + 1.6} = \frac{10^{-5} t}{9.6} \text{ amp.}$$

$$\text{But } i = \frac{V}{R_G} = \frac{8 \times 10^{-3}}{8}$$

$$\therefore \frac{10^{-5} t}{9.6} = \frac{8 \times 10^{-3}}{8} \text{ or } t = \frac{9.6 \times 10^{-3}}{10^{-5}} = 960^\circ \text{C}$$

33. (a) \therefore Peltier coefficient $\pi = T \frac{de}{dT}$ and $t^\circ \text{C} = T - 273$

$$\therefore e = a(T - 273) + b(T - 273)^2$$

$$\text{Differentiating w.r.t. } T \quad \frac{de}{dT} = a + 2b(T - 273)$$

$$\pi = T \frac{de}{dT} = T[a + 2b(T - 273)] \Rightarrow \pi = (t + 273)(a + 2bt)$$

34. (d) $\frac{Q}{t} = \frac{V^2}{4.2 R} = \frac{m}{t} \cdot L$

$$\therefore \frac{m}{t} = \frac{V^2}{4.2 RL} = \frac{(210)^2}{4.2 \times 50 \times 80} \approx 2.625 \text{ gm}$$

35. (d) $H = i^2 RT = i^2 \left(\frac{\rho L}{A} \right) t = \frac{i^2 \rho V t}{A^2}$ ($V = \text{volume} = AL$)

$$\Rightarrow H \propto \frac{1}{r^4} \Rightarrow \frac{H_1}{H_2} = \left(\frac{r_2}{r_1} \right)^4 = \left(\frac{2}{1} \right)^4 = \frac{16}{1}$$

36. (d) Thermoelectric power $P \propto \theta$

$$\Rightarrow \frac{P_{100} - P_{80}}{P_{80}} \times 100 = \frac{100 - 80}{80} \times 100 = 25\%$$


37. (d) The sensitivity of the thermocouple will be $= 500 \mu\text{V}/^\circ \text{C} - (-72 \mu\text{V}/^\circ \text{C}) = 572 \mu\text{V}/^\circ \text{C}$

Therefore for a 100°C temperature difference, the thermo e.m.f. will be

$$E = 572 \times 10^{-6} \times 100 (\text{volt}) = 57.2 \times 10^{-3} = 57.2 \text{ mV.}$$

38. (d) At cold junction, current flows from copper to nickel and from iron to copper, and at hot junction from nickel to iron, thus the contributions add.

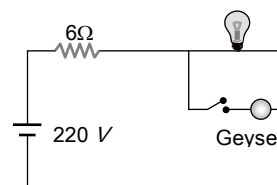39. (b) $R_{\text{Bulb}} = \frac{220^2}{100} = 484 \Omega$, $R_{\text{Geyser}} = \frac{220^2}{1000} = 48.4 \Omega$



- (i) When only bulb is ON,

$$V_{\text{Bulb}} = \frac{220 \times 484}{490} = 217.4 \text{ V}$$

- (ii) When geyser is also switched ON, equivalent resistance of bulb and geyser is

$$R = \frac{484 \times 48.4}{484 + 48.4} = 44 \Omega$$

$$\text{Voltage across the bulb } V_{\text{Bulb}} = \frac{220 \times 44}{50} = 193.6 \text{ V}$$

Hence the potential drop is $217.4 - 193.6 = 23.8 \text{ V}$

40. (b) $i = \frac{24 - 12}{3} = 4 \text{ A}$, Time of charging $t = \frac{360}{V \cdot i}$

$$\Rightarrow t = \frac{360}{12 \times 4} = 7.5 \text{ hours.}$$

41. (a) $I = \frac{m}{Zt} = \frac{2.68}{\frac{108}{96500} \times 10 \times 60} = \frac{2.68}{108} \times \frac{965}{6} \approx 4 \text{ A}$


$$\text{Energy} = I^2 R t = 4^2 \times 20 \times 600 = 192 \text{ kJ.}$$

42. (d) Comparing with standard equation $E = \alpha t + \frac{1}{2} \beta t^2$

$$\alpha = a \text{ and } \beta = 2b \Rightarrow t_n = -\frac{a}{2b} = -\frac{1}{2} \times 700 = -350^\circ \text{C}$$

This is not possible.

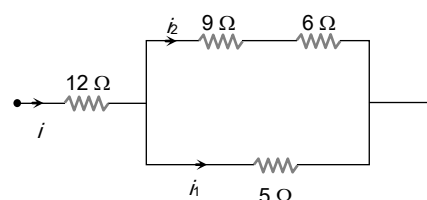43. (b) $\frac{i_1}{i_2} = \frac{15}{5} = \frac{3}{1}$... (i)



$$\text{Also } \frac{H}{t} = i^2 R \Rightarrow 45 = (i_1)^2 \times 5$$

$$\Rightarrow i_1 = 3 \text{ A and from equation (i) } i_2 = 1 \text{ A}$$

$$\text{So } i = i_1 + i_2 = 4 \text{ A}$$

Hence power developed in 12Ω resistance

$$P = i^2 R = (4)^2 \times 12 = 192 \text{ W}$$

44. (a) Heat gained by water = Heat supplied by container - heat lost $\Rightarrow mS\Delta\theta = 1000t - 160t$

$$\Rightarrow t = \frac{2 \times 4.2 \times 1000 \times 50}{840} = 8 \text{ min } 20 \text{ sec}$$

45. (c) As the voltage in R_2 and R_3 is same therefore, according to,


$$H = \frac{V^2}{R} \cdot t, \quad R_2 = R_3$$

Also the energy in all resistance is same.

$$\therefore i^2 R_1 t = i_1^2 R_2 t$$

$$\text{Using } i_1 = \frac{R_3}{R_2 + R_3} i = \frac{R_3}{R_3 + R_3} i = \frac{1}{2} i$$
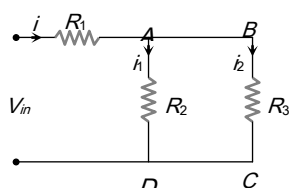
$$\text{Thus } i^2 R_1 t = \frac{i^2}{4} R_2 t \text{ or, } R_1 = \frac{R_2}{4}$$



Graphical Questions

- (b) Area = $it = 2 \text{ Coulomb}$ and $m = zit \Rightarrow z = \frac{m}{it} = \frac{m}{2}$
- (d) $U \propto i^2$, hence the graph between U and i is parabolic in nature and should be above graph (b).
- (d) $E = \alpha t + \frac{1}{2} \beta t^2$, graph between E and t will be a parabola, such that first emf increases and then decreases.
- (a) Thermo electric power $P = \frac{dE}{d\theta} = \alpha + \beta\theta$
Comparing it with $y = mx + c$, option (a) is correct.
- (b) The filament of the heater reaches its steady resistance when the heater reaches its steady

temperature, which is much higher than the room temperature. The resistance at room temperature is thus much lower than the resistance at its steady state. When the heater is switched on, it draws a larger current than its steady state current. As the filament heats up, its resistance increases and current falls to steady state value.

6. (a) Cu voltameter with soluble electrodes obeys ohms law. In water voltameter, in the beginning when V is small ($< 1.7 \text{ volt}$), very little current flows, the voltameter does not obey ohms law. As soon as V exceeds 1.7 volt (back e.m.f.) the current increases steadily according to ohms law.

7. (d) Thermal energy in resistor is $U = i^2 R t$

$$\text{where } R = R_0(1 + \alpha t) \Rightarrow U = i^2 R_0(1 + \alpha t)t = i^2 R_0 t + i^2 R_0 \alpha t^2$$

$$\text{So } \frac{dU}{dt} = i^2 R_0(1 + \alpha t)$$

With the time temperature increases, hence dU/dt increases. This is best shown by curve (d).

8. (b) $m = Zit$ and it = Area of given curve

$$= \text{Area of triangle} + \text{Area of rectangle}$$

$$\Rightarrow it = \frac{1}{2} \times (2 \times 60) \times 1 + (6 - 2) \times 60 \times 1 = 300$$

$$\therefore Z = \frac{m}{it} = \frac{m}{300}$$

9. (d) Terminal voltage $V = E - Ir$. Hence the graph between V and i will be a straight line having negative slope and positive intercept.

Thermal power generated in the external circuit

$$P = EI - I^2 r. \text{ Hence graph between } P \text{ and } I \text{ will be a parabola passing through origin.}$$

Also at an instant, thermal power generated in the cell = $i^2 r$ and total electrical power generated in the

$$\text{cell} = Ei. \text{ Hence the fraction } \eta = \frac{I^2 r}{EI} = \left(\frac{r}{E}\right) I; \text{ so}$$

$\eta \propto I$. It means graph between η and I will be a straight line passing through origin.

Assertion and Reason

1. (a) The possibility of an electric bulb fusing is higher at the time of switching ON and switching OFF because inductive effect produces a surge at the time of switching ON and OFF.
2. (a) The resistance, $R = \frac{V^2}{P} \Rightarrow R \propto 1/P$



i.e., higher is the wattage of a bulb, lesser is the resistance and so it will glow bright.
3. (c) Assertion is true but reason is false. Fuse wire must have high resistance because in series current remains same, therefore according to Joule's law $H = \frac{i^2 R t}{4.2}$, heat produced is high if R is high. The melting point must be low so that wire may melt with increase in temperature. As the current equal to maximum safe value, flows through the fuse wire, it heats up, melts and break the circuit.
4. (a) Resistance of 50 W bulb is two times the resistance of 100 W bulb. When bulbs are connected in series, 50 W bulb will glow more as $P = i^2 R$ (current remains same in series). In parallel the 100 W bulb will glow more as $P = V^2 / R$ (potential difference remain same in parallel).
5. (d) When two bulbs are connected in series, the resistance of the circuit increases and so the voltage in each decreases, hence the brightness and the temperature also decreases. Due to decrease in temperature, the resistance of the carbon filament will slightly increase while that of metal filament will decrease. Hence, carbon filament bulb will glow more brightly ($P = i^2 R$). Also carbon is not a semiconductor.
6. (e) Voltage of dc source is constant but in ac, peak value of voltage is $\sqrt{2}$ times the *rms.* voltage. Hence bulb will glow with more brightness when connected to an ac source of the same voltage.
7. (a) When cold water is poured on half portion of the wire, its resistance decreases due to decrease in temperature. As a result of this total resistance of circuit decreases i.e. current through each portion of wire increases i.e. rest of the half portion becomes still more hot.
8. (a) As filament of bulb and line wire are in series, hence current through both is same. Now, because $H = \frac{i^2 R t}{4.2}$ and resistance of the filament of the bulb is much higher than that of line wires, hence heat produced in the filament is much higher than that in line wires.
9. (b) Neutral temperature is the temperature of hot junction, at which the thermo e.m.f. produced in the thermocouple becomes maximum. It is independent of cold junction and depends on the nature of materials of two metals used to form thermocouple.
10. (d) Because of heat production every resistance has a maximum power rating, the maximum power that can be dissipated without overheating the device. When this rating is exceeded, heat is produced, due to which resistance may change unpredictably.
11. (a) The e.m.f. of a Leclanche cell falls, because of the partial polarisation due to accumulation of hydrogen gas. In case, Leclanche cell is used in experiment, where current is drawn after short breaks, then during each break, hydrogen gas escapes and

Mn_2O_3 converts into MnO_2 by taking oxygen from the atmosphere. As a result, the cell regains its original e.m.f.

12. (a) When lamp B or C gets fused equivalent resistance of B and C increases. In series voltage distributes in the ratio of resistance, so voltage appears across B increases or in other words voltage across A decreases.
13. (d) When switch S is closed, bulb C is short circuited, so voltage V distributes only in two parts *i.e.* voltage on Bulb A and B increases as compared previously. Hence illumination of Bulb A and B increases.
14. (a)
15. (c) The electrical appliances with metallic body like heater, press *etc.* have three pin connections. Two pins are for supply line and third pin is for earth connection for safety purposes.
16. (c) A laser beam is a beam of light which is light amplification by stimulated emission of radiation.
- The energy per unit area of the laser beam is very high as compared to the torch light.
17. (a) Follow hint of question 15 of this section.
18. (c) Thomson e.m.f. in lead is practically zero.
19. (b) The presence of water molecules reduces force between ions by $1/81$ times because the value of dielectric constant of water is 81. That is why the separation between ions becomes easier.
20. (b) Here reason is not the correct explanation of the assertion, which is correct.
21. (d) Here assertion and reason are not correct.

Heating and Chemical Effect of Current

SET Self Evaluation Test -20

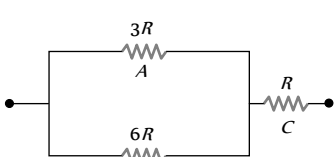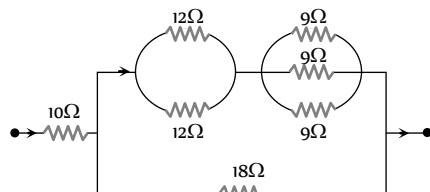- An electric kettle has two coils. When one of these is switched on, the water in the kettle boils in 6 minutes. When the other coil is switched on, the water boils in 3 minutes. If the two coils are connected in series, the time taken to boil the water in the kettle is
 - 3 minutes
 - 6 minutes
 - 2 minutes
 - 9 minutes
- A 3° rise in temperature is observed in a conductor by passing a certain current. When the current is doubled, the rise in temperature will be
 - 15°C
 - 12°C
 - 9°C
 - 3°C
- Two identical electric lamps marked 500 W, 220 V are connected in series and then joined to a 110 V line. The power consumed by each lamp is
 - $\frac{125}{4} \text{ W}$
 - $\frac{25}{4} \text{ W}$
 - $\frac{225}{4} \text{ W}$
 - 125 W
- When 1 gm hydrogen (e.c.e. = $1.044 \times 10^{-8} \text{ kg/C}$) forms water, 34 kcal heat is liberated. The minimum voltage required to decompose water is
 - 0.75 V
 - 3 V
 - 1.5 V
 - 4.5 V
- In how much time, one litre of H_2 will be collected by 5 A current ? (If $Z = 1 \times 10^{-8} \text{ kg/C}$ and density of $\text{H}_2 = 0.09 \text{ kg/m}^3$)
 - 30 minutes
 - 15 minutes
 - 45 minutes
 - 60 minutes
- The three resistances A, B and C have values $3R$, $6R$ and R respectively. When some potential difference is applied across the network, the thermal powers dissipated by A, B and C are in the ratio
 - 2 : 3 : 4
 - 2 : 4 : 3
 - 4 : 2 : 3
 - 3 : 2 : 4
- If the length of the filament of a heater is reduced by 10%, the power of the heater will
 - Increase by about 9%
 - Increase by about 11%
 - Increase by about 19%
 - Decrease by about 10%
- A thermo couple develops $40 \mu\text{V/kelvin}$. If hot and cold junctions be at 40°C and 20°C respectively then the emf develops by a thermopile using such 150 thermo couples in series shall be
 - 150mV
 - 80mV
 - 144mV
 - 120mV
- Amount of electricity required to pass through the H_2O voltmeter so as to liberate 11.2 litre of hydrogen will be
 - 1 Faraday
 - $\frac{1}{2}$ Faraday
 - 2 Faraday
 - 3 Faraday
- The resistance of the filament of a lamp increases with the increase in temperature. A lamp rated 100 W, 220 V is connected across 220 V power supply. If the voltage drops by 10% then the power of lamp will be
 - 90 W
 - 81 W
 - Between 90 W and 100 W
 - Between 81 W and 90 W
- In the following circuit, 18Ω resistor develops 2 J/sec due to current flowing through it. The power developed across 10Ω resistance is
 - 125 W
 - 10 W
 - $\frac{4}{5} \text{ W}$
 - 25 W
- If resistance of the filament increases with temperature, what will be power dissipated in a 220 V- 100 W lamp when connected to 110 V power supply
 - 25 W
 - < 25 W
 - > 25 W
 - None of these
- Total surface area of a cathode is 0.05m^2 and 1 A current passes through it for 1 hour. Thickness of nickle deposited on the cathode is (Given that density of nickle = 9gm/cc and it's E.C.E. = $3.04 \times 10^{-4} \text{ gm/C}$)
 - 2.4 m
 - $2.4 \mu\text{m}$
 - $2.4 \mu\text{m}$
 - None of these
- Two bulbs consume same power when operated at 200 V and 300 V respectively. When these bulbs are connected in series across a D.C. source of 500 V, then
 - Ratio of potential difference across them is 3/2
 - Ratio of potential difference across them is 9/4
 - Ratio of power consumed across them is 4/9
 - Ratio of power consumed across them is 2/3

1172 Heating and Chemical Effect of Current


1. (d) In series $\frac{1}{P_s} = \frac{1}{P_1} + \frac{1}{P_2} \Rightarrow \frac{1}{(H_s/t_s)} = \frac{1}{(H_1/t_1)} + \frac{1}{(H_2/t_2)}$
 $\therefore H_s = H_1 = H_2$ So $t_s = t_1 + t_2 = 6 + 3 = 9 \text{ min}$

2. (b) $i^2 R t = C \theta = 3C$; C = Thermal capacity
 when $i_1 = 2i \Rightarrow C \theta_1 = 4i^2 R t = 4 \times 3C \Rightarrow \theta_1 = 12^\circ \text{C}$

3. (a) Voltage across each bulb $V' = \frac{110}{2} = 55 \text{ V}$ so, power consumed by each bulb will be

$$P' = \left(\frac{55}{220} \right)^2 \times 500$$

$$= \frac{125}{4} \text{ W}$$

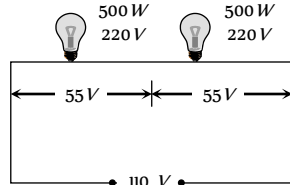

4. (c) $m = Zit \Rightarrow it = \frac{m}{Z} = \frac{1 \times 10^{-3}}{1.044 \times 10^{-8}} \text{ C} = \frac{10^5}{1.044} \text{ C}$

Given $H = 34 \text{ kcal} = 4.2 \times 34 \times 10^3 \text{ J}$

\Rightarrow Heat generated $H = Vit = V \cdot \frac{10^5}{1.044}$

$\Rightarrow V = \frac{4.2 \times 34 \times 1.044}{10^2} = 4.2 \times 0.34 \times 1.044 = 1.5 \text{ V}$

5. (a) $m = zit \Rightarrow 10^{-3} \times 0.09 = 1 \times 10^{-8} \times 5 \times t \Rightarrow t = 30 \text{ min}$

6. (c) Thermal power in $A = P_A = \left(\frac{2i}{3} \right)^2 3R = \frac{4}{3} i^2 R$


Thermal power in $B = P_B = \left(\frac{i}{3} \right)^2 6R = \frac{2}{3} i^2 R$

Thermal power in

$C = P_C = i^2 R$

$\Rightarrow P_A : P_B : P_C$

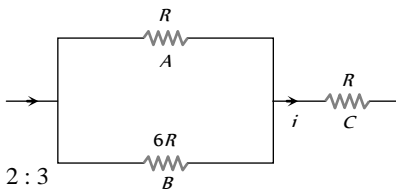$= \frac{4}{3} : \frac{2}{3} : 1 = 4 : 2 : 3$



7. (b) $P \propto \frac{1}{R}$ and $R \propto l \Rightarrow P \propto \frac{1}{l}$

$\Rightarrow \frac{P_1}{P_2} = \frac{l_2}{l_1} \Rightarrow \frac{P_1}{P_2} = \frac{(100-10)}{100} = \frac{90}{100} \Rightarrow P_2 = 1.11 P_1$

% change in power = $\frac{P_2 - P_1}{P_1} \times 100 = 11\%$

8. (d) The temperature difference is $20^\circ \text{C} = 20 \text{ K}$. So that thermo emf developed $E = \alpha \theta = 40 \frac{\mu \text{V}}{\text{K}} \times 20 \text{ K} = 800 \mu \text{V}$

Hence total emf = $150 \times 800 = 12 \times 10^4 \mu \text{V} = 120 \text{ mV}$

9. (a) 22.4 litre H_2 = 1 mole of H_2 = N molecules of H_2
 = $2N$ atoms of H .

So charge required to liberate 22.4 litre of H_2 = $2Ne = 2F$.

Hence charge required to liberate 11.2 litre of H_2 = F .

10. (d) Let the resistance of the lamp filament be R . Then $100 = \frac{(220)^2}{R}$. When the voltage drops, expected power is

$P = \frac{(220 \times 0.9)^2}{R'}$. Here R' will be less than R , because now the rise in temperature will be less. Therefore P is more than $\frac{(220 \times 0.9)^2}{R} = 81 \text{ W}$


But it will not be 90% of earlier value, because fall in temperature is small. Hence (d) is correct.

11. (b) The given circuit can be redrawn as follows

$\frac{i_1}{i_2} = \frac{9}{18} = \frac{1}{2}$

and $i = i_1 + i_2$

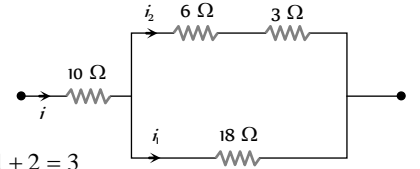$\Rightarrow \frac{i}{i_1} = 1 + \frac{i_2}{i_1} = 1 + 2 = 3$



From $P = i^2 R \Rightarrow \frac{P_{10\Omega}}{P_{18\Omega}} = \left(\frac{i}{i_1} \right)^2 \times \frac{10}{18} \Rightarrow P_{10\Omega} = 10 \text{ W}$

12. (c) If resistance does not vary with temperature P consumed = $\left(\frac{V_A}{V_R} \right)^2 \times P_R = \left(\frac{110}{220} \right)^2 \times 100 = 25 \text{ W}$. But in second cases resistance decreases so consumed power will be more than 25 W

13. (c) Mass deposited = density \times volume of the metal

$m = \rho \times A \times X$ (i)

Hence from Faraday's first law $m = Zit$ (ii)

So from equation (i) and (ii)

$Zit = \rho \times Ax \Rightarrow x = \frac{Zit}{\rho A}$

$= \frac{3.04 \times 10^{-4} \times 10^{-3} \times 1 \times 3600}{9000 \times 0.05} = 2.4 \times 10^{-6} \text{ m} = 2.4 \mu \text{m}$

14. (c) $P = \frac{V^2}{R} \therefore R = \frac{V^2}{P}$ or $R \propto V^2$ i.e. $\frac{R_1}{R_2} = \left(\frac{200}{300} \right)^2 = \frac{4}{9}$

When connected in series potential drop and power consumed

are in the ratio of their resistances. So, $\frac{P_1}{P_2} = \frac{V_1}{V_2} = \frac{R_1}{R_2} = \frac{4}{9}$