

# CHAPTER

# 1.1

## BASIC CONCEPTS

1. A solid copper sphere, 10 cm in diameter is deprived of  $10^{20}$  electrons by a charging scheme. The charge on the sphere is

- (A) 160.2 C                      (B) -160.2 C  
(C) 16.02 C                      (D) -16.02 C

2. A lightning bolt carrying 15,000 A lasts for 100  $\mu$ s. If the lightning strikes an airplane flying at 2 km, the charge deposited on the plane is

- (A) 13.33  $\mu$ C                      (B) 75 C  
(C) 1500  $\mu$ C                      (D) 1.5 C

3. If 120 C of charge passes through an electric conductor in 60 sec, the current in the conductor is

- (A) 0.5 A                      (B) 2 A  
(C) 3.33 mA                      (D) 0.3 mA

4. The energy required to move 120 coulomb through 3 V is

- (A) 25 mJ                      (B) 360 J  
(C) 40 J                      (D) 2.78 mJ

5.  $i = ?$

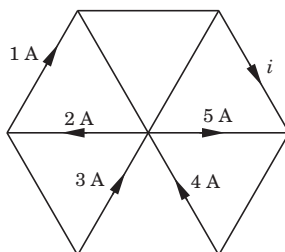


Fig. P.1.1.5

- (A) 1 A                      (B) 2 A  
(C) 3 A                      (D) 4 A

6. In the circuit of fig P1.1.6 a charge of 600 C is delivered to the 100 V source in a 1 minute. The value of  $v_1$  must be

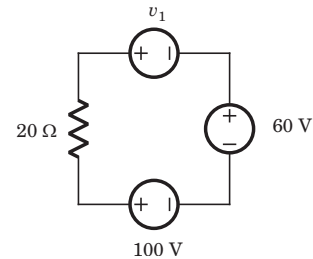


Fig. P.1.1.6

- (A) 240 V                      (B) 120 V  
(C) 60 V                      (D) 30 V

7. In the circuit of the fig P1.1.7, the value of the voltage source  $E$  is

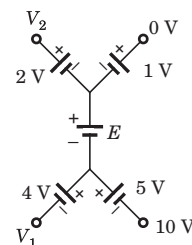


Fig. P.1.1.7

- (A) -16 V                      (b) 4 V  
(C) -6 V                      (D) 16 V

8. Consider the circuit graph shown in fig. P.1.1.8. Each branch of circuit graph represent a circuit element. The value of voltage  $v_1$  is

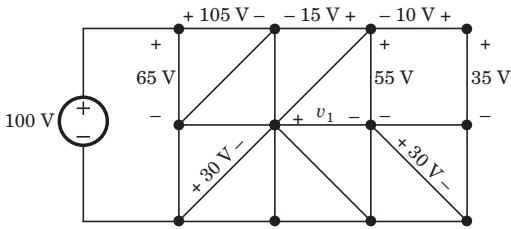


Fig. P.1.1.8

- (A) -30 V (B) 25 V  
(C) -20 V (D) 15 V

9. For the circuit shown in fig P.1.1.9 the value of voltage  $v_o$  is

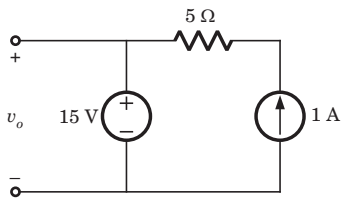


Fig. P.1.1.9

- (A) 10 V (B) 15 V  
(C) 20 V (D) None of the above

10.  $R_1 = ?$

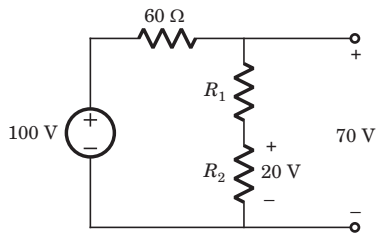


Fig. P.1.1.10

- (A) 25  $\Omega$  (B) 50  $\Omega$   
(C) 100  $\Omega$  (D) 2000  $\Omega$

11. Twelve  $6 \Omega$  resistor are used as edge to form a cube. The resistance between two diagonally opposite corner of the cube is

- (A)  $\frac{5}{6} \Omega$  (B)  $\frac{6}{5} \Omega$   
(C) 5  $\Omega$  (D) 6  $\Omega$

12.  $v_1 = ?$

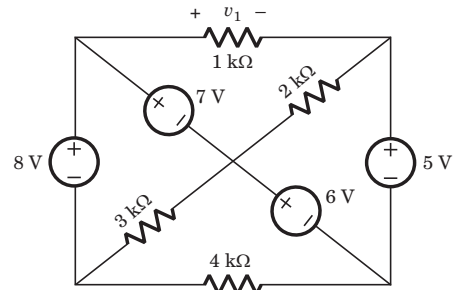


Fig. P.1.1.12

- (A) -11 V (B) 5 V  
(C) 8 V (D) 18 V

13. The voltage  $v_o$  in fig. P.1.1.11 is always equal to

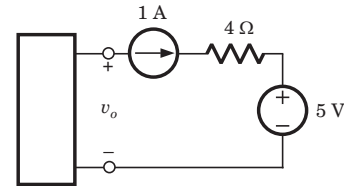


Fig. P.1.1.11

- (A) 1 V (B) 5 V  
(C) 9 V (D) None of the above

14.  $R_{eq} = ?$

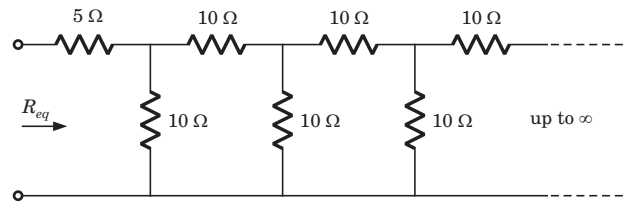


Fig. P.1.1.14

- (A) 11.86  $\Omega$  (B) 10  $\Omega$   
(C) 25  $\Omega$  (D) 11.18  $\Omega$

15.  $v_s = ?$

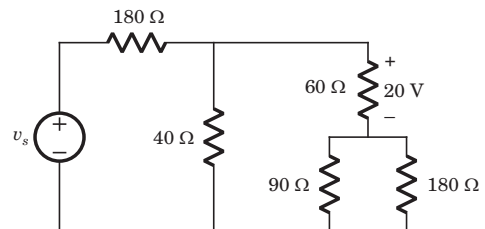


Fig. P.1.1.15

- (A) 320 V (B) 280 V  
(C) 240 V (D) 200 V

24. Let  $i(t) = 3te^{-100t}$  A and  $v(t) = 0.6(0.01 - t)e^{-100t}$  V for the network of fig. P.1.1.24. The power being absorbed by the network element at  $t = 5$  ms is

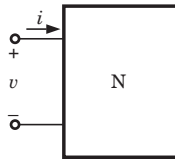


Fig. P.1.1.24

- (A) 18.4  $\mu$ W (B) 9.2  $\mu$ W  
(C) 16.6  $\mu$ W (D) 8.3  $\mu$ W

25. In the circuit of fig. P.1.1.25 bulb A uses 36 W when lit, bulb B uses 24 W when lit, and bulb C uses 14.4 W when lit. The additional A bulbs in parallel to this circuit, that would be required to blow the fuse is

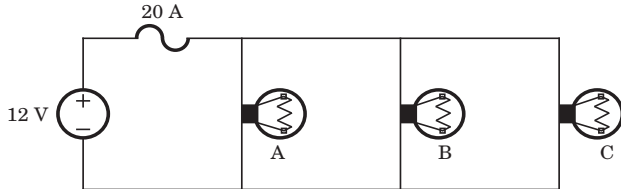


Fig. P.1.1.25

- (A) 4 (B) 5  
(C) 6 (D) 7

26. In the circuit of fig. P.1.1.26, the power absorbed by the load  $R_L$  is

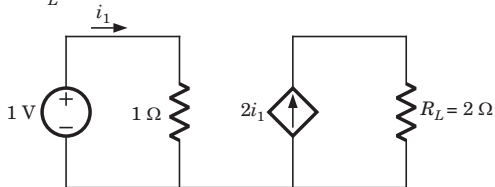


Fig. P.1.1.26

- (A) 2 W (B) 4 W  
(C) 6 W (D) 8 W

27.  $v_o = ?$

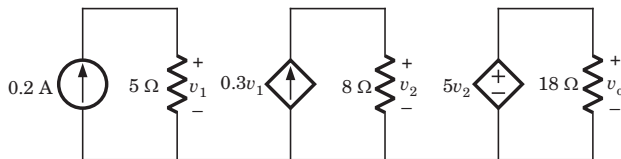


Fig. P.1.1.27

- (A) 6 V (B) -6 V  
(C) -12 V (D) 12 V

28.  $v_{ab} = ?$

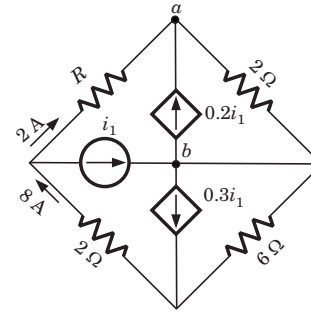


Fig. P.1.1.28

- (A) 15.4 V (B) 2.6 V  
(C) -2.6 V (D) 15.4 V

29. In the circuit of fig. P.1.1.29 power is delivered by

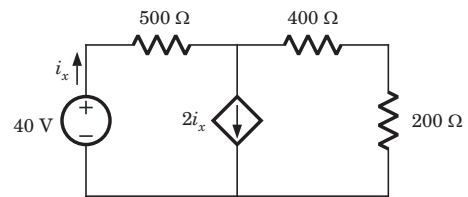


Fig. P.1.1.29

- (A) dependent source of 192 W  
(B) dependent source of 368 W  
(C) independent source of 16 W  
(D) independent source of 40 W

30. The dependent source in fig. P.1.1.30

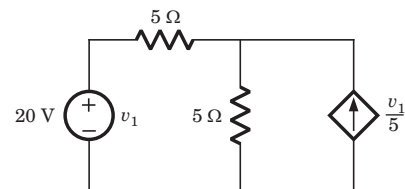


Fig. P.1.1.30

- (A) delivers 80 W (B) delivers 40 W  
(C) absorbs 40 W (D) absorbs 80 W

31. In the circuit of fig. P.1.1.31 dependent source

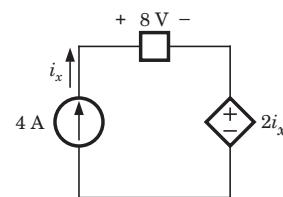


Fig. P.1.1.31

- (A) supplies 16 W (B) absorbs 16 W  
(C) supplies 32 W (D) absorbs 32 W

32. A capacitor is charged by a constant current of 2 mA and results in a voltage increase of 12 V in a 10 sec interval. The value of capacitance is

- (A) 0.75 mF (B) 1.33 mF  
(C) 0.6 mF (D) 1.67 mF

33. The energy required to charge a 10  $\mu\text{F}$  capacitor to 100 V is

- (A) 0.10 J (B) 0.05 J  
(C)  $5 \times 10^{-9}$  J (D)  $10 \times 10^{-9}$  J

34. The current in a 100  $\mu\text{F}$  capacitor is shown in fig. P.1.1.34. If capacitor is initially uncharged, then the waveform for the voltage across it is


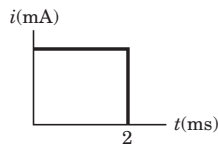


Fig. P. 1.1.34

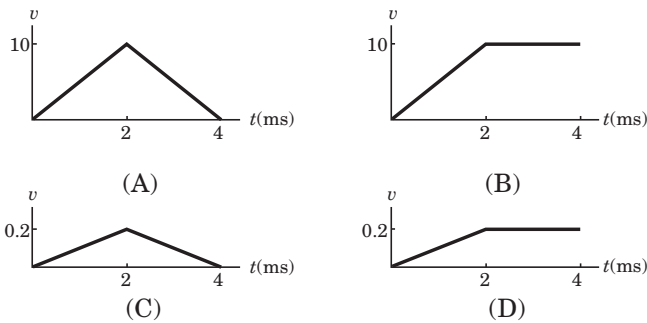

35. The voltage across a 100  $\mu\text{F}$  capacitor is shown in fig. P.1.1.35. The waveform for the current in the capacitor is


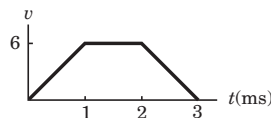


Fig. P.1.1.35

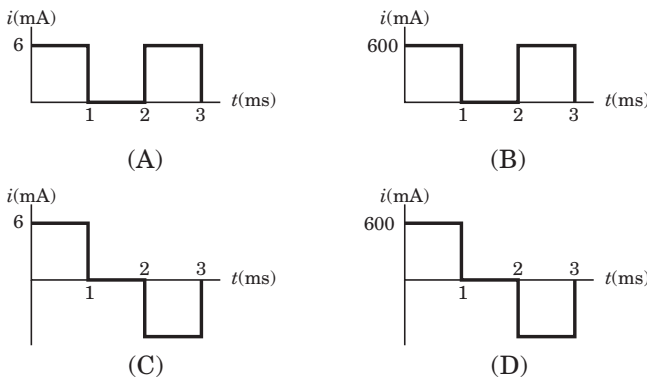

36. The waveform for the current in a 200  $\mu\text{F}$  capacitor is shown in fig. P.1.1.36. The waveform for the capacitor voltage is


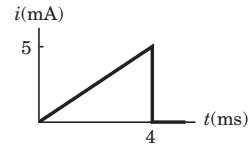


Fig. P. 1.1.36

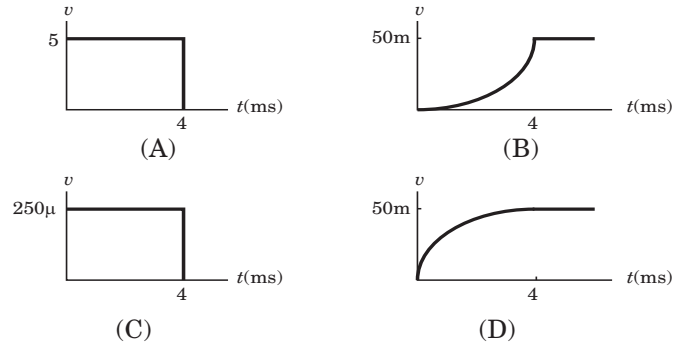

37.  $C_{eq} = ?$

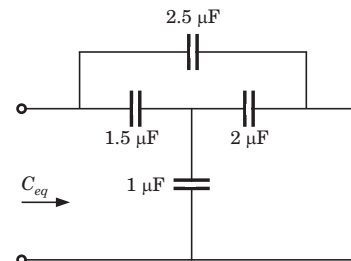


Fig. P.1.1.37

- (A) 3.5  $\mu\text{F}$  (B) 1.2  $\mu\text{F}$   
(C) 2.4  $\mu\text{F}$  (D) 2.6  $\mu\text{F}$

38. In the circuit shown in fig. P.1.1.38

$$i_{in}(t) = 300 \sin 20t \text{ mA, for } t \geq 0.$$

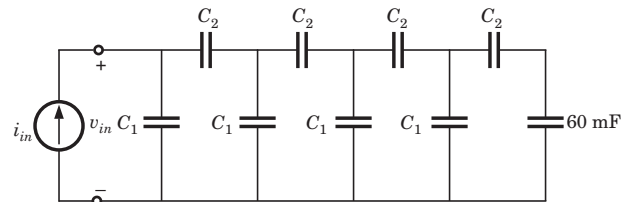


Fig. P. 1.1.38

- Let  $C_1 = 40 \mu\text{F}$  and  $C_2 = 30 \mu\text{F}$ . All capacitors are initially uncharged. The  $v_{in}(t)$  would be  
(A)  $-0.25 \cos 20t \text{ V}$  (B)  $0.25 \cos 20t \text{ V}$   
(C)  $-36 \cos 20t \text{ mV}$  (D)  $36 \cos 20t \text{ mV}$

# SOLUTIONS

1. (C)  $n = 10^{20}$ ,  $Q = ne = e10^{20} = 16.02 \text{ C}$

Charge on sphere will be positive.

2. (D)  $\Delta Q = i \times \Delta t = 15000 \times 100\mu = 1.5 \text{ C}$

3. (B)  $i = \frac{dQ}{dt} = \frac{120}{60} = 2 \text{ A}$

4. (B)  $W = Qv = 360 \text{ J}$

6. (A)

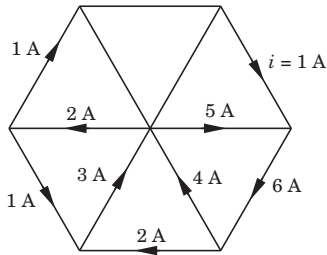


Fig. S 1.1.5

6. (A) In order for 600 C charge to be delivered to the 100 V source, the current must be anticlockwise.

$$i = \frac{dQ}{dt} = \frac{600}{60} = 10 \text{ A}$$

Applying KVL we get

$$v_1 + 60 - 100 = 10 \times 20 \text{ or } v_1 = 240 \text{ V}$$

7. (A) Going from 10 V to 0 V

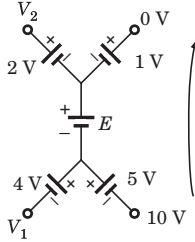


Fig. S 1.1.7

$$10 + 5 + E + 1 = 0 \text{ or } E = -16 \text{ V}$$

8. (D)  $100 = 65 + v_2 \Rightarrow v_2 = 35 \text{ V}$

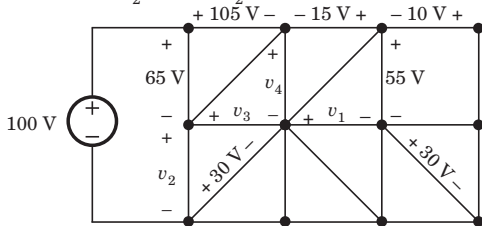


Fig. S 1.1.8

$$v_3 - 30 = v_2 \Rightarrow v_3 = 65 \text{ V}$$

$$105 + v_4 - v_3 - 65 = 0 \Rightarrow v_4 = 25 \text{ V}$$

$$v_4 + 15 - 55 + v_1 = 0 \Rightarrow v_1 = 15 \text{ V}$$

9. (B) Voltage is constant because of 15 V source.

10. (C) Voltage across 60  $\Omega$  resistor = 30 V

$$\text{Current} = \frac{30}{60} = 0.5 \text{ A}$$

Voltage across  $R_1$  is  $= 70 - 20 = 50 \text{ V}$

$$R_1 = \frac{50}{0.5} = 100 \Omega$$

11. (C) The current  $i$  will be distributed in the cube branches symmetrically

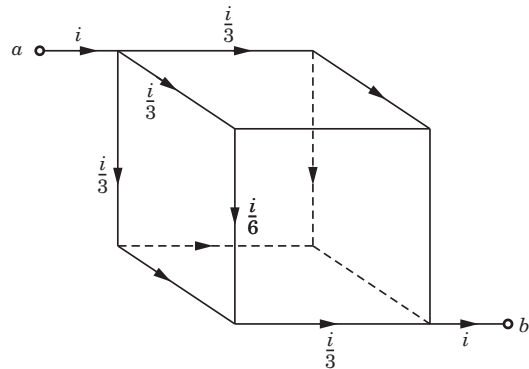


Fig. S 1.1.11

$$v_{ab} = \frac{6i}{3} + \frac{6i}{6} + \frac{6i}{3} = 5i,$$

$$R_{eq} = \frac{v_{ab}}{i} = 5 \Omega$$

12. (C) If we go from +side of 1 k $\Omega$  through 7 V, 6 V and 5 V, we get  $v_1 = 7 + 6 - 5 = 8 \text{ V}$

13. (D) It is not possible to determine the voltage across 1 A source.

14. (D)  $R_{eq} = 5 + \frac{10(R_{eq} + 5)}{10 + 5 + R_{eq}}$

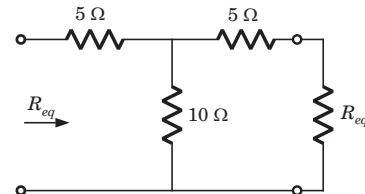


Fig. S 1.1.14

$$\Rightarrow R_{eq}^2 + 15R_{eq} = 5R_{eq} + 75 + 10R_{eq} + 50$$

$$\Rightarrow R_{eq} = \sqrt{125} = 11.18 \Omega$$

$$\frac{v_o - 20}{5} + \frac{v_o}{5} = \frac{20}{5} \Rightarrow v_o = 20 \text{ V}$$

$$\text{Power is } P = v_o \times \frac{v_o}{5} = 20 \times \frac{20}{5} = 80 \text{ W}$$

31. (D) Power  $P = vi = 2i_x \times i_x = 2i_x^2$   
 $i_x = 4 \text{ A}$ ,  $P = 32 \text{ W}$  (absorb)

32. (D)  $v_{i2} - v_{i1} = \frac{1}{C} \int_{t_1}^{t_2} i dt \Rightarrow 12 = \frac{1}{C} 2m(t_2 - t_1)$   
 $\Rightarrow 12C = 2m \times 10 \Rightarrow C = 1.67 \text{ mF}$

33. (B)  $E = \frac{1}{2} C v^2 = 5 \times 10^{-6} \times 100^2 = 0.05 \text{ J}$

34. (D)  $v_c = \frac{1}{C} \int_0^{2m} i dt = \frac{10 \times 10^{-3}}{100 \times 10^{-6}} (2 \times 10^{-3}) = 0.2 \text{ V}$

This 0.2 V increases linearly from 0 to 0.2 V. Then current is zero. So capacitor hold this voltage.

35. (D)  $i = C \frac{dv}{dt}$

For  $0 < t < 1$ ,  $C \frac{dv}{dt} = 100 \times 10^{-6} \times \frac{6-0}{10^{-3}-0} = 600 \text{ mA}$

For  $1 \text{ ms} < t < 2 \text{ ms}$ ,

$$C \frac{dv}{dt} = 100 \times 10^{-6} \times \frac{0-6}{(3-2)m} = -600 \text{ mA}$$

36. (B) For  $0 \leq t \leq 4$ ,

$$v_c = \frac{1}{C} \int i dt = \frac{1}{200 \times 10^{-6}} \int \frac{5m}{4m} t dt = 3125 t^2$$

At  $t = 4 \text{ ms}$ ,  $v_c = 0.05 \text{ V}$

It will be parabolic path. at  $t = 0$   $t$ -axis will be tangent.

37. (A)  $2 \mu\text{F}$  is in parallel with  $1 \mu\text{F}$  and this combination is in series with  $1.5 \mu\text{F}$ .

$$C_1 = \frac{1.5(2+1)}{1.5+2+1} = 1 \mu\text{F}, C_1 \text{ is in parallel with } 2.5 \mu\text{F}$$

$$C_{eq} = 1 + 2.5 = 3.5 \mu\text{F}$$

38. (A)  $C_a = \frac{30 \times 60}{30 + 60} = 20 \text{ mF}$ ,  $C_b = \frac{30(20 + 40)}{30 + 20 + 0} = 20 \text{ mF}$

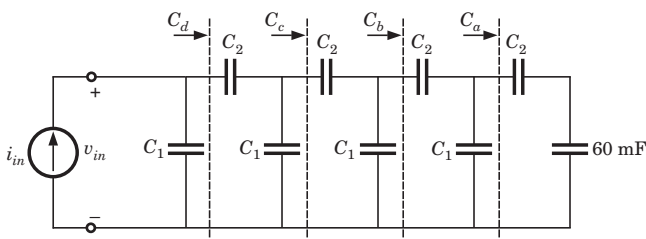


Fig. S 1.1.38

We can say  $C_d = 20 \text{ mF}$ ,  $C_{eq} = 20 + 40 = 60 \text{ mF}$

$$v_c = \frac{1}{C} \int i dt = \frac{1}{60m} \left( -\frac{300}{20} \cos 20t \right) \times 10^{-3} = -0.25 \cos 20t \text{ V}$$

39. (C)  $i_{C1} = \frac{i_{in} C_1}{C_1 + C_2} = 0.8 \sin 600t \text{ mA}$

At  $t = 2 \text{ ms}$ ,  $i_{C1} = 0.75 \text{ mA}$

40. (B)  $v_{C1} = \frac{v_{in} C_2}{C_1 + C_2} = \frac{4v_{in}}{6 + 4} \Rightarrow \frac{v_{C1}}{v_{in}} = 0.4$

41. (D)  $V = 2 + 3 + 5 = 10$ ,  $Q = 1 \text{ C}$ ,  $C = \frac{Q}{V} = 0.1 \text{ F}$

42. (A)  $v_L = L \frac{di}{dt} \Rightarrow 100m = L \frac{200m}{4m} \Rightarrow L = 2 \text{ mH}$

43. (B)  $v_L = L \frac{di}{dt} = 0.01 \times 2(377 \cos 377t) \text{ V}$   
 $= 7.54 \cos 377t \text{ V}$

44. (A)  $i = \frac{1}{L} \int v dt = \frac{1}{0.01} \int 120 \cos 3t dt = \frac{12000}{377} \sin 377t$

$$P = vi = \frac{12000 \times 120}{377} (\sin 377t)(\cos 377t)$$

$$= 1910 \sin 754t \text{ W}$$

45. (D)  $v_L = L \frac{di_L}{dt}$ ,  $i_C = C \frac{dv_C}{dt}$

$$v_C = 3v_L \Rightarrow i_C = 3LC \frac{d^2 i_L}{dt^2} = -9.6 \sin 4t \text{ A}$$

46. (B)  $v_L = L \frac{di_L}{dt}$

For  $2 < t \leq 4$ ,  $v_L = (0.05) \left( \frac{-100 - 0}{2} \right) = -2.5 \text{ V}$

For  $4 < t \leq 8$ ,  $v_L = (0.05) \left( \frac{100 + 100}{4} \right) = 2.5 \text{ V}$

For  $8 < t \leq 10$ ,  $v_L = (0.05) \left( \frac{0 - 100}{2} \right) = -2.5 \text{ V}$

Thus (B) is correct option.

47. (C) Algebraic sum of the current entering or leaving a cutset is equal to 0.

$$i_2 + i_4 + i_3 = 0 \Rightarrow \frac{6}{2} + \frac{16}{4} + i_3 = 0$$

$$i_3 = -7 \text{ A}, \quad v_3 = -7 \times 3 = -21 \text{ V}$$

\*\*\*\*\*