

Introduction

- It is a sequential circuit forming by the cascading of FFs.
- Counter are basically used for
 - (i) Counting of the number of clock pulses applied
 - (ii) Frequency division
 - (iii) Timers
 - (iv) Frequency measurement
 - (v) Waveform generation
- Counters are classified as:
 - (i) Asynchronous counter
 - (ii) Synchronous counter

Remember:

- If N = total number of states and ' n ' = number of FFs then

$$N \leq 2^n$$

$$n \geq 3.32 \log_{10} N \quad \text{or} \quad n \geq \log_2 N$$

- If $N = 2^n$, then we get BINARY COUNTER.
- If $N < 2^n$, then we get NON-BINARY COUNTER.

MOD number

- The "MOD-number" indicates the number of states in counting sequence.
- For n -FFs, counter will have 2^n different states and then this Counter is said to be "MOD- 2^n Counter".
- MOD number indicates the frequency division factor obtained from the Last FF.
- It would be capable of counting upto $(2^n - 1)$ before returning to zero state.

Note:

- ### Asynchronous (Series) Counter

- For proper operation of the ripple counter:*

$$f_{CLK} \leq \frac{1}{n t_{pd}(FF)}$$


$$f_{CLK,m} = \frac{1}{n t_{pd(FF)}}$$

Decoding error is present due to propagation delay of FFs i.e. $t_{pd(FF)}$.

An "Up/Down Counter" can count in any direction depending upon the control input.

Triggering with	CLK connection In	Access as
(-ve) edge	Q	UP Counter
(-ve) edge	\overline{Q}	Down Counter
(+ve) edge	Q	Down Counter
(+ve) edge	\overline{Q}	UP Counter


Decade Counter or Mod-10 Counter

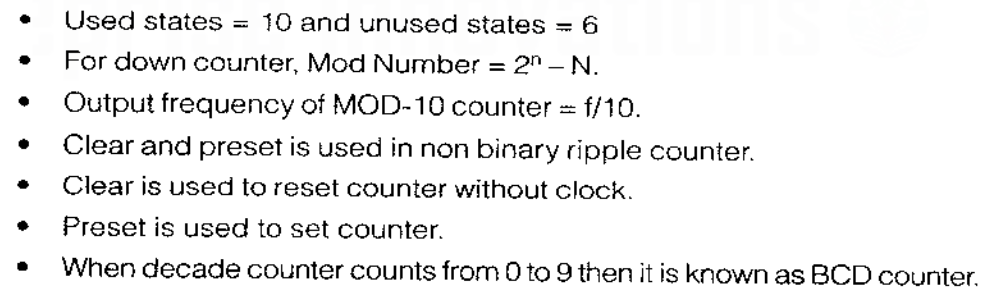

Synchronous (Parallel) Counters

Ring Counter

It is SISO shift register.

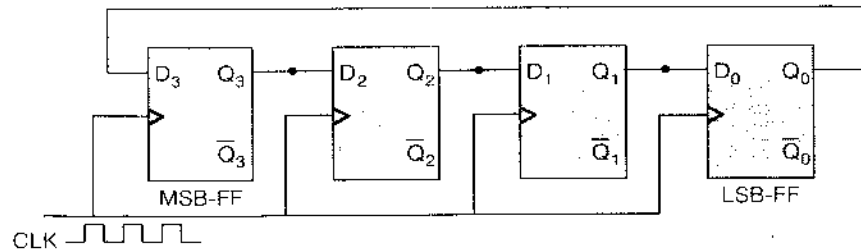

Remember:

- Ring counter is a non-self starting counter.
- With 'n' FFs, there are n-states present in ring counter.
- With 'n' FFs, maximum count possible in ring counter is $(2^n - 1)$.
- Decoding is very easy in Ring counter, because there is no aid of extra circuit.

In a 4-bit ring counter:


Used states = 4

Unused states = $2^4 - 4 = 12$

- In a ring counter if CLK frequency is "f" the FFs output frequency is "f/N" (where N = Number of states = modulus of the counter).

Twisted-Ring Counter

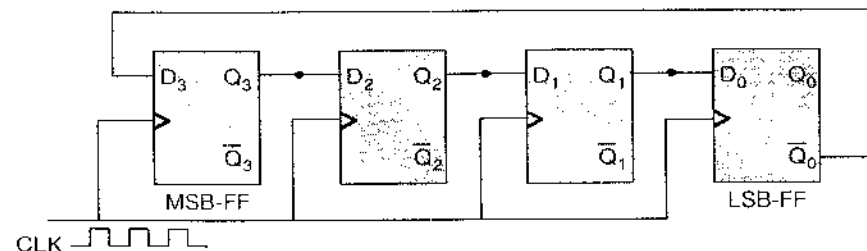
Also known as Johnson Counter or Switch Tail Ring Counter



Remember:

- With 'n' FFs there are '2n' states in this counter.
- With 'n' FFs the maximum count by this counter is $(2^n - 1)$.
- In normal "Johnson Counter" with 'n' FFs and the input frequency is 'f' then output frequency of FFs is "f/2n"
- In a "Counter" if a feedback connection is used the number of possible states will decrease.

Synchronous-Series Carry Counter

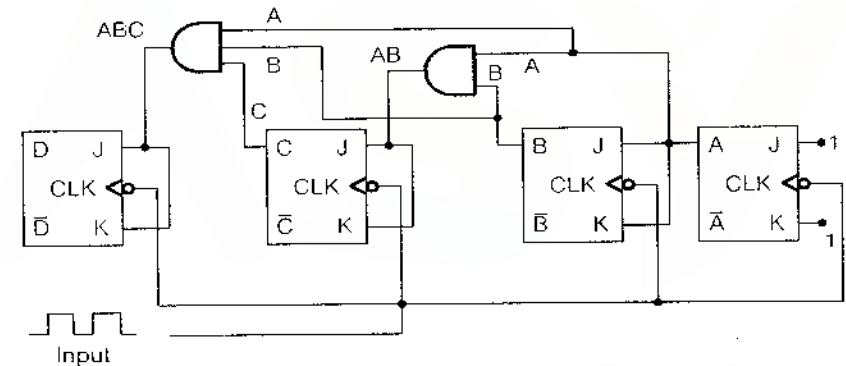

□ Clock frequency

$$f_{CLK} \leq \frac{1}{t_{pd(FF)} + (n-2)t_{pd(AND\text{-}gate)}}$$

Remember:

- Total delay of this counter is much lower than an asynchronous counter with same number of FFs.

$$\text{total delay} = FF t_{pd(FF)} + t_{pd(AND\text{-}gate)}$$

Synchronous-Parallel Carry Counter

It is the "Fastest Counter".

Clock frequency:

$$f_{CLK} = \frac{1}{t_{pd(FF)} + t_{pd(AND\text{-}gate)}}$$