

NETWORKS TEST 2

Number of Questions: 35


Time: 90 min.

Directions for questions 1 to 35: Select the correct alternative from the given choices.

1. Twelve 1H inductors are used as edges to form a cube. The inductors between two diagonally opposite corners of the cube is


(A) $\frac{5}{6}$ H (B) 1H
(C) $\frac{6}{5}$ H (D) $\frac{3}{2}$ H

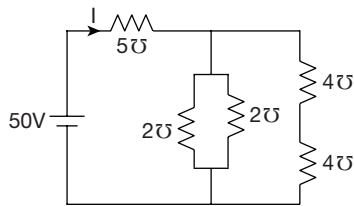2. Determine the current drawn from the battery of the given figure.




(A) 8.49 A (B) 49.8 A
(C) 36 A (D) 136.36 A

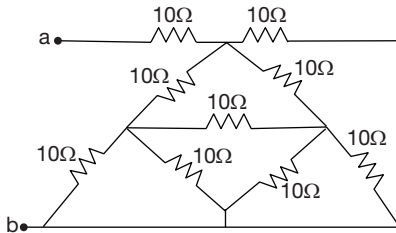3. Find equivalent resistance between a, and b terminals.




(A) 6.3Ω (B) 4.3Ω
(C) 14.3Ω (D) 16.3Ω

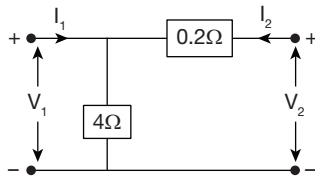4. Find transition matrix of given 2 port network.



(A) $\begin{bmatrix} 1 & 5 \\ 4 & 21 \end{bmatrix}$
(B) $\begin{bmatrix} 1 & 4 \\ 5 & 21 \end{bmatrix}$
(C) $\begin{bmatrix} 1 & 0.2 \\ 0.25 & 1.05 \end{bmatrix}$
(D) Transition matrix does not exist

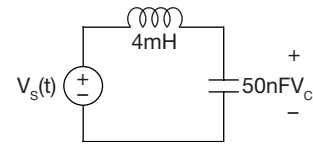5. If $V_c(t) = 5 \sin 10^5 t$ V in below circuit then $V_s(t)$ would be



(A) $5 \sin 10^5 t$ volts (B) $-5 \sin 10^5 t$ volts
(C) zero (D) $-10 \cos 10^5 t$ volts

6. How many number of tie set matrixes are possible for a graph which has N nodes?

(A) $N^{\frac{N}{2}}$ (B) N^{2N}
(C) N^{N-2} (D) N^{N+2}


7. Two set of networks are connected in series and each Network contains N number of Resistors each are having RΩ are connected in parallel then find R – equivalence of Total Network?

(A) $\frac{R}{2n}$ (B) $\frac{2R}{n}$
(C) $\left(\frac{R}{n}\right)^2$ (D) $\sqrt{\frac{R}{n}}$

8. A voltage of $V(t) = 8 \sin 314 t$ volts is applied to an inductance of 4mH. Determine the instantaneous power (p)


(A) zero (B) $-25.48 \sin 628 t$
(C) $-6.37 \cos 314 t$ (D) $-50.96 \cos 314 t$

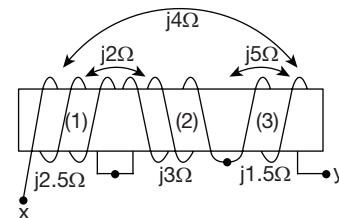9. Find the net inductance of the iron core coupled coils are in series connection.




(A) j7 (B) j1H
(C) j4 (D) j13

10. Find time constant of below circuit

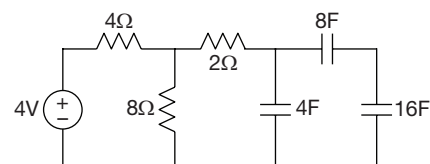


(A) 45.6sec (B) 43.56sec
(C) 53.4sec (D) 54.3sec

11. A series LCR circuit with $R = 20\Omega$, $|X_L| = |X_C| = 40\Omega$ is connected across an AC supply of 200Vrms. The rms voltage across the inductor is
 (A) $200\angle -90^\circ\text{V}$ (B) $200\angle 90^\circ\text{V}$
 (C) $400\angle -90^\circ\text{V}$ (D) $400\angle 90^\circ\text{V}$
12. If half power frequencies are given as 5KHz, 8KHz respectively. Then resonance frequency is
 (A) 13 KHz (B) 3 KHz
 (C) 7 KHz (D) 6.32 KHz
13. Consider the following circuit

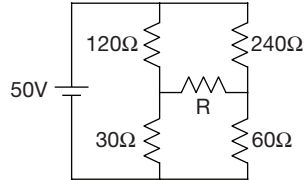


What is the power delivered to resistor R in the above circuit?

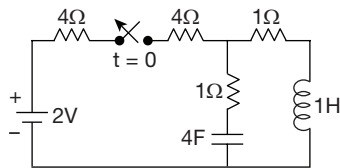- (A) 156 watts (B) -156 W
 (C) zero (D) 82.52 W
14. The conditions, under which a passive two – port network represented by h if parameters is reciprocal and symmetrical,
 (A) $h_{12} = h_{21}$, $h_{11}h_{22} - h_{12}h_{21} = 1$
 (B) $h_{12} = -h_{21}$, $h_{11}h_{22} - h_{12}h_{21} = 1$
 (C) $h_{12} = h_{21}$, $h_{11}h_{22} - h_{12}h_{21} = 1$
 (D) $h_{12} = -h_{21}$, $h_{12}h_{21} - h_{11}h_{22} = 1$
15. In the circuit shown, the switch is opened at $t = 0$. Then the circuit is



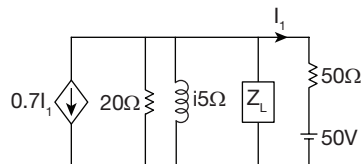- (A) critically damped
 (B) under damped
 (C) over damped
 (D) undamped
- 16.




In the given circuit, the maximum power delivered to Z_L if its value is

- (A) $(0.084 - j0.2)\Omega$ (B) $(0.084 + j0.2)\Omega$
 (C) $(1.785 - j4.25)\Omega$ (D) $(1.785 + j4.25)\Omega$
17. 2 – Two port Networks are connected in series with open circuit impedance parameter matrix is $\begin{bmatrix} 3 & 4 \\ 5 & 2 \end{bmatrix}$

and other two port Network has short circuit admittance parameters matrix $\begin{bmatrix} 5 & 10 \\ 4 & 2 \end{bmatrix}$, then find overall two-port network impedance matrix.


- (A) $\begin{bmatrix} 8 & 14 \\ 8 & 4 \end{bmatrix}$ (B) $\begin{bmatrix} 2 & 6 \\ -1 & 0 \end{bmatrix}$
 (C) $\begin{bmatrix} 37 & 38 \\ 33 & 54 \end{bmatrix}$ (D) $\begin{bmatrix} 2.933 & 4.333 \\ 5.133 & 1.833 \end{bmatrix}$

18. Find current flowing in 5Ω resistor.

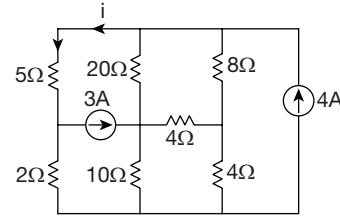


- (A) 3.2A (B) 2.32A
 (C) 1.25A (D) 6.23A

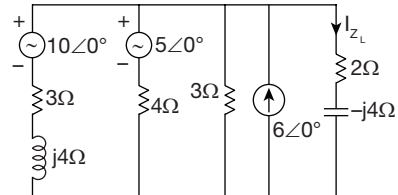19. Find the current in load Z_L in below network.




- (A) $2.43\angle 60^\circ$ (B) $24.3\angle 3^\circ$
 (C) $34.2\angle -30^\circ$ (D) $43.2\angle 60^\circ$

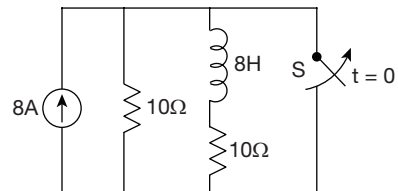20. Find the voltage across inductor ($t > 0$) where switch is opened at $t = 0$.



- (A) $80e^{-\frac{10t}{2}}\text{V}$ (B) $80e^{-\frac{4t}{5}}\text{V}$
 (C) $80e^{-\frac{5t}{2}}\text{V}$ (D) zero

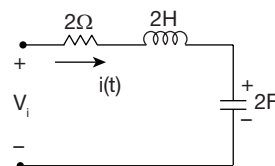
21. The circuit shown below has initial current $i(0^-) = -1\text{A}$ and initial voltage $V_c(0^-) = 1\text{V}$. For unit step response the voltage across the inductor is




- (A) $e^{-0.5t}$ (B) $(2 - 0.5t)e^{-0.5t}$
 (C) $(10 - t)e^{-0.5t}$ (D) $10(2.4 - t)e^{-\frac{1}{2}t}$

3.16 | Networks Test 2

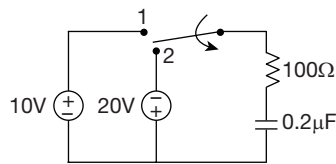
22. Given circuit is attains steady state when the switch at 1. At $t = 0$, the switch is moved to 2. find energy stored across the capacitor at 0.1m sec



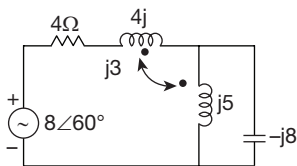
- (A) $89.2\mu\text{J}$ (B) $392\mu\text{J}$
 (C) $19.79\mu\text{J}$ (D) $197\mu\text{J}$
23. Two coupled coils have $K = 0.7$, $N_1 = 400$ turns, $N_2 = 800$ turns and mutual flux being 0.8 wb, if the primary current be 10A, then find the secondary coil inductance
 (A) 45.7 H (B) 183 H
 (C) 137 H (D) 173 H
24. Find the Voltage drop across the capacitor



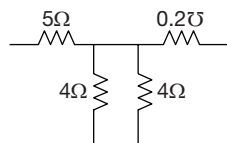- (A) $18\angle -90^\circ$ (B) $42.1\angle 15.95^\circ$
 (C) $42.1\angle -20.5^\circ$ (D) $21.4\angle +90^\circ$
25. Find h parameters for below 2 port network.



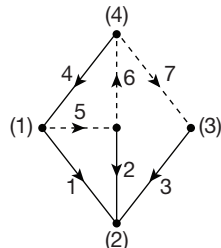
- (A) $\begin{bmatrix} -6.428 & 35 \\ -35 & 0.142 \end{bmatrix}$ (B) $\begin{bmatrix} 4.8 & 0.285 \\ 1.4 & 0.142 \end{bmatrix}$
 (C) $\begin{bmatrix} 4.8 & 1.4 \\ 0.285 & 0.2 \end{bmatrix}$ (D) $\begin{bmatrix} 6.428 & 0.285 \\ -0.285 & 0.142 \end{bmatrix}$
26. Find out which one of the following is tie – set matrix of given graph.




- (A) $\begin{bmatrix} -1 & +1 & 0 & 0 & +1 & 0 & 0 \\ +1 & -1 & 0 & +1 & 0 & 1 & 0 \\ -1 & 0 & +1 & -1 & 0 & 0 & 1 \end{bmatrix}$
 (B) $\begin{bmatrix} -1 & +1 & 0 & 0 & +1 & 0 & 0 \\ +1 & -1 & -1 & -1 & 0 & -1 & +1 \\ 0 & 0 & +1 & +1 & 1 & 1 & -1 \end{bmatrix}$

- (C) $\begin{bmatrix} +1 & -1 & 0 & 0 & +1 & 0 & 0 \\ +1 & -1 & 0 & -1 & 0 & 0 & 0 \\ 0 & 0 & +1 & -1 & 0 & 0 & 1 \end{bmatrix}$
 (D) $\begin{bmatrix} 0 & 0 & 1 & -1 & 0 & -1 & +1 \\ 0 & 1 & 0 & -1 & 0 & -1 & +1 \\ 1 & 0 & 0 & 0 & 1 & 0 & +1 \end{bmatrix}$

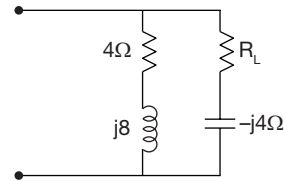
27. Find the value of R_L in the circuit shown below will make it resonant.



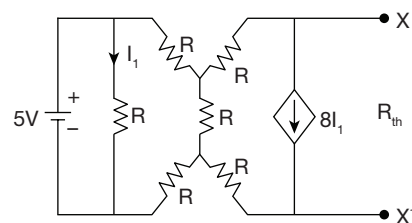- (A) 4.9Ω (B) 24Ω
 (C) 5.56Ω (D) None of these
28. A star connector alternator supplies a delta connected load. The impedance of each branch is $(3 + j4)\Omega$. The line voltage is 400 V. Then find reactive power of the load.
 (A) 67.8 VAR (B) 57.6 KVAR
 (C) 33.255 KVAR (D) 76.8 KVAR
29. Find thevenin's equivalent resistor for given circuit where all resistances are equal to $R\Omega$.




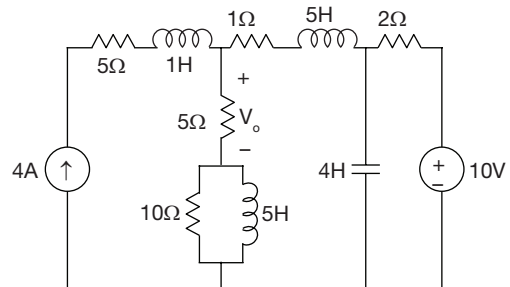- (A) $\frac{3}{8}R$ (B) $\frac{8}{3}R$
 (C) $\frac{R}{4}$ (D) $4R$
30. Find V_o at steady state.




- (A) zero V (B) 6.1 V
 (C) 4 V (D) 13.75 V

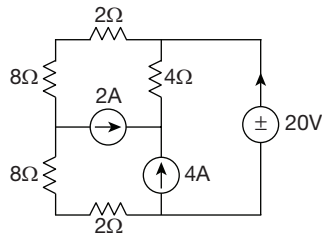31. Find the power delivered by the voltage source is




- (A) 80 W (B) 20 W
(C) 40 W (D) -80 W



Common data for Questions 32 and 33:

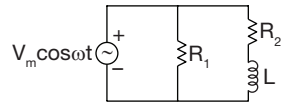

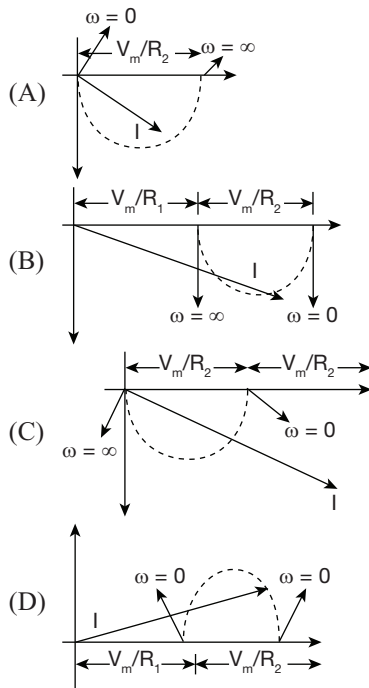32. In above network ω is varies then locus of total current




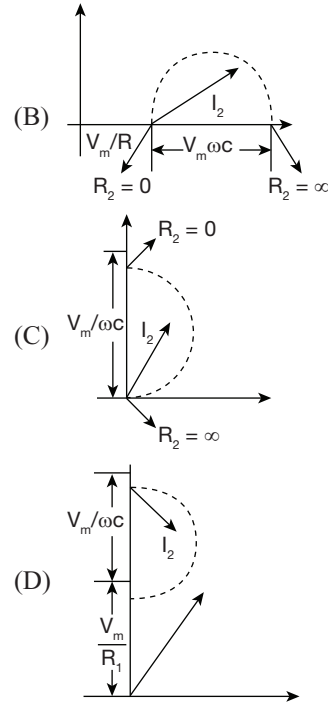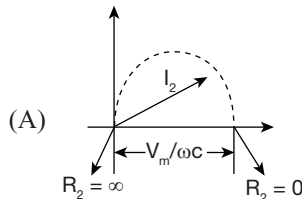33. In the above circuit inductor is replaced by a capacitor and instead of ω if R_2 is varied then locus of I_2 current.



Statement for Linked answer Questions 34 and 35:

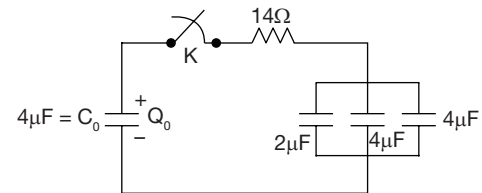A $4\mu\text{F}$ capacitor is initially charged with $600\mu\text{C}$. At $t = 0$, the switch is closed.



34. Determine the voltage drop across resistor at $t < T$ where T is time constant.

- (A) $600 e^{-25 \times 10^3 t} \text{ V}$ (B) $600 e^{-14 \times 10^3 t} \text{ V}$
(C) $150 e^{-25 \times 10^3 t} \text{ V}$ (D) $150 e^{-14 \times 10^3 t} \text{ V}$

35. Find voltage drop across resistor at $40\mu\text{sec}$


- (A) 22 V (B) 339 V
(C) 55.18 V (D) 85 V

ANSWER KEYS

- | | | | | | | | | | |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 1. A | 2. D | 3. C | 4. C | 5. B | 6. C | 7. B | 8. B | 9. B | 10. B |
| 11. D | 12. D | 13. C | 14. B | 15. C | 16. C | 17. D | 18. B | 19. A | 20. C |
| 21. B | 22. A | 23. B | 24. C | 25. D | 26. A | 27. A | 28. D | 29. B | 30. D |
| 31. D | 32. B | 33. C | 34. C | 35. C | | | | | |

HINTS AND EXPLANATIONS

1.


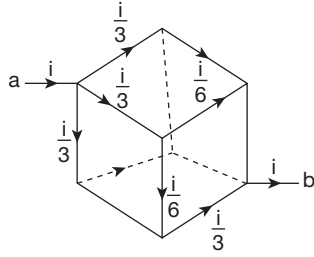


$$V_{ab} = \frac{1}{3} \frac{di}{dt} + \frac{1}{6} \frac{di}{dt} + \frac{1}{3} \frac{di}{dt} = \frac{5}{6} \frac{di}{dt}$$

$$L_{eq} = \frac{5}{6} \text{ H}$$

Choice (A)

2.

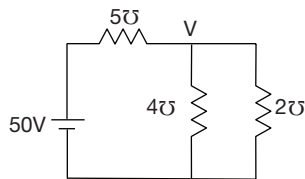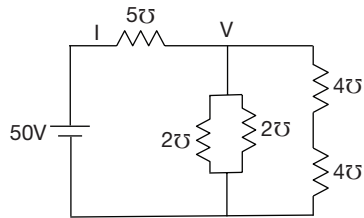

$$(V - 50) 5 + V 4 + 2 V = 0$$



$$11 V = 250$$

$$V = \frac{250}{11}$$

$$i = \left(50 - \frac{250}{11} \right) 5 = 136.36 \text{ A}$$

Choice (D)


3.

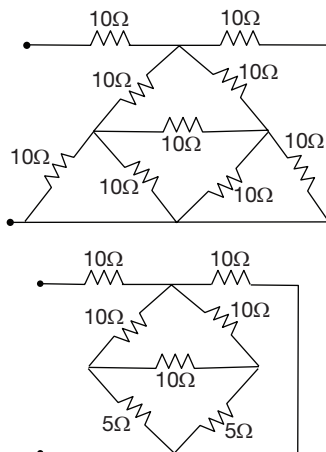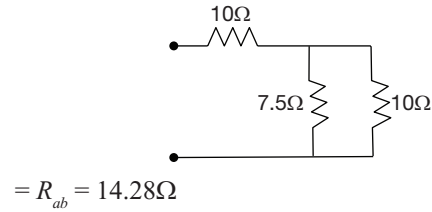
 $\Rightarrow$ from bridge balance


$$= R_{ab} = 14.28 \Omega$$

Choice (C)


4.

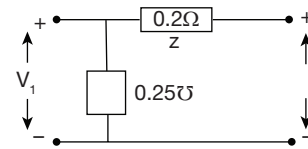

$$\Rightarrow \begin{bmatrix} 1 & z \\ y & zy + 1 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} 1 & 0.2 \\ 0.25 & 1.05 \end{bmatrix}$$

Choice (C)

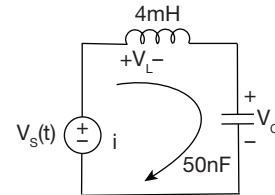5. If $V_c(t) = 5 \sin 10^5 t$ V in below circuit then $V_s(t)$


$$i_c = i = \frac{C dv_c}{dt} \text{ where } (V_c) = 5 \sin 10^5 t$$

$$= 50 \times 10^{-9} \times 5 \times 10^5 \cos 10^5 t = 25 \cos 10^5 t \text{ mA}$$

$$V_s = V_L + V_C$$

$$V_L = L \frac{di}{dt} = 4 \times 10^{-3} 25 \times 10^5 \sin 10^5 t \times 10^{-3}$$


$$= -10 \sin 10^5 t$$

$$V_s = -5 \sin 10^5 t \text{ volts.}$$

Choice (B)

6. Choice (C)

7.

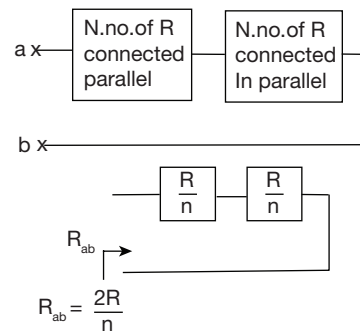

$$R_{ab} = \frac{2R}{n}$$

Choice (B)

8. Current through the inductance is

$$I = \frac{1}{L} \int V dt$$

$$= \frac{10^3 \times 8}{4} \int \sin 314 t dt$$

$$= 2 \times 10^3 \left[\frac{-\cos 314 t}{314} \right]$$

$$= -6.37 \cos 314 t \text{ amps}$$

Instantaneous power

$$P = Vi = (8 \sin 314 t) (-6.37 \cos 314 t)$$

$$= -50.96 \sin 314 t \cos 314 t$$

$$= -25.48 \sin 628 t$$

Choice (B)

9. $L_1 = j2.5\Omega$; $M_{12} = j2\Omega$

$$L_2 = j3\Omega$$
; $M_{23} = j5\Omega$

$$L_3 = j1.5\Omega$$
; $M_{13} = j4\Omega$


Net inductance is $L_1 + L_2 + L_3 - 2M_{12} - 2M_{23} + 2M_{13}$

$$= j(2.5 + 1.5 + 3) - 2 \times j2 - 2 \times j5 + 2(j4)$$

$$= j7 - j4 - j10 + j8 = j1$$

Choice (B)

10. Find time constant of below circuit

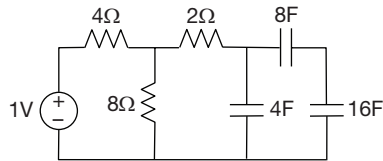

$$T = R_{eq} \cdot C_{eq} = (4/8 + 2)(4 + 8/16)$$

$$= \frac{28}{3} \times \frac{14}{3} = 43.56 \text{ sec}$$

Choice (B)

11. Quality factor $Q = \frac{|x_L|}{R} = \frac{|x_C|}{R} = 2$

rms voltage across inductor

$$V_{L_{rms}} = QV \angle 90^\circ = 400 \angle 90^\circ$$

Choice (D)


12. $f_r = \sqrt{f_1 f_2} = \sqrt{5 \times 8} = 6.32 \text{ KHz}$

Choice (D)

13. It is balanced wheat stone bridge. The current through R is zero so power delivered to R is zero

Choice (C)

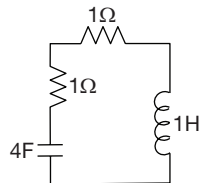15. At $t = 0$ when the switch is opened then the circuit can be redrawn as



$$\xi = \frac{R}{2} \sqrt{\frac{C}{L}}$$

$$R = 1 + 1 = 2\Omega$$


$$L = 1\text{H}$$

$$C = 4\text{F}$$

$$\xi = \frac{2}{2} \sqrt{\frac{4}{1}} = 2 > 1$$

Choice (C)

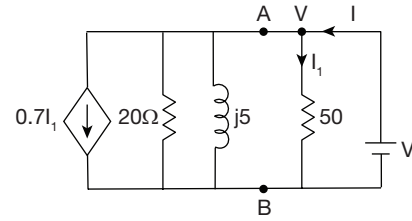16. maximum power delivered to open circuit Z



$$I_1 = \frac{V}{50}$$

$\Rightarrow$ KCL at node V

$$\frac{V}{20} + \frac{V}{j5} + \frac{V}{50} + 0.7I_1 = I$$

$$V \left[\frac{1}{20} + \frac{1}{50} + \frac{0.7}{50} - \frac{j}{5} \right] = I$$

$$\frac{I}{V} = \left[\frac{1}{20} + \frac{1.7}{50} - \frac{j}{5} \right] = (0.084 - j0.2)$$

$$\frac{V}{I} = Z_{th} = \frac{1}{(0.084 - j0.2)}$$


$$= (1.785 + j4.25)\Omega$$

But $Z_L = Z_{th}$

$$Z_L = (1.785 - j4.25)\Omega$$

Choice (C)

17.

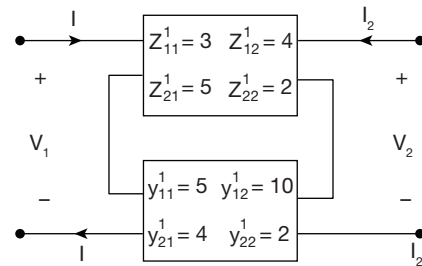

$$z_{eq} = [Z_1] + [Z_2]$$


$\rightarrow$ Convert y matrix in to Z - matrix


$$[Z_2] = [y_2]^{-1} = \begin{bmatrix} 5 & 10 \\ 4 & 2 \end{bmatrix}^{-1} = \begin{bmatrix} 2 & -10 \\ -4 & 5 \end{bmatrix} \times \frac{1}{-30}$$

$$\Rightarrow Z_{eq} = \begin{bmatrix} 3 & 4 \\ 5 & 2 \end{bmatrix} + \begin{bmatrix} \frac{-1}{15} & \frac{1}{3} \\ \frac{2}{15} & -\frac{1}{6} \end{bmatrix} = \begin{bmatrix} 2.933 & 4.333 \\ 5.133 & 1.833 \end{bmatrix}$$

Choice (D)

18.

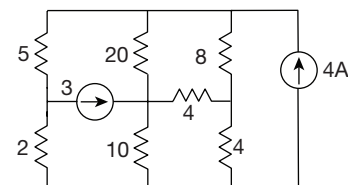

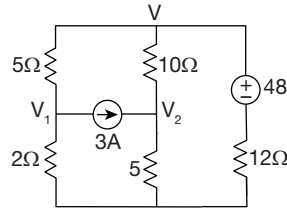

$$\Rightarrow \text{KCL at } V$$

$$\frac{V - V_2}{10} + \frac{V - 48}{12} + \frac{V - V_1}{5} = 0$$

$$23V = 6V_2 + 12V_1 + 240$$

$$\text{KCL at } V_1, \frac{V_1}{2} + \frac{V_1 - V}{5} = 3$$

$$7V_1 - 2V = 30$$

$$\Rightarrow V_1 = \frac{30 + 2V}{7}$$

$$\text{KCL at } V_2, 3 = \frac{V_2 - V}{10} + \frac{V_2}{5}$$

$$15V_2 - 5V = 150$$

$$3V_2 - V = 50$$

$$\frac{50 + V}{3} = V_2$$

$$\Rightarrow 23V = 6 \left(\frac{50 + V}{3} \right) + 12 \left(\frac{30 + 2V}{7} \right) + 240$$

$$V \left[23 - \frac{6}{3} - \frac{24}{7} \right] = 100 + \frac{360}{7} + 240$$

$$\frac{123V}{7} = \frac{2740}{7}$$

$$V = 22.3$$

$$V_1 = 10.65$$

$$5i = V - V_1$$


$$i = \frac{V - V_1}{5} = 2.32 \text{ A}$$

→ (2)

→ (3)

Choice (B)

19. Redrawing given circuit

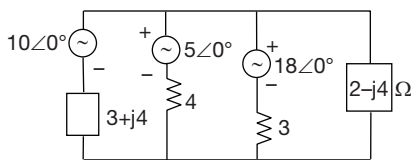

$$\text{According to millman's theorem } V = \frac{V_1 Y_1 + V_2 Y_2 + V_3 Y_3}{Y_1 + Y_2 + Y_3}$$

$$E = \frac{\frac{10}{3+j4} + \frac{5}{4} + \frac{18}{3}}{\frac{1}{3+j4} + \frac{1}{4} + \frac{1}{3}} = \frac{\frac{10(3-j4)}{5} + \frac{5}{4} + \frac{18}{3}}{\frac{3-j4}{5} + \frac{1}{4} + \frac{1}{3}}$$

$$= \frac{6-j8+6+1.25}{\frac{71}{60} - \frac{j48}{60}}$$

$$= \frac{(13.25 - j8)60}{71 - j48}$$


$$= \frac{15.48 \angle -31^\circ \times 60}{85.7 \angle -34^\circ}$$

$$E = 10.83 \angle -3^\circ$$

$$i_{ZL} = \frac{E}{Z_L} = \frac{10.83 \angle -3^\circ}{2 - j4} = \frac{10.83 \angle -3^\circ}{4.47 \angle -63^\circ} = 2.43 \angle 60^\circ \text{ A}$$


Choice (A)

20.

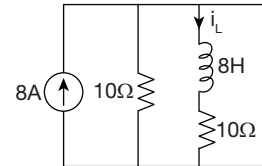

$$i_L = 0 \text{ at } t = 0^-$$

$$\text{at } t = \infty$$

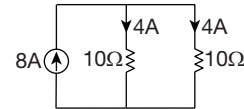

$$i_L = 4 \text{ A}$$

$$T = \frac{L}{R} = \frac{8}{20} = 0.4$$

$$i_L = 4 + (0 - 4) e^{\frac{-t}{0.4}} = 4 \left(1 - e^{\frac{-t}{2}} \right)$$

$$V_L = \frac{L di_L}{dt} \text{ volts.} = 8 \times 4 \times \frac{5}{2} e^{\frac{-5t}{2}}$$

$$V_L = 80 e^{\frac{-5t}{2}} \text{ V}$$


Choice (C)

21. From the given data

$$I(0^-) = -1 \text{ A and } V_c(0^-) = 1 \text{ V.}$$

$$V_i(t) = u(t) \text{ volts.}$$

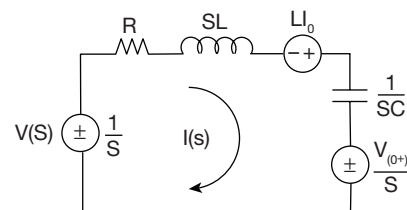Converting the given circuit into S-Domain. It becomes.



Applying KVL

$$\therefore \frac{1}{S} = \left(R + SL + \frac{1}{SC} \right) I(S) - L I_0 + \frac{V_0}{s}$$

$$\frac{1}{S} = \left(2 + 2s + \frac{1}{2s} \right) I(s) + 2 + \frac{1}{s}$$

$$I(s) = \frac{-2 \times 2s}{4s^2 + 4s + 1} = \frac{-s}{s^2 + s + \frac{1}{4}}$$

$$I(s) = \frac{-s}{\left(s + \frac{1}{2}\right)^2}$$

$$V_L = L \cdot \frac{di}{dt(t)}$$

$$I(s) = \frac{A}{s + \frac{1}{2}} + \frac{B}{\left(s + \frac{1}{2}\right)^2}$$

$$B \text{ at } s = -\frac{1}{2}$$

$$B = \frac{1}{2}$$

$$-s = A \left(s + \frac{1}{2}\right) + B$$

Compare both sides s^1 terms.

$$A = -1$$

$$\therefore I(s) = \frac{-1}{\left(s + 2\right)} + \frac{\left(\frac{1}{2}\right)}{\left(s + \frac{1}{2}\right)}$$

$$I(t) = \left\{ -e^{-\frac{1}{2}t} + \frac{1}{2}te^{-\frac{1}{2}t} \right\} \text{ wts.}$$

$$V_{2(t)} = L \cdot \frac{di(t)}{dt} = 2 \left\{ \frac{d}{dt} \left\{ -e^{-\frac{1}{2}t} \right\} + \frac{d}{dt} \left\{ t e^{-\frac{1}{2}t} \right\} \right\}$$


$$= e^{-\frac{1}{2}t} + t \left\{ -\frac{1}{2} e^{-\frac{1}{2}t} \right\} + e^{-\frac{1}{2}t} \cdot 1$$

$$V_L(t) = (2 \cdot e^{-0.5t} - 0.5t \cdot e^{-0.5t})$$

$$V_L(t) = \{2 - 0.5t\} \cdot e^{-0.5t} \cdot V(t).$$

Choice (B)

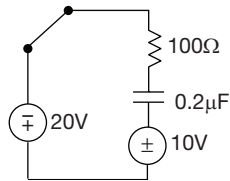22. From the given data $V_c(0^+) = 10V$, $V_c(0^-)$ for $t \geq 0$, the circuit becomes.



$$V_c(\infty) = 30V$$

$$\tau = RC = 100 \times 0.2 \times 10^{-6} = 20 \mu \text{ sec}$$

$$V_c(t) = V_c(\infty) + \{V_c(0^+) - V_c(\infty)\} \cdot e^{-t/\tau} \text{ volts}$$

$$= 30 - 20 \cdot e^{-50 \times 10^3 t} \text{ volts}$$

at $t = 0.1$ in sec.

$$V_c = 30 - 20 \cdot e^{-5} = 29.86$$

$$E = \frac{1}{2} CV^2$$

$$= \frac{1}{2} \times 0.2 \times 10^{-6} \times 892 \approx 89.2 \mu J$$

Choice (A)

23. Let ϕ_1 = primary flux ; ϕ_{12} mutual flux, K co-efficient of coupling $I_1 = 10$ A

$$\phi_{12} = K \phi \Rightarrow 0.8 = 0.7 \phi_1$$

$$\Rightarrow \phi_1 = 1.1428$$

$$L_1 = \frac{N_1 \phi_1}{I_1} = \frac{400 \times 1.1428}{10} = 45.7H$$

$$M = K \sqrt{L_1 L_2}$$


$$N_2 = \frac{\phi_{12}}{I_1} = M = 800 \times \frac{0.8}{10}$$

$$\Rightarrow 64 = 0.7 \sqrt{45.7 L_2}$$

$$\Rightarrow L_2 = 183H$$

Choice (B)

- 24.

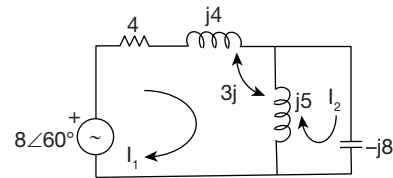

Applying KVL in loop 1

$$8 \angle 60^\circ = 4I_1 + j4I_1 + j5(I_1 - I_2) - j3(I_1 - I_2)$$

$$8 \angle 60^\circ = I_1(4 + j6) - j2I_2$$

Apply KVL in loop 2

$$j5(I_2 - I_1) - j8I_2 - j3I_1 = 0$$

$$\Rightarrow I_1 8j = 3j I_2$$

$$I_1 = \frac{3}{8} I_2$$

$$\Rightarrow 8 \angle 60^\circ = I_2 \left(\frac{3}{8}(4 + j6) - 2j \right)$$

$$8 \angle 60^\circ I_2 \left(\frac{3}{2} - \frac{j}{4} \right)$$

$$I_2 = \frac{8 \angle 60^\circ}{1.52 \angle -9.5^\circ} = 5.263 \angle 69.5^\circ$$


Drop across capacitors is $(-j8) \times (5.263 \angle 69.5^\circ)$

$$= 8 \angle -90^\circ \times 5.263 \angle 69.5^\circ$$

$$= 42.1 \angle -20.5^\circ$$

Choice (C)

- 25.

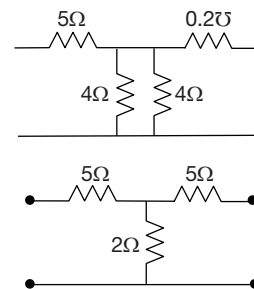

$$Z \text{ matrix is } \begin{bmatrix} 7 & 2 \\ 2 & 7 \end{bmatrix}$$

Converting zmatrix in h parameter

3.22 | Networks Test 2

$$h_{11} = \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{22}} = 6.428\Omega$$

$$h_{12} = \frac{Z_{12}}{Z_{22}} = \frac{2}{7} = 0.285$$


$$h_{21} = \frac{-Z_{12}}{Z_{22}} = \frac{-2}{7} = -0.285$$

$$h_{22} = \frac{1}{Z_{22}} = \frac{1}{7} = 0.142$$

$$\Rightarrow h \text{ matrix is } \begin{bmatrix} 6.428 & 0.285 \\ -0.285 & 0.142 \end{bmatrix}$$

Choice (D)

26.

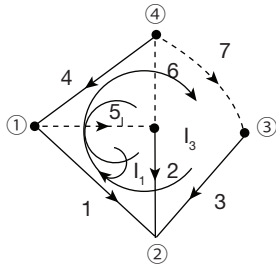

Tie – set 1 (loop current I_1) → formed by twigs 1 & 2 with link 5

Tie – set 2 (loop current I_2) → twigs 1, 2, 4 with link 6

Tie – set 3 (loop current I_3) → twigs 3, 1, 4, & link 7

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} \begin{bmatrix} -1 & +1 & 0 & 0 & +1 & 0 & 0 \\ +1 & -1 & 0 & +1 & 0 & 1 & 0 \\ -1 & 0 & +1 & -1 & 0 & 0 & 1 \end{bmatrix}$$

Choice (A)

27. At resonant frequency imaginary part of Total impedance or admittance must be zero

$$Y_L = \frac{1}{4 + j8} = \frac{4 - j8}{80} = \frac{1 - 2j}{20}$$

$$Y_C = \frac{1}{R_L - j4} = \frac{R_L + j4}{R_L^2 + 16}$$

Thus imaginary part of $Y_t = y_c + y_L$ must be zero

$$\frac{-2j}{20} + \frac{j4}{R_L^2 + 16} = 0$$

$$\frac{4}{R_L^2 + 16} = \frac{2}{20}$$

$$40 = R_L^2 + 16$$

$$R_L^2 = 24$$

$$R_L = \sqrt{24} = 4.9\Omega$$

Choice (A)

28. $Z_{ph} = 3 + j4 = 5 \angle 53.13^\circ \Omega$

$$V_L = 400 \text{ V}$$

$$I_{ph} = \frac{400}{5} = 80 \text{ A}$$

$$I_L = 80\sqrt{3} \text{ A}$$

$$\text{Power factor of load} = \cos \phi = \frac{R_{ph}}{Z_{ph}} = \frac{3}{5} = 0.6 \text{ lag}$$


$$\text{Reactive power of load} = \sqrt{3} V_L I_L \sin \phi$$

$$= \sqrt{3} \times 400 \times \sqrt{3} \times 80 \times 0.8$$

$$= 76.8 \text{ KVAR}$$

Choice (D)

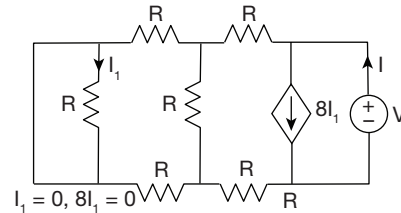29. To find thevenins Resistor, short circuit voltage source



$$\frac{V_1}{2R} + \frac{V_1}{R} + \frac{V_1 - V}{2R} = 0 \text{ and}$$

$$\frac{V - V_1}{2R} = I \quad \text{----- (i)}$$

$$V_1 \left[\frac{1}{2R} + \frac{1}{R} + \frac{1}{2R} \right] = \frac{V}{2R}$$

$$V_1 \left[\frac{2}{R} \right] = \frac{1}{2R}$$


$$\Rightarrow V_1 = \frac{V}{4} \quad \text{----- (ii)}$$

Sub (ii) in (i)

$$\frac{V - \frac{V}{4}}{2R} = I; \quad \frac{3V}{I} = 8R$$

$$\Rightarrow \frac{V}{I} = \frac{8}{3} R = R_{th} \quad \text{Choice (B)}$$

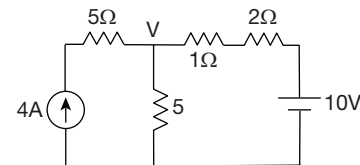30. At steady state inductor is short circuited and capacitor is open circuited so redrawing given circuit




$$4 = \frac{V}{5} + \frac{V - 10}{3}$$

$$V = \frac{110}{8} = 13.75$$

Choice (D)

31. Given Network is

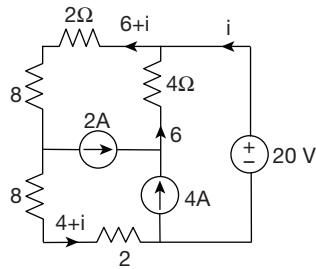

Apply KVL

$$20 = 10(6+i) + 10(4+i)$$

$$20 = 10[10+2i]$$

$$2 = 10 + 2i$$


$$\Rightarrow 2i = -8$$

$$i = -4$$

$$\text{Power} = 20 \times -4 = -80 \text{ W}$$

Choice (D)

32.

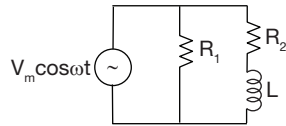


$$I = I_1 + I_2 = \frac{V_m \angle 0^\circ}{R_1} + \frac{V_m \angle 0^\circ}{R_2 + j\omega L}$$

$$\frac{V_m \angle 0^\circ}{R_1} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} - \tan^{-1}\left(\frac{\omega L}{R}\right)$$


Choice (B)

33.

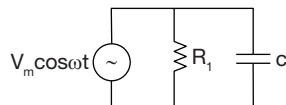

If $R_2 = 0$

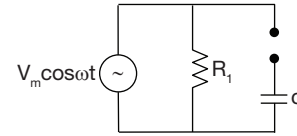
$$I_2 = \frac{E_m}{\frac{1}{\omega C}} \angle -90^\circ = E_m \omega C \angle -90^\circ$$



If $R_2 = \infty$ $I_2 = 0$

Choice (C)

34. Given circuit is

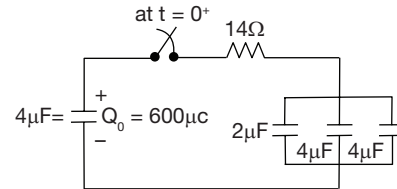

$$T = RC_{eq} = 14 \left(\frac{10}{4}\right) \times 10^{-6} = 14 \times \frac{20}{7} \times 10^{-6}$$

$$= 40 \mu \text{ sec}$$

The initial voltage V_0 across capacitor C_0 is given as

$$V_0 = \frac{Q_0}{C_0} = \frac{600 \times 10^{-6}}{4 \times 10^{-6}} = 150 \text{ V}$$

→ With closing of k_1 the capacitor C_0 will start discharging, and at $t = 0^+$ there will be no voltage across $2\mu\text{F}$, $4\mu\text{F}$, $4\mu\text{F}$, because at $t = 0^-$ switch is opened. So the entire voltage drop across R at $t = 0^+$ time

$$V_R = V_0 e^{-t/RC} = 150 e^{-\frac{t}{40 \times 10^{-6}}} = 150 e^{-25 \times 10^3 t}$$

Choice (C)

$$35. V_R = 150 e^{-25 \times 10^3 \times 40 \times 10^{-6}} = 150 e^{-1} = 55.18$$

Choice (C)