

ANALOG CIRCUITS TEST I

Number of Questions: 35

Time: 90 min.

Directions for questions 1 to 35: Select the correct alternative from the given choices.


1. For a voltage controlled current source, the Input impedance and output impedances are respectively
 (A) low, high (B) high, high
 (C) high, low (D) low, low
2. Which of the following conditions must be satisfied to avoid thermal runaway?

$$(1) \frac{\partial P_C}{\partial T_j} < \frac{1}{\theta_{jA}} \quad (2) 2V_{CE} < V_{CC}$$

$$(3) V_{CE} \geq 1/2 V_{CC} \quad (4) \frac{\partial P_C}{\partial T_j} > \frac{1}{\theta_{jA}}$$

- (A) 1 and 2 only (B) 3 only.
 (C) 1 and 3 only (D) 2 and 4 only
3. In a JFET amplifier, the source resistance R_s is unbypassed. Find the voltage gain of the amplifier. Given $g_m = 4\text{ms}$, $R_D = 2\text{k}\Omega$ and $R_s = 500\Omega$
 (A) 2.66 (B) 1.53
 (C) 2.25 (D) 1.8

4. The output voltage V_0 is

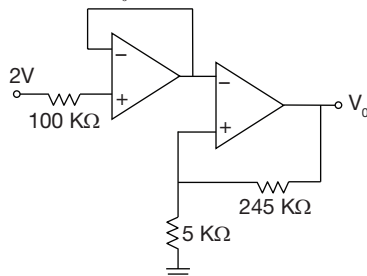

- (A) 100 V (B) -98 V
 (C) 1.96 V (D) 10 V
5. What are the effects of Darlington pair?
 (1) High input impedance (2) High current gain
 (3) Unity voltage gain (4) Low current gain
 (A) 1, 2 and 3 (B) 1, 2 and 4
 (C) 1, 3 and 4 (D) 1 and 3 only
6. An RC amplifier stage has the rise time $0.75\mu\text{sec}$, what will be the bandwidth of this amplifier stage?
 (A) 500 KHz (B) 450 KHz
 (C) 540 KHz (D) 467 KHz
7. The open loop voltage gain of an amplifier is 250. The noise level in the output without feedback is 100mV. If a negative feedback with $\beta = \frac{1}{50}$ is used, the noise level


in the output will be

- (A) 16.66 mV (B) 20 mV
 (C) 1.66 mV (D) 0.6 V

8. What is the main source of distortion in a push – pull amplifier?

- (A) All odd harmonics
 (B) All even harmonics
 (C) Third harmonic
 (D) Fundamental components


- 9.

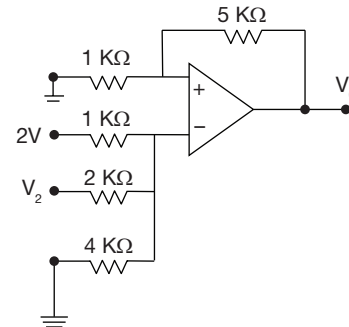

If the output $V_0 = 12\text{ V}$, then the input voltage V_2 is _____

- (A) 3 V (B) 2 V
 (C) -3 V (D) 6 V

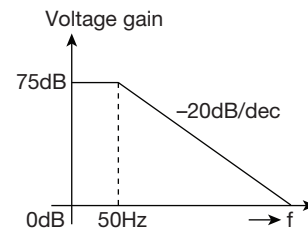
10. The voltage gain versus frequency curve of an op – amp is shown in the given figure



The gain – bandwidth product of the op – amp is

- (A) 250 KHz (B) 2.5 MHz
 (C) 281 KHz (D) 2.8 MHz

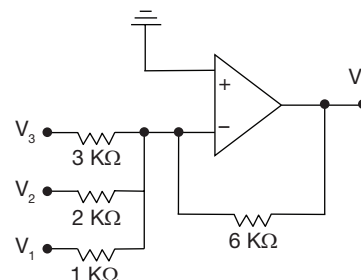
11. If $V_1 = 2\text{V}$, $V_2 = -3\text{V}$ and $V_3 = 1\text{V}$, then the output voltage V_0 is



- (A) 0 V (B) -10 V
 (C) -5 V (D) 2.5 V

12. An ideal operational amplifier is a
 (A) CCVS (B) CCCS
 (C) VCVS (D) VCCS


13.

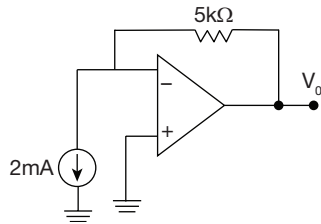

The output voltage V_o is


- (A) -10 V (B) 5 V
 (C) 10 V (D) -2.5 V
14. A dc voltage supply provides 50 V when the output is unloaded. When connected to a load, the output drops to 45 V. Then the voltage regulation is
 (A) 7.3% (B) 10%
 (C) 11.11% (D) 13.24%

15.

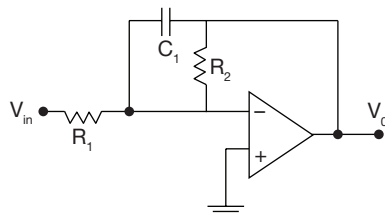


The given circuit represents a

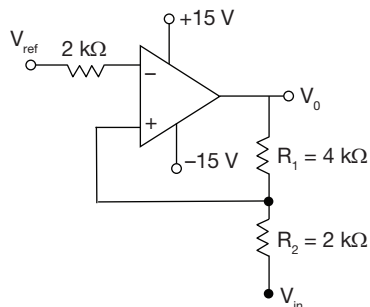- (A) BPF (B) HPF
 (C) APF (D) BSF
16. The schmitt trigger circuit shown in the figure



If $V_{ref} = -2V$, then the values of V_{UT} and V_{LT} are
 (A) 4.5 V, -10.5 V (B) 10.5 V, -4.5 V
 (C) 7.5 V, -7.5 V (D) 5.5 V, -9.5 V



17.

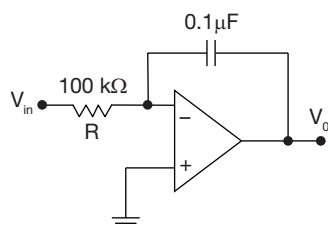


If $V_{in} = 5 + 1.5t^2$ Volts, then the output voltage of the given circuit at $t = 0.5$ sec is

- (A) -1.5 V (B) -3.84 V
 (C) -5.375 V (D) -2.5625 V

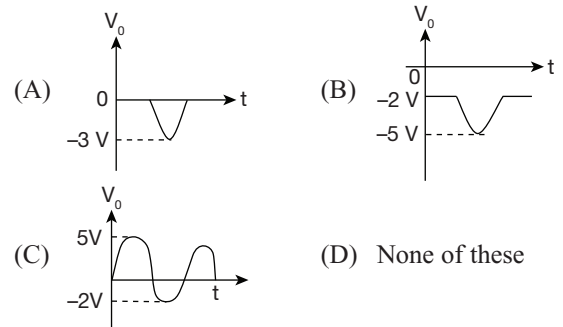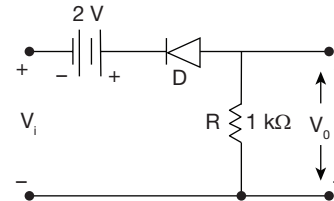18. Determine V_o for the network of figure, for the input $V_i(t) = 5 \sin \omega t$ Volts.



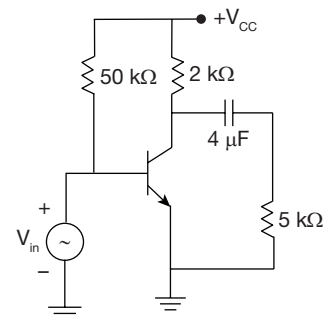
19. The cut - off frequency due to the output capacitor is _____



- (A) 35.71 Hz (B) 5.68 Hz
 (C) 47.746 Hz (D) 8.25 Hz


20. The unity gain bandwidth of a n - channel MOSFET amplifier having $V_{tn} = 2V$, and biased at $V_{GS} = 4 V$. The high frequency n - channel MOSFET parameters are $K_n = 0.5\mu A/V^2$, $C_{gd} = 0.05pF$, $C_{gs} = 0.2pF$.
 (A) 2.546 kHz (B) 2.546 MHz
 (C) 1.273 kHz (D) 1.273 MHz

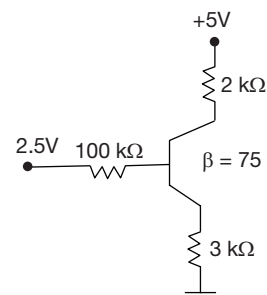21. Find the region of operation of the transistor.



- (A) Cut – off (B) Saturation
(C) Active (D) Inverse active

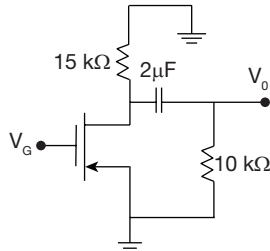22. The ac schematic of an PMOS common – source gate is shown in the figure below. For P – channel MOSFET, the trans conductance, $g_m = 2\text{mA/V}$, body effect and channel length modulation effects are to be neglected. Then the lower cut – off frequency of the circuit is approximately at



- (A) 20 Hz (B) 25 Hz
(C) 83.33 Hz (D) 523.59 Hz


23. Match List – I (amplifier mode of operation) with List – II (Characteristics) and select the correct answer using the codes given below the lists.

	List – I		List – II
p	Class – A	1	Transistor acts as switch
q	Class – B	2	Leads to most stable biasing circuit
r	Class – C	3	Amplification of the resonant frequency only
s	Class – D	4	Operating point is at the cut – off point.

Codes;

- (A) $p - 2, q - 4, r - 1, s - 3$
(B) $p - 4, q - 2, r - 3, s - 1$
(C) $p - 2, q - 4, r - 3, s - 1$
(D) $p - 4, q - 2, r - 1, s - 3$

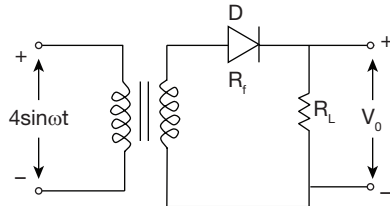24. Consider the circuit given below where $R_f = 250\Omega$, $R_L = 3\text{ k}\Omega$. Then the average and RMS currents would be



- (A) $I_{\text{avg}} = 1.23\text{ mA}, I_{\text{rms}} = 0.615\text{ mA}$
(B) $I_{\text{avg}} = 0.87\text{ mA}, I_{\text{rms}} = 0.39\text{ mA}$
(C) $I_{\text{avg}} = 0.39\text{ mA}, I_{\text{rms}} = 0.87\text{ mA}$
(D) $I_{\text{avg}} = 0.39\text{ mA}, I_{\text{rms}} = 0.615\text{ mA}$


25. Determine the output voltage of an op – amp for input voltages of $V_{i1} = 150\text{ }\mu\text{V}$ and $V_{i2} = 110\text{ }\mu\text{V}$. The amplifier has a differential gain of $A_d = 2000$ and the value of CMRR is 80

- (A) 83.25 mV (B) 75 mV
(C) 8.32 mV (D) 60 mV

26. Calculate the total harmonic distortion for an output signal having fundamental amplitude 2.5V, second harmonic amplitude of 0.5V, third harmonic amplitude of 0.1V.

- (A) 20.40% (B) 10.20%
(C) 4.16% (D) 16%

- 27.

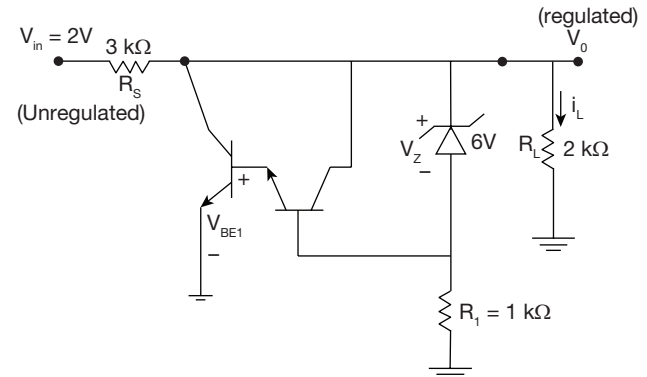


If $V_{BE1} = 0.7\text{V}$, $V_{BE2} = 0.3\text{V}$ and $\beta = 100$. Then the current flowing through the load resistor R_L would be

- (A) 3.7 mA (B) 2.5 mA
(C) –2.5 mA (D) 3.5 mA

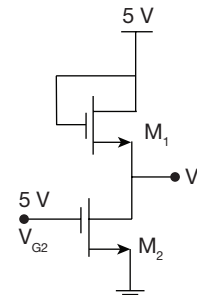
28. The transistors in the circuit of figure have parameters $V_{TN} = 0.3\text{ V}$, $K_n = 50\text{ }\mu\text{A/V}^2$ and $\lambda = 0$. The width – to – length ratio of M_2 is $\left(\frac{W}{L}\right)_1 = 2$. If $V_O = 0.5\text{V}$, when $V_{in} =$

5 V. Then $\left(\frac{W}{L}\right)_2$ is



- (A) 15 (B) 16.8
(C) 2.38 (D) 1.6

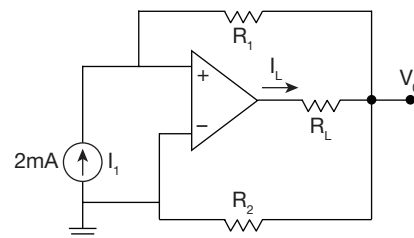
29. For the circuit shown below, if $R_1 = 1.5\text{ k}\Omega$, $R_2 = 3\text{ k}\Omega$, and $R_L = 2\text{ k}\Omega$. Then the value of current I_L is _____.



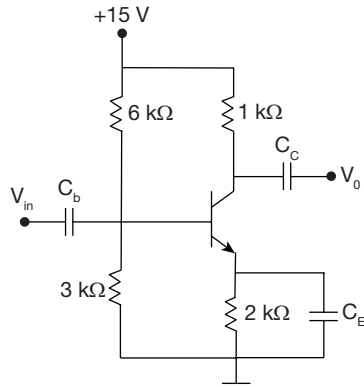
- (A) 6 mA (B) 2 mA
(C) –2 mA (D) 4 mA

Common data for Questions 30 and 31:

The circuit shown in figure, uses silicon transistor having $\beta = 99$.



30. Find the operating point of the given circuit.
 (A) $V_{CE} = 8.643 \text{ V}$, $I_C = 2.1 \text{ mA}$
 (B) $V_{CE} = 7.125 \text{ V}$, $I_C = 1.8 \text{ mA}$
 (C) $V_{CE} = 7.5 \text{ V}$, $I_C = 2.1 \text{ mA}$
 (D) $V_{CE} = 8.643 \text{ V}$, $I_C = 2.5 \text{ mA}$
31. The stability factor is
 (A) $S = 1.5$ (B) $S = 1.75$
 (C) $S = 1.98$ (D) $S = 2.5$

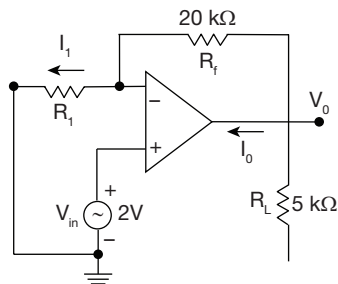Statement for Linked Answer Questions 32 and 33:


32. If $i_1 = 0.5 \text{ mA}$, the output voltage V_o and input impedances are respectively
 (A) 12 V , $4 \text{ k}\Omega$
 (B) $+10 \text{ V}$, $1 \text{ k}\Omega$
 (C) -10 V , $4 \text{ k}\Omega$
 (D) -12 V , $1 \text{ k}\Omega$
33. The current I_o is
 (A) 2.9 mA
 (B) 2.5 mA
 (C) -2.5 mA
 (D) -2.9 mA

Statement for Linked Answer Questions 34 and 35:

When a negative voltage feedback is applied to an amplifier of gain 100, the overall gain falls to 60.

34. The fraction of the output voltage feedback is
 (A) $\frac{60}{100}$ (B) $\frac{1}{150}$
 (C) $\frac{1}{140}$ (D) $\frac{100}{120}$
35. If the cut-off frequencies are $f_1 = 1.5 \text{ KHz}$ and $f_2 = 250 \text{ KHz}$, then the bandwidth of the amplifier with negative feedback is
 (A) 416 KHz
 (B) 410 KHz
 (C) 147.5 KHz
 (D) 295 KHz

ANSWER KEYS

1. B	2. A	3. A	4. D	5. A	6. D	7. A	8. C	9. A	10. C
11. C	12. C	13. C	14. C	15. D	16. A	17. D	18. A	19. B	20. D
21. C	22. A	23. C	24. D	25. A	26. A	27. D	28. B	29. A	30. A
31. C	32. A	33. D	34. B	35. A					

HINTS AND EXPLANATIONS
1. Ideal VCCS

$$R_{in} = \infty$$

$$R_o = \infty$$

But practical case

R_{in} & R_o are very large values.


Choice (B)

2. Choice (A)

$$3. A_v = \frac{g_m R_D}{1 + g_m R_S}; \text{ for } R_S \text{ un by passed } [R_S \neq 0]$$

$$A_v = \frac{4 \times 10^{-3} \times 2 \times 10^3}{1 + 4 \times 10^{-3} \times 0.5 \times 10^3} = \frac{8}{3} = 2.66$$

Choice (A)

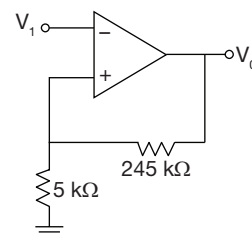4. Redrawing the given circuit


But $V_1 = 2 \text{ V}$, because voltage follower

$$O/P = V_o = V_1 = 2 \text{ V}$$

$$\therefore V_+ = V_-$$

$$V_1 = V_0 \times \frac{5}{250}$$

$$V_0 = 5V_1 = 10 \text{ V}$$

Choice (D)

5. Choice (A)

6. From the given data

$$t_r = 0.75 \mu \text{ sec}$$

$$t_r = \frac{0.35}{BW}$$

$$BW = \frac{0.35}{0.75} \times 10^6$$

$$BW \approx 467 \text{ KHz}$$

Choice (D)

7. From the given data

$$N = 100 \text{ mV}$$

$$A = 250$$

$$\beta = \frac{1}{50}$$

$$1 + A\beta = 1 + \frac{250}{50} = 6$$

$$N_f = \frac{N}{1 + A\beta}$$

$$N_f = \frac{100 \text{ mV}}{6} = 16.66 \text{ mV}$$

Choice (A)

 8. Push – Pull amplifier contains only odd harmonics at the O/P, all the even harmonics are cancelled. The most effective in distortion is third harmonics $3f$, it has highest amplitude among all odd components. Choice (C)

9. Applying virtual GND concept

$$\text{Let } V_+ = V_- = V_a$$

$$\therefore V_0 = \left[1 + \frac{R_f}{R_1} \right] V_a$$

$$V_0 = 6V_a$$

 Apply nodal analysis at node V_+ or V_a

$$\frac{V_a - 2}{1} + \frac{V_a - V_2}{2} + \frac{V_a}{4} = 0$$

$$4[V_a] - 8 + 2V_a - 2V_2 + V_a = 0$$

$$7V_a = 8 + 2V_2$$

$$V_a = \frac{V_0}{6} = 2$$

$$14 - 8 = 2V_2$$

$$V_2 = 3 \text{ Volts}$$

Choice (A)

10. From the given figure

$$\text{At } f = 50 \text{ Hz, gain} = 75 \text{ dB}$$

$$A_{v_{\text{inds}}} = 20 \log_{10} A_v$$

$$20 \log_{10} A_v = 75$$

$$A_v = 10^{3.75} = 5623$$

$$\therefore f_T = B.W \times A_v$$

$$= 50 \times 5623 = 281 \text{ KHz}$$

Choice (C)

11. The given circuit represents a inverting summing amplifier

$$\therefore V_0 = \frac{-R_f}{R_1} V_1 - \frac{R_f}{R_2} V_2 - \frac{R_f}{R_3} V_3$$

$$\therefore V_0 = -\{6 \times 2 + 3 \times (-3) + 2 \times 1\}$$

$$= -\{12 - 9 + 2\} = -5 \text{ Volts.}$$

Choice (C)

12. Choice (C)

13. Form the given circuit

$$\frac{V_0}{5K\Omega} = 2 \text{ mA}$$

$$V_0 = 10 \text{ V}$$

Choice (C)

14. Voltage regulation is given by

$$\%V.R = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100$$

$$= \frac{50 - 45}{45} \times 100 = 11.11\%$$

Choice (C)


15. At low frequencies

Inductor acts as a short circuit and capacitor open circuit.

$$\therefore \frac{V_0}{V_{in}} = -\frac{R_2}{R_1}$$

 At high frequency $f \rightarrow \infty \text{ Hz}$
 $C \rightarrow \text{Short circuit}$
 $L \rightarrow \text{Open circuit}$

The given circuit becomes

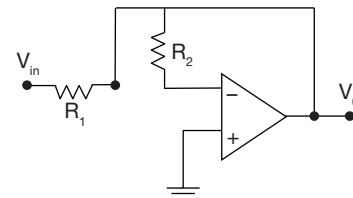


$$\frac{V_0 - V_{in}}{R_1} + \frac{V_0}{R_2} = 0$$

$$V_0 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_{in}}{R_1}$$

$$V_0 \frac{(R_2 + R_1)}{R_1 R_2} = \frac{V_{in}}{R_1}$$


$$\frac{V_0}{V_{in}} = \left(\frac{R_2}{R_1 + R_2} \right)$$

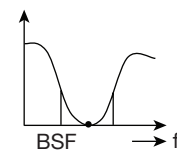
 { $\therefore$ The O/P existing at low & higher frequency range.

 $\therefore$ It indicates Band stop filter.

Choice (D)

16. Redrawing the given circuit

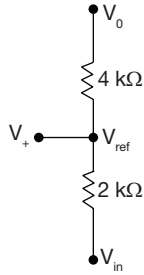

Applying nodal analysis at node V_{ref}

$$\frac{V_{ref} - V_0}{4} + \frac{V_{ref} - V_{in}}{2} = 0$$

$$V_{ref} - V_0 + 2(V_{ref} - V_{in}) = 0$$

$$3V_{ref} - V_0 = 2V_{in}$$

$$V_{in} = \frac{1}{2}[3V_{ref}] - \frac{V_0}{2}$$

if

$$\therefore V_0 = +V_{sat} = 15V$$

$$V_{in} = V_x$$

$$V_x = 1.5(-2) - 7.5$$

$$= -10.5 \text{ volts}$$

If $V_0 = -V_{sat} = -15V$

Let $V_{in} = V_y$

$$V_y = -3 + 7.5 = 4.5 \text{ volts}$$

$\therefore$ upper threshold voltage

$$V_{UT} = 4.5 \text{ V and}$$

$$V_{LT} = -10.5 \text{ V}$$

—————(1)

17. The given circuit represents an integrator

$$\therefore V_0 = \frac{-1}{RC} \int V_{in} dt$$

$$V_0 = \frac{-1}{100 \times 10^3 \times 10^{-5}} \int [5 + 1.5t^2] dt$$

$$= -\int \left[5 + \frac{3}{2}t^2 \right] dt$$

$$= -\left[5t + \frac{3}{2} \cdot \frac{t^3}{3} \right] = -\left[5t + \frac{t^3}{2} \right]$$

At $t = 0.5 \text{ sec}$

$$V_0 = -\left[\frac{5}{2} + \frac{1}{16} \right] = -2.5625 \text{ Volts}$$


Choice (D)

18. If diode $D \rightarrow \text{OFF}$

$$V_0 = 0V$$


Diode $D \rightarrow \text{ON}$ only when

$$V_{in} \leq -2 \text{ V}$$

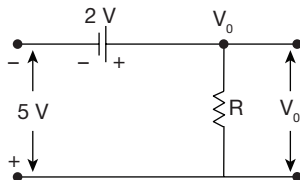

Applying input loop $-5 + 2 - V_0 = 0$


$$V_0 = -3V$$

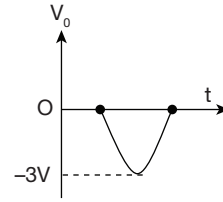


Choice (A)

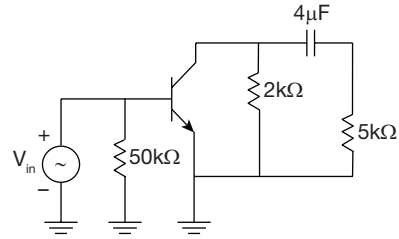19. For A, C analysis deactivate all the D, C Sources.

$$\therefore V_{CC} \rightarrow \text{GND}$$



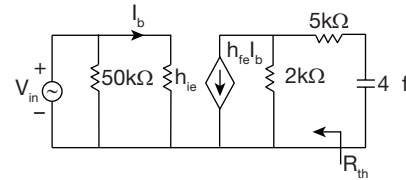The hybrid equivalent model of given circuit is



$$\text{We know } \omega = \frac{1}{\tau} = \frac{1}{R_{th}C}$$

$$\text{But } R_{th} = (5k + 2k) = 7 \text{ k}\Omega$$

$$C = 4\mu\text{F}$$

$$f = \frac{1}{2\pi RC} = \frac{1}{2\pi \times 7 \times 10^3 \times 4 \times 10^{-6}} = 5.68 \text{ Hz}$$

Choice (B)

$$20. f_T = \frac{g_m}{2\pi \{C_{gs} + C_{gd}\}}$$

$$I_D = k_n \{V_{GS} - V_{TN}\}^2$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = 2K_n [V_{GS} - V_{TN}]$$

$$g_m = 2 \times 0.5 \times 2\mu\text{A/V}^2$$

$$= 2\text{mA/V}^2$$

$$\therefore f_T = \frac{2 \times 10^{-6} \times 10^{12}}{2\pi \{0.25\}} = 1.273 \text{ MHz}$$

Choice (D)

21. Applying KVL to the input loop

$$5 - I_E R_E - 0.7 - R_B I_B - 2.5 = 0$$

$$I_B = 7.14\mu\text{A}$$

Applying KVL to the O/P loop.

$$I_C = \frac{5 - 0}{5} \text{ mA}$$

$$I_{Csat} = 1 \text{ mA}$$

$$I_{\text{cactive}} = \beta \cdot I_{\text{Bactive}} \\ = 75 \times 7.14 \times 10^{-6} \text{ A} \\ = -0.5355 \text{ mA}$$

$$I_{\text{cactive}} < I_{\text{csat}} \\ \therefore \text{Transistor is in active mode.}$$

Choice (C)

22. We know

$$f = 1/\tau$$

$$\tau = R_{eq} \cdot C_{eq}$$

$$\therefore R_{eq} = (10 + 15) \text{ k}\Omega = 25 \text{ k}\Omega$$

$$C_{eq} = 2 \text{ }\mu\text{F}$$

$$R_{eq} \cdot C_{eq} = 50 \text{ m sec}$$

$$f = \frac{1000}{50} \text{ Hz} = 20 \text{ Hz}$$

Choice (A)

23. Class A: Most stable biasing circuit

Operating point is in the mid of DC load line

Class B: Operations point is at the cut – off region.

Class C: Operating point is below cut off region and this is suitable for resonant frequency

Class D: Highest efficiency among all power amplifiers and transistor used in this act as switch. It operates in saturation and cut – off.

Choice (C)

24. During +Ve half cycle $D \rightarrow \text{ON}$ –Ve half cycle $D \rightarrow \text{OFF}$ t indicates half wave rectifier

$$\therefore I_{\text{avg}} = \frac{I_m}{\pi}$$

$$\text{But } I_m = \frac{V_m}{R_f + R_L} = \frac{4}{3.25} \text{ mA} = 1.23 \text{ mA}$$

$$I_{\text{avg}} = \frac{1.23}{\pi} \text{ mA} = 0.39 \text{ mA}$$

$$I_{\text{rms}} = \frac{I_m}{2} = 0.615 \text{ mA}$$

Choice (D)

$$25. V_0 = A_d V_d + A_c V_c$$

$$V_0 = A_d V_d \left(1 + \frac{A_c}{A_d} \cdot \frac{V_c}{V_d} \right) \text{ volts}$$

$$\text{But CMRR} = \frac{A_d}{A_c}$$

$$V_0 = A_d V_d \left\{ 1 + \frac{1}{\text{CMRR}} \cdot \frac{V_c}{V_d} \right\}$$

From the given data

$$A_d = 2000; V_{i1} = 150 \mu\text{V}; V_{i2} = 110 \mu\text{V}$$

$$\text{CMRR} = 80$$

$$V_d = \{V_{i1} - V_{i2}\} = 40 \mu\text{V}$$

$$V_c = \frac{1}{2} \{V_{i1} + V_{i2}\} = 130 \mu\text{V}$$

$$V_0 = 2 \times 10^3 \times 4 \times 10^{-5} \left\{ 1 + \frac{1}{80} \times \frac{130}{40} \right\}$$

$$V_0 = 83.25 \text{ mV}$$

Choice (A)

$$26. \%n^{\text{th}} \text{ harmonic distortion} = \%D_n = \left| \frac{A_n}{A_1} \right| \times 100\%,$$

Total harmonic distortion

$$= \sqrt{D_2^2 + D_3^2 + \dots + D_n^2} \times 100\%$$

$$D_2 = \frac{0.5}{2.5} = 0.2$$

$$D_3 = 0.04$$

$$\text{T. H. D}\% = \sqrt{(0.2)^2 + (0.04)^2} \times 100\%$$

$$= \sqrt{0.04 + 1.6 \times 10^{-3}} \times 100\%$$

$$\text{THD} = 20.40\%$$

Choice (A)

27. From the given circuit

Applying KVL to the output loop

$$V_0 - V_z - V_{BE2} - V_{BE1} = 0$$

$$\therefore V_0 = V_z + V_{BE1} + V_{BE2} \\ = 6 + 0.7 + 0.3 = 7 \text{ V}$$

$$\text{But } I_L = \frac{V_0}{R_L} = \frac{7}{2} \text{ mA}$$

$$I_L = 3.5 \text{ mA}$$

Choice (D)

28. For M_2 transistor

$$V_{GS2} = 5 - 0 = 5 \text{ V}$$

$$V_{DS2} = V_0 = 0.5 \text{ V}$$

$$\therefore V_{DS2} < V_{GS2} - V_T$$

$$\therefore M_2 \text{ is in non saturation region given } V_T = 0.3 \text{ V}$$

For M_1 transistor

$$V_{GS1} = 5 - V_0 = 5 - 0.5 = 4.5 \text{ V}$$

$$V_{DS1} = 5 - V_0 = 4.5$$

$$V_{GS} - V_T = 4.5 - 0.3 = 4.2$$

$$V_{DS1} > V_{GS1} - V_T$$

 M_1 in saturation region

$$\therefore V_{DS1} = 4.5 > 4.2 \text{ V}$$

$$\therefore M_1 \text{ in saturation region}$$

$$K_n^1 \times \left(\frac{W}{L} \right)_1 [V_{GS1} - V_T]^2 = K_n^1 \left(\frac{W}{L} \right)_2$$

$$[(V_{GS2} - V_T)V_{DS2} - V_{DS}^2]$$

$$2 \times 17.64 = \left(\frac{W}{L} \right)_2 \times [4.7 \times 0.5 - 0.25]$$

$$\left(\frac{W}{L} \right)_2 = \frac{35.28}{2.1} = 16.8$$

Choice (B)

29. Redrawing the given circuit

Applying virtual GND concept

$$\text{So } V_+ = V_- = 0 \text{ V}$$


$$0 + 2 \times 3 - V_0 = 0$$

$$V_0 = 6 \text{ V}$$

$$i_L = i_{R1} + i_{R2}$$

$$i_{R1} = \frac{V_0}{1.5} \text{ mA} = \frac{6}{1.5} \text{ mA}$$

3.152 | Analog Circuits Test 1

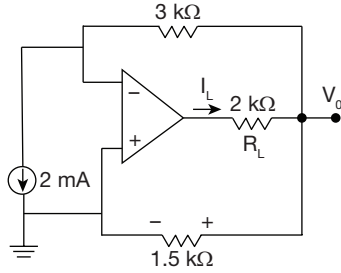


$$\begin{aligned} i_{R1} &= 4 \text{ mA} \\ i_{R2} &= 2 \text{ mA} \\ i_L &= 6 \text{ mA} = i_{R1} + i_{R2} \end{aligned}$$

30. $V_{th} = 15 \times \frac{3}{9} = 5 \text{ V}$

$$R_{th} = (6k \parallel 3k) = 2 \text{ k}\Omega$$

Redrawing the given circuit

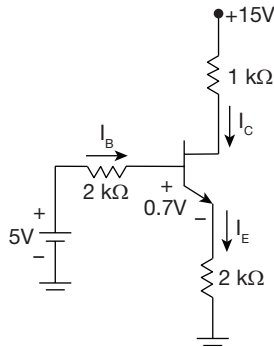

$$I_B = \frac{5 - 0.7}{2k + 100 \times 2k} = \frac{4.3}{202} \text{ mA} = 21.287 \mu\text{A}$$

$$I_C = \beta \cdot I_B = 99 \times 21.287 \times 10^{-6} = 2.1 \text{ mA}$$

Applying KVL to the output loop

$$\begin{aligned} V_{CE} &= V_{CC} - I_C R_C - I_E R_E \\ &= 15 - 2.1 - 4.257 \\ &= 8.463 \text{ Volts} \end{aligned}$$

Operating point

$$(V_{CE}, I_E) = (8.463 \text{ V}, 2.1 \text{ mA})$$

31. We know stability factor

$$S = \frac{1 + \beta}{1 - \beta \cdot \frac{\partial \beta}{\partial C}}$$

Applying KVL to the input loop

$$V_{th} - I_B \cdot R_B - V_{BE} - I_E R_E = 0$$

$$V_{th} = I_B R_B + V_{BE} + I_E R_E + I_C R_E$$

Differentiating both sides w. r. t I_C

$$0 = \frac{\partial \beta}{\partial C} R_B + 0 + \frac{\partial \beta}{\partial C} \cdot R_E + R_E$$

Choice (A)

Choice (A)

$$\therefore S = (1 + \beta) \times \frac{1}{1 + \beta \left(\frac{R_E}{R_B + R_E} \right)}$$

$$S = \frac{100}{1 + 99 \times \left[\frac{2k}{4k} \right]} = 1.98$$

Choice (C)

32. From the given data

$$i_1 = \frac{V_0 - V_{in}}{R_f}$$

$$\begin{aligned} V_0 &= i_1 R_f + V_{in} \\ &= 0.5 \times 20 + 2 \\ &= 12 \text{ Volts} \end{aligned}$$

And input impedance $R_{in} = R_1 = \frac{V_{in}}{i_1}$

$$R_1 = \frac{2}{0.5} \text{ k}\Omega = 4 \text{ k}\Omega$$

Choice (A)

33. From the given data

Applying KCL at output loop $i_L + i_0 + i_1 = 0$

$$\begin{aligned} i_0 &= -i_1 - i_L \\ &= \left(0.5 \times 10^{-3} - \frac{12}{5} \right) \text{ mA} \end{aligned}$$

$$I_0 = -2.9 \text{ mA}$$

Choice (D)

34. From the given data $A_v = 100$ & $A_{vf} = 60$

We know $A_{vf} = \frac{A_v}{1 + A_v \cdot \beta}$

$$60 = \frac{100}{1 + 100 \cdot \beta}$$

$$1 + 100\beta = \frac{2}{3}$$

$$\beta = \frac{1}{150}$$

Choice (B)

35. For a 've' feedback amplifier, BW increases

$$\therefore f_1^1 = \frac{f_1}{1 + A_v \beta}; f_2^1 = f_2(1 + A_v \beta)$$

$$f_1^1 = \frac{1.5 \text{ KHz}}{\left(\frac{5}{3} \right)} = 0.9 \text{ KHz}$$

$$f_2^1 = 250 \times \left(\frac{5}{3} \right) \text{ KHz}$$

$$= 416.66 \text{ KHz}$$

$$BW_f = f_2^1 - f_1^1 = 415.766 \text{ KHz}$$

$$BW_f \approx 416 \text{ KHz}$$

Choice (A)