

The Signal Generators and Wave Shaping Circuits


Oscillators

The oscillators are positive feedback amplifier in which the part of output is feedback to the input via feedback circuit.

The gain, $\frac{V_o}{V_i} = \frac{A}{1 - A\beta}$

$\therefore V_i = 0$ (Noise)

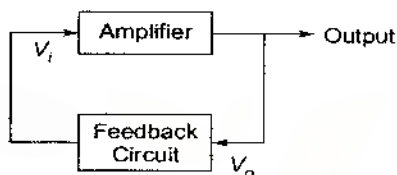$A\beta = 1$ or $1 \angle 0^\circ \approx 1 \angle 360^\circ$



Barkhausen criterion


- The magnitude of loop gain $A\beta$ must be atleast 1.
- The total phase shift of the loop gain $A\beta$ must be equal to 0° or 360° .

Oscillator Types

Type of Component	Frequency of oscillation	Waveform generated
RC oscillator	Audio frequency	Sinusoidal
LC oscillator	Radio frequency	Square wave
Crystal oscillator	Radio frequency	Triangular wave sawtooth wave etc.

RC Phase Shift Oscillator

RC phase shift oscillator using BJT

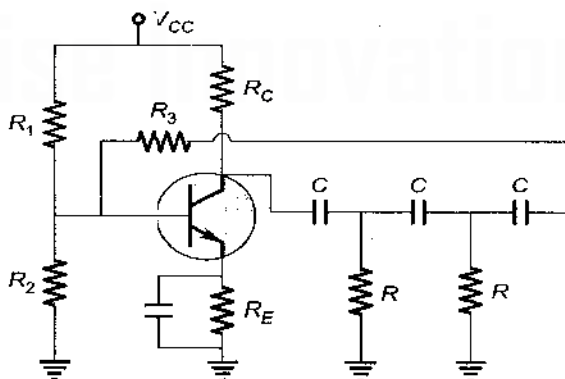

- Frequency of oscillation is

$$\omega = \frac{1}{RC\sqrt{4K+6}} \quad ; \quad f = \frac{1}{2\pi RC\sqrt{4K+6}}$$

where, $K = \frac{R_C}{R}$

Note:

- For transistor to work as oscillator

$$h_{fe} \geq \left(4K + 23 + \frac{29}{K}\right)$$


- $h_{fe(\min)} = 44.5$.

RC Phase Shift Oscillator using FET

- Frequency of Oscillation

$$f = \frac{1}{2\pi RC\sqrt{6}}$$
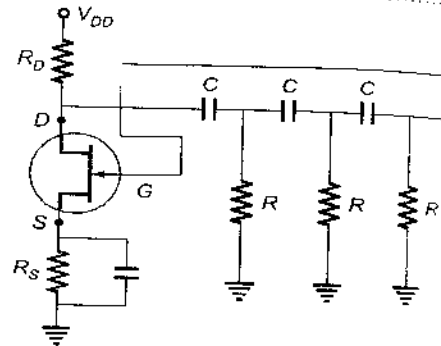
$$\beta = -\frac{1}{29} \text{ (feedback factor)}$$



Note:

Amplification factor for FET to work as an Oscillator is $\mu \geq 29$.


RC Phase Shift Oscillator using Op-Amp

- Feedback factor

$$\beta = \frac{V_f}{V_o} = -\frac{1}{29} \text{ (for oscillation)}$$

- Frequency of oscillation

$$f = \frac{1}{2\pi RC\sqrt{6}}$$

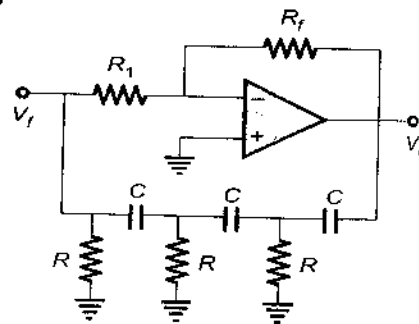

Note:

$R_f \geq 29R_1 \rightarrow$ for oscillation.

Wein Bridge Oscillator


- Frequency of oscillation

$$f = \frac{1}{2\pi\sqrt{R_3 R_4 C_1 C_2}}$$

if $R_3 = R_4 = R$
and $C_1 = C_2 = C$

then

$$f = \frac{1}{2\pi R.C}$$

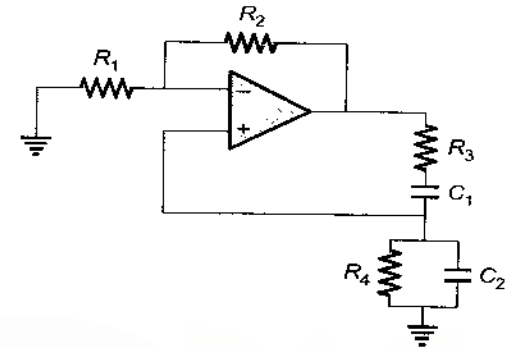

Remember:

- $\beta = \frac{1}{3}$ for oscillation.
- $R_2 \geq 2R_1$ for oscillation.

LC Oscillator


Colpitt's Oscillator

- Frequency of oscillation

$$f = \frac{1}{2\pi\sqrt{L\left(\frac{C_1 C_2}{C_1 + C_2}\right)}}$$


and

$$g_m R_C \geq \frac{C_2}{C_1}$$

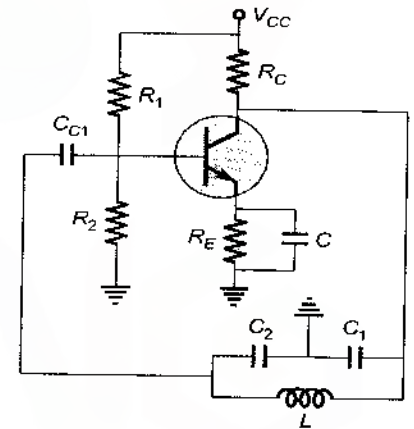

Hartley Oscillator

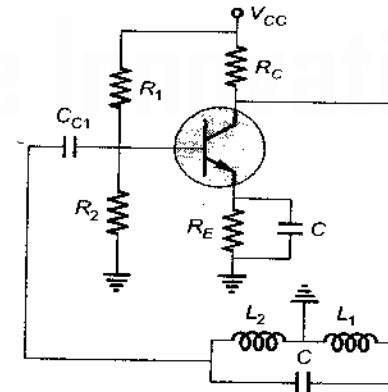- If in place of C_1, C_2 there is L_1 and L_2 and in place of L there is C then it becomes Hartley Oscillator.



- Frequency of oscillation for Hartley Oscillator is

$$f = \frac{1}{2\pi\sqrt{C(L_1 + L_2)}} \quad \text{and} \quad g_m RC \geq \frac{L_1}{L_2}$$

Clapp Oscillator

- If in Colpitt oscillator circuit inductor is replaced by a variable capacitor (C_3) then frequency of oscillation becomes

$$f = \frac{1}{2\pi\sqrt{LC_3}} \quad \text{it happens if} \quad \left(\frac{C_1}{C} \gg 1\right) \quad \text{and} \quad \frac{C_1}{C} \gg \frac{C_1}{C_2}$$


Crystal Oscillator

- It is electrical equivalent circuit is
- Series resonance frequency

$$f_s = \frac{1}{2\pi\sqrt{LC}}$$

- Parallel resonance frequency

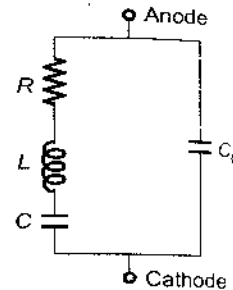
$$f_p = \frac{1}{2\pi\sqrt{LC_{eq}}} \quad \text{where,} \quad C_{eq} = \frac{CC_0}{(C + C_0)}$$



Note:

Frequency of oscillation is chosen between f_p and f_s .

Relaxation Oscillator

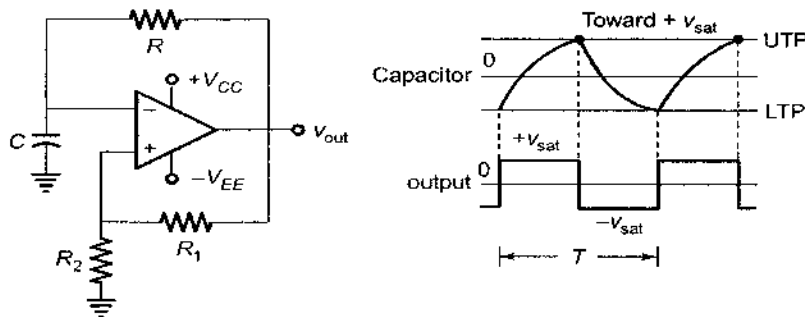

Time period of output signal

$$T = 2RC \ln\left(\frac{1+B}{1-B}\right)$$

where, R = Feedback resistance ; B = Feedback fraction


Note:

- Linear oscillator generates sinewaves utilizing resonance phenomenon.
- Non linear oscillators or function generators generate square-wave, triangular wave, pulses etc. waveforms. They use function blocks as multivibrators.
- Relaxation oscillator and UJT oscillator are non-linear oscillators.
- The oscillators which use a tunnel diode or UJT possess a current-voltage characteristic curve of negative slope within some range of operation are known as negative resistance oscillators.
- Wein's Bridge oscillator is a variable frequency oscillator.

Linear Wave Shaping Circuits

High Pass RC Circuit

Pulse response of high pass R.C circuit

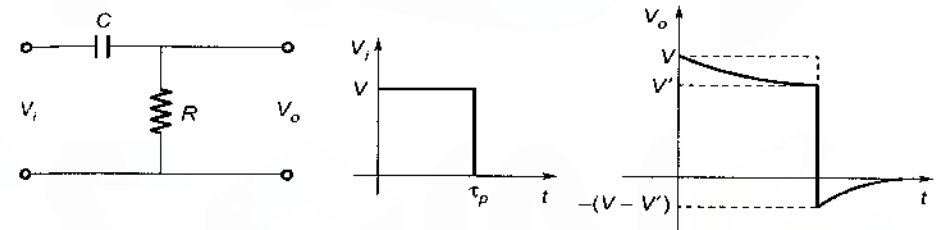

$(V - V')$ is called tilt or sag.

$$\% \text{ tilt} = \frac{V - V'}{V} \times 100\%$$


Note:

Sag or tilt will be obtained if $RC \gg \tau_p$.

- If input is a square wave of time period T then

$$\% \text{ tilt} = \frac{\pi f_L}{f} \times 100 \quad \text{where,} \quad f_L = \frac{1}{2\pi RC} \quad \text{and} \quad f = \frac{1}{T}$$

Low Pass RC Circuit

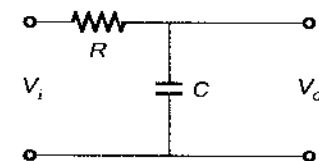


- Rise time $t_r = \frac{0.35}{f_H}$ (rise from 10% to 90%)

where, $f_H = \frac{1}{2\pi RC}$


555 Timer

The 555 is a timing circuit that can produce accurate and highly stable time delays or oscillation.

555 Timer Pin Configuration

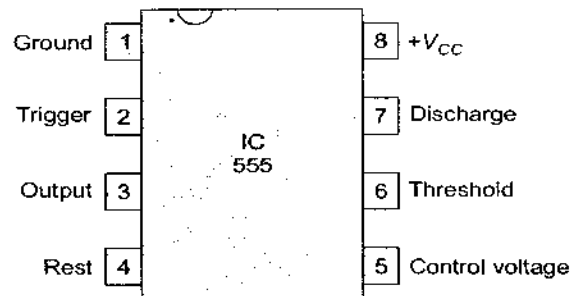


Monostable Multivibrator

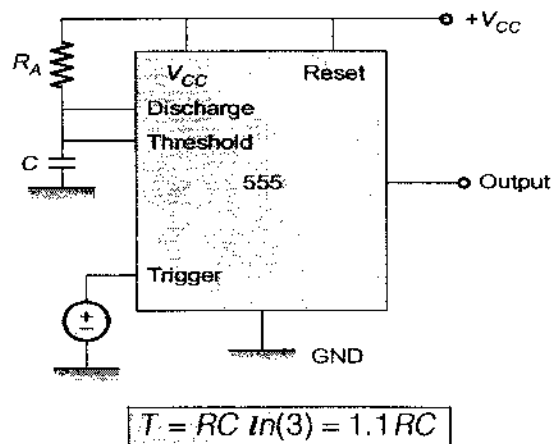

Note: The main applications of monostable multivibrator are pulse width modulator, linear ramp generator, frequency divider, pulse stretcher etc.

Astable Multivibrator

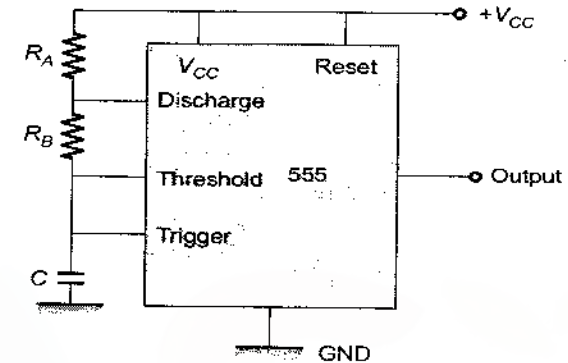

$$T = \tau \ln(2)$$

- Charging time constant, $T_C = 0.693(R_A + R_B)C$
- Discharging time constant, $T_D = 0.693 R_B C$
- Total time, $T = T_C + T_D = 0.693 (R_A + 2R_B)C$
- Duty cycle, $D = \frac{T_C}{T_C + T_D} \times 100\% = \frac{R_A + R_B}{R_A + 2R_B} \times 100\%$

Note: The main applications of astable are square-wave generator, voltage control oscillator, FSK generator, free running oscillator etc.

Remember:

- Duty cycle (D) > 50%. (Because $T_C > T_D$)
- By placing a diode parallel to R_B and making $R_A + R_f = R_B$, we get square wave output of duty cycle 50%.

■■■■■