

Lecture -14

Filters:-

N/w + to components present in the N/w filters are classified as

(I) Active Filter


(II) Passive Filter

- Active filter consist of op-amp and capacitor
- In the active filter it is possible to inc. the gain of the system
- Generally inductor is not preferred in the active filter since its size is bulky and cost is high
- Passive filter consist of LC series and parallel sections (Reactive N/w)
- Based on the operating frequency filters are classified as

- (I) LPF (II) HPF (III) BPF (IV) BEF (Band stop)
(V) All pass

LPF:-


First order

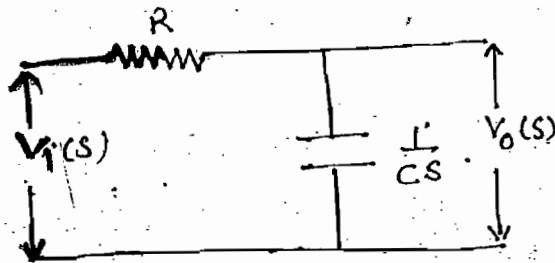


$$V_o(s) = V_i(s) \frac{\frac{1}{Cs}}{R + \frac{1}{Cs}}$$

$$\Rightarrow \boxed{\frac{V_o(s)}{V_i(s)} = \frac{1}{1 + RCs}}$$


Second order

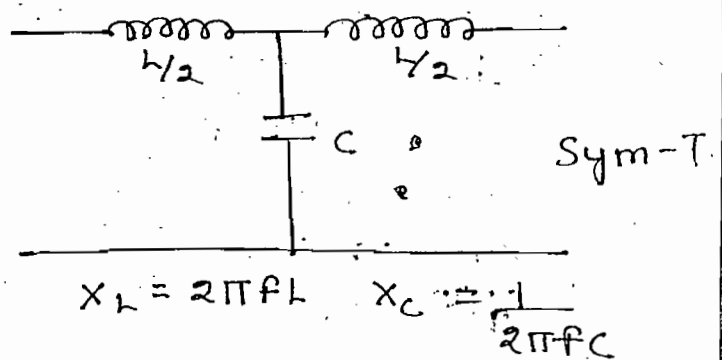
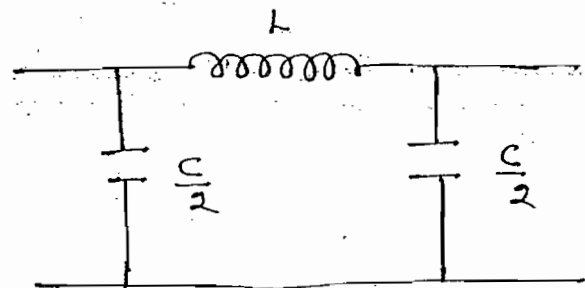
$$X_L = 2\pi fL \quad X_C = \frac{1}{2\pi fC}$$



Sym-Π

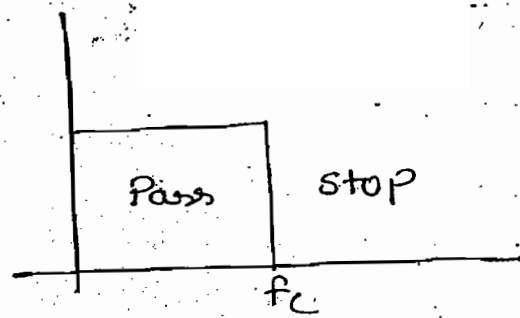


→ Inductor provide low resistance path and capacitor bypass higher frequency

L →

HPF :-

→ For lower freq. capacitor provides high impedance




First Order

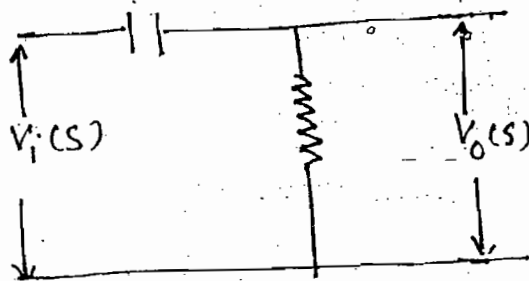


$$V_o(s) = V_i(s) \frac{R}{R + \frac{1}{Cs}}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{RCS}{RCS + 1}$$

Second Order

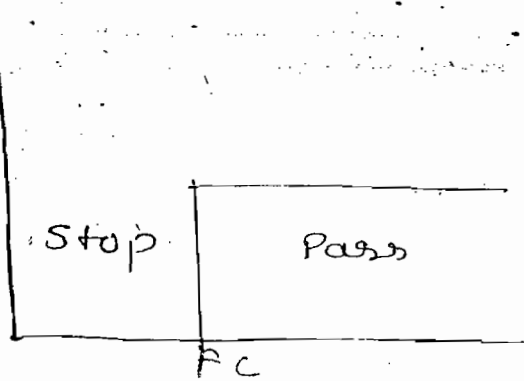
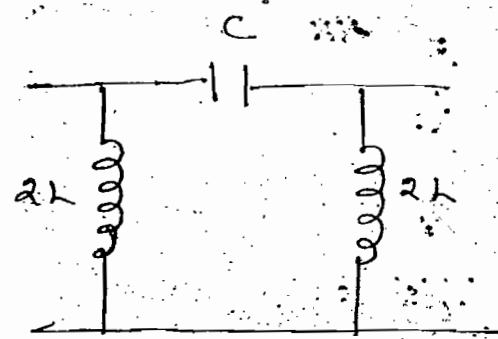
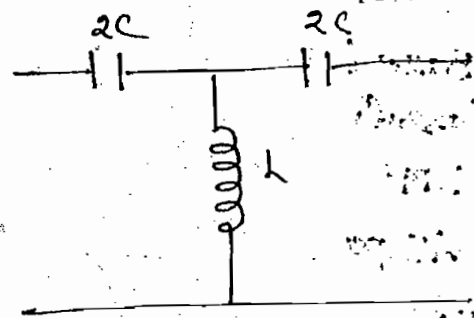


BPF! —

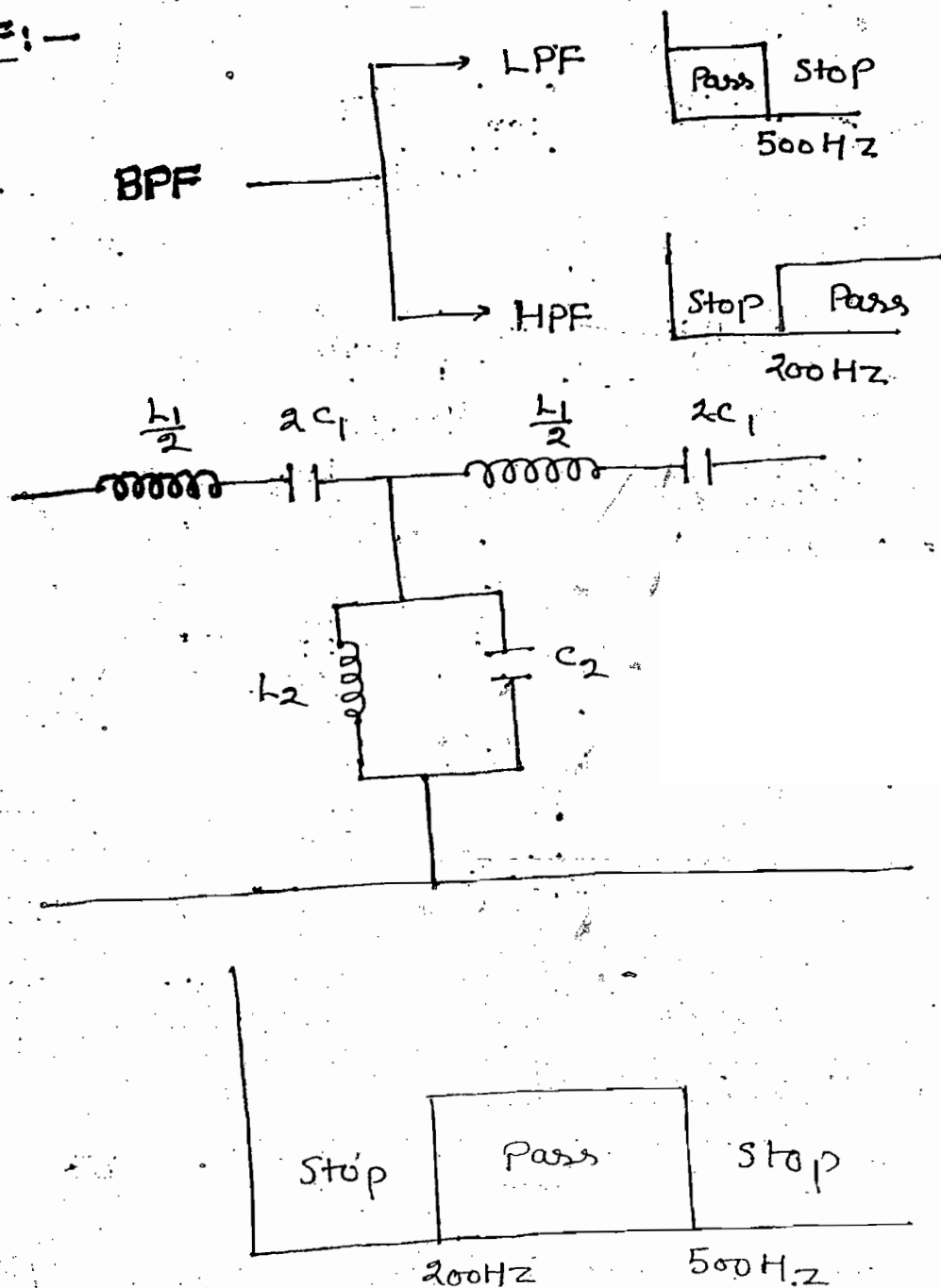

- BPF is obtained with a combination of LPF & HPF and cut-off freq. of LPF should be greater than cut-off freq. of HPF
- In the BPF first cut-off frequency is calculated w.r.t series resonance and second cut-off freq. is calculated w.r.t parallel resonance.

BEP :-

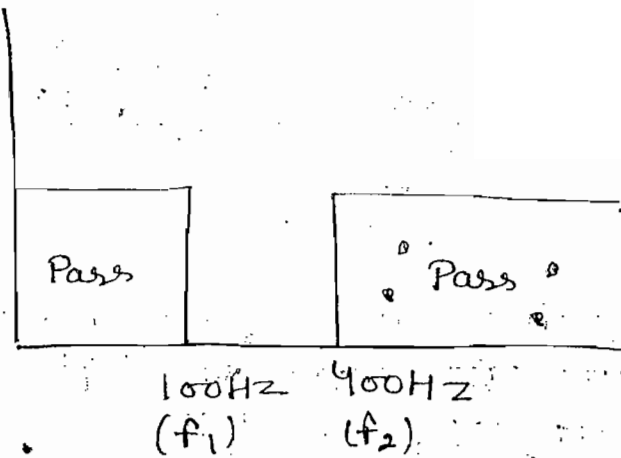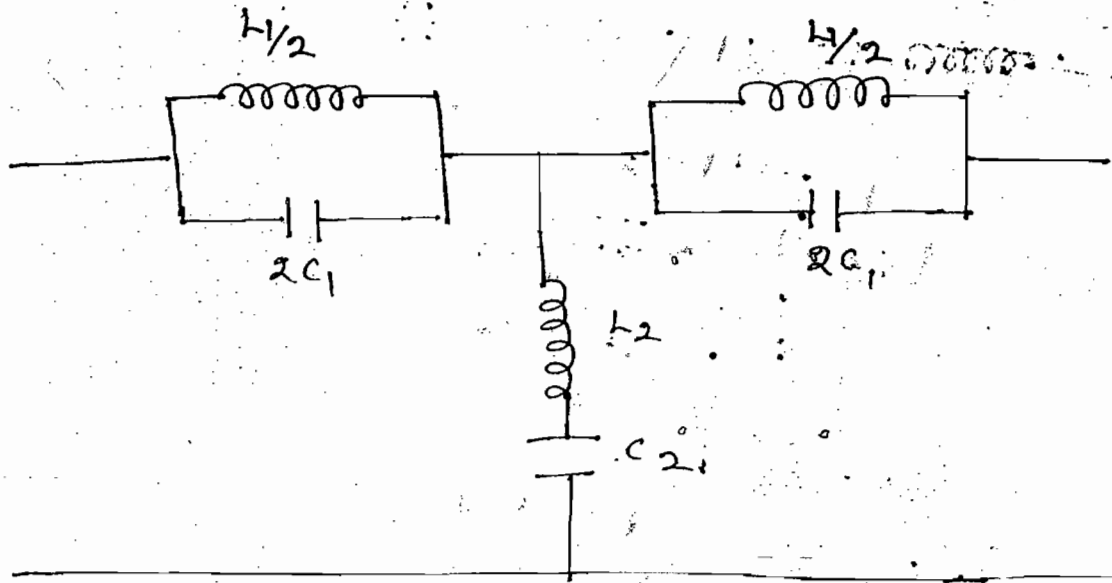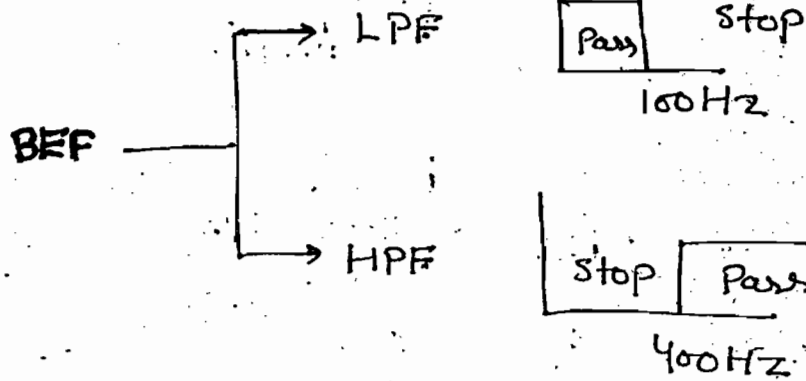

⇒ BEP is obtained with a combination of LPF and HPF and cut-off frequency of high pass filter should be greater than cut-off freq. of low pass filter

Transfer Function of first order filter:-

$\frac{1}{1+Ts}$	→ LPF
$\frac{Ts}{1+Ts}$	→ HPF
$\frac{1-Ts}{1+Ts}$	→ All pass

Note!— In all pass filter zero's are present in the right half of plane and poles are present in left half of plane

Transfer Function of second order filter:-

$$\frac{P}{s^2 + as + b} \rightarrow \text{LPF}$$

$$\frac{Ps^2 + q}{s^2 + as + b} \rightarrow \text{BEF}$$

$$\frac{Ps^2}{s^2 + as + b} \rightarrow \text{HPF}$$


$$\frac{s^2 - Ps + q}{s^2 + as + b} \rightarrow \text{All Pass}$$

$$\frac{Ps}{s^2 + as + b} \rightarrow \text{BPF}$$

Note!—

Poles and zeroes are symmetrical about $j\omega$ -axis (All pass)

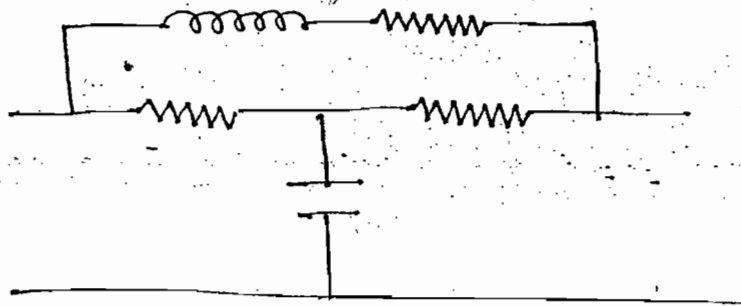Ques! Identify type of the filter of the ckt shown



Soln:-

Soln:-


$$f = 0$$

$$X_L = 2\pi fL = 0$$

$$L \rightarrow SC$$

$$X_C = \frac{1}{2\pi fC} = \infty$$

$$C \rightarrow OC$$

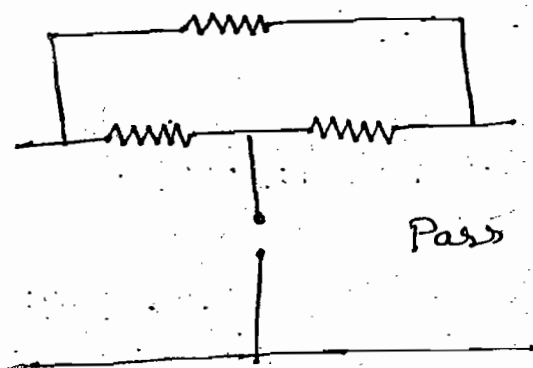


$$f = \infty$$

$$X_L = 2\pi fL = \infty$$


$$L \rightarrow OC$$

$$X_C = \frac{1}{2\pi fC} = 0$$

$$C \rightarrow SC$$

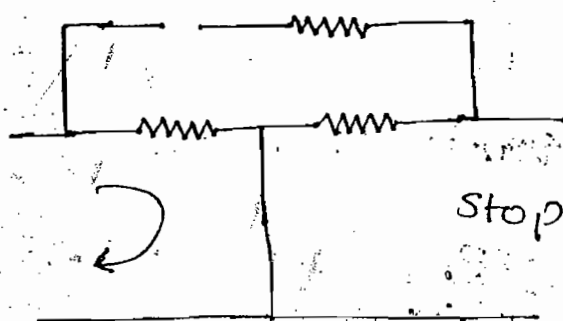

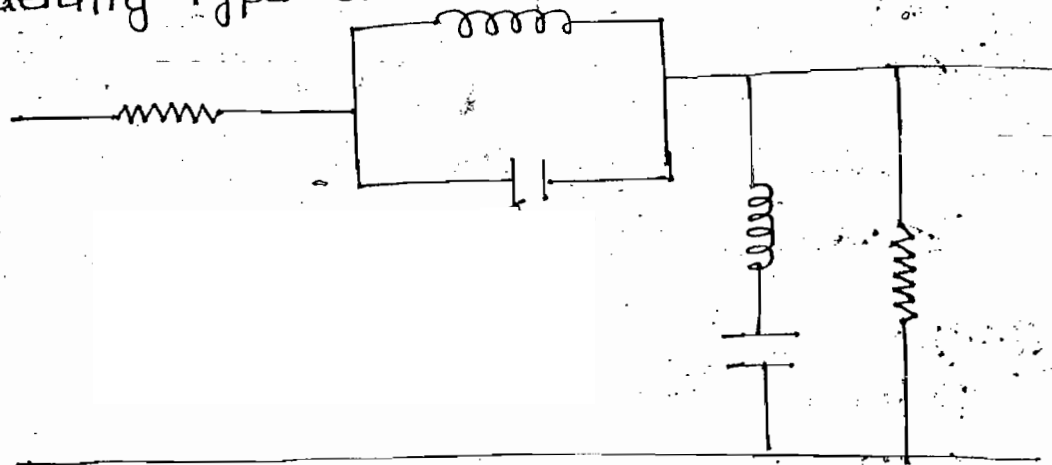Ques:- Identify type of the filter of ckt. shown.



Soln:-


$$f = 0$$

$$X_L = 2\pi fL = 0$$

$$L \rightarrow SC$$

$$X_C = \frac{1}{2\pi fC} = \infty$$

$$C \rightarrow OC$$

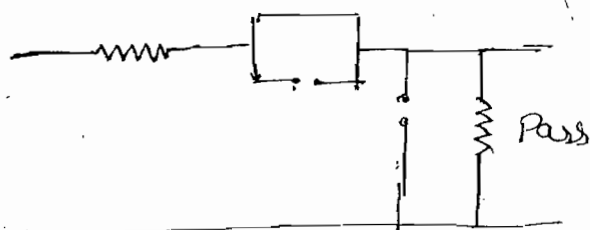


$$f = \infty$$

$$X_L = 2\pi fL = \infty$$



$$L \rightarrow OC$$

$$X_C = \frac{1}{2\pi fC} = 0$$

$$C \rightarrow SC$$

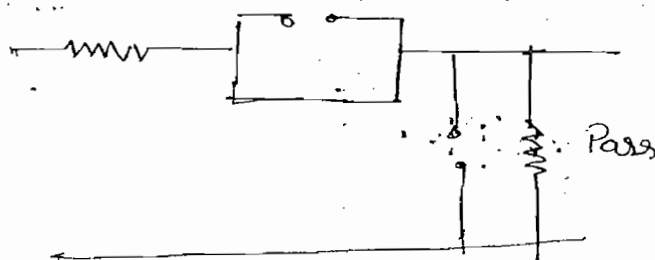

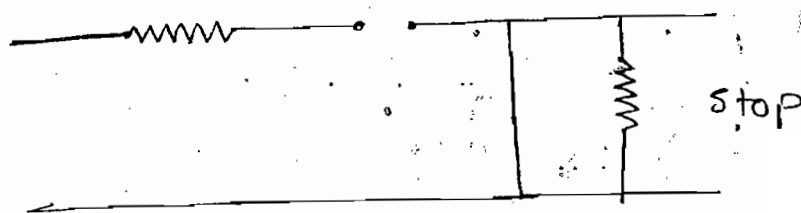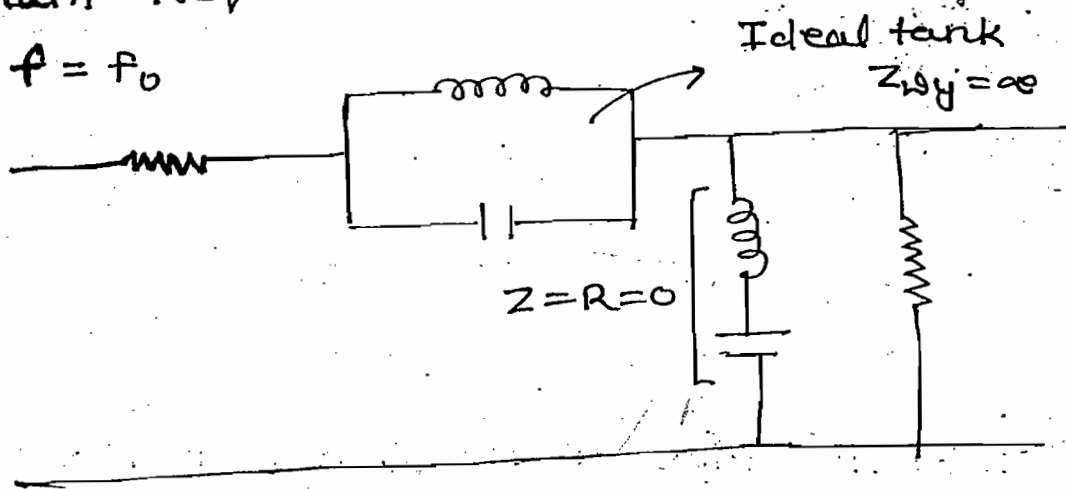For BPF & All pass filter draw eq. ckt at resonant freq.




→ BPF, Ans

Note:-

When BPF eliminates only few frequency then it is also called as Notch filter

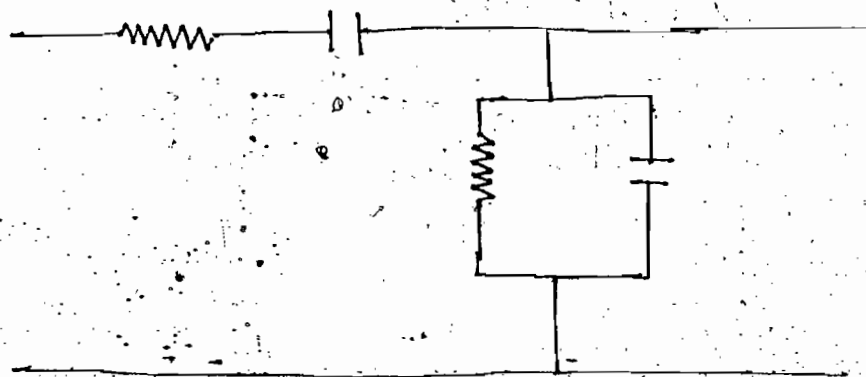ques:- Identify type of the filter of the ckt shown




Soln:- $f = 0$

$$X_L = 2\pi fL = 0$$

$h \rightarrow S.C$

$$X_C = \frac{1}{2\pi fC} = \infty$$

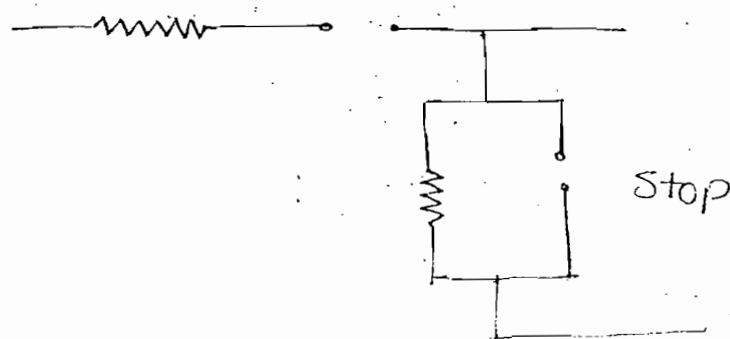

1106

$C \rightarrow O.C$


$$f = \infty$$

$$X_L = 2\pi fL = \infty$$

$$L \rightarrow \text{O.C}$$


$$X_C = \frac{1}{2\pi fC} = 0$$

$$C \rightarrow \text{S.C}$$

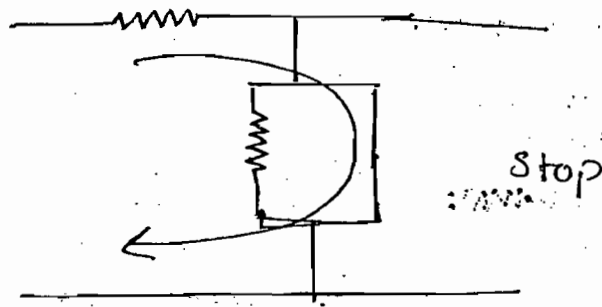

→ BPF

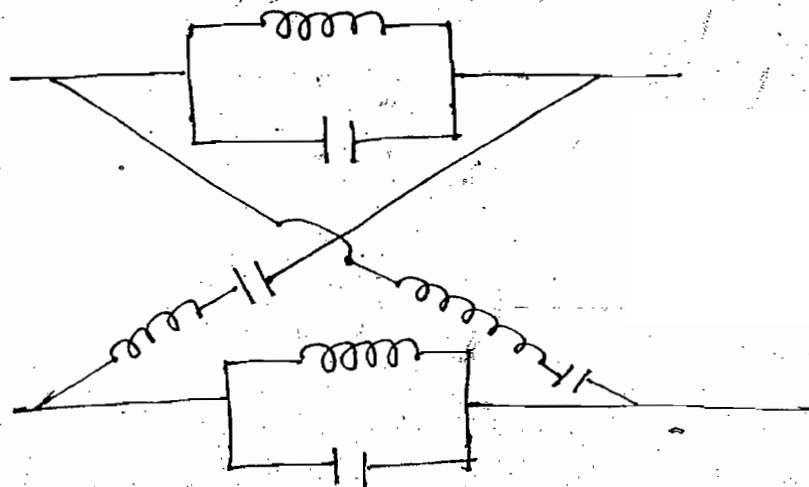
Ques:- Identify type of the filter of the ckt shown



Ans:- All pass ($f = 0, f = \infty, f = f_0$)

Magnetic Coupled Circuits:-

Case-(1):-

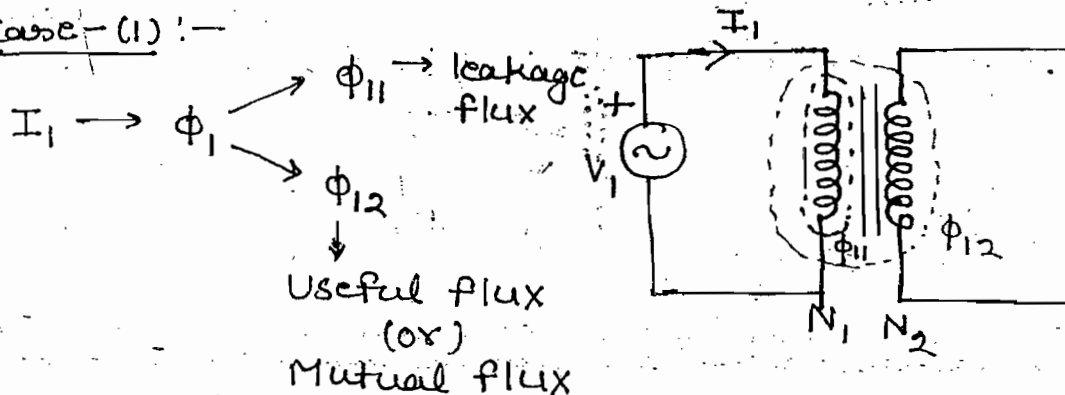

$$e_1 \propto \frac{d\phi_1}{dt}$$

$$e_1 = -N_1 \frac{d\phi_1}{dt}$$

$$e_1 = -N_1 \frac{d\phi_1}{di_1} \cdot \frac{di_1}{dt} \quad \left(L = \frac{N\phi}{i} \right)$$

$$e_1 = -L_1 \frac{di_1}{dt}$$

Self induced emf

$$e_2 \propto \frac{d\phi_{12}}{dt}$$

$$e_2 = -N_2 \frac{d\phi_{12}}{dt}$$

$$e_2 = -N_2 \frac{d\phi_{12}}{di_1} \frac{di_1}{dt}$$


$$e_2 = -M_{21} \frac{di_1}{dt}$$

Mutual Induced emf

$$\left(M_{21} = \frac{N_2 \phi_{12}}{i_1} \right)$$

Mutual inductance of second inductor w.r.t. 1

Case-(II):-

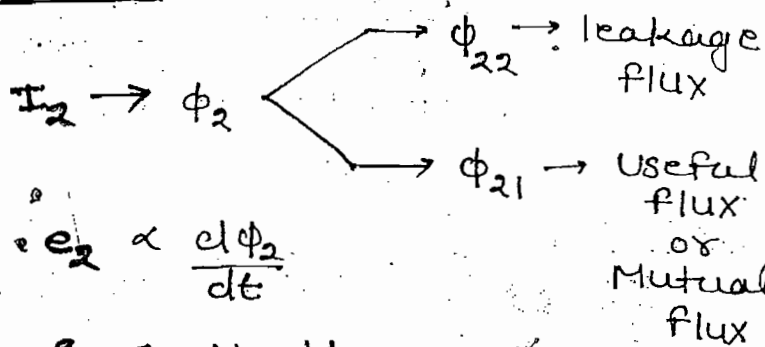


$$e_2 = -N_2 \frac{d\phi_2}{dt}$$

$$e_2 = -N_2 \frac{d\phi_2}{di_2} \frac{di_2}{dt} \quad \left(L = \frac{N\phi}{i} \right)$$

$$e_2 = -L_2 \frac{di_2}{dt}$$

Self induced emf

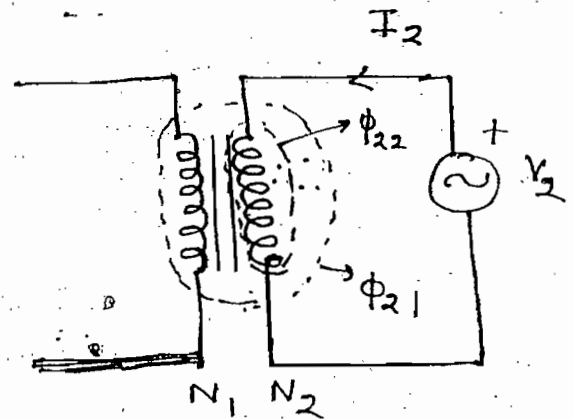

$$e_1 \propto \frac{d\phi_{21}}{dt}$$

$$e_1 = -N_1 \frac{d\phi_{21}}{dt}$$

$$e_1 = -N_1 \frac{d\phi_{21}}{di_2} \cdot \frac{di_2}{dt}$$


$$(M_{12} = \frac{N_1 \phi_{21}}{i_2})$$

$$e_1 = -M_{12} \frac{di_2}{dt}$$

Mutual induced emf


If current is flowing in any one of inductor then the sign of self & mutually induced voltage is same

Note:-

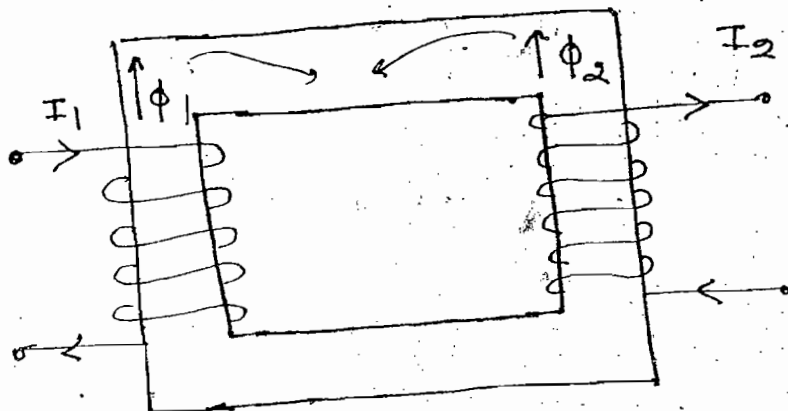


In above figure flux of the two inductors are completely closed path in opposite direction. Hence sign of mutually induced voltage is opposite to sign of self induced voltage


Dot convention:-

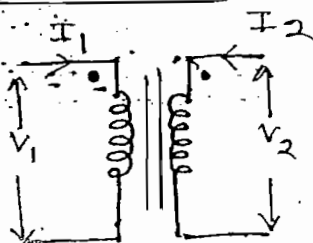


(I)

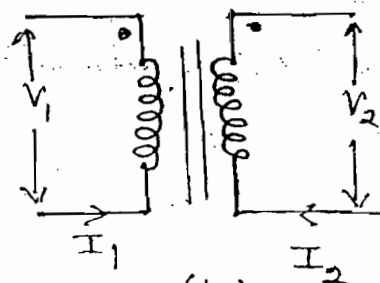

(II)

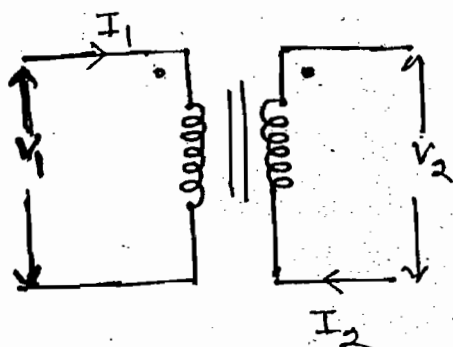

(III)

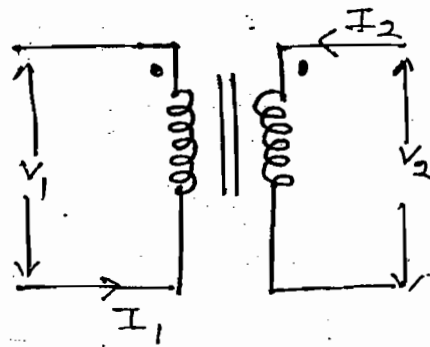

(IV)

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$M_{12} = M_{21} = M$
Valid for (I) & (II)

$$V_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

Valid for (III) & (IV)


Note:-

- When either both currents are entering or both are leaving at dotted terminal sign of mutually induced voltage is same as the sign of self induced voltage.
- When one current is entering and other current is leaving at dotted terminal sign of the mutually induced voltage is opposite to sign of self induced voltage.

Coefficient of Coupling / Coupling Factor:-

$$k = \frac{\text{Useful flux}}{\text{Total flux}}$$
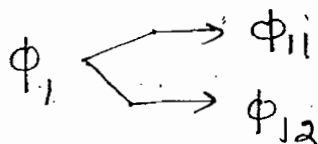
$$\rightarrow k_1 = k_2 \rightarrow \text{condition}$$



$$k_1 = \frac{\Phi_{12}}{\Phi_1}$$

14/11/21



$$k_2 = \frac{\Phi_{21}}{\Phi_2}$$

$$k = \sqrt{k_1 k_2}$$

For ideal system $k=1$ and for practical system the range of k is 0 to 1

$$M_{21} = \frac{N_2 \Phi_{12}}{i_1}$$

$$M_{12} = \frac{N_1 \Phi_{21}}{i_2}$$

$$M_{12} = M_{21} = M$$

$$M^2 = M_{12} M_{21}$$

$$\Rightarrow M^2 = \frac{N_1 \Phi_{12}}{i_1} \cdot \frac{N_2 \Phi_{21}}{i_2} \quad \text{--- (i)}$$

$$\Phi_{12} = k_1 \Phi_1 \quad \text{--- (ii)}$$

$$\Phi_{21} = k_2 \Phi_2 \quad \text{--- (iii)}$$

substitute eq- (ii) & (iii) in eq- (i)

$$M^2 = k_1 k_2 \frac{N_1 \Phi_1}{i_1} \cdot \frac{N_2 \Phi_2}{i_2}$$

$$M^2 = k^2 L_1 L_2$$

$$\Rightarrow \boxed{M = k \sqrt{L_1 L_2}}$$

$$V = L_1 \frac{di}{dt} + M \frac{di}{dt} + L_2 \frac{di}{dt} + M \frac{di}{dt}$$

$$L_{eq} \frac{di}{dt} = (L_1 + L_2 + 2M) \frac{di}{dt}$$

$$L_{eq} = L_1 + L_2 + 2M$$

→ Series Aiding

→ Series Opposing:-





$$L_{eq} = L_1 + L_2 - 2M$$

→ Parallel Aiding:-


$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$

→ Parallel Opposing:-
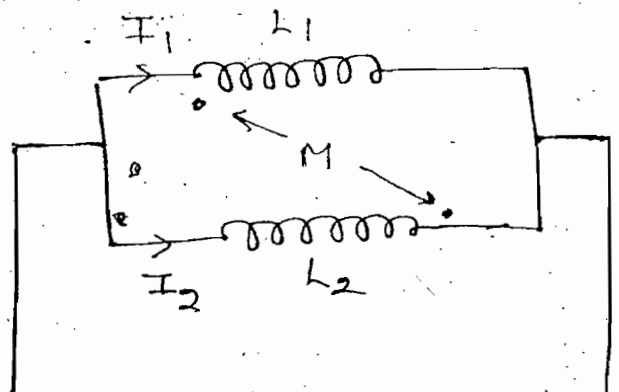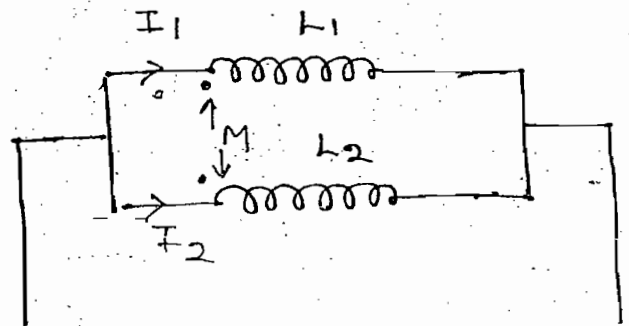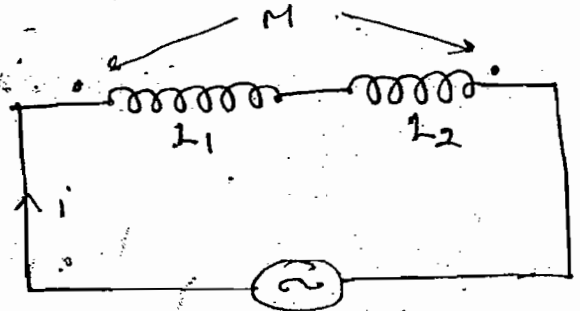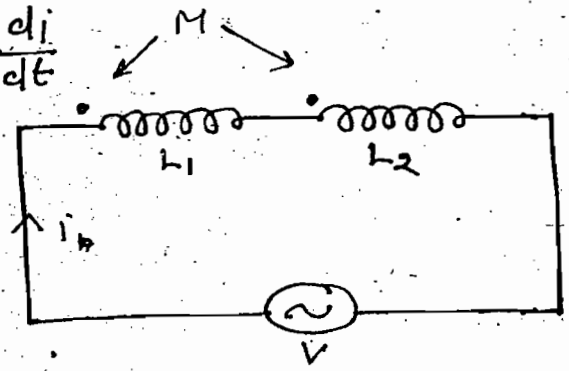
$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$



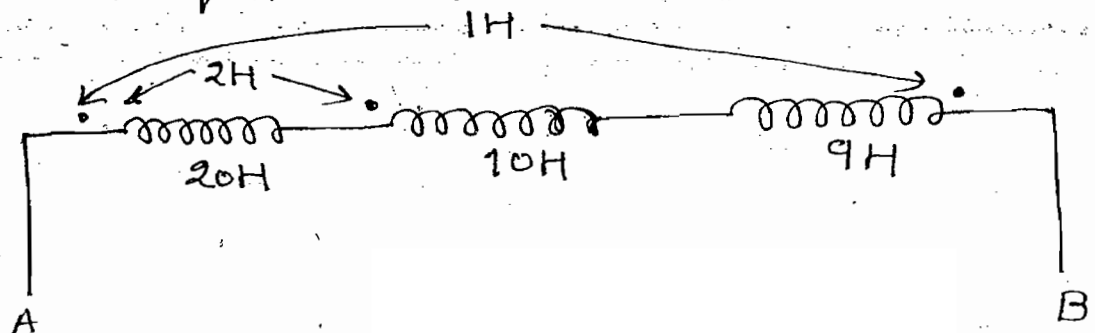
Ques:- Find equivalent inductance w.r.t A and B



Soln:- $L_{eq} = L_1 + L_2 + L_3 \pm 2M_1 \pm 2M_2 \pm 2M_3$

$\Rightarrow L_{eq} = 20 + 10 + 9 + 2(2) + 0 - 2(1)$

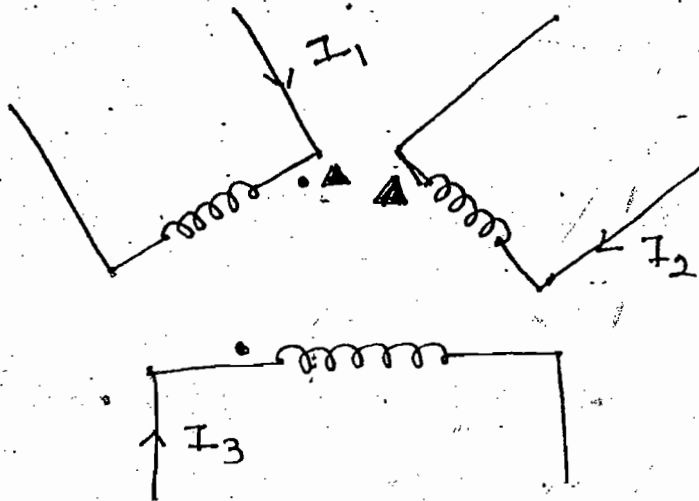ques:- Develop inductance matrix of the figure shown




• 1H
▲ 2H

Soln:- Diagonal points denotes self inductance

$$L = \begin{bmatrix} L_{11} & L_{12} & L_{13} \\ L_{21} & L_{22} & L_{23} \\ L_{31} & L_{32} & L_{33} \end{bmatrix}$$

$$L = \begin{bmatrix} 15 & -2 & 1 \\ -2 & 20 & 0 \\ 1 & 0 & 10 \end{bmatrix}$$

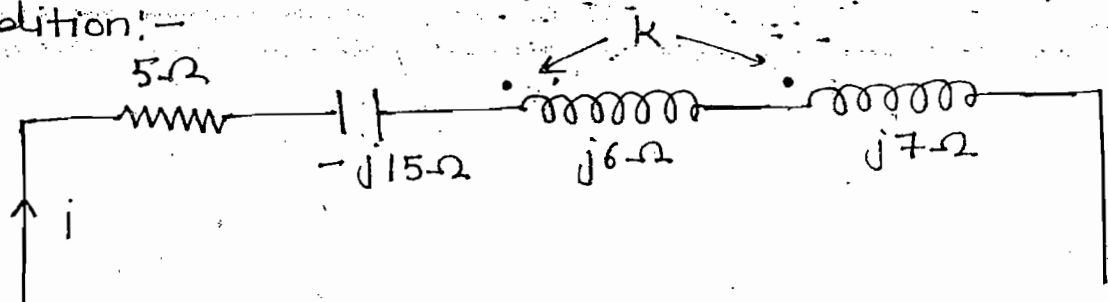ques:- Find the value of K under resonance condition:-



Soln:-

$$2\pi f (L_{eq} = L_1 + L_2 + 2M)$$

$$M = k \sqrt{L_1 L_2}$$

$$\Rightarrow 2\pi f M = 2\pi f k \sqrt{L_1 L_2}$$



$$X_M = k \sqrt{X_1 X_2}$$

$$X_{eq} = X_1 + X_2 + 2X_M$$

$$\Rightarrow X_{eq} = X_1 + X_2 + 2k \sqrt{X_1 X_2}$$

$$\Rightarrow 15 = 6 + 7 + 2k \sqrt{6 \times 7}$$
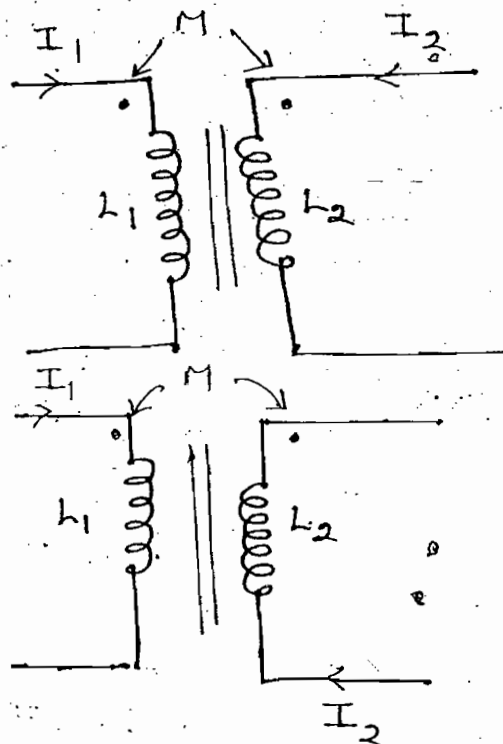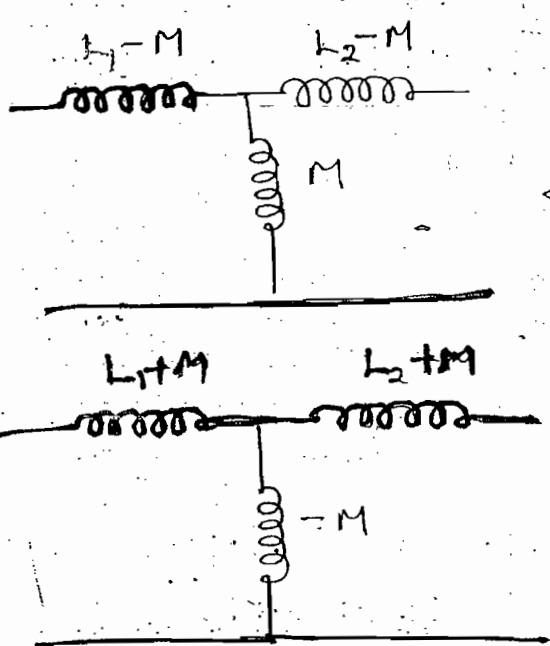
$$\Rightarrow \boxed{k = \frac{1}{\sqrt{42}}} \quad \text{Ans}$$




$$\boxed{W = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 \pm M I_1 I_2}$$


+ $\rightarrow$ fig-(i) -ve $\rightarrow$ fig(ii)

Energy stored in the coupled coils.


Ques:- Find L_{eq} w.r.t A and B

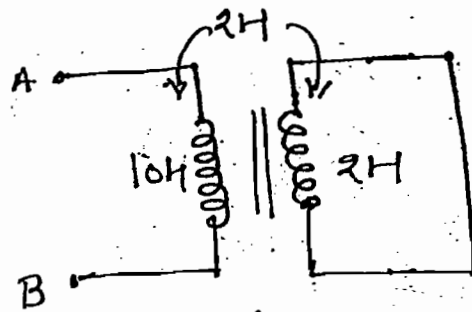

Soln:-

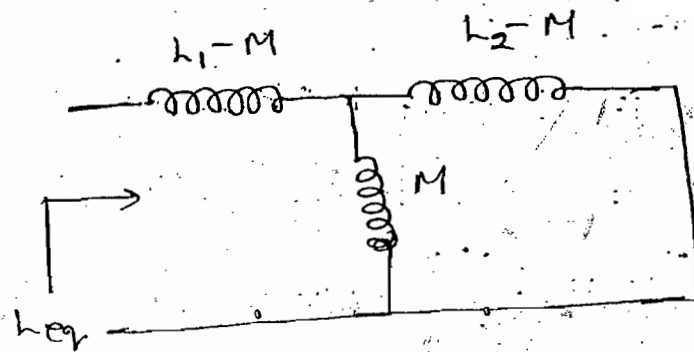
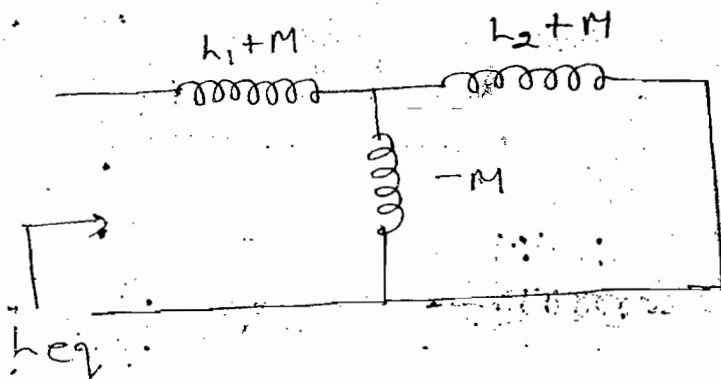
$$L_{eq} = L_1 - M + \frac{M(L_2 - M)}{L_2 - M + M} = L_1 - \frac{M^2}{L_2}$$



$$L_{eq} = (L_1 + M) + \frac{(-M)(L_2 + M)}{L_2 + M - M}$$

$$L_{eq} = L_1 - \frac{M^2}{L_2}$$

$$\Rightarrow L_{eq} = 10 - \frac{2^2}{2} = 8 \text{ H, Ans}$$