

Steady State AC Circuits :-

$$V(t) = V_m \sin \omega t$$

V_m = Peak or Max. value

ω = Angular frequency
 \rightarrow rad/sec



ωt = Argument - rad

$$\omega T = 2\pi$$


$$\Rightarrow T = \frac{2\pi}{\omega} \text{ sec.}$$

$$f = \frac{1}{T}$$
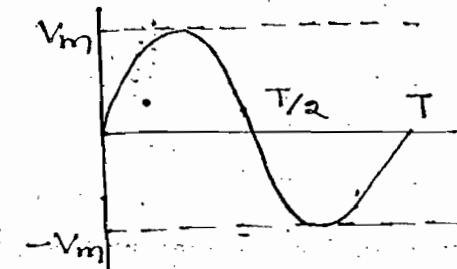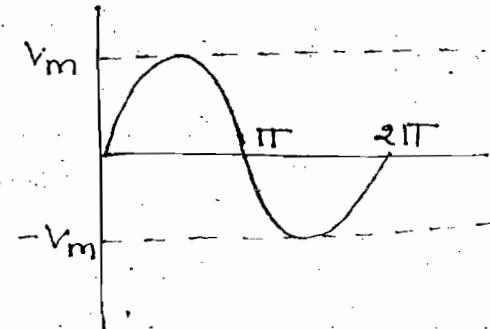
$$f = \frac{\omega}{2\pi} \text{ Hz or cycles/sec.}$$




$$V(t) = V_m \sin \omega t$$

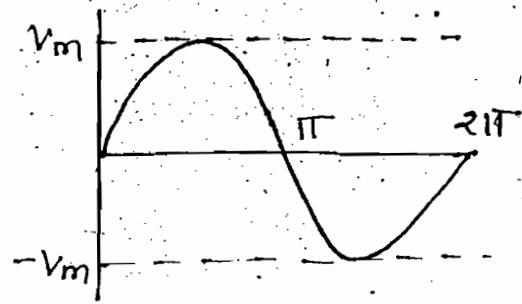


$$V(t) = V_m \sin(\omega t + \theta)$$

→ Leading

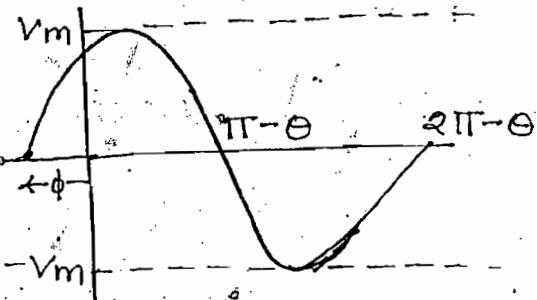


$$V(t) = V_m \sin(\omega t - \theta)$$

→ Lagging

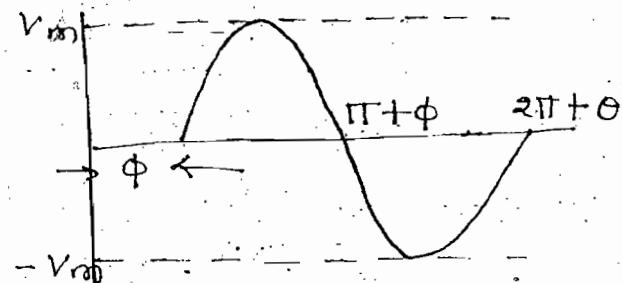

RMS Value :-

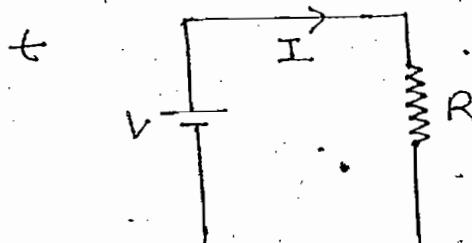


$$P = I^2 R$$

$$W = I^2 R t$$

↓ DC

Heat

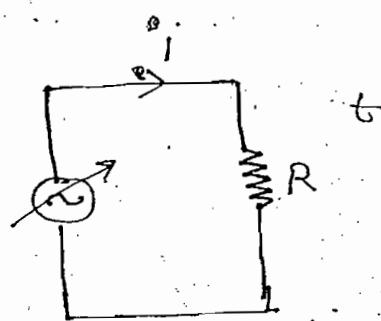

$$P = i^2 R$$

$$W = i^2 R t$$

↓ AC

Heat

$$W_{AC} = W_{DC}$$

- RMS value is defined based on heating effect of the waveform.
- The voltage at which heat dissipation in A.C circuit is equal to heat dissipation in D.C circuit is called as V_{RMS} provided both AC and DC circuit having equal value of resistance and operated for same time.


$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V^2 dt}$$

$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T V^2 dt}$$

Lecture - 4

ques:- Find RMS value of following waveforms

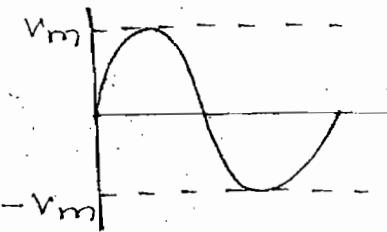
$$(I) V_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V^2 dt}$$



$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (V_m \sin \omega t)^2 dt}$$

$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_m^2 \left(\frac{1-\cos 2\omega t}{2}\right) dt}$$

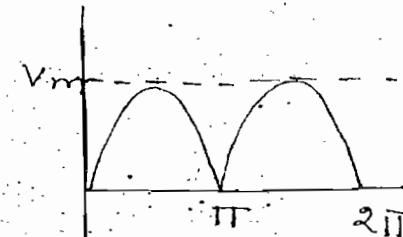
$$\Rightarrow V_{RMS} = \frac{V_m}{\sqrt{2}}$$



$$(II) V_{RMS} = \frac{V_m}{\sqrt{2}}$$




$$V_{RMS} = \frac{V_m}{2}$$

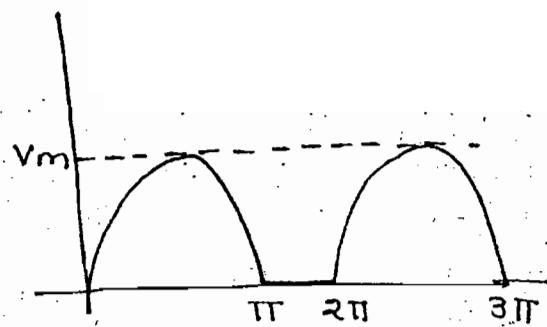

$$V_{RMS} = \frac{V_m}{\sqrt{2}}$$

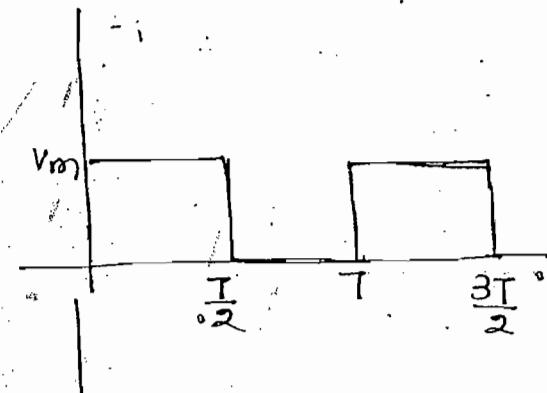
$$V_{RMS} = \sqrt{\frac{1}{T} \left[\int_0^{T/2} V_m^2 dt + \int_{T/2}^T 0 dt \right]}$$



$$V_{RMS} = \frac{V_m}{\sqrt{2}}$$

Note: RMS value is independent
on the position of waveform.


But it depends on the shape
of Waveform

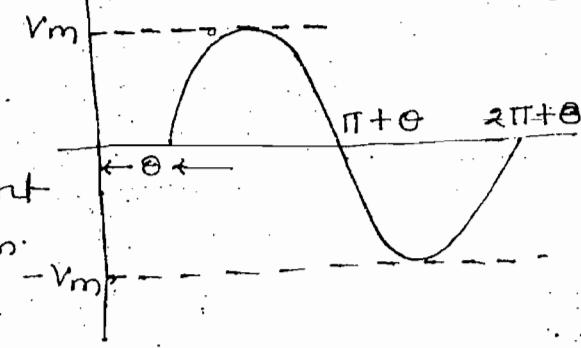


$$V_{RMS} = \frac{V_m}{\sqrt{3}}$$

$$0 < t < T \quad y = mx$$

$$\Rightarrow V = \frac{V_m}{T} t$$

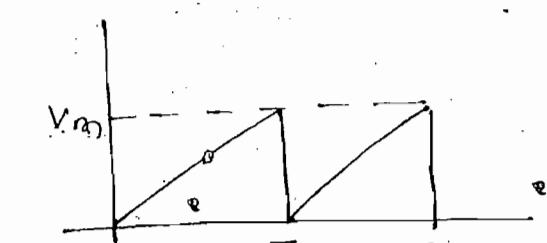


$$V_{RMS} = V_m$$

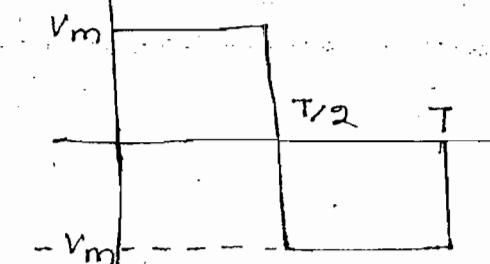

$$\rightarrow V_{RMS} = \sqrt{\frac{1}{T} \int_0^T v^2 dt}$$

$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T \left(\frac{V_m t}{T}\right)^2 dt}$$
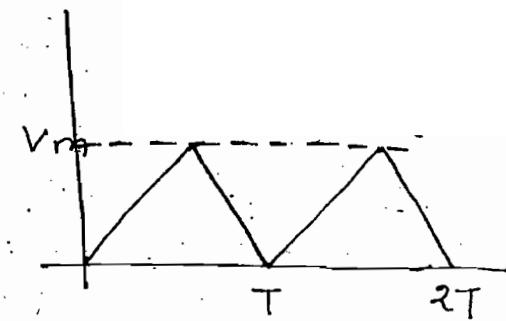
$$\Rightarrow V_{RMS} = \frac{V_m}{\sqrt{3}}$$




$$\rightarrow 0 < t < 2$$

$$y = m x$$

$$m = \frac{y_2 - y_1}{x_2 - x_1} = \frac{10 - 0}{2 - 0} \\ = 5$$

$$v = 5t$$

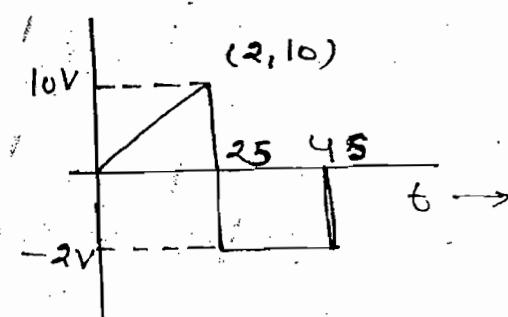


$$V_{RMS} = \sqrt{\frac{1}{4} \left[\int_0^2 (5t)^2 dt + \int_2^4 (-2)^2 dt \right]}$$

$$\Rightarrow V_{RMS} = \sqrt{\frac{1}{4} [25(t^{3/2})_0^2 + (4t)_2^4]}$$

$$\Rightarrow V_{RMS} = 4 - \dots$$

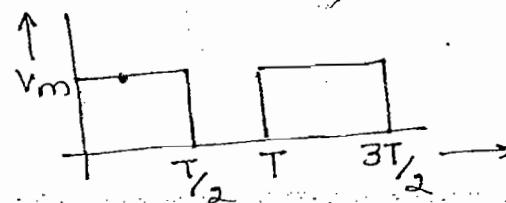ques: Find power dissipation in the resistor for the given voltage waveform



$$(a) P_{av} = \frac{P_{peak}}{\sqrt{2}}$$

$$(b) P_{av} = \frac{P_{peak}}{2}$$

$$(c) P_{av} = P_{peak}$$

Soln:- B. $P_{peak} = \frac{V_m^2}{R}$

$$(d) P_{av} = \frac{P_{peak}}{\sqrt{3}}$$

$$P_{av} = \frac{V_{RMS}^2}{R} = \frac{(V_m/\sqrt{2})^2}{R} = \frac{V_m^2}{2R} = \frac{P_{peak}}{2}$$

M&M

Note:-

$$\rightarrow P_{RMS} = \frac{V_{RMS}^2}{R}$$

**

→

$$\frac{P_{AC}}{P_{RMS}} = \frac{I_{av}^2 R}{\frac{I^2_{RMS} R}{2}}$$

ques:- Find RMS value for the following function

$$V(t) = 3 + \sin 3t + \cos t$$

Soln:-


$$V_{RMS} = \sqrt{V_{RMS_1}^2 + V_{RMS_2}^2 + V_{RMS_3}^2 + \dots + V_{RMS_n}^2}$$

[Used when different waves present]

$$\Rightarrow V_{RMS} = \sqrt{(3)^2 + \left(\frac{1}{\sqrt{2}}\right)^2 + \left(\frac{1}{\sqrt{2}}\right)^2}$$


$$\Rightarrow V_{RMS} = \sqrt{10}$$

Average Value:-

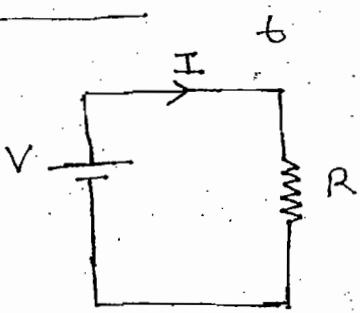

$$I = \frac{V}{R}$$

$$Q = It \rightarrow DC$$

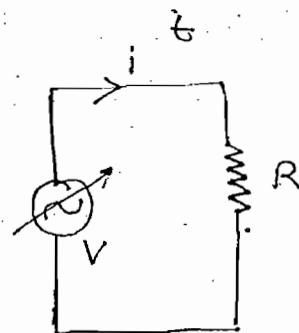


$$i = \frac{V}{R}$$

$$Q = it \rightarrow AC$$

$$Q_{AC} = Q_{DC}$$

- Average value is defined based on charge transfer in the circuit
- The voltage at which charge transfer in AC circuit is equal to charge transfer in DC circuit is called as V_{avg} . provided both AC and DC circuit having equal value of resistance and operated for same time.

Symmetrical Wave :-

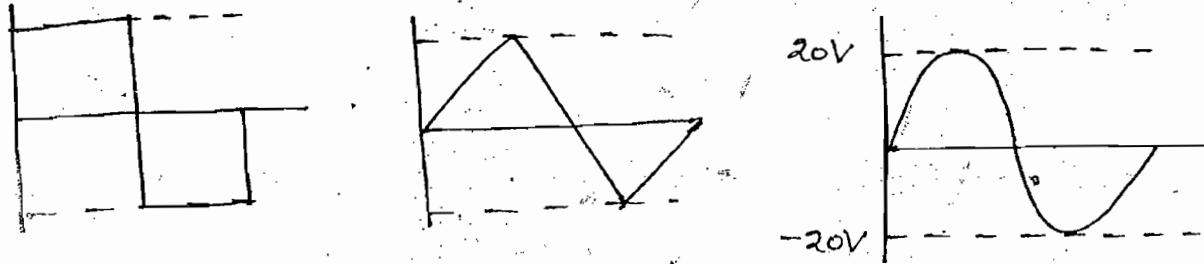

$$\text{Form factor} = \frac{V_{RMS}}{V_{avg}}$$


- Avg. Value for complete unsymmetrical wave = 0
- Hence we can find Average value only for half cycles for symmetrical waveform

$$V_{avg} = \frac{1}{\pi} \int_0^{\pi} V dt$$

{ For current and voltage waveform

Unsymmetrical Wave :-

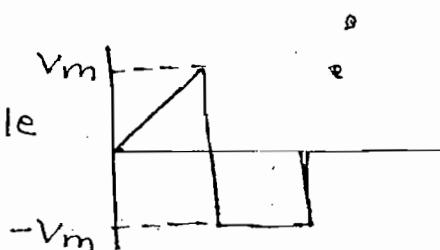- Finding average value of V_m unsymmetrical wave angle of complete cycle is considered



$$V_{avg} = \frac{1}{2\pi} \left[\int_0^{\pi} V dt + \int_{\pi}^{2\pi} V dt \right]$$

ques:- Find Avg. value of following waveforms

$$\rightarrow V_{av} = \frac{1}{\pi} \int_0^{\pi} v dt$$

$$V_{av} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t dt$$






$$\Rightarrow V_{av} = \boxed{\frac{2V_m}{\pi}}$$

$$\rightarrow V_{av} = \frac{V_m}{2}$$

$$\rightarrow V_{av} = \frac{2V_m}{\pi}$$


$$\rightarrow V_{av} = \frac{V_m}{\pi}$$

$$\rightarrow V_{RMS} = V_{av} = V_m$$

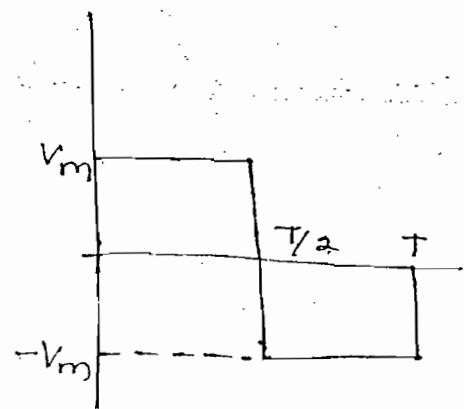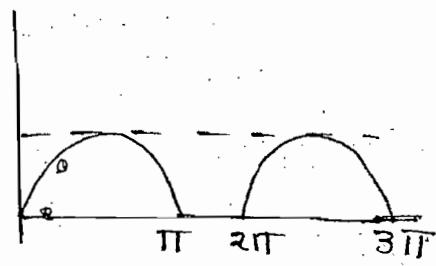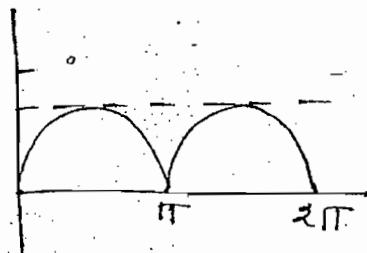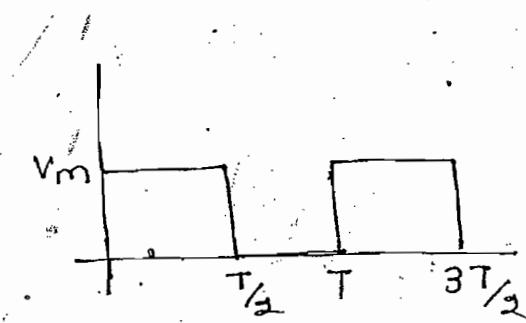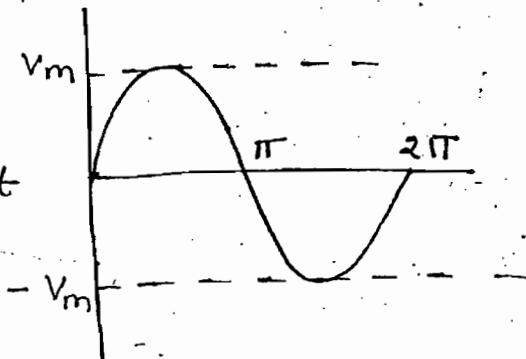


$$\rightarrow V_{av} = \frac{1}{4} \left[\int_0^2 10dt + \int_2^4 20dt \right] = 20V$$


$$V_{av} = 15$$

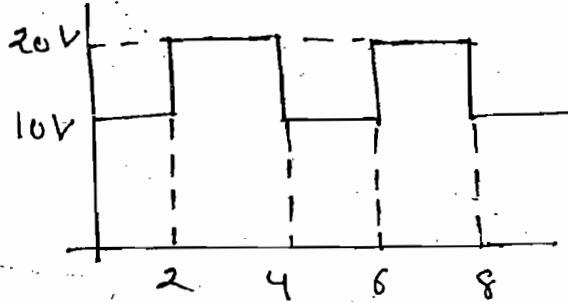


$$\rightarrow V_{av} = \frac{V_m}{2}$$

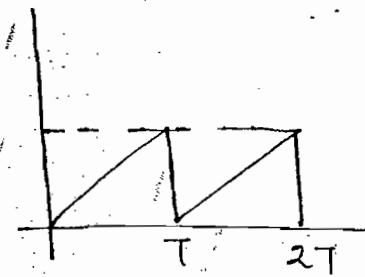

$$\rightarrow V_{av} = \frac{V_m}{2}$$

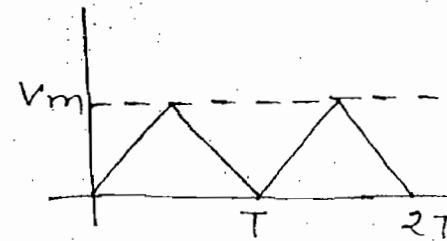

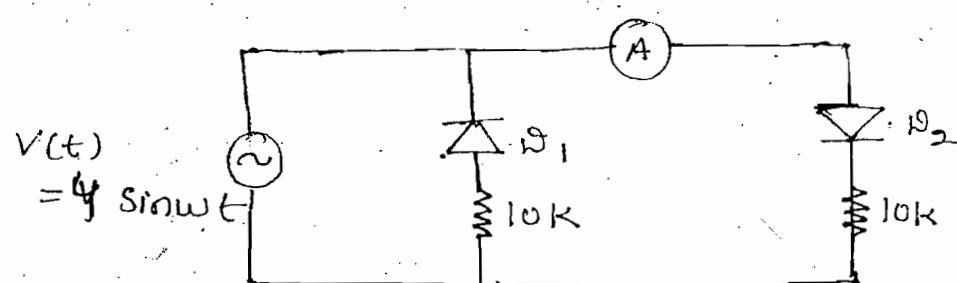ques) - When the circuit is having ideal diodes and avg. value of indicating ammeter. Find reading of ammeter



$$\text{Soln:- } V_{av} = \frac{V_m}{\pi} = \frac{4}{\pi}$$

$$I_{av} = \frac{V_{av}}{10 \times 10^3} = \frac{4/\pi}{10 \times 10^3}$$

$$\Rightarrow I_{av} = \frac{0.4}{\pi} \text{ mA}$$

Note:-

$$\text{Form factor} = \frac{V_{\text{RMS}}}{V_{\text{av}}} = \frac{\frac{V_m}{\sqrt{2}}}{\frac{2V_m}{\pi}} = 1.11$$

→ For sine wave





$$\text{Peak factor} = \frac{V_m}{V_{\text{RMS}}} = \frac{V_m}{\frac{V_m}{\sqrt{2}}} = \sqrt{2}$$

Power System :-

[11 kV, 33 kV, 66 kV, 132 kV, 220 kV] → basis of form factor

→ To justify above shape of waveform form factor and peak factor concepts are introduced

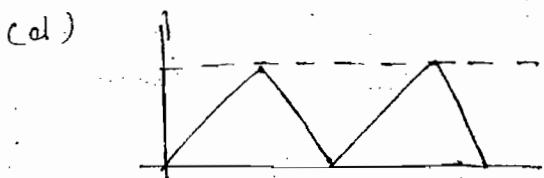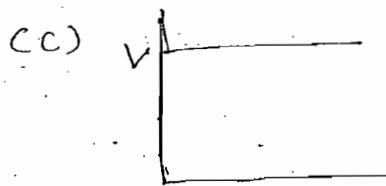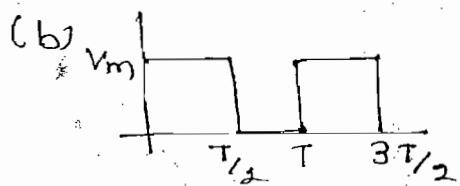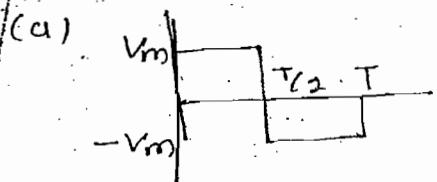Ques:- Which of the following waveforms have
form factor = peak factor?



Soln:- (a) $V_{\text{RMS}} = V_{\text{av}} = V_m$

Form factor = 1

Peak factor = 1

(b) $V_{\text{RMS}} = \frac{V_m}{\sqrt{2}}$, $V_{\text{av}} = \frac{V_m}{2}$

$$\text{Form factor} = \frac{V_{\text{RMS}}}{V_{\text{av}}} = \sqrt{2}$$

$$\text{Peak factor} = \frac{V_m}{V_{\text{RMS}}} = \sqrt{2}$$

(c) $V_{\text{RMS}} = V_m = V_{\text{av}}$

= V

Form factor = 1

Peak factor = 1

(d) $V_{\text{RMS}} = \frac{V_m}{\sqrt{3}}$

$$V_{\text{av}} = \frac{V_m}{2}$$

$$\text{Form factor} = 2/\sqrt{3}$$

$$\text{Peak factor} = \sqrt{3}$$

AC Source Across Resistor:-

$$i(t) = \frac{V(t)}{R}$$


$$i(t) = \frac{V_m}{R} \sin \omega t$$

$$\Rightarrow i(t) = I_m \sin \omega t$$


$$P(t) = V(t) i(t)$$

$$P(t) = V_m \sin \omega t I_m \sin \omega t$$
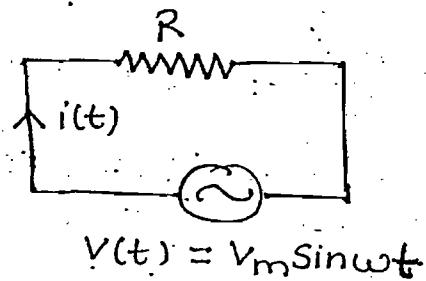
$$P(t) = \frac{V_m I_m}{2} (1 - \cos 2\omega t)$$



$$V(t) = V_m \sin \omega t$$

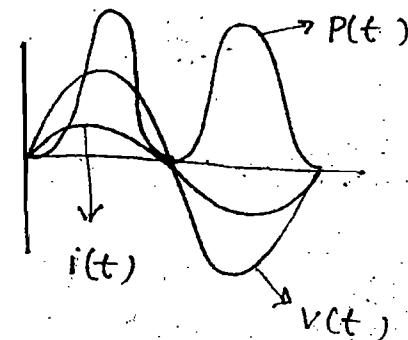

$$P_{av} = \frac{1}{2\pi} \int_0^{2\pi} P(t) d\omega t$$

$$\Rightarrow P_{av} = \frac{V_m I_m}{2} = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} = V_{RMS} I_{RMS}$$

e.g! — $f = 50 \text{ Hz}$ or c/sec

$$\Rightarrow f_p = 100 \text{ Hz} \quad (\text{Power of frequency})$$

→ When voltage or current completes one cycle then power completes two cycles.


AC Source across Inductor:-

$$V = L \frac{di}{dt}$$

$$\therefore V(t) = L \frac{d}{dt} (I_m \sin \omega t)$$

$$V(t) = \omega L I_m \cos \omega t \quad (X_L = \omega L)$$

$$V(t) = V_m \sin(\omega t + 90^\circ)$$

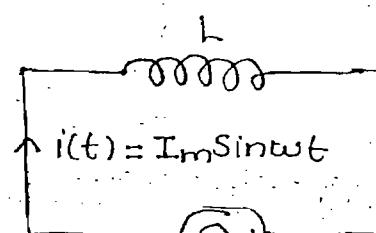

$$\begin{aligned}
 P &= I^2 R = VI \cos \theta \\
 Q_L &= I^2 X_L = VI \sin \theta \\
 S &= I^2 Z = VI^* \rightarrow \text{conjugate}
 \end{aligned}$$

eg:- $V = 10 \angle 40^\circ$ $i = 5 \angle 15^\circ$

$$S = Vi$$

$$\Rightarrow S = 10 \angle 40^\circ \ 5 \angle 15^\circ$$

$$\Rightarrow S = 50 \angle 55^\circ$$


Wrong

$$S = Vi^*$$

$$\Rightarrow S = 10 \angle 40^\circ \ 5 \angle -15^\circ$$

$$\Rightarrow S = 50 \angle -25^\circ$$

Correct

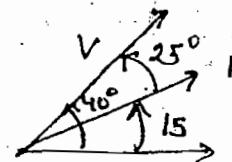



R-C Series Circuit :-

By KVL

$$V = V_R \angle 0^\circ + V_C \angle -90^\circ$$


$$\Rightarrow IZ = IR - jIX_C$$

$$\Rightarrow Z = R - jX_C$$

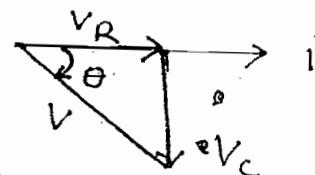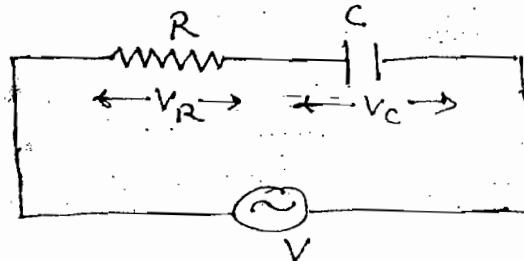


$$V = \sqrt{V_R^2 + V_C^2}$$
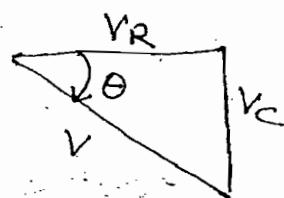
$$\theta = \tan^{-1} \left(\frac{-V_C}{V_R} \right)$$



$$Z = \sqrt{R^2 + X_C^2}$$

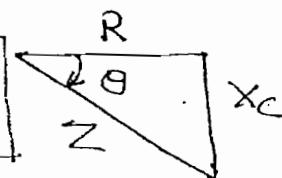
$$\theta = \tan^{-1} \left(\frac{-X_C}{R} \right)$$



$$S = \sqrt{P^2 + Q^2}$$

$$\theta = \tan^{-1} \left(-\frac{Q_c}{P} \right)$$

$$I^2 R = P$$

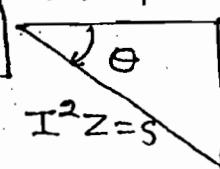


$$Q_c = I^2 X_c$$

Power Factor :-

$$\text{Power Factor} = \cos \theta = \frac{V_R}{V} = \frac{R}{Z} = \frac{P}{S} \rightarrow \text{leading}$$

ques:- Find voltage across inductor

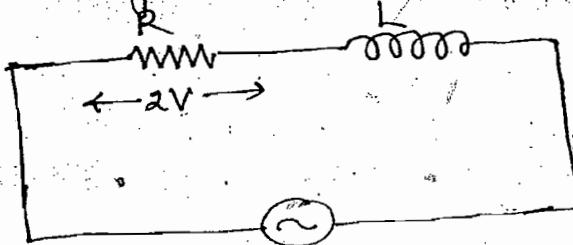


$$20V \text{ (P-P)}$$

Soln:-

$$V_m = 10$$

$$V_{RMS} = \frac{10}{\sqrt{2}} = V$$

$$V = \sqrt{V_R^2 + V_L^2}$$

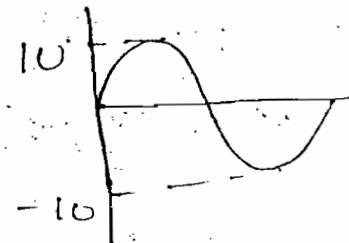

$$\Rightarrow \frac{10}{\sqrt{2}} = \sqrt{2^2 + V_L^2} \Rightarrow V_L = \sqrt{46} V$$

ques:- Find circuit element for given voltage and current equations



$$V(t) = 9 \sin(t + 45^\circ)$$

$$i(t) = 3 \sin(t - 45^\circ)$$

Soln:-

$$X_L = \frac{V}{i}$$

$$X_L = \frac{9/\sqrt{2}}{3/\sqrt{2}}$$

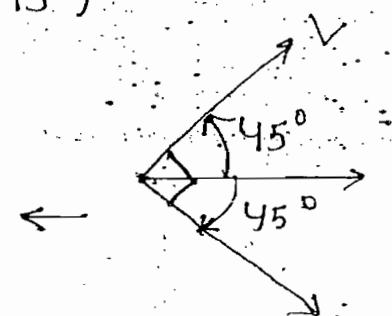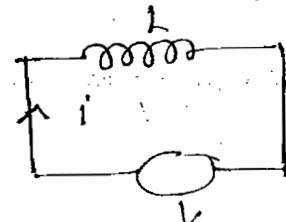

$$\Rightarrow X_L = 3 = \omega L \Rightarrow L = 3 \quad (\because \omega = 1)$$

Ques:- Find circuit element for given voltage and current equations

$$V(t) = 9 \sin(t + 30^\circ)$$

$$i(t) = 3 \sin(2t + 60^\circ)$$

Note:-

By using above equations it is not possible to design the network since frequency of voltage and current are unequal.

Ans:- Find active power, reactive power and apparent power by using following equations:-


$$V(t) = 9 \sin(t + 30^\circ)$$

$$i(t) = 3 \sin(t + 60^\circ)$$

Soln:-

$$P = VI \cos\theta$$
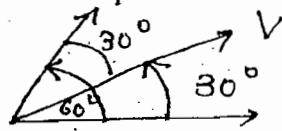
$$\Rightarrow P = \frac{9}{\sqrt{2}} \cdot \frac{3}{\sqrt{2}} \cos 30^\circ$$



$$\Rightarrow P = 27 \times \frac{\sqrt{3}}{2}$$

→ R-C circuit (I leading)

$$Q_C = VI \sin\theta$$

$$\Rightarrow Q_C = \frac{9}{\sqrt{2}} \cdot \frac{3}{\sqrt{2}} \sin 30^\circ$$

$$\Rightarrow Q_C = \frac{27}{4}$$

$$S = \sqrt{P^2 + Q_C^2} =$$

Alternate Way:-

$$Z = \frac{V}{I}$$

$$Z = \frac{9/\sqrt{2}}{3/\sqrt{2}}$$

$$Z = 3$$

$$\cos\theta = \frac{R}{Z}$$

$$\Rightarrow \cos 30^\circ = R/3 \Rightarrow R = 3 \cos 30^\circ$$

$$X_C = \sqrt{Z^2 - R^2}$$


$$P = i^2 R = (3/\sqrt{2})^2 R$$

$$Q_C = I^2 X_C = (3/\sqrt{2})^2 X_C$$

Ques - Find ammeter reading and power factor of the ckt shown

$$V_1(t) = 10 \sin t$$

$$V_2(t) = 10\sqrt{5} \sin \omega t$$

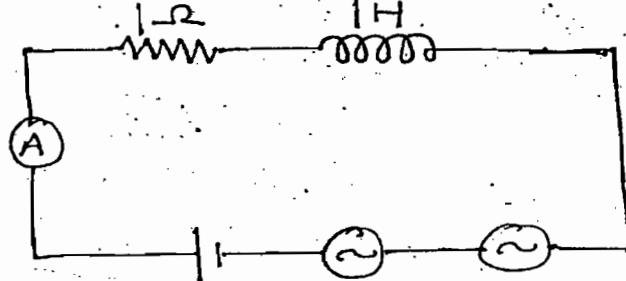

Soln - When multiple sources are present then at one time only one source is activated.

$$\text{For } V_1 \quad X_{L1} = \omega_1 L = 1$$

$$Z_1 = \sqrt{R^2 + X_{L1}^2} = \sqrt{1^2 + 1^2} = \sqrt{2}$$

$$i_1 = \frac{V_1}{Z_1} = \frac{10/\sqrt{2}}{\sqrt{2}} = 5$$

$$\text{For } V_2 \quad X_{L2} = \omega_2 L = 2$$

$$Z_2 = \sqrt{1^2 + 2^2} = \sqrt{5}$$

$$i_2 = \frac{V_2}{Z_2} = \frac{10\sqrt{5}/\sqrt{2}}{\sqrt{5}} = \frac{10}{\sqrt{2}}$$

$$\text{For } V_3 \quad \text{AC} \rightarrow \omega = 6$$

$$i_3 = \frac{V_3}{R} = \frac{5}{1} \Rightarrow i_3 = 5$$

When assume frequency are present then directly add them But above question different frequency are present Hence use general formula $(i = \sqrt{i_1^2 + i_2^2 + i_3^2} = 10\text{A}) \text{ Ans}$

For power factor use power triangle not impedance triangle (same reason)


$$P.F = \cos \theta = P/S \Rightarrow \cos \theta = iR/V_1 = \frac{iR}{V}$$

$$= 0.55$$

$$V = \sqrt{V_1^2 + V_2^2 + V_3^2} = \sqrt{\left(\frac{10}{\sqrt{2}}\right)^2 + \left(\frac{10\sqrt{5}}{\sqrt{2}}\right)^2 + 5^2}$$

$$=$$

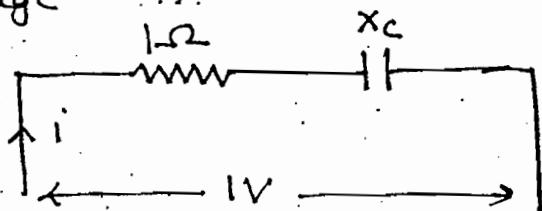Cause:- In the circuit shown power dissipation in the resistor is 500 mW. Find angle of current w.r.t. source voltage.



$$\text{SOLN: } P = i^2 R \Rightarrow P = \left(\frac{V}{Z}\right)^2 R$$

$$\Rightarrow P = \frac{V^2}{R^2 + X_C^2} R$$

$$\Rightarrow \frac{500}{1000} = \frac{I^2}{I^2 + X_C^2} \quad (1) \Rightarrow X_C = 1$$

$$Z = R - jX_C$$

$$Z = 1 - j1 \Rightarrow \theta = \tan^{-1}(-\frac{1}{1}) = -45^\circ$$


$$i = \frac{V \angle 0^\circ}{Z \angle -45^\circ} = \frac{V \angle 45^\circ}{Z} \Rightarrow \theta = 45^\circ \text{ Ans}$$

R-L-C Series Circuit:-

By KVL

$$V = V_R \angle 0^\circ + V_L \angle 90^\circ + V_C \angle -90^\circ$$



$$\Rightarrow IZ = IR + jIX_L - jX_C$$

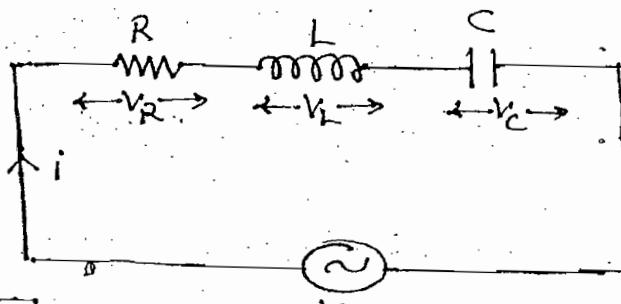

$$\Rightarrow Z = R + j(X_L - X_C)$$


$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$
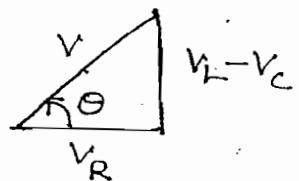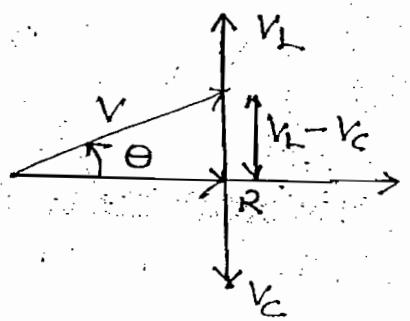
$$\theta = \tan^{-1} \left(\frac{V_L - V_C}{V_R} \right)$$



$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$
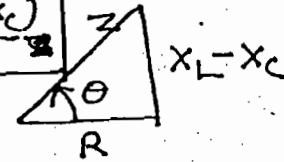
$$\theta = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$



$$S = \sqrt{P^2 + (Q_L - Q_C)^2}$$

$$\theta = \tan^{-1} \left(\frac{Q_L - Q_C}{P} \right) \quad z^2 = S \\ I^2 R = P \\ I^2 (X_L - X_C) = Q_L - Q_C$$

Power factor :-


$$\cos \theta = \frac{V_R}{V} = \frac{R}{Z} = \frac{P}{S}$$

(i) If $V_L > V_C \rightarrow$ lagging power factor

(ii) If $V_L < V_C \rightarrow$ leading power factor

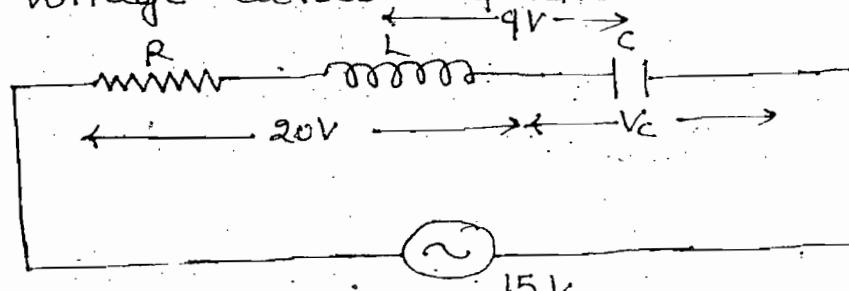(iii) If $V_L = V_C \rightarrow$ Unity power factor

Ques:- Find voltage across capacitor of circuit shown



- (a) 7 (b) 25 (c) 7 or 25 (d) 20

Soln:- $V_L - V_C = 9V$

$V = 15V$


$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$\Rightarrow 15^2 = V_R^2 + 9^2$$

$$V_R = \sqrt{225 - 81} = 12V$$

$$20 = \sqrt{V_R^2 + V_L^2} = \sqrt{12^2 + V_L^2} \Rightarrow V_L = 16$$
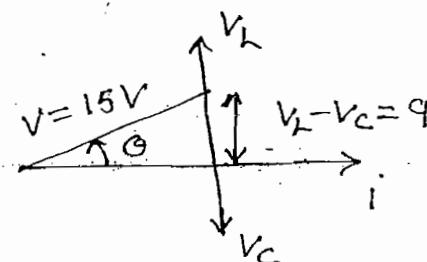
$$V_L - V_C = 9 \Rightarrow V_C = 7V, \text{ Ans}$$



Lecture - 5

R-L Parallel Circuit:-

By KCL



$$I = I_R \angle 0^\circ + I_L \angle 90^\circ$$

$$\Rightarrow \frac{V}{Z} = \frac{V}{R} - j \frac{V}{X_L}$$

$$\Rightarrow VY = VG_1 - jVB_L$$

$$\Rightarrow \boxed{Y = G_1 - jB_L}$$

mho mho mho

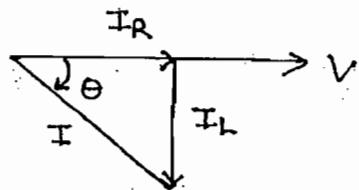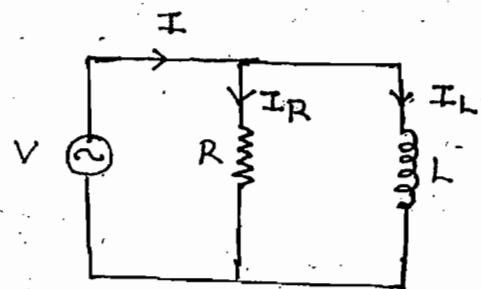

$$I = \sqrt{I_R^2 + I_L^2}$$

$$\theta = \tan^{-1} \left(\frac{-I_L}{I_R} \right)$$

$$I_R = VG_1$$

$$\begin{array}{c} \cancel{\triangle} \\ I = Vy \end{array} \quad I_L = VB_L$$

$$Y = \sqrt{G_1^2 + B_L^2}$$

$$\theta = \tan^{-1} \left(\frac{-B_L}{G_1} \right)$$

$$\begin{array}{c} \cancel{\triangle} \\ G_1 \\ B_L \\ Y \end{array}$$

$$S = \sqrt{P^2 + Q_L^2}$$

$$\theta = \tan^{-1} \left(\frac{-Q_L}{P} \right)$$

$$\begin{array}{c} \cancel{\triangle} \\ G_1 V^2 G_1 = P \\ B_L V^2 = Q_L \end{array}$$

Power factor:-


$$\rightarrow \cos \theta = \frac{I_R}{I} = \frac{G_1}{Y} = \frac{P}{S} = \text{Lagging}$$

R-C Parallel circuit:-

By KCL

$$I = I_R \angle 0^\circ + I_C \angle 90^\circ$$

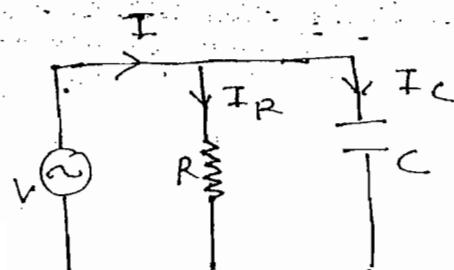
$$\Rightarrow \frac{V}{Z} = \frac{V}{R} + j \frac{V}{X_C}$$



$$\Rightarrow VY = VG_I + jVB_C$$


$$\Rightarrow Y = G_I + jB_C$$

M_{ho} M_{ho} M_{hb}

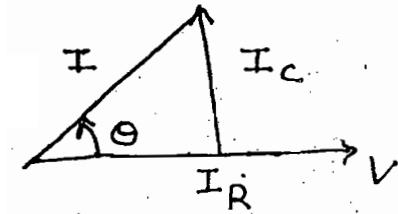


$$I = \sqrt{I_R^2 + I_C^2}$$
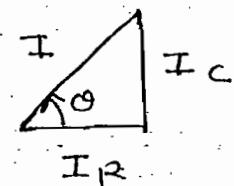
$$\theta = \tan^{-1} \left(\frac{I_C}{I_R} \right)$$




$$Y = \sqrt{G_I^2 + B_C^2}$$
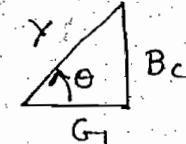
$$\theta = \tan^{-1} \left(\frac{B_C}{G_I} \right)$$



$$S = \sqrt{P^2 + Q_C^2}$$
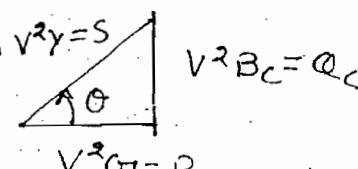
$$\theta = \tan^{-1} \left(\frac{Q_C}{P} \right)$$



Power Factor \Rightarrow

$$\cos \theta = \frac{I_R}{I} = \frac{G_I}{Y} = \frac{P}{S} = \text{leading}$$

RLC Parallel Circuit:



By KCL

$$I = I_R \angle 0^\circ + I_L \angle -90^\circ + I_C \angle +90^\circ$$


$$\Rightarrow \frac{V}{Z} = \frac{V}{R} - j \frac{V}{X_L} + j \frac{V}{X_C}$$

$$\Rightarrow VY = V [G_I + j(B_C - B_L)]$$


$$\Rightarrow Y = G_I + j(B_C - B_L)$$

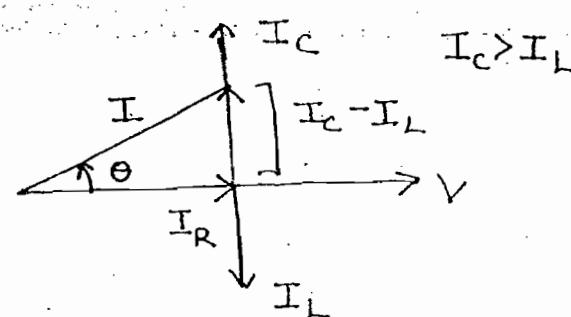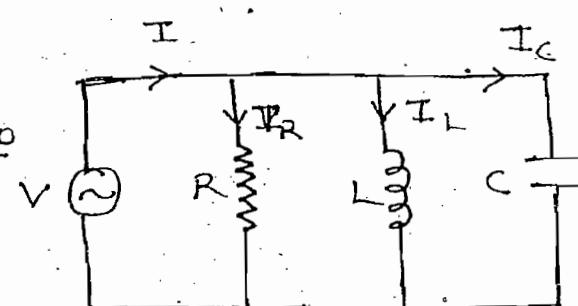

$$I = \sqrt{I_R^2 + (I_C - I_L)^2}$$

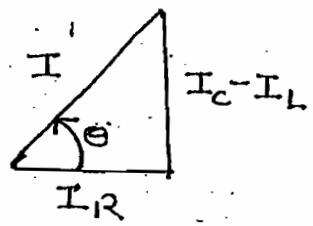

$$Y = \sqrt{G^2 + (B_C - B_L)^2}$$

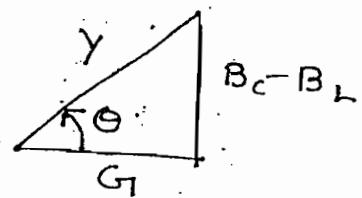

$$\text{Power Factor} = \cos\theta = \frac{I_R}{I} = \frac{G}{Y} = \frac{P}{S}$$

(I) $I_C > I_L \rightarrow$ leading

(II) $I_C < I_L \rightarrow$ lagging

(IV) $I_C = I_L \rightarrow$ Unity Power factor


Note:-

When combinational elements are present then we can't directly find conductance, admittance etc. Then following procedure is used

$$I_1 = \left(\frac{V}{R_1 + jX_L} \right) \left(\frac{R_1 - jX_L}{R_1 + jX_L} \right)$$

$$\Rightarrow \frac{V_1}{Z_1} = V \left[\frac{R_1}{R_1^2 + X_L^2} - j \frac{X_L}{R_1^2 + X_L^2} \right]$$

$$\Rightarrow Y_1 = G_1 - jB_L$$

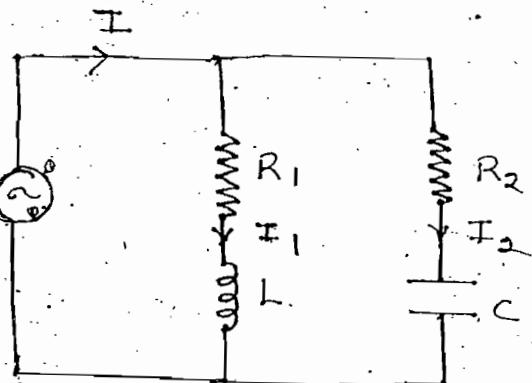

$$I_2 = \frac{V}{R_2 - jX_C} \frac{R_2 + jX_C}{R_2 - jX_C}$$

$$\Rightarrow \frac{V}{Z_2} = V \left[\frac{R_2}{R_2^2 + X_C^2} + j \frac{X_C}{R_2^2 + X_C^2} \right]$$

$$Y_2 = G_2 + jB_C$$


$$I = I_1 + I_2$$

$$\Rightarrow VY_{eq} = VY_1 + VY_2$$

$$\Rightarrow Y_{eq} = Y_1 + Y_2$$

$$\Rightarrow Y_{eq} = (G_1 + G_2) + j(B_C - B_L)$$

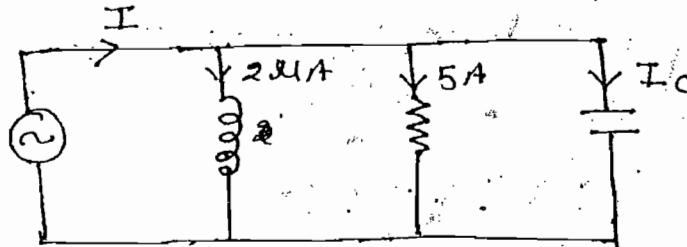ques: — Find I_c and I of the circuit shown



$$13 = \sqrt{5^2 + I_c^2} \Rightarrow I_c = 12A$$

$$I = \sqrt{I_R^2 + (I_c - I_L)^2}$$

$$\Rightarrow I = \sqrt{5^2 + (12 - 2\text{mA})^2} = 13 A$$

Note: —

A.C \rightarrow (KVL, KCL) \rightarrow Phasor sum

D.C \rightarrow (KVL, KCL) \rightarrow Arithmetic sum

ques: — Find capacitance of the capacitor when power factor of the circuit


is -0.8 lagging

$$V(t) = 5\sin t$$

Soln: — For Branch -1

$$X_L = \omega L = 1$$
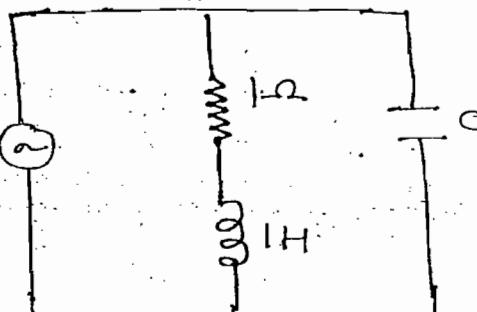
$$G_1 = \frac{R_1}{R_1^2 + X_L^2} = \frac{1}{1^2 + 1^2} = \frac{1}{2}$$



$$B_L = \frac{X_L}{R^2 + X_L^2} = \frac{1}{1^2 + 1^2} = \frac{1}{2}$$

$$Y_1 = G_1 - jB_L$$

$$\Rightarrow Y = \frac{1}{2} - j\frac{1}{2}$$

For Branch-2

$$Y_2 = +jB_C$$

$$Y_2 = j \frac{1}{X_C} = j\omega C \Rightarrow Y_2 = \omega C$$

$$Y_{eq} = Y_1 + Y_2$$

$$\Rightarrow Y_{eq} = \frac{1}{2} + j\left(C - \frac{1}{2}\right)$$

$$\cos \theta = \frac{G_1}{\sqrt{G_1^2 + (B_C - B_L)^2}}$$

$$\Rightarrow 0.8 = \frac{Y_2}{\sqrt{(Y_2)^2 + (C - \frac{1}{2})^2}}$$

$$\Rightarrow C = \frac{7}{8} \text{ or } \frac{1}{8}$$


Since $B_L > B_C$

$$\frac{1}{2} > C$$

Hence, $C = \frac{1}{8}$ Ans

Ques Find voltage across A and B of the circuit shown (a) 55 (b) 56 (c) 60 (d) 65

Soln:-

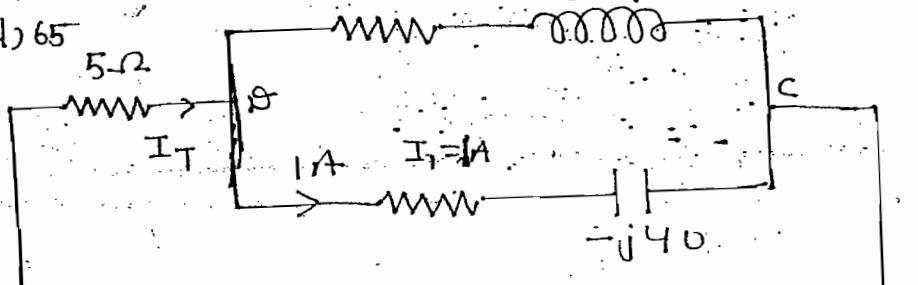

Apply current division technique.

$$I_1 = I_T \frac{30 + j40}{30 + j40 + 30 - j40} =$$

$$\Rightarrow I = I_T \cdot \frac{50 \lfloor \tan^{-1}(4/3) \rfloor}{60}$$

$$\Rightarrow I_T = \frac{60}{50 \lfloor \tan^{-1}(4/3) \rfloor} = 1.2 \lfloor \tan^{-1}(-4/3) \rfloor$$

$$V_{AB} = I_T \times 5$$

$$\Rightarrow V_{AB} = (1.2 \times 5) \lfloor \tan^{-1}(-4/3) \rfloor$$

$$\Rightarrow V_{AB} = 6 \lfloor \tan^{-1}4/3 \rfloor$$

$$V_{BC} = (30 - j40) \text{ } \Omega$$

$$V_{BC} = 50 \lfloor \tan^{-1}(-4/3) \rfloor$$

Angles are same hence they can be added

$$V_{AB} = V_{AC} = V_{AB} + V_{BC}$$

$$\Rightarrow V_{AB} = 56 \lfloor \tan^{-1}(-4/3) \rfloor \text{ Ans}$$


Locus Diagram:

$$X_L = 2\pi f L$$

$$X_L = 0$$

$$Z = R \Rightarrow I = \frac{V}{R}$$


$$\Rightarrow \theta = 0$$

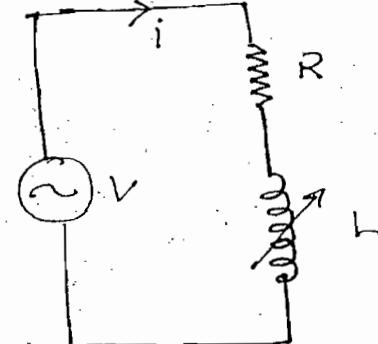

$$X_L \uparrow \quad Z \uparrow \quad I \downarrow$$

$$\theta = \tan^{-1}\left(\frac{X_L}{R}\right)$$
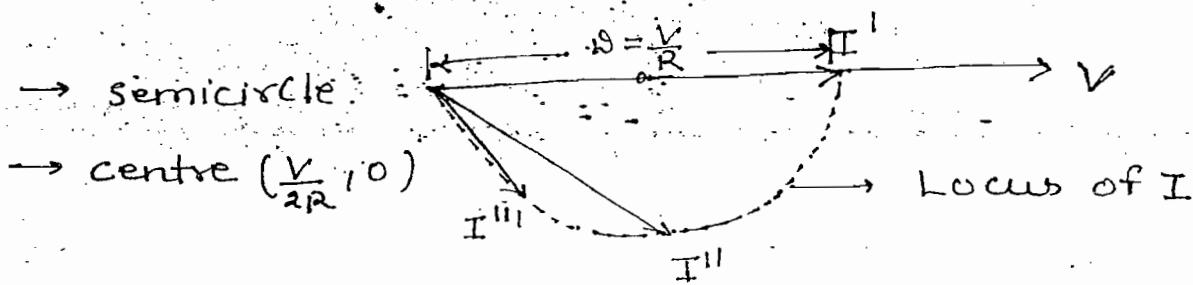
$$X_L \approx \infty \quad Z \approx \infty \quad I = 0$$



- Locus diagram are useful for analysis and designing of the circuit. e.g.: filters
- With respect to practical application it is possible to develop the following locus diagram
 - (i) Current locus diagram
 - (ii) Voltage locus diagram
 - (iii) Impedance locus diagram
 - (iv) Admittance locus diagram
- The path traced by terminous of current vectors by varying either any of the circuit elements or by varying source frequency is called as current locus

→ In the above circuit by keeping all the elements constant and by varying source frequency also same shape of the current locus diagram is obtained.

→ Develop current locus of the circuit shown

$$R=0$$

$$Z=X_L$$

$$I = \frac{V}{X_L}$$



$$\theta = 90^\circ$$

$$R \uparrow$$

$$Z \uparrow$$

$$I \downarrow$$
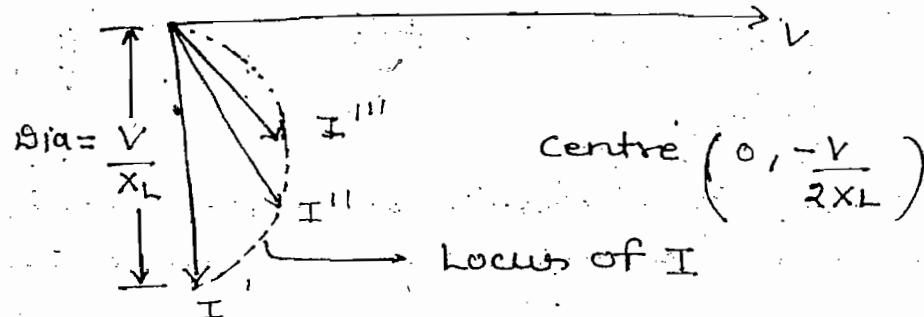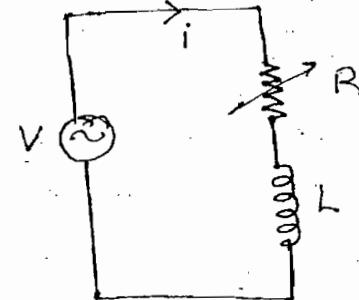
$$\theta = \tan^{-1} \left(\frac{X_L}{R} \right) \downarrow$$



→ Diameter is always due to constant element

Ques:- Develop current locus of I_1 and I of the circuit shown:-

Solⁿ:- $R_1 \approx 0.1\Omega$

$$I_1 = \frac{V}{R_1}$$

$$\theta_1 = 0$$

$$I = I_1 + I_2$$



$$R_1 \uparrow \quad R_1 \approx \infty$$

$$I_1 \downarrow \quad I_1 = 0$$

$$\theta_1 = 0 \quad I_2 = I$$

$$I_2 = \text{constant}$$

$$I \downarrow$$

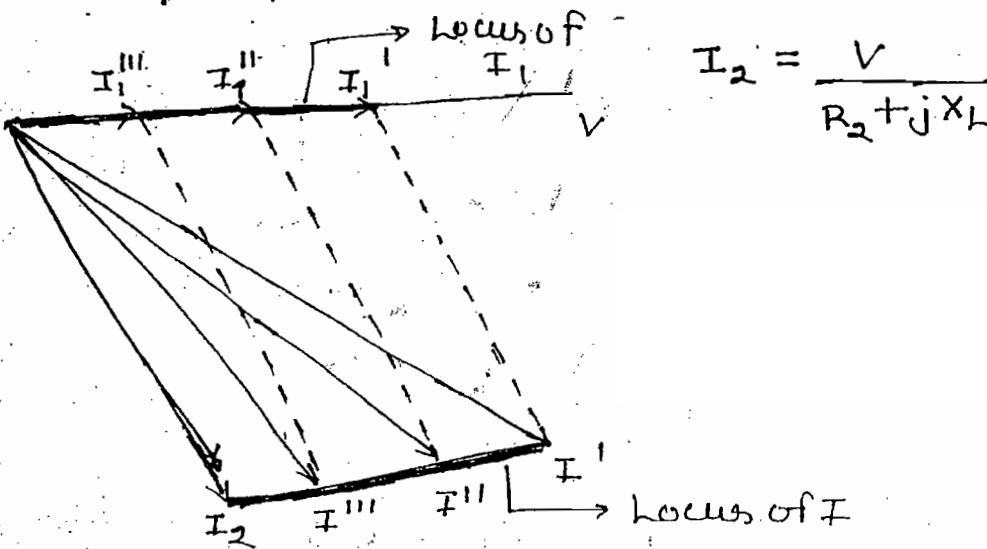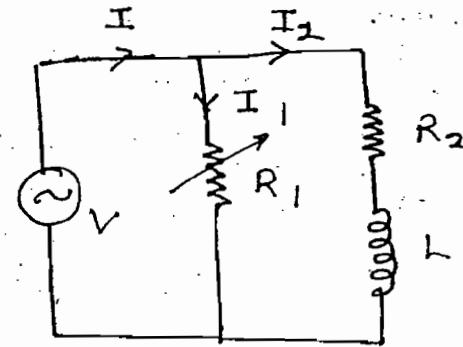

Note:-

→ When power factor angle is variable the shape of current locus is semi-circle

→ When power factor angle is constant the shape of the current locus diagram is straight line.

Ques:- Develop current locus of I_1 and I of the circuit shown

Solⁿ:- $X_C = \frac{1}{2\pi f C}$

$$X_C \approx 0$$

$$I_1 = \frac{V}{R_1}$$

$$\theta_1 = 0$$

$$I = I_1 + I_2$$

$$X_C \uparrow$$

$$Z_1 = \sqrt{R_1^2 + X_C^2} \uparrow$$

$$I_1 \downarrow$$

$$\theta_1 = \tan^{-1}\left(\frac{-X_C}{R_1}\right) \uparrow$$


$$I_2 = \text{constant}$$

$$I_1 \downarrow$$

$$X_C \approx \infty$$


$$I_1 = 0$$

$$I = I_2$$

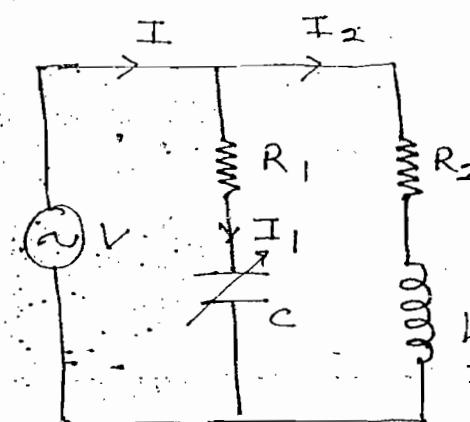


$$I_2 = \frac{V}{R_2 + jX_L}$$

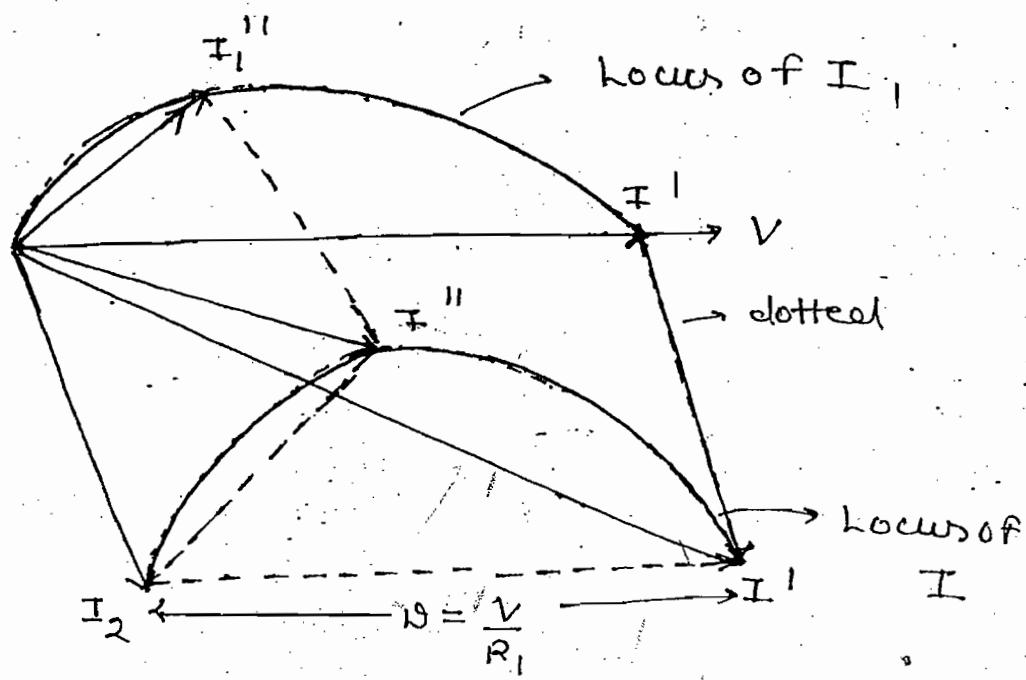
Focus only angles not signs but focus on magnitude




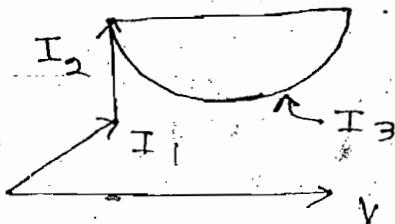
ques:- Design a N/w for given current locus diagram



Solⁿ:

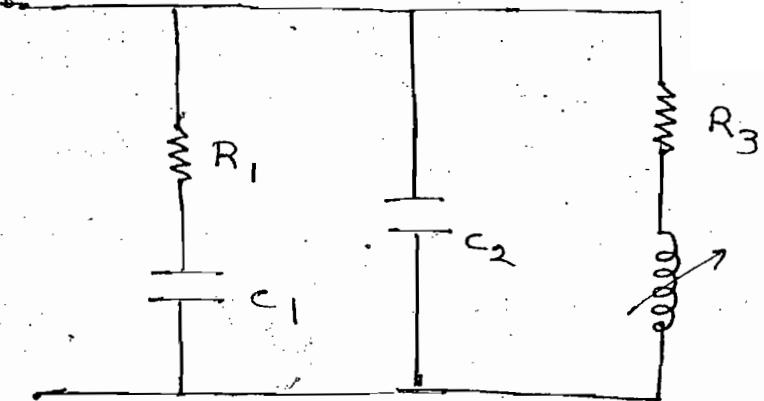

Resonance:-

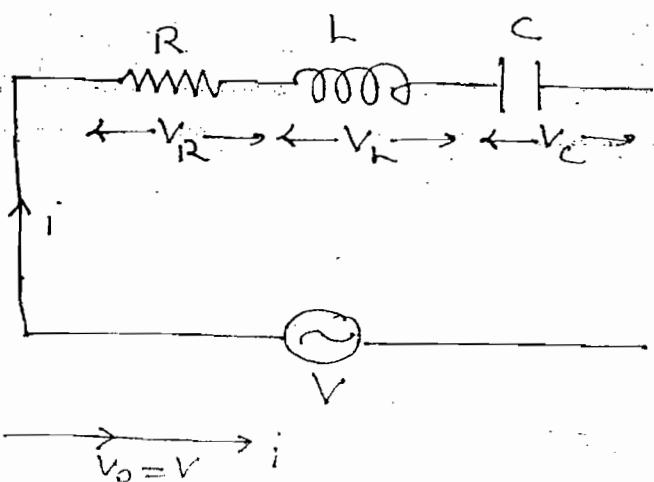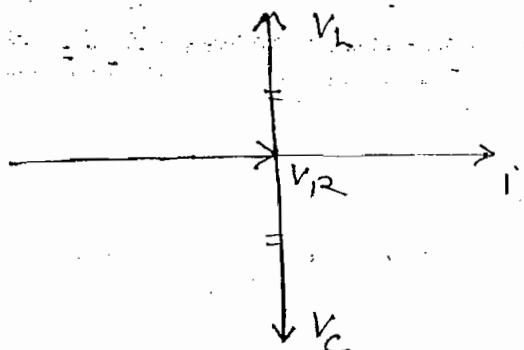

By KVL, $V = V_R \angle 0^\circ + V_L \angle 90^\circ + V_C \angle -90^\circ$

At resonance,

$$V_L = V_C$$

$$I X_L = I X_C$$

$$\Rightarrow \omega L = \frac{1}{\omega C}$$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$

$$\Rightarrow f_0 = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

→ For occurrence of resonance in any circuit two energies are required. In RLC circuit inductor is having energy in the form of magnetic field capacitor is having energy in the form of electric field. When these two energies are present at particular frequency wide variations are present in the system is called as resonance.

- The circuit is said to be resonance when source current is ~~in phase~~ with source voltage
- The frequency at which $X_C = X_L$ is called as resonant frequency
- The resonant frequency indicates rate at which energy transformation is done b/w inductor and capacitor

$$1 \rightarrow Z = R + j(X_L - X_C) \\ \underline{\quad \quad \quad = 0}$$

$$Z_{min} = R$$

$$2 \rightarrow I_{max} = \frac{V}{Z_{min}} = \frac{V}{R}$$

$$3 \rightarrow \cos \theta = 1$$

$$4 \rightarrow V_R = V$$

5. Net Reactive.

6. Voltage across inductor or voltage across capacitor greater than source. This phenomenon is called as voltage magnification.

Application:-

- Oscillators
- Filters (BP, BE)
- Tuning circuits
- Induction heating

Variation of voltage across inductor and voltage across capacitor w.r.t frequency:-


$$V_C = I X_C$$

$$X_L = 2\pi f L, \quad X_C = \frac{1}{2\pi f C}$$

$$\rightarrow f \approx 0, \quad X_L = 0, \quad X_C = \infty$$

$$\rightarrow X = |X_L - X_C| = \infty$$
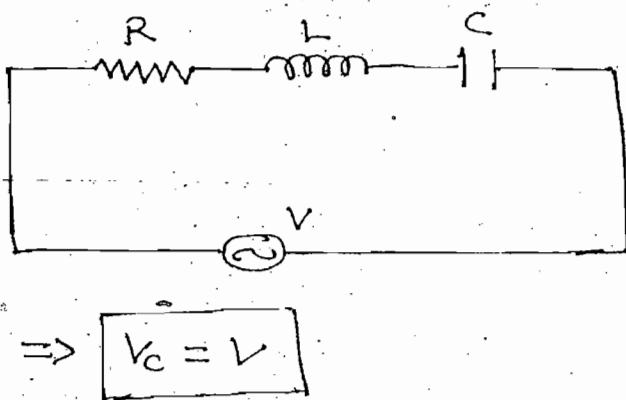
$$\Rightarrow Z = \infty \quad \& \quad I = 0$$



$$\Rightarrow V_C = V$$

For Inductor:-

$$\rightarrow f \uparrow \quad X_L \uparrow \quad X_C \downarrow \quad X = |X_L - X_C| \downarrow \downarrow \quad Z \downarrow \downarrow \quad I \uparrow \uparrow \quad V_C \uparrow$$

(10Ω) (100Ω) (90Ω)

$$\rightarrow f \uparrow \uparrow \quad X_L \uparrow \uparrow \quad X_C \downarrow \downarrow \quad Z = R + j(X_L - X_C) \uparrow \uparrow \uparrow \quad I \downarrow \downarrow \downarrow$$

(Very low)

$$V_C \downarrow$$

$$\rightarrow V_C = \frac{V X_C}{\sqrt{R^2 + (X_L - X_C)^2}} \Rightarrow V_C = \frac{V \frac{1}{\omega C}}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \quad (1)$$

Differentiate eq-(1) w.r.t ω and equal to zero we get

$$f_C = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \left(\frac{R_C}{2L}\right)^2}$$

For inductor :-

$$\rightarrow V_L = I X_L$$

$$\rightarrow X_L = 2\pi f L \quad \& \quad X_C = \frac{1}{2\pi f C}$$

$$\rightarrow f = 0, \quad X_L = 0, \quad X_C = \infty \quad X = |X_L - X_C| = \infty$$

$$Z = \infty, \quad I = 0,$$

$$\boxed{V_L = 0}$$

$$\rightarrow f \uparrow \quad X_L \uparrow \quad X_C \downarrow \quad X = |X_L - X_C| \downarrow \downarrow \quad Z \downarrow \downarrow$$

(10Ω) (100Ω)

$$\boxed{I \uparrow \uparrow} \quad \boxed{V_L \uparrow}$$

$$\rightarrow f \uparrow \uparrow \quad X_L \uparrow \uparrow \quad X_C \downarrow \downarrow$$


(Very low)

$$Z = R + j(X_L - X_C) \uparrow \uparrow \quad I_C \downarrow \downarrow \downarrow \quad \boxed{V_L \downarrow}$$

$$\rightarrow V_L = \frac{V X_L}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{V \omega L}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \quad - (ii)$$

Differentiate eq-(ii) w.r.t ω and equal to zero
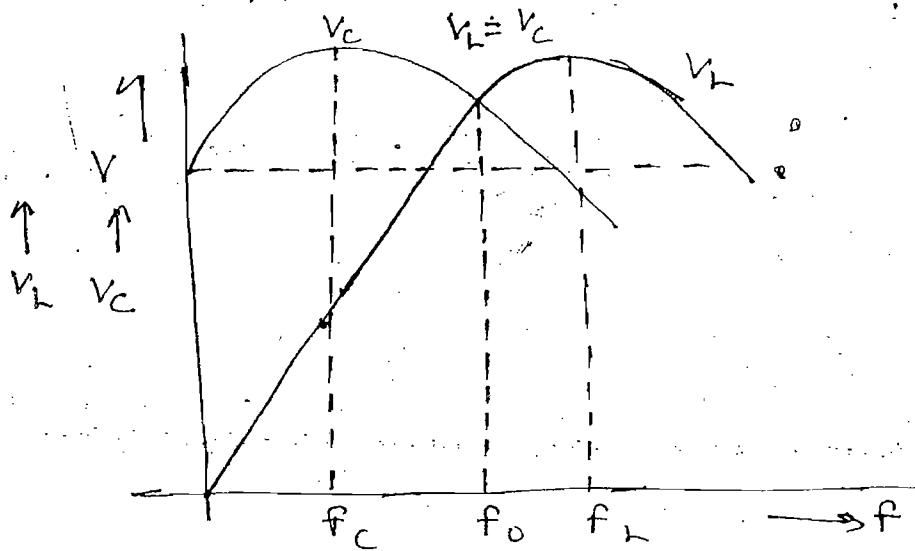
$$\boxed{f_L = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{1}{1 - \left(\frac{R^2 C}{2L}\right)}}}$$



Quality factor :-

→ Q-factor is a ratio of max. energy stored in the circuit to power dissipation per cycle

$$Q =$$

$$i(t) = I_m \sin \omega t \quad (i)$$

$$V_c(t) = \frac{1}{C} \int i(t) dt = \frac{1}{C} \int I_m \sin \omega t dt$$

$$\Rightarrow V_c(t) = -\frac{I_m}{\omega C} \cos \omega t \quad (ii)$$

$$w_g = \frac{1}{2} L I_m^2 + \frac{1}{2} C V_c^2$$

$$\Rightarrow w_g = \frac{1}{2} L (I_m \sin \omega t)^2 + \frac{1}{2} C \left(-\frac{I_m}{\omega C} \cos \omega t\right)^2$$

$$\Rightarrow w_g = \frac{1}{2} L I_m^2 \sin^2 \omega t + \frac{1}{2} C \frac{I_m^2}{\omega^2 C^2} \cos^2 \omega t$$

$$\Rightarrow w_g = \frac{1}{2} L I_m^2 \sin^2 \omega t + \frac{1}{2} L I_m^2 \cos^2 \omega t$$

$$\Rightarrow w_g = \frac{1}{2} L I_m^2$$

$$w_g = \frac{1}{2} C V_{cm}^2$$

$$\begin{aligned} \omega^2 &= \frac{1}{LC} \\ L &= \frac{1}{\omega^2 C} \end{aligned}$$

$$\left(\therefore V_{cm} = \frac{I_m}{\omega C} \right)$$

$$Q = \frac{\frac{1}{2} L I_m^2}{\left(\frac{I_m}{\sqrt{2}}\right)^2 R \frac{1}{\omega}}$$

$$I^2 R = \left(\frac{I_m}{\sqrt{2}}\right)^2 R$$

$$\Rightarrow Q = \frac{\omega L}{R}$$

$$\left(\omega = \frac{1}{\sqrt{C}} \right)$$

$$\Rightarrow Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\rightarrow Q = \frac{\omega L}{R} = \frac{I X_L}{I R} = \frac{V_L}{V_R} = \frac{V_L}{V} \quad (V_R = V)$$

$$Q = \frac{V_L \text{ or } V_C}{V}$$

($\because V_L = V_C$)

$$Q = \frac{I^2 X_L}{I^2 R} = \frac{Q_L}{P}$$

$$Q = \frac{X_L \text{ or } X_C}{R}$$

($\because X_L = X_C$)

$$Q = \frac{X_C}{R} = \frac{1}{\omega R C}$$

$$\rightarrow Q > 1, \quad X_L > R, \quad X_C > R$$

$$\rightarrow Q \propto \frac{1}{\text{Power loss } (I^2 R = P)}$$


$$\rightarrow Q \propto \frac{1}{\text{BW}}$$

Note:-

- To obtain high efficiency circuit is designed with high Q-factor
- To obtain wide BW circuit is designed with low Q-factor

Bandwidth:-

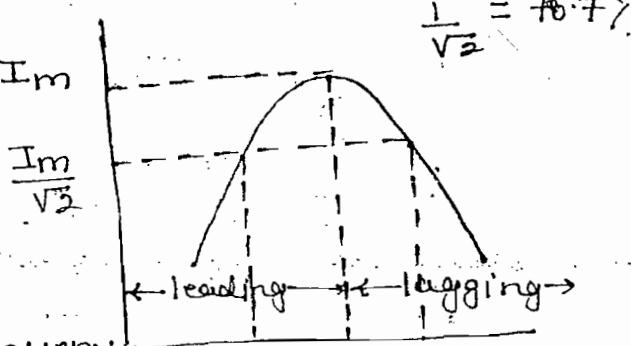- When the curve is Im developed b/w current and frequency then curve is called as resonance curve



- BW is the range of frequencies on either side of the resonant frequencies where the current falls from max. value to 70.7% of the max. value and it is given by

$$BW = f_2 - f_1$$

where f_2 = upper cut-off frequency

f_1 = lower " "

f_1, f_2 = 3dB points or half power frequencies

1. $f_0 \rightarrow Im \quad z=R$

$$f_1, f_2 \rightarrow \frac{Im}{\sqrt{2}} \Rightarrow z = \sqrt{2}R$$

2. $f_0 \rightarrow \cos\theta = 1$

$$f_1, f_2 \rightarrow z = R \pm jx \quad x = x_L - x_C$$

$$z = \sqrt{R^2 + x^2} = \sqrt{2}R$$

$$x_L = 2\pi f L$$

$$x_C = \frac{1}{2\pi f C}$$

$$\Rightarrow x = R$$

$$f_1 \rightarrow x_C > x_L$$

$$f_1 \rightarrow z = R - jx \quad x = R$$

$$x \rightarrow -ve$$

$$\text{Impedance Angle} = \tan^{-1}\left(\frac{-x}{R}\right)$$

$$f_2 \rightarrow x_L > x_C$$

$$= -45^\circ$$

$$x \rightarrow +ve$$

$$I = \frac{V_{L0}}{Z \angle -45^\circ} = \frac{V}{Z} \angle +45^\circ$$

$$\text{Power factor angle} = -45^\circ$$

$$\Rightarrow \text{Power factor} = \cos 45^\circ = \frac{1}{\sqrt{2}} \rightarrow \text{leading}$$

w.r.t f_2 :

$$f_2 \rightarrow z = R + jx \quad x = R$$

$$\text{Impedance angle} = \theta = \tan^{-1}\left(\frac{x}{R}\right) = +45^\circ$$

$$\text{Power factor angle} = -45^\circ$$

$$\text{Power factor} = \cos(-45^\circ) = \frac{1}{\sqrt{2}} \rightarrow \text{lagging}$$

3. $f_1 \rightarrow x_C > x_L \quad x = R$

$$\frac{1}{\omega_C} - \omega_L = R \rightarrow (1)$$

$$f_2 \rightarrow X_L > X_C \quad x=R$$

$$\omega_2 L - \frac{1}{\omega_2 C} = R \rightarrow (II)$$

From (I) & (II)

$$\omega_1 \omega_2 = \frac{1}{LC} \rightarrow (III)$$

$$\Rightarrow \omega_0^2 = \frac{1}{LC} \rightarrow (IV)$$

From (III) & (IV)

$$\omega_0^2 = \omega_1 \omega_2$$

$$\Rightarrow \omega_0 = \sqrt{\omega_1 \omega_2}$$

$$f_0 = \sqrt{f_1 f_2}$$

Add eq (I) & (II)

$$\frac{1}{C} \left[\frac{1}{\omega_1} + \frac{1}{\omega_2} \right] + L [\omega_2 - \omega_1] = 2R$$

$$\Rightarrow \frac{1}{C} \left[\frac{\omega_2 - \omega_1}{\omega_1 \omega_2} \right] + L [\omega_2 - \omega_1] = 2R$$

$$\Rightarrow L [\omega_2 - \omega_1] + L [\omega_2 - \omega_1] = 2R$$

$$\Delta \omega = \omega_2 - \omega_1 = \frac{R}{L} \text{ rad/sec}$$

$$\Delta \omega = f_2 - f_1 = \frac{R}{2\pi L} \text{ Hz}$$

$$Q = \frac{\omega_0 L}{R} \Rightarrow Q' = \frac{\omega_0}{R/L}$$

\therefore

$$Q = \frac{\omega_0}{\omega_2 - \omega_1} = \frac{f_0}{f_2 - f_1}$$

Lecture-6

By KVL

$$V = iR + L \frac{di}{dt} + \frac{1}{C} \int i dt$$

Diffr w.r.t t.

$$V' = R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{i}{C}$$

Dividing both sides of L

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{V'}{L}$$

$$\left(\omega^2 + \frac{R}{L} \omega + \frac{1}{LC} \right) i = 0 \quad \boxed{\omega = \frac{1}{\sqrt{LC}}}$$

$$\omega^2 + 2s\omega_n s + \omega_n^2 = 0$$

$$2s\omega_n = \frac{R}{L}$$



$$2s \frac{1}{\sqrt{LC}} = \frac{R}{L}$$

$$\omega = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\text{Damping ratio} = \zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$

$$\boxed{\zeta = \frac{1}{2\omega}}$$

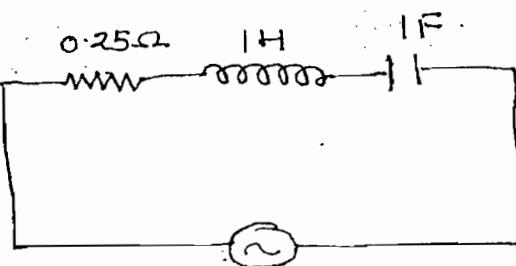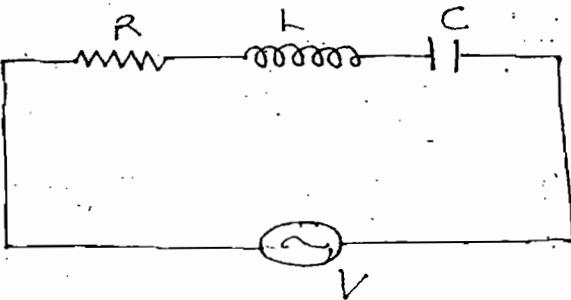Ques: Find f_0 , ω , ζ , BW, f_1, f_2 , I at f_0



$$V(t) = 10 \sin \omega t$$

$$\text{Soln:- (i) } f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi}$$

$$(ii) Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{0.25} \sqrt{\frac{1}{1}} = 4$$

$$(iii) s = \frac{1}{2Q} = \frac{1}{8}$$

$$(iv) \text{ BW} = \frac{f_0}{Q} = \frac{\frac{1}{2\pi}}{4} = \frac{1}{8\pi} \quad (f_2 - f_1)$$

$$(v) f_2 - f_1 = \frac{1}{8\pi}$$

$$f_1 f_2 = f_0^2 = \left(\frac{1}{2\pi}\right)^2$$

$$(f_2 + f_1)^2 - (f_2 - f_1)^2 = 4f_1 f_2$$

$$f_1 =$$


$$f_2 =$$

$$(vi) I = \frac{V}{Z} = \frac{V}{R} \quad (\text{At Resonance})$$

$$I = \frac{10/\sqrt{2}}{0.25}$$

$$I = \frac{40}{\sqrt{2}}, \text{ Ans.}$$

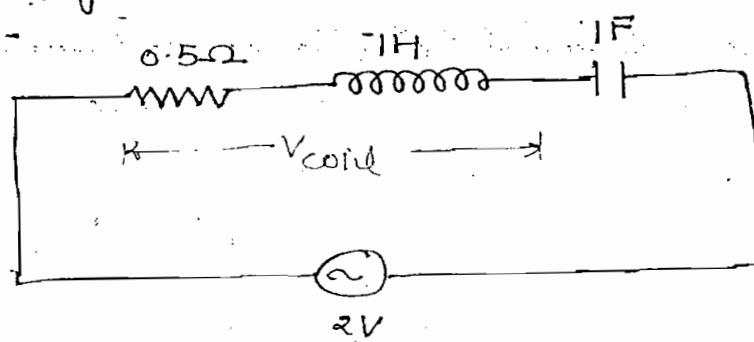ques:- Find voltage across the coil under resonance condition.



Soln:-

$$V_R = V = 2$$

[When nothing is given take it
as RMS]

$$\textcircled{1} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\textcircled{2} = \frac{1}{0.5} \sqrt{\frac{1}{1}} = 2$$

$$\textcircled{3} = \frac{V_L}{V}$$

$$\Rightarrow 2 = \frac{V_L}{2}$$

$$\Rightarrow V_L = 4$$

$$V_{\text{coil}} = \sqrt{V_R^2 + V_L^2}$$

$$\Rightarrow V_{\text{coil}} = \sqrt{2^2 + 4^2}$$

$$= \sqrt{20}, \text{ Ans.}$$

Parallel Resonance :-

Case - (I) :-

$$I_C = I_L$$



$$\frac{V}{X_C} = \frac{V}{X_L} \quad X_L = X_C$$

$$\Rightarrow B_C = B_L$$

$$\omega C = \frac{1}{\omega L}$$

$$w_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec.}$$
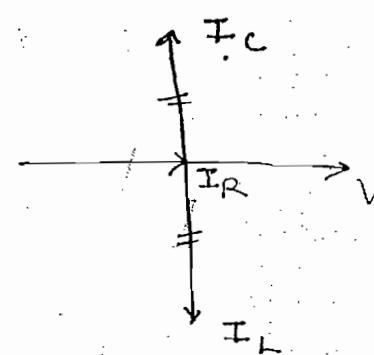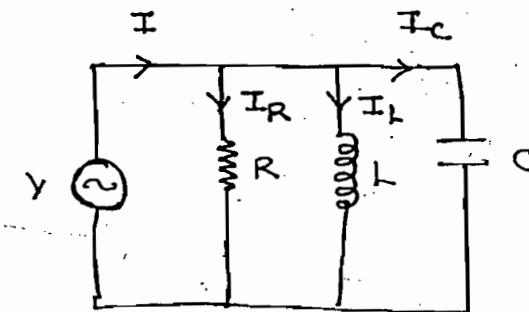
$$f_0 = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$



$$(I) \quad Y = G_T + j \left(\frac{B_C - B_L}{\omega} \right)$$

$$I_R = I$$

$$Y_{\min} = G_T$$

$$(II) \quad Z_{\max} = \frac{1}{Y_{\min}}$$

$$(III) \quad I_{\min} = \frac{V}{Z_{\max}}$$

$$(IV) \quad \text{case } \theta = 1$$

$$(V) \quad I_R = I$$

$$(VI) \quad \text{Net Reactive current} = 0$$

(VII) Current in inductor or current in capacitor is greater than total current. This phenomena is called as current magnification.

viii) Parallel Resonance circuit is also called as Anti-Resonance circuit.

Cause-(II):-

$$AB = I_1 \cos\theta_1$$

$$AF = BC = I_1 \sin\theta_1$$

$$AB = I_2 \cos\theta_2$$

$$AK = BF = I_2 \sin\theta_2$$

$$BL = BC$$

$$\frac{X_L}{R_1^2 + X_L^2} = \frac{X_C}{R_2^2 + X_C^2}$$

$$\frac{\omega L}{R_1^2 + (\omega L)^2} = \frac{1/\omega C}{R_2^2 + (1/\omega C)^2}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \quad \boxed{\sqrt{\frac{R_1^2 - \frac{L}{C}}{R_2^2 - \frac{L}{C}}}}$$

$$I = VY$$

$$\Rightarrow I = V [(G_1 + G_2) + j(B_C - B_L)]$$

$$\Rightarrow I = V \left[\frac{R_1}{R_1^2 + X_L^2} + \frac{R_2}{R_2^2 + X_C^2} \right]$$




Cause-(III):-

$$AB = I_1 \cos\theta_1$$


$$AF = BC = I_1 \sin\theta_1$$

$$\cos\theta_1 = \frac{R_1}{Z_1}$$

$$\sin\theta_1 = \frac{X_L}{Z_1}$$

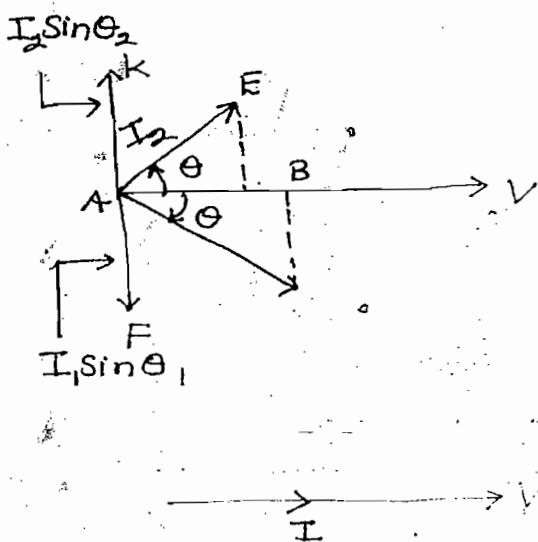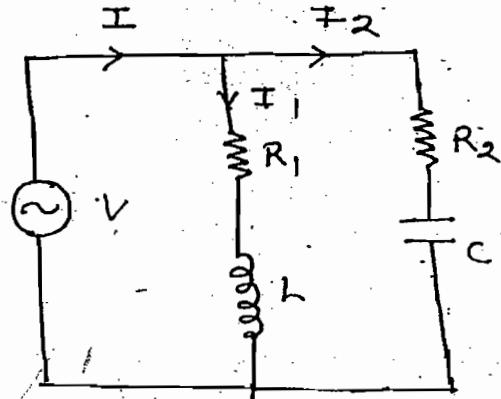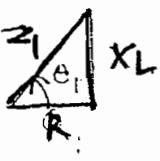
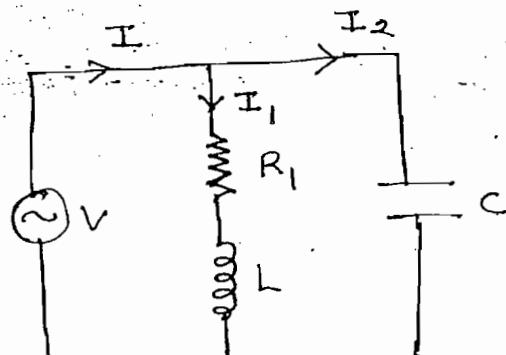
$$I = I_1 \cos\theta_1 + I_2 \cos\theta_2$$



Tank Ckt

$$I_2 = I_1 \sin \theta_1$$

$$\frac{V}{X_L} = \frac{V}{Z_1} \cdot \frac{X_L}{Z_1}$$

$$\Rightarrow Z_1^2 = X_L X_C$$

$$\Rightarrow Z_1^2 = \frac{VOL}{VOC}$$

$$\Rightarrow Z_1^2 = \frac{L}{C}$$

$$\Rightarrow Z_1 = \sqrt{\frac{L}{C}}$$

$$\rightarrow B_L = B_C$$

$$Z_1^2 = R_1^2 + X_L^2$$

$$\frac{L}{C} = R_1^2 + (2\pi f_0 L)^2$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R_1^2}{L^2}}$$

$$\rightarrow I = I_1 \cos \theta_1$$

$$\Rightarrow I = \frac{V}{Z_1} \cdot \frac{R_1}{Z_1}$$

$$\Rightarrow I = \frac{VR_1}{Z_1^2} \quad \Rightarrow \quad I = \frac{VR_1}{L/C}$$



$$\Rightarrow I = \frac{V}{\frac{L}{R_1 C}}$$

$$\Rightarrow Z_{DyN} = \frac{1}{R_1 C}$$

Ideal Tank Circuit :-

$$Z_{DyN} = \frac{L}{R_1 C} = \infty$$

$$f_0 = \frac{1}{2\pi \sqrt{LC}}$$

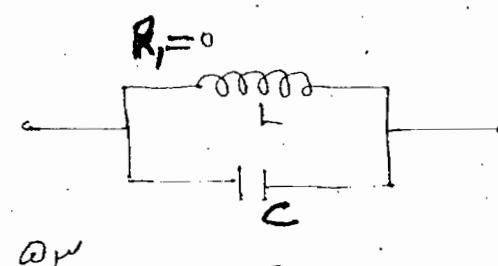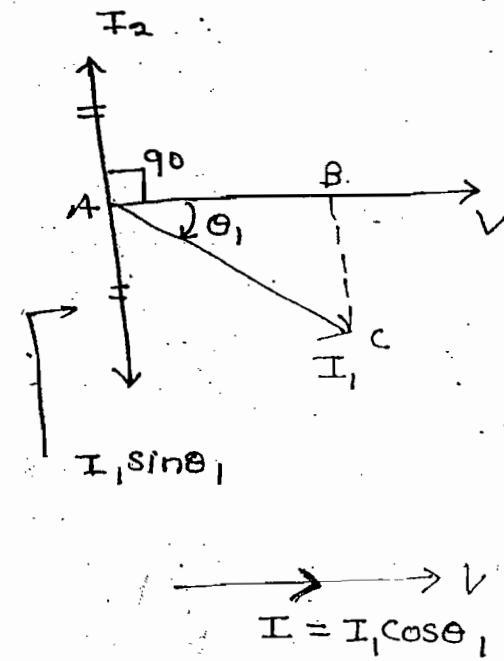


Q-Factor :-

$$Q = \frac{V_L \text{ or } V_C}{V}$$

Series

$$Q = \frac{I_L \text{ or } I_C}{I}$$

Parallel

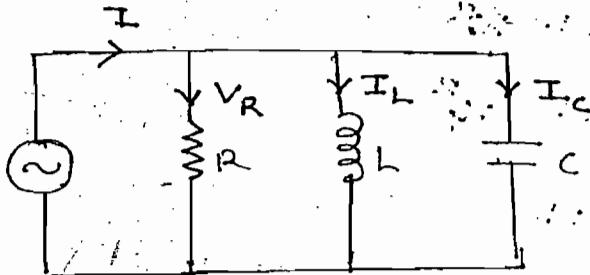

$$Q = \frac{I_L}{I} = \frac{I_L}{I_R} = \frac{\text{Reactive component of current}}{\text{Active component of current}}$$

This combination is valid for any combination of parallel circuit

$$Q = \frac{I_L}{I_R} = \frac{V/X_L}{V/R} = \frac{R}{X_L} = \frac{R}{\omega L} \quad (\omega = \sqrt{\frac{1}{LC}})$$

$$Q = \frac{X_L}{R} = \frac{B_L \text{ or } B_C}{G} \quad (B_L = B_C)$$

$$Q = R \sqrt{\frac{C}{L}}$$

$$Q = \frac{I_C}{I} = \frac{I_C}{I_R} = \frac{V/X_C}{V/R} = \frac{R}{X_C} = R\omega C$$


For

$$Q > 1, \quad R > X_L, \quad R > X_C$$

Tank circuit :-

$$Q = \frac{\text{Reactive component of current}}{\text{Active comp. of current}}$$

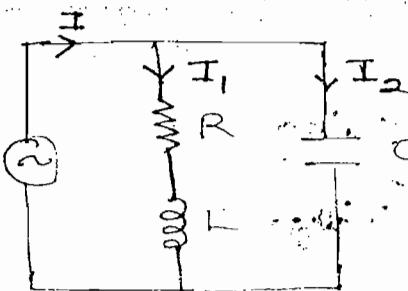
$$Q = \frac{I_1 \sin \theta, \text{ or } I_2}{I}$$




$$\alpha = \frac{I_2}{I} = \frac{\frac{V/X_C}{V}}{\frac{1}{R/C}} = \frac{\frac{1}{X_C}}{\frac{1}{R/C}} = \frac{\omega_L}{R} = \frac{X_L}{R}$$

For $\alpha > 1$, $X_L > R$

$$B.W = f_2 - f_1$$

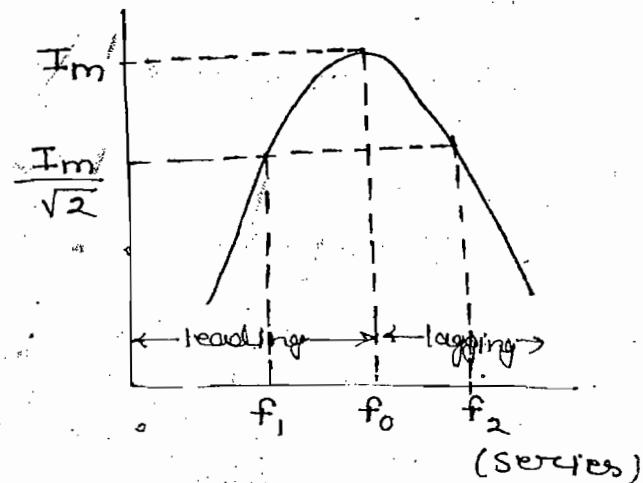


$$B.W = f_2 - f_1$$

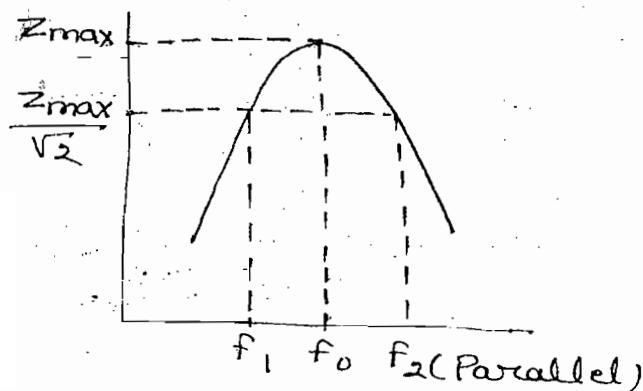

$$B.W = f_2 - f_1$$

$$B_L = \frac{1}{2\pi f L}$$

$$B_C = 2\pi f C$$

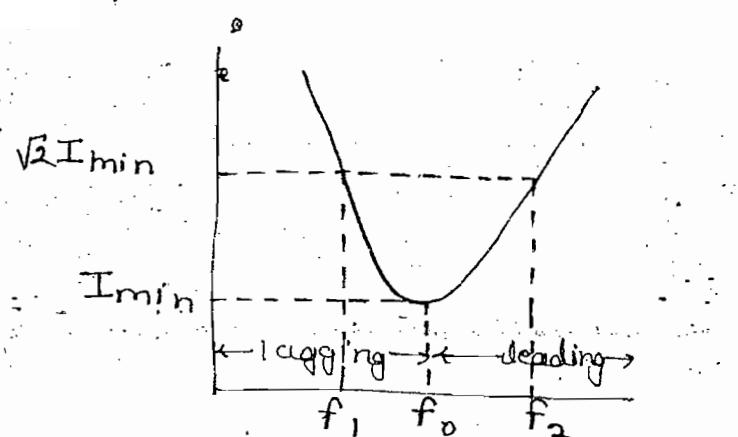

For parallel circuit we concentrate on the value of B_L and B_C (Parallel)

By KCL

$$I = \frac{V}{R} + C \frac{dV}{dt} + \frac{1}{L} \int V dt$$

Difff. w.r.t t

$$I' = \frac{1}{R} \frac{dV}{dt} + C \frac{d^2V}{dt^2} + \frac{V}{L}$$

Dividing both sides by C, we get

$$\frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{V}{LC} = \frac{I'}{C}$$

$$\theta = \frac{dV}{dt}$$

$$\left(\theta^2 + \frac{1}{RC} \theta + \frac{1}{LC} \right) V = 0$$

Compare with $s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$ we get

$$2\zeta\omega_n = \frac{1}{RC}, \quad \omega_n^2 = \frac{1}{LC}$$


$$2\zeta \frac{1}{\sqrt{LC}} = \frac{1}{RC}, \quad \omega_n = \frac{1}{\sqrt{LC}}$$

$$\zeta = R \sqrt{\frac{C}{L}}$$

$$\text{Damping Ratio} = \zeta = \frac{1}{2R} \sqrt{\frac{L}{C}}$$

$$\zeta = \frac{1}{2R}$$

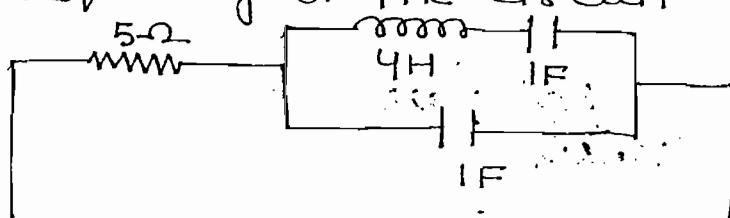Ques:- Find resonant frequency of the circuit shown



Soln:- At resonance in any of the case if $\text{Imag. part} = 0$.

Note:-

To find resonant frequency for any combination of the network

(I) Find Z_{eq}

(II) Equate imag. part of $Z = 0$

$$Z_1 = j(X_L - X_C) = j(\omega L - \frac{1}{\omega C}) = j(4\omega - \frac{1}{\omega})$$

$$Z_2 = -jX_C = -\frac{j}{\omega C} = -j\frac{1}{\omega}$$

$$Z_{eq}^1 = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$\Rightarrow Z_{eq}^1 = \frac{j(4\omega - \frac{1}{\omega})(-j/\omega)}{j(4\omega - \frac{1}{\omega}) - j/\omega}$$


$$\Rightarrow Z_{eq}^1 = \frac{(4\omega - \frac{1}{\omega})(+\frac{1}{\omega})}{j(4\omega - \frac{1}{\omega}) - j/\omega} \times \frac{j}{j}$$

$$\text{Im } Z_{eq}^1 = 0$$

$$(4\omega - \frac{1}{\omega}) \frac{1}{\omega} = 0$$


$$\Rightarrow \boxed{\omega = 0.5 \text{ rad/sec}}$$

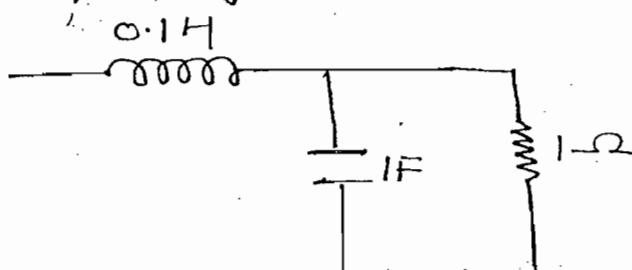Ques:- Find resonant frequency of the circuit shown




Ans:- $\omega_0 = 3 \text{ rad/sec}$

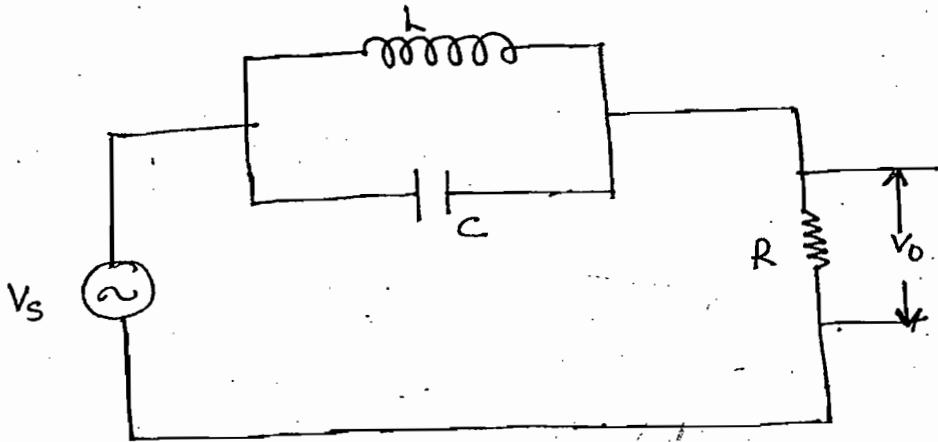ques1- Find V_o under resonance condition




solt-

Ideal tank circuit, $Z_{syn} = \infty$

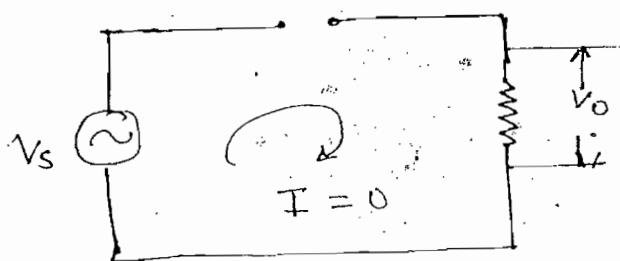


$$V_o = 0 \text{ V rms}$$

Note:

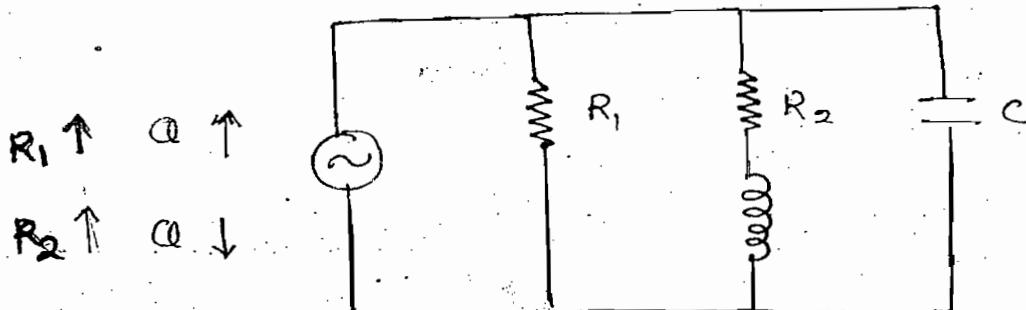

$$\therefore Q = \frac{R_1}{E_f}$$

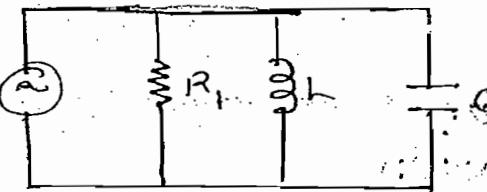

$$Q = \frac{\omega L}{R_2}$$

