

★ Boolean Algebra :

⇒

'AND' Law

'OR' Law

Identity element ⇒ '1'

$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$

'0'

$$A + 0 = A$$

$$A + 1 = 1$$

② Commutative Law:

Proof

$$\begin{cases} A + B = B + A \\ A \cdot B = B \cdot A \end{cases}$$

NAND : ↑

$$A \uparrow B = B \uparrow A$$

Proof

$$\therefore \overline{A \cdot B} = \overline{B \cdot A}$$

$$A \downarrow B = B \downarrow A$$

⇒ Inhibition: (/)

$$\Rightarrow x|y = x \cdot \bar{y}$$

✓

$$\boxed{\begin{array}{l} A|B \neq B|A \\ \therefore A \cdot \bar{B} \neq \bar{B} \cdot A \end{array}}$$

→ 'Inhibition is not Commutative.'

⑥ Associative Law:

Proof

$$\begin{array}{l} (A+B)+C = A+(B+C) \\ (A \cdot B) \cdot C = A \cdot (B \cdot C) \end{array}$$

$$\begin{array}{ccc} \overset{1}{A} \uparrow \overset{1}{B} & \overset{0}{\uparrow} C & \neq \overset{1}{A} \uparrow \overset{0}{(B \uparrow C)} \\ & 0 \uparrow 0 & 1 \uparrow 1 \\ & = 1 & = 0 \end{array}$$

→ The NAND and NOR operation are Commutative but not Associative.

⑦ Consensus Law:

$$\underline{A} \cdot \underline{B} + \underline{\bar{A}} \cdot \underline{C} + \underline{B \cdot C} = A \cdot B + \bar{A} \cdot C$$

$$\begin{aligned} \therefore A \cdot B + \bar{A} \cdot C + B \cdot C & \{ A + \bar{A} \} \\ & = \underline{A \cdot B} + \underline{\bar{A} \cdot C} + \underline{A \cdot B \cdot C} + \underline{\bar{A} \cdot B \cdot C} \\ & = \underline{A \cdot B} + \underline{\bar{A} \cdot C} + \underline{A \cdot B \cdot C} + \underline{\bar{A} \cdot B \cdot C} \\ & = ABC(1+C) + \bar{A}C(1+B) \\ & = AB + \bar{A}C \end{aligned}$$

$$\boxed{x \cdot y + \bar{y} \cdot z + w \vee x \bar{z} = x \cdot y + \bar{y} \cdot z}$$

Dual $(\underbrace{A+B}) \cdot (\underbrace{\bar{A}+C}) \cdot (\underbrace{B+C}) = (A+B) \cdot (\bar{A}+C).$

(4) Distribution Law:

→ $A \cdot (B+C) = AB + AC.$

Dual $\left(\begin{array}{l} A \cdot (B+C) = AB + AC \\ A + (B \cdot C) = (A+B) \cdot (A+C) \end{array} \right.$

i) $\bar{X} + X\bar{Y} = (\bar{X}+X)(\bar{X}+\bar{Y})$

$$\therefore \boxed{\bar{X} + X\bar{Y} = \bar{X} + \bar{Y}}$$

(ii) $\underline{AB} + \underline{\bar{A}B}C = (AB + \bar{A}B)(A+B+C).$
 $= AB + C.$

(5) Transposition Law:

→ $\overbrace{AB + \bar{A}C} = (\bar{A}+B)(A+C).$

$$= \bar{A} \cdot A + \bar{A}C + AB + BC.$$

$$= AC + AB + BC.$$

$$= \bar{A}C + AB \quad (\because \text{Consensus Law}).$$

$$= \text{L.H.S}$$

→ $\boxed{x \cdot y + \bar{y} \cdot z = (x+\bar{y})(y+z).$

⑥ De Morgan's Law:

→ (a) NOR gate = Bubbled AND gate

$$\overline{A+B+C+\dots} = \bar{A} \cdot \bar{B} \cdot \bar{C} \dots$$

→ (b) NAND gate = Bubbled OR gate.

$$\overline{A \cdot B \cdot C \cdot D \dots} = \bar{A} + \bar{B} + \bar{C} + \bar{D} + \dots$$

⑦ Shannon's Law:

→ To find Complement of a fun 'F'.

- (i) Find the Dual of F i.e. 'F_D'.
- (ii) Complement all variables.

Ex-1 $F = AB + BC + CA$ then $\bar{F} = \bar{A} \cdot \bar{B} + \bar{B} \cdot \bar{C} + \bar{C} \cdot \bar{A}$
[↓ (F)]

Ans: $F = AB + BC + CA$

$$\therefore \bar{F} = (\bar{A} + \bar{B}) \cdot (\bar{B} + \bar{C}) \cdot (\bar{C} + \bar{A})$$

$$= (\bar{A}\bar{B} + \bar{A}\bar{C} + \bar{B}\bar{C} + \bar{A}\bar{B}) \cdot (\bar{C} + \bar{A})$$

$$= \bar{A}\bar{B} + \bar{A}\bar{C} + \bar{B}\bar{C} + \bar{A}\bar{B}$$

$$= \bar{A}\bar{B} + \bar{A}\bar{C} + \bar{B}\bar{C}$$

i) $F_D = (A+B) \cdot (B+C) \cdot (C+A)$

$$(ii) \quad \bar{F} = (\bar{A} + \bar{B}) (\bar{B} + \bar{C}) (\bar{C} + \bar{A})$$

$$= (\bar{B} + \bar{A}\bar{C}) \cdot (\bar{C} + \bar{A})$$

$$= \bar{B}\bar{C} + \bar{A}\bar{B} + \bar{A}\bar{C} + \bar{A}\bar{C}$$

$$\therefore \bar{F} = \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{C}\bar{A}$$

☆☆

Ex-2 Simplify the following boolean expression to four literals.

$$(1) \quad F = \underline{\bar{A}C} + \underline{\bar{C}D} + \underline{\bar{B}C} + \underline{AB} \rightarrow \underline{4 \text{ literals}}$$

Note: Literal: variable (or) complement of variables.

$$\text{Eg: } F(A, B, C) \Rightarrow \underline{A, \bar{A}, B, \bar{B}, C, \bar{C}}$$

$$F = (\bar{A} + \bar{B})C + \bar{C}D + AB$$

$$F = \underline{\bar{A}\bar{B}} \cdot C + \bar{C}D + \underline{AB}$$

$$\therefore F = \underline{AB + C + \bar{C}D}$$

$$\boxed{F = AB + C + D}$$

Ex-3 Determine the number of two input NAND gates required to implement the following:

$$\text{Ans: } (1) \quad F = (\bar{X} + \bar{Y})(W + Z)$$

$$F = \overline{\underline{P}W \cdot \underline{P}Z}$$

$$\therefore \bar{F} = \underline{(\bar{X} + \bar{Y}) \cdot (W + Z)}$$

4 NAND gates req.

$$F = \bar{X} \cdot \bar{Y} \cdot (W + Z)$$

$$\therefore F = \frac{\bar{X} \cdot \bar{Y} \cdot W + \bar{X} \cdot \bar{Y} \cdot Z}{PW + PZ} \quad P = \bar{X} \cdot \bar{Y}$$


$$(b) F = A + AB + ABC.$$

$$= A + AB(1+C).$$

$$= A + AB.$$

$$= A(1+B)$$

$$\therefore \boxed{F = A}$$

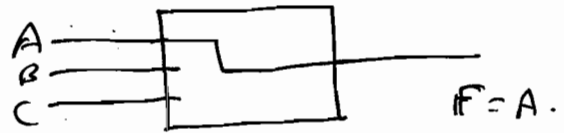

'0' NAND gates.

$\Rightarrow$ 0 NAND gate is required.

★
★

(c) n-input AND gate = ?

NAND gates

$$\rightarrow 2 \text{ i/p AND } \Rightarrow F = \overline{\overline{A \cdot B}} = \textcircled{2}$$

$$3 \text{ i/p AND } \Rightarrow F = \overline{\overline{ABC}} = \overline{\overline{AB} \cdot C} = \textcircled{4}$$

$$4 \text{ i/p AND } \Rightarrow F = \overline{\overline{ABCD}} = \textcircled{6}$$

$\therefore$
n i/p AND $\Rightarrow$ ~~for~~ $(2n-2)$ no. of 2 i/p NAND gate req.

Ex-4 Implement EX-OR gate using minimum no. of $\textcircled{a}$ NAND gate $\textcircled{b}$ NOR gate.

Ans:

$$\rightarrow A \oplus B = \overline{A} \cdot B + A \cdot \overline{B}$$


$$= \overline{A} \cdot B + \overline{A \cdot B} + \boxed{\overline{A \cdot \overline{A}} + \overline{B \cdot \overline{B}}}$$

$$= B(\overline{A} + \overline{A}) + A(\overline{A} + \overline{B})$$

$$= \underline{\underline{A \cdot \overline{AB} + B \cdot \overline{AB}}}$$

$$\overline{A \cdot B} = \overline{A \cdot \overline{A}B + A \cdot \overline{B}} = \overline{A \cdot \overline{A}B + A \cdot \overline{B}}$$
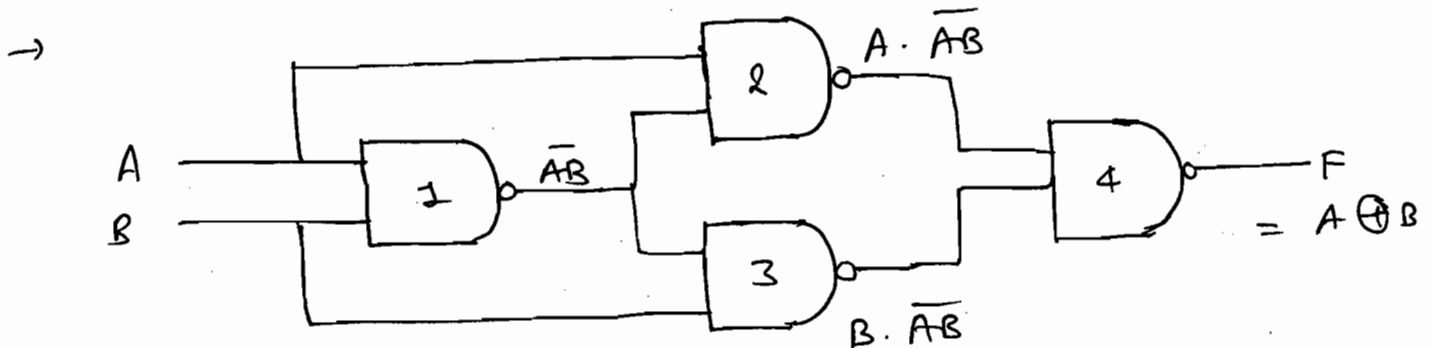
$$\therefore \overline{F} = \overline{A \cdot \overline{A}B + A \cdot \overline{B}}$$



(b) Using NOR gate:

$$F = A \oplus B$$

$$F = \overline{A(\overline{A} + \overline{B}) + B(\overline{A} + \overline{B})}$$


$$\therefore \cancel{F} = \cancel{A(\overline{A} + \overline{B}) + B(\overline{A} + \overline{B})}$$


$$\overline{F} = \boxed{(\overline{A} + \overline{B})(A + B)} \quad \checkmark$$

$$= \overline{(\overline{A} + \overline{B})(A + B)}$$

$$F = \overline{\overline{A} + \overline{B}} + \overline{A + B}$$


∴ 5 NOR gate.

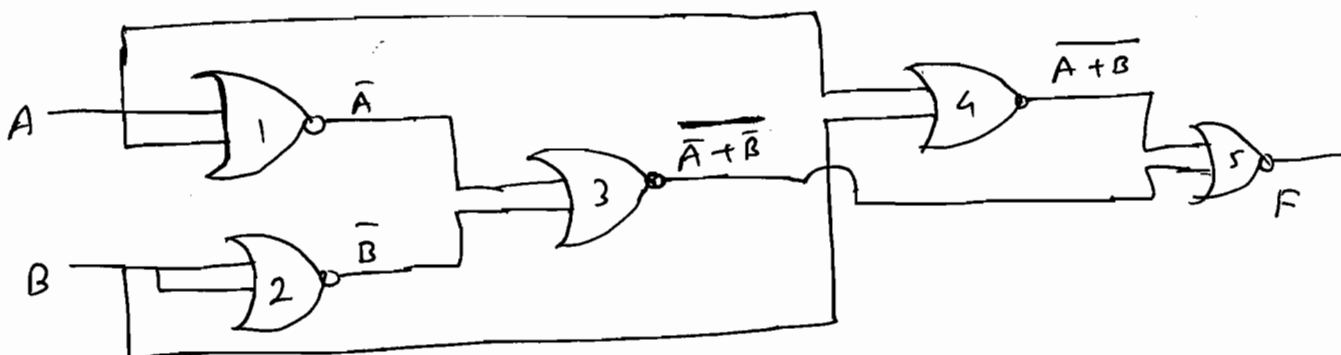

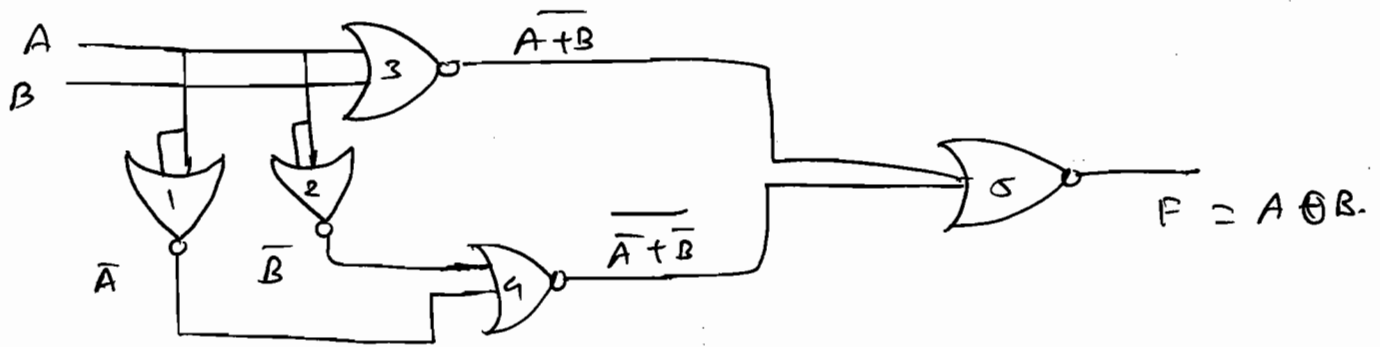


→ If complement of I/P variables are given i.e. $\bar{A}$, $\bar{B}$ are available then only 3 NOR gates are required to implement $A \oplus B$.

* X-NOR using min. no. of NOR gates:

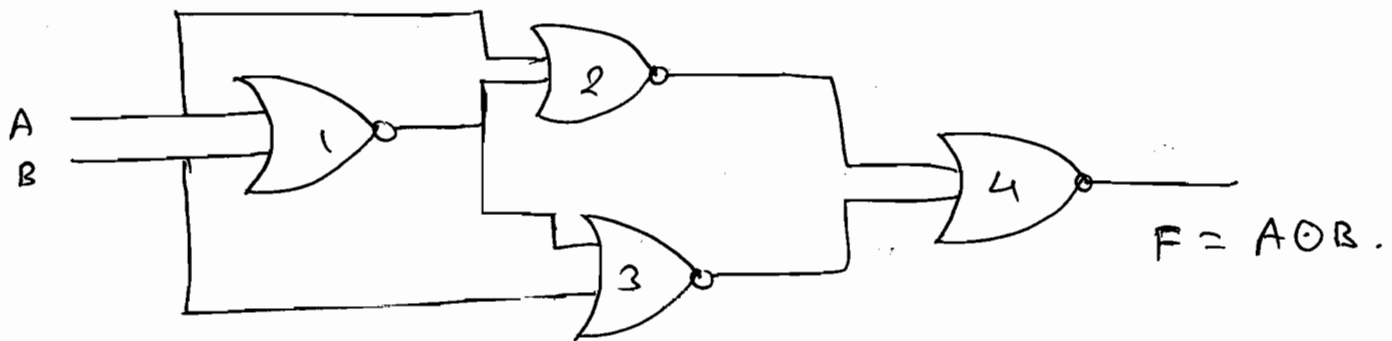

* X-NOR using min. no. NAND gates:

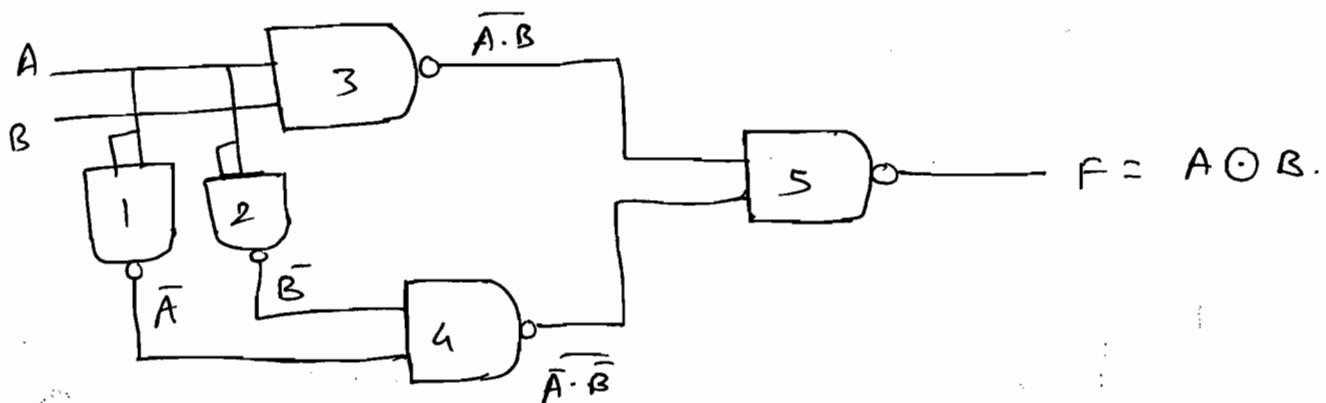

* Minterms, Maxterms & Properties.

→ Minterms → Standard Product term.

→ maxterms → Standard Sum term.

⇒ Minterms → 8

$$m_0 \quad \begin{matrix} 0 & 0 & 0 \\ \bar{A} & \cdot & \bar{B} & \cdot & \bar{C} \end{matrix}$$

$$m_1 \quad \begin{matrix} 0 & 0 & 1 \\ \bar{A} & \cdot & \bar{B} & \cdot & C \end{matrix}$$

$$m_2 \quad \begin{matrix} 0 & 1 & 0 \\ \bar{A} & \cdot & B & \cdot & \bar{C} \end{matrix}$$

$$m_3 \quad \bar{A} \cdot B \cdot C$$

$$m_4 \quad A \cdot \bar{B} \cdot \bar{C}$$

$$m_5 \quad A \cdot \bar{B} \cdot C$$

$$m_6 \quad \begin{matrix} 1 & 1 & 0 \\ A & \cdot & B & \cdot & \bar{C} \end{matrix}$$

$$m_7 \quad \begin{matrix} 1 & 1 & 1 \\ A & \cdot & B & \cdot & C \end{matrix}$$

$$\boxed{\text{Var} = 1}$$

$$\boxed{\overline{\text{Var}} = 0}$$

Maxterms → 8

$$M_7 \quad \begin{matrix} \phi & \phi & \phi \\ \bar{A} & + & \bar{B} & + & \bar{C} \end{matrix}$$

$$M_6 \quad \begin{matrix} 1 & 1 & 0 \\ \bar{A} & + & \bar{B} & + & C \end{matrix}$$

$$M_5 \quad \begin{matrix} 1 & 0 & 1 \\ \bar{A} & + & B & + & \bar{C} \end{matrix}$$

$$M_4 \quad \begin{matrix} 1 & 0 & 0 \\ \bar{A} & + & B & + & C \end{matrix}$$

$$\underline{M_3} \quad \begin{matrix} 0 & 1 & 1 \\ A & + & \bar{B} & + & \bar{C} \end{matrix}$$

$$M_2 \quad A + \bar{B} + C$$

$$M_1 \quad A + B + \bar{C}$$

$$M_0 \quad \begin{matrix} 0 & 0 & 0 \\ A & + & B & + & C \end{matrix}$$

$$\boxed{\text{Var} = 0}$$

$$\boxed{\overline{\text{Var}} = 1}$$

Ex-1 $F(A, B, C, D, E)$ and find $m_{23} = ?$, $M_{19} = ?$

Ans: $m_{23} = \begin{matrix} 1 & 0 & 1 & 1 & 1 \\ \bar{A} & \cdot & \bar{B} & \cdot & C & D & E \end{matrix}$

$$M_{19} = \begin{matrix} 1 & 0 & 0 & 1 & 1 \\ \bar{A} & + & B & + & \bar{C} & + & \bar{D} & + & \bar{E} \end{matrix}$$

* Properties:

① n-var Function $\Rightarrow$ 2^n minterms
 2^n max terms.

② $M_j = \overline{m_j}$ and vice versa.

③ $m_i^D = M_{(2^n - 1 - i)}$.
 $D = \text{dual}$

e.g. $m_3 = \overline{A} B C$

$m_3^D = \overline{\overline{A} B C} = A + \overline{B} + \overline{C}$

✓

$= M_4$

$m_3^D = M_{2^3 - 1 - 3}$

④ (a) Sum of all minterms = 1

i.e. $\sum_{i=0}^{2^n-1} m_i = 1$

⑥ Product of all maxterms = 0 i.e.

$\prod_{j=0}^{2^n-1} M_j = 0$

BEL ★★

Ex-1

How many minterms are present at the o/p of ^{6 i/p} Ex-OR gate: $2^{6-1} = 32$ no. of minterms.

Ans:

$A \oplus B = A \cdot \overline{B} + \overline{A} \cdot B$

$A \oplus B \oplus \overline{A} \oplus \overline{B} = A \cdot \overline{B}$

$A \oplus B = m_1 + m_2$ [2 out of 4 minterms]

$\therefore A \oplus B \oplus C = m_1 + m_2 + m_4 + m_3$ [4 out of 8 minterms]

$\therefore A \oplus B \oplus C$
 n-input Ex-OR gate output contains $= \frac{2^n}{2}$
 $= 2^{n-1}$ no. of output minterms.

NOTE: Same for X-NOR.

Ex-2 How many boolean fⁿs can be formed using n-boolean variables?

Ans: 'n' Boolean variable $\rightarrow$ Boolean functions $= 2^{2^n}$.
 $\downarrow$
 $x = 2^n$ minterms $\nearrow 2^x = 2^{2^n}$

$F(A, B)$

	AB	F ₀	F ₁	F ₂	F ₃	...	F ₁₅
m ₀ $\leftarrow$	00	0	0	0	0		1
m ₁ $\leftarrow$	01	0	0	0	0		1
m ₂ $\leftarrow$	10	0	0	1	1		1
m ₃ $\leftarrow$	11	0	1	0			1

$\downarrow$ (Null)
 $\downarrow$ AND
 $\downarrow$ Inhibition (A/B)
 $\downarrow$ Transfer
 $\downarrow$ Identity.

* Forms of Boolean Functions:

- 1) a) Sum of Products (SOP) form. $\rightarrow$ DNF
 b) Product of Sum (POS) form. $\rightarrow$ CNF
- 2) a) Canonical (or) Standard SOP form. (Sum of minterms) $\rightarrow$ DCF
 b) Canonical (or) Standard POS form. (Product of max terms) $\rightarrow$ CCF

$\checkmark$ DNF = Disjunctive Normal form

$\checkmark$ CNF = Conjunctive normal form.

$\checkmark$ DCF = Disjunctive canonical form

$\checkmark$ CCF = Conjunctive Canonical form.

(sum of minterms) form

Ans: $F(A, B, C, D) = \bar{A}B + \bar{A}\bar{B} + \bar{A}BC\bar{D} + \bar{A}\bar{B}C\bar{D} +$

$F(A, B, C, D) = \frac{\bar{A}}{\downarrow} + \frac{\bar{A}C\bar{D}}{\downarrow} + \frac{\bar{B}C}{\downarrow}$

	$\bar{A}$ ----	$\bar{A} - C \bar{D}$	0000
$m_0 \leftarrow$	0 0 0 0	0010	0011
$\vdots$	0 0 0 1	0110	1 0 1 0 $\rightarrow m_1$
$\vdots$	0 0 1 0 ✓		01 0 1 1 $\rightarrow m_2$
$\vdots$	0 0 1 1 ✓		
$\vdots$	0 1 0 0		
$\vdots$	0 1 0 1		
$\vdots$	0 1 1 0		
m_7	0 1 1 1		

$$\therefore P(A, B, C, D) = \sum m(0, 1, \dots, 7, 10, 11) \leftarrow \text{Can SOP form.}$$

$$\therefore F(A, B, C, 0) = \text{TTM}(8, 9, 12, 13, 14, 15) \leftarrow \text{Can pos to 9m.}$$

Ex-2 Convert $F(A, B, C) = A \cdot B + \bar{A} \cdot C$ into
Canonical POS term (product of maxterms)

Ans: $F(A, B, C) = \frac{A \cdot B}{\downarrow} + \frac{1}{A} \cdot C$

$\therefore$

$$\begin{array}{r} m_2 \quad 0 \quad 0 \quad 0 \\ m_1 \quad 0 \quad 0 \quad 1 \end{array} \quad \begin{array}{r} 1 \quad 0 \quad 0 \quad m_4 \\ 1 \quad 0 \quad 1 \quad m_5 \end{array}$$



$$F = A \cdot B + \bar{A} \cdot C$$

$$\circ (\bar{A} + B) \cdot (\bar{A} + C)$$

$$F = (\bar{A} + C) \cdot (\bar{A} + B)$$

$$F = \sum m(0, 2, 4, 5)$$

	A	B	C
m_0	0	0	0
m_2	0	1	0


	A	B	C
m_4	1	0	0
m_5	1	0	1

* Two Level Logic:


→ (a) SOP form:

$$F = AB + CD$$

AND-OR Logic

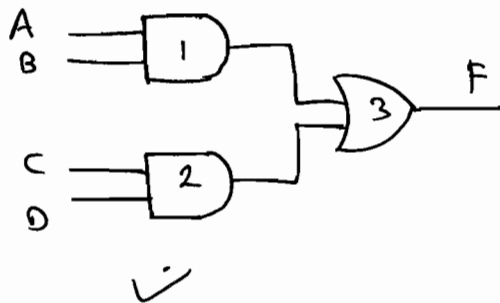



$\equiv$ NAND-NAND Logic

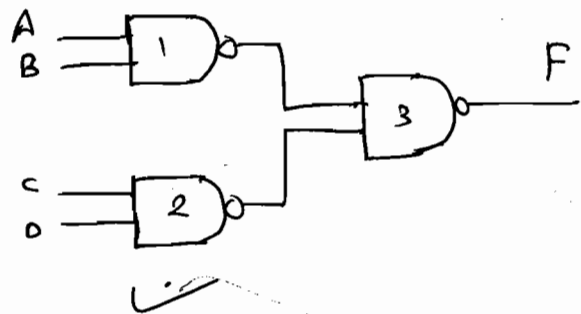

(2) POS form:


$$F = (A+B) \cdot (C+D)$$

OR-AND Logic : $\equiv$ NOR-NOR Logic

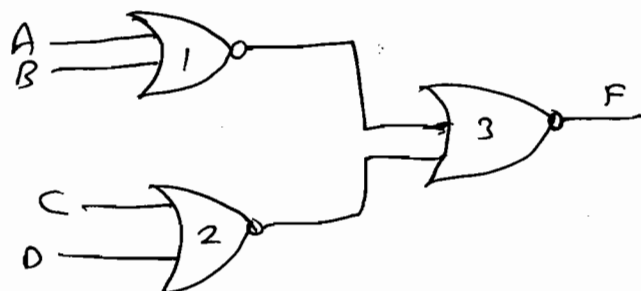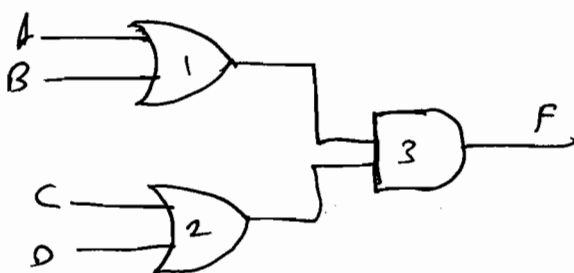

* Hybrid Logic.

$$F = AB + AC = A \cdot (B + C)$$

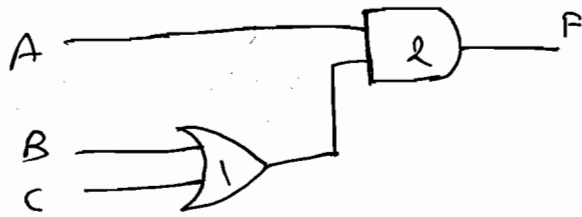

→ The advantages of two level logic is the propagation for all the input variables is same.


☆ Types of Two Level Logic:

- Ex. (1) Degenerative
(2) Non-Degenerative.

① Degenerative.

⇒ There are only one logical operation in o/p, then it is called Degenerative type.

e.g. NAND-NOR Logic

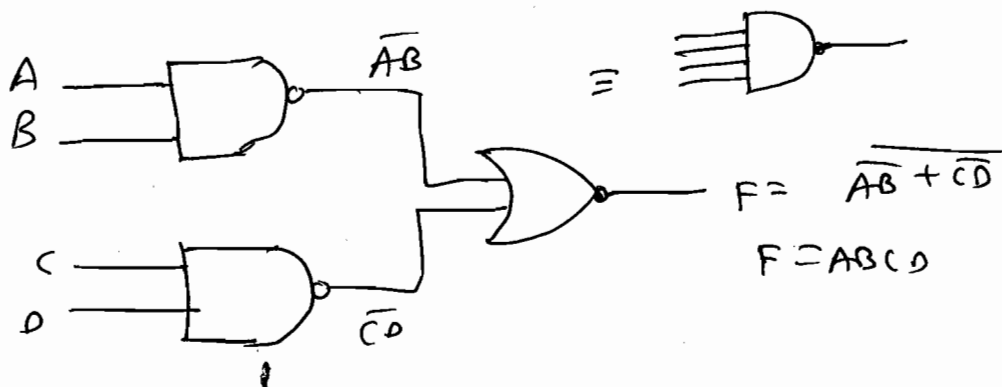

→ The advantages of Degenerative form is the ~~function~~ of the gate is increase.
fun-in