


ANALOG CIRCUITS TEST 2

Number of Questions: 35

Time: 90 min.


Directions for questions 1 to 35: Select the correct alternative from the given choices.

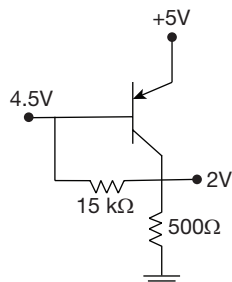1. The purpose of resistance in the emitter circuit of a transistor amplifier is to
 - (A) provide base – emitter bias
 - (B) limit the maximum emitter current
 - (C) is sensitive to changes in β
 - (D) limit the change in I_E .
2. The purpose of emitter capacitor across R_E is to
 - (A) reduce noise in the amplifier
 - (B) protect the transistor
 - (C) avoid voltage gain drop
 - (D) provide biasing
3. What is the effect of cascading the amplifier stages?
 - (1) Increases voltage gain
 - (2) Increases current gain
 - (3) Decreases the bandwidth
 - (4) Increases the bandwidth
 - (A) (1), (2) and (3)
 - (B) (1), (2) and (4)
 - (C) (2) and (3) only
 - (D) (1) and (3) only
4. What are the effects of cascode amplifier stages?
 - (1) Low input impedance
 - (2) High input impedance
 - (3) Wideband amplifier
 - (4) Narrow band amplifier
 - (A) (1) and (3) only
 - (B) (2) and (3) only
 - (C) (1) and (4) only
 - (D) (2) and (4) only
5. When a transistor is used in switching mode then what is the turn – on time?
 - (A) Sum of delay time and rise time
 - (B) Sum of rise time and fall time
 - (C) Sum of delay time and storage time
 - (D) Sum of rise time and storage time
6. A Bipolar junction transistor works in three regions.
 - (1) Cut – off
 - (2) Active
 - (3) Saturation
 If BJT is to be used in amplifier circuit, the region it works in is/are
 - (A) (2) only
 - (B) (1), (2) and (3)
 - (C) (1) and (3) only
 - (D) (2) and (3) only
- 7.




The value of β is

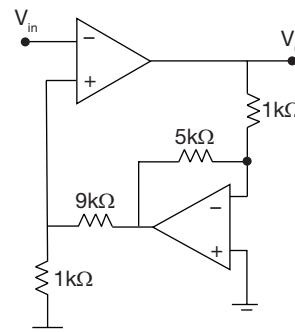- (A) 24
 - (B) 25
 - (C) 26
 - (D) 27
8. For the circuit shown in figure, the voltage gain $\left(\frac{V_o}{V_i}\right)$ is



- (A) $-\frac{1}{2}$
 - (B) 1
 - (C) -2
 - (D) 4
9. Calculate the CMRR (In dB) for the circuit measurements of $V_d = 1\text{mV}$, $V_o = 100\text{mV}$, and $V_c = 0.5\text{mV}$, $V_o = 20\mu\text{V}$
- (A) -6
 - (B) 68
 - (C) 74
 - (D) 80
10. Which one of the following oscillators is well suited for the generation of wide range audio – frequency waves?
- (A) Hartley oscillator
 - (B) Wein – bridge oscillator
 - (C) Colpitt's oscillator
 - (D) Crystal oscillator
11. An amplifier has a d. c power supply of 15 V and draws a current of 12 mA. It produces an output of 8 V peak across load resistance of 500Ω for a signal frequency of 2 KHz. What will be the it's a. c power output?
- (A) 64 mW
 - (B) 0.256 W
 - (C) 32 mW
 - (D) 72 mW
12. An amplifier using BJT has two identical stages each having a lower cut – off frequency of 60 Hz due to coupling capacitor. Then the lower cut – off frequency of the overall amplifier is nearly.
- (A) 48.2 Hz
 - (B) 38 Hz
 - (C) 100 Hz
 - (D) 93 Hz

13.

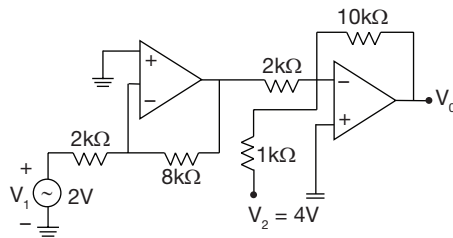


The resulting output V_0 is

- (A) zero (B) -40 V
(C) -10 V (D) -8 V

14. The tuned collector oscillator circuit used in the local oscillator of a radio receiver makes use of an LC tuned circuit with $L_1 = 50\mu\text{H}$, and $C_1 = 250\text{pF}$. Then the frequency of oscillators is


- (A) 14.23 KHz (B) 1.423 MHz
(C) 284 MHz (D) 1.5 MHz

15. The output voltage V_0 is

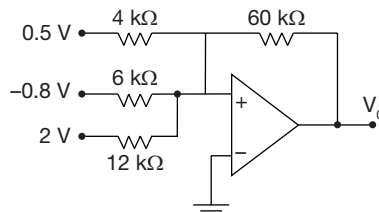


- (A) 9.5 V (B) -8.23 V
(C) 12 V (D) -9.5 V

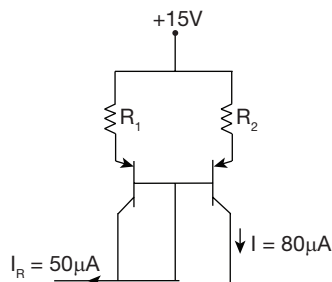16. If $V_{EB} = 0.7\text{ V}$, and $\beta = 100$. Then the ratio of $\frac{R_2}{R_1}$ would be



- (A) 1.6 (B) 1.2
(C) 0.5 (D) 0.625


17.

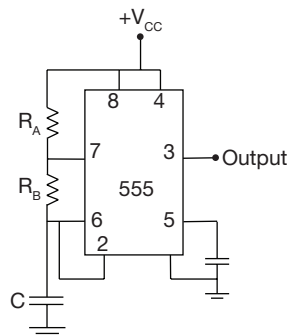

If $R_A = 4.5\text{k}\Omega$, $R_B = 1.5\text{k}\Omega$ and $C = 1\mu\text{F}$, then the output frequency of the 555 timer would be



- (A) 193.33 KHz
(B) 193.33 Hz
(C) 200 Hz
(D) 2 KHz

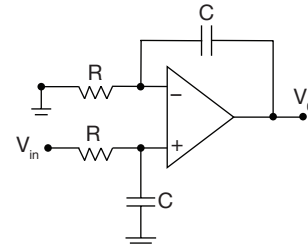18. The op – amp circuit shown in the given figure is




- (A) a high pass circuit
(B) a band – pass circuit
(C) a low pass circuit
(D) an – all pass circuit

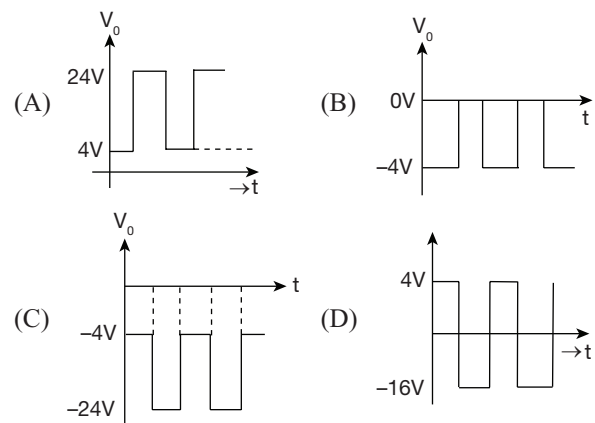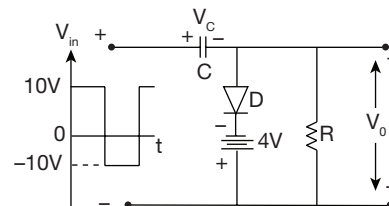19. Determine V_0 for the network of figure shown below,




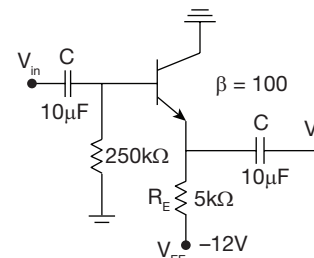20. Determine V_{CEQ} for the network of figure.



- (A) 7.425 V (B) 3.75 V
(C) 4.425 V (D) 5.25 V


21.

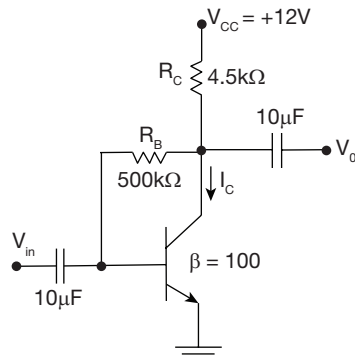

The collector to Emitter voltage is _____

- (A) 6.623 V (B) 5.37 V
(C) 7.23 V (D) 4.8 V

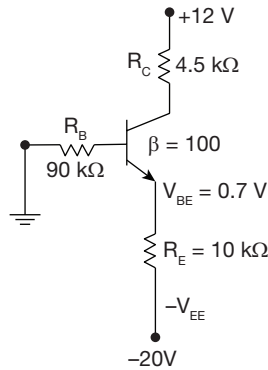
22. For the emitter bias circuit shown in the figure, find the operating point of the circuit?



- (A) 12.5V, 1.5 mA (B) 6.335V, 1.77 mA
(C) 7.35V, 1.77 mA (D) 6.5V, 1.5 mA


 23. In a current amplifier, with $A = 1000$ and $\beta = 0.25$, the input resistance is 100Ω before negative feedback is applied. After negative feedback is applied its input resistance will be

- (A) 0.4Ω (B) 251Ω
(C) 150Ω (D) 100Ω

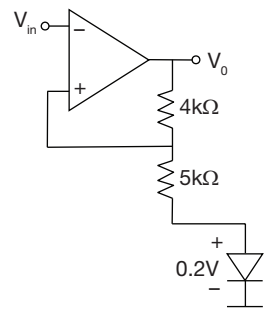
 24. The Schmitt trigger circuit is shown in the below figure. If $V_{sat} = \pm 12V$, the upper threshold voltage would be


- (A) 1.38 V (B) 1.02 V
(C) 13.8 V (D) -15 V

25. In the rectifier circuit shown in figure. The minimum peak – inverse – voltage (PIV) rating of the diode is

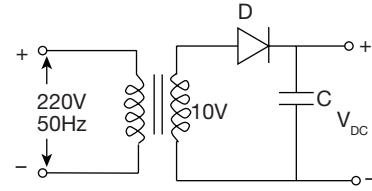
 Consider diode D is ideal.

- (A) 10 V (B) $20\sqrt{2}$ V
(C) $10\sqrt{2}$ V (D) 20V

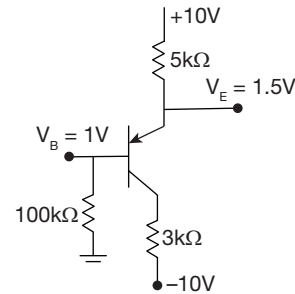
 26. A circuit using the BJT is shown in the below figure, the value of β is, if the transistor is operating in the active region.


- (A) 150 (B) 170
(C) 169 (D) 165

 27. Calculate the ripple of a capacitor filter for a peak rectified voltage of 25V, with $C = 30\mu F$, and a load current of 40mA.


- (A) 16.46% (B) 5.24%
(C) 11.63% (D) 32.92%

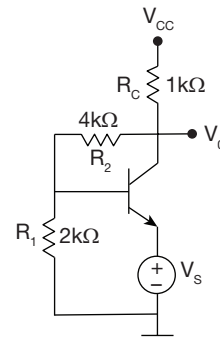28. The type of feedback network and feedback factor for the amplifier shown below is




- (A) Voltage series, $\beta = 1/3$
(B) Voltage shunt, $\beta = 3$
(C) Current shunt, $\beta = 1/3$
(D) Current series, $\beta = 3$

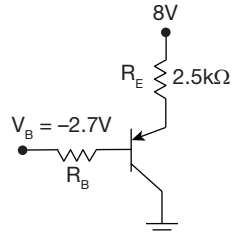 29. For the circuit shown below the value of R_B such that the quiescent voltage is 2.5 V, assume $\beta = 75$ and $V_{BE} = 0.7$ V




- (A) 125 kΩ (B) 225 kΩ
(C) 155 kΩ (D) 93 kΩ

30.

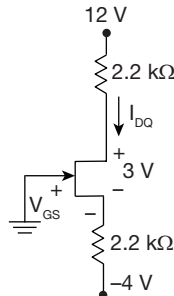

The common – gate configuration has $V_{DS} = 3\text{ V}$ and $V_P = -5\text{ V}$. Then the gate – to – source voltage V_{GS} is
(A) -6.5 V (B) 3.5 V
(C) 4.25 V (D) -2.5 V

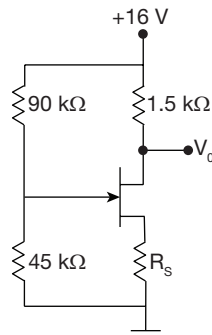
31. The voltage – divider bias configuration shown in the below figure.



If $V_D = 8\text{ V}$ and $V_{GSQ} = -4\text{ V}$, then the value of R_S is
(A) $1.25\text{ k}\Omega$ (B) $1.75\text{ k}\Omega$
(C) $1.5\text{ k}\Omega$ (D) $2\text{ k}\Omega$

Common data for questions 32 and 33:

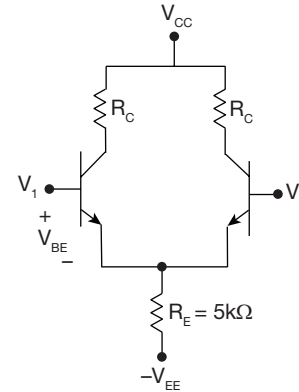Differential amplifier shown in figure, uses a transistor with $\beta = 125$ and is biased at $I_{CQ} = 80\text{ }\mu\text{A}$.



32. Determine the value of R_C if $|A_{DM}| = 500$.


- (A) 150 kΩ (B) 125 kΩ
(C) 200 kΩ (D) 160 kΩ

33. The common mode – rejection ratio (CMRR) of the differential amplifier is

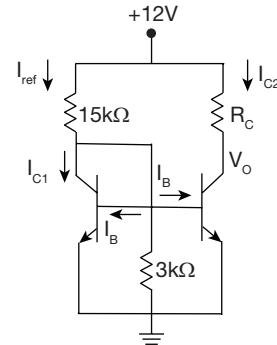- (A) 32.25 (B) 32.25 dB
(C) 40 dB (D) 50

Statement for linked answer questions 34 and 35:

For the circuit shown in figure, consider $V_{BE} = 0.7\text{ V}$; $V_T = 26\text{ mV}$ and $\beta = 125$.



34. Determine the currents I_{C1} and I_{C2}

- (A) $I_{C1} = 0.511\text{ mA}$; $I_{C2} = 0.73\text{ mA}$
(B) $I_{C1} = I_{C2} = 0.511\text{ mA}$
(C) $I_{C1} = 0.753\text{ mA}$, $I_{C2} = 0.511\text{ mA}$
(D) $I_{C1} = I_{C2} = 0.753\text{ mA}$

35. If $V_0 = 8\text{ V}$, then the value of collector resistance R_C would be

- (A) 7.827 kΩ (B) 5.31 kΩ
(C) 7 kΩ (D) 4.32 kΩ

ANSWER KEYS

- | | | | | | | | | | |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 1. D | 2. C | 3. D | 4. B | 5. A | 6. A | 7. A | 8. C | 9. B | 10. B |
| 11. A | 12. D | 13. A | 14. B | 15. D | 16. D | 17. B | 18. C | 19. C | 20. C |
| 21. A | 22. B | 23. A | 24. A | 25. B | 26. C | 27. A | 28. A | 29. C | 30. D |
| 31. B | 32. D | 33. A | 34. B | 35. A | | | | | |

HINTS AND EXPLANATIONS


- Choice (D)
- For D , C analysis R_E advantage it improves the stability.
But A , C analysis R_E decrease the gain.
 $\therefore$ Capacitor across R_E it eliminates the R_E effect
 $\therefore$ Short circuit parallel to R_E Choice (C)
- Effects of cascading amplifier is
 - (1) Voltage gain $A_v = A_{v1} \cdot A_{v2}$
 $\therefore$ It is increases
 - (2) Current gain equal to unity
 - (3) BW decreases
 $\therefore f_L$ and $f_H \downarrow$ Choice (D)
- (1) Cascode amplifier (CE – CB) gives the high input impedance
(2) It is providing high frequency performance of CB
(3) It is also used as wide band amplifier Choice (B)
- $T_{on} = t_d + t_r$ Choice (A)
- Choice (A)
- From the given circuit

$$I_C = \frac{2}{500} = 4 \text{ mA}$$

$$I_B = \frac{4.5 - 2}{15} \text{ mA} = 0.1666 \text{ mA}$$

$$I_C = \beta I_B$$
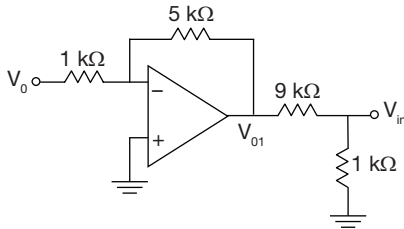
$$\beta = \frac{I_C}{I_B} = 24$$
 Choice (A)
- Applying virtual GND concept and redrawing the given circuit.



$$V_{01} = \frac{-R_f}{R_i} \cdot V_0$$

$$V_{01} = -5V_0$$

$$V_{in} = \frac{1K}{10K} \times V_{01}$$

$$V_{in} = \frac{-1}{2} V_0$$

$$\frac{V_0}{V_{in}} = -2$$

Choice (C)

- From the given data
 $V_d = 1 \text{ mV}$, $V_{od} = 100 \text{ mV}$
 $V_c = 0.5 \text{ mV}$, $V_{oc} = 20 \text{ } \mu\text{V}$

$$\text{But CMRR} = 20 \log_{10} \frac{A_d}{A_c}$$

$$\text{We know } V_{od} = A_d \cdot V_d$$

$$A_d = \frac{100 \text{ mV}}{1 \text{ mV}} = 100$$

$$A_c = \frac{V_{oc}}{V_c} = \frac{20 \times 10^{-6}}{5 \times 10^{-4}}$$

$$A_c = 4 \times 10^{-2} = 0.04$$

$$\text{CMRR in dB} = 20 \log \left\{ \frac{100}{0.04} \right\} = 68 \text{ dB} \quad \text{Choice (B)}$$

- Audio frequency oscillators (<20 KHz)

(1) RC – phase shift

(2) Wein bridge

RF oscillators (> 20 KHz)

(1) Colpitt's oscillator

(2) Crystal oscillator

(3) Hartly oscillator

(4) Clapp oscillator

.....etc

Choice (B)

$$11. P_{0a.c} = \frac{(V_0 / \sqrt{2})^2}{R_L}$$

$$= \frac{V_0^2}{2R_L} = \frac{(8)^2}{2 \times 500} = 64 \text{ mW}$$

Choice (A)

$$12. \text{ We know } f_\ell^1 = \frac{f_\ell}{\sqrt{2^{1/n} - 1}}$$

Where $n = 2$ and $f_1 = 60 \text{ Hz}$


$$f_\ell^1 = \frac{60}{\sqrt{2^{\frac{1}{2}} - 1}} = 93.226 \text{ Hz}$$

$$f_\ell^1 \approx 93 \text{ Hz}$$

$$\text{And } f_H^1 = f_H \cdot \sqrt{2^{\frac{1}{n}} - 1} \text{ Hz}$$

Choice (D)

-

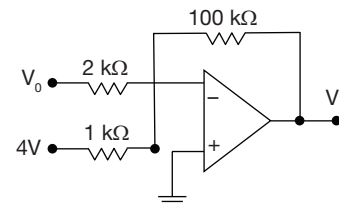The o/p voltage of 1st stage is V_{01}

$$V_{01} = \frac{-8}{2} \times 2 = -8 \text{ volts}$$

Redrawing the given circuit

$$V_0 = -5 \times (-8) - 10 \times 4 = 40 - 40 = 0 \text{ V}$$

Choice (A)

14. Frequency of oscillation, $f = \frac{1}{2\pi\sqrt{L_1 C_1}}$


$$f = \frac{1}{2\pi\sqrt{50 \times 10^{-6} \times 250 \times 10^{-12}}}$$

$$= \frac{1 \times 10^8}{2\pi\sqrt{125}} = 1.426 \text{ MHz}$$

Choice (B)

15. Applying virtual GND concept
 $V_+ = V_- = 0V$

$\therefore$ Redrawing given circuit

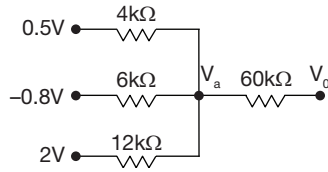

Applying KCL at node Va

$$\frac{V_a - 0.5}{4K} + \frac{V_a + 0.8}{6K} + \frac{V_a - 2}{12K} + \frac{V_a - V_0}{60K} = 0$$

But $V_a = 0V$


$$-0.5 \times 15 + 0.8 \times 10 - 2 \times 5 - V_0 = 0$$

$$-V_0 = +7.5 + 10 - 8 = 0$$

$$V_0 = -9.5V$$

Choice (D)

16. Redrawing the given circuit

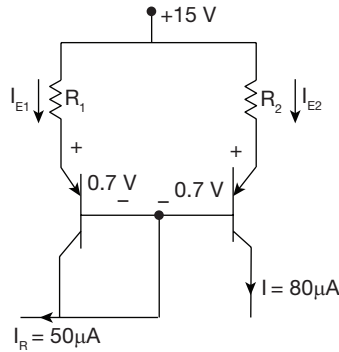

We know $I_E \approx I_C$

$$I_{E2} = I = \frac{15 - 0.7}{R_2}$$

$$R_2 = \frac{14.3}{80} \times 10^6 \Omega$$

$$R_2 = 178.75 \text{ K}\Omega$$

Applying KVL to the input loop

$$I_{E1} = I_C + I_B$$

$$I_R \approx I_{E1}$$

$$50 \times 10^{-6} = \frac{15 - 0.7}{R_1}$$

$$R_1 = 286 \text{ K}\Omega$$

$$\frac{R_2}{R_1} = 0.625$$

Choice (D)

17. Given circuit indicates an Astable multi vibrator

We know $T = t_{\text{high}} + t_{\text{low}}$


Both R_A and R_B are in charging path, but only R_B is in the discharge path.

$$\therefore T = 0.69 (R_A + 2R_B)C$$

$$\therefore f = \frac{1}{T} = \frac{1.45}{(R_A + 2R_B)C}$$

$$f = \frac{1.45}{(4.5 + 3) \times 1 \times 10^{-3}} = 193.33 \text{ Hz} \quad \text{Choice (B)}$$

- 18.

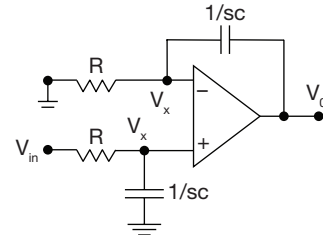

$$V_x = \frac{1}{sC} \times \frac{V_{in}}{R + 1/sC}$$

$$V_x = \frac{V_{in}}{1 + sRC}$$

Apply virtual GND concept

$$V_+ = V_- = V_x$$

$$\frac{V_x}{R} + \frac{V_x - V_0}{1/sC} = 0$$

$$V_x \left[\frac{1}{R} + sC \right] = sC V_0$$

$$V_x [1 + RCs] = sRC V_0$$

$$V_{in} = sRC V_0$$

$$\frac{V_0(s)}{V_{in}(s)} = \frac{1}{sRC}$$

The transfer function indicates LPF

Choice (C)

19. For a +Ve cycle

Diode D $\rightarrow$ ON

$$V_0 = -4 \text{ Volts}$$

Voltage across capacitor


$$10 - V_C + 4 = 0$$

$$V_C = 14V$$

for a $-V_e$ cycle


D $\rightarrow$ OFF

$$\therefore V_0 = -10 - 14 = -24V$$

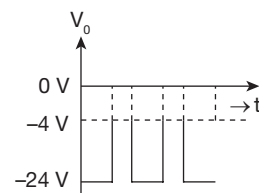

Choice (C)

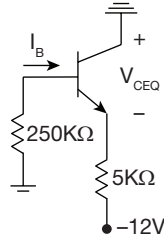20. Redrawing the given circuit for D.C analysis $C \rightarrow$ Open circuit



$$I_B = \frac{12 - 0.7}{250 + 101 \times 5} \text{ mA} = 15 \mu\text{A}$$


Applying KVL to O/P loop.

$$-V_{CEQ} - I_E \cdot R_E + 12 = 0$$

$$V_{CEQ} = 12 - 101 \times 15 \times 10^{-6} \times 5 \times 10^3 = 4.425 \text{ Volts}$$

Choice (C)

21. Redrawing given circuit

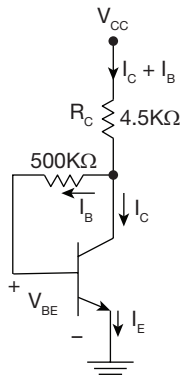

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1 + \beta)R_C}$$

$$= \frac{12 - 0.7}{500 + 454.5} \text{ mA}$$

$$= 11.83 \mu\text{A}$$

$$I_C = \beta \cdot I_B = 1.183 \text{ mA}$$

$$V_{CE} = V_{CC} - (I_B + I_C) \cdot R_C$$

$$= 12 - 5.378$$

$$= 6.623 \text{ Volts}$$

Choice (A)

22. We know $I_C \approx I_E$
- $$\therefore I_C = \frac{V_{EE} - V_{BE}}{R_E + R_B / \beta} = \frac{20 - 0.7}{10 + 0.9} \text{ mA}$$

$$I_C = 1.77 \text{ mA}$$

Applying KVL to the output loop

$$12 - 4.5 \times 1.77 - V_{CE} - 10 \times 1.77 + 20 = 0$$

$$V_{CE} = 6.335 \text{ Volts}$$

$$Q - \text{Point } (V_{CE}, I_C) = (6.335 \text{ V}, 1.77 \text{ mA})$$

Choice (B)

23. From the given data

$$A = 1000; \beta = 0.25$$

$$R_i = 80 \Omega$$

$$1 + A\beta = 1 + 1000 \times 0.25 = 251$$

Current amplifier

$i/p \Rightarrow$ current source

$o/p \Rightarrow$ current source

i.e, it is a current shunt amplifier

$\therefore R_i \Rightarrow$ decreases

$R_o \Rightarrow$ increases


$$\therefore R_{if} = \frac{R_i}{1 + A\beta} = \frac{100}{251} \approx 0.4 \Omega$$

Choice (A)

24. Max. output $V_o = \pm V_{sat} = \pm 12 \text{ V}$

If $V_{in} = V_{UT}$, redrawing the given circuit.

$$V_+ = V_- = V_{UT}$$

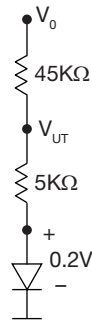

Applying nodal analysis at node V_{UT}

$$\frac{V_{UT} - V_o}{45K} + \frac{V_{UT} - 0.2}{5K} = 0$$

$$V_{UT} - V_o + 9V_{UT} - 1.8 = 0$$

$$10V_{UT} = V_o + 1.8$$

$$\text{But } V_o = +V_{sat} = +12 \text{ V}$$

$$V_{UT} = 1.38 \text{ Volts}$$


Choice (A)

25. During +Ve half cycle

$D \rightarrow$ ON

$\therefore$ Voltage across capacitor


$$V_C = 10 \text{ Vrms.}$$

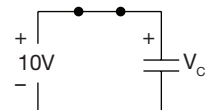

$$\therefore V_C = 10 \text{ V}_{rms}$$

During -Ve half cycle

$D \rightarrow$ OFF

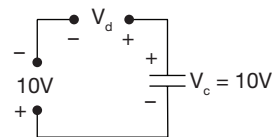

$$\text{PIV} = V_d = (10 + 10) \text{ V}_{rms}$$

$$= 20\sqrt{2} \text{ volts.}$$

Choice (B)

26. $I_E = \frac{V_{CC} - V_E}{R_E}$

$$= \frac{10 - 1.5}{5} \text{ mA} = 1.7 \text{ mA}$$

$$I_B = \frac{V_B}{R_B} = \frac{1}{100} \text{ mA} = 0.01 \text{ mA}$$

3.160 | Analog Circuits Test 2

But we know $I_E = I_B + I_C$

$$I_E = (1 + \beta) \cdot I_B$$

$$(1 + \beta) = \frac{I_E}{I_B} \quad I_E/I_B = 170$$

$$\beta = 169$$

Choice (C)

27. We know $r = \frac{V_{r(rms)}}{V_{dc}} = \frac{2.4I_{dc}}{C.V_{dc}} \times 100\%$

But $V_{dc} = V_m - 4.17 \frac{I_{dc}}{C}$


$$= 25 - 4.17 \times \frac{40 \times 10^{-6}}{30 \times 10^{-6}} = 19.44 \text{ volts}$$

$$r = \frac{2.4 \times 40 \times 10^{-6}}{30 \times 10^{-6} \times 19.44} \times 100\%$$

$$r = 16.46\%$$

Choice (A)

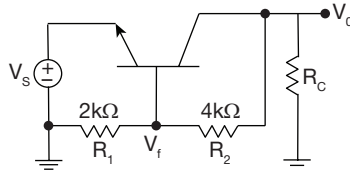28. Consider the given CB – amplifier with A. C equivalent



From the given circuit

i/p source voltage (Sereis) variable

o/p source voltage

∴ Voltage series feedback (or) voltage amplifier

$$\beta = \frac{V_f}{V_o} = \frac{R_1}{R_1 + R_2} = \frac{2}{2 + 4} = 1/3 \quad \text{Choice (A)}$$

29. Given

$$V_{ECQ} = 2.5V$$

$$I_E = \frac{8 - 2.5}{2.5} \text{ mA} = 2.2 \text{ mA}$$


$$I_E = I_B + I_C$$

$$I_E = I_B [1 + \beta]$$

$$I_B = 28.94 \mu A$$

Given $V_E = 2.5V$

Applying KVL to the input loop

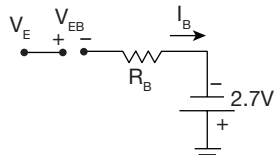

$$V_E - V_{BE} - I_B R_B + 2.7 = 0$$

$$2.5 - 0.7 + 2.7 = I_B R_B$$

$$R_B \leq \frac{4.5}{I_B} = 155.4545 \text{ K}\Omega$$

$$R_B = 155 \text{ K}\Omega$$

Choice (C)

30. Applying KVL to the output loop

$$12 - 2.2 \text{ K}\Omega \cdot I_D - V_{DS} - 2.2 \text{ K}\Omega \cdot I_D + 4 = 0$$

$$16 - 3 = 4.4 \times 10^3 \times I_D$$

$$I_D = \frac{13}{44} \text{ mA} = 2.9545 \text{ mA}$$

Applying KVL to the input loop

$$-V_{GS} - 2.2 \text{ K}\Omega \cdot I_D + 4 = 0$$


$$V_{GS} = 4 - 2.2 \times 2.9545 = -2.5 \text{ V}$$

Choice (D)

31. $V_G = \frac{45}{90 + 45} \times 16 = 5.333 \text{ V}$

$$R_G = (45 \text{ K} \parallel 90 \text{ K}) = 30 \text{ K}\Omega$$

Redrawing the given circuit

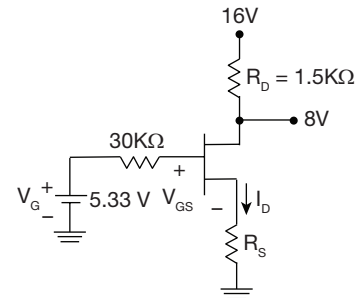

$$I_D = \frac{16 - 8}{1.5} \text{ mA}$$

$$I_D = 5.333 \text{ mA}$$

From the input loop

$$V_{GS} = V_G - I_D \cdot R_S$$

$$R_S = \frac{V_G - V_{GS}}{I_D} = \frac{9.333}{5.333} \text{ k}\Omega$$

$$R_S = 1.75 \text{ k}\Omega$$

Choice (B)

32. Given $I_{CQ} = 80 \mu A$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{80 \times 10^{-6}}{25.6 \times 10^{-3}} = 30125 \text{ m}\Omega$$

$$\text{But } A_{DM} = -g_m \cdot R_C$$

$$R_C = \frac{|A_{DM}|}{g_m} = \frac{500}{3.125} \text{ K}\Omega$$

$$R_C = 160 \text{ K}\Omega$$

Choice (D)

33. From the given data

$$I_{CQ} = 80 \mu A$$

$$V_T \approx 26 \text{ mV}$$

$$g_m = \frac{I_{CQ}}{V_T} = 3.125 \text{ m}\Omega$$

$$\text{CMRR} = \left| \frac{A_{DM}}{A_{CM}} \right| = 1 + 2g_m \cdot R_E$$

$$= 1 + 2 \times 3.125 \times 10^{-3} \times 5 \times 10^3$$

$$= 1 + 31.25 = 32.25$$

Choice (A)

34. From the given data

$$\beta = 125 \text{ and } V_{BE} = 0.7 \text{ V}$$

Applying KVL to the input loop

$$V_{CC} - R_{C1} I_{\text{ref}} - V_{BE} = 0$$

$$I_{ref} = \frac{V_{CC} - V_{BE}}{R_{C1}} = \frac{12 - 0.7}{15} \text{ mA} = 0.753 \text{ mA}$$

$$\text{But } I_{ref} = I_{C1} + 2I_B + I_R$$

$$I_R = \frac{V_{BE}}{3\text{K}\Omega} = \frac{0.7}{3} \text{ mA}$$

$$I_R = 0.233 \text{ mA}$$

$$I_{ref} - I_R = I_{C1} \left[1 + \frac{2}{\beta} \right]$$

$$\frac{0.5199 \times 10^{-3}}{1.016} = I_{C1}$$

$$I_{C1} = 0.511 \text{ mA}$$

$$\text{But } I_{C1} = I_{C2} \text{ (Due to mirror effect)}$$

$$I_{C1} = I_{C2} = 0.511 \text{ mA}$$

Choice (B)

35. Applying KVL to the output loop

$$V_{CC} - I_{C2} R_C - V_0 = 0$$

$$R_C = \frac{V_{CC} - V_0}{I_{C2}} = \frac{4}{0.511} \text{ k}\Omega = 7.827 \text{ k}\Omega \quad \text{Choice (A)}$$