

ANALOG ELECTRONICS TEST 5

Number of Questions: 25


Time: 60 min.

Directions for questions 1 to 25: Select the correct alternative from the given choices.

- Class AB operation is often used in power amplifiers in order to
 - get maximum efficiency
 - reduce collector dissipation
 - remove even harmonics
 - overcome a crossover distortion
- Calculate the harmonic distortion components for an output signal having fundamental amplitude of 3V, second harmonic amplitude of 0.3V. Third harmonic amplitude of 0.03V
 - 3%
 - 10%
 - 11%
 - 9%
- Single stage transformer coupled class A amplifier uses a transistor with maximum dissipation capability of 3 watts. The maximum a.c power in the load is
 - 1.5 watt
 - 0.75 watt
 - 3 watt
 - 6 watt
- Higher order active filters are used for
 - variable bandwidth
 - variable impedance
 - variable roll-off rate
 - all of the above
- Match List-I with List-II where List-I contains devices and List-II contains characteristic of the device

List-I	List-II
(p) BJT	(1) negative conductance device
(q) UJT	(2) current controlled device
(r) FET	(3) voltage controlled device
(s) IMPATT diode	(4) conductivity modulation device

- $p - 2, q - 4, r - 3, s - 1$
 - $p - 3, q - 1, r - 2, s - 4$
 - $p - 2, q - 1, r - 3, s - 4$
 - $p - 3, q - 4, r - 2, s - 1$
- The most commonly used amplifier in sample and hold circuits is
 - an inverting amplifier with a gain of 100
 - a unity gain inverting amplifier
 - an non-inverting amplifier with a gain of 10
 - a unit gain non-inverting amplifier
 - A class C transistor amplifier is operating at 200 kHz. The transistor is conducting for 1 μ sec in each cycle. Transistor has $V_{CE(sat)} = 0.2$ V, $I_{C(sat)} = 80$ mA. Find average power dissipation. [assume that output swing over the entire load line]
 - 16 mW
 - 8 mW
 - 3.2 mW
 - 11.3 mW
 - In below circuit Op-Amp is ideal. If $\beta = 50$, the total current supplied by the 12V.

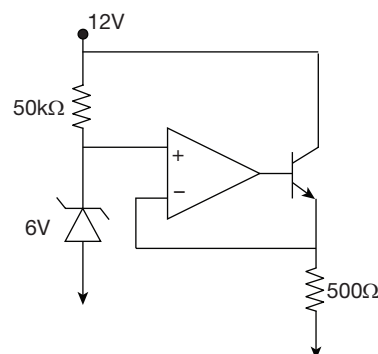

- 12.12 mA
- 11.88 mA
- 12 mA
- 11.6 mA

- Match List-I with List-II where List-I contains oscillator and List-II has characteristics.

List-I	List-II
(p) clapp oscillator	(1) RC oscillator for audio frequency applications
(q) colpittes oscillator	(2) RF oscillator: Two inductances and one capacitance on the reactance network.
(r) Hartley oscillator	(3) LC oscillator for RF frequency: Three capacitances and one inductance in the resistance network.
(s) wein bridge oscillator	(4) RF oscillator: Two capacitance and one inductance as the reactance network.

- $p - 1, q - 2, r - 3, s - 4$
- $p - 4, q - 3, r - 2, s - 1$
- $p - 1, q - 4, r - 2, s - 3$
- $p - 3, q - 2, r - 1, s - 4$

- The time base voltage of an oscilloscope can be generated by using
 - time delay circuit
 - a controlled circuit
 - boot strap integrator circuit
 - miller sweep circuit
 - 2, 3, 4 only
 - 1, 3, 4 only
 - 1, 2, 3 only
 - All the above
- A power amplifier delivers 10W output at 50% of collector efficiency. If the maximum allowable junction temperature is 125°C, then maximum thermal resistance θ_{jc} that can be tolerated [$\therefore$ ambient temperature = 25°C]
 - 20° C/W
 - 5° C/W
 - 10° C/W
 - 40° C/W
- In a complementary symmetry transistor emitter follower type class B push-pull amplifier works at power conversion efficiency of 40%; given that $R_L = 10 \Omega$ and

peak output voltage V_m across R_L is volts, the dc power drawn by each transistor is

- (A) 8W (B) 12W
(C) 20W (D) 16W


13. In class B push-pull operation the power delivered to the load $R_L = 10 \Omega$ is $P_{ac} = 20W$. Then peak load current is

- (A) $\sqrt{2}A$ (B) 2A
(C) 1A (D) 0.5A

14. A colpitt's oscillator has a coil with an inductance of $25 \mu H$ and is tuned by a capacitor of $150 pF$ across the amplifier input and $50 pF$ across the output. The minimum gain for maintaining oscillation is


- (A) 1/3 (B) 3
(C) 1/2 (D) 6

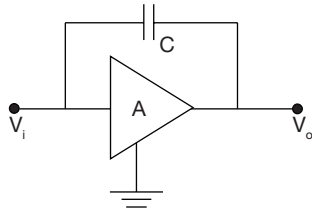15. An amplifier of gain A is bridge by a capacitance C as shown in below circuit, then the effective input capacitance is



- (A) C/A (B) AC
(C) $C(1 + A)$ (D) $C(1 - A)$

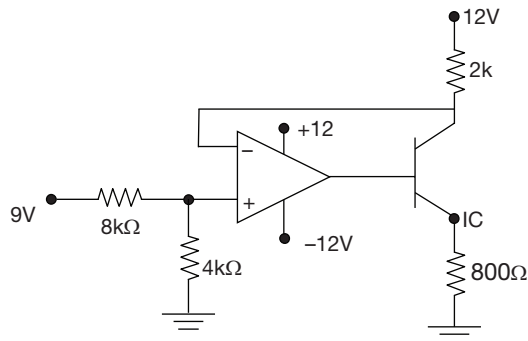16. In below circuit, find I_C if $\beta = 50$



- (A) 4.5 mA (B) 1.5 mA
(C) 4.41 mA (D) 3 mA

17. Consider the following statements with reference to a CE transistor amplifier

- (1) high voltage and current gains
(2) The use of step-up transformer
(3) The use of negative feedback
(4) The conversion of d.c power to a.c power


The power gain is due to

- (A) 1, 2 and 3 (B) 2, 3 and 4
(C) 1 and 4 only (D) All the above

18. Given circuit is to be used as a divided by 2 network. The frequency of the input trigger signal is 4 kHz. If the value of capacitor is 1 nF then value of R is

- (A) 39 kΩ (B) 120 kΩ
(C) 140 kΩ (D) 272 kΩ

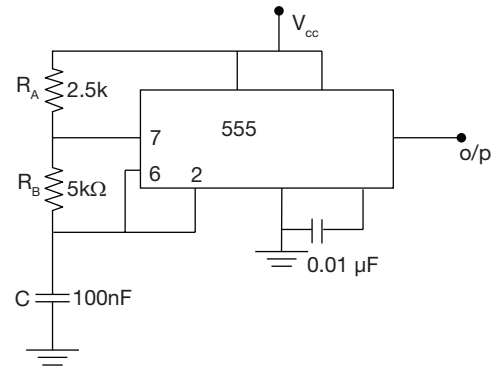19. In astable multivibrator, determine free running frequency f_o




- (A) 635 Hz (B) 1.27 kHz
(C) 1.16 kHz (D) 2.32 kHz

20. In the Astable multivibrator $R_A = 2.5 k\Omega$, $R_B = 5 k\Omega$ and $C = 0.1 \mu F$ then duty cycle is


- (A) 50% (B) 60%
(C) 40% (D) 80%

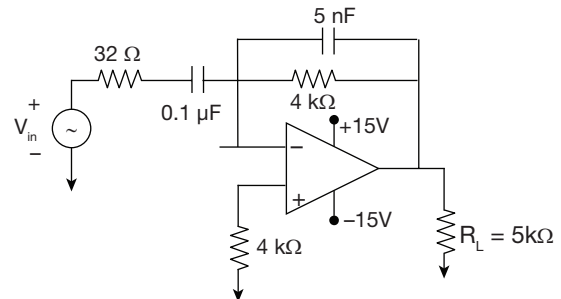21. Differentiation amplifier is given below. Find the unity gain frequency (f_a) and gain limiting frequency (f_b).



- (A) $f_a = 49.7 KHz, f_b = 398 KHz$
(B) $f_a = 398 Hz, f_b = 49.7 KHz$
(C) $f_a = 398 KHz, f_b = 49.7 Hz$
(D) $f_a = 49.7 Hz, f_b = 398 Hz$

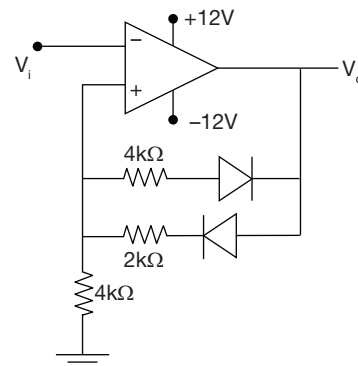
22. Hysteresis loop width of below Schmitt trigger is [diodes and Op-Amps are ideal]



- (A) 24V (B) 8V
(C) -6V (D) 14V


3.140 | Analog Electronics Test 5

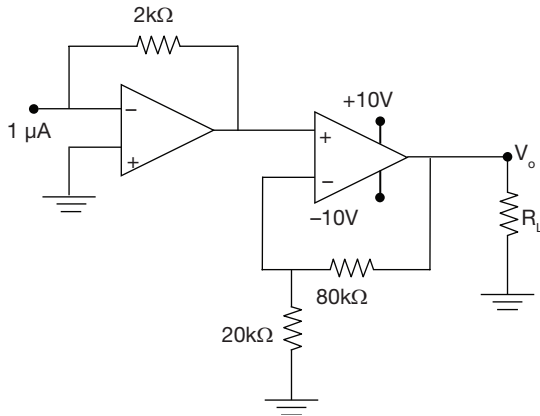23. An ideal sawtooth voltage waveform of frequency 1 kHz and amplitude 5V is generated by charging capacitor of 4 mF in every cycle. The charging requires
 (A) constant voltage source of 5V for 1 ms
 (B) constant voltage source of 5V for 2 ms
 (C) constant current source of 20A for 1 ms
 (D) constant current source of 20A for 2 ms
24. The output voltage V_o of the below given figure



- (A) 0.1 mV
 (B) 1 mV
 (C) 10 mV
 (D) 10 V

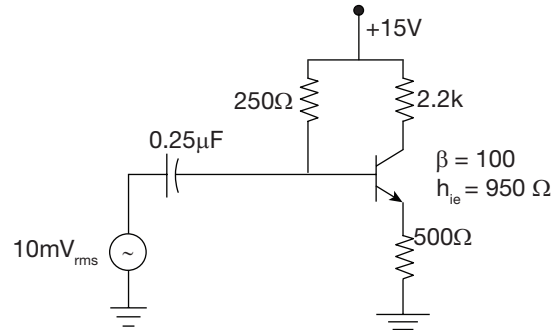25. Find the voltage gain of below circuit.



- (A) 0.0689
 (B) 1.94×10^{-3}
 (C) -0.028
 (D) 0.087

ANSWER KEYS

- | | | | | | | | | | |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 1. D | 2. B | 3. C | 4. C | 5. C | 6. D | 7. C | 8. B | 9. C | 10. B |
| 11. C | 12. D | 13. B | 14. B | 15. D | 16. C | 17. C | 18. D | 19. C | 20. B |
| 21. B | 22. D | 23. C | 24. C | 25. B | | | | | |

HINTS AND EXPLANATIONS

1. Choice (D)

$$2. \%D_2 = \frac{|A_2|}{|A_1|} \times 100\% = \frac{0.3}{3} \times 100\% = 10\%$$

$$\%D_3 = \frac{|A_3|}{|A_1|} \times 100\% = \frac{0.03}{3} \times 100\% = 1\%$$

$$\text{Total harmonic distortion \%} = \sqrt{D_2^2 + D_3^2} \times 100\%$$

$$= \sqrt{(0.1)^2 + (0.01)^2} \times 100\% = 10.04\% \quad \text{Choice (B)}$$

3. In transformer action we assume ideal power transfer from primary winding to secondary i.e. power loss.

Choice (C)

4. High order active filters are used for variable roll-off rate.

Choice (C)

5. UJT is negative conductance device.

Choice (C)

6. Choice (D)

7. Given that $f = 200$ kHz


$$T = \frac{1}{f} = 5 \mu\text{sec}$$

$$P_{\text{avg}} = \frac{T_{\text{on}}}{T} \times I_{C(\text{sat})} \times V_{CE(\text{sat})}$$

$$= \frac{1}{5} \times 0.2 \times 80 \times 10^{-3} = 3.2 \text{ mW}$$

Choice (C)

- 8.

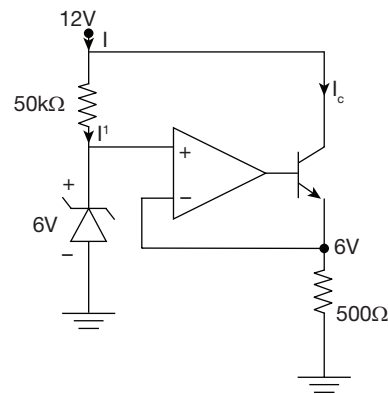

$$I = I^1 + I_C; I_E = \frac{6}{500} = 12 \text{ mA}$$

$$I_C = \alpha I_E = \frac{\beta}{1 + \beta} I_E = \frac{50}{51} \times 12 \times 10^{-3} = 11.76 \text{ mA}$$

$$I^1 = \frac{12 - 6}{50} \text{ mA} = \frac{6}{50} \text{ mA} = 0.12 \text{ mA}$$

$$I = I_C + I^1 = 11.88 \text{ mA}$$

Choice (B)

9. Choice (C)

10. Choice (B)

11. $P = 10\text{W}$, $\eta = 50\%$, $T_a = 25^\circ\text{C}$, $T_i = 125^\circ\text{C}$

$$\theta_{jc} P_D = T_j - T_a$$

$$\theta_{jc} = \frac{100}{10} = 10^\circ \text{C/W}$$

Choice (C)

$$12. P = \frac{V_m^2}{R_L} = \frac{400}{10} = 40; \eta = 40\%$$

$\Rightarrow$ power drawn by each transistor is 16W.

Choice (D)

$$13. P_{ac} = I_{ac}^2 R_L \Rightarrow 20 = I_{ac}^2 (10)$$

$$\Rightarrow I_{ac} = \sqrt{2}$$

$$\Rightarrow I_m = \sqrt{2} I_{ac} = 2$$

Choice (B)

14. For maintaining oscillation $A_{loop} \geq 1$

$$\Rightarrow A_{loop} = 1 = A_{v_o} \frac{C_2}{C_1}$$

$$\Rightarrow A_{v_o} = \frac{150}{50} = 3$$

Choice (B)


15. Assuming voltage amplifier with zero input current

$$Q_i = C(V_i - AV_i)$$

$$\Rightarrow \frac{Q_i}{V_i} = C_{eq} = C(1 - A)$$

Choice (D)

16.

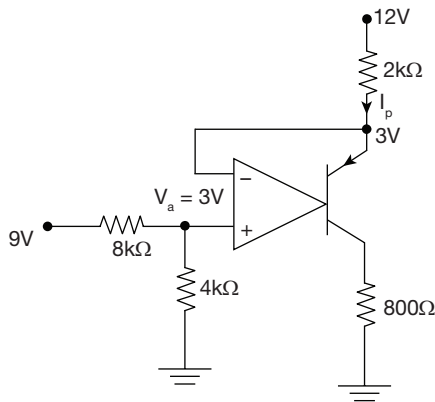

$$V_a = \frac{9 \times 4}{12} = 3\text{V}$$

$$I_E = \left(\frac{12 - 3}{2} \right) \text{mA} = 4.5 \text{mA}$$

$$I_C = \alpha I_E = \frac{\beta}{1 + \beta} I_E = \frac{50}{51} \times 4.5 = 4.41 \text{mA} \quad \text{Choice (C)}$$

17. Power gain is due to high voltage and current gains and the conversion of d.c power to a.c power Choice (C)

$$18. t_p = 1.2T = \frac{1.2}{4} \times 10^{-3} = 1.1 RC$$

$$= \frac{1.2 \times 10^{-3}}{4 \times 1.1 \times 10^{-9}} = R = 272 \text{k}\Omega$$

Choice (D)

19. Free running oscillator frequency

$$f_o = \frac{1}{T} = \frac{1.45}{(R_A + 2R_B)C}$$

$$= \frac{1.45}{(2.5 + 2 \times 5) \times 10^3 \times 100 \times 10^{-9}}$$

$$= \frac{1.45 \times 10^4}{12.5} = 1.16 \text{kHz}$$

Choice (C)

$$20. \text{Duty cycle} = \frac{T_{on}}{T_{off}} \times 100\% = \frac{R_A + R_B}{R_A + 2R_B} \times 100$$

$$= \frac{2.5 + 5}{2.5 + 5 \times 2} \times 100 = \frac{7.5}{12.5} \times 100 = 60\%$$

Choice (B)


$$21. f_a = \frac{1}{2\pi R_F C_1}$$

$$= \frac{1}{2\pi \times 4 \times 10^3 \times 0.1 \times 10^{-6}} = 398 \text{Hz}$$

$$f_b = \frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi \times 32 \times 0.1 \times 10^{-6}} = 49.7 \text{kHz}$$

Choice (B)

22.

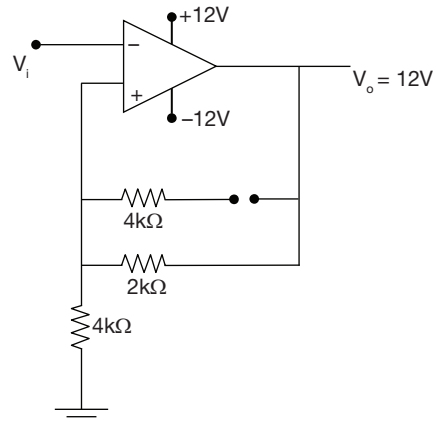

If $V_o = +12\text{V}$ then

$$V_1 = \frac{12 \times 4}{6} = 8\text{V}$$

If $V_o = -12\text{V}$ then

$$V_2 = \frac{-12 \times 4}{8} = -6\text{V}$$

$$V_H = V_1 - V_2 = 14\text{V}$$

Choice (D)


$$23. T = \frac{1}{f} = 1\text{ms}$$

$$I_c = c \cdot \frac{dV_c}{dt}$$

$$= \frac{4 \times 10^{-3} \times 5}{10^{-3}} = 20\text{A}$$

Choice (C)

24.

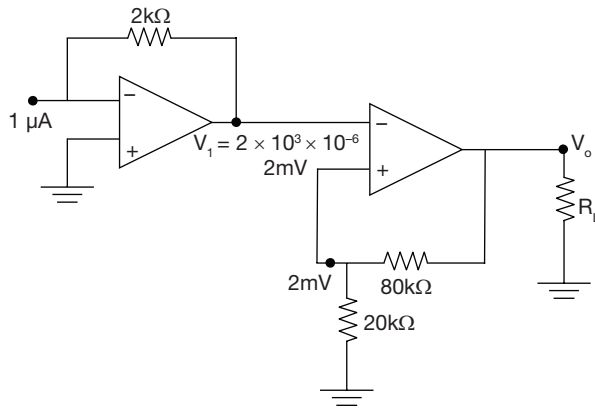

$$\frac{V_o \times 20}{100} = 2 \times 10^{-3}$$

$$V_o = 10 \text{ mV}$$

Choice (C)

$$25. A = \frac{I_o}{I_i} = \frac{-h_{fe}}{h_{ie} + R_E}$$

$$= \frac{-100}{950 + 500} = \frac{-100}{1450} = -0.689$$

$$\beta = \frac{V_f}{I_o} = -R_E = -500$$

$$A_f = \frac{A}{1 + A\beta} = \frac{-0.689}{1 + \beta A} = 1.94 \times 10^{-3}$$

Choice (B)