

CHAPTER

3.2

BASIC BJT CIRCUITS

Use $V_{BE(ON)} = 0.7 \text{ V}$, $V_{CE(Sat)} = 0.2 \text{ V}$ for *npn* transistor if not given in problem.

- (A) 8.4 V
(C) 4.1 V

- (B) 6.2 V
(D) None of the above

Statement for Q.1-4:

The common-emitter current gain of the transistor is $\beta = 75$. The voltage V_{BE} in ON state is 0.7 V.

1. I_E , $R_C = ?$

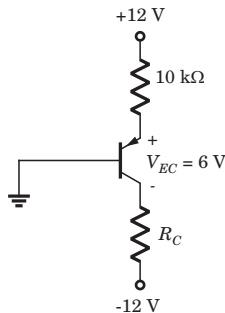


Fig. P3.3.1

- (A) 1.46 mA, 6.74 kW
(C) 1.13 mA, 5.98 kW
- (B) 0.987 mA, 3.04 kW
(D) None of the above

2. $V_{EC} = ?$

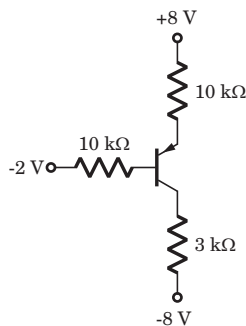


Fig. P3.3.2

3. I_C , $R_C = ?$

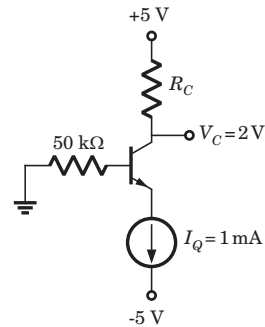


Fig. P3.3.3

- (A) 0.987 mA, 3.04 kΩ
(B) 1.013 mA, 2.96 kΩ
(C) 0.946 mA, 4.18 kΩ
(D) 1.057 mA, 3.96 kΩ

4. $V_C = ?$

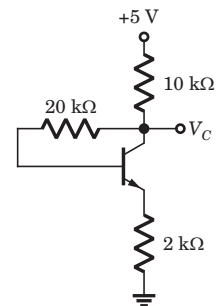


Fig. P3.3.4

- (A) 1.49 V
(C) 1.78 V
- (B) 2.9 V
(D) 2.3 V

Statement for Q.5-6:

In the circuit of fig.P3.3.5-6 $V_B = -1$ V

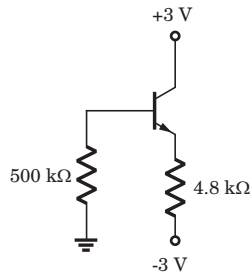


Fig. P3.3.5-6

5. $\beta = ?$

- (A) 103.4 (B) 135.5
(C) 134.5 (D) 102.4

6. $V_{CE} = ?$

- (A) 6.4 V (B) 4.7 V
(C) 1.3 V (D) 4.2 V

7. In the circuit shown in fig. P3.3.7 voltage $V_E = 4$ V. The value of α and β are respectively

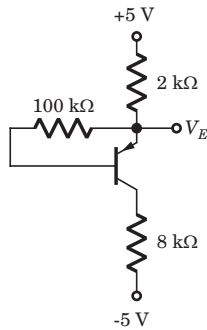


Fig. P3.3.7

- (A) 0.943, 17.54 (B) 0.914, 17.54
(C) 0.914, 11.63 (D) 0.914, 11.63

Statement for Q.8-10:

For the transistor in circuit shown in fig. P3.3.8-10, $\beta = 200$. Determine the value of I_E and I_C for given value of V_B in question.

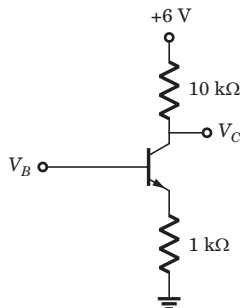


Fig. P3.3.8-10

8. $V_B = 0$ V

- (A) 6.43 mA, 2.4 V (B) 2.18 mA, 3.4 V
(C) 0 A, 6 V (D) None of the above

9. $V_B = 1$ V

- (A) 4 V (B) 3 V
(C) 1 V (D) 1.9 V

10. $V_B = 2$ V

- (A) -7 V (B) 1.5 V
(C) 2.6 V (D) None of the above

Statement for Q.11-12:

The transistor in circuit shown in fig. P3.3.11-12 has $\beta = 200$. Determine the value of voltage V_o for given value of V_{BB} .

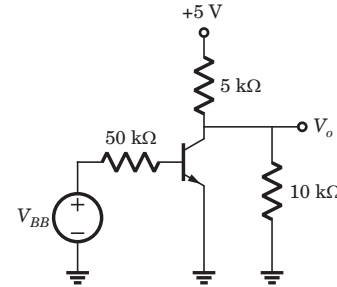


Fig. P3.3.11-12

11. $V_{BB} = 0$

- (A) 2.46 V (B) 1.83 V
(C) 3.33 V (D) 4.04 V

12. $V_{BB} = 1$ V

- (A) 4.11 V (B) 1.83 V
(C) 2.46 V (D) 3.44 V

13. $V_{BB} = 2$ V

- (A) 3.18 V (B) 1.46 V
(C) 0.2 V (D) None of the above

Statement for Q.14-16:

The transistor shown in the circuit of fig. P3.3.14-16 has $\beta = 150$. Determine V_o for given value of I_Q in question.

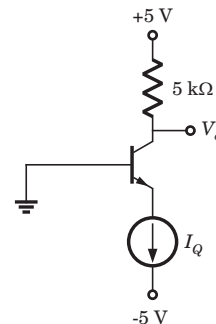


Fig. P3.3.14-16

14. $I_Q = 0.1$ mA

- (A) 1.4 V (B) 4.5 V
(C) 3.2 V (D) None of the above

15. $I_Q = 0.5 \text{ mA}$

- (A) 3.16 V (B) 2.52 V
(C) 2.14 V (D) 3.94V

16. $I_Q = 2 \text{ mA}$

- (A) 4.9 V (B) -4.9 V
(C) 0.5 V (D) -0.5 V

17. For the circuit in fig. P3.3.17 $V_B = V_C$ and $\beta = 50$. The value of V_B is

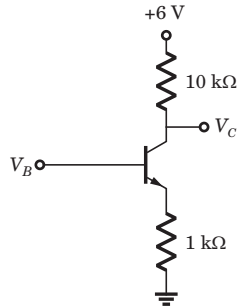


Fig. P3.3.17

- (A) 0.9 V (B) 1.19 V
(C) 2.14 V (D) 1.84 V

18. For the circuit shown in fig. P3.3.18, $V_{CB} = 0.5 \text{ V}$ and $\beta = 100$. The value of I_Q is

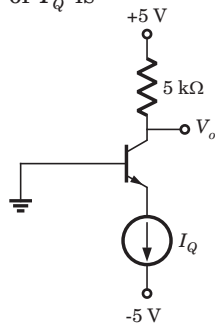


Fig. P3.3.18

- (A) 1.68 mA (B) 0.909 mA
(C) 0.134 mA (D) None of the above

19. For the circuit shown in fig. P3.3.19 the emitter voltage is $V_E = 2 \text{ V}$. The value of α is

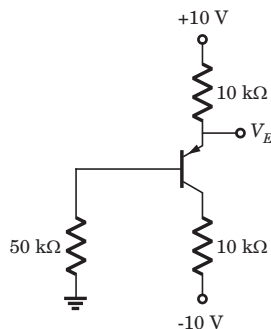


Fig. P3.3.19

- (A) 0.991 (B) 0.939
(C) 0.968 (D) 0.914

20. For the transistor in fig. P3.3.20, $\beta = 50$. The value of voltage V_{EC} is

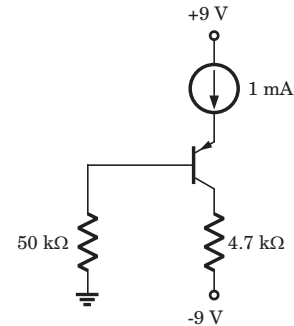


Fig. P3.3.20

- (A) 3.13 V (B) 4.24 V
(C) 5.18 V (D) 6.07 V

21. In the circuit shown in fig. P3.3.21 if $\beta = 50$, the power dissipated in the transistor is

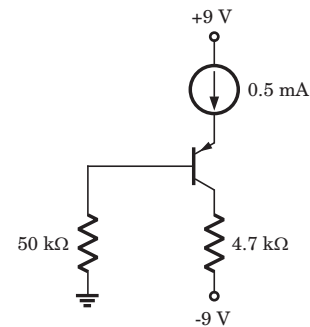


Fig. P3.3.21

- (A) 3.87 mW (B) 10.46 mW
(C) 7.49 mW (D) 18.74 mW

22. For the circuit shown in fig. P3.3.22 the Q-point is $V_{CEQ} = 12 \text{ V}$ and $I_{CQ} = 2 \text{ A}$ when $\beta = 60$. The value of resistor R_C and R_B are

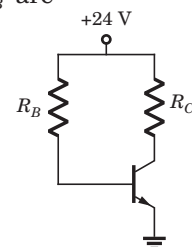


Fig. P3.3.22

- (A) 10 kΩ, 241 kΩ (B) 10 kΩ, 699 kΩ
(C) 6 kΩ, 699 kΩ (D) 6 kΩ, 241 kΩ

29. For the transistor in the circuit of fig. P3.3.29, $\beta = 100$. The voltage V_B is

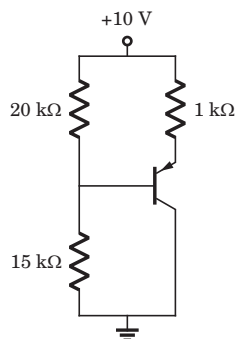


Fig. P3.3.29

- (A) 3.6 V (B) 4.29 V
(C) 3.9 V (D) 4.69 V

30. The current gain of the transistor shown in the circuit of fig. P3.3.30 is $\beta = 125$. The Q-point values (I_{CQ} , V_{CEQ}) are

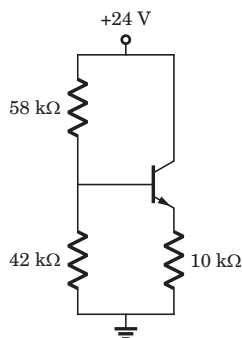


Fig. P3.3.30

- (A) (0.418 mA, 20.4 V) (B) (0.915 mA, 14.8 V)
(C) (0.915 mA, 16.23 V) (D) (0.418 mA, 18.43 V)

31. For the circuit shown in fig. P3.3.31, let $\beta = 75$. The Q-point (I_{CQ} , V_{CEQ}) is

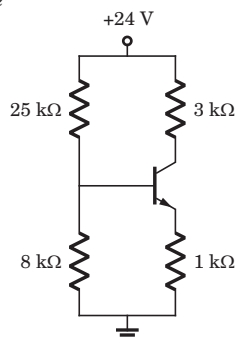


Fig. P3.3.31

- (A) (4.68 mA, 16.46 V) (B) (3.12 mA, 1.86 V)
(C) (3.12 mA, 8.46 V) (D) (4.68 mA, 5.22 V)

32. The current gain of the transistor shown in the circuit of fig. P3.3.32 is $\beta = 100$. The values of Q-point (I_{CQ} , V_{CEQ}) is

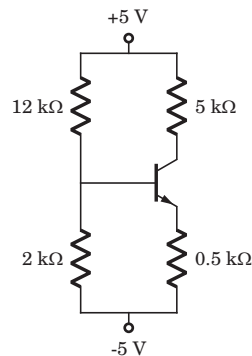


Fig. P3.3.32

- (A) (1.8 mA, 2.1 V) (B) (1.4 mA, 2.3 V)
(C) (1.4 mA, 1.8 V) (D) (1.8 mA, 1.4 V)

33. For the circuit in fig. P3.3.33, let $\beta = 60$. The value of V_{ECQ} is

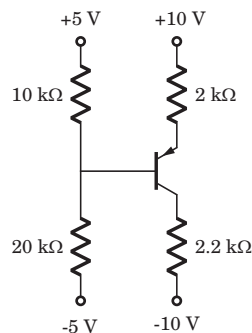


Fig. P3.3.33

- (A) 2.68 V (B) 4.94 V
(C) 3.73 V (D) 5.69 V

34. In the circuit of fig. P3.3.34 Zener voltage is $V_Z = 5$ V and $\beta = 100$. The value of I_{CQ} and V_{CEQ} are

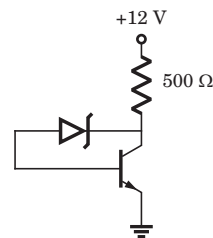


Fig. P3.3.34

- (A) 12.47 mA, 4.3 V (B) 12.47 mA, 5.7 V
(C) 10.43 A, 5.7 V (D) 10.43 A, 4.3 V

35. The two transistor in fig. P3.2.35 are identical. If $\beta = 25$, the current I_{C2} is

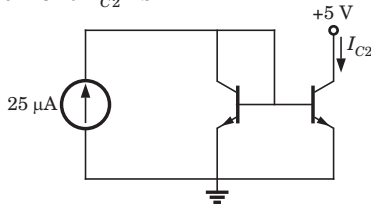


Fig. P3.2.35

- (A) 28 μA (B) 23.2 μA
(C) 26 μA (D) 24 μA

36. In the shunt regulator of fig. P3.2.26, the $V_Z = 8.2 \text{ V}$ and $V_{BE} = 0.7 \text{ V}$. The regulated output voltage V_o is

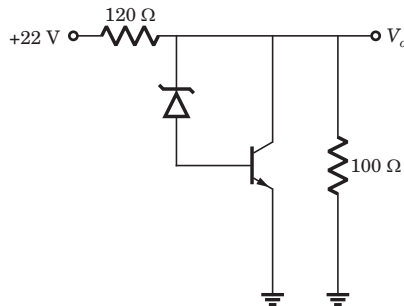


Fig. P3.2.36

- (A) 11.8 V (B) 7.5 V
(C) 12.5 V (D) 8.9 V

37. In the series voltage regulator circuit of fig. P3.2.37 $V_{BE} = 0.7 \text{ V}$, $\beta = 50$, $V_Z = 8.3 \text{ V}$. The output voltage V_o is

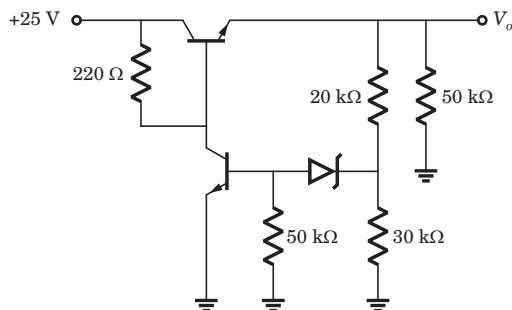


Fig. P3.2.37

- (A) 25 V (B) 25.7 V
(C) 15 V (D) 15.7 V

38. In the regulator circuit of fig. P3.2.38 $V_Z = 12 \text{ V}$, $\beta = 50$, $V_{BE} = 0.7 \text{ V}$. The Zener current is

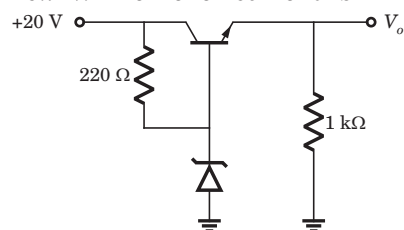


Fig. P3.2.38

- (A) 36.63 mA (B) 36.17 mA
(C) 49.32 mA (D) 49.78 mA

39. In the bipolar current source of fig. P3.2.39 the diode voltage and transistor BE voltage are equal. If base current is neglected then collector current is

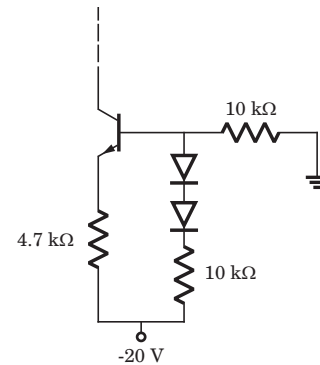


Fig. P3.2.39

- (A) 6.43 mA (B) 2.13 mA
(C) 1.48 mA (D) 9.19 mA

40. In the current mirror circuit of fig. P3.2.40, the transistor parameters are $V_{BE} = 0.7 \text{ V}$, $\beta = 50$ and the Early voltage is infinite. Assume transistor are matched. The output current I_o is

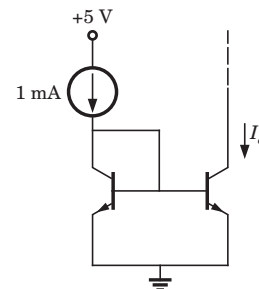


Fig. P3.2.40

- (A) 1.04 mA (B) 1.68 mA
(C) 962 μA (D) 432 μA

41. All transistor in the N output mirror in fig. P3.2.41 are matched with a finite gain β and early voltage $V_A = \infty$. The expression for each load current is

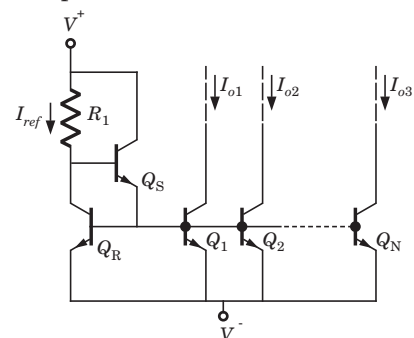


Fig. P3.2.41

$$(A) \frac{I_{ref}}{\left(1 + \frac{(1+N)}{\beta(\beta+1)}\right)} \quad (B) \frac{I_{ref}}{\left(1 + \frac{N}{(\beta+1)}\right)}$$

$$(C) \frac{\beta I_{ref}}{\left(1 + \frac{(1+N)}{(\beta+1)}\right)} \quad (D) \frac{\beta I_{ref}}{\left(1 + \frac{N}{\beta+1}\right)}$$

42. Consider the basic three transistor current source in fig. P3.2.42. Assume all transistor are matched with finite gain and early voltage $V_A = \infty$. The expression for I_o is

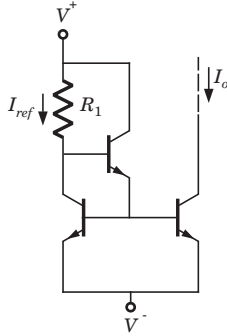


Fig. P3.2.42

$$(A) \frac{I_{ref}}{\left(1 + \frac{2}{(1+\beta)}\right)} \quad (B) \frac{I_{ref}}{\left(1 + \frac{1}{(2+\beta)}\right)}$$

$$(C) \frac{I_{ref}}{\left(1 + \frac{2}{\beta(1+\beta)}\right)} \quad (D) \frac{I_{ref}}{\left(1 + \frac{1}{\beta(2+\beta)}\right)}$$

43. Consider the wilder current source of fig. P3.2.43. Both of transistor are identical and $\beta \gg 1$ and $V_{BE1} = 0.7$ V. The value of resistance R_1 and R_E to produce $I_{ref} = 1$ mA and $I_o = 12 \mu A$ is ($V_t = 0.026$)

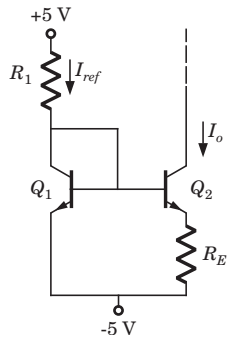


Fig. P3.2.43

$$(A) 9.3 \text{ k}\Omega, 18.23 \text{ k}\Omega \quad (B) 9.3 \text{ k}\Omega, 9.58 \text{ k}\Omega$$

$$(C) 15.4 \text{ k}\Omega, 16.2 \text{ k}\Omega \quad (D) 15.4 \text{ k}\Omega, 32.4 \text{ k}\Omega$$

SOLUTIONS

$$1. (C) I_E = \frac{12 - 0.7}{10k} \Rightarrow I_E = 1.13 \text{ mA}$$

$$I_C = \left(\frac{75}{75+1}\right)(1.13) = 1.12 \text{ mA}$$

$$V_{CE} = 12 - 1.13 \times 10 - 1.12 R_C - (-12) = 6 \text{ V}$$

$$R_C = 5.98 \text{ k}\Omega$$

$$2. (C) 8 = 10 \times (75 + 1)I_B + 0.7 + 10I_B - 2$$

$$I_B = \frac{9.3}{10 + 760} = 12.08 \mu A,$$

$$I_C = \beta I_B = 0.906 \text{ mA}, I_E = (\beta + 1)I_B = 0.918 \text{ mA}$$

$$8 = 10(0.918) + V_{EC} + 3(0.906) - 8$$

$$\Rightarrow V_{EC} = 4.1 \text{ V}$$

$$3. (A) I_C = \left(\frac{75}{75+1}\right)I_E = \frac{75}{76} (1m) = 0.987 \text{ mA}$$

$$R_C = \frac{5.2}{0.987m} = 3.04 \text{ k}\Omega$$

$$4. (A) 5 = (1 + \beta)10kI_B + 20kI_B + 0.7 + \beta 2kI_B$$

$$5 = (760k + 20k + 150k)I_B + 0.7$$

$$\Rightarrow I_B = 4.62 \mu A,$$

$$I_C = \beta I_B = 0.347 \text{ mA}$$

$$V_C = 5 - (\beta + 1)I_B R_C = 5 - 760 \times 4.62 \times 10^{-3} = 1.49 \text{ V}$$

$$5. (C) V_B = -I_B R_B$$

$$\Rightarrow I_B = \frac{-V_B}{R_B} = \frac{1}{500k} = 2.0 \mu A$$

$$V_E = -1 - 0.7 = -1.7 \text{ V}$$

$$I_E = \frac{V_E - (-3)}{4.8k} = \frac{-1.7 + 3}{4.8k} = 0.271 \text{ mA}$$

$$\frac{I_E}{I_B} = (\beta + 1) = \frac{0.271m}{2\mu}$$

$$\Rightarrow \beta = 134.5$$

$$6. (B) V_{CE} = 3 - V_E = 3 - (-1.7) = 4.7 \text{ V}$$

$$7. (C) I_E = \frac{5.4}{2k} = 0.5 \text{ mA}$$

$$4 = 0.7 + I_B R_B + I_C R_C - 5, I_C \approx I_E,$$

$$8.3 = 100I_B + 0.5 \times 8$$

$$\Rightarrow I_B = 43 \mu A,$$

$$\frac{I_E}{I_B} = 1 + \beta = \frac{0.5m}{43\mu} = 11.63$$

$$\beta = 10.63, \alpha = \frac{\beta}{1 + \beta} \rightarrow \alpha = 0.914$$

8. (C) $V_B = 0$ Transistor is in cut-off region.

$$I_E = 0, V_C = 6 \text{ V}$$

$$9. \text{ (B) } V_B = 1 \text{ V}, I_E = \frac{1 - 0.7}{1k} = 0.3 \text{ mA}$$

$$I_C \approx I_E = 0.3 \text{ mA}$$

$$V_C = 6 - I_C R_C = 6 - (0.3)(10) = 3 \text{ V}$$

$$10. \text{ (B) } V_B = 2 \text{ V}, I_E = \frac{2 - 0.7}{1} = 1.3 \text{ mA},$$

$$I_C \approx I_E = 1.3 \text{ mA}$$

$$V_C = 6 - (1.3)(10) = -7 \text{ V}$$

Transistor is in saturation. The saturation voltage

$$V_{CE} = 0.2 \text{ V}$$

$$V_E = (1.3)(1) = 1.3 \text{ V}, V_C = V_{CE} + V_E = 1.5 \text{ V}$$

11. (C) $V_{BB} = 0$, Transistor is in cutoff region

$$V_o = \frac{R_L}{R_C + R_L} V_{CC} = \frac{10(5)}{10} + 5 = 3.33 \text{ V}$$

$$12. \text{ (B) } I_B = \frac{1 - 0.7}{50k} = 6 \mu\text{A}$$

$$I_C = \beta I_B = 75 \times 6 \mu = 0.45 \text{ mA}$$

$$\frac{5 - V_o}{5k} = I_C + \frac{V_o}{10k}$$

$$(1 - 0.45) = \frac{V_o}{5} + \frac{V_o}{10}, \Rightarrow V_o = 1.83 \text{ V}$$

$$13. \text{ (C) } I_B = \frac{2 - 0.7}{50k} = 26 \mu\text{A}$$

$$I_C = \beta I_B = 75 \times 26 \mu\text{A} = 1.95 \text{ mA}$$

$$V_C = 5 - I_C R_C = 5 - 5 \times 1.95 = -4.75 \text{ V}$$

Transistor is in saturation, $V_{CE} = 0.2 \text{ V} = V_C = V_o$

$$14. \text{ (B) } I_E = 0.1 \text{ mA}$$

$$I_C = \frac{\beta}{(\beta + 1)} I_E = \frac{150}{151} (0.1) = 0.099 \text{ mA}$$

$$V_o = 5 - R_C I_C = 5 - 5(0.099) = 4.50 \text{ V}$$

$$15. \text{ (B) } I_E = I_Q = 0.5 \text{ mA}$$

$$I_C = \left(\frac{150}{150 + 1} \right) (0.5\text{mA}) = 0.497 \text{ mA}$$

$$V_o = 5 - R_C I_C = 2.517 \text{ V}$$

16. (D) Transistor is in saturation

$$V_o = V_{CE(sat)} - V_{BE} = 0.2 - 0.7 = -0.5 \text{ V}$$

$$17. \text{ (B) } I_E = \frac{V_B - 0.7}{1k}$$

$$I_C = \left(\frac{\beta}{\beta + 1} \right) I_E = \left(\frac{50}{51} \right) (V_B - 0.7) \text{ mA}$$

$$I_C = \frac{6 - V_C}{10} \text{ mA}, V_C = V_B$$

$$\frac{50}{51} (V_B - 0.7) = \frac{6 - V_B}{10}$$

$$10.8 V_B = 12.86, V_B = 1.19 \text{ V}$$

$$18. \text{ (B) } V_{CB} = 0.5 \text{ V}, V_C = 0.5 \text{ V}$$

$$I_C = \frac{5 - 0.5}{5k} = 0.9 \text{ mA}, I_Q = \left(\frac{101}{100} \right) 0.9 = 0.909 \text{ mA}$$

$$19. \text{ (C) } I_E = \frac{10 - V_E}{10k} = 0.8 \text{ mA}$$

$$V_B = V_E - 0.7 = 1.3 \text{ V}$$

$$I_B = \frac{V_B}{R_B} = \frac{1.3}{50k} = 26 \mu\text{A}$$

$$\beta + 1 = \frac{I_E}{I_B} = \frac{0.8\text{mA}}{26\mu} = 30.77 \Rightarrow \beta = 29.77$$

$$\alpha = \frac{\beta}{\beta + 1} = \frac{29.77}{30.77} = 0.968$$

$$20. \text{ (D) } I_C = \left(\frac{\beta}{\beta + 1} I_E \right) = \frac{50}{51} \text{ mA} = 0.98 \text{ mA}$$

$$V_C = I_C R_C - 9 = (0.98)(4.7) - 9 = -4.394 \text{ V}$$

$$I_B = \frac{I_E}{(\beta + 1)} = \frac{1}{51} \text{ mA} = 19.6 \mu\text{A}$$

$$V_E = I_B R_B + V_{EB} = 50(0.0196) + 0.7 = 1.68 \text{ V}$$

$$V_{EC} = 1.68 - (-4.394) = 6.074 \text{ V}$$

$$21. \text{ (A) } I_C = \left(\frac{\beta}{\beta + 1} \right) I_E = \frac{50}{51} (0.5) = 0.49 \text{ mA}$$

$$I_B = \frac{0.5}{51} = 9.8 \mu\text{A}$$

$$V_E = I_B R_B + V_{EB} = (0.0098)(50) + 0.7 = 1.19 \text{ V}$$

$$V_C = I_C R_C - 9 = (0.49)(4.7) - 9 = -6.7 \text{ V}$$

$$V_{EC} = 1.19 - (-6.7) = 7.89 \text{ V}$$

$$P_Q = I_C V_{EC} + I_B V_{EB}$$

$$= (0.49)(7.89) + (0.0098)(0.7) \text{ mW} = 3.87 \text{ mW}$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{15}{20 + 15} \right) (10) = 4.29 \text{ V}$$

$$10 = I_E(1\text{k}) + V_{EB} + \frac{I_E}{\beta + 1}(8.57\text{k}) + 4.29$$

$$10 = I_E + 0.7 + \frac{I_E}{101}(8.57\text{k}) + 4.29$$

$$\Rightarrow I_E = 4.62 \text{ mA}$$

$$I_B = \frac{I_E}{\beta + 1} = 0.046 \text{ mA}$$

$$V_B = (8.57)(0.046) + 4.29 = 4.69 \text{ V}$$

30. (B) $R_1 = 58 \text{ k}\Omega$, $R_2 = 42 \text{ k}\Omega$

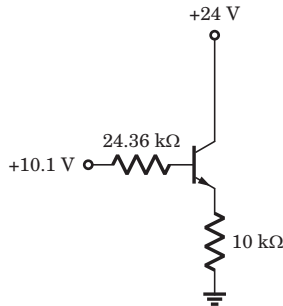


Fig. S3.3.30

$$R_{TH} = 58 \parallel 42 = 24.36 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{42}{42 + 58} \right) (24) = 10.1 \text{ V}$$

$$10.1 = I_{BQ}(24.36\text{k}) + V_{BE} + (\beta + 1)I_{BQ}(10\text{k})$$

$$10.1 - 0.7 = I_{BQ}(24.36\text{k} + 1260\text{k})$$

$$I_{BQ} = 7.32 \text{ }\mu\text{A}$$

$$I_{CQ} = \beta I_{BQ} = 0.915 \text{ mA}$$

$$I_{EQ} = (\beta + 1)I_{BQ} = 0.922 \text{ mA}$$

$$V_{CEQ} = 24 - (0.922)(10) = 14.8 \text{ V}$$

31. (D) $R_1 = 25 \text{ k}\Omega$, $R_2 = 8 \text{ k}\Omega$

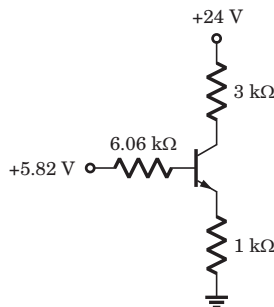


Fig. S3.3.31

$$R_{TH} = 25 \parallel 8 = 6.06 \text{ k}\Omega, V_{TH} = \left(\frac{8}{25 + 8} \right) (24) = 5.82 \text{ V}$$

$$5.82 = (6.06\text{k})(I_{BQ}) + V_{BE} + (\beta + 1)I_B(1\text{k})$$

$$5.82 - 0.7 = (6.06\text{k} + 76\text{k})I_{BQ}$$

$$\Rightarrow I_{BQ} = 62.4 \text{ }\mu\text{A}$$

$$I_{EQ} = (\beta + 1)I_{BQ} = 4.74 \text{ mA}$$

$$I_{CQ} = \beta I_{BQ} = 4.68 \text{ mA}$$

$$V_{CEQ} = 24 - I_{CQ}R_C - I_{EQ}R_E = 24 - (4.68)(3) - (4.74)(1) = 5.22 \text{ V}$$

32. (B) $R_1 = 12 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$

$$R_{TH} = R_1 \parallel R_2 = 12 \parallel 2 = 1.71 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{2}{12 + 2} \right) (10) - 5 = -3.57 \text{ V}$$

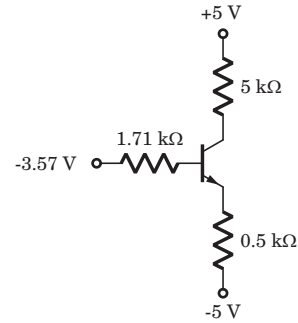


Fig. S3.3.32

$$-3.57 = I_{BQ}(1.71\text{k}) + V_{BE} + (\beta + 1)I_{BQ}(0.5\text{k}) - 5$$

$$5 - 3.57 - 0.7 = (1.71 + 50.5)I_{BQ}$$

$$\Rightarrow I_{BQ} = 14 \text{ }\mu\text{A}$$

$$I_{EQ} = (100 + 1)I_{BQ} = 1.412 \text{ mA}$$

$$I_{CQ} = 100I_{BQ} = 1.4 \text{ mA}$$

$$V_{CEQ} = 5 - R_C I_{CQ} - R_E I_{EQ} + 5 = 5 - (5)(1.4) - (0.5)(1.412) + 5 = 2.3 \text{ V}$$

33. (B) $R_{TH} = 20 \parallel 10 = 6.67 \text{ k}\Omega$

$$V_{TH} = \left(\frac{20}{10 + 20} \right) 10 - 5 = 1.67 \text{ V}$$

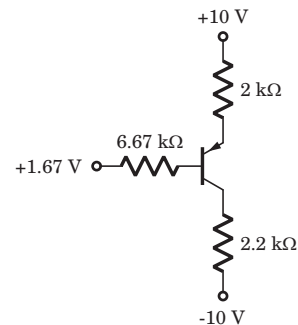


Fig. S3.3.33

$$10 = (1 + \beta)I_{BQ}(2) + V_{EB} + I_{BQ}(6.67) + 1.67$$

$$10 - 1.67 - 0.7 = I_{BQ}(6.67 + 122)$$

$$41. (A) I_{ref} = I_{CR} + I_{BS} = I_{CR} + \frac{I_{ES}}{1 + \beta}$$

$$I_{ES} = I_{BR} + I_{B1} + I_{B2} + \dots I_{BN}$$

$$I_{BR} = I_{Bi}, \quad I_{CR} = I_{Ci} = I_{oi}$$

$$I_{ES} = (1 + N)I_{BR} = \frac{(1 + N)I_{CR}}{\beta}$$

$$\text{Then } I_{ref} = I_{CR} + \frac{I_{ES}}{\beta + 1} = I_{CR} + \frac{(1 + N)I_{CR}}{\beta(\beta + 1)}$$

$$= I_{oi} \left(1 + \frac{(1 + N)}{\beta(\beta + 1)} \right)$$

$$I_{oi} = \frac{I_{ref}}{\left(1 + \frac{(1 + N)}{\beta(\beta + 1)} \right)}$$

$$42. (C) I_{ref} = I_{C1} + I_{B3}, \quad I_{B1} = I_{B2}, \quad I_{E3} = 2I_{B2}$$

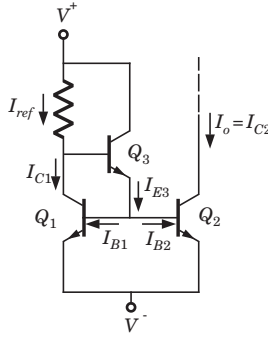


Fig. S3.2.42

$$I_{E3} = (1 + \beta)I_{B3}$$

$$I_{ref} = I_{C1} + \frac{I_{E3}}{(1 + \beta)} = I_{C1} + \frac{2I_{B2}}{(1 + \beta)}$$

$$I_{C1} = I_{C2} = \beta I_{B2}$$

$$I_{ref} = I_{C2} + \frac{2I_{C2}}{\beta(1 + \beta)} = I_{C2} \left(1 + \frac{2}{\beta(1 + \beta)} \right)$$

$$I_{C2} = I_o = \frac{I_{ref}}{\left(1 + \frac{2}{\beta(1 + \beta)} \right)}$$

$$43. (B) \text{ If } \beta \gg 1 \text{ and transistors are identical}$$

$$I_{ref} \approx I_{C1} = I_S e^{\frac{V_{BE1}}{V_t}}, \quad I_o = I_{C2} = I_S e^{\frac{V_{BE2}}{V_t}}$$

$$V_{BE1} = V_t \ln \left(\frac{I_{ref}}{I_S} \right), \quad V_{BE2} = V_t \ln \left(\frac{I_o}{I_S} \right)$$

$$V_{BE1} - V_{BE2} = V_t \ln \left(\frac{I_{ref}}{I_o} \right)$$

From the circuit,

$$V_{BE1} - V_{BE2} = I_{E2} R_E \approx I_o R_E$$

$$I_o R_E = V_t \ln \left(\frac{I_{ref}}{I_o} \right)$$

$$R_E = \frac{0.026}{12 \times 10^{-6}} \ln \left(\frac{1 \times 10^{-3}}{12 \times 10^{-6}} \right) = 9.58 \text{ k}\Omega$$

$$R_1 = \frac{V^+ - V_{BE1} - V^-}{I_{ref}} = \frac{5 - 7 - (-5)}{1\text{m}} = 9.3 \text{ k}\Omega$$
