


ANALOG AND DIGITAL ELECTRONICS TEST I

Number of Questions: 25

Section Marks: 25

Directions for questions 1 to 25: Select the correct alternative from the given choices.

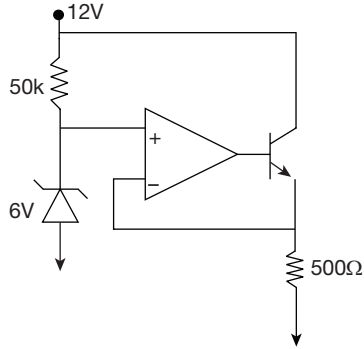1. In below circuit Op-Amp is ideal. If $\beta = 50$, the total current supplied by the 12V.



- (A) 12.12 mA (B) 11.88 mA
(C) 12 mA (D) 11.6 mA

2. Match List-I with List-II where List-I contains oscillator and List-II has characteristic

List-I	List-II
(p) clapp oscillator	(1) RC oscillator for audio frequency applications
(q) colpitts oscillator	(2) RF oscillator: Two inductances and one capacitance as the reactance network.
(r) Hartley oscillator	(3) LC oscillator for RF frequency: Three capacitances and one inductance in the reactance network.
(s) wein bridge oscillator	(4) RF oscillator: Two capacitance and one inductance as the reactance network.

- (A) $p-1, q-2, r-3, s-4$
(B) $p-4, q-3, r-2, s-1$
(C) $p-3, q-4, r-2, s-1$
(D) $p-3, q-2, r-1, s-4$


3. A power amplifier delivers 10W output at 50% of collector efficiency. If the maximum allowable junction temperature is 125°C , then maximum thermal resistance θ_{jc} that can be tolerated [$\therefore$ ambient temperature = 25°C]

- (A) 20°C/W (B) 5°C/W
(C) 10°C/W (D) 40°C/W

4. In class B push-pull operation the power delivered to the load $R_L = 10\Omega$ is $P_{ac} = 20\text{W}$. Then peak load current is


- (A) $\sqrt{2}\text{A}$ (B) 2A
(C) 1A (D) 0.5A

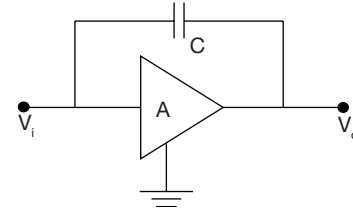5. An amplifier of gain A is bridge by a capacitance C as shown in below circuit, then the effective input capacitance is




- (A) C/A
(B) AC
(C) $C(1+A)$
(D) $C(1-A)$

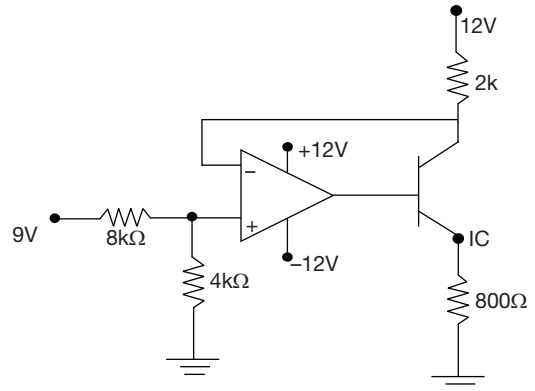6. In below circuit, find I_C if $\beta = 50$




- (A) 4.5 mA (B) 1.5 mA
(C) 4.41 mA (D) 3 mA

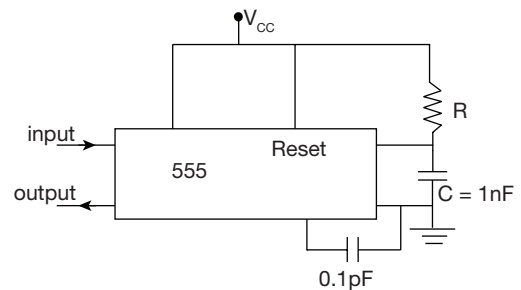7. Given circuit is to be used as a divided by 2 network. The frequency of the input trigger signal is 4 kHz. If the value of capacitor is 1 nF then value of R is




- (A) 39 kΩ (B) 120 kΩ
(C) 140 kΩ (D) 272 kΩ

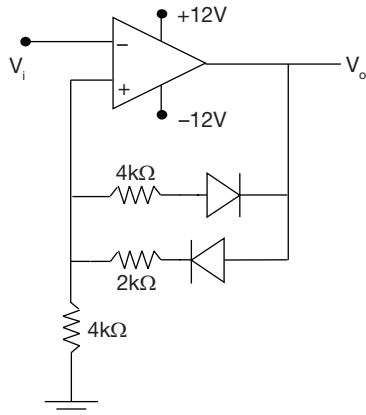8. Hysteresis loop width of below Schmitt trigger is [diodes and Op-Amps are ideal]




- (A) 2V (B) 8V
(C) -6V (D) 14V

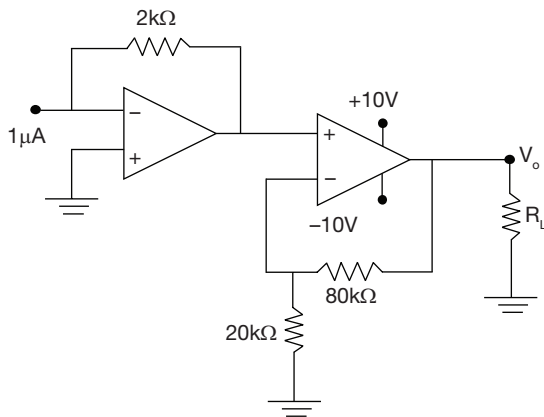9. The output voltage V_o of the below given figure



- (A) 0.1 mV (B) 1 mV
(C) 10 mV (D) 10V

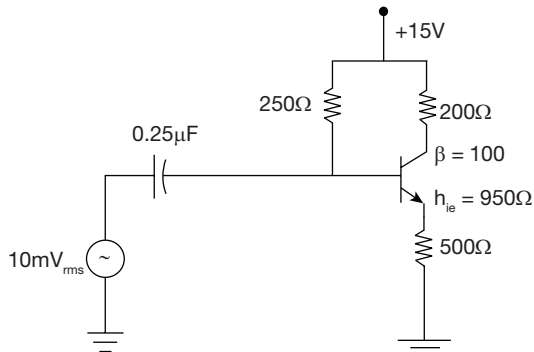10. Find the voltage gain of below circuit?




- (A) 28.17 (B) 217.4
(C) 505 (D) 150.3

11. An amplifier with open loop voltage gain $A_v = 800 \pm 50$ is available. It is required to have an amplifier whose gain varies by not more than $\pm 0.5\%$. Find reverse transmission factor β of the feedback network.

- (A) 1.43% (B) 2.5%
(C) 4% (D) 3.7%

12. Below network represents a

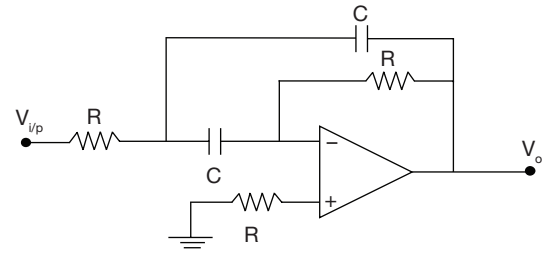


- (A) Low pass filter
(B) High pass filter
(C) Band pass filter
(D) Band stop filter

13. Match List-I with List-II where List-I contains type of feedback and List-II have input impedance ($Z_{i/p}$) and output impedance ($Z_{o/p}$)

List-I	List-II
(p) current series	(1) $Z_{i/p}$ increases and $Z_{o/p}$ decreases
(q) current shunt	(2) $Z_{i/p}$ increases and $Z_{o/p}$ increases
(r) voltage series	(3) $Z_{i/p}$ decreases and $Z_{o/p}$ decreases
(s) voltage shunt	(4) $Z_{i/p}$ decreases and $Z_{o/p}$ increases


- (A) p-2, q-4, r-1, s-3
(B) p-4, q-2, r-3, s-1
(C) p-3, q-1, r-2, s-4
(D) p-2, q-3, r-4, s-1

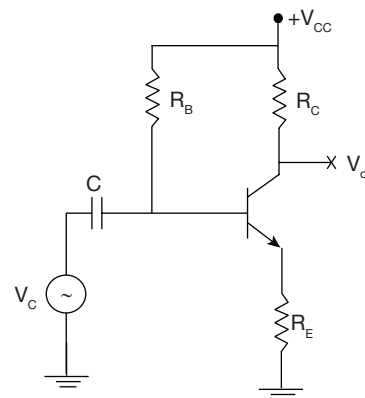14. Below circuit configuration indicates which type of feedback connection?




- (A) voltage series feedback
(B) voltage shunt feedback
(C) current series feedback
(D) current shunt feedback

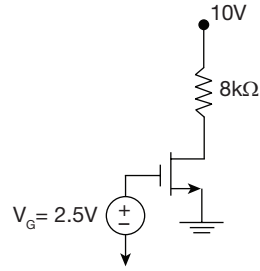15. For FET shown in below figure has $V_{TN} = 1.5V$, $k_n = 2 \text{ mA/V}^2$. The FET is in saturation and $I_D = 1\text{mA}$ then small signal voltage gain A_v is




- (A) -64 (B) -32
(C) 16 (D) 48

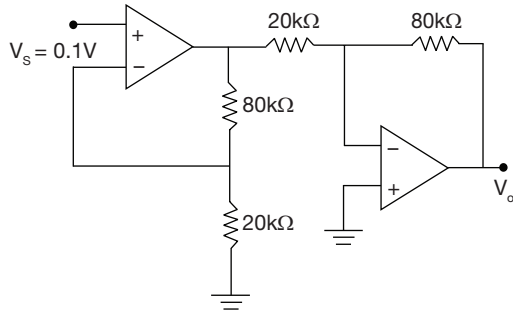16. Find out output voltage (V_o), assume that the op-Amps in below circuit are ideal




- (A) 2 V (B) 0.5 V
(C) -0.5 V (D) -2 V

17. Output voltage of below circuit is

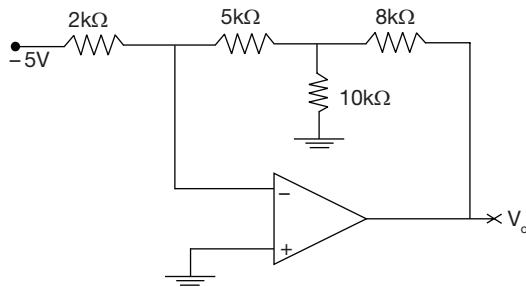


- (A) -40.5 V (B) 12.5 V
(C) 42.5 V (D) 35 V

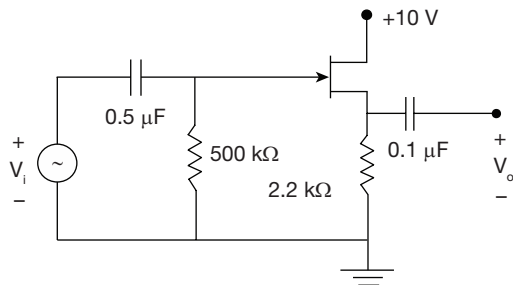18. A dc analysis of the source follower network has $V_{GSQ} = -2.5$ V and $I_{DQ} = 2.36$ mA. Then find voltage gain A_v ? [$I_{DSS} = 12$ mA, $V_p = -5$ V, $Y_{OS} = 74$ μ S]




- (A) 0.48 (B) 0.84
(C) 0.24 (D) 1.2

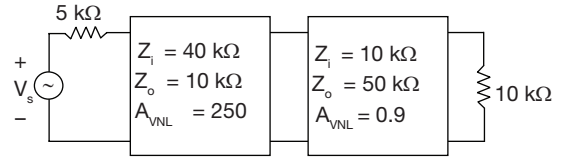19. Find total current gain for the system




- (A) -497.5 (B) 277.7
(C) -208 (D) 187

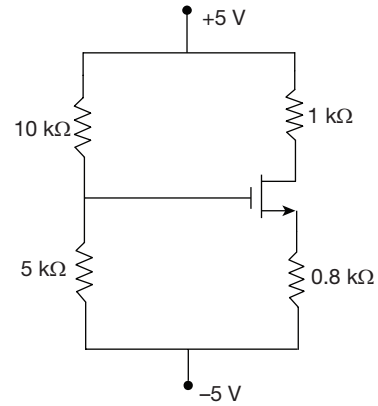
20. In below circuit the transistor parameters are $V_{Th} = -1.2$ V and $K_n = 0.8$ mA/V² then find drain current




- (A) 1.27 mA (B) 1.75 mA
(C) 1.55 mA (D) 1.97 mA

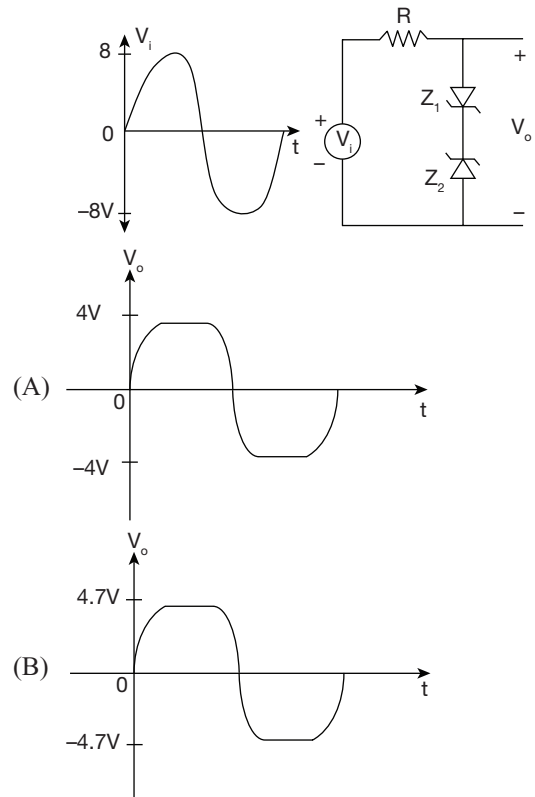21. In below shown circuit zener voltage $V_{Z1} = 4$ V and $V_{Z2} = 4$ V, $V_\gamma = 0.7$ V, then output voltage V_o is



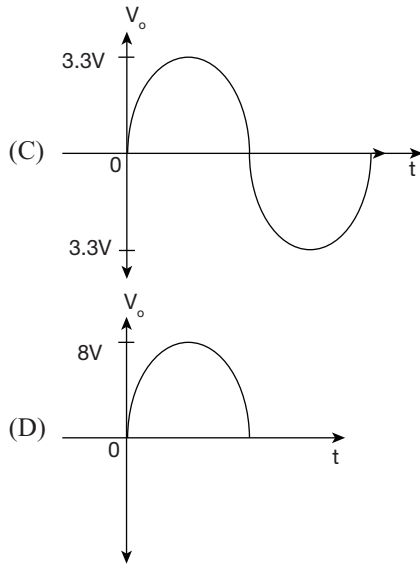


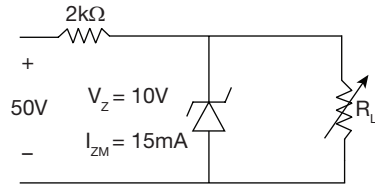22. Find the range of R_L in below circuit




- (A) $533\ \Omega < R_L < 1\ \text{k}\Omega$
 (B) $2\ \text{k}\Omega < R_L < 4\ \text{k}\Omega$
 (C) $800\ \Omega < R_L < 2\ \text{k}\Omega$
 (D) $500\ \Omega < R_L < 2\ \text{k}\Omega$

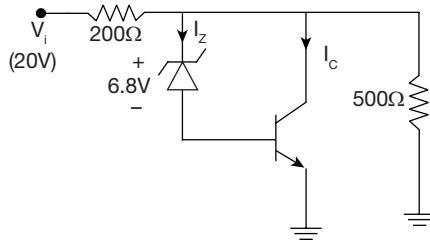23. Determine collector current for the below shown shunt regulator? Consider β is very high.




- (A) 3.75 mA (B) 62 mA
 (C) 58.25 mA (D) 25 mA

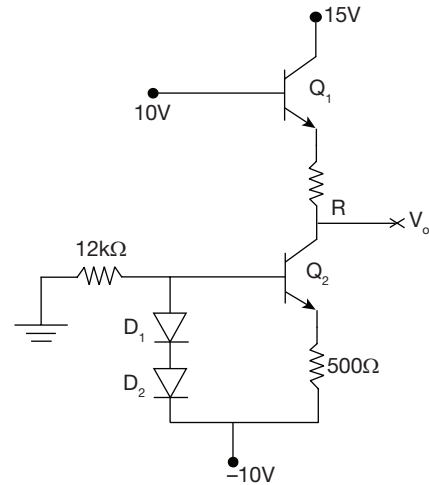24. Calculate the value of R for V_o to become 3V. [$V_{BE} = V_D = 0.7$ and β is large]



- (A) 2.25 kΩ (B) 4.5 kΩ
 (C) 6 kΩ (D) None of the above

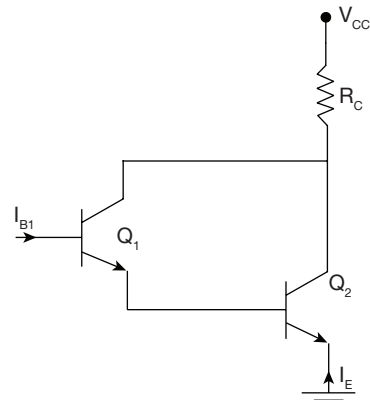25. For the circuit below shown, $\alpha_1 = 0.96, \alpha_2 = 0.98$, $V_{CC} = 15\text{V}$, $R_C = 250\ \Omega$ and $I_E = -120\text{mA}$, calculate I_B ?




- (A) $-86\ \mu\text{A}$ (B) 2.4 mA
 (C) $-2.4\ \text{mA}$ (D) $96\ \mu\text{A}$

ANSWER KEYS

- | | | | | | | | | | |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 1. B | 2. C | 3. C | 4. B | 5. D | 6. C | 7. D | 8. D | 9. C | 10. B |
| 11. A | 12. C | 13. A | 14. C | 15. B | 16. D | 17. C | 18. B | 19. A | 20. B |
| 21. B | 22. D | 23. C | 24. B | 25. D | | | | | |

HINTS AND EXPLANATIONS

1.

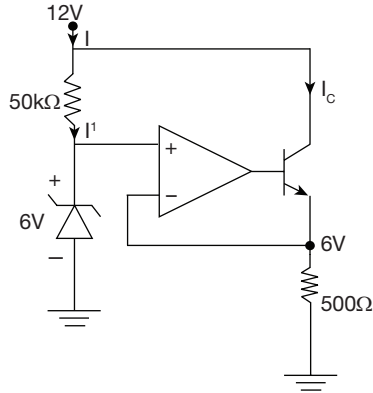

$$I = I^1 + I_C$$

$$I_E = \frac{6}{500} = 12 \text{ mA}$$

$$I_C = \alpha I_E = \frac{\beta}{1 + \beta} I_E = \frac{50}{51} \times 12 \times 10^{-3} = 11.76 \text{ mA}$$

$$I^1 = \frac{12 - 6}{50} \text{ mA} = \frac{6}{50} \text{ mA} = 0.12 \text{ mA}$$

$$I = I_C + I^1 = 11.88 \text{ mA}$$

Choice (B)

2. Choice (C)

 3. $P = 10 \text{ W}$, $\eta = 50\%$, $T_a = 25^\circ \text{C}$, $T_i = 125^\circ \text{C}$

$$\theta_{jc} P_D = T_j - T_a$$

$$\theta_{jc} = \frac{100}{10} = 10^\circ \text{ C/W}$$

Choice (C)

 4. $P_{ac} = I_{ac}^2 R_L \Rightarrow 20 = I_{ac}^2 (10)$

$$\Rightarrow I_{ac} = \sqrt{2}$$

$$\Rightarrow I_m = \sqrt{2} I_{ac} = 2$$

Choice (B)


5. Assuming voltage amplifier with zero input current

$$Q_i = C(V_i - AV_i)$$

$$\Rightarrow \frac{Q_i}{V_i} = C_{eq} = C(1 - A)$$

Choice (D)

6.

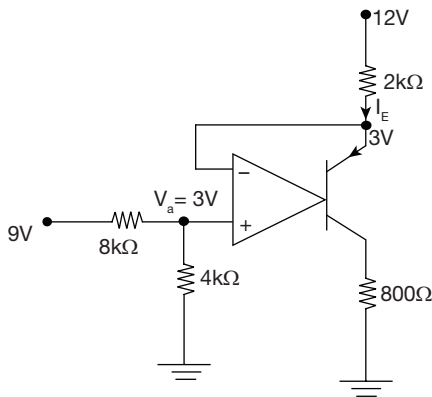

$$V_a = \frac{9 \times 4}{12} = 3 \text{ V}$$

$$I_E = \left(\frac{12 - 3}{2} \right) \text{ mA} = 4.5 \text{ mA}$$

$$I_C = \alpha I_E = \frac{\beta}{1 + \beta} I_E = \frac{50}{51} \times 4.5 = 4.41 \text{ mA} \quad \text{Choice (C)}$$


 7. $t_p = 1.2T$

$$= \frac{1.2}{4} \times 10^{-3} = 1.1 \text{ RC}$$

$$\frac{1.2 \times 10^{-3}}{4 \times 1.1 \times 10^{-9}} = R = 272 \text{ k}\Omega$$

Choice (D)

8.

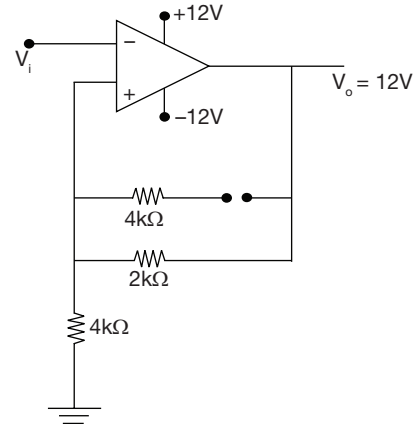
 If $V_o = +12 \text{ V}$ then

$$V_1 = \frac{12 \times 4}{6} = 8 \text{ V}$$


 If $V_o = -12 \text{ V}$ then

$$V_2 = \frac{-12 \times 4}{8} = -6 \text{ V}$$

$$V_H = V_1 - V_2 = 14 \text{ V}$$

Choice (D)

9.

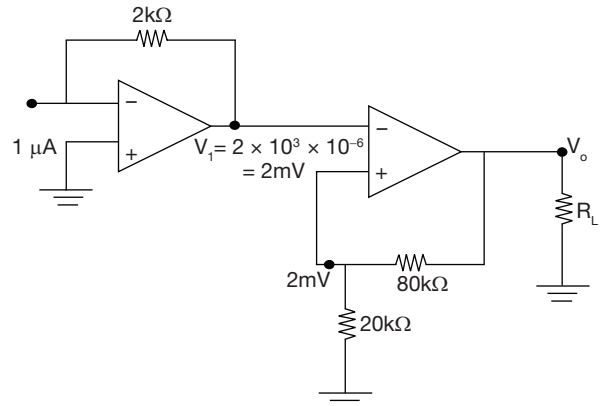

$$\frac{V_o \times 20}{100} = 2 \times 10^{-3}; V_o = 10 \text{ mV}$$

Choice (C)

$$10. A_v = \frac{R_e}{r_e}$$

$$r_e = \frac{V_T}{I_E}$$

$$I_E = \frac{15 - 0.7 \times 100}{250 + 101 \times 500} = 28.17 \text{ } \mu\text{A}$$

$$r_e = \frac{26}{28.17} = 0.92 \Omega$$

$$A_v = \frac{200}{0.92} = 217.4$$

Choice (B)

$$11. A_v = 800 \pm 50$$

$$\frac{\partial A_v}{\partial A} = \pm 0.5\%$$


$$\frac{\partial A_v}{A} = \frac{\partial A}{A} \left(\frac{1}{1 + \beta A} \right)$$

$$\Rightarrow \frac{0.5}{100} = \frac{50}{800} \left(\frac{1}{1 + \beta(800)} \right)$$


$$\Rightarrow \beta = 1.43\%$$

Choice (A)

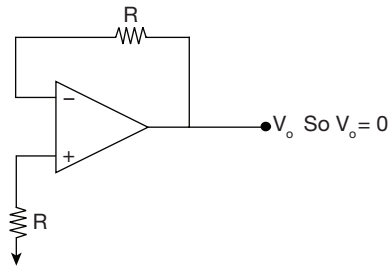12. If $f \rightarrow 0$, capacitor is open circuited then n/w looks like



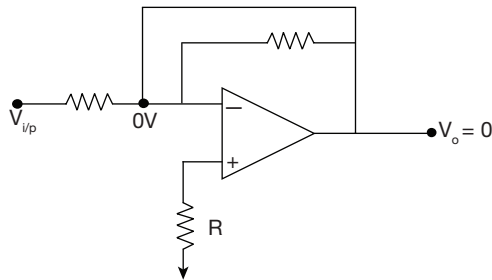If $f \rightarrow \infty$, capacitors will short circuited then n/w looks like



So it represents a band pass filter

Choice (C)

13. Choice (A)

14. The current through R_E results in a feedback voltage that opposes the source signal applied, so that V_o is reduced. It has current series feedback connection.

Choice (C)

$$15. A_v = -g_m R_D$$

$$\Rightarrow g_m = 2k(V_{GS} - V_{Th})$$


$$\Rightarrow V_{GS} = 2.5 \text{ V}$$

$$\Rightarrow g_m = 2 \times 2 \times 10^{-3} [2.5 - 1.5] = 4 \text{ mS}$$

$$A_v = -4 \times 10^{-3} \times 8 \times 10^3 = -32$$

Choice (B)

16.

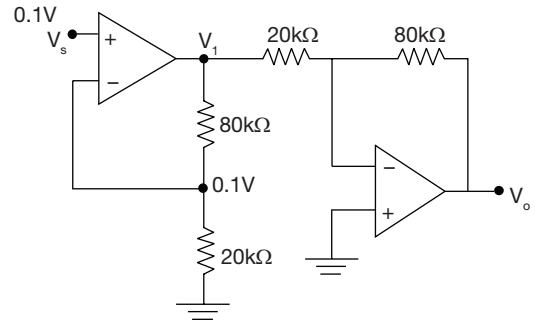


$$0.1 \text{ V} = \frac{V_1 \times 20}{80 + 20}$$

$$V_1 = 0.5 \text{ V}$$

$$\Rightarrow V_o = \frac{-R_F}{R_i} \times V_1 = -2 \text{ V}$$

Choice (D)

17.

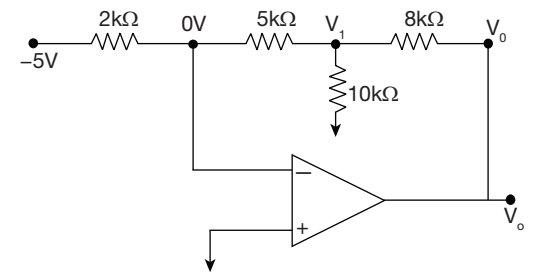

$$\text{KCL at Node } 0 \text{ V is } \frac{0 - (-5)}{2} + \frac{0 - V_1}{5} = 0$$

$$\frac{25}{2} = V_1$$

$$\Rightarrow \text{KCL at Node } V_1 \text{ is } \frac{V_1 - 0}{5} + \frac{V_1}{10} + \frac{V_1 - V_o}{8} = 0$$

$$\Rightarrow V_1 \left[\frac{1}{5} + \frac{1}{10} + \frac{1}{8} \right] = \frac{V_o}{8}$$

$$\Rightarrow V_o = 42.5 \text{ V}$$

Choice (C)

$$18. g_m = \frac{2I_{DSS}}{|V_P|} \left[1 - \frac{V_{GSQ}}{V_P} \right]$$

$$= \frac{2 \times 12}{5} \left[1 - \frac{(-2.5)}{(-5)} \right] = 2.4 \text{ mS}$$


$$A_v = \frac{g_m R_s}{1 + g_m R_s} = \frac{2.4 \times 10^{-3} \times 2.2 \times 10^3}{1 + 2.4 \times 10^{-3} \times 2.2 \times 10^3}$$

$$= \frac{5.28}{6.28} = 0.84$$

Choice (B)

$$19. A_{v1} = \frac{V_{o1}}{V_{i1}} = \frac{Z_{i2}}{Z_{i2} + Z_{o1}} A_{vNL1} = \frac{10 \times 10^3 \times 250}{(10 + 10) \times 10^3} = 125$$
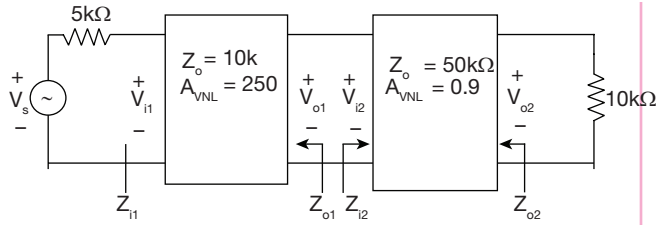
$$A_{v2} = \frac{R_L}{R_L + Z_{o2}} A_{vNL2} = \frac{10^4}{10^4 + 50} \times 0.9 = 0.99$$



$$A_{V_T} = A_{V_1} \cdot A_{V_2} = 124.37$$

$$A_{i_T} = -A_{V_T} \frac{Z_i}{R_L}$$

$$= 124.37 \times \frac{40}{10} = -497.5$$


Choice (A)

$$20. V_{th} = \frac{5 \times 5}{15} = \frac{5}{3} \text{ V}$$

$$5 + V_G = \frac{5}{3}$$

$$V_G = \frac{-10}{3} \text{ V}$$

$$V_{GS} = V_G - V_S$$

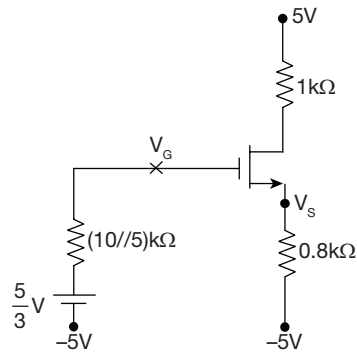

$$I_D = \frac{V_S + 5}{0.8 \text{ k}\Omega} = k_n [C_{GS(on)} - V_T]^2$$

$$\frac{(V_S + 5)}{0.8} = 0.8 \left[\frac{-10}{3} - V_S + 1.2 \right]^2$$

$$\Rightarrow V_S = -3.6$$


$$\Rightarrow I_D = \frac{(-3.6 + 5)10}{8} \text{ mA}$$

$$= 1.75 \text{ mA}$$

Choice (B)

 21. For $|V_i| \leq 4.7 \text{ V}$, $V_o = V_i$

Choice (B)

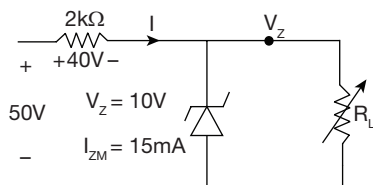 22. To determine the value of R_L that will turn on zener diode


$$V_Z = \frac{50 \times R_L}{R_L + 2K} = 10$$

$$R_{Lmin} = 500 \Omega$$

$$I = \frac{40}{2 \text{ k}\Omega} = 20 \text{ mA}$$


$$I_{Lmin} = I - I_{ZM} = 5 \text{ mA}$$

$$R_{Lmax} = \frac{V_Z}{I_{Lmin}} = \frac{10 \times 10^3}{5} = 2 \text{ k}\Omega$$

$$\Rightarrow R_L \text{ range is } 500 \Omega < R_L < 2 \text{ k}\Omega$$

Choice (D)

23.

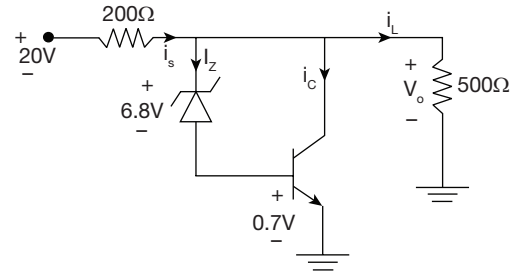

$$\Rightarrow V_o = 6.8 + 0.7 = 7.5 \text{ V}$$

$$i_L = \frac{7.5}{500} = 3.75 \text{ mA}$$


$$i_s = \frac{20 - 7.5}{200} = \frac{12.5}{200} = 62 \text{ mA}$$

 as I_Z is very small (β is very high)

$$i_c \approx i_s - i_L \approx 58.25 \text{ mA}$$

Choice (C)

24. Write KVL loop equation

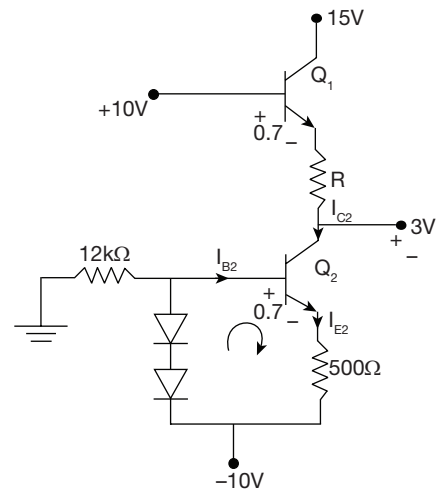

$$\Rightarrow 0.7 + 0.7 - 0.7 - I_{E2} 500 = 0$$

$$\Rightarrow I_{E2} = 1.4 \text{ mA}$$

$$\Rightarrow I_{C1} \approx I_{E2} = I_{C2} \text{ } [\beta \text{ is large}]$$


 $\Rightarrow$ write KVL equation

$$10 = 0.7 + I_{C2} R + 3$$

$$\Rightarrow R = \frac{10 - 3.7}{1.4} \text{ k}\Omega$$

$$= 4.5 \text{ k}\Omega$$

25.

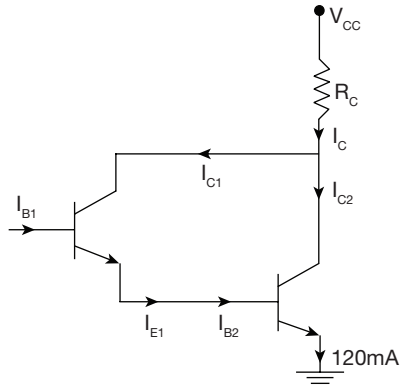

Choice (B)

$$\beta_1 = \frac{\alpha_1}{1 - \alpha_1} = 24$$

$$\beta_2 = \frac{\alpha_2}{1 - \alpha_2} = 49$$

$$I_{B_2} = \frac{I_E}{(1 + \beta_2)} = \frac{120 \text{ mA}}{50}$$

$$= 2.4 \text{ mA} = I_{E_1}$$

$$\Rightarrow I_{B_1} = \frac{I_{E_1}}{1 + \beta_1} = \frac{2.4 \text{ mA}}{25} = 96 \mu\text{A}$$

Choice (D)