



Power System Transients

Transient in Simple Circuits

The transients will depend upon the driving source, whether it is d.c. source or an a.c. source

DC Source



1. Resistance only

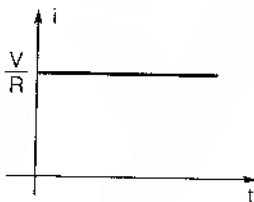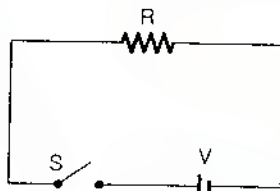

Transient current:

$$I = \frac{V}{R}$$



2. Inductance only

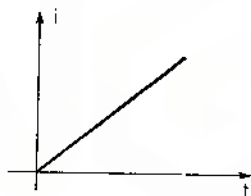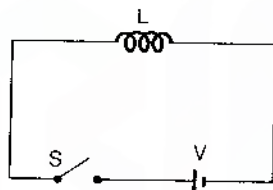

Transient current:

$$i(t) = \frac{V}{L} t$$

3. Capacitance only

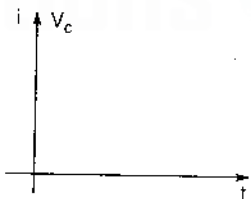
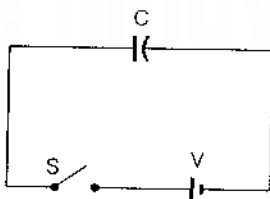


Transient current:

$$I(s) = \frac{V(s)}{Z(s)} = \frac{V}{s} \cdot sC = VC$$



which is an impulse of magnitude VC .

4. R-L circuit

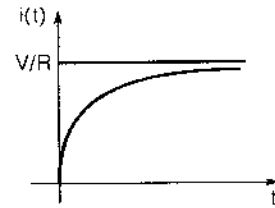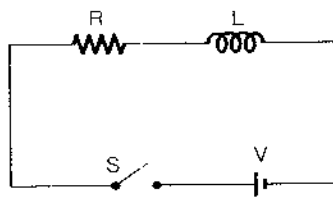


Transient current:
$$i(t) = \frac{V}{R} \left[1 - \exp\left(-\frac{R}{L}t\right) \right]$$

5. R-C circuit

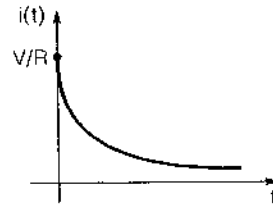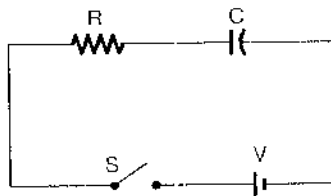


Transient current:
$$i(t) = \frac{V}{R} \exp\left(-\frac{t}{RC}\right)$$

6. R-L-C circuit

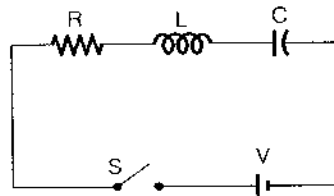

Transient current
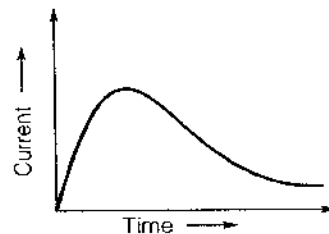
$$i(t) = \frac{V}{2bL} \left[e^{-(a-b)t} - e^{-(a+b)t} \right]$$



where, $a = \frac{R}{2L}$ and $b = \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}$

(a) Case-1

When b is real

then
$$\frac{R^2}{4L^2} > \frac{1}{LC}$$

and
$$i(t) = \frac{V}{2bL} \left[e^{-(a-b)t} - e^{-(a+b)t} \right]$$




(b) Case-2

When b = 0

$$i(t) = \frac{V}{2bL} (e^{-at} - e^{-at})$$

which is indeterminate form or $\left(\frac{0}{0}\right)$ form

$$i(t) = \frac{V}{L} t e^{-at}$$

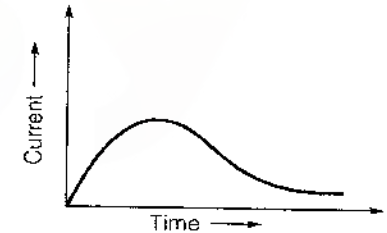


(c) Case-3

When b is imaginary

then
$$\frac{1}{LC} > \frac{R^2}{4L^2}$$

and
$$i(t) = \frac{V}{2bL} e^{-at} \cdot 2 \sin kt$$

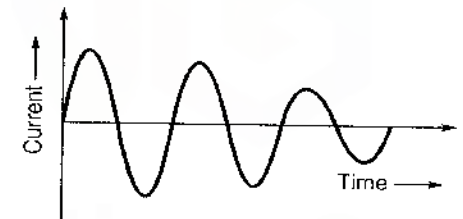where, $k = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$



■■■■