

CHAPTER

1.11

FREQUENCY RESPONSE

Statement for Q.1-3:

A parallel resonant circuit has a resistance of $2\text{ k}\Omega$ and half power frequencies of 86 kHz and 90 kHz .

1. The value of capacitor is

- (A) $6\text{ }\mu\text{F}$ (B) 20 nF
(C) 2 nF (D) $60\text{ }\mu\text{F}$

2. The value of inductor is

- (A) 4.3 mH (B) 43 mH
(C) 0.16 mH (D) 1.6 mH

3. The quality factor is

- (A) 22 (B) 100
(C) 48 (D) 200

Statement for Q.4-5:

A parallel resonant circuit has a midband admittance of $25 \times 10^{-3}\text{ S}$, quality factor of 80 and a resonant frequency of 200 krad/s .

4. The value of R is

- (A) $40\text{ }\Omega$ (B) $56.57\text{ }\Omega$
(C) $80\text{ }\Omega$ (D) $28.28\text{ }\Omega$

5. The value of C is

- (A) $2\text{ }\mu\text{F}$ (B) $28.1\text{ }\mu\text{F}$
(C) $10\text{ }\mu\text{F}$ (D) $14.14\text{ }\mu\text{F}$

6. A parallel RLC circuit has $R = 1\text{ k}\Omega$ and $C = 1\text{ }\mu\text{F}$. The quality factor at resonance is 200. The value of inductor is

- (A) $35.4\text{ }\mu\text{H}$ (B) $25\text{ }\mu\text{H}$
(C) $17.7\text{ }\mu\text{H}$ (D) $50\text{ }\mu\text{H}$

7. A parallel circuit has $R = 1\text{ k}\Omega$, $C = 50\text{ }\mu\text{F}$ and $L = 10\text{ mH}$. The quality factor at resonance is

- (A) 100 (B) 90.86
(C) 70.7 (D) None of the above

8. A series resonant circuit has an inductor $L = 10\text{ mH}$. The resonant frequency $\omega_0 = 10^6\text{ rad/s}$ and bandwidth is $BW = 10^3\text{ rad/s}$. The value of R and C will be

- (A) $100\text{ }\mu\text{F}$, $10\text{ }\Omega$ (B) 100 pF , $10\text{ }\Omega$
(C) 100 pF , $10\text{ M}\Omega$ (D) $100\text{ }\mu\text{F}$, $10\text{ M}\Omega$

9. A series resonant circuit has $L = 1\text{ mH}$ and $C = 10\text{ }\mu\text{F}$. The required R for the BW 15.9 Hz is

- (A) $0.1\text{ }\Omega$ (B) $0.2\text{ }\Omega$
(C) $15.9\text{ m}\Omega$ (D) $500\text{ }\Omega$

10. For the RLC parallel resonant circuit when $R = 8\text{ k}\Omega$, $L = 40\text{ mH}$ and $C = 0.25\text{ }\mu\text{F}$, the quality factor Q is

- (A) 40 (B) 20
(C) 30 (D) 10

11. The maximum voltage across capacitor would be

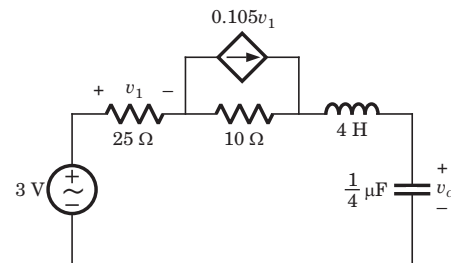


Fig. P1.11.11

- (A) 3200 V (B) 3 V
(C) -3 V (D) 1600 V

12. For the circuit shown in fig. P1.1.11 resonant frequency f_o is

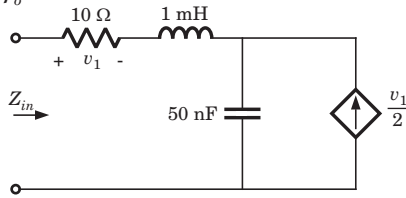


Fig. P1.1.12

- (A) 346 kHz (B) 55 kHz
(C) 196 kHz (D) 286 kHz

13. For the circuit shown in fig. P1.1.13 the resonant frequency f_o is

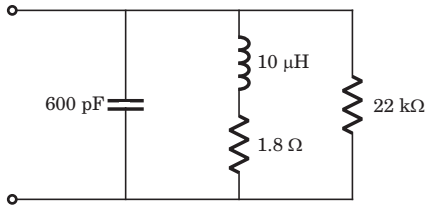


Fig. P1.1.13

- (A) 12.9 kHz (B) 12.9 MHz
(C) 2.05 MHz (D) 2.05 kHz

14. The network function of circuit shown in fig.P1.1.14 is

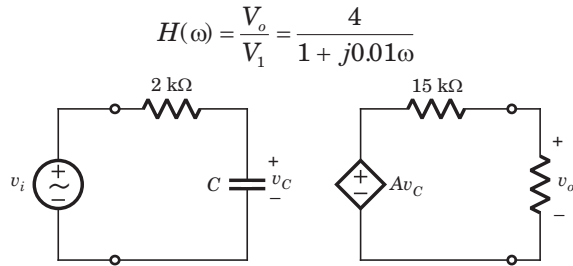


Fig. P1.1.14

The value of the C and A is

- (A) 10 μ F, 6 (B) 5 μ F, 10
(C) 5 μ F, 6 (D) 10 μ F, 10

15. $H(\omega) = \frac{V_o}{V_i} = ?$

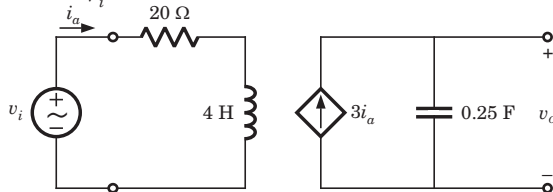


Fig. P1.1.15

- (A) $\frac{0.6}{j\omega(1 + j0.2\omega)}$ (B) $\frac{0.6}{j\omega(5 + j\omega)}$
(C) $\frac{3}{j\omega(1 + j\omega)}$ (D) $\frac{3}{j\omega(20 + j4\omega)}$

16. $H(\omega) = \frac{V_o}{V_i} = ?$

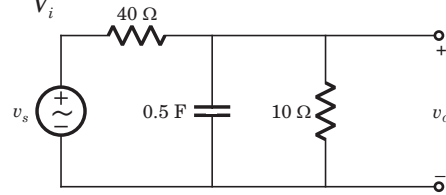


Fig. P1.1.16

- (A) $(5 + j20\omega)^{-1}$ (B) $(5 + j4\omega)^{-1}$
(C) $(5 + j30\omega)^{-1}$ (D) $5(1 + j6\omega)^{-1}$

17. The value of input frequency is required to cause a gain equal to 1.5. The value is

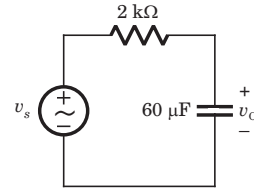


Fig. P1.1.17

- (A) 20 rad/s (B) 20 Hz
(C) 10 rad/s (D) No such value exists.

18. In the circuit of fig. P1.1.18 phase shift equal to -45° is required at frequency $\omega = 20$ rad/s. The value of R is

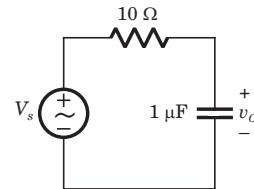


Fig. P1.1.18

- (A) 200 k Ω (B) 150 k Ω
(C) 100 k Ω (D) 50 k Ω

19. For the circuit of fig. P1.1.19 the input frequency is adjusted until the gain is equal to 0.6. The value of the frequency is

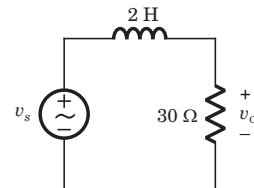


Fig. P1.1.19

- (A) 20 rad/s (B) 20 Hz
(C) 40 rad/s (D) 40 Hz

31. Bode diagram of the network function V_o/V_s for the circuit of fig. P1.11.30 is


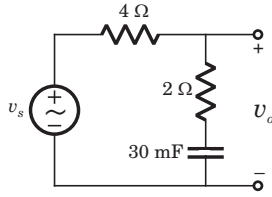


Fig.P1.11.30

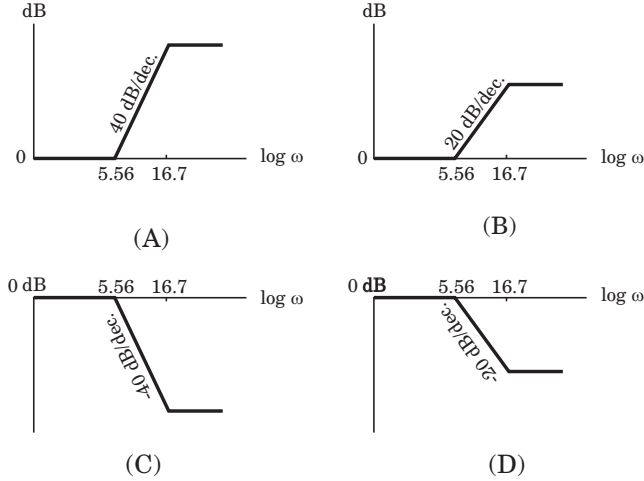

SOLUTIONS

1. (B) $BW = \omega_2 - \omega_1 = 2\pi(90 - 86)\text{k} = 8\pi \text{ krad/s}$

$$BW = \frac{1}{RC} \Rightarrow C = \frac{1}{RBW} = \frac{1}{8\pi \times 10^3 \times 2 \times 10^3} = 19.89 \text{ nF}$$

2. (C) $\omega_o = \frac{(\omega_1 + \omega_2)}{2} = \frac{2\pi(90 + 86)\text{k}}{2} = 176\pi \text{ krad/s}$

$$\omega_o = \frac{1}{\sqrt{LC}} \Rightarrow L = \frac{1}{\omega_o^2 C} = \frac{1}{(176\pi \times 10^3)^2 (20 \times 10^{-9})} = 0.16 \text{ mH}$$

3. (A) $Q = \frac{\omega_o}{B} = \frac{176\pi\text{k}}{8\pi\text{k}} = 22$

4. (A) At mid-band frequency $Z = R$, $Y = \frac{1}{R}$

$$R = \frac{1}{25 \times 10^{-3}} = 40 \Omega$$

5. (C) $Q = \omega_o RC$

$$\Rightarrow C = \frac{Q}{\omega_o R} = \frac{80}{200 \times 10^3 \times 40} = 10 \mu\text{F}$$

6. (B) $Q_o = R\sqrt{\frac{C}{L}} \Rightarrow 200 = 10^3 \sqrt{\frac{10^{-6}}{L}}$

$$\Rightarrow L = 25 \mu\text{H}$$

7. (C) $Q_o = R\sqrt{\frac{C}{L}} = 10^3 \sqrt{\frac{50 \times 10^{-6}}{10 \times 10^{-3}}} = 70.7$

8. (B) $\omega_o = \frac{1}{\sqrt{LC}}$

$$\Rightarrow C = \frac{1}{10 \times 10^{-3} \times (10^6)^2} = 100 \text{ pF}$$

$$BW = \frac{R}{L} \Rightarrow R = 10 \times 10^{-3} \times 10^3 = 10$$

9. (A) $BW = \frac{R}{L}$

$$\Rightarrow \frac{R}{1 \times 10^{-3}} = 15.9 \times 2\pi = 0.1 \Omega$$

10. (B) $Q = R\sqrt{\frac{C}{L}}$

$$= 8 \times 10^3 \sqrt{\frac{0.25 \times 10^{-6}}{40 \times 10^{-3}}} = 20$$

11. (A) Thevenin equivalent seen by L-C combination

$$3 = v_1 + 10 \left(\frac{v_1 - 0.105v_1}{125} \right) \Rightarrow v_1 = 100$$

$$I_{sc} = \frac{1100}{125} = 0.8 \text{ V}$$

Open Circuit : $v_1 = 0$, $v_{oc} = 3 \text{ V}$

$$R_{TH} = \frac{3}{0.8} = 3.75 \Omega, \omega_o = \frac{1}{\sqrt{LC}} = 1000$$

$$Q_o = \frac{\omega_o L}{R} = \frac{1000 \times 4}{3.75} = 1066.67$$

$$|v_C|_{\max} = Q_o v_{TH} = 1066.67 \times 3 = 3200 \text{ V}$$

12. (B) Applying 1 A at input port $V_1 = 10 \text{ V}$
voltage across 1 A source

$$V_{test} = 10 + j\omega 10^{-3} - \frac{j}{\omega 50 \times 10^{-9}} (5 + 1)$$

$$Z_{in} = V_{test}$$

At resonance $\text{Im}\{Z_{in}\} = 0$

$$\Rightarrow \omega_o 10^{-3} = \frac{6}{\omega_o 50 \times 10^{-9}} \Rightarrow \omega_o = 346 \text{ kHz}$$

$$f_o = 55 \text{ kHz}$$

$$13. (C) Y = j\omega 600 \times 10^{-12} + \frac{1}{2 \times 10^3} + \frac{1}{1.8 + j\omega 10^{-5}}$$

$$= j\omega 6 \times 10^{-10} + 45.45 + \frac{1.8 - j\omega 10^{-5}}{3.24 + \omega^2 10^{-50}}$$

At resonance $\text{Im}\{Y\} = 0$

$$\omega_o 6 \times 10^{-10} (3.24 + \omega_o^2 10^{-50}) - \omega_o 10^{-5} = 0$$

$$3.24 + \omega_o^2 10^{-50} = 16.67 \times 10^3 \omega_o = 12.9 \text{ Mrad/s}$$

$$f_o = \frac{\omega_o}{2\pi} = 2.05 \text{ MHz}$$

$$14. (C) V_C = \frac{\frac{V_i}{jC\omega}}{2 \times 10^3 + \frac{1}{jC\omega}} = \frac{V_i}{1 + j2 \times 10^3 C\omega}$$

$$V_o = AV_c \frac{(15k)}{16k + 30k} = \frac{2AV_c}{3} = \frac{2AV_i}{3(1 + j2 \times 10^3 C\omega)}$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{\frac{2A}{3}}{1 + j2\pi \times 10^3 C\omega}$$

$$\frac{2A}{3} = 4 \Rightarrow A = 6, \quad 2 \times 10^3 C = 0.01$$

$$\Rightarrow C = 5 \mu\text{F}$$

$$15. (A) I_a = \frac{V_i}{20 + j4\omega}, \quad V_o = \frac{3I_a}{0.25j\omega}$$

$$\frac{V_o}{V_i} = \frac{3}{j\omega(5 + j\omega)} = \frac{0.6}{j\omega(1 + j0.2\omega)}$$

$$16. (A) Z_1 = \frac{\frac{10}{j\omega(0.51)}}{\frac{1}{j\omega 0.5} + 10} = \frac{10}{1 + j3\omega}$$

$$\frac{V_o}{V_i} = \frac{Z_1}{40 + Z_1} = \frac{\frac{10}{1 + j5\omega}}{\frac{10}{1 + j5\omega} + 40}$$

$$= \frac{10}{50 + j200\omega} = (5 + j20\omega)^{-1}$$

$$17. (D) H(\omega) = \frac{V_o}{V_i} = \frac{1}{1 + j\omega RC}$$

$$\text{gain} = \frac{1}{\sqrt{1 + \omega^2 RC^2}}$$

For any value of ω , R , C gain ≤ 1 .

Thus (D) is correct option.

$$18. (D) H(\omega) = \frac{V_o}{V_s} = \frac{1}{1 + j\omega CR}$$

$$\text{phase shift} = -\tan^{-1} \omega CR = -45^\circ$$

$$\omega CR = 1,$$

$$20 \times 1 \times 10^{-6} R = 1 \Rightarrow R = 50 \text{ k}\Omega.$$

$$19. (A) H(\omega) = \frac{V_o}{V_s} = \frac{R}{\sqrt{1 + j\omega L}}$$

$$\text{gain} = \frac{R}{\sqrt{R^2 + \omega^2 L^2}} = \frac{30}{\sqrt{900^2 + 4\omega^2 + 0.6}}$$

$$\omega = \frac{\sqrt{50^2 - 30^2}}{2} = 20 \text{ rad/s}$$

$$20. (A) H(\omega) = \frac{V_o}{V_s} = \frac{1}{1 + j\omega CR} = \frac{1}{1 + j}$$

$$\text{Phase shift} = -\tan^{-1} \omega CR = -45^\circ$$

$$\text{gain} = \frac{1}{|1 + j|} = \frac{1}{\sqrt{2}} = 0.707$$

$$21. (B) BW = \omega_2 - \omega_1 = 2\pi(456 - 434) = 44\pi$$

$$\omega_o = 2\pi f_o = QBW = 20 \times 44\pi$$

$$f_o = 440 \text{ Hz}$$

$$22. (C) f_o = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{360 \times 10^{-12} \times 240 \times 10^{-6}}} = 541 \text{ kHz}$$

$$f_o = \frac{1}{2\pi\sqrt{50 \times 10^{-12} \times 240 \times 10^{-6}}} = 1.45 \text{ MHz}$$

$$23. (B) f_o = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$\frac{R}{L} = \frac{400}{240 \times 10^{-6}} = \frac{10^7}{6}$$

$$\frac{1}{LC} = \frac{1}{240 \times 10^{-6} \times 120 \times 10^{-12}} = \frac{10^{16}}{288}$$

$$\frac{R}{L} < \frac{1}{LC}, f_o = \frac{1}{2\pi\sqrt{LC}} = 938 \text{ kHz}$$

$$24. (B) \omega_o = \frac{1}{RC}, R \text{ and } C \text{ should be as small as possible.}$$

$$R = (3.3) \frac{(1.8)}{3.3+1.8} = 1.165 \text{ k}\Omega$$

$$C = (10) \frac{(30)}{(10+30)} = 7.5 \text{ pF}$$

$$\omega = \frac{1}{1.165 \times 7.5 \times 10^{-9}} = 114.5 \times 10^6 \text{ rad/s}$$

$$25. (D) R' = K_m R = 800 \times 12 \times 10^3 = 9.6 \text{ M}\Omega$$

$$L' = \frac{K_m}{K_f L} = \frac{800}{1000} 40 \times 10^{-6} = 32 \mu\text{F}$$

$$C' = \frac{C}{K_m} K_F = 30 \times \frac{10^{-9}}{80} \times 1000 = 0.375 \text{ pF}$$

$$26. (A) L'C' = \frac{LC}{K_f^2} \Rightarrow K_f^2 = \frac{4 \times 20 \times 10^{-3} \times 10^{-6}}{1 \times 6}$$

$$\Rightarrow K_f = 2 \times 10^{-4}$$

$$\frac{L'}{C'} = \frac{L}{C} K_m^2 \Rightarrow K_m^2 = \frac{(1)(20 \times 10^{-6})}{(2)(4 \times 10^{-3})}$$

$$\Rightarrow K_m = 0.05$$

$$27. (D) \omega_c = 2\pi f_c = \frac{1}{RC}$$

$$\Rightarrow R = \frac{1}{2\pi \times 20 \times 10^3 \times 0.5 \times 10^{-6}} = 15.9 \Omega$$

$$28. (A) R_{TH} \text{ across the capacitor is}$$

$$R_{TH} = (1\text{k} + 4\text{k}) || 5\text{k} = 2.5 \text{ k}\Omega$$

$$f_c = \frac{1}{2\pi \times 2.5 \times 10^3 \times 40 \times 10^{-9}} = 1.06 \text{ kHz}$$

$$29. (B) \omega_c = 2\pi f_c = \frac{1}{RC}$$

$$\Rightarrow R = \frac{1}{2\pi \times 15 \times 10 \times 10^{-6}} = 1.06 \text{ k}\Omega$$

$$30. (B) 20 \log H = 20 \log \frac{1}{\omega^2} = -40 \log \omega$$

$$31. (D) \frac{V_o}{V_s} = \frac{2 + \frac{1}{j\omega 30 \times 10^{-3}}}{6 + \frac{1}{j\omega 30 \times 10^{-3}}} = \frac{1 + \frac{j\omega}{16.67}}{1 + \frac{j\omega}{3.56}}$$

-20 dB/decade line starting from $\omega = 5.56 \text{ rad/s}$

20 dB/decade line starting from $\omega = 16.67 \text{ rad/s}$

Hence -20 dB/decade line for $5.56 < \omega < 16.67$

parallel to ω axis to $\omega > 16.67$
