

CHAPTER

3.5

OPERATIONAL AMPLIFIERS

1. $A_v = \frac{v_o}{v_i} = ?$

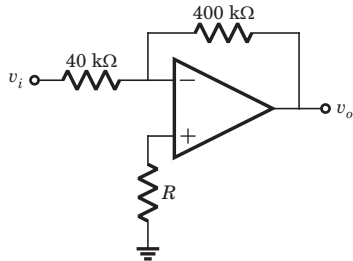


Fig. P3.5.1

- (A) -10
(B) 10
(C) -11
(D) 11

2. $A_v = \frac{v_o}{v_i} = ?$

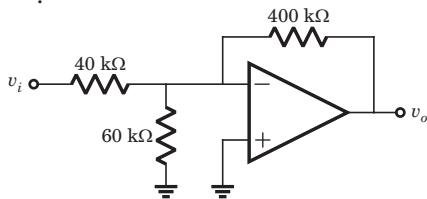


Fig. P3.5.2

- (A) -10
(B) 10
(C) 13.46
(D) -13.46

3. The input to the circuit in fig. P3.5.3 is $v_i = 2 \sin \omega t$ mV. The current i_o is

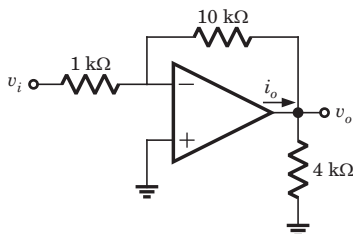


Fig. P3.5.3

- (A) $-2 \sin \omega t \mu A$
(B) $-7 \sin \omega t \mu A$
(C) $-5 \sin \omega t \mu A$
(D) 0

4. In circuit shown in fig. P3.5.4, the input voltage v_i is 0.2 V. The output voltage v_o is

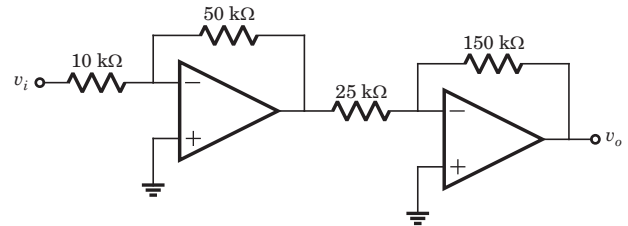


Fig. P3.5.4

- (A) 6 V
(B) -6 V
(C) 8 V
(D) -8 V

5. For the circuit shown in fig. P3.5.5 gain is $A_v = v_o/v_i = -10$. The value of R is

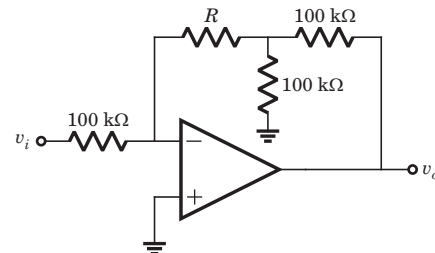


Fig. P3.5.5

- (A) 600 kΩ
(B) 450 kΩ
(C) 4.5 MΩ
(D) 6 MΩ

6. For the op-amp circuit shown in fig. P3.5.6 the voltage gain $A_v = v_o/v_i$ is

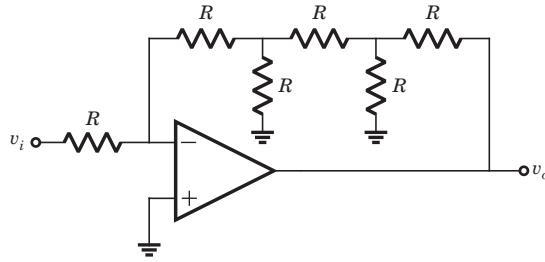


Fig. P3.5.6

- (A) -8
(B) 8
(C) -10
(D) 10

7. For the op-amp shown in fig. P3.5.7 open loop differential gain is $A_{od} = 10^3$. The output voltage v_o for $v_i = 2$ V is

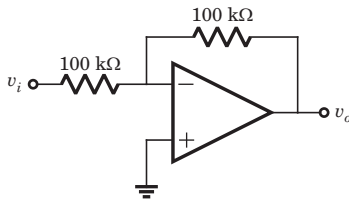


Fig. P3.5.7

- (A) -1.996
(B) -1.998
(C) -2.004
(D) -2.006

8. The op-amp of fig. P3.5.8 has a very poor open-loop voltage gain of 45 but is otherwise ideal. The closed-loop gain of amplifier is

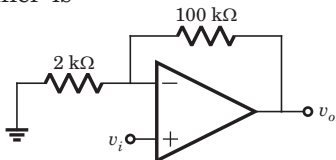


Fig. P3.5.8

- (A) 20
(B) 4.5
(C) 4
(D) 5

9. For the circuit shown in fig. P3.5.9 the input voltage v_i is 1.5 V. The current i_o is

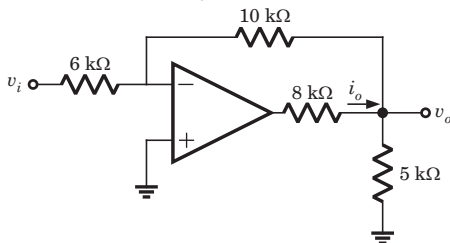


Fig. P3.5.9

- (A) -1.5 mA
(B) 1.5 mA
(C) -0.75 mA
(D) 0.75 mA

10. In the circuit of fig. P3.5.10 the output voltage v_o is

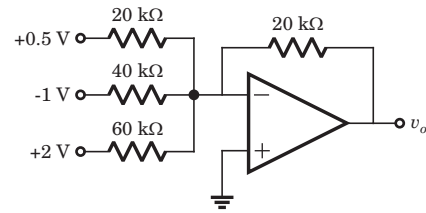


Fig. P3.5.10

- (A) 2.67 V
(B) -2.67 V
(C) -6.67 V
(D) 6.67 V

11. In the circuit of fig. P3.5.11 the voltage v_{i1} is $(1 + 2 \sin \omega t)$ mV and $v_{i2} = -10$ mV. The output voltage v_o is

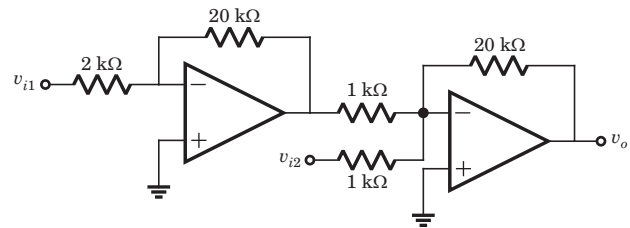


Fig. P3.5.11

- (A) $-0.4(1 + \sin \omega t)$ mV
(B) $0.4(1 + \sin \omega t)$ mV
(C) $0.4(1 + 2 \sin \omega t)$ mV
(D) $-0.4(1 + 2 \sin \omega t)$ mV

12. For the circuit in fig. P3.5.12 the output voltage is $v_o = 2.5$ V in response to input voltage $v_i = 5$ V. The finite open-loop differential gain of the op-amp is

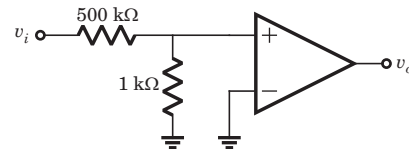


Fig. P3.5.12

- (A) 5×10^4
(B) 250.5
(C) 2×10^4
(D) 501

13. $v_o = ?$

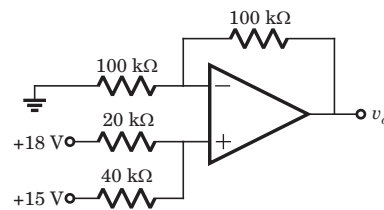


Fig. P3.5.13

- (A) 34 V
(B) -17 V
(C) 32 V
(D) -32 V

28. For the circuit shown in fig. P3.5.28 the input resistance is

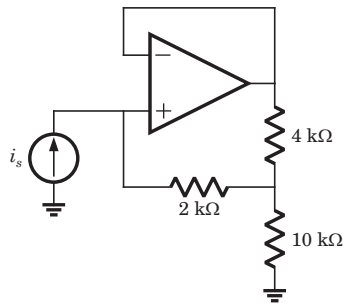


Fig. P3.5.28

- (A) 38 kΩ (B) 17 kΩ
(C) 25 kΩ (D) 47 kΩ

29. In the circuit of fig. P3.5.29 the op-amp slew rate is $SR = 0.5 \text{ V}/\mu\text{s}$. If the amplitude of input signal is 0.02 V, then the maximum frequency that may be used is

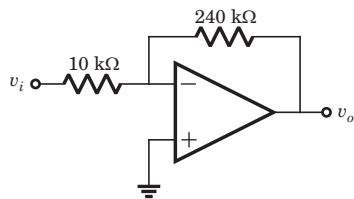


Fig. P3.5.29

- (A) $0.55 \times 10^6 \text{ rad/s}$ (B) 0.55 rad/s
(C) $1.1 \times 10^6 \text{ rad/s}$ (D) 1.1 rad/s

30. In the circuit of fig. P3.5.30 the input offset voltage and input offset current are $V_{io} = 4 \text{ mV}$ and $I_{io} = 150 \text{ nA}$. The total output offset voltage is

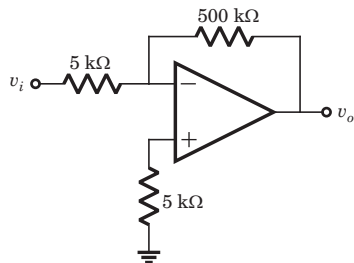


Fig. P3.5.30

- (A) 479 mV (B) 234 mV
(C) 168 mV (D) 116 mV

31. $i_o = ?$

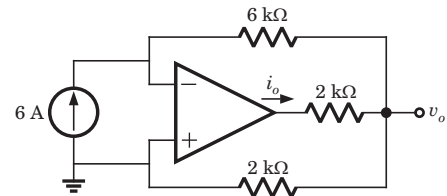


Fig. S3.5.31

- (A) -18 A (B) 18 A
(C) -36 A (D) 36 A

Statement for Q.32–33:

Consider the circuit shown below

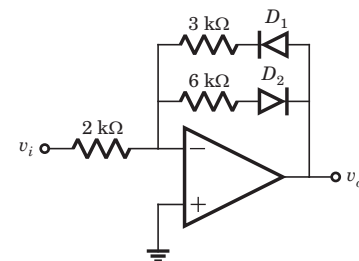


Fig. P3.5.32–33

- 32.** If $v_i = 2 \text{ V}$, then output v_o is
(A) 4 V (B) -4 V
(C) 3 V (D) -3 V

- 33.** If $v_i = -2 \text{ V}$, then output v_o is
(A) -6 V (B) 6 V
(C) -3 V (D) 3 V

34. $v_o(t) = ?$

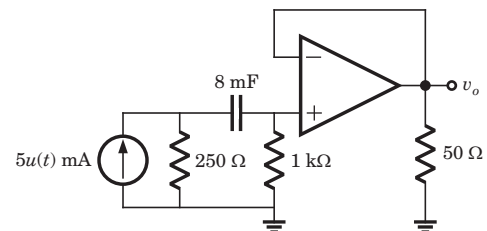


Fig. P3.5.34

- (A) $e^{-\frac{t}{10}} u(t) \text{ V}$ (B) $-e^{-\frac{t}{10}} u(t) \text{ V}$
(C) $e^{-\frac{t}{1.6}} u(t) \text{ V}$ (D) $-e^{-\frac{t}{1.6}} u(t) \text{ V}$

35. The circuit shown in fig. P3.5.35 is at steady state before the switch opens at $t=0$. The $v_C(t)$ for $t>0$ is

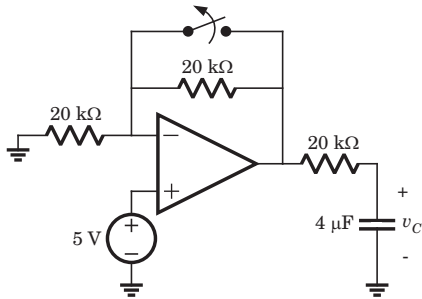


Fig. P3.5.35

- (A) $10 - 5e^{-12.5t}$ V (B) $5 + 5e^{-12.5t}$ V
(C) $5 + 5e^{-\frac{t}{12.5}}$ V (D) $10 - 5e^{-\frac{t}{12.5}}$ V

36. The LED in the circuit of fig. P3.5.36 will be on if v_i is

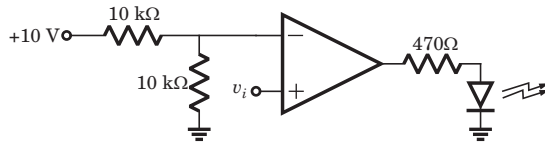


Fig. P3.5.36

- (A) > 10 V (B) < 10 V
(C) > 5 V (D) < 5 V

37. In the circuit of fig. P3.5.37 the CMRR of the op-amp is 60 dB. The magnitude of the v_o is

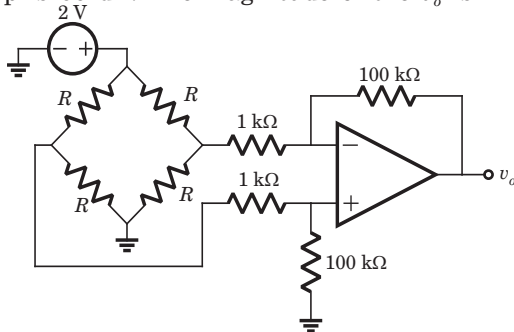


Fig. P3.5.37

- (A) 1 mV (B) 100 mV
(C) 200 mV (D) 2 mV

38. The analog multiplier X of fig. P3.5.38 has the characteristics $v_p = v_1 v_2$. The output of this circuit is

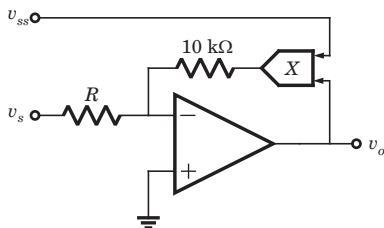


Fig. P3.5.38

- (A) $v_s v_{ss}$ (B) $-v_s v_{ss}$
(C) $-\frac{v_s}{v_{ss}}$ (D) $\frac{v_s}{v_{ss}}$

39. If the input to the ideal comparator shown in fig. P3.5.39 is a sinusoidal signal of 8 V (peak to peak) without any DC component, then the output of the comparator has a duty cycle of

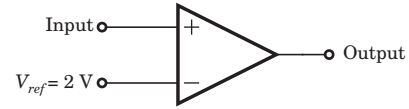


Fig. P3.5.39

- (A) $\frac{1}{2}$ (B) $\frac{1}{3}$
(C) $\frac{1}{6}$ (D) $\frac{1}{12}$

40. In the op-amp circuit given in fig. P3.5.40 the load current i_L is

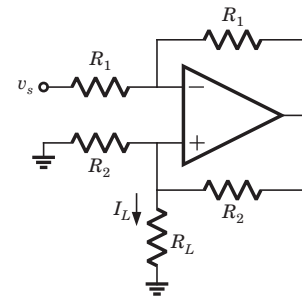


Fig. P3.5.40

- (A) $-\frac{v_s}{R_2}$ (B) $\frac{v_s}{R_2}$
(C) $-\frac{v_s}{R_L}$ (D) $\frac{v_s}{R_L}$

41. In the circuit of fig. P3.5.41 output voltage is $|v_o| = 1$ V for a certain set of ω , R , and C . The $|v_o|$ will be 2 V if

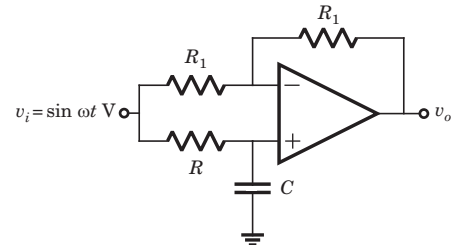


Fig. P3.5.41

- (A) ω is doubled (B) ω is halved
(C) R is doubled (D) None of the above

42. In the circuit of fig. P3.5.42. the 3 dB cutoff frequency is

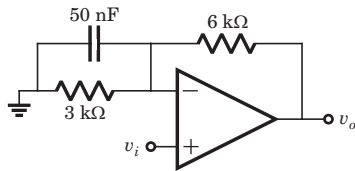


Fig. P3.5.42

- (A) 10 kHz (B) 1.59 kHz
(C) 354 Hz (D) 689 Hz

43. The phase shift oscillator of fig. P3.5.43 operate at $f = 80$ kHz. The value of resistance R_F is

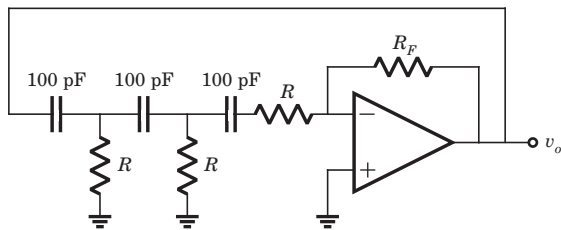


Fig. P3.5.43

- (A) 148 kΩ (B) 236 kΩ
(C) 438 kΩ (D) 814 kΩ

44. The value of C required for sinusoidal oscillation of frequency 1 kHz in the circuit of fig. P3.5.44 is

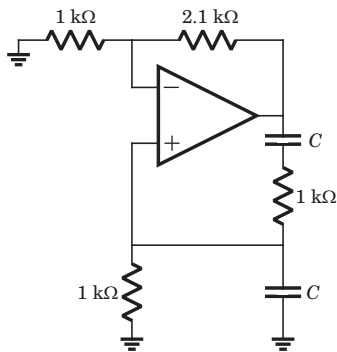


Fig. P3.5.44

- (A) $\frac{1}{2\pi}$ μF (B) 2π μF
(C) $\frac{1}{2\pi\sqrt{6}}$ μF (D) $2\pi\sqrt{6}$ μF

45. In the circuit shown in fig. P3.5.45 the op-amp is ideal. If $\beta_F = 60$, then the total current supplied by the 15 V source is

- (A) 123.1 mA (B) 98.3 mA
(C) 49.4 mA (D) 168 mA

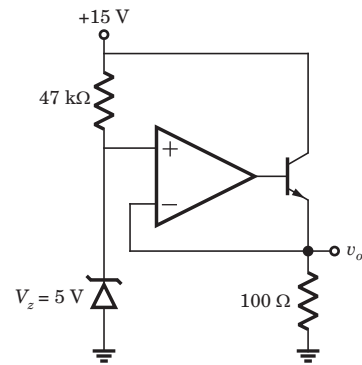


Fig. P3.5.45

46. In the circuit in fig. P3.5.46 both transistor Q_1 and Q_2 are identical. The output voltage at $T = 300$ K is

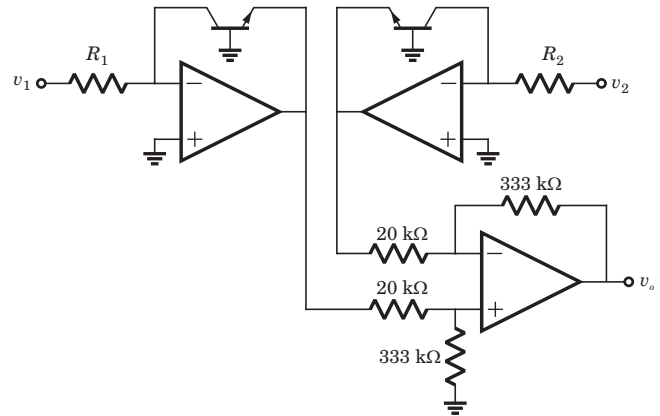


Fig. P3.5.46

- (A) $2 \log_{10} \left(\frac{v_2 R_1}{v_1 R_2} \right)$ (B) $\log_{10} \left(\frac{v_2 R_1}{v_1 R_2} \right)$
(C) $2.303 \log_{10} \left(\frac{v_2 R_1}{v_1 R_2} \right)$ (D) $4.605 \log_{10} \left(\frac{v_2 R_1}{v_1 R_2} \right)$

47. In the op-amp series regulator circuit of fig. P8.3.47 $V_z = 62$ V, $V_{BE} = 0.7$ V and $\beta = 60$. The output voltage v_o is

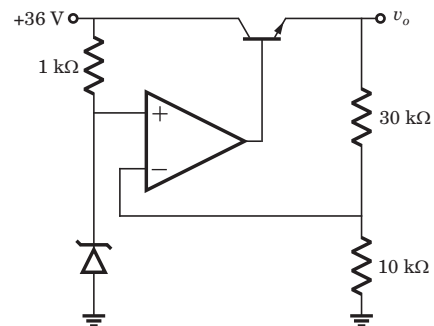


Fig. P3.5.47

- (A) 35.8 V (B) 24.8 V
(C) 29.8 V (D) None of the above

26. (C) $v_{2+} = v_{2-} = 0$ V, current through 6 V source

$$i = \frac{6}{3k} = 2 \text{ mA}, v_o = -2m(3k + 2k) = -10 \text{ V}$$

27. (D) $v_+ = \frac{v_o(1)}{1+3} = \frac{v_o}{4}, v_- = \frac{v_i(2)}{2+1} + \frac{v_o(1)}{2+1}$

$$v_+ = v_-, \frac{v_o}{4} = \frac{v_o}{3} + \frac{2v_i}{3}, \frac{v_o}{v_i} = -8$$

28. (B) Since op-amp is ideal

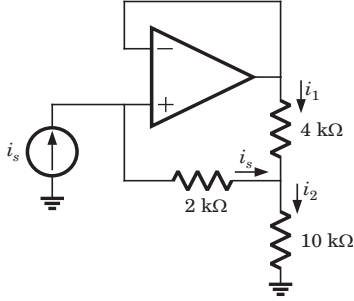


Fig. S3.5.28

$$v_- = v_+, 2ki_s = 4ki_1 \Rightarrow i_s = 2i_1$$

$$v_s = 2ki_s + 10ki_2$$

$$i_2 = i_s + i_1, v_s = 2ki_s + 10k(i_s + i_1), i_1 = \frac{i_s}{2}$$

$$v_s = 2ki_s + 10k\left(i_s + \frac{i_s}{2}\right) \Rightarrow \frac{v_s}{i_s} = 17k = R_{in}$$

29. (C) Closed loop gain $A = \left| \frac{R_F}{R_1} \right| = \frac{240k}{10k} = 24$

The maximum output voltage $v_{om} = 24 \times 0.02 = 0.48$ V

$$\omega \leq \frac{SR}{v_{om}} = \frac{0.5 / \mu}{0.48} = 1.1 \times 10^6 \text{ rad/s}$$

30. (A) The offset due to V_{io} is $v_o = \left(1 + \frac{R_1}{R_1}\right) V_{io}$

$$= \left(1 + \frac{500}{5}\right) 4m = 404 \text{ mV}$$

$$\text{Due to } I_{io}, v_o = R_F I_{io} = (500k)(150n) = 75 \text{ mV}$$

$$\text{Total offset voltage } v_o = 404 + 75 = 479 \text{ mV}$$

31. (A) $6 = \frac{-v_o}{6k}, i_o = -6 + \frac{v_o}{3k}$

$$i_o = -6 + \frac{-6(6k)}{3k} = -18 \text{ A.}$$

32. (B) If $v_i > 0$, then $v_o < 0$, D_1 blocks and D_2 conducts

$$A_v = -\frac{6k}{3k} = -2 \Rightarrow v_o = (-2)(2) = -4 \text{ V}$$

33. (D) If $v_i < 0$, then $v_o > 0$, D_2 blocks and D_1 conduct

$$A_v = -\frac{3k}{2k} = -1.5, v_o = (-2)(-1.5) = 3 \text{ V}$$

34. (A) Voltage follower $v_o = v_- = v_+$

$$v_+(0^+) = 5m(250 \parallel 1000) = 1 \text{ V}, v_+(\infty) = 0$$

$$\tau = 8m(1000 + 250) = 10 \text{ s}$$

35. (A) $v_c(0^-) = 5 \text{ V} = v_c(0^+) = 5 \text{ V}$

For $t > 0$ the equivalent circuit is shown in fig. S3.5.35

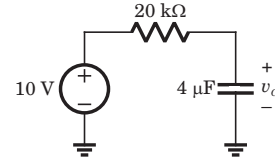


Fig. S3.5.35

$$\tau = 20k \times 4\mu = 0.08 \text{ s}$$

$$v_c = 10 + (5 - 10)e^{-\frac{t}{0.08}} = 10 - 5e^{-12.5t} \text{ V for } t > 0$$

36. (C) $v_- = \frac{(10)(10k)}{10k + 10k} = 5 \text{ V}$

When $v_+ > 5$ V, output will be positive and LED will be on. Hence (C) is correct.

37. (B) $v_+ = (2)\frac{R}{2R} = 1 \text{ V}, v_- = (2)\frac{R}{2R} = 1 \text{ V}, v_d = 0$

$$V_{CM} = \frac{v_+ + v_-}{2} = 1, v_o = \frac{R_F}{1} \frac{V_{CM}}{CMRR}$$

$$CMRR = 60 \text{ dB} = 10^3, v_o = \frac{100}{1} \frac{1}{10^3} = 100 \text{ mV}$$

38. (C) $v_+ = 0 = v_-$,

Let output of analog multiplier be v_p .

$$\frac{v_s}{R} = -\frac{v_p}{R} \Rightarrow v_s = -v_p, v_p = v_{ss}v_o$$

$$v_s = -v_{ss}v_o, v_o = -\frac{v_s}{v_{ss}}$$

39. (B) When $v_i > 2$ V, output is positive. When $v_i < 2$ V, output is negative.

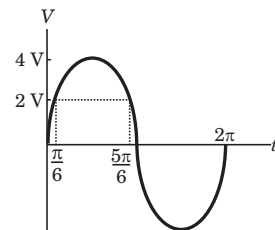


Fig. S3.5.39

$$\text{Duty cycle} = \frac{T_{ON}}{T} = \frac{\frac{5\pi}{6} - \frac{\pi}{6}}{2\pi} = \frac{1}{3}$$

$$40. (A) \quad \frac{v_s - v_-}{R_1} = \frac{v_- - v_o}{R_1} \Rightarrow 2v_1 = v_s + v_o$$

$$\frac{v_+}{R_2} + \frac{v_+}{R_L} + \frac{v_+ - v_o}{R_2} = 0 \Rightarrow v_o = \left(2 + \frac{R_2}{R_L}\right) v_+$$

$$2v_- = v_s + \left(2 + \frac{R_2}{R_L}\right) v_+, \quad v_- = v_+$$

$$\Rightarrow 0 = v_s + \frac{R_2}{R_L} v_+$$

$$v_+ = -\frac{R_L}{R_2} v_s, \quad i_L = \frac{v_+}{R_L}, \quad i_L = -\frac{v_s}{R_2}$$

41. (D) This is a all pass circuit

$$\frac{v_o}{v_i} = H(j\omega) = \frac{1 - j\omega RC}{1 + j\omega RC}, \quad |H(j\omega)| = \frac{\sqrt{1 + (\omega RC)^2}}{\sqrt{1 + (\omega RC)^2}} = 1$$

Thus when ω and R is changed, the transfer function is unchanged.

42. (B) Let $R_1 = 3 \text{ k}\Omega$, $R_2 = 6 \text{ k}\Omega$, $C = 50 \text{ nF}$

$$\frac{v_i}{R_1 \parallel \left(\frac{1}{sC}\right)} + \frac{v_i - v_o}{R_2} = 0 \Rightarrow \left(\frac{v_i}{\frac{R_1}{1 + sR_1C}}\right) + \frac{v_i}{R_2} = \frac{v_o}{R_2}$$

$$v_i \left[\frac{R_2}{R_1} (1 + sR_1C) + 1 \right] = v_o$$

$$\frac{v_i}{R_1} [R_2 + R_1 + sR_1R_2C] = v_o$$

$$\frac{v_o}{v_i} = \frac{R_2 + R_1}{R_1} \left[1 + \frac{sR_1R_2C}{R_1 + R_2} \right]$$

$$\Rightarrow \frac{v_o}{v_i} = \left(1 + \frac{R_2}{R_1}\right) (1 + s(R_1 \parallel R_2)C)$$

$$f_{3dB} = \frac{1}{2\pi(R_1 \parallel R_2)C}$$

$$= \frac{1}{2\pi(3\text{k} \parallel 6\text{k})50\text{n}} = \frac{1}{2\pi(2\text{k})50\text{n}} = 159 \text{ kHz}$$

43. (B) The oscillation frequency is

$$f = \frac{1}{2\pi\sqrt{6}RC} \Rightarrow 80\text{k} = \frac{1}{2\pi\sqrt{6}R(100\pi)}$$

$$\Rightarrow R = \frac{1}{(80\text{k})(2\pi\sqrt{6})(100\pi)} = 8.12 \text{ k}\Omega$$

$$\frac{R_F}{R} = 29 \Rightarrow R_F = (8.12\text{k})(29) = 236 \text{ k}\Omega$$

44. (A) This is Wien-bridge oscillator. The ratio $\frac{R_2}{R_1} = \frac{2.1\text{k}}{1\text{k}} = 2.1$ is greater than 2. So there will be oscillation

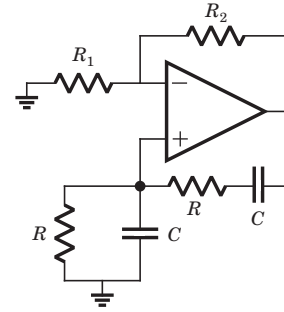


Fig. S3.5.44

$$\text{Frequency} = \frac{1}{2\pi RC} \Rightarrow 1 \times 10^3 = \frac{1}{2\pi(1\text{k})C}$$

$$C = \frac{1}{2\pi} \mu\text{F}$$

45. (C) $v_+ = 5 \text{ V} = v_- = v_E$,

The input current to the op-amp is zero.

$$\begin{aligned} i_{+15\text{V}} &= i_Z + i_C = i_Z + \alpha_F i_E \\ &= \frac{15 - 5}{47\text{k}} + \frac{60}{61} \left(\frac{5}{100} \right) = 49.4 \text{ mA} \end{aligned}$$

$$46. (B) \quad v_o = \frac{333}{20} (v_{o1} - v_{o2})$$

$$v_{o1} = -v_{BE1} - V_t \ln \left(\frac{i_{c1}}{i_s} \right), \quad v_{o2} = -v_{BE2} - V_t \ln \left(\frac{i_{c2}}{i_s} \right)$$

$$v_{o1} - v_{o2} = -V_t \ln \left(\frac{i_{c1}}{i_{c2}} \right) = V_t \ln \left(\frac{i_{c2}}{i_{c1}} \right)$$

$$i_{c1} = \frac{v_1}{R_1}, \quad i_{c2} = \frac{v_2}{R_2}$$

$$v_{o1} - v_{o2} = V_t \ln \left(\frac{v_2}{v_1} \frac{R_1}{R_2} \right), \quad V_t = 0.0259 \text{ V}$$

$$v_o = \frac{333}{20} (v_{o1} - v_{o2}) = \frac{333}{20} (0.0259) \ln \left(\frac{v_2}{v_1} \frac{R_1}{R_2} \right)$$

$$= 0.4329 \ln \left(\frac{v_2}{v_1} \frac{R_1}{R_2} \right) = 0.4329 (2.3026) \log_{10} \left(\frac{v_2}{v_1} \frac{R_1}{R_2} \right)$$

$$= \log_{10} \left(\frac{v_2}{v_1} \frac{R_1}{R_2} \right)$$

$$47. (B) \quad v_+ = v_-, \quad v_Z = \frac{10v_o}{10 + 30} = \frac{v_o}{4}$$

$$v_o = 4v_Z = 6.2 \times 4 = 24.8 \text{ V}$$
