

**GENERAL APTITUDE**

**Q. No. 1 – 5 Carry One Mark Each**

1. Choose the word most similar in meaning to the given word: Educe

- (A) Exert                      (B) Educate                      (C) Extract                      (D) Extend

**Answer: (C)**

2. If  $\log_x (5/7) = -1/3$ , then the value of x is

- (A) 343/125                      (B) 12/343                      (C) -25/49                      (D) -49/25

**Answer: (A)**

3. Operators  $\square$ ,  $\diamond$  and  $\rightarrow$  are defined by :  $a \square b = \frac{a-b}{a+b}$  ;  $a \diamond b = \frac{a+b}{a-b}$  ;  $a \rightarrow b = ab$ .

Find the value  $(66 \square 6) \rightarrow (66 \diamond 6)$ .

- (A) -2                      (B) -1                      (C) 1                      (D) 2

**Answer: (C)**

4. Choose the most appropriate word from the options given below to complete the following sentence.

The principal presented the chief guest with a \_\_\_\_\_, as token of appreciation.

- (A) momento                      (B) memento                      (C) momentum                      (D) moment

**Answer: (B)**

5. Choose the appropriate word/phrase, out of the four options given below, to complete the following sentence:

Frogs \_\_\_\_\_.


- (A) Croak                      (B) Roar                      (C) Hiss                      (D) Patter

**Answer: (A)**

6. A cube of side 3 units is formed using a set of smaller cubes of side 1 unit. Find the proportion of the number of faces of the smaller cubes visible to those which are NOT visible.
- (A) 1 : 4                      (B) 1 : 3                      (C) 1 : 2                      (D) 2 : 3

**Answer: (C)**

7. Fill in the missing value

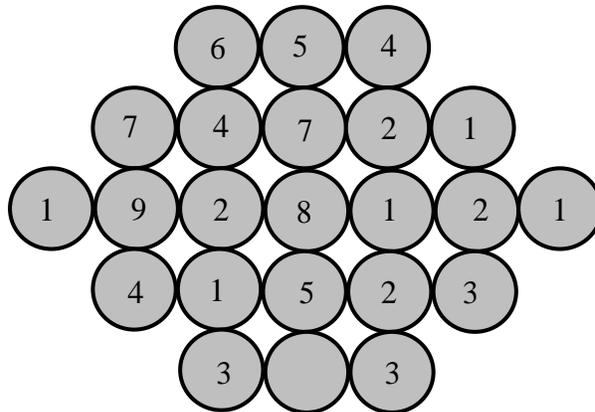

**Answer: (3)**

8. Humpty Dumpty sits on a wall every day while having lunch. The wall sometimes breaks. A person sitting on the wall falls if the wall breaks.

Which one of the statements below is logically valid and can be inferred from the above sentences?

- (A) Humpty Dumpty always falls having lunch  
 (B) Humpty Dumpty does not fall sometimes while having lunch  
 (C) Humpty Dumpty never falls during dinner  
 (D) When Humpty Dumpty does not sit on the wall, the wall does not break

**Answer: (B)**

9. The following question presents a sentence, part of which is underlined. Beneath the sentence you find four ways of phrasing the underlined part. Following the requirements of the standard written English, select the answer that produces the most effective sentence.

Tuberculosis, together with its effects, ranks one of the leading causes of death in India.

- (A) ranks as one of the leading causes of death
- (B) rank as one of the leading causes of death
- (C) has the rank of one of the leading causes of death
- (D) are one of the leading causes of death

**Answer: (A)**

**10.** Read the following paragraph and choose the correct statement.

Climate change has reduced human security and threatened human well being. An ignored reality of human progress is that human security largely depends upon environmental security. But on the contrary, human progress seems contradictory to environmental security. To keep up both at the required level is a challenge to be addressed by one and all. One of the ways to curb the climate change may be suitable scientific innovations, while the other may be the Gandhian perspective on small scale progress with focus on sustainability.

- (A) Human progress and security are positively associated with environmental security.
- (B) Human progress is contradictory to environmental security.
- (C) Human security is contradictory to environmental security.
- (D) Human progress depends upon environmental security.

**Answer: (D)**

## ELECTRONICS & COMMUNICATION ENGINEERING

### Q. No. 1 – 25 Carry One Mark Each

1. A region of negative differential resistance is observed in the current voltage characteristics of a silicon PN junction if
- (A) Both the P-region and the N-region are heavily doped
  - (B) The N-region is heavily doped compared to the P-region
  - (C) The P-region is heavily doped compared to the N-region
  - (D) An intrinsic silicon region is inserted between the P-region and the N-region

**Answer: (A)**

2. A silicon sample is uniformly doped with donor type impurities with a concentration of  $10^{16} / \text{cm}^3$ . The electron and hole mobilities in the sample are  $1200 \text{cm}^2 / \text{V-s}$  and  $400 \text{cm}^2 / \text{V-s}$  respectively. Assume complete ionization of impurities. The charge of an electron is  $1.6 \times 10^{-19} \text{C}$ . The resistivity of the sample (in  $\Omega\text{-cm}$ ) is \_\_\_\_\_.

**Answer: (0.52)**

3. A unity negative feedback system has the open-loop transfer function  $G(s) = \frac{k}{s(s+1)(s+3)}$ . The value of the gain  $k (>0)$  at which the root locus crosses the imaginary axis is \_\_\_\_\_.


**Answer: (12)**

4. Suppose A and B are two independent events with probabilities  $P(A) \neq 0$  and  $P(B) \neq 0$ . Let  $\bar{A}$  and  $\bar{B}$  be their complements. Which one of the following statements is FALSE?

- (A)  $P(A \cap B) = P(A)P(B)$
- (B)  $P(A \setminus B) = P(A)$
- (C)  $P(A \cup B) = P(A) + P(B)$
- (D)  $P(\bar{A} \cap \bar{B}) = P(\bar{A})P(\bar{B})$

**Answer: (C)**

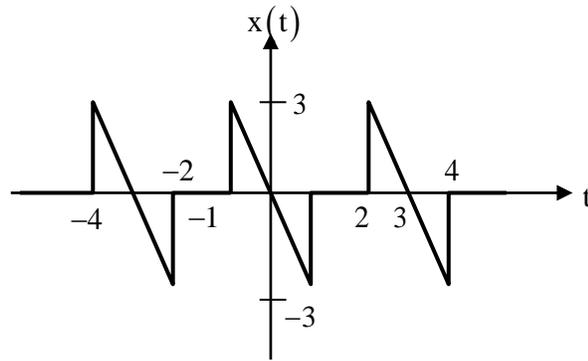
5. The waveform of a periodic signal  $x(t)$  is shown in the figure.



A signal  $g(t)$  is defined by  $g(t) = x\left(\frac{t-1}{2}\right)$ . The average power of  $g(t)$  is \_\_\_\_\_.

**Answer: (2)**

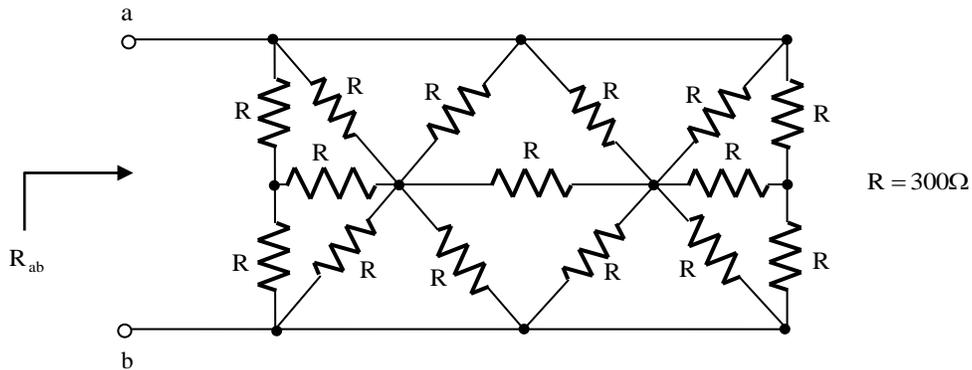6. In the network shown in the figure, all resistors are identical with  $R = 300\Omega$ .



The resistance  $R_{ab}$  (in  $\Omega$ ) of the network is \_\_\_\_\_.

**Answer: (100)**

7. Consider a system of linear equations:

$$x - 2y + 3z = -1$$

$$x - 3y + 4z = 1 \text{ and}$$





$$-2x + 4y - 6z = k.$$

The value of  $k$  for which the system has infinitely many solutions is \_\_\_\_\_.

**Answer: (2)**



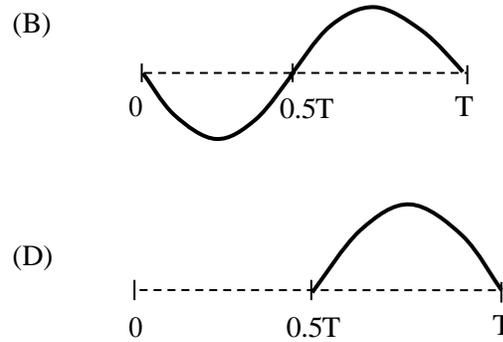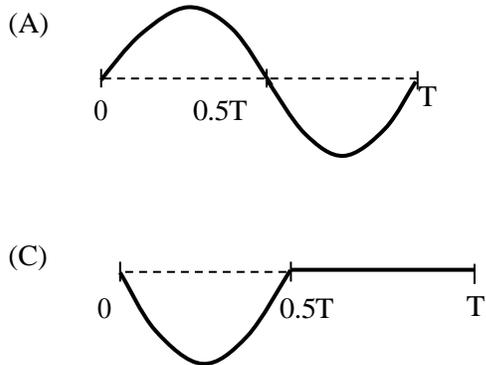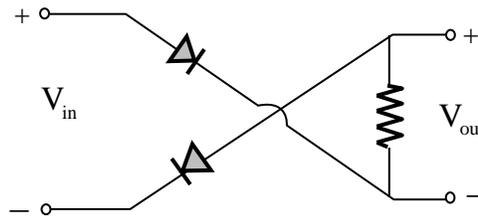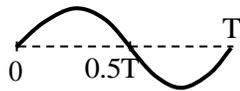11. For the circuit with ideal diodes shown in the figure, the shape of the output ( $V_{out}$ ) for the given sine wave input ( $V_{in}$ ) will be



Answer: (C)

12. The result of the convolution  $x(-t) * \delta(-t - t_0)$  is


- (A)  $x(t + t_0)$       (B)  $x(t - t_0)$       (C)  $x(-t + t_0)$       (D)  $x(-t - t_0)$

Answer: (D)

13. The value of  $p$  such that the vector  $\begin{bmatrix} 1 \\ 2 \\ 3 \end{bmatrix}$  is an eigenvector of the matrix  $\begin{bmatrix} 4 & 1 & 2 \\ p & 2 & 1 \\ 14 & -4 & 10 \end{bmatrix}$  is \_\_\_\_\_.

Answer: (17)

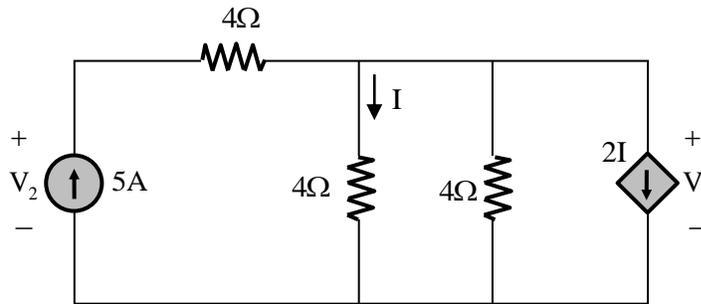14. In the given circuit, the values of  $V_1$  and  $V_2$  respectively are



- (A) 5V, 25V      (B) 10V, 30V      (C) 15V, 35V      (D) 0V, 20V

Answer: (A)

15. In an 8085 microprocessor, the shift registers which store the result of an addition and the overflow bit are, respectively

- (A) B and F      (B) A and F      (C) H and F      (D) A and C

Answer: (B)

16. Negative feedback in a closed-loop control system DOES NOT

- (A) reduce the overall gain  
 (B) reduce bandwidth  
 (C) improve disturbance rejection  
 (D) reduce sensitivity to parameter variation

Answer: (B)

17. A 16 Kb (=16,384 bit) memory array is designed as a square with an aspect ratio of one (number of rows is equal to the number of columns). The minimum number of address lines needed for the row decoder is

\_\_\_\_\_.

Answer: (7)

18. A function  $f(x) = 1 - x^2 + x^3$  is defined in the closed interval  $[-1, 1]$ . The value of  $x$ , in the open interval  $(-1, 1)$  for which the mean value theorem is satisfied, is

- (A)  $-\frac{1}{2}$                       (B)  $-\frac{1}{3}$                       (C)  $\frac{1}{3}$                       (D)  $\frac{1}{2}$


Answer: (B)

19. The electric field component of a plane wave traveling in a lossless dielectric medium is given by

$\vec{E}(z, t) = \hat{a}_y 2 \cos\left(10^8 t - \frac{z}{\sqrt{2}}\right)$  V/m. The wavelength (in m) for the wave is \_\_\_\_\_.

Answer: (8.885)

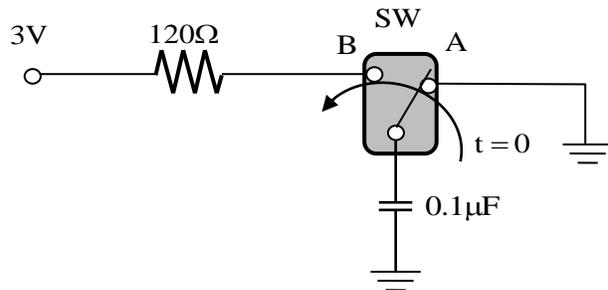
20. In the circuit shown, the switch SW is thrown from position A to position B at time  $t = 0$ . The energy (in  $\mu\text{J}$ ) taken from the 3V source to charge the  $0.1\mu\text{F}$  capacitor from 0V to 3V is



- (A) 0.3                      (B) 0.45                      (C) 0.9                      (D) 3

Answer: (C)

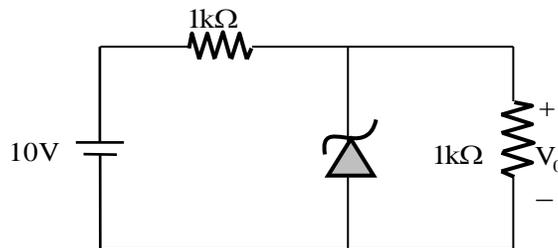21. In the circuit shown below, the Zener diode is ideal and the Zener voltage is 6V. The output voltage  $V_0$  (in volts) is \_\_\_\_\_.




Answer: (5)

22. Consider a four bit D to A converter. The analog value corresponding to digital signals of values 0000 and 0001 are 0V and 0.0625V respectively. The analog value (in Volts) corresponding to the digital signal 1111 is \_\_\_\_\_.

**Answer: (0.9375)**

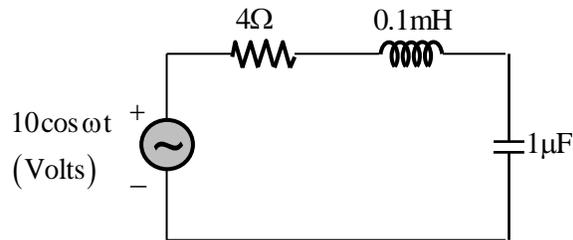23. In the circuit shown, at resonance, the amplitude of the sinusoidal voltage (in Volts) across the capacitor is \_\_\_\_\_.




**Answer: (25)**

24. A sinusoidal signal of 2 kHz frequency is applied to a delta modulator. The sampling rate and step-size  $\Delta$  of the delta modulator are 20,000 samples per second and 0.1V, respectively. To prevent slope overload, the maximum amplitude of the sinusoidal signal (in Volts) is

- (A)  $\frac{1}{2\pi}$       (B)  $\frac{1}{\pi}$       (C)  $\frac{2}{\pi}$       (D)  $\pi$

**Answer: (A)**

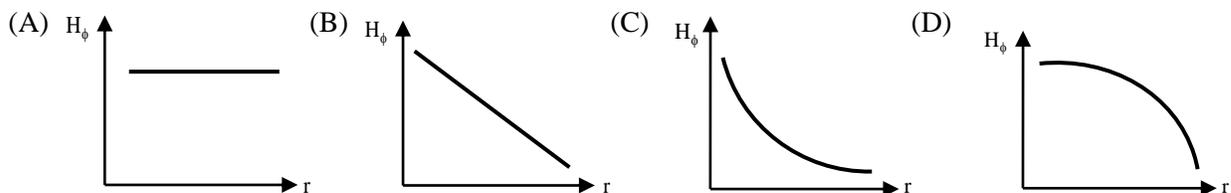
25. Consider a straight, infinitely long, current carrying conductor lying on the z-axis. Which one of the following plots (in linear scale) qualitatively represents the dependence of  $H_\phi$  on  $r$ , where  $H_\phi$  is the magnitude of the azimuthal component of magnetic field outside the conductor and  $r$  is the radial distance from the conductor?



**Answer: (C)**

**Q. No. 26 – 55 carry Two Marks Each**

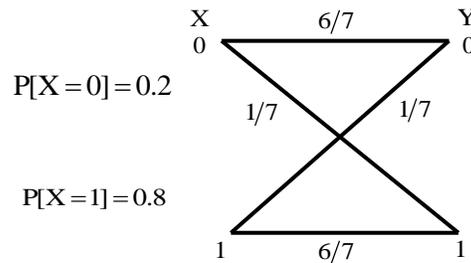26. The input X to the Binary Symmetric Channel (BSC) shown in the figure is '1' with probability 0.8. The cross-over probability is 1/7.




If the received bit  $Y = 0$ , the conditional probability that '1' was transmitted is \_\_\_\_\_.

**Answer: (0.4)**

27. The transmitted signal in a GSM system is of 200 kHz bandwidth and 8 users share a common bandwidth using TDMA. If at a given time 12 users are talking in a cell, the total bandwidth of the signal received by the base station of the cell will be at least (in kHz) \_\_\_\_\_.

**Answer: (400)**

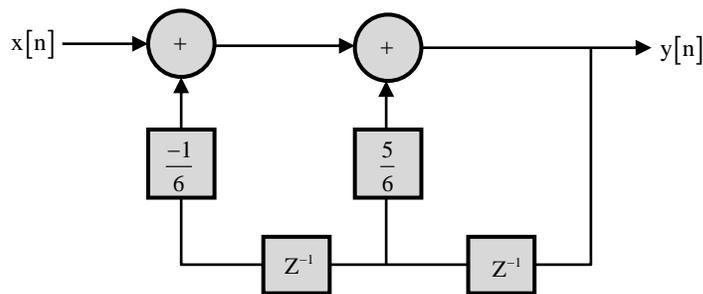
28. For the discrete-time system shown in the figure, the poles of the system transfer function are located at



- (A) 2,3                      (B)  $\frac{1}{2}, 3$                       (C)  $\frac{1}{2}, \frac{1}{3}$                       (D)  $2, \frac{1}{3}$

**Answer: (C)**

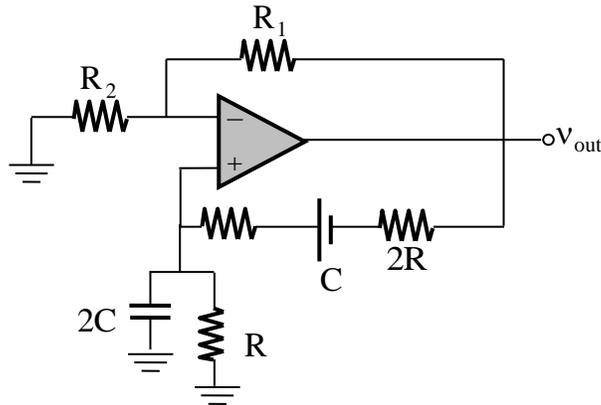29. The circuit shown in the figure has an ideal op amp. The oscillation frequency and the condition to sustain the oscillations, respectively, are



- (A)  $\frac{1}{CR}$  and  $R_1 = R_2$                       (B)  $\frac{1}{CR}$  and  $R_1 = 4R_2$   
 (C)  $\frac{1}{2CR}$  and  $R_1 = R_2$                       (D)  $\frac{1}{2CR}$  and  $R_1 = 4R_2$

**Answer: (D)**

30. A source emits bit 0 with probability  $\frac{1}{3}$  and bit 1 with probability  $\frac{2}{3}$ . The emitted bits are communicated to the receiver. The receiver decides for either 0 or 1 based on the received value R. It is given that the conditional density functions of R are as

$$f_{R|0}(r) = \begin{cases} \frac{1}{4}, & -3 \leq x \leq 1, \\ 0, & \text{otherwise,} \end{cases} \quad \text{and}$$

$$f_{R|1}(r) = \begin{cases} \frac{1}{6}, & -1 \leq x \leq 5, \\ 0, & \text{otherwise.} \end{cases}$$

The minimum decision error probability is (approximately)

- (A) 0                      (B) 1/12                      (C) 1/9                      (D) 1/6


**Answer: (D)**

31. For a silicon diode with long P and N regions, the acceptor and donor impurity concentrations are  $1 \times 10^{17} \text{ cm}^{-3}$  and  $1 \times 10^{15} \text{ cm}^{-3}$ , respectively. The lifetimes of electrons in P region and holes in N region are both  $100 \mu\text{s}$ . The electron and hole diffusion coefficients are  $49 \text{ cm}^2/\text{s}$  and  $36 \text{ cm}^2/\text{s}$  respectively. Assume


$kT/q = 26\text{mV}$ , the intrinsic carrier concentration is  $1 \times 10^{10} \text{ cm}^{-3}$  and  $q = 1.6 \times 10^{-16} \text{ C}$ . When a forward voltage of 208 mV is applied across the diode, the hole current density (in  $\text{nA/cm}^2$ ) injected from P region to N regions is \_\_\_\_\_.

**Answer: (28.59)**

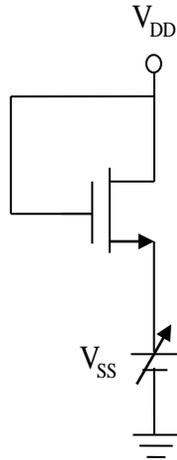**32.** For the N-MOSFET in the circuit shown, the threshold voltage is  $V_{th}$ , where  $V_{th} > 0$ .




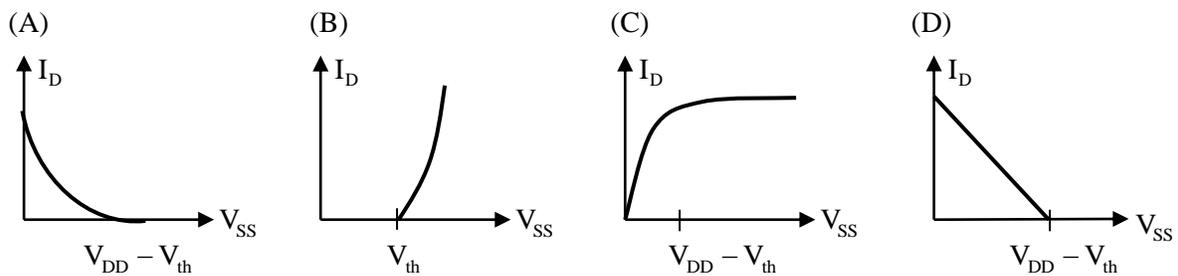The source voltage  $V_{ss}$  is varied from 0 to  $V_{DD}$ . Neglecting the channel length modulation, the drain current  $I_D$  as a function  $V_{ss}$  is represented by.




**Answer: (A)**

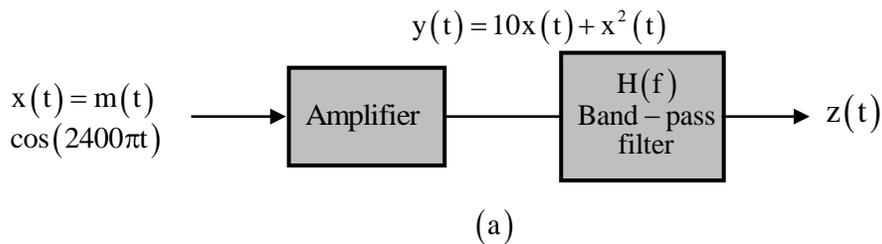**33.** In the system shown in figure (a),  $m(t)$  is a low-pass signal with bandwidth  $W$  Hz.



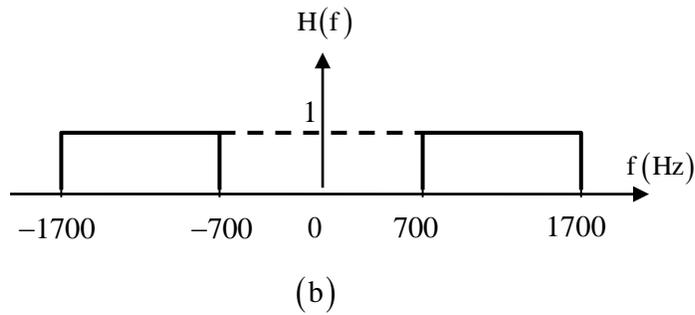
The frequency response of the band-pass filter  $H(f)$  is shown in figure (b).



If it is desired that the output signal  $z(t) = 10x(t)$ , the maximum value of  $W$  (in Hz) should be strictly less than \_\_\_\_\_.

**Answer: (350)**

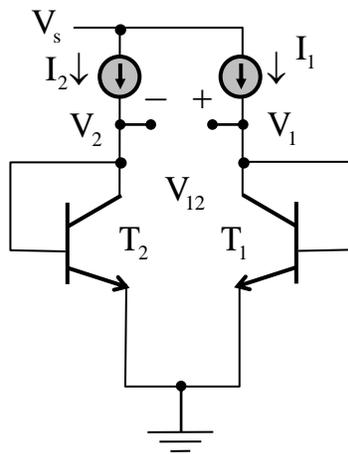34. In the circuit shown,  $I_1 = 80\text{mA}$  and  $I_2 = 4\text{mA}$ . Transistors  $T_1$  and  $T_2$  are identical.



Assume that the thermal voltage  $V_T$  is 26 mV at 27°C. At 50°C, the value of the voltage  $V_{12} = V_1 - V_2$  (in mV) is \_\_\_\_\_.

**Answer: (83.88)**

35. The electric field intensity of a plane wave traveling in free space is given by the following expression

$$E(x, t) = a_y 24\pi \cos(\omega t - k_0 x) \text{ (V/m)}$$


In this field, consider a square area 10cm x 10 cm on a plane  $x + y = 1$ . The total time-averaged power (in mW) passing through the square area is \_\_\_\_\_.

**Answer: (53.31)**

36. The maximum area (in square units) of a rectangle whose vertices lie on the ellipse  $x^2 + 4y^2 = 1$  is \_\_\_\_\_.

Answer: (1)

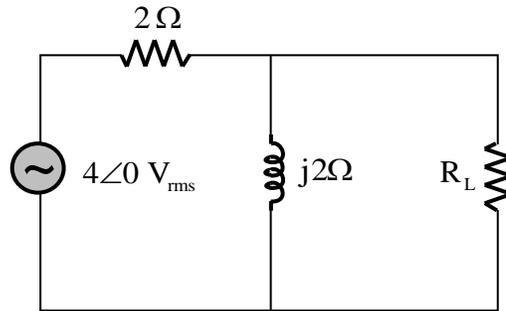37. In the given circuit, the maximum power (in Watts) that can be transferred to the load  $R_L$  is \_\_\_\_\_.



Answer: (1.66)

38. A lead compensator network includes a parallel combination of R and C in the feed-forward path. If the transfer function of the compensator is  $G_c(s) = \frac{s+2}{s+4}$ , the value of RC is \_\_\_\_\_.

Answer: (0.5)


39. A MOSFET in saturation has a drain current of 1mA for  $V_{DS} = 0.5\text{V}$ . If the channel length modulation coefficient is  $0.05 \text{ V}^{-1}$ , the output resistance (in  $\text{k}\Omega$ ) of the MOSFET is \_\_\_\_\_.

Answer: (20)

40. The built-in potential of an abrupt p-n junction is 0.75V. If its junction capacitance ( $C_J$ ) at a reverse bias ( $V_R$ ) of 1.25V is 5pF, the value of  $C_J$  (in pF) when  $V_R = 7.25\text{V}$  is \_\_\_\_\_.

Answer: (2.5)

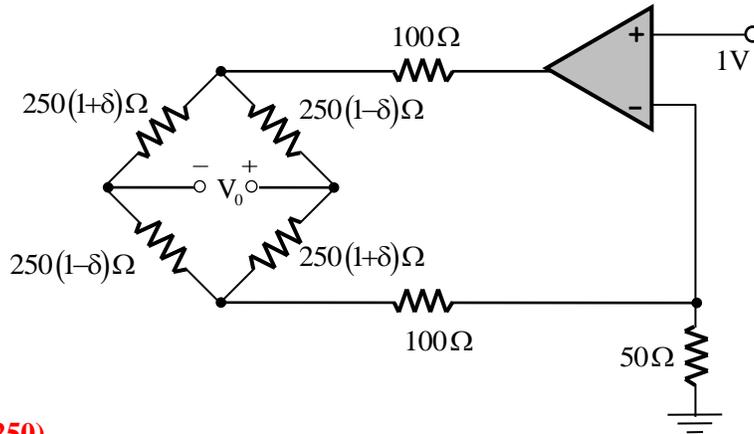41. In the circuit shown, assume that the opamp is ideal. The bridge output voltage  $V_0$  (in mV) for  $\delta = 0.05$  is \_\_\_\_\_.




Answer: (250)

42. The damping ratio of a series RLC circuit can be expressed as

- (A)  $\frac{R^2 C}{2L}$       (B)  $\frac{2L}{R^2 C}$       (C)  $\frac{R}{2} \sqrt{\frac{C}{L}}$       (D)  $\frac{2}{R} \sqrt{\frac{L}{C}}$

Answer: (C)

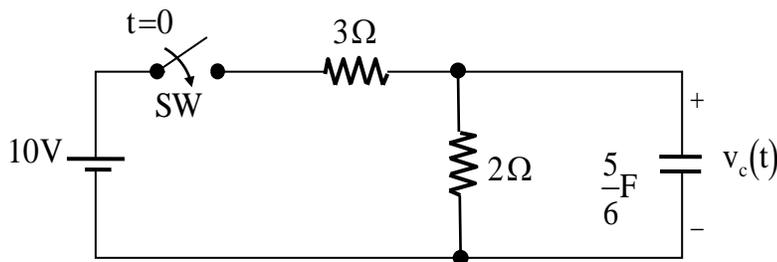
43. In the circuit shown, switch SW is closed at  $t = 0$ .



Assuming zero initial conditions, the value of  $v_c(t)$  (in Volts) at  $t = 1$  sec is \_\_\_\_\_.

Answer: (2.528)

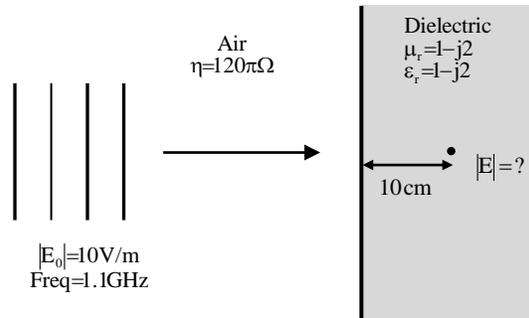44. Consider a uniform plane wave with amplitude ( $E_0$ ) of 10V/m and 1.1GHz frequency travelling in air, and incident normally on a dielectric medium with complex relative permittivity ( $\epsilon_r$ ) and permeability ( $\mu_r$ ) as shown in the figure.



The magnitude of the transmitted electric field component (in V/m) after it has travelled a distance of 10 cm inside the dielectric region is \_\_\_\_\_.


**Answer: (0.1)**

45. A vector  $\vec{P}$  is given by  $\vec{P} = x^3y\vec{a}_x - x^2y^2\vec{a}_y - x^2yz\vec{a}_z$ . Which one of the following statements is TRUE?

- (A)  $\vec{P}$  is solenoidal, but not irrotational
- (B)  $\vec{P}$  is irrotational, but not solenoidal,
- (C)  $\vec{P}$  is neither solenoidal nor irrotational
- (D)  $\vec{P}$  is both solenoidal and irrotational

**Answer: (A)**

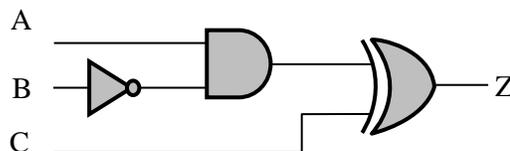46. All the logic gates shown in the figure have a propagation delay of 20 ns. Let  $A=C=0$  and  $B=1$  until time  $t=0$ . At  $t=0$ , all the inputs flip (i.e.,  $A=C=1$  and  $B=0$ ) and remain in that state. For  $t > 0$ , output  $Z = 1$  for a duration (in ns) of



**Answer: (40)**

47. A plant transfer function is given as  $G(s) = \left(k_p + \frac{k_I}{s}\right) \frac{1}{s(s+2)}$ . When the plant operates in a unity feedback configuration, the condition for the stability of the closed loop system is

- (A)  $k_p > \frac{k_I}{2} > 0$       (B)  $2k_I > k_p > 0$       (C)  $2k_I < k_p$       (D)  $2k_I > k_p$

**Answer: (A)**

48. A 3-input majority gate is defined by the logic function  $M(a,b,c) = ab + bc + ca$ . Which one of the following gates is represented by the function  $M(\overline{M(a,b,c)}, M(a,b,\bar{c}), c)$ ?

- (A) 3-input NAND gate      (B) 3-input XOR gate  
(C) 3-input NOR gate      (D) 3-input XNOR gate

**Answer: (B) and (D)**

49. The longitudinal component of the magnetic field inside an air-filled rectangular waveguide made of a perfect electric conductor is given by the following expression

$$H_z(x, y, z, t) = 0.1 \cos(25\pi x) \cos(30.3\pi y) \cos(12\pi \times 10^9 t - \beta z) \text{ (A / m)}$$

The cross-sectional dimensions of the waveguide are given as  $a = 0.08\text{m}$  and  $b = 0.033\text{m}$ . The mode of propagation inside the waveguide is

- (A)  $TM_{12}$       (B)  $TM_{21}$       (C)  $TE_{21}$       (D)  $TE_{12}$

**Answer: (C)**

50. The open-loop transfer function of a plant in a unity feedback configuration is given as

$$G(s) = \frac{k(s+4)}{(s+8)(s^2-9)}$$

The value of the gain  $k(>0)$  for which  $-1 + j2$  lies on the root locus is \_\_\_\_\_.


**Answer: (25.5)**



- (A)  $h[n]$  is real for all  $n$
- (B)  $h[n]$  is purely imaginary for all  $n$
- (C)  $h[n]$  is real for only even  $n$
- (D)  $h[n]$  is purely imaginary for only odd  $n$

**Answer: (C)**

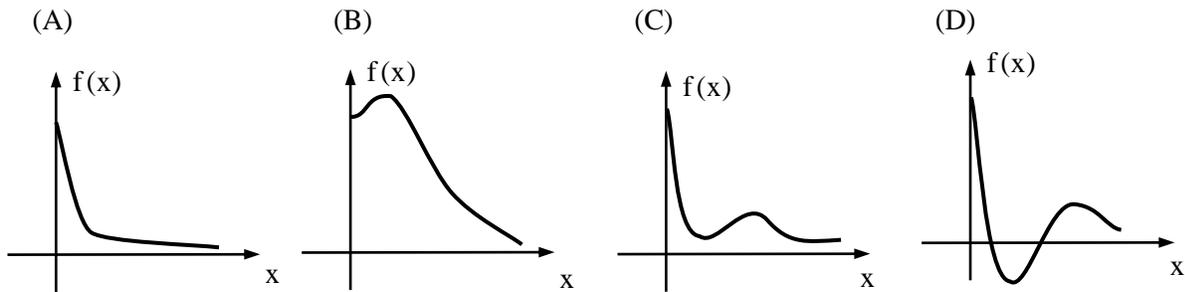**54.** Which one of the following graphs describes the function  $f(x) = e^{-x}(x^2 + x + 1)$ ?



**Answer: (B)**

**55.** The Boolean expression  $F(X, Y, Z) = \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XY\bar{Z} + XYZ$  converted into the canonical product of sum (POS) form is

- (A)  $(X + Y + Z)(X + Y + \bar{Z})(X + \bar{Y} + \bar{Z})(\bar{X} + Y + \bar{Z})$
- (B)  $(X + \bar{Y} + Z)(\bar{X} + Y + \bar{Z})(\bar{X} + \bar{Y} + Z)(\bar{X} + \bar{Y} + \bar{Z})$
- (C)  $(X + Y + Z)(\bar{X} + Y + \bar{Z})(X + \bar{Y} + Z)(\bar{X} + \bar{Y} + \bar{Z})$
- (D)  $(X + \bar{Y} + \bar{Z})(\bar{X} + Y + Z)(\bar{X} + \bar{Y} + Z)(X + Y + Z)$

**Answer: (A)**